

Power I

NoteBook

Dr. Hisham Hamdan

By: Luma & Asma' Hakouz



Generator



18/2/14

* Generation System :-

* To change any process (concerns):

1. Technical
2. economical
3. environment

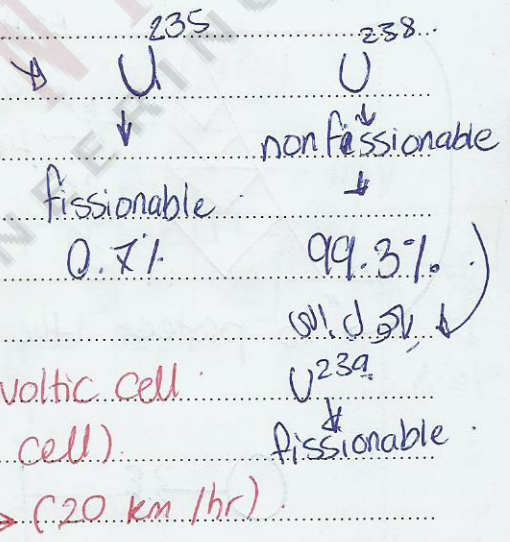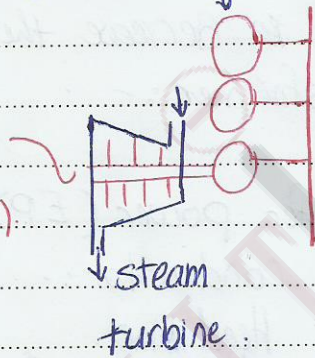
1. (Fuel oil)
2. (gas)
3. (Coal)
4. (nuclear reactor)



* if we want to have more "S" :-

- more $I_L \rightarrow$ more copper
- more $V_L \rightarrow$ more insulation

P.S

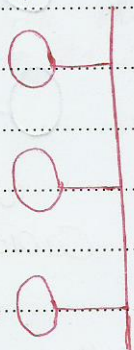

* where to put the generators :-

- near Load centre
- near water & fuel supplies



(11-24) KV

$$S = \sqrt{3} V_L I_L$$

note \rightarrow cheaper to transfer electrical power than to transfer water & fuel

* to decrease the voltage drop we use $(P \propto V^2)$
 Transfor. mer. :- busbar.

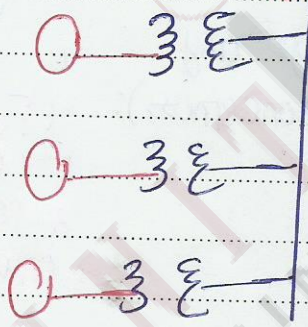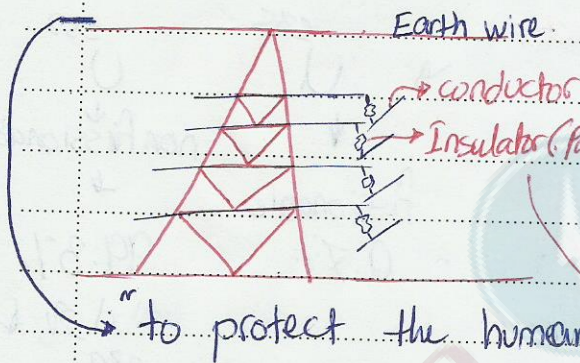⊗ to transfer power (EP) we use a conductor :-
 1. Over Head Line





more voltage more power.
 AC very small

132 KV	400 kVA
220 (230) KV	500 KV
(275) (300) (345) KV	765 KV
	1000 KV
	1500 KV



T.L.
 arrive here with high voltage.

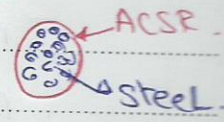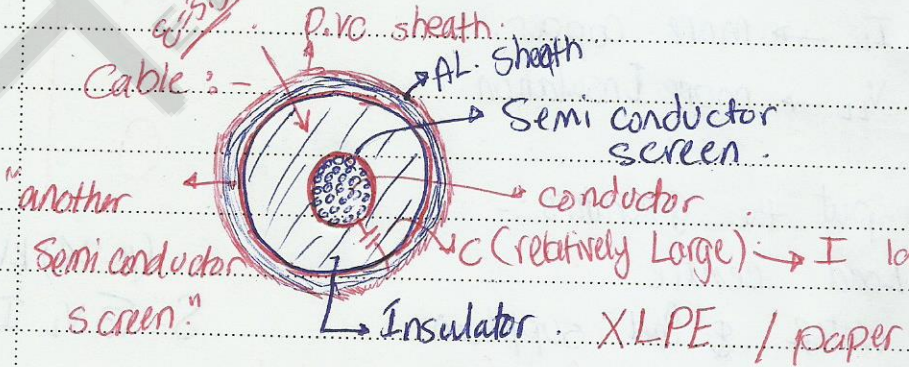note Insulators made from polymers or parclain. ACSR (Aluminum conductor steel Reinforce).



C (relatively large) $\rightarrow I$ large $\rightarrow I = j\omega CV$

* OHL → over head Line.

No.

* Cost of cable

Cost OHL

18

Voltage
400 kV

13

275 kV

8


132 kV

2-3

LV


Lecture "2"


12/20/14

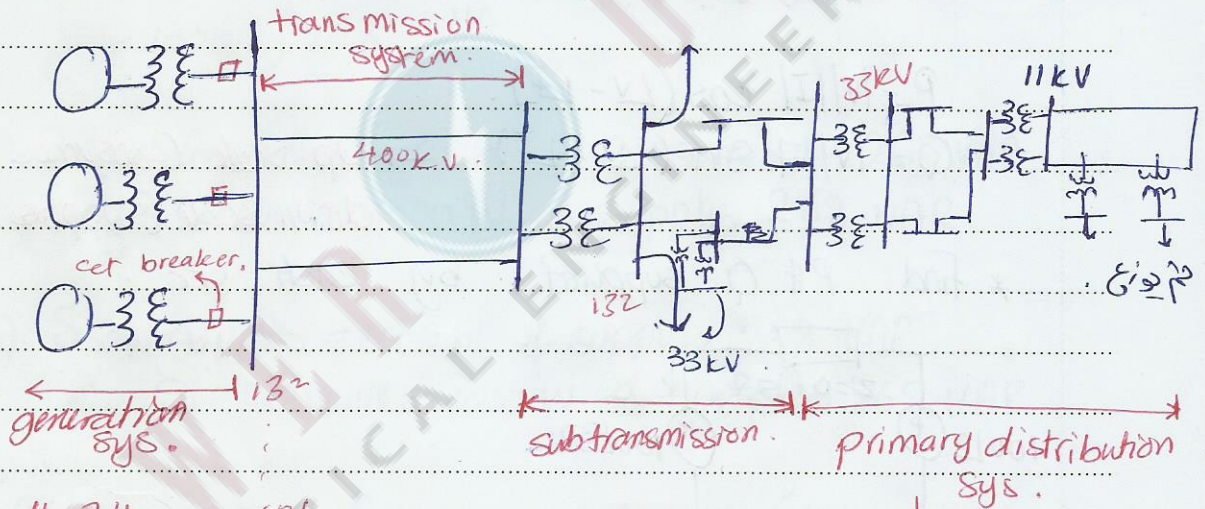

for a circle that has radius of 500 m.

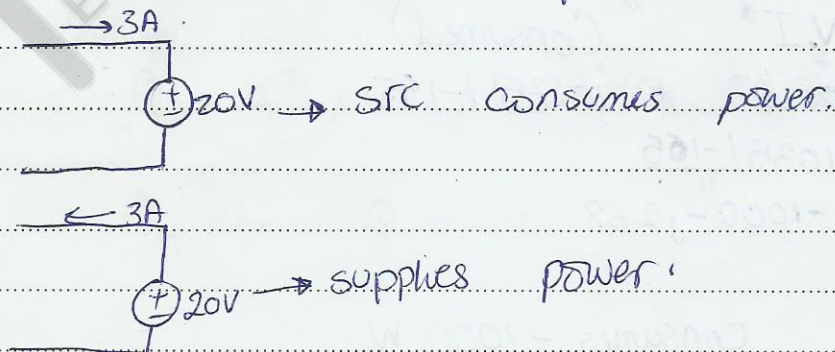* CH.1 → 1.7 "Direction of power flow" :-



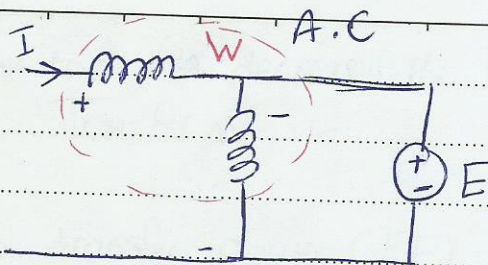

$$W = V \cdot I$$


$$= VI \cos \theta$$

- if the wattmeter reads up scale, src is consuming power.
- if the wattmeter reads down scale, src is supplying power.

$$P = |V||I| \cos(\angle V - \angle I)$$

$$Q = |V||I| \sin(\angle V - \angle I) \rightarrow \begin{array}{l} \text{up scale (consumes } Q) \\ \text{down scale (supplies } Q) \end{array}$$

* find P & Q supplied by each src.

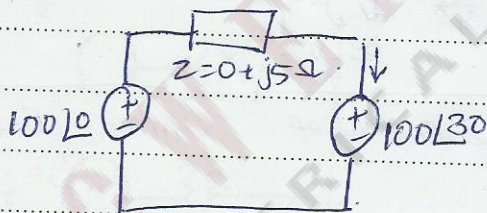

$$I = \frac{100\angle 0 - 100\angle 30}{j5} = -10 - j2.68 \text{ A}$$

$$= 10.35 \angle 195^\circ \text{ A}$$

$$S_2 = V_2 \cdot I^* \quad \text{" Consumed)}$$

$$= 100\angle 30 \cdot 10.35 \angle -195$$

$$= 1035 \angle -165$$

$$= -1000 - j268$$

src 1 Consumes -1000 W.

src 2 Consumes -268 VAR.

OR SRC 2 supplies 1000 W & supplies 268 VAR.

Src 1 \rightarrow A) Consumed.

B) Supplied

$$S_1 = V_1 \cdot (-I^*)$$

$$S_1 = V_1 \cdot I^*$$

$$= 100 (-10 + j2.68)$$

$$\leftarrow S_1 = 100 \angle 0 \cdot (-10.35 \angle -195)$$

$$= -1000 + j268 \text{ VA}$$

$$= 100 (10 - j2.68)$$

$$= 1000 - j268 \text{ VA}$$

$$(-I = 10 + j2.68)$$

For (A) $S_1 \rightarrow$ consumes 1000 W & consumes -268 VAR

OR S_1 consumes 1000 W & supplies 268 VAR

For (B) $S_1 \rightarrow$ supplies -1000 W & supplies 268 VAR

OR S_1 consumes 1000 W & supplies 268 VAR

"Active power \rightarrow Supplies = consumes (no resistance) -

Reactive power \rightarrow both src are supplying so the reactance must consumes the sum of Q from

S_1 & S_2 .

So \Rightarrow

$$Q_2 = I^2 X = (10.35)^2 (5) = 536 \text{ VAR "consumes"}$$

So

$$Q_{\text{supplies}} = Q_{\text{consumes}} \neq "$$

"who leads gives power"

100L30 → lead 100L0 so 100L30 gives power that's ~~causing~~ being consumed by 100L0.

Q → depends on the magnitude.
P → depends on who leads who.

1.10 Per Unit System :-

V, I, S, Z

$$V_{pu} = \frac{\text{Actual value}}{\text{Base value}}$$

* Lecture "3" * Continue to PU quantities :-

V, I, S, Z

* Base kVA_{1φ}, Base kV_{LN} :-

① Base current (A) = $\frac{\text{Base kVA}_{1\phi}}{\text{Base kV}_{LN}}$ #

② Base Impedance (Ω) = $\frac{\text{Base kV}_{LN} \times 1000}{\text{Base current}}$
 just for Units

always Proud

Smile 49

No.

⊕ to find the Base value of Z :-

$$\rightarrow \text{Base}(Z) = \frac{(\text{Base value of KV})^2 * 1000}{\text{Base kVA}}$$

$$= \frac{(\text{base KV}_{LN})^2}{\text{base MVA}_{1\phi}}$$

// Just take two base values of V_{LN} & $S_{1\phi}$ of Z .

→ for Power :-

→ $S = P + jQ$ * if we divide S by S_{base} , then P & Q must be divided by S_{base} too.*

$$\rightarrow \frac{S}{S_{base}} = \frac{P + jQ}{S_{base}}$$

* Base value of P & Q is the same value of S *

* Take a 1⊕ Gen. where :-


$V_{actual} = 10,000 \text{ V}$, → Line to Neutral

$S_{actual} = 10 \text{ MVA}$ → 1⊕ S

$Z = 0.5 \underline{180} \Omega$

→ Base $KV_{LN} = 10$

Base $MVA_{1\phi} = 10$

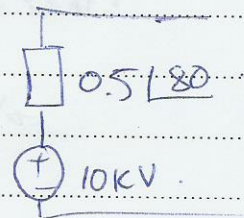

* $V_{pu} = \frac{\text{actual value}}{\text{Base Value}} = \frac{10}{10} = 1 \text{ PU} = V_{pu}$ *

* $S_{pu} = \frac{\text{Actual}}{\text{Base}} = \frac{10}{10} = 1 \text{ PU} = S$


* $Z_{base} = \frac{(\text{Base kV LN})^2}{\text{Base MVA}_{\phi}} = \frac{(10)^2}{10} = 10 \Omega$

* $Z_{pu} = \frac{0.5 \angle 80}{10} = 0.05 \angle 80 \text{ PU}$

* $I_{sc(p.u)} = \frac{110}{0.05 \angle 80} = 20 \angle -80$

* if we put a load \rightarrow have voltage V_t


$V_t = 110 - IZ$
 $= 110 - |I| \angle \phi \cdot |Z| \angle 80$

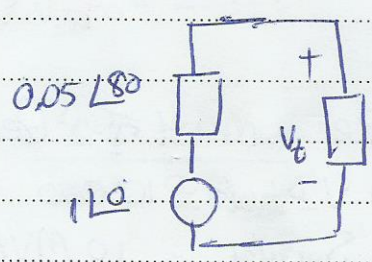

make the Gen. take its full load @ $I = 1 \text{ PU}$

~~if we put a load~~

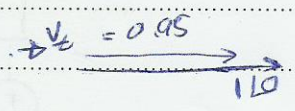$V_t = 1 - 0.05 = 0.95$
 $I = 11 \angle -80$




$$\text{if } I = 1 \angle 20^\circ$$

$$V_t = 110 - 1120 \times 0.05 \angle 180^\circ$$

$$= 110 - 0.05 \angle 100^\circ$$

Capacitive load
-0.05/100

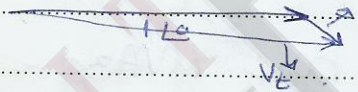

* See the current lag or lead to know Z_L inductive or capacitive load respectively *


$$\text{if } V_t \rightarrow \text{min when } |B| = -1 \angle \theta \quad *$$

$$V_t = 110 - \frac{I Z}{\downarrow}$$

$$1 \angle -20^\circ$$

$$= 110 - 0.05 \angle 160^\circ$$

Inductive load

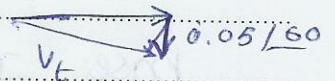

* when I (leads) \rightarrow gives the max value of V_t & the opposite when it lags

$$* \frac{1}{\text{P.U.}(z)} = \text{max value of } I_{sc}$$

* For ϕ values

3 ϕ system (Y)

Actual values
 \rightarrow MVA_{3 ϕ} = 18 MVA

\rightarrow KV_{LL} = 108 KV

equivalent 1- ϕ sys.

MVA_{1 ϕ} = 18/3 = 6 MVA

KV_{LN} = 18/ $\sqrt{3}$

Base MVA_{3 ϕ} = 30 MVA

\rightarrow base MVA_{1 ϕ} = 10 MVA

Base KV_{LL} 3 ϕ = 120 KV

base KV_{LN} = 120/ $\sqrt{3}$

PV values must be the same :-

PV(S) = 0.6

= 0.6

PV(V) = 0.9

= 0.9

Lecture "4"

* base current = $\frac{\text{base kVA}_{3\phi}}{\sqrt{3} \times \text{base KV}_{LL}}$

base Impedance = $\frac{\text{base KV}_{LL} / \sqrt{3} \times 1000}{\text{base current (A)}}$


to balance
units

\rightarrow Base Impedance (Ω) = $\frac{(\text{base KV}_{LL} / \sqrt{3}) (\sqrt{3} \text{ base KV}_{LL}) \times 1000}{\text{base kVA}_{3\phi}}$
 $= \frac{(\text{base KV}_{LL})^2}{\text{base MVA}_{3\phi}}$

$\left[\begin{array}{l} \text{in } 3\phi \rightarrow V_{LL}, S_{3\phi} \\ \text{in } 1\phi \rightarrow V_{LN}, S_{1\phi} \end{array} \right]$

♥♥♥♥♥

No.

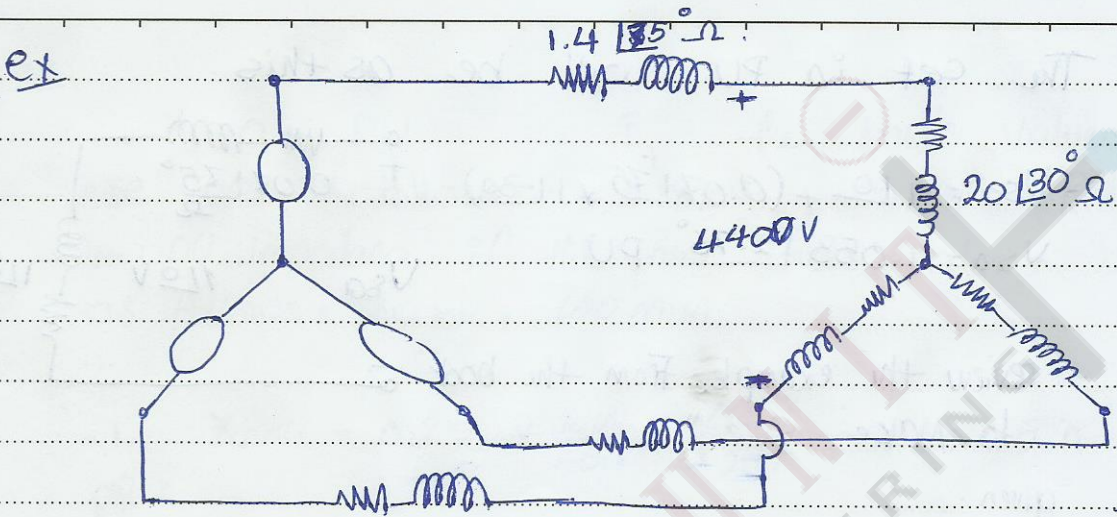

$$V_{sa} = \frac{4400 \angle 0}{\sqrt{3}} + I (1.4 \angle 85^\circ)$$

⊕ to find I =

$$I = \frac{4400 \angle 0}{\sqrt{3}}$$

$$20 \angle 30^\circ$$

$$I = 127 \angle -30^\circ \text{ A} \quad \text{---**}$$

then : $V_{sa} = 2670 \angle 2.7^\circ$

$$V_{LL} = 2670 \sqrt{3}$$

(as a magnitude if he doesn't give me the sequence)

* Solve previous example using Per Unit if base values as follows :


$$V_{base} = 4400 \text{ V} \rightarrow I_{base} = 12.7 \text{ A}$$

$$\text{base MVA} = V_{base} * I_{base} * \sqrt{3} \rightarrow \text{L to L voltage}$$

$$= 4.4 * \sqrt{3} * 0.127$$

$$= 0.96787 \text{ MVA}$$

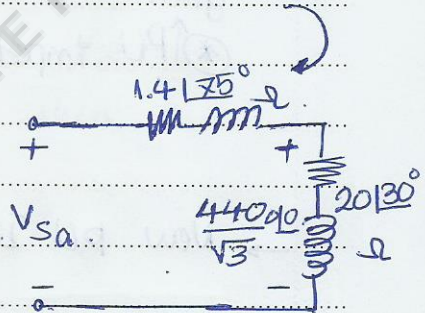
$$\text{base Impedance} = \frac{(4.4)^2}{0.96787} = 20 \Omega$$



♡ I can if I want ♡

No.

The ckt in PU will be as this
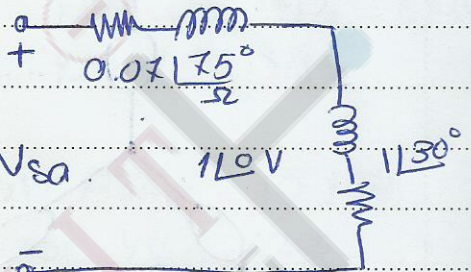
$$V_{sa} = 110 + (0.07175 \times 11 \angle 30^\circ)$$
$$V_{sa} = 1.053 \angle 2.76^\circ \text{ PU}$$


"review the example from the book to make sure"

given:

$$\text{PU impedance} = \text{actual imp.} \times \frac{\text{Given base MVA}}{(\text{given base KV})^2} \quad \text{--- (1)}$$

$$\rightarrow \text{New PU Imp.} = \text{actual imp} \times \frac{\text{new base MVA}}{(\text{new base KV})^2} \quad \text{--- (2)}$$

∴ divide (2) by (1)

$$\frac{\text{new PU Imp.}}{\text{Given PU imp.}} = \frac{\text{new base MVA} \times (\text{Given base KV})^2}{\text{Given base MVA} \times (\text{new base KV})^2}$$

thus -

$$\text{new PU Imp} = \text{Given PU imp.} \times \frac{\text{new base MVA}}{\text{Given base MVA}} \times \left(\frac{\text{Given base KV}}{\text{new base KV}} \right)^2$$



ex

$X = 0.25 \text{ pu}$ & the base's values are as follows: 18 kV, 500 MVA. Find the new pu impedance if the new base's values become as follows: 20 kV, 100 MVA.

-1- $X_{\text{new}} = 0.25 \times \frac{100}{500} \times \left(\frac{18}{20}\right)^2 = 0.45 \Omega$



OR:

we can find the actual value of X_{old} :-


$X_{\text{old}} = 0.25 \times \frac{(18)^2}{500}$ & then


$X_{\text{pu}} = \frac{0.25 \times (18)^2 / 500}{(20)^2 / 100}$

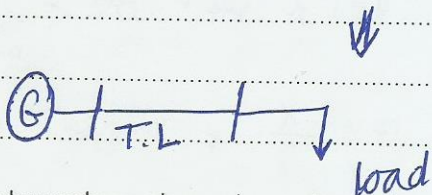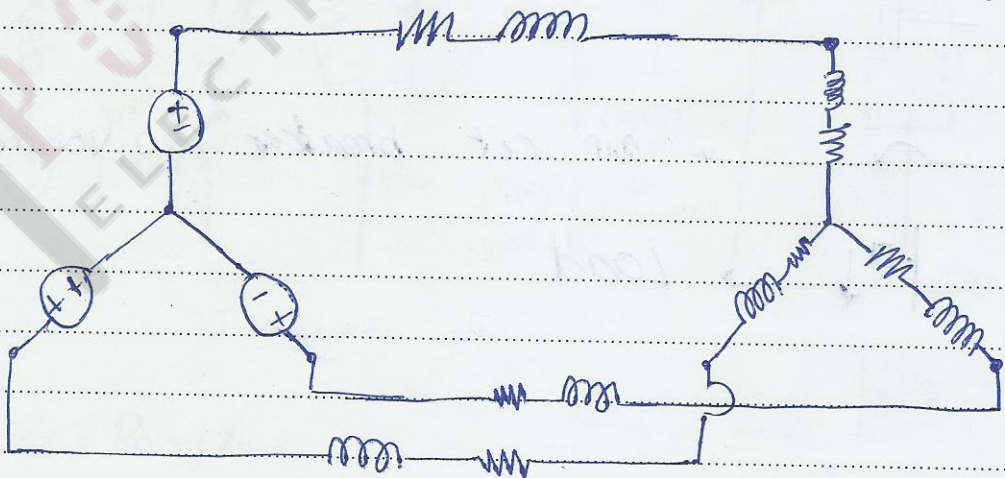
* One Line Diagram * "Single line Diagram"




Some Symbols :-


 → synchronous Generator (SG)

 → Power Transformer.

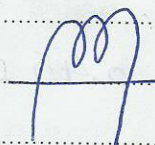 → Current Transformer.

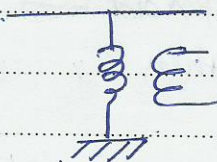 → voltage Transformer.


 → Transmission Line.

 → cut breaker "high voltage"

 → bus bar.

 → air cut breaker "low voltage"

 → Load.

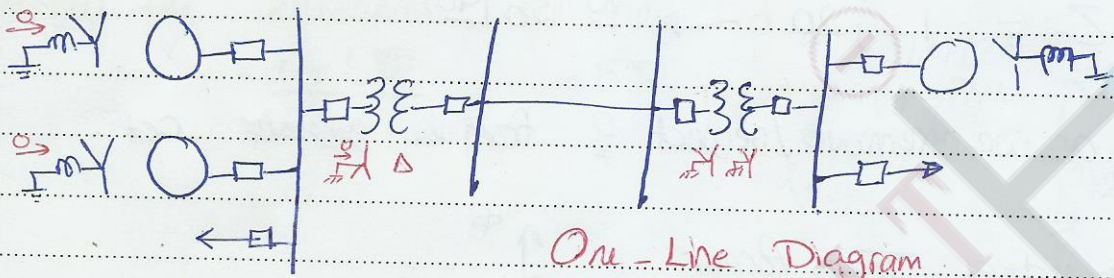

One-Line Diagram


* generator → cct breaker → Step up transformer → T.L
 → Step down Trans. → Load
 ↳ motor or any other type of machine.

Lecture "5" *

Tue. 27/2/2014.

In Balance $\sum I$ in Y Connection = 0

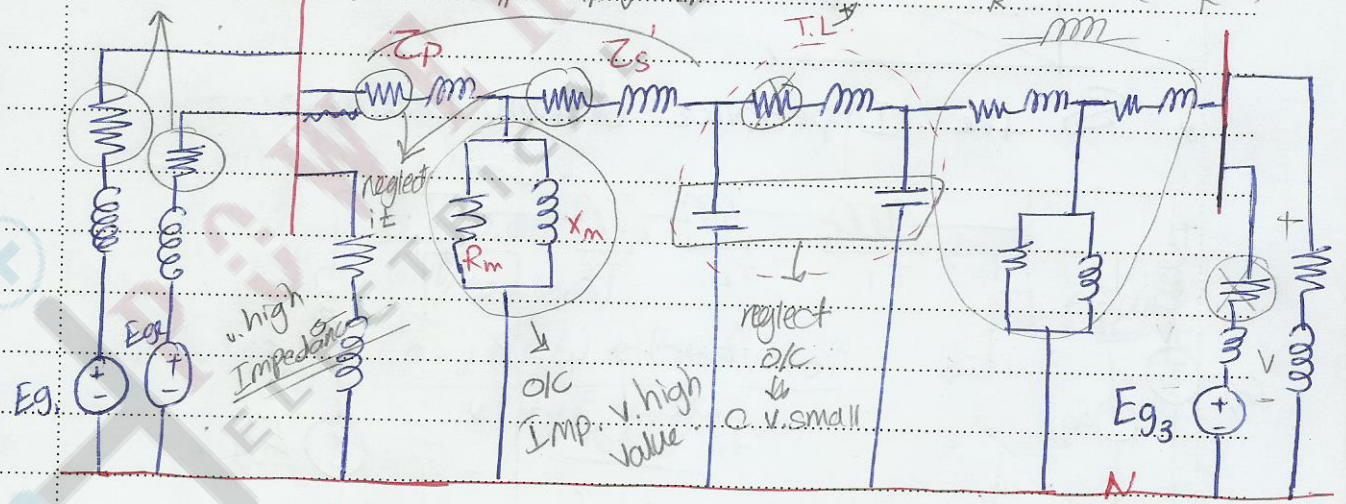As we remove this $Z_{eq} = R_{eq} + jX_{eq}$ H.V.TL = $\frac{X}{R} = 3-7$ (neglect R)



"Impedance diagram"

$$Z_s = R_a + jX_s$$

$\frac{X_s}{R_a} > 20$ "For a well-designed generator"

For the Transformer $\rightarrow \frac{X}{R} \approx 10$


* $Z_L \gg Z_{Line}$

No.

eg) $Z_s = 1 + j20 \rightarrow \sim 20 \angle 90^\circ$

as we remove / neglect R from the generator set


* ideal Transformer

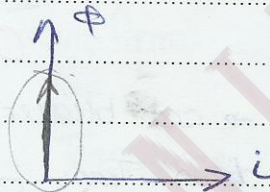


* for practical Transformer




* Linear Transformer

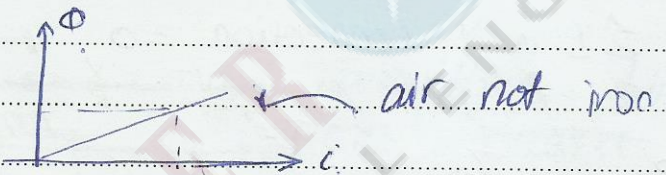

* So the Impedance diagram becomes :-

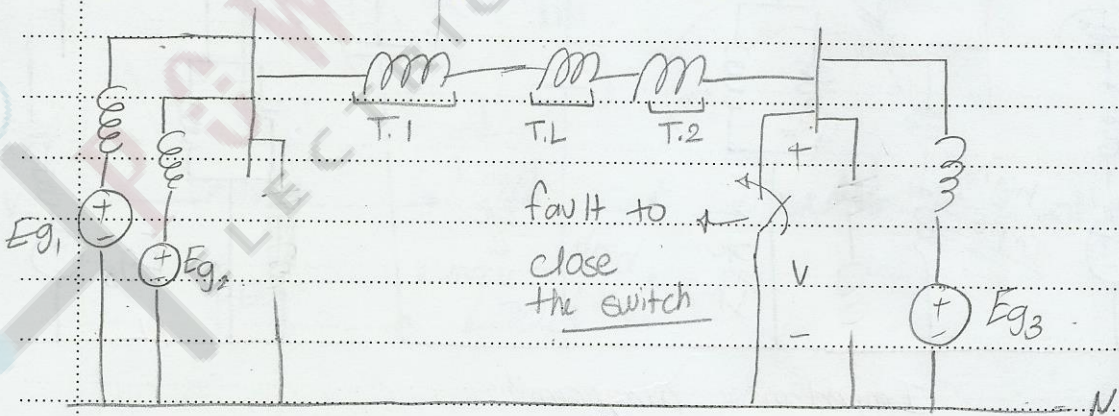


Reactance Diagram

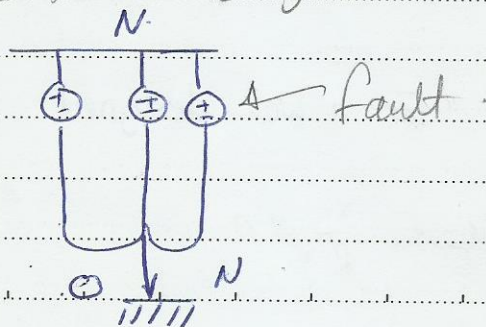


* all the resistances were neglected *

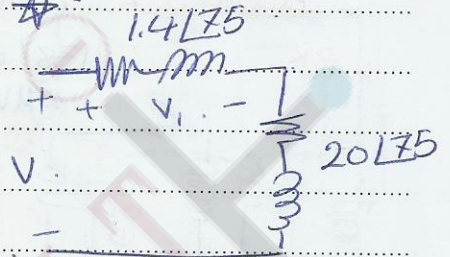
$$V_1 = \frac{1.4175}{1.4175 + 20.175} = 5\%$$



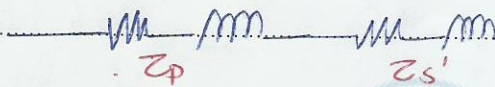" * PU calculations in Transformer circuits "



referred to primary.

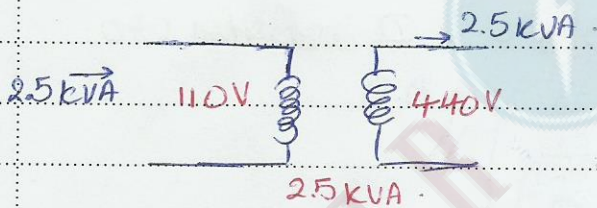

base values:

110V, 2.5 kVA.

$$Z_{1,eq} = 0 + j0.06 \Omega$$

→ pu calculations :-

$$PU Z_{q1} = \frac{0 + j0.06}{6.11^2 / (2.5/1000)}$$

$$PU Z_{eq2} = \frac{(0 + j0.06) * (440)^2 / (110)^2}{(0.44)^2 / (2.5/1000)}$$

equal

1. V_1 → given V_2 → taken as it's good with turns ratio

2. $kVA_{in} = kVA_{out}$

* Lecture "6" * $Z = 0 + j0.8$

* ex


138/69 KV

10 MVA

base values :-

69 KV

10 MVA

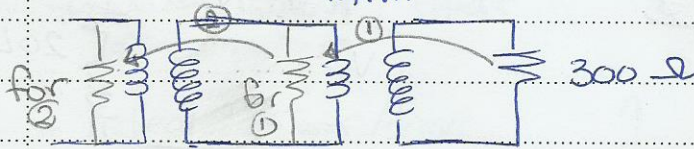

13.8/138 KV

10 MVA

$Z = 0 + j0.1$ PU

10 MVA

$$PU.R = \frac{300}{(69)^2/10} = 0.63 \text{ PU} \quad \text{① and then to}$$

reflect it \rightarrow

$$= \frac{300 \times (138)^2}{(69)^2} = 0.63 \text{ PU} \quad \text{②}$$


② then to reflect it again :-

$$= \frac{300 \times \frac{(138)^2}{(69)^2} \times \frac{(13.8)^2}{(138)^2}}{(13.8)^2/10} = 0.63 \text{ PU}$$


66KV (*) for 3-ph connections :- (Y-Y) connection

10 MVA

a 6.6KV

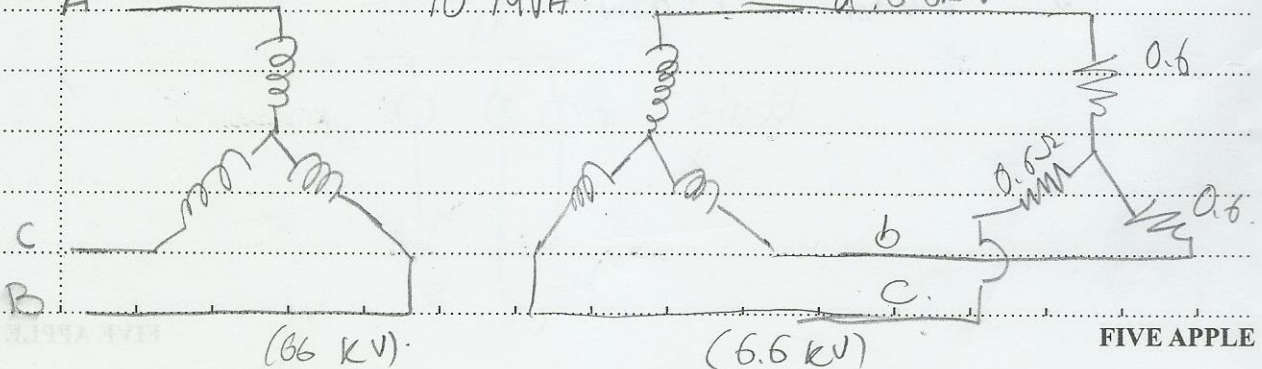

for 3-phase transformer :-

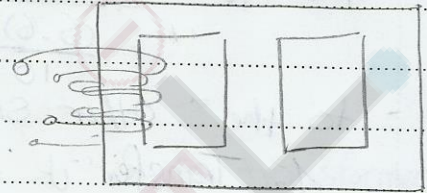

Continue :-

Base MVA for all system is 10 MVA.

to find the PU of R = $\frac{0.6}{\left(\frac{6.6^2}{10}\right)}$ PU

to reflect R to the other side :-

$0.6 \times \left(\frac{\frac{66}{\sqrt{3}}}{\frac{6.6}{\sqrt{3}}}\right)^2$ phase voltage / $\frac{66^2}{10}$




equal

= \square PU

= $0.6 \times \frac{66^2}{6.6^2}$ if we multiply it by (turns

ratio OR transformation ratio) i.s the same

For Y-Δ connection :-

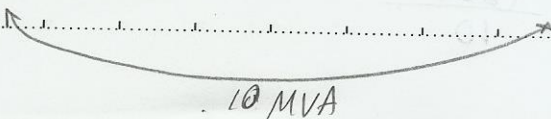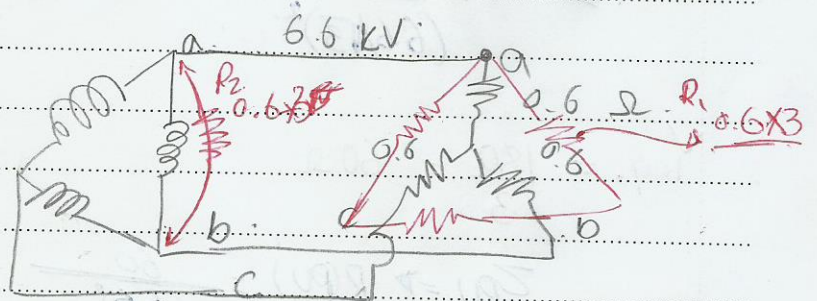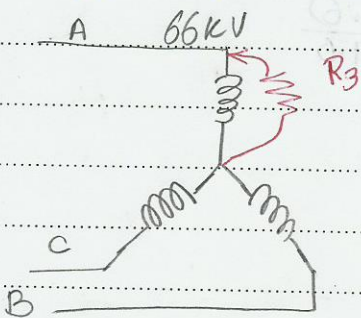

* load is Δ & we want to reflect it to

No.

Δ -load.

$$PU \cdot R = \frac{0.6}{\frac{(6.6)^2}{10}} \quad \& \quad \text{then to reflect it}$$


to the other side:-

1. Transfer it to $\Delta \rightarrow R_1 \times 3$

$$\begin{aligned} R_3 &= 0.6 \times 3 \times \left(\frac{66\sqrt{3}}{6.6} \right)^2 \\ &= 0.6 \times \left(\frac{66}{6.6} \right)^2 \quad \underline{Q.} \end{aligned}$$

$$PU \cdot R = \frac{0.6 \left(\frac{66}{6.6} \right)^2}{66^2/10}$$

* For Δ -connection:-

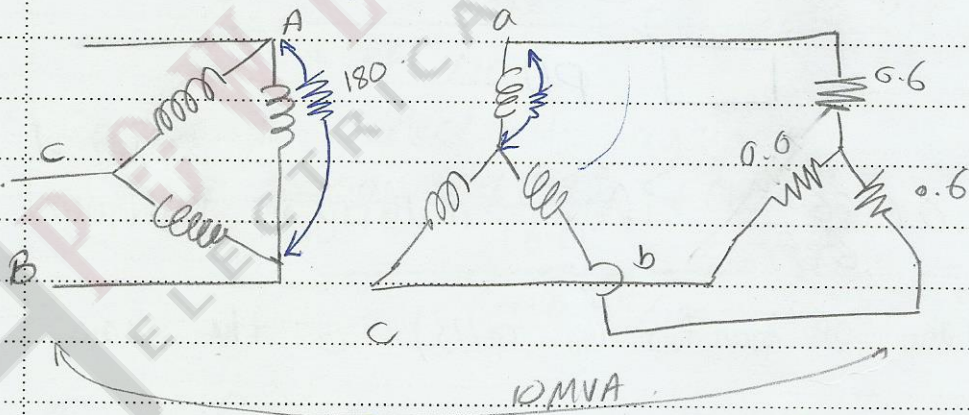

$$\frac{0.6 \times 66^2}{(6.6/\sqrt{3})^2}$$

$$\frac{0.6}{\frac{(6.6)^2}{10}}$$

$$Y_{eq.} = \frac{180}{3} = 60 \Omega$$

$$Z_{PU} \Rightarrow R(PU) = \frac{60}{\frac{(6.6)^2}{10}}$$

⊗ multiply it by the (transformation ratio)² irrespective to the transformer connection.

ex 3 single phase transformer → 3-φ transformer



25 MVA.

38.1 kV / 3.81 kV
LN

Δ / Δ
75 MVA

66 / 3.81 kV
LL Δ doesn't change.

3.81 kV
0.6 Ω

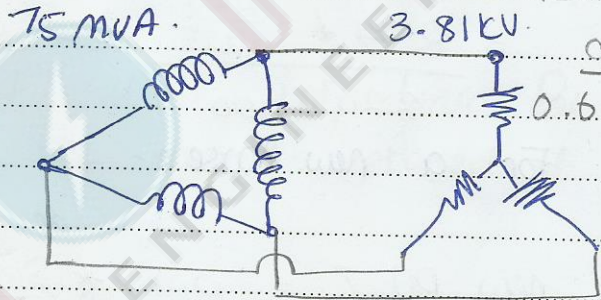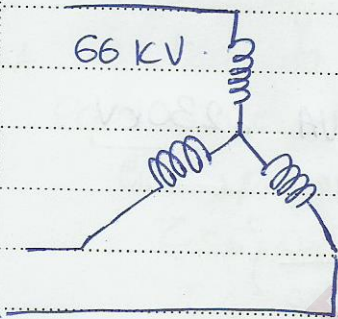


$$R \text{ in PU} \rightarrow = \frac{0.6}{(3.81)^2 / 75} = 3.1 \text{ PU.}$$

reflect it in PU. →

$$= \frac{0.6 \times 66^2}{(3.81)^2} = 3.1 \text{ PU.}$$

$\frac{I_N}{I_R}$

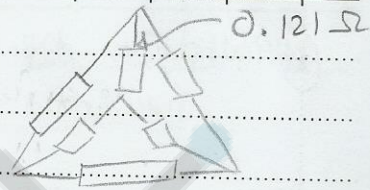ex 3- ϕ transformer
 400 MVA
 220Y/22 Δ kV



$$I_n \text{ pu} \rightarrow \frac{0.121}{(22^2/400)} = 0.1 \text{ pu}$$

$\&$ then to reflect it :-

$$= \frac{0.121 \times \frac{220^2}{22^2}}{220^2/400} = 0.1 \text{ pu}$$


For a new base :- 100MVA, 230kV
 on the primary

$$\text{New pu } Z = 0.1 \times \frac{100}{400} \times \left(\frac{220}{230}\right)^2$$

$$= 0.0228 \text{ pu}$$

Lecture "7" :-

3-winding 3-phase transformer :-

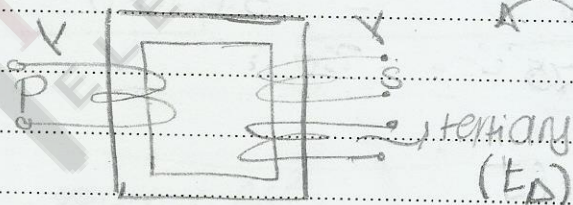

Some MVA

"because of the 3rd harmonic"

* and if Δ -Y we put (E) to take power as a low voltage put it on it (step down the voltage)

* if we make (s) s/c & (t) o/s then P won't be affected by t so we will calculate Z in (p) called Z_{ps}

$$Z_{ps} = Z_p + Z'_s (\Omega)$$

* & if we make (s) o/c & (t) s/c then we will calculate $Z_{pt} = Z_p + Z'_t$ in (p) (Ω)

* or Z_{st} as will $\rightarrow Z_{st} = Z_s + Z'_t (\Omega)$ in Secondary

* we had to reflect all the impedance to the same side so if we must referred it to the primary.

$$Z_{st}' = Z'_s + Z'_t$$

"In all examples we should reflect all the impedances to the primary"

* $Z_{ps} + Z_{pt} - Z_{st} = 2Z_p$ thus:

$$Z_p = \frac{1}{2} (Z_{ps} + Z_{pt} - Z_{st}) \quad \text{So:}$$

$$Z_s = \frac{1}{2} (Z_{ps} + Z_{st} - Z_{pt}) \quad \&$$

$$Z_t = \frac{1}{2} (Z_{st} + Z_{pt} - Z_{ps})$$

$$* \underline{S_S + S_t = S_p}$$

No.

ex

3- ϕ rating of a 3-winding transformer

P: Y-connected 66 kV, 15 MVA

S: Y-connected 13.2 kV, 10 MVA

t: Δ -connected 2.3 kV, 5 MVA

neglect R

$Z_{ps} = 0.07$ PU, with base 15 MVA & 66 kV


$Z_{pt} = 0.09$ PU, " " 15 MVA & 66 kV

$Z_{st} = 0.08$ PU, " " 10 MVA & 13.2 kV

find Z with 15 MVA, 66 kV in P?

Sol
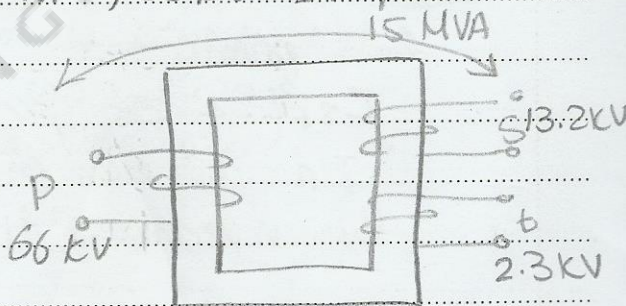
$$Z_{st} = 0.08 \times \frac{15}{10} \text{ PU}$$



base 15 MVA, 13.2 kV

$$Z_{st}(\Omega) = \text{PU} \times \text{base}$$

$$= 0.08 \times \frac{(13.2)^2}{10} \text{ in secondary}$$

$$= 0.08 \times \frac{(13.2)^2}{10} \times \left(\frac{66}{13.2}\right)^2 \text{ in primary}$$

In PU : to 15 MVA base, 66 kV

$$= 0.08 \times \frac{(13.2)^2}{10} \times \left(\frac{66}{13.2}\right)^2 \div \frac{(66)^2}{15}$$

No.

$$Z_{st} \text{ (PU)} = 0.12 \text{ PU in primary.}$$


$$Z_p = \frac{1}{2} (0.07 + 0.09 - 0.12) j$$

$$Z_p = 0.02 j \text{ PU}$$

↳ neglecting R

$$Z_s = \frac{1}{2} (0.07 + 0.12 - 0.09) = j0.05 \text{ PU}$$

$$Z_t = j0.07$$

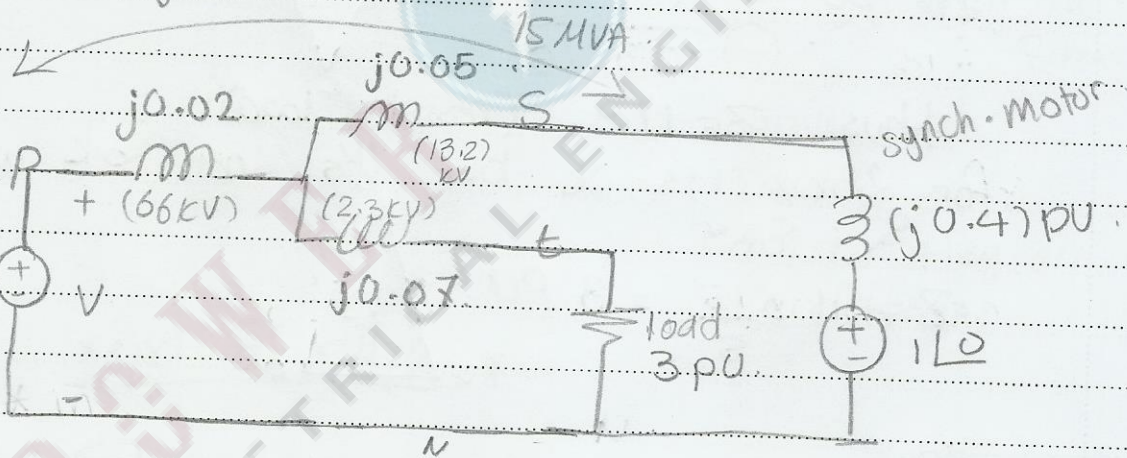

* infinite bus:

✓ constant (infinite number of generators)

f. constant

$$Z_s = 0$$


* the resistive load:-

5 MW, 2.3 kV

to a base of 2.3 kV, 5 MVA

$$Z = 1 \text{ PU}$$

(prove it) →

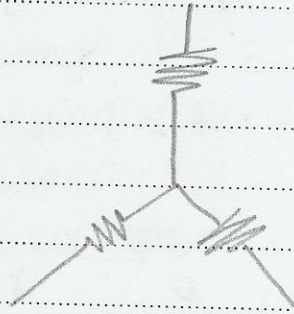

$$Z = \frac{V_{LN}}{I}$$

$$I = \frac{S}{3V_{LN}}$$

$$Z = \frac{3V_{LN}^2}{S} = \frac{V_{LL}^2}{S} = \frac{(2.3)^2}{5} \text{ (in } \Omega \text{)}$$

$$\text{Im PU} = \frac{(2.3)^2/5}{(2.3)^2/5} = 1$$

thus $Z = 1 \angle 0^\circ$ (resistive load)

for 2.3 kV it's ok but it's not ok with S, so..

$$Z = 1 \times 15 = 3 \text{ PU}$$

* for synchronous motor :-

$$7.5 \text{ MVA}$$

$$13.2 \text{ kV}$$

$$X = 0.2j \text{ PU}$$


$$X_{\text{new}} (\text{PU}) = 0.2j \times \frac{15}{7.5} = j0.4 \text{ (in S)}$$

Base values: 15 MVA

13.2 kV


Experience makes you perfect Dr. Hisham Hamdan

No.

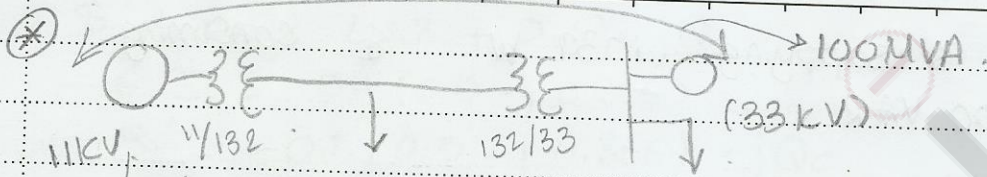

base kV = 132 kV
base MVA = 100 MVA

Z rating Z rating

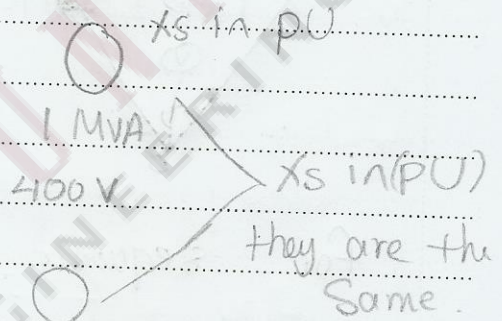

In (a) they are different


*end of CH.2 *

Solving problems of ch.1

1.10 $E_{an} = -120 \angle 210^\circ \text{ V}$

$I_{na} = 10 \angle 60^\circ \text{ A}$

$E_{an} = 120 \angle 30^\circ$ add 180°

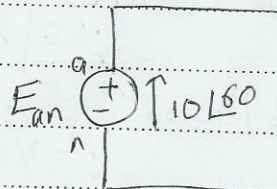


source is supplying.

$$S = EI^* = 120 \angle 30^\circ * 10 \angle -60^\circ$$


$$= 1200 \angle -30^\circ$$

$$= 1039 - j600 \text{ VA}$$

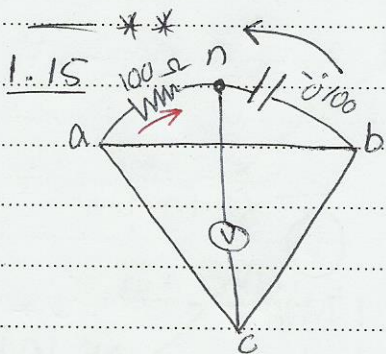Source is supplying 1039 W & consuming 600 VAR




Leading Lab \rightarrow Capacitor

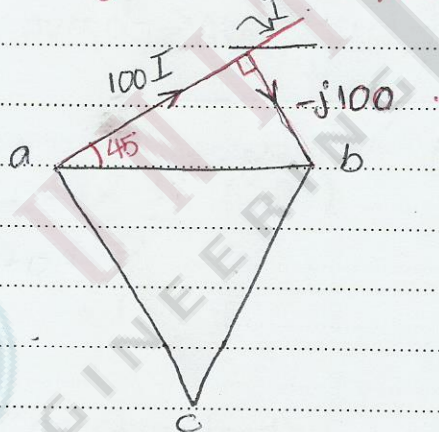

for sequence abc


for sequence cba

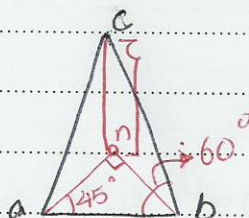

1.21

V = constant

* motor consumes

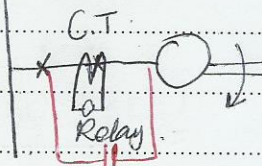

$$S_1 = 0.92 \angle 36.87^\circ = 0.92 (0.8 + j0.6) \text{ MVA}$$

* S_2 generator supplies $0.1 \angle -60^\circ = 0.1 (0.5 - j0.866)$
 leading PF

For successful operation $|I_1| = |I_2|$
 Condenser consumes $-jQ_c$

No.

$$S_1' = 0.92 (0.8 + j0.6) - jQ_c$$

$$\rightarrow S_2 = -0.1 (0.5 - j0.866)$$

$$S_2' = -0.1 (0.5 - j0.866) - jQ_c$$


$$|S_1| = |V| |I_1^*|$$

$$\& |I_1| = |I_2'|$$


$$|S_1| = |S_2'|$$

Solve it to find Q_c

Using phasor Diagram :-

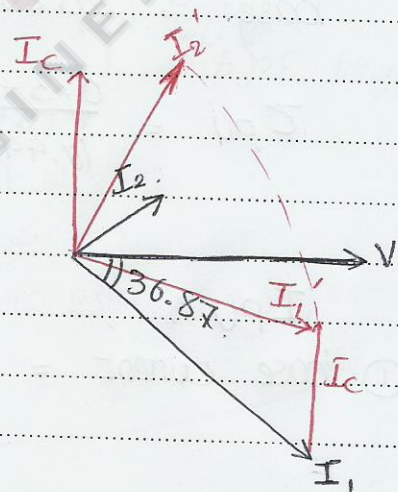

1.16 3- ϕ motor

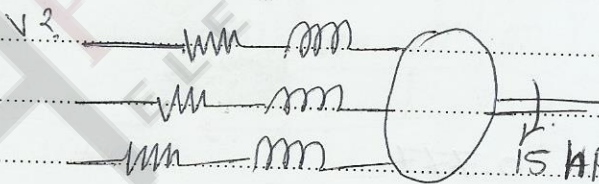

15 HP, $\eta = 90\%$

PF = 0.8 lag.

V = 440V.

$$P_{in} = \frac{15 \times 746}{0.9}$$


$$S_{in} = \frac{15 \times 746}{0.9 \times 0.8} \angle 36.87^\circ = 15514.67 \angle 36.87^\circ \text{ VA}$$

$$V_s = 1 \angle 0 + (0.777 \angle -36.87) (0.0301 + j 0.301)$$


~~VR = 271.45 - (440/\sqrt{3})~~

$$V_R = \frac{271.45 - (440/\sqrt{3})}{(440/\sqrt{3})}$$

**
Problems of CH.2


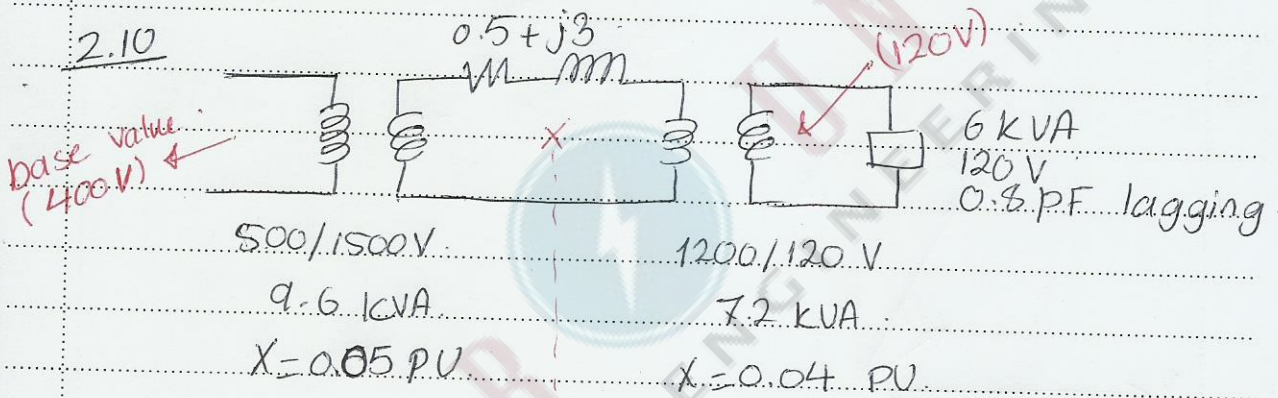


base values "10 kVA, 1200V"

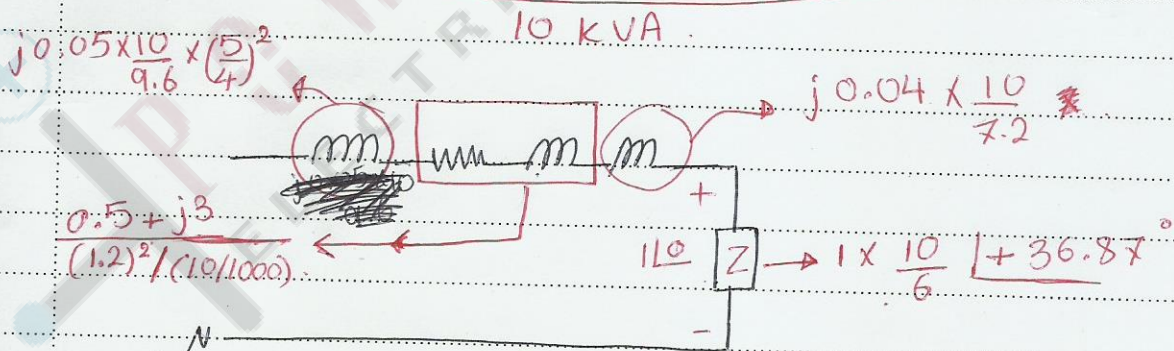

$$I (pu) = \frac{1 \angle 0}{10/6 \angle 36.87} = 0.6 \angle -36.87^\circ$$

Lecture "9" CH.3

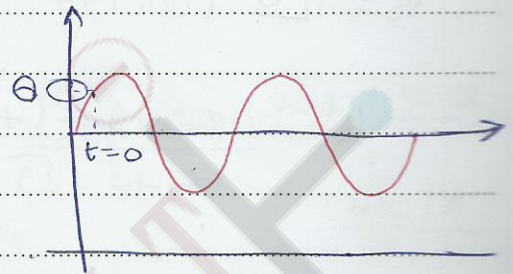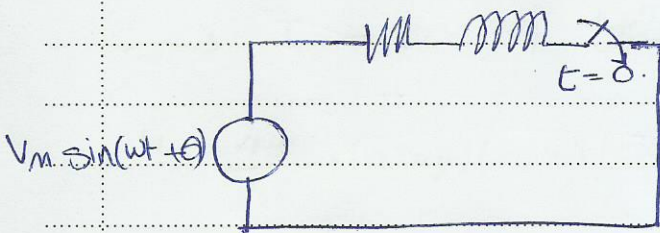

$$i_{tot} = i_{ss} + i_{tr}$$

$$i_{tot} = \frac{V_{max}}{Z} \sin(\omega t + \theta - \phi) + A e^{-\frac{R}{L}t}$$

$$\phi = \tan^{-1} \frac{\omega L}{R}$$

θ : point on wave at which the switch closes.

at $t=0 \rightarrow$

$$i(t) = 0 = \frac{V_{max}}{Z} \sin(\theta - \phi) + A$$

$$\text{So: } A = -\frac{V_{max}}{Z} \sin(\theta - \phi)$$

$$i(t) = \frac{V_{max}}{Z} (\sin(\omega t + \theta - \phi) - \sin(\theta - \phi) e^{-\frac{R}{L}t})$$

for $\theta=0$ & $\phi=90 \rightarrow R \leq 0$

AC component of $i \rightarrow$ fig(1)

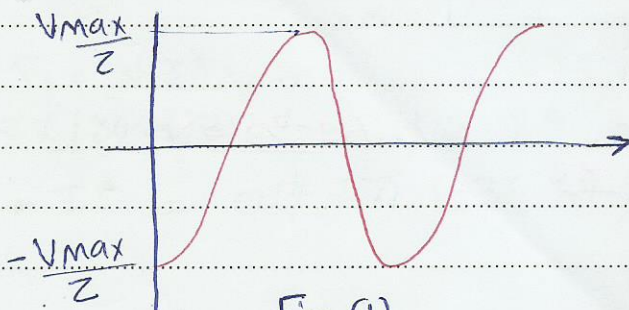


Fig (1)

for $\theta \ \& \ \phi = 90$ (fig 2)

& for the DC component
fig (3):



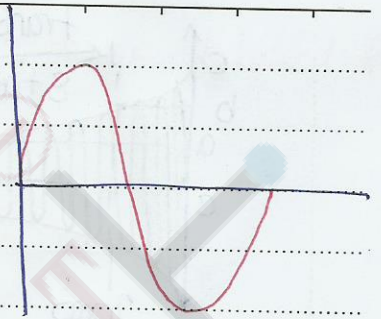



fig (2)

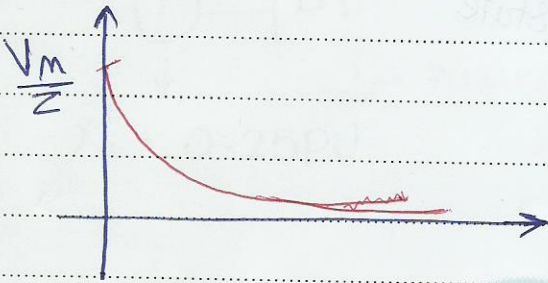

oscilloscope

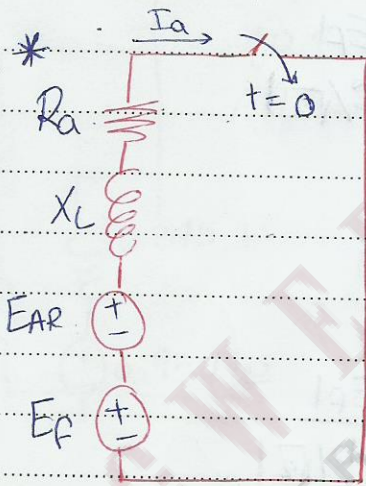

Put a
→ short
resistor.

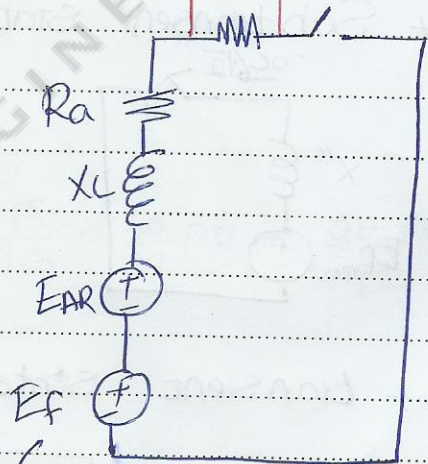

$$E_f = 4.44 \phi N_f k_d k_p$$

flux ϕ \downarrow freq \downarrow constant of speed the gen.

$$E_{AR} = -j k I_a$$


$$-E_f - E_{AR} + j I_a X_L + I_a R_a = 0$$

$$E_{AR} = (-j k I_a)$$


$$-E_f + j k I_a + j I_a X_L + I_a R_a = 0$$

$$-E_f + j I_a (k + X_L) + I_a R_a = 0$$


$X_s \rightarrow$ at steady state

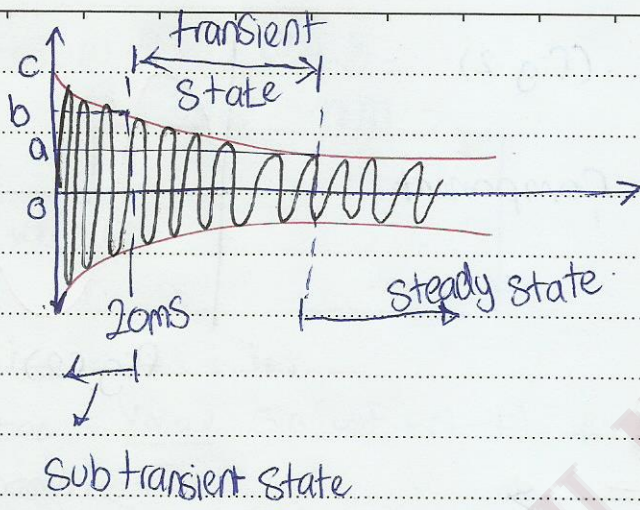


* Subtransient state $\rightarrow x_d'' = \frac{|E_f|}{|0.6/\sqrt{2}|}$


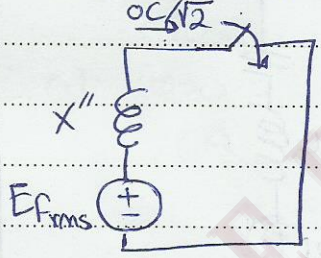


* transient state $\rightarrow x_d' = \frac{|E_f|}{|0.6/\sqrt{2}|}$
 direct axis

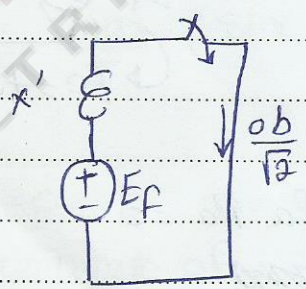

* Steady state $\rightarrow x_d = \frac{|E_f|}{|0.9/\sqrt{2}|}$

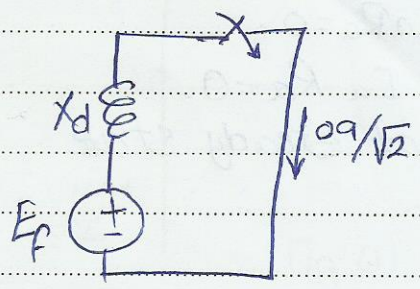


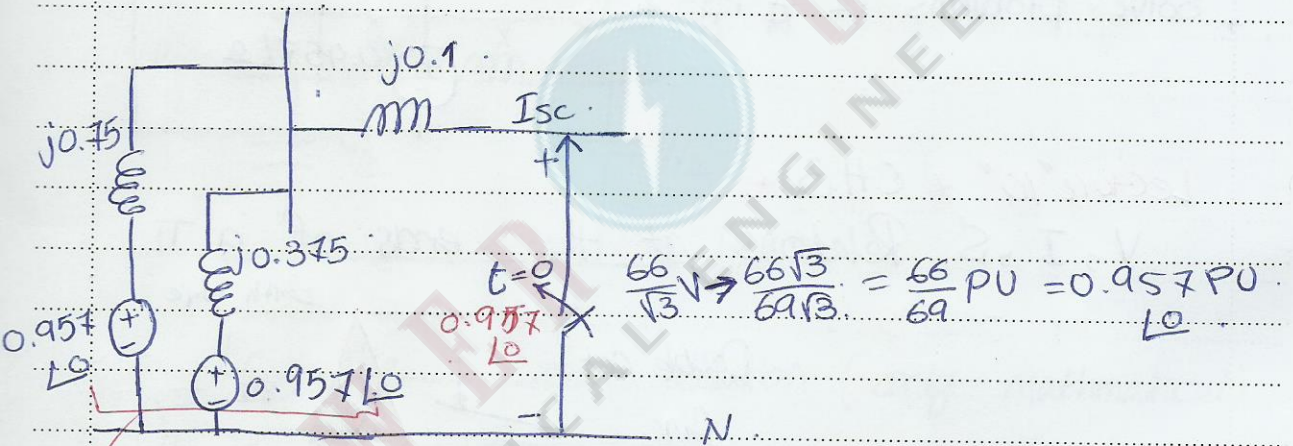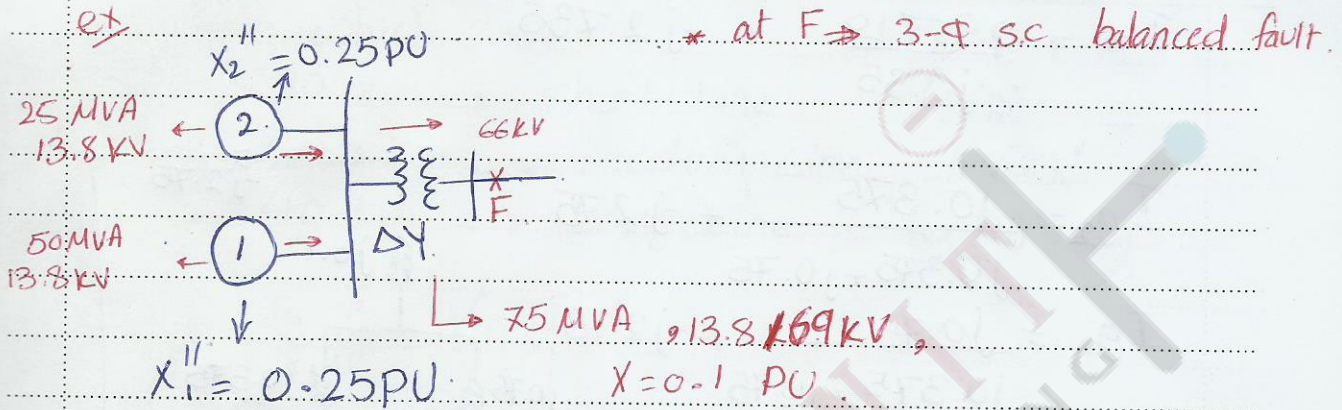

$$j0.75 = 0.25 \times \frac{75}{25}$$

$$j0.375 = 0.25 \times \frac{75}{50}$$

there's no circulating current.

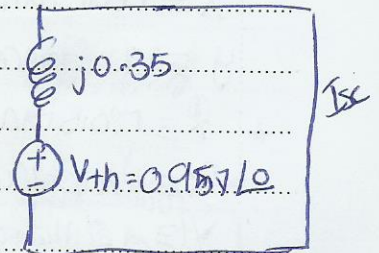

when the switch is open.


$$V_{th} = 0.957 \angle 0$$

$$Z_{th} = j0.1 + \frac{j0.75 \times j0.375}{j0.75 + j0.375} = j0.35 \text{ pu}$$

$$I_{sc} = \frac{0.95710}{j0.35} = -j2.735$$

$$I_{g2} = \frac{j0.375}{j0.375 + j0.75} * -j2.75$$
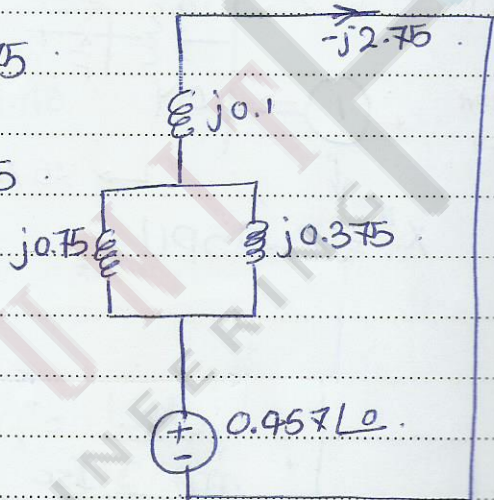
$$I_{g1} = \frac{j0.75}{j0.375 + j0.75} * -j2.75$$



Solve problems 12 & 13 *

Lecture "10" * CH.3 *

V, I, S Relations at the ends of a TL

Earth wire

Double cat

line

* r \equiv resistance per unit length
(Ω/km)


X \equiv reactance per unit length

Y \equiv admittance per unit length

* R \equiv resistance of a total line

X \equiv reactance of a total line

Y \equiv admittance of the total line

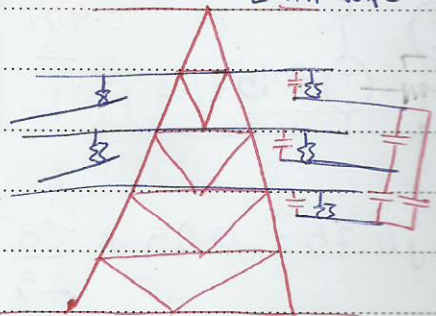

each line

have $\frac{r}{m}$ $\frac{X}{m}$
 $Y = j\omega C$

$$r + jX = Z$$


$$R + jX = Z$$

* Line which is:

$< 80 \text{ km}$ \rightarrow short Line "fig(1)"

$80 - 240 \text{ km}$ \rightarrow medium Line "fig(2)"

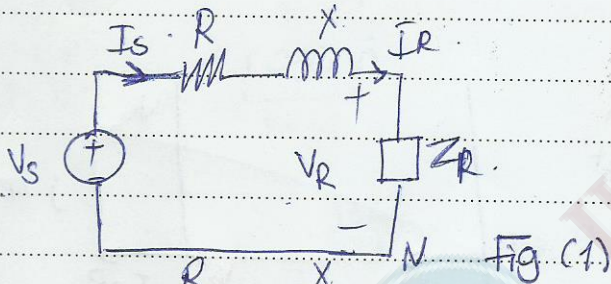$> 240 \text{ km}$ \rightarrow Long Line "fig(3)"



Long Line : exact solution (only mathematical)

Fig(3)

* The relationship between V_s & V_R


$$I_s = I_R \quad \text{--- (1)}$$

$$V_s = V_R + I_R Z_R \quad \text{--- (2)}$$


Using two ports network:

$$V_s = \boxed{t_{11}} V_R - \boxed{t_{12}} I_R$$
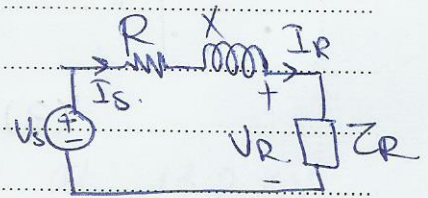
$$I_s = \boxed{t_{21}} V_R + \boxed{t_{22}} I_R$$




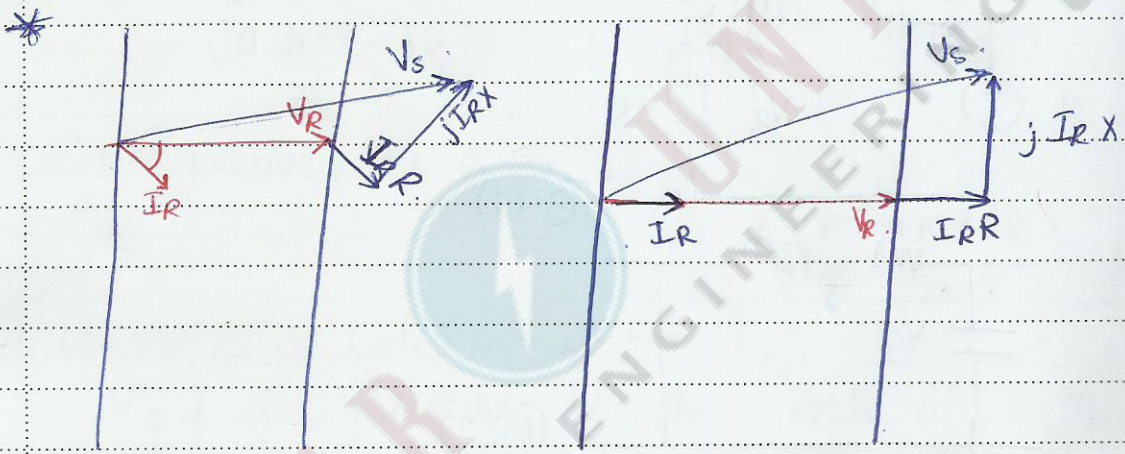* $A = 1$
 $B = Z$
 $C = 0$
 $D = 1$ } "according to the equations"
 (1) & (2)



(1) Lagging PF

(2) Unity PF

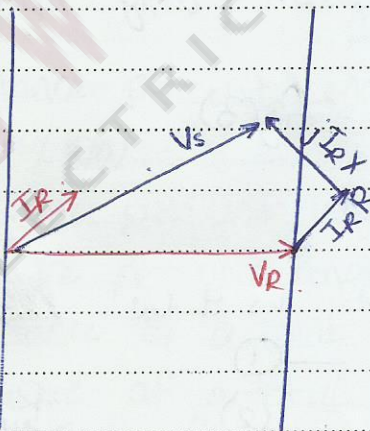



(3) Leading PF

$$V_R = \frac{|V_{NL}| - |V_{FL}|}{|V_R|}$$
 then :-

$$V_R = \frac{|V_S| - |V_R|}{|V_R|}$$

(300 MVA) base.

No.

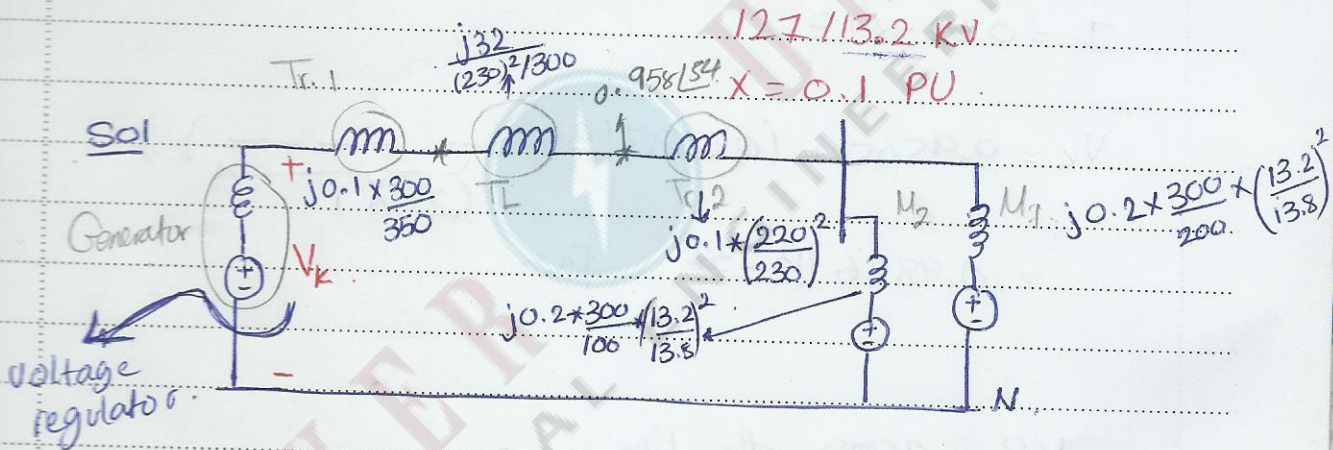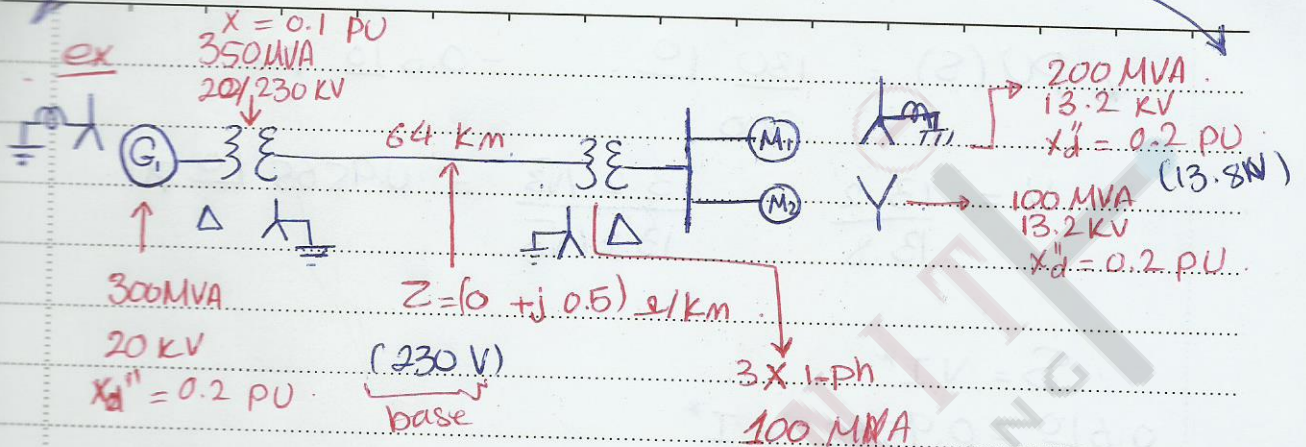

3-ph Rating :

300 MVA

$$127\sqrt{3} \neq 13.2 \rightarrow 220/13.2$$

$$\frac{230 \times 13.2}{220} = 13.8$$

220

$M_1 \rightarrow 120 \text{ MW at U.PF at } 13.2 \text{ kV}$

$M_2 \rightarrow 60 \text{ MW at U.PF at } 13.2 \text{ kV}$

$$M_1 + M_2 = 180 \text{ MW}$$

$$S = 180 \text{ MVA}$$

$$* \text{PU}(S) = \frac{180 \text{ LO}}{300} = 0.6 \text{ LO PU}$$

$$* V = \frac{13.2}{13.8} = \frac{13.2 \sqrt{3}}{13.8 / \sqrt{3}} = 0.9565 \text{ LO PU}$$

$$S = VI^*$$

$$0.6 \text{ LO} = 0.9565 * I^*$$

$$I = 0.6237 \text{ LO}$$

$$V_k = 0.9565 + (0.6237 \text{ LO} * (\underbrace{- + - + -}_{(2 \times)}))$$


$$= 0.9826 \angle 13.237^\circ \text{ PU}$$

V_R across the Line is

$$V_R = \frac{0.9826 - 0.9582}{0.9582}$$

Continue Solving problem for ch. 2

Q. 2

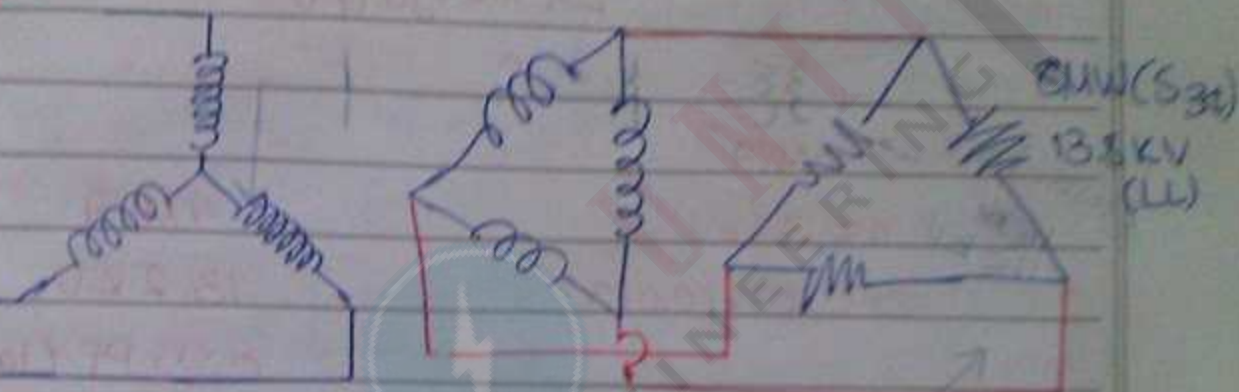

COZ it's $\Delta \rightarrow \frac{(13.8)^2}{R} = \frac{8}{3}$


$\rightarrow R = \underline{71.415 \Omega}$

Note If it was Y-connected to


Find $R \rightarrow \frac{(13.8)^2}{R} = \frac{8}{3} \rightarrow R = \underline{71.415}$

COZ (V) is already divided by $\sqrt{3}$.

base values "10MVA, 13.2KV"

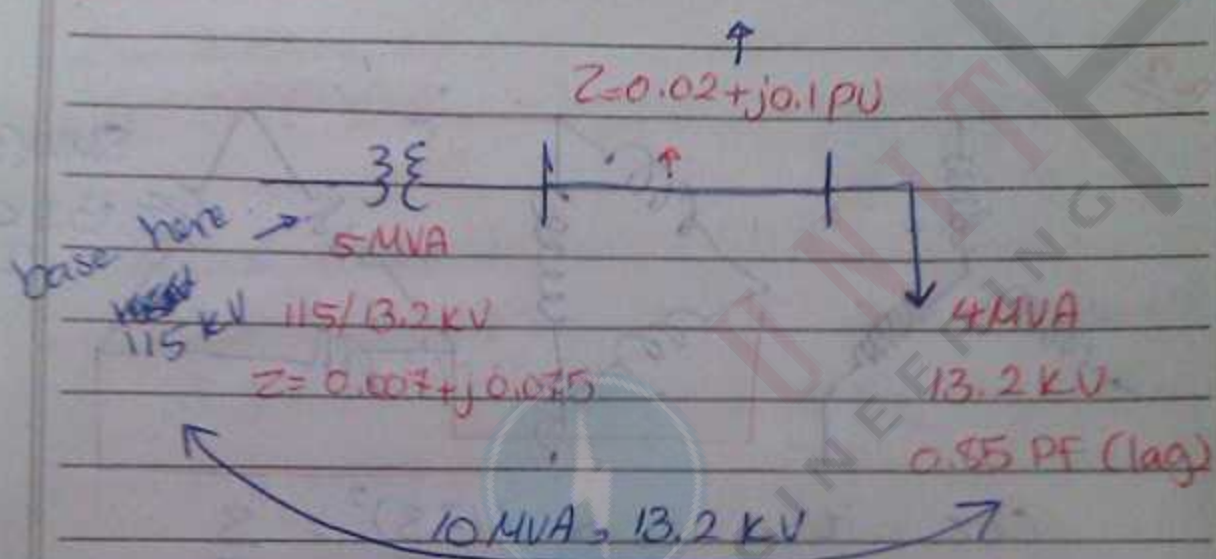

Impedance diagram =

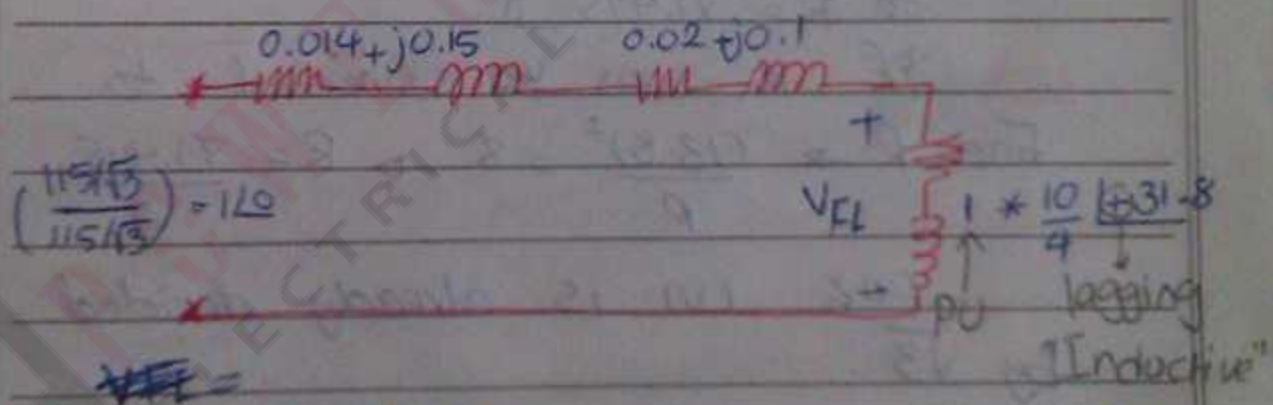


~~$V_{FL} =$~~
 $V_{FL} = 2.5 | 31.8^\circ$



$2.5 | 31.8^\circ + 0.14 + j0.15 + 0.02 + j0.1$

$V_R = \frac{V_{NL} - V_{FL}}{V_{FL}}$

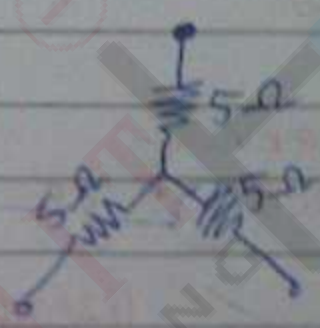6.2 3x 1-ph
 1.2 / 0.12 KV
 7.2 KVA
 $X = 0.05 \text{ PU}$



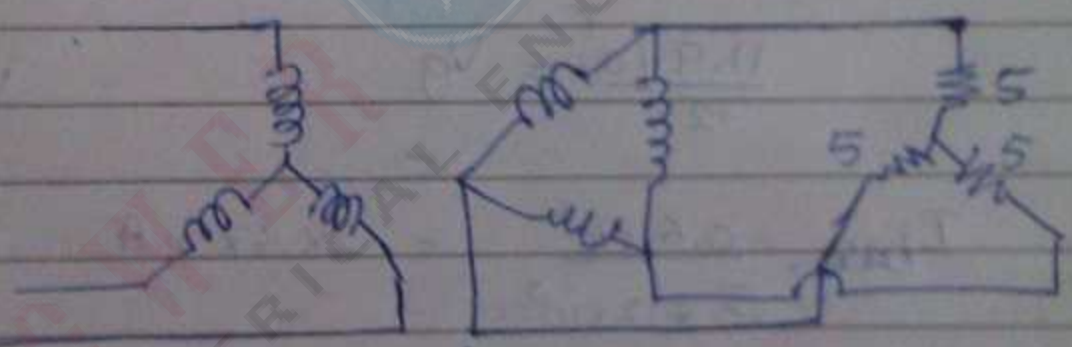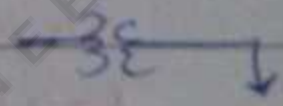If we make it Y-Δ
 $(1.2 \times \sqrt{3} / 0.12) \text{ KV}$
 $7.2 \times 3 = 21.6 \text{ KVA}$
 $X = 0.05 \text{ PU}$



$$5 \times \left(\frac{(1.2\sqrt{3})^2}{(21.6/1000)} \right) = j10 \Omega$$

We see the Impedance as
 $(1500 + j10) \Omega$


In PU $\rightarrow \frac{1500 + j10}{(1.2/\sqrt{3})^2 / (21.6/1000)}$

17.2

PF = 0.8 lagging

$$V_{LL} = 11.9 \text{ kV}$$

$$I_L = 20 \text{ A}$$

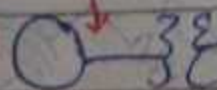

Need the (V) here

base \Rightarrow (12/0.6 kV) Δ Δ base values:
 12 kV 0.6 MVA Δ 0.6 kV, 0.6 MVA
 $X = 0.1 \text{ pu}$

$$\frac{11.9}{12} \angle 0^\circ = V_g$$

$$I_{\text{base}} = \frac{0.6 \times 10^6}{\sqrt{3} \times 12 \times 10^3} = 28.875 \text{ A}$$

$$I (\text{in pu}) = \frac{20}{28.875} = 0.693 \angle -36.87^\circ$$



$$V_L = \frac{11.9}{12} \angle 0^\circ - j0.1 \times 0.693 \angle -36.87^\circ$$

$$V_L = 0.95174 \angle -3.33^\circ$$

$$V_L = 0.95174 \times \frac{600}{\sqrt{3}} = \boxed{} \text{ V}_{\text{ph}}$$

$$V_{LL} = 0.95174 \times 600 = \boxed{} \text{ V}_{LL}$$


Problems of CH.3 :-

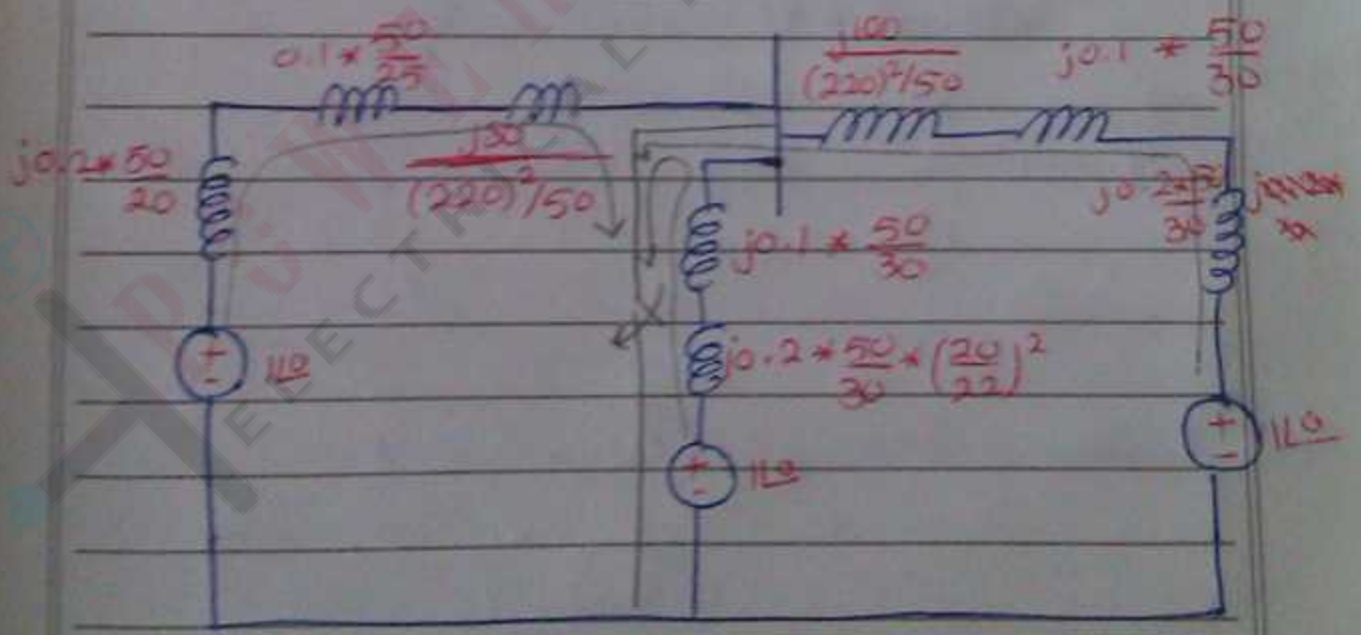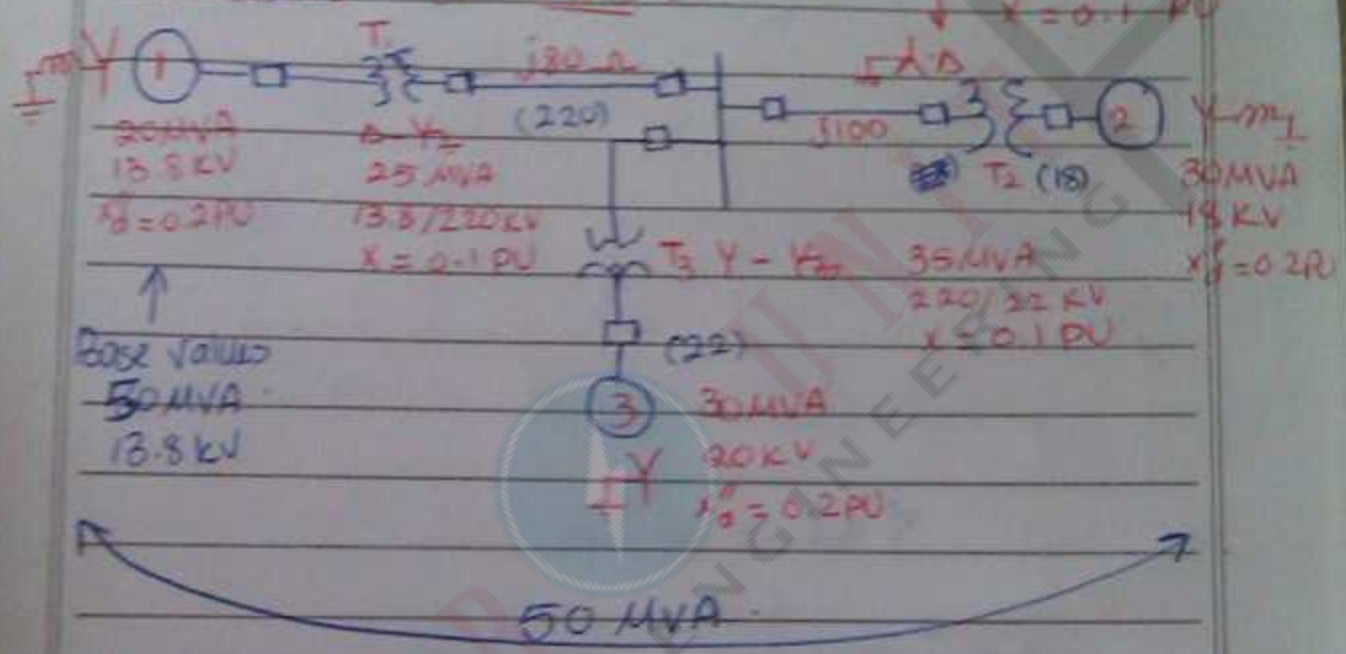

all the three current moves to the
SLC $\rightarrow S = VI^*$

* back to our material :- $j\omega \frac{C}{2}$

Medium Line :-

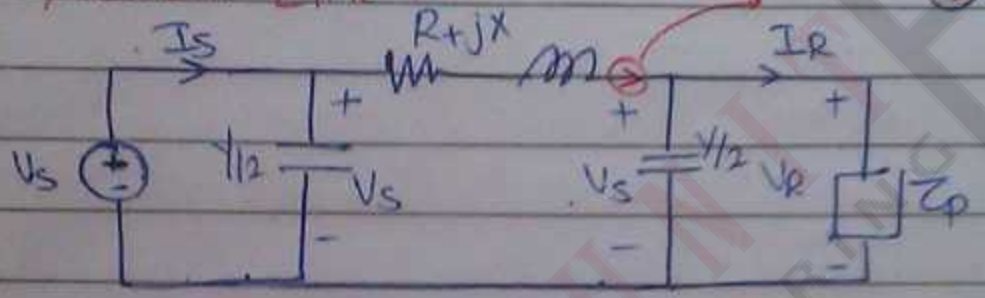

$$* V_s = V_R + (I_R + V_R \cdot Y/2) Z$$

$$V_s = (1 + ZY/2) V_R + I_R Z$$

$$* I_s = (V_s \cdot Y/2) + (V_R \cdot Y/2) + I_R$$

$$= \left[\left(1 + \frac{ZY}{2}\right) V_R + I_R Z \right] Y/2 + (V_R \cdot Y/2) + I_R$$

$$I_s = Y \left(1 + \frac{YZ}{4}\right) V_R + \left(1 + \frac{YZ}{2}\right) I_R$$

$$A = 1 + \frac{YZ}{2} \quad (\text{dimensionless})$$


$$B = Z \quad (\Omega)$$

$$C = Y \left(1 + \frac{YZ}{4}\right) \quad (S)$$

$$D = \left(1 + \frac{YZ}{2}\right) \quad (\text{dimensionless})$$

* medium Line :-
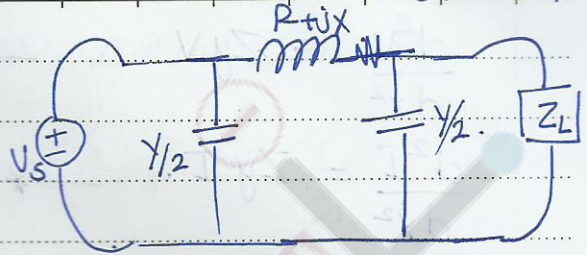
$$V_s = \left(1 + \frac{Y Z}{2}\right) V_R + Z I_R$$



$$I_s = Y \left(1 + \frac{Y Z}{4}\right) V_R + \left(1 + \frac{Y Z}{2}\right) I_R$$

$$V_R = \frac{|V_{NL}| - |V_{FL}|}{|V_{FL}|}$$

$$\rightarrow V_R = \frac{|V_s|}{|A|} - \frac{V_{FL}}{V_{FL}}$$

$$V_s = A V_R + B I_R$$

$$|V_{RNL}| = \frac{|V_s|}{|A|}$$

* For $A \leq 1$

$$|A| = 0.85 - 1$$

$$\angle A = \alpha = 0 - 3^\circ$$

* Long Line *

$$dv = \frac{I + (dI + I)}{2} \cdot Z dx$$

$$= Z I dx$$


$$\frac{dv}{dx} = Z I$$

where: Z = impedance / unit length

y = admittance / unit length

$$dI = \frac{V + dv + V}{2} \cdot y dx$$

$$\frac{dI}{dx} = y V$$

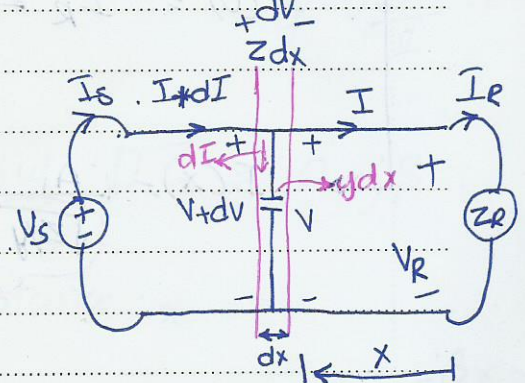

$$\frac{d^2 V}{dx^2} = ZyV \quad \text{--- * --- (1)}$$

$$\frac{d^2 I}{dx^2} = ZyI \quad \text{--- * --- (2)}$$

* For (1) *

$$\frac{d^2 V}{dx^2} - yZV = 0$$

$$(s^2 - yZ)V(s) = 0$$

$$* V(x) = A_1 e^{\sqrt{yZ}x} + A_2 e^{-\sqrt{yZ}x} \quad \text{--- **}$$

$$\& I(x) = \left(\frac{dV}{dx} \right) / Z = \frac{A_1 \sqrt{yZ} e^{\sqrt{yZ}x} - A_2 \sqrt{yZ} e^{-\sqrt{yZ}x}}{Z}$$

$$V(0) = V_R = A_1 + A_2 \quad (\text{for } x=0) \quad \text{--- (3)}$$

$$I(0) = I_R Z_C = A_1 - A_2 \quad \text{--- (4)}$$

$$\rightarrow I(x) = \frac{A_1}{\sqrt{Z/Y}} e^{\sqrt{yZ}x} - \frac{A_2}{\sqrt{Z/Y}} e^{-\sqrt{yZ}x}$$

characteristic impedance Z_C

Solving for (3) & (4) :

$$A_1 = \frac{V_R + I_R Z_C}{2}$$

$$A_2 = \frac{V_R - I_R Z_C}{2}$$

For $\sqrt{YZ} = \text{propagation constant } (\gamma) \quad (\delta)$

then :-

$$V(x) = \frac{V_R + I_R Z_c}{2} e^{\delta x} + \frac{V_R - I_R Z_c}{2} e^{-\delta x}$$

$$\& \quad I(x) = \frac{V_R + I_R}{Z_c} e^{\delta x} - \frac{V_R - I_R}{Z_c} e^{-\delta x}$$

For $\delta = \alpha + j\beta \rightarrow \text{phase constant (rad/unit length)}$
 $\downarrow \quad \downarrow$
 attenuation constant (nepers/unit length)

propagation
constant

$\delta = \sqrt{ZY}$; for a lossless line: $Z = (j\omega L)/l$

$$Y = \frac{j\omega C}{l} \quad \text{total line}$$

thus

$$\delta = \sqrt{\frac{j\omega L}{l} \cdot \frac{j\omega C}{l}} = \frac{j\omega}{l} \sqrt{LC} = 0 + j\beta$$

* $\alpha = 0 \rightarrow \text{no resistance} \cdot *$


$$V(x) = \frac{V_R + I_R Z_c}{2} e^{\alpha x} e^{j\beta x} + \frac{V_R - I_R Z_c}{2} e^{-\alpha x} e^{-j\beta x}$$

incident wave
src is end)
(بنا ویرا /)

reflected wave
 \downarrow
incident
end pnt.

if $(Z_R = Z_C)$: no reflected wave.
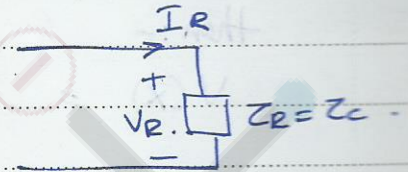
$$\frac{V_R - I_R Z_C}{2} e^{-\alpha x} e^{-j\beta x} = 0$$



→ So the line is called flat line, or infinite long line or infinite length.

$$* Z_C = 400 \angle 0 - (-15)^\circ \quad * \quad \text{\$}$$

$$Z_C = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{18 \angle 60-90}{14 \angle 90}} = \sqrt{\frac{18}{14} \angle 0 - (-15)}$$

$$* \text{ For lossless line } \rightarrow Z_C = \sqrt{\frac{j\omega L}{j\omega C}} \rightarrow \text{phase} = 0$$

* For two parallel lines:

$$Z_C = 200 \angle 0 - (-15)$$

$$= \sqrt{\frac{\frac{1}{2} |Z| \angle 60-90}{2 |Y| \angle 90}} = 200 \angle 0 - (-15)$$

↳ same phase

For $Z_C = 400 \angle 0$; Z_C is called "Surge Impedance".

* Surge Impedance Loading (SIL) → '3φ' value

$$SIL = \frac{V_{LL}^2}{Z_C}$$

$$* \lambda = \text{wave length} = \frac{2\pi}{\beta}$$

$$* V = \text{wave velocity} = f \cdot \lambda = \frac{2\pi f}{\beta}$$

$$\text{For } \beta \text{ (In a lossless line)} = \frac{\omega}{l} \sqrt{LC}$$

$$\text{thws } V = \frac{l}{\sqrt{LC}} \text{ (m/s)} = 3 \times 10^8 \text{ m/s.}$$

$$* \cosh \theta = (e^{\theta} + e^{-\theta}) / 2$$

$$\sinh \theta = (e^{\theta} - e^{-\theta}) / 2$$

We will use them to simplify $V(x)$ & $I(x)$:-

$$* V(x) = \cosh(\gamma x) V_R + I_R Z_C \sinh \gamma x$$

$$* I(x) = \frac{\sinh(\gamma x) V_R}{Z_C} + I_R \cosh(\gamma x)$$

all of them are (+)

For $(x=l)$

$$V(l) = V_S = \overbrace{V_R \cosh(\gamma l)}^A + I_R Z_C \overbrace{\sinh(\gamma l)}^B$$

$$I(l) = I_S = \underbrace{\frac{\sinh(\gamma l) V_R}{Z_C}}_C + I_R \underbrace{\cosh(\gamma l)}_D$$

$$\rightarrow A = D$$

$$\rightarrow AD - BC = 1$$

$$\cosh \gamma l = \frac{e^{\gamma l} + e^{-\gamma l}}{2} = \frac{e^{\alpha l} | \beta l + e^{-\alpha l} | - \beta l}{2}$$


$$\sinh \gamma l = \frac{e^{\gamma l} | \beta l - e^{-\alpha l} | - \beta l}{2}$$

$$\textcircled{*} \cosh \delta L = 1 + \frac{(\delta L)^2}{2!} + \frac{(\delta L)^4}{4!} + \dots$$


(تقریباً)

$$\sinh \delta L = \delta L + \frac{(\delta L)^3}{3!} + \frac{(\delta L)^5}{5!} + \dots$$

تقریباً (تقریباً)

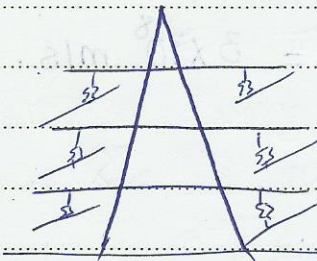

double circuit

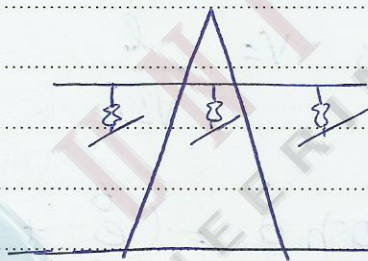

single circuit

ex Single circuit

230 mi

$$Z = 0.8431 \angle 79.04^\circ \quad \Omega/\text{mi}$$

$$y = 5.105 \times 10^{-6} \angle 90^\circ \quad \text{S}/\text{mi}$$

receiving end

$$S_R = 125 \text{ MVA}$$

215 kW

at u.p.F.

Find: V_s , I_s , S_s

Sol

$$\begin{aligned} \delta L &= \sqrt{0.8431 \angle 79.04^\circ * 5.105 \times 10^{-6} \angle 90^\circ * 230} = \sqrt{42} \text{ e} \\ &= 0.4772 \angle 184.52^\circ \\ &= 0.0456 + j0.475 \end{aligned}$$

$$Z_c = \sqrt{\frac{Z}{y}} = \sqrt{\frac{0.8431 \angle 79.04^\circ}{5.105 \times 10^{-6} \angle 90^\circ}} = 406.4 \angle -5.48^\circ$$

$$\cosh \delta L = \frac{e^{0.0456} |0.475^{\text{rad}} + e^{-0.0456} |-0.475^{\text{rad}}}{2}$$

$$= 0.8904 |1.34^{\circ}$$

$$\sinh \delta L = 0.4597 |84.93^{\circ}$$

$$V_s = \left(0.8904 |1.34^{\circ} * \frac{215000 |0}{\sqrt{3}} \right) + \left(406.4 |-5.48^{\circ} * 0.4597 |84.93^{\circ} * 335 |0 \right)$$

↑
per phase

$$= 137860 |27.77^{\circ}$$

$$I_s = \left(\frac{0.4597 |84.93^{\circ}}{406.4 |-5.48^{\circ}} * \frac{215000 |0}{\sqrt{3}} \right) + \left(0.8904 |1.34^{\circ} * 335.7 |0 \right)$$

$$= 332.31 |26.33^{\circ}$$

$$S_s = 3 V_s I_s^*$$


$$= 3 |V_s| |I_s| |27.77^{\circ} - 26.33^{\circ} = 3 |V_s| |I_s| |1.44^{\circ}$$


* before finding V_s & I_s *

$$I_R = \frac{125 \times 10^6}{\sqrt{3} \times 215 \times 10^3}$$

$$= 335.7 |0$$

* phasor Diagram for medium Line:-

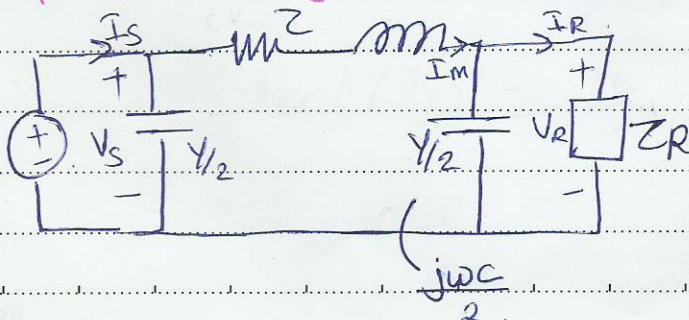

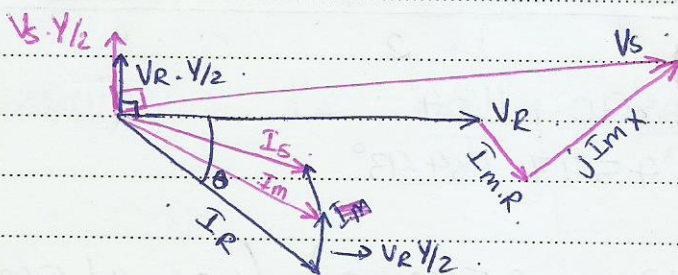

~~That is~~
Continue Solving the example:

$$V_R = \frac{|V_s|}{|A|} - |V_R|$$

$$= \frac{137860}{0.8904} - \frac{215000}{\sqrt{3}} = 24.7\%$$

* Solving the same example in PU:-

Base values: 125 MVA
215 KV

$$\text{base } Z = (215)^2 / 125$$

$$S_{pu} = 1.0 = 1.0 * I_e^*$$

$$I_R = 1.0$$

$$V_s = A V_R + B I_R$$


$$\text{cos}(\phi) = (0.8904 \cdot 1.34 * 1.0) + \frac{370 \sin \theta}{Z} * 1.0$$

is dimensionless

$$= 1.102 \angle 27.75^\circ \quad \text{PU} \Rightarrow * \frac{215000}{\sqrt{3}} = 137860 \angle 27.75^\circ$$

* ~~equi~~ π equivalent circuit for a long line :-


for medium line -

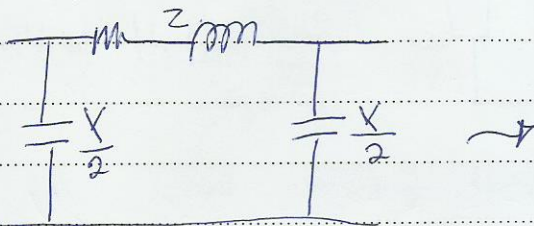

$$V_S = \left(1 + \frac{YZ}{2}\right) V_R + Z I_R$$

(nominal π)

for long line

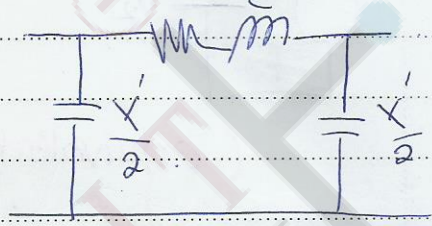

$$V_S = \cosh \delta L V_R + Z_c \sinh \delta L I_R$$

$$V_S = \left(1 + \frac{Y'Z'}{2}\right) V_R + Z' I_R$$

proof \rightarrow

$$\cosh \delta L = \left(1 + \frac{Y'Z'}{2}\right)$$

$$Z_c \sinh \delta L = Z'$$

$$(*) \quad Z' = Z_c \sinh \delta L$$


$$= \frac{\sqrt{Z}}{\sqrt{Y}} \frac{\sqrt{Z}}{\sqrt{Y}} \cdot \frac{l}{l} \sinh \delta L$$

$$Z' = Z \cdot \frac{\sinh \delta L}{\delta L} \quad \rightarrow \quad \sinh \delta L \approx \delta L$$

$$(*) \quad 1 + \frac{Y'Z'}{2} = \cosh \delta L$$

$$\frac{Y'}{2} = \frac{\cosh \delta L - 1}{Z_c \sinh \delta L} = \frac{Y}{2} \frac{\tanh\left(\frac{\delta L}{2}\right)}{\left(\frac{\delta L}{2}\right)}$$
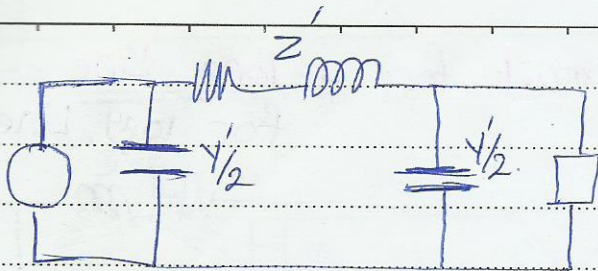
$$\tanh\left(\frac{\delta L}{2}\right) \approx \frac{\delta L}{2}$$



(equivalent π)

ex

$$Z = 230 \times 0.8431 \quad | 79.04$$

$$= 193.9 \quad | 79.04$$

$$Z' = Z_C \sinh \gamma L = Z \frac{\sinh \gamma L}{\gamma L}$$

$$= 193.9 \quad | 79.04 \quad * \quad \frac{0.4597 \quad | 84.93}{0.4772 \quad | 84.52}$$

$$= 186.82 \quad | 79.45$$

$$\frac{Z'}{Z} = 96.2\% \quad \rightarrow \text{error} = -3.8\%$$

$$\frac{Y'}{2} = \frac{0.8904 \quad | 11.34^\circ - 1}{186.82 \quad | 79.45} = 0.000599 \quad | 89.52$$

$$\frac{Y'}{2} = \frac{5.105 \times 10^{-6} \times 230}{2} = 0.000587 \quad | 90$$

$$\frac{Y'/2}{Y/2} = 1.02 \quad \rightarrow \text{error} = +2\%$$

$$V_s = A V_R \rightarrow V_R = \frac{V_s}{A} \quad (\text{at no load})$$

$$(|V_s| = |V_R|)$$



at resonance.

$$I = 0 \rightarrow$$

$$V_s = V_p$$

Circle Diagram: - (receiving end)

$$V_s = A V_R + B I_R$$

$$I_R = \frac{V_s - A V_R}{B}$$

$$I_R = |I_R| \angle \theta$$

$$V_R = |V_R| \angle 0^\circ$$

$$V_s = |V_s| \angle \delta \rightarrow \text{Power Angle.}$$

$$A = |A| \angle \alpha$$

$$B = |B| \angle \beta$$

$$I_R = \frac{|V_s| \angle \delta - |A| |V_R| \angle \alpha}{|B| \angle \beta}$$

$$= \frac{|V_s| \angle \delta - \beta}{|B|} - \frac{|A| |V_R| \angle \alpha - \beta}{|B|}$$

$$I_R^* = \frac{|V_s| \angle \beta - \delta}{|B|} - \frac{|A| |V_R| \angle \beta - \alpha}{|B|}$$

multiply by V_R

$$V_R I_R^* = \frac{|V_s| |V_R| \angle \beta - \delta}{|B|} - \frac{|A| (|V_R|^2) \angle \beta - \alpha}{|B|}$$

single phase

$$L \rightarrow = S_{R1\phi}$$

* V_s & V_r are both L-N voltages.

* multiply by 3 - $\therefore V_s$ & V_r by $\sqrt{3}$ * \leftarrow

$$\underline{S_{3\phi}} = \frac{|V_{LLs}| |V_{LLr}|}{|B|} \cos(\beta - \delta) - \frac{|A| |V_{LLr}|^2}{|B|} \cos(\beta - \alpha)$$

thus:

$$S_R = \frac{|V_s| |V_r|}{|B|} \cos(\beta - \delta) - \frac{|A| |V_r|^2}{|B|} \cos(\beta - \alpha)$$

$$= P + jQ \quad \rightarrow$$

constant \uparrow

$$\textcircled{1} \quad P = \frac{|V_s| |V_r|}{|B|} \cos(\beta - \delta) - \frac{|A| |V_r|^2}{|B|} \cos(\beta - \alpha)$$

to make P maximum: - ($\beta = \delta$)

exact term \leftarrow


$$P_{\max} = \frac{|V_s| |V_r|}{|B|} - \frac{|A| |V_r|^2}{|B|} \cos(\beta - \alpha)$$

Approximate term \leftarrow

$$P_{\max} = \frac{|V_s| |V_r|}{|B|} \quad \text{when } \beta \approx 90^\circ \quad \& \\ \alpha \approx 0^\circ$$

$$\textcircled{2} \quad Q = \frac{|V_s| |V_r|}{|B|} \sin(\beta - \delta) - \frac{|A| |V_r|^2}{|B|} \sin(\beta - \alpha)$$

(*) P-Q plane.

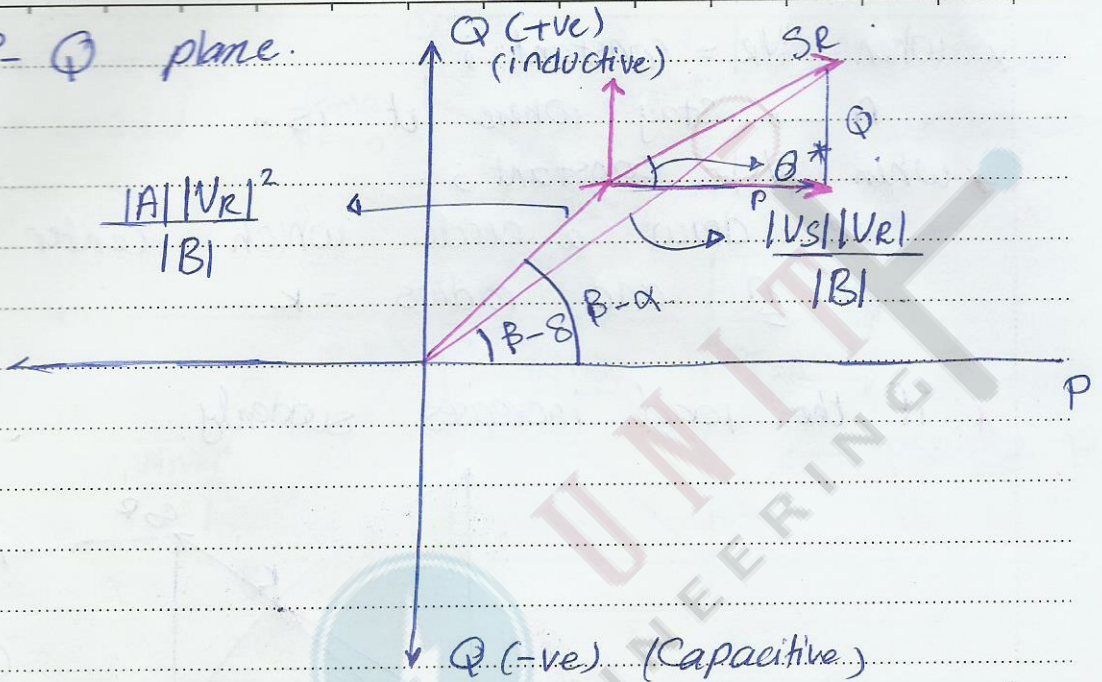


(*) Prove that (S) at no load equals to (alpha).

$$V_s = A V_r + B I_r \text{ at no load}$$

$$|V_s| / S = |A| / \alpha |V_r| / I_0 \text{ thus}$$

$$(S = \alpha) \text{ at no load}$$

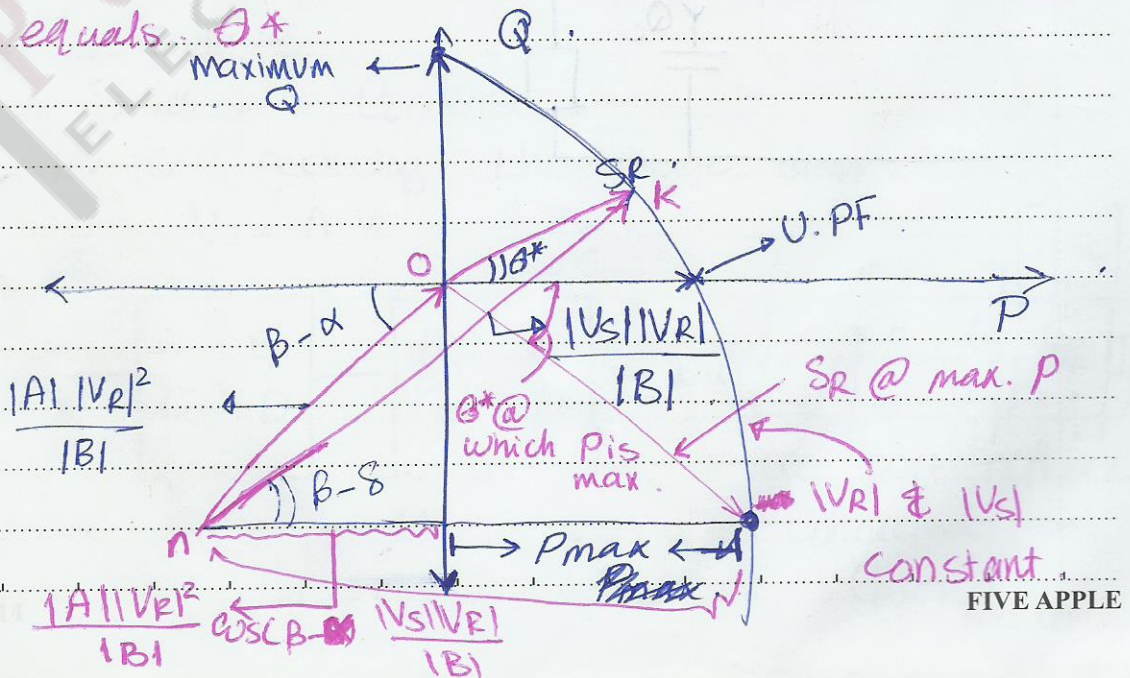move the axis to point at when the angle equals θ^*





* when $|V_R| = \text{constant}$;

$n \rightarrow$ stay where it is .

* when $|V_S| = \text{constant}$;

we draw a circle which center is at \underline{n} and radius = k

* if the load increases suddenly

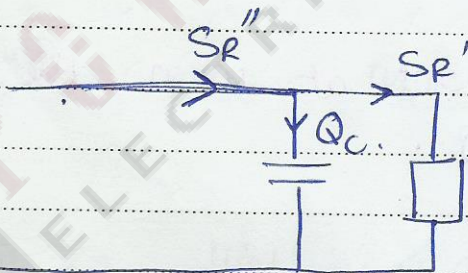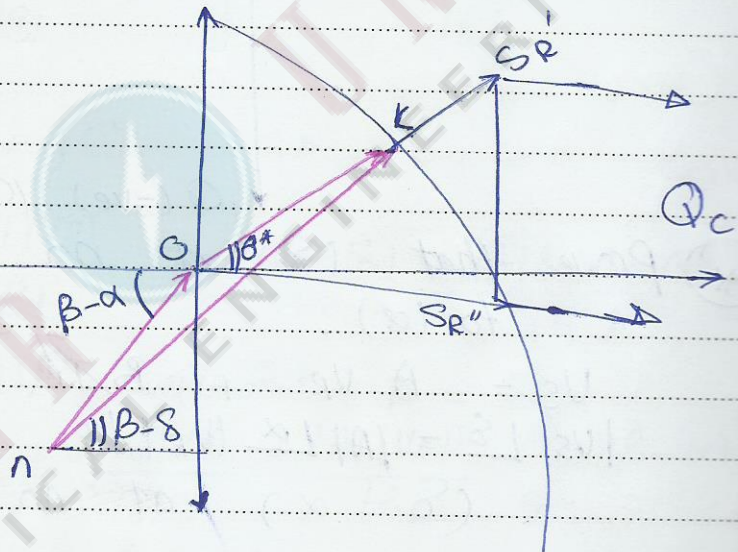



$P_{em} = \dots \text{ MVA}$

$$V_s = V_R + I_R(-jX_c)$$

$$I_s = I_R$$

$$A = 1 \quad B_c = -jX_c$$

$$C = 0 \quad D = 1$$

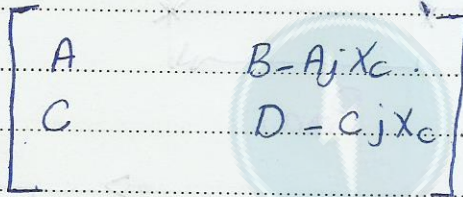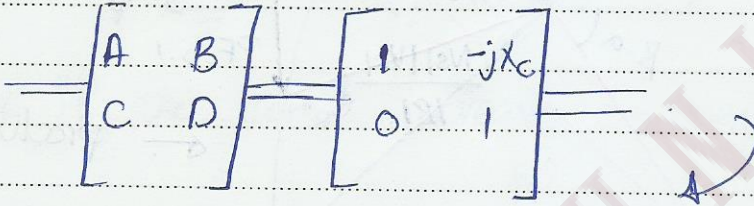


In this case \rightarrow B decreases. So

$V_d = |V_s| - |V_R|$ is less.

~~Note for medium line:~~

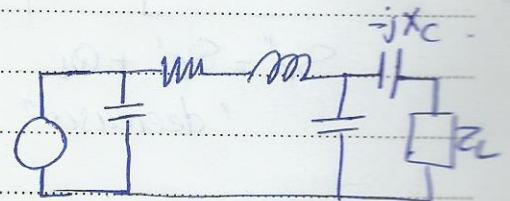
In medium line we put C in that way $\circ -$



B $P_{max} \approx \frac{|V_s||V_R|}{|B|}$, So to increase the transmission Capacity of the line

$$Z_2 > Z_1$$

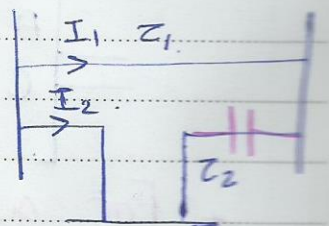C to restore loading balance between two parallel feeders of an equal Impedances.



* There is no series Inductor.

No.

* Series Compensation Factor (Series C.F) :

$$\text{Series C.F} = \frac{X_C}{X_L} = 50\%$$

ex

$$B = 186.78 \angle 77.46^\circ$$

~~Series~~ Series Compensation with

$$\text{C.F} = 70\%$$

1. What is the increase in transmission Capability?

$$0.7 = \frac{X_C}{X_L} \rightarrow 230 \angle 10.8277$$

$$X_C = 0.7 * 230 * 0.8277 \quad (\text{in } \Omega)$$

$$B_{\text{new}} = B_{\text{old}} - \frac{jX_C}{A} \\ = 186.78 \angle 77.46^\circ - \frac{j(0.7 * 230 * 0.8277) * (0.8404 \angle 1.34^\circ)}{A}$$

$$B_{\text{new}} \approx 75 \angle 60.5^\circ \Omega$$

$$P_{\text{max}} \propto \frac{|V_s| |V_r|}{|B|} \quad \text{for } (V_r \& V_s = \text{constants})$$

$$\rightarrow \frac{P_{\text{max}}(\text{new})}{P_{\text{max}}(\text{old})} = \frac{B_{\text{old}}}{B_{\text{new}}} = \frac{186.78}{75} = 250\%$$

• Load (Power) flow analysis:-


$$V = ZI$$

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} & Z_{13} \\ Z_{21} & Z_{22} & Z_{23} \\ Z_{31} & Z_{32} & Z_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} \rightarrow \text{mesh analysis (linear equations).}$$

$$I = yV$$

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} & y_{13} \\ y_{21} & y_{22} & y_{23} \\ y_{31} & y_{32} & y_{33} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} \rightarrow \text{Nodal analysis (linear equ.)}$$

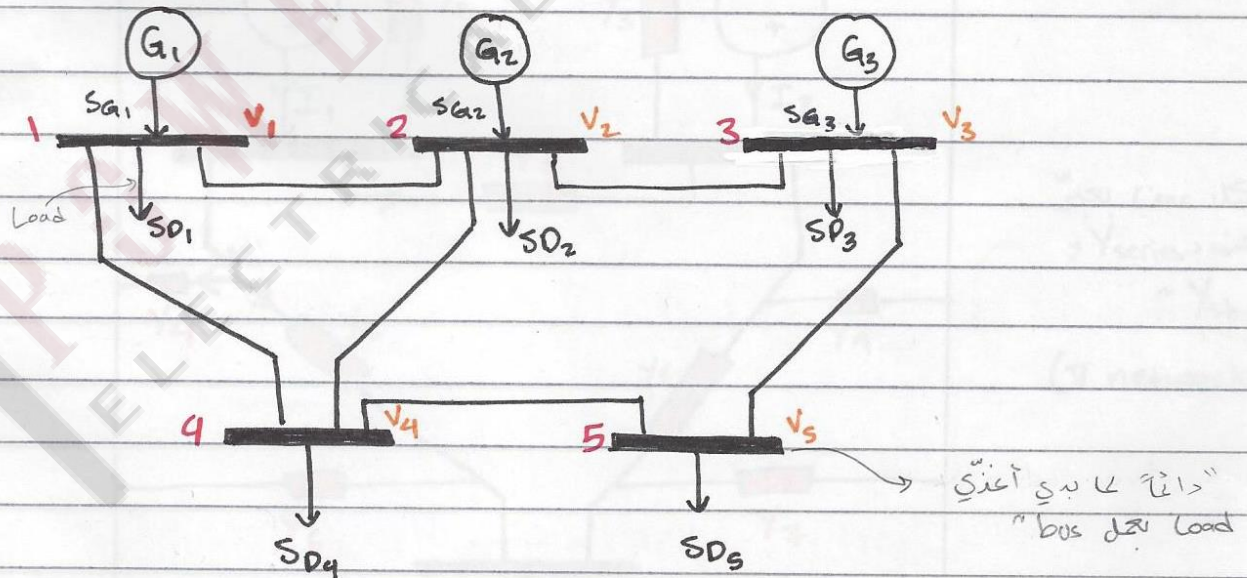What about $S \propto V^2$ (non-linear)? this is solve using numerical methods (i.e newton-raphson, gauss seidel, ..).



S_{G1} : complex power generated by gen. 1.

S_{D1} : ~ ~ delivered (drawn) by load at bus 1.


V_i : voltage at bus i. $= |V_i| \angle \theta_i$

at every bus (i) there are S_{Gi} , S_{Di} (might be zero).

$$\rightarrow S_i = S_{Gi} - S_{Di}$$

$S_i \equiv$ complex power injected from bus (i) to the system.

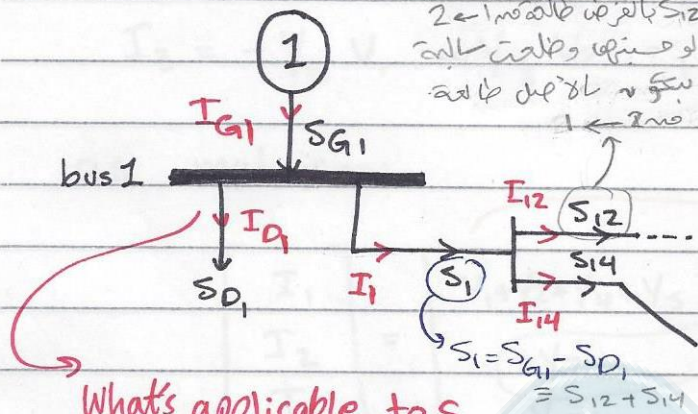
* I have to supply power at all times with acceptable V & frequency limits, with minimum cost.



What's applicable to S , is applicable to I . ($I = S/V$).

xx في حالة حدوث fault في faulty section.

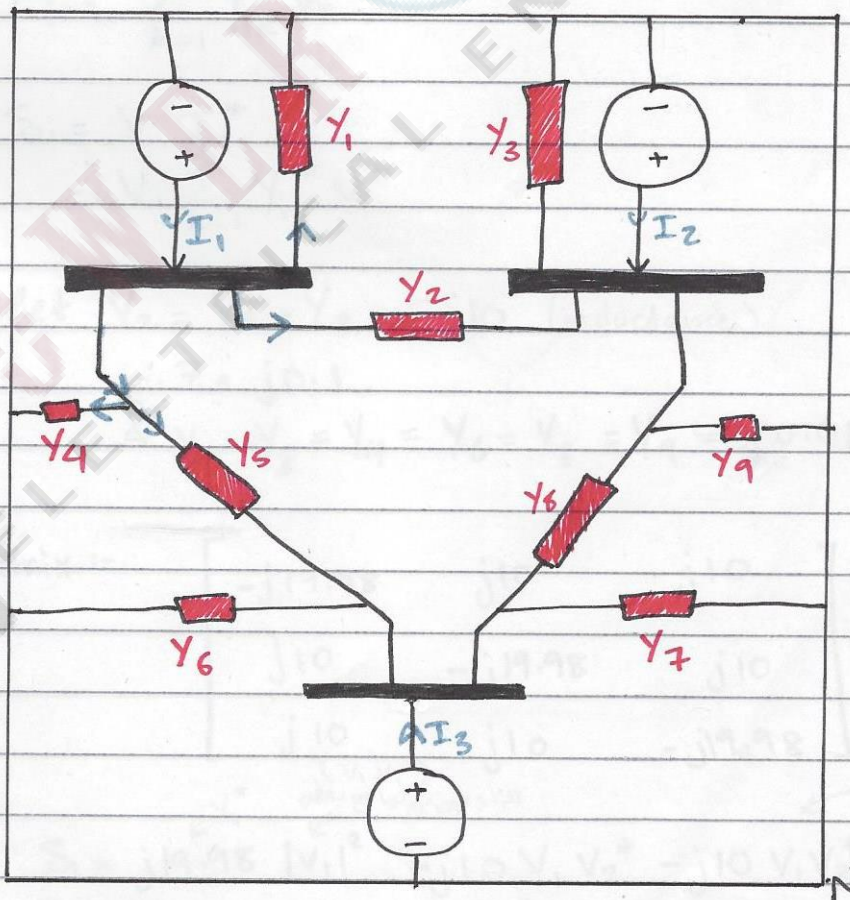و يستخدم (Load flow Program) في حساب I و V على كل من lines و buses في كل وقت أو في القيم التي يتغير (line).



"Line كس" Y_{series} و Y_{shunt} (PI network).

$$I_1 = Y_1 V_1 + Y_2 (V_1 - V_2) + Y_4 V_1 + Y_5 (V_1 - V_3)$$

$$= (Y_1 + Y_2 + Y_4 + Y_5) V_1 - Y_2 V_2 - Y_5 V_3$$

bus 1 ← مجموع التفرقة على bus 1 من 1, 2, 3 و 0

$$I_2 = -Y_2 V_1 + (Y_2 + Y_3 + Y_8 + Y_9) V_2 - Y_8 V_3$$

bus 2 ← مجموع التفرقة على bus 2

$$I_3 = -Y_5 V_1 - Y_8 V_2 + (Y_5 + Y_6 + Y_7 + Y_8) V_3$$

as matrices:-

Y-matrix

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} Y_1 + Y_2 + Y_4 + Y_5 & -Y_2 & -Y_5 \\ -Y_2 & Y_2 + Y_3 + Y_8 + Y_9 & -Y_8 \\ -Y_5 & -Y_8 & Y_5 + Y_6 + Y_7 + Y_8 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

($Y_{ij} = Y_{ji}$)

$$I_i = \sum_{k=1}^n Y_{ik} V_k$$

$$S_i = V_i I_i^*$$

$$= V_i \sum_{k=1}^n Y_{ik}^* V_k^*$$

ex:- let $Y_2 = Y_5 = Y_8 = -j10$ (inductance)

$$\therefore Z = j0.1$$

& $Y_1 = Y_3 = Y_4 = Y_6 = Y_7 = Y_9 = +j0.01$ (capacitance).

Y matrix :-

$$\begin{bmatrix} -j19.98 & j10 & j10 \\ j10 & -j19.98 & j10 \\ j10 & j10 & -j19.98 \end{bmatrix}$$

equations:-

$$S_1 = j19.98 |V_1|^2 - j10 V_1 V_2^* - j10 V_1 V_3^* \dots (1)$$



$$S_2 = -j10 V_2 V_1^* + j19.98 |V_2|^2 - j10 V_2 V_3^* \dots (2)$$

$$S_3 = -j10 V_3 V_1^* - j10 V_3 V_2^* + j19.98 |V_3|^2 \dots (3)$$

non-linear equations.

↳ solved using numerical methods (gauss, gauss seidel, newton-raphson...).

bus bar types:-

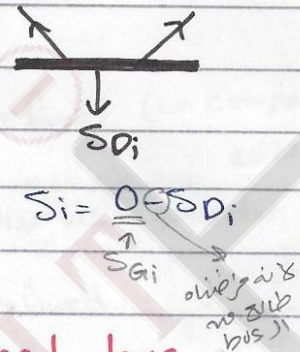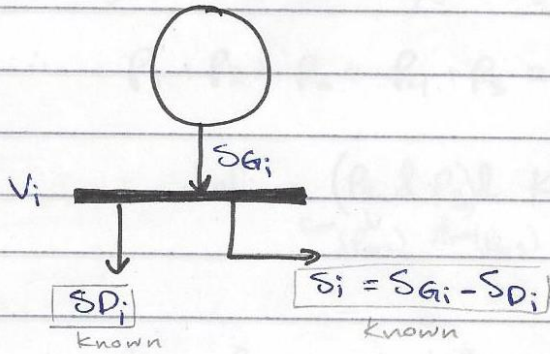

Generator bus.

Load bus.

Using steam value.

- in generator bus, we can control P_{Gi} (by controlling steam input to the generator) "بشوفنى الangle"
 - we can control $|V_i|$ by controlling I_f (field current).
- ∴ at generator bus we know:-


① $|V_i|$, ② $P_i = P_{Gi} - P_{Di}$

↑ loss S_{Gi} ← known

while $Q_i = Q_{Gi} - Q_{Di}$
I don't know this.

- @ load bus, we can't control V_i , but we know S_i

∴ ① $P_i = -P_{Di}$
② $Q_i = -Q_{Di}$

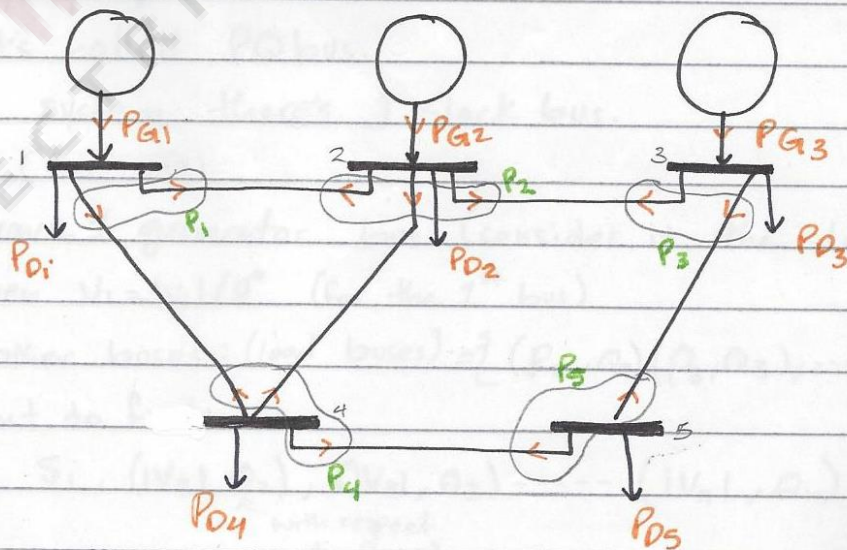

given $P_{D4} = 80 \text{ MW}$, $P_{D5} = 70 \text{ MW}$

∴ $P_4 = -80 \text{ MW}$, $P_5 = -70 \text{ MW}$

but $P_1 + P_2 + P_3 + P_4 + P_5 \neq 0$ (there are losses in T.L.s that must be considered).
 $70 \quad 30 \quad 50 \quad -70 \quad -80 \neq 0$

$\therefore P_1 + P_2 + P_3 + P_4 + P_5 = P_{Loss}$

\therefore define $(P_2 \& P_3)$ & keep (P_1) undefined (to compensate for Losses).
 from (P_{G2}) & from (P_{G3}) → عادةً جتار هاعنه انكبر $\approx (70 + \text{losses})$.
 generator \rightarrow عاده جتار هاعنه انكبر يعوضنا (losses)

$\therefore P_{G1}, P_1$ aren't defined, but $|V_1|$ is defined.

* let this bus be your reference

$V_1 = |V_1| \angle 0^\circ$

(P undefined)
 "سببنا صفر" امستاراس بي انكبر
 "امستاراس آخر (reference)"

• buses types (based on the info. given at the bus):

1. $V_i, (\theta_i = \angle V_i = 0^\circ)$, if it wasn't bus 1, rename your buses to make it 1.
 it's called "Slack bus" / "Swing bus" / "voltage reference bus".
 why swing? \rightarrow "ستاد اللى بيحفظنا" (لحفظنا losses) ~ Neutral confusion

2. $P_i, |V_i| \rightarrow$ generator bus

it's called $P, |V|$ bus / Voltage control bus.

3. $P_i, Q_i \rightarrow$ load bus

it's called PQ bus.

* in each system there's 1 slack bus.

Case 1:- (الأقل شيئا)

we have 1 generator bus (consider it the slack bus).

given \therefore given $V_1 = |V_1| \angle 0^\circ$ (for the 1st bus)

for other buses: (load buses) = $\{(P_2, Q_2), (P_3, Q_3), \dots, (P_n, Q_n)\}$

we want to find:-

$S_1, (|V_2|, \theta_2), (|V_3|, \theta_3) \dots (|V_n|, \theta_n)$
 with respect to $\theta_1 = 0^\circ$

Case 2 :- ($\hat{V}_1 \rightarrow \hat{S}^g$)

(m) generator buses

Load buses


given (Known) : $(V_1 / \angle 0^\circ)$, (V_2, P_2) , ... (V_m, P_m) , $(P_{m+1}, Q_{m+1}) \dots (P_n, Q_n)$

Slack bus.

* Chapter 6 Problems:-

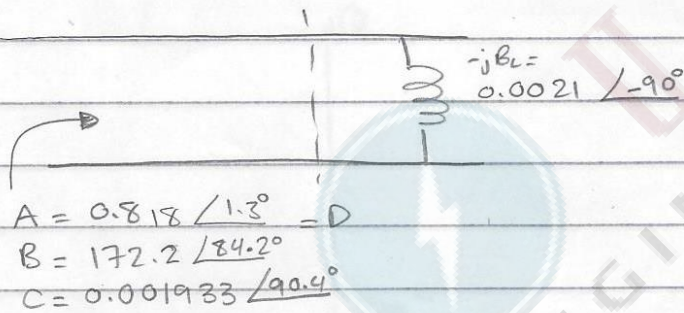6.25 250 MVAR
345 KV
shunt reactor.

$$Y = \frac{1}{j\omega L} = jB_L = 0.0021 / -90^\circ \text{ is added.}$$



$$A_{new} = A - jB_L B$$

$$= 0.818 / 1.3^\circ - j(0.0021)(172.2 / 84.2^\circ) = 1.178 / -0.88^\circ$$

$$C_{new} = C_{old} - jB_L D$$

D & B are the same.

$$S = \frac{V^2}{Z} = j\omega L$$


$$Z = \frac{V^2}{S}, \quad |Y| = \frac{|S|}{|V|^2} = \frac{250}{(345)^2} = 0.0021$$

6.24: $Y_c = 0 + j6.89 \times 10^{-6} \text{ S/mi}$

$$C.F = 0.6 = \frac{B_L}{B_c} \times 300 \text{ mi}$$

$$\therefore B_L = 0.001237 \text{ S}$$

calculate A, B, C, D ...

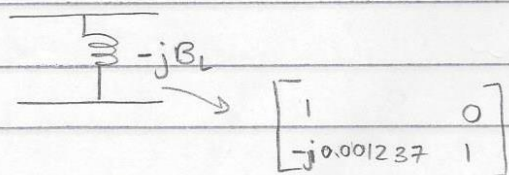

6.16:- 3-phase, long line

$$Z = 35 + j140 \Omega$$

$$Y = 930 \times 10^{-6} \angle 90^\circ \text{ S}$$

$$\delta l = \sqrt{YZ} l$$


$$= \sqrt{YZ} = 0.3663 \angle 83^\circ$$

$$A = \cosh(\delta l) = 0.9355 \angle 0.98^\circ$$

$$Z_c = \sqrt{\frac{Z}{Y}} = 394 \angle -7.02^\circ$$

$$B = Z_c \sinh(\delta l) = 141.428 \angle 76.28^\circ$$

$$C = \sinh(\delta l) / Z_c \dots$$

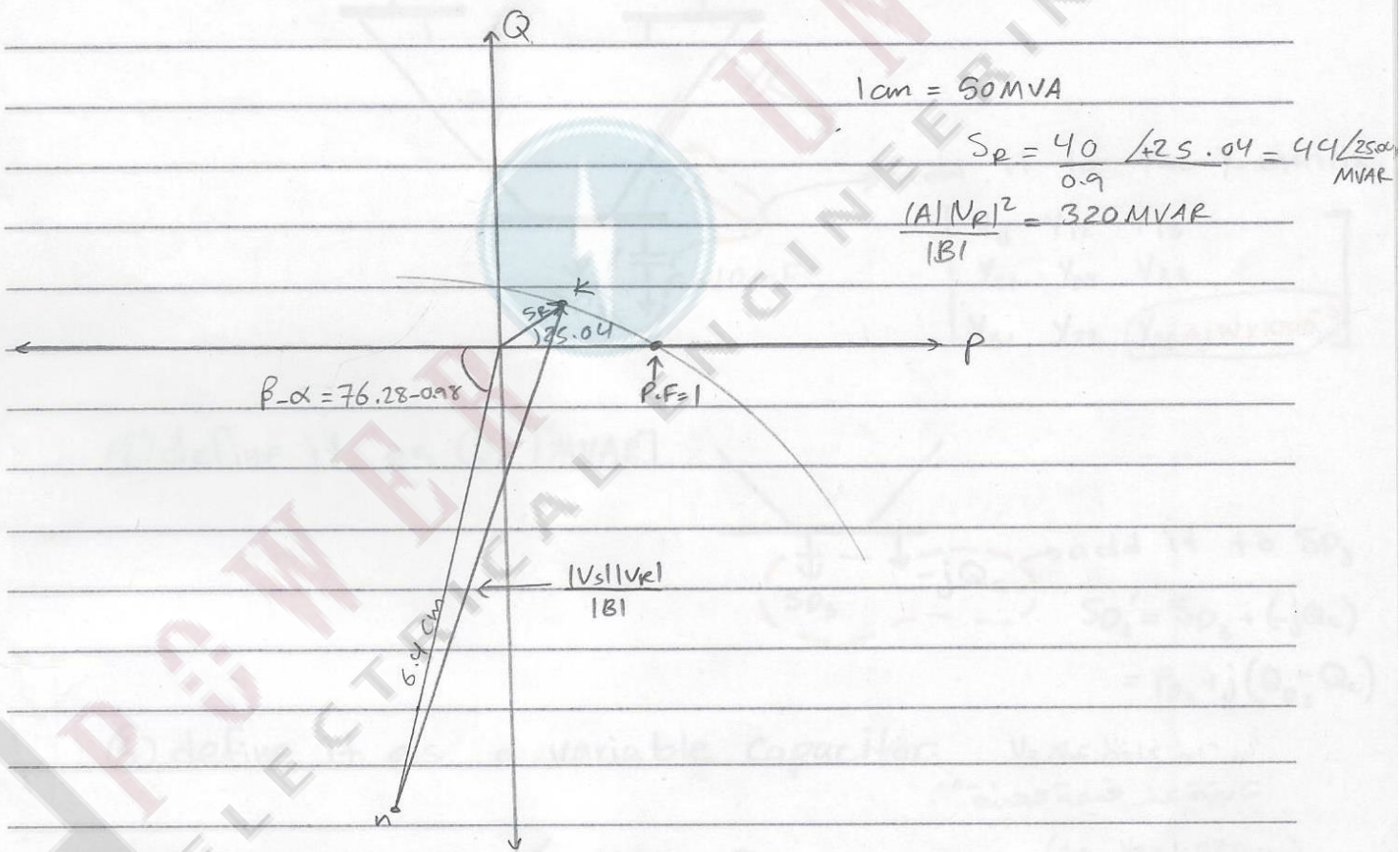

Lecture # 21

1/9/2014

from previous lec:-

Case 1:-

Known:- $V_1, S_2, S_3, \dots, S_n$


find:- $S_1, V_2, V_3, \dots, V_n$

Case 2:-

Known:- $V_1, \underbrace{(P_2, V_2), (P_3, V_3) \dots (P_m, V_m)}_{PV \text{ buses}}, \underbrace{S_{m+1}, S_{m+2} \dots S_n}_{PQ \text{ buses}}$

if I want to add a capacitor at a PQ bus (load bus):

① define it as (C)

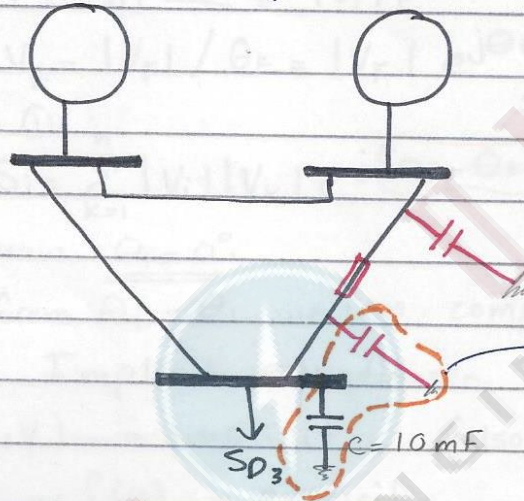


تعريفه كحامل شحنات
مختلفة في وقت
مختلف (C)

add it to the Y-matrix

$$\begin{bmatrix} Y_{11} & Y_{12} & Y_{13} \\ Y_{21} & Y_{22} & Y_{23} \\ Y_{31} & Y_{32} & Y_{33} + j\omega \times 10 \times 10^{-3} \end{bmatrix}$$

② define it as Q_c [MVAR]

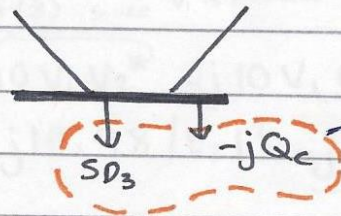


add it to SD_3

$$SD_3' = SD_3 + (-jQ_c)$$

$$= P_3 + j(Q_{D3} - Q_c)$$

③ define it as a variable capacitor:

"تعريفه كحامل شحنات
مختلفة في وقت مختلف"

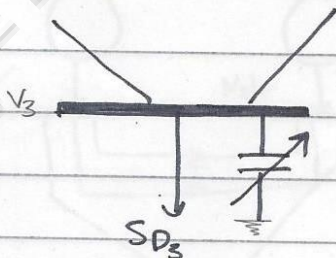

it's a PQ bus, but (eg $V_3 = 1.02 \text{ p.u.}$)
we'll define it as a PV bus
(after adding $\frac{1}{j}$). since $|V_3|$ is now
known. & Q_3 variable.

$$P_3 = P_{G3} - P_{D3} = 0 - P_{D3}$$

capacitor doesn't generate active power

***Notes:-**

* أنواع buses التي نركز عليهم (Load bus, gen. bus)
 واهم صفتهم Slack

* على كل bus في 2 معروفين (P, V, Q, θ)
 * واهم الزاوية يتم تعريفها بالمعادلة؟

$$S_i = V_i \sum_{k=1}^n Y_{ik}^* V_k^* \quad \dots (1)$$

$$V_i = |V_i| \angle \theta_i = |V_i| e^{j\theta_i}$$

$$\therefore V_k = |V_k| \angle \theta_k = |V_k| e^{j\theta_k}$$

Plug in (1)

$$S_i = \sum_{k=1}^n |V_i| |V_k| e^{j(\theta_i - \theta_k)} Y_{ik}^*$$

"angle difference" $\theta_i - \theta_k$

We know $\theta_1 = 0^\circ$

\therefore from $\theta_i - \theta_1$ we can compute θ_i

Explicit & Implicit equations:-

• $f(x, y) \rightarrow$ implicit (also $f(x^2)$ is implicit)

• $f(x)$ or $f(y) \rightarrow$ explicit.


for p. system equ.:

1 explicit $S_1 = j19.98 |V_1|^2 - j10 V_1 V_2^* - j10 V_1 V_3^* \leftarrow$ explicit.

implicit $S_2 = -j10 V_2 V_1^* + j19.98 |V_2|^2 - j10 V_2 V_3^* \leftarrow$ implicit

$f(x, y)$ 2 variables

• if the current is exceeded?

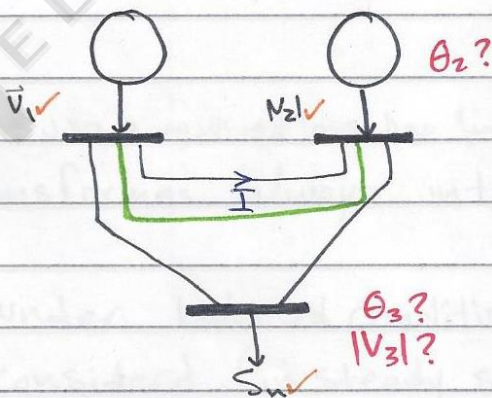

if we find $V_1, V_2 \dots V_n$, it's solved.

$$I = \frac{V_2 - V_1}{(T.L. imp.)} \quad \dots \quad I_n$$


this current must not exceed the thermal capability of the line.

Prob. 1 * if the current is exceeded suggested solution add parallel line.

Prob 2:- eg: $\theta_2 = 10, \theta_3 = 40!$

الفرد المفروض يكون $5-4^\circ$ to maintain stability.

- if Q_i isn't enough?

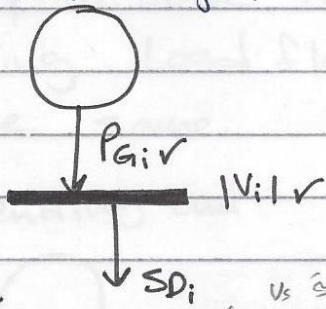

$Q_i?$
 $\theta_i?$

I might put a constraint to Q_i :

$$Q_i^{\min} \leq Q_i \leq Q_i^{\max}$$

eg $70 \leq Q_i \leq 70$ MVAR

$P_i = P_{Gi} - P_{Di}$ ✓

θ_i (power angle)

"بَدَل تَوَدِّي Q بَدَل تَرَفَع (Voltage) Q و V و P و θ عَرَبِيَّةً بَدَل"

if $Q_i = 50$ MVAR ✓

$Q_i = 30$ MVAR ✗ not within the range!

↳ solution:- $Q_i' = 40$ MVAR


the lower bound (أدنى قيمة مقبولة) 30 MVAR

P_i ✓ known & $Q_i = Q_i'$ ✓ known

& $|V_i|$ is no longer known

& this bus is considered as a PQ bus since $|V_i|$ it gives does not satisfy my constraints, thus $|V_i|$ is changed.

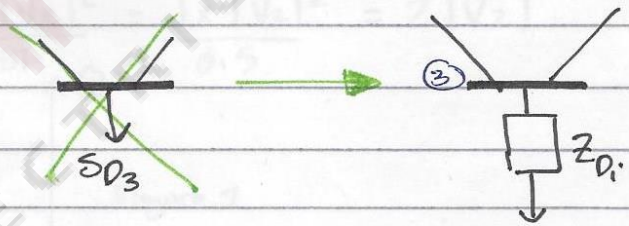- if the load was defined as an impedance instead of S_{Di} ?



Sol:- add it to the Y-matrix. ($\rightarrow Y_{ii}$)

$$\begin{bmatrix} \dots & \dots & \dots \\ \dots & \dots & \dots \\ \dots & \dots & -Y_{33} + \frac{1}{Z_{D3}} \end{bmatrix}$$

& $S_{D3}' = 0$


Y-matrix ← بلخصه bus لا يهبط، داخل كمنظومة loss على الالمانه من خلال تعديل ال Y-matrix well see it (ch#11). "vector groups." (0°, 30°, 180°, 60°, ...).

- Transformers always introduce a phase shift!

↳ under balanced conditions this phase shift isn't considered (in steady state solution). Shift في الجهد و ال V نفسه. فازاوية بعض ثابتة. "مع تنوعها أكثر كما نرغب على أنها ثابتة"

ex:- try to solve this using ch#6 method then using Load flow, & see that answers will be the same.

sending end

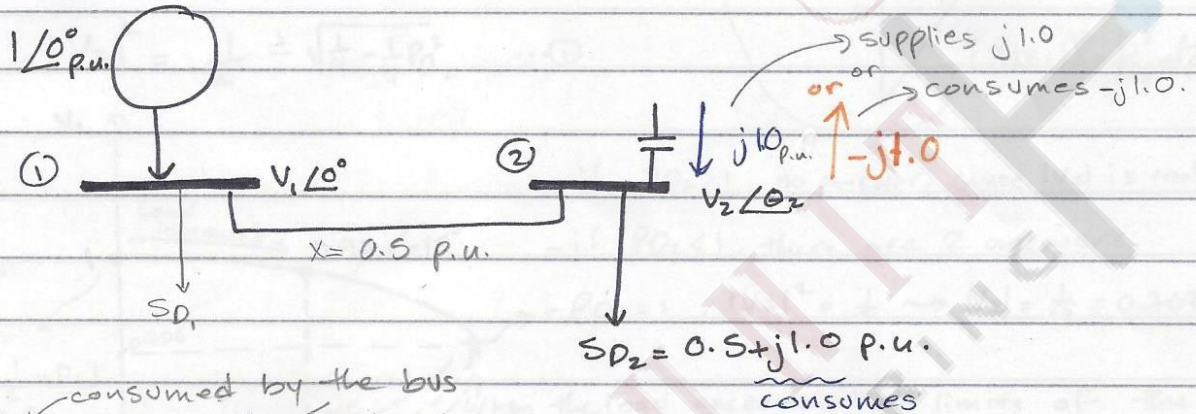

consumed by the bus

$$S_{D2} = 0.5 + j1.0 - j1.0$$

$$S_2 = -(0.5 + j0) = -0.5$$

supplied from the bus.

Lecture #21
3/4/2014

→ Chapter 6 method:- (I-L analysis & circle diagram)


$$S_R = P_{D2} + j1.0 - j1.0 = P_{D2} = 0.5$$

for the line:- (short line; since $\gamma=0$)

$$A = 1 \angle 0^\circ$$

$$B = 0.5 \angle 90^\circ \Omega$$

$$\frac{|A||V_R|^2}{|B|} = \frac{|x||V_2|^2}{0.5} = 2|V_2|^2$$

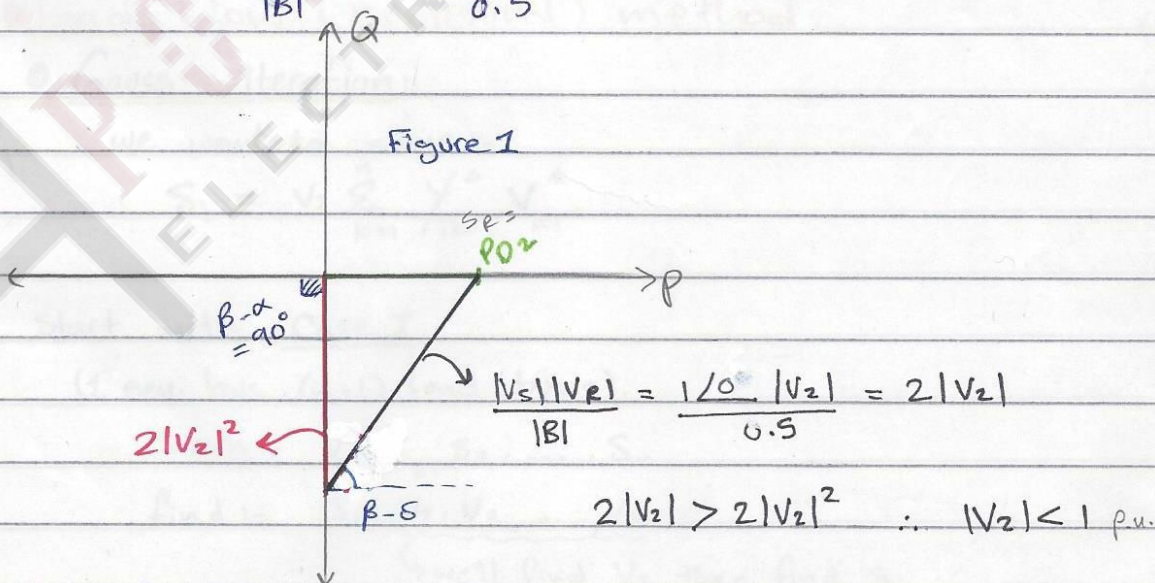


ex (cont.)

$$|V_2|^4 - |V_2|^2 + \frac{1}{4} P_{D2}^2 = 0$$

$$|V_2|^2 = \frac{-(-1) \pm \sqrt{1 - P_{D2}^2}}{2}$$


$$|V_2|^2 = \frac{1}{2} \pm \sqrt{\frac{1}{4} - \frac{1}{4} P_{D2}^2} \quad \dots \textcircled{1}$$

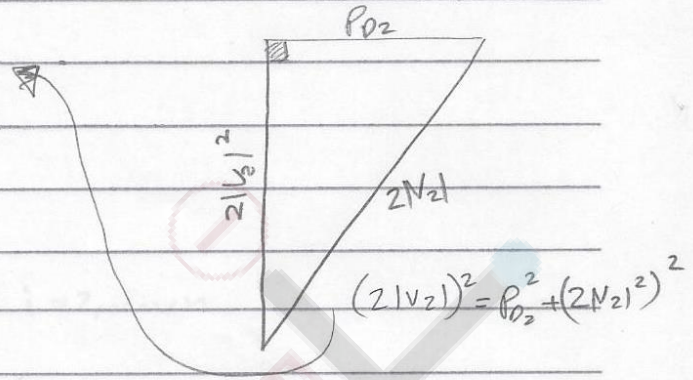

- if $P_{D2} > 1$, no answer, since $|V_2|$ is real (not imag)
 - if $P_{D2} < 1$, there are 2 answers.

@ no-load:

$P_{D2} = 0$
 $|V_2|^2 = \frac{1}{2} + \frac{1}{2} = 1$

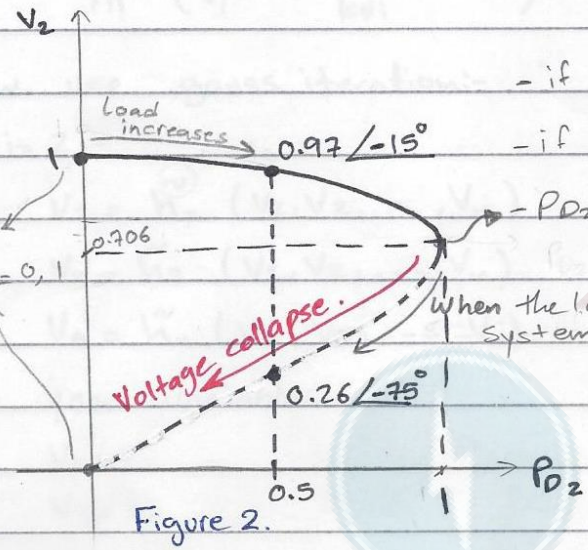

- $P_{D2} = 1$, $|V_2|^2 = \frac{1}{2} \rightarrow |V_2| = \frac{1}{\sqrt{2}} = 0.707$

When the load exceeds the limits of the gen. system collapses.

"Voltage Stability Problem".

• we find $|V_2|$ from equation $\textcircled{1}$ (Figure 2), & $\angle V_2$ from (Figure 1)

* $\angle V_2 = -\delta \rightarrow$ since V_s was my reference = $\angle 0^\circ$

• at $P_{D2} = 0.5$ there are two solutions, $0.97 \angle -15^\circ$ / $0.26 \angle -75^\circ$

this is not Acceptable (this voltage is too weak to drive the load)

→ Load flow (numerical) method:

• Gauss iteration:

we want to solve:-

$$S_i = V_i \sum_{k=1}^n \frac{1}{Y_{ik}} V_k^*$$

Start with Case I:

(1 gen. bus, (n-1) load buses).

Known:- $V_1, S_2, S_3, \dots, S_n$

find:- $S_1, V_2, V_3, \dots, V_n$

↳ we'll find V_s then find S_1 .

∴ iteration from $i=2$ to n .

$$S_i^* = V_i^* \sum_{k=1}^n Y_{ik} V_k$$

$$\frac{S_i^*}{V_i^*} = \underbrace{Y_{ii}}_{\substack{\text{no } k \text{ value} \\ k=i}} V_i + \sum_{\substack{k=1 \\ k \neq i}}^n Y_{ik} V_k$$

$$V_i = \frac{1}{Y_{ii}} \left(\frac{S_i^*}{V_i^*} - \sum_{\substack{k=1 \\ k \neq i}}^n Y_{ik} V_k \right), \quad i=2, \dots, n$$

now, use gauss iteration:-

$i=2$:-

$$V_2 = h_2^{\sim} (V_2, V_3, \dots, V_n)$$

$$V_3 = h_3^{\sim} (V_2, V_3, \dots, V_n)$$

$$V_n = h_n^{\sim} (V_2, V_3, \dots, V_n)$$

rename your variables:-

$$V_2 = X_1$$

$$V_3 = X_2$$

$$V_n = V_{n-1} = X_N, \quad N=n-1$$

now,

$$X_1^{v+1} = h_1 (X_1^v, X_2^v, \dots, X_N^v)$$

$$X_2^{v+1} = h_2 (X_1^v, X_2^v, \dots, X_N^v)$$

$$X_N^{v+1} = h_N (X_1^v, X_2^v, \dots, X_N^v)$$

in general,

$$X^{v+1} = h(X)$$

1st step, we use V_2^v, V_3^v, \dots "كلهم قريبان على 1 لا نأبشغل P.m."

* we stop the iteration when

$$X^{v+1} - X^v \leq \epsilon \quad (\text{for both phase \& magnitude})$$

* In gauss iteration we complete the whole iteration based on the same initial values.

↳ we use X^v to calculate X^{v+1} for all $i \in [2, n]$ $\uparrow X_1 \rightarrow X_N$

then we use X^{v+1} to calculate X^{v+2}, \dots and so on.

* In gauss seidel we update the values of X step by step:-

G.S:-

$$X_1^{v+1} = h_1 (X_1^v, X_2^v, \dots, X_N^v) \dots \textcircled{1}$$

$$X_2^{v+1} = h_2 (X_1^{v+1}, X_2^v, \dots, X_N^v)$$

↳ calculated from 1.

$$X_3^{v+1} = h_3 (X_1^{v+1}, X_2^{v+1}, \dots, X_N^v)$$

⋮

$$X_N = h_N (X_1^{v+1}, X_2^{v+1}, X_3^{v+1}, \dots, X_N^v)$$

for our example both methods are the same because I have 1 variable only. (V_2)

↳ given:- $S_2 = -S_{D2} = -0.5$

$$V_1 = 1/0^\circ$$

Find:- S_1, V_2 ?

↳ low no

$$V_2^{v+1} = \frac{1}{Y_{22}} \left(\frac{S_2^*}{V_2^{v*}} - \sum_{\substack{k=1 \\ k \neq 2}}^n Y_{ik} V_k^v \right) \dots \textcircled{1}$$

Y-matrix (2x2)

$$\frac{1}{j0.5} \begin{bmatrix} -j2 & j2 \\ j2 & -j2 \end{bmatrix}$$

back to ①

$$V_2^{v+1} = \frac{1}{-j2} \left(\frac{-0.5}{(V_2^v)^*} - (j2 \times 1) \right)$$

$$V_2^{v+1} = \frac{-j0.25}{(V_2^v)^*} + 1$$

start من نقطة
 $V_2 = V_1 = 1 \angle 0^\circ$ مع فرض
 كانه نقطة اكل

Iteration	V_2	V_2 (another guess) using
0	$1 \angle 0^\circ$ ← initial guess	$0.1 \angle 0^\circ$
1	$1.030776 / -14.03624^\circ$	$1.092582 / -68.7$
2	$0.970143 / -14.036$	⋮
⋮	⋮	⋮
6	$0.965948 / -14.990572^\circ$	iteration #8: $-0.965918 / -14.995^\circ$

بجواب لنفس اكل بي بعد iter. 8
 لا انا ل guess بعد

"unstable point" 0.26

6/4/2014
 lecture #23

Case II

gen. buses load buses

Known:- V_1 , $(V_2, P_2), \dots, (V_m, P_m), (S_{m+1}), \dots, (S_n)$

Find:- $S_1, (Q_2, \theta_2), \dots, (Q_m, \theta_m), V_{m+1}, \dots, V_n$


? Q_i : unknown.

$$V_i^{v+1} = \frac{1}{Y_{ii}} \left(\frac{S_i^*}{V_i^*} - \sum_{\substack{k=1 \\ k \neq i}}^n Y_{ik} V_k \right) \quad \text{--- (1)}$$

but for PV buses we don't know Q_i !

$$Q_i^v = I_m \{ S_i^v \} = I_m \{ V_i^v \sum_{k=1}^n Y_{ik}^* V_k^* \} \quad \text{--- (2)}$$

ex:

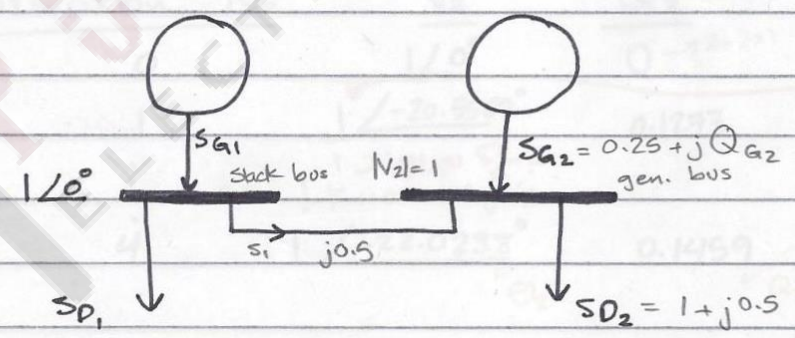

$$S_2 = S_{G2} - S_{D2} = -0.75 + j(Q_{G2} - 0.5)$$

given $V_1, (P_2, V_2)$

find $S_1, (Q_2, \theta_2)$

2nd step 1st step

$$V_2^{v+1} = \frac{1}{Y_{22}} \left(\frac{S_i^*}{V_2^{v*}} - \sum_{\substack{k=1 \\ k \neq 2}}^n Y_{2k} V_k \right) \dots \textcircled{1}$$

$$Y\text{-matrix} = \begin{bmatrix} -j2 & j2 \\ j2 & -j2 \end{bmatrix}$$

$$V_2^{v+1} = \frac{1}{-j2} \left(\frac{-0.75 - jQ_2^v}{V_2^{v*}} - j2 \times 1 \right)$$

$$V_2^{v+1} = 1 + \frac{-0.75 - jQ_2^v}{V_2^{v*}} \textcircled{1}$$

$$Q_2^v = \text{Im} \left\{ V_2^v \sum_{k=1}^n Y_{2k}^* V_k^* \right\}$$

$$= \text{Im} \left\{ V_2^v (-j2 \times V_1^* + j2 V_2^{v*}) \right\}$$

$$= \text{Im} \left\{ -j2 V_2^v + j2 \times 1 \right\} = \text{Im} \left\{ j(2 - 2V_2^v) \right\}$$

$$Q_2^v = 2 - 2 \text{Re} \{ V_2^v \} \textcircled{2}$$

هو الذي يدخل في Im في المعادلة (2)

We start with initial guess for V_2 , $V_2 = 1 \angle 0^\circ = V_1$ (flat start).

iteration No	V_2	Q_2	V_2^{v+1}
0	$1 \angle 0^\circ$	0 $\rightarrow 2 - 2 \times 1$	$1.068 \angle -20.5560^\circ$
1	$1 \angle -20.5560^\circ$	0.1273	$1.003 \angle -21.9229^\circ$
⋮			
4	$1 \angle -22.0238^\circ$	0.1459	

2nd Step:- S_i ?


$$S_i = V_1 \sum_{k=1}^n Y_{1k}^* V_k^* = 1 \angle 0^\circ (j2 \times 1 \angle 0^\circ + -j2 \times 1 \angle +22.0238^\circ)$$

$$S_i = 0.75 + j0.1459$$

"بسيط الـ S_i ونفعلها كالتالي"

* 0.75 is supplied by G_1 & consumed by G_2 since no (R) through line. (2) both G_1, G_2 supplies the same amount of reactive power since they have the same $|V|$.

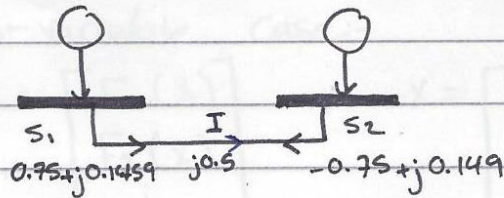لأنه الذي يقدر منه بقدر Q هو V والي يقدر منه P هو الزاوية $\angle V$ (leading source) supplies P



$$I = \frac{1 \angle 0^\circ}{j0.5} - \frac{1 \angle -22.0238^\circ}{j0.5} = 0.764 \angle -11.011^\circ$$

$$I^2 = (0.764)^2 + 0.5 = 0.292 = \frac{2 \times 0.1459}{Q_1 + Q_2}$$

Newton-Raphson Method N-R


(better; faster convergent more stable).

let $F(x) = 0$

then solve for x

$$F'(x_0) = \frac{F(x_0)}{\Delta x}$$
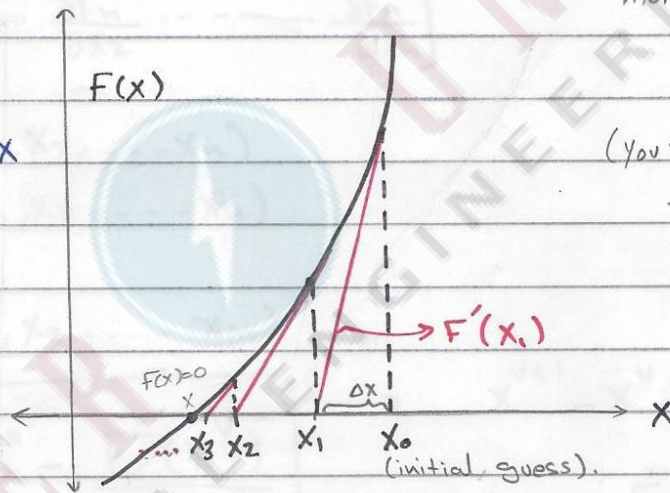
$$\Rightarrow \Delta x = x_0 - x_1 = \frac{F(x_0)}{F'(x_0)}$$



(you're linearizing the problem).

$$x_1 = x_0 - \frac{F(x_0)}{F'(x_0)}$$

in general:-

$$x^{v+1} = x^v - \frac{F(x^v)}{F'(x^v)}$$

Simple example:- find $\sqrt[3]{64}$?

$$x = \sqrt[3]{64}$$

$$x^3 = 64 \rightarrow x^3 - 64 = 0$$

start with initial guess $x_0 = 5$

$$x_1 = 5 - \frac{125 - 64}{3 \times 25} = 4.1867$$

$$x_2 = 4.1867 - \frac{(4.1867)^3 - 64}{3(4.1867)^2} = 4.0082 \approx 4 \text{ from 2 iterations only!}$$

For multi-variable case:-

$$F(x) = \begin{bmatrix} F_1(x) \\ F_2(x) \\ \vdots \\ F_n(x) \end{bmatrix}, \quad x = \begin{bmatrix} x_1 \\ x_2 \\ \vdots \\ x_n \end{bmatrix}$$

$$F'(x) = \begin{bmatrix} \frac{\partial F_1}{\partial x_1} & \frac{\partial F_1}{\partial x_2} & \dots & \frac{\partial F_1}{\partial x_n} \\ \frac{\partial F_2}{\partial x_1} & \frac{\partial F_2}{\partial x_2} & \dots & \frac{\partial F_2}{\partial x_n} \\ \vdots & \vdots & \ddots & \vdots \\ \frac{\partial F_n}{\partial x_1} & \frac{\partial F_n}{\partial x_2} & \dots & \frac{\partial F_n}{\partial x_n} \end{bmatrix} \equiv \text{jacobian } J(x)$$

$$F_1(x) = F_1(x_1, x_2, \dots, x_n)$$

$$F_2(x) = F_2(x_1, x_2, \dots, x_n)$$

⋮

$$F_n(x) = F_n(x_1, x_2, \dots, x_n)$$

$$x^{v+1} = x^v - \frac{F(x^v)}{J(x^v)}$$


$$\rightarrow x^{v+1} - x^v = \Delta x^v = \frac{-F(x^v)}{J(x^v)}$$

$$= -[J(x^v)]^{-1} F(x^v)$$

it might cause problems for very large J matrix

ex:- DC load flow

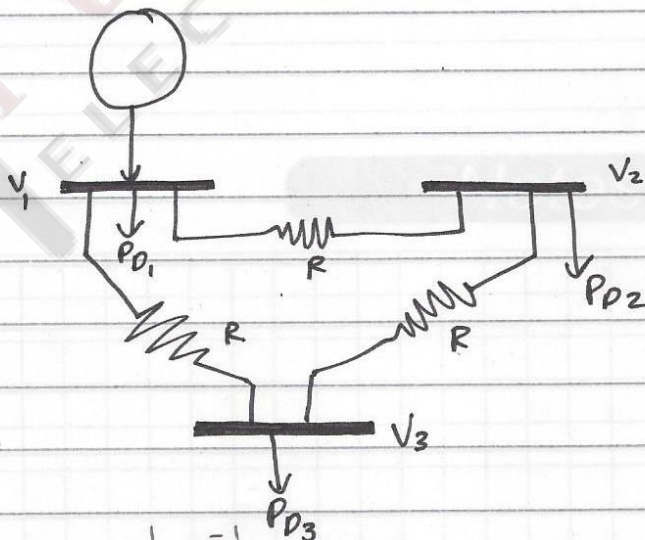نقل الطاقة من المصدر إلى الأحمال
" 0 = Qs "



$$R = 0.01 \text{ p.u.}$$

$$V_1 = 1.0 \text{ V}$$

$$V_2, V_3 ?$$

$$P_{02} = 1 \text{ p.u.}$$

$$P_{03} = 0.5 \text{ p.u.}$$

$$P_{01} = 0.5 \text{ p.u.}$$

$$\therefore P_2 = -1.0 \text{ p.u.}$$

$$P_3 = -0.5 \text{ p.u.}$$

known: V_1, P_2, P_3

find: S_1, V_2, V_3

y-matrix:
$$\begin{bmatrix} 200 & -100 & -100 \\ -100 & 200 & -100 \\ -100 & -100 & 200 \end{bmatrix}$$

$F(x) = ?$

$$S_i = V_i \sum_{k=1}^n Y_{ik}^* V_k^*$$

For D.C:

$$P_i = V_i \sum_{k=1}^n Y_{ik} V_k$$

$$P_1 = 200 V_1^2 - 100 V_1 V_2 - 100 V_1 V_3 \dots (1)$$

$$F_1(x) \rightarrow P_2 = -100 V_2 V_1 + 200 V_2^2 - 100 V_2 V_3 \dots (2)$$

$$F_2(x) \rightarrow P_3 = -100 V_3 V_1 - 100 V_2 V_3 + 200 V_3^2 \dots (3)$$

$$X = \begin{bmatrix} V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

استعملنا P_1 (D.C.)
 في بقية المعادلات
 التي بالأسفل

8/4/2014
 Lecture #24

$$X^{v+1} = X^v - [J(X^v)]^{-1} F(X^v) \dots$$

$$X^1 = X^0 - [J(X^0)]^{-1} F(X^0)$$

 guess \Rightarrow flat start $[1]$

$$\begin{bmatrix} V_2^1 \\ V_3^1 \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \end{bmatrix} - [J(X^0)]^{-1} F(X^0) \dots (A)$$

 we have to find $F(X^0)$ then calculate the jacobian.

from (2) & (3)

$$P_2(x) = -100 V_1 V_2 + 200 V_2^2 - 100 V_2 V_3 = -1$$

$$\hookrightarrow F_1(x) = -100 V_1 V_2 + 200 V_2^2 - 100 V_2 V_3 + 1 = 0$$

$$P_3(x) = -100 V_1 V_3 - 100 V_2 V_3 + 200 V_3^2 = -0.5$$

$$\hookrightarrow F_2(x) = -100 V_1 V_3 - 100 V_2 V_3 + 200 V_3^2 + 0.5 = 0$$

8/4/2014

$$J(x) \rightarrow \begin{bmatrix} \left(-100V_1 + 400V_2 - 100V_3 \right) & \left(\frac{\partial F_1}{\partial V_3} \right) \\ \left(-100V_3 \right) & \left(\frac{\partial F_1}{\partial V_2} \right) \\ \left(-100V_1 - 100V_2 + 400V_3 \right) & \left(\frac{\partial F_2}{\partial V_3} \right) \\ & \left(\frac{\partial F_2}{\partial V_2} \right) \end{bmatrix}$$

plug $x = \begin{bmatrix} 1 \\ 1 \end{bmatrix} \rightarrow \begin{matrix} V_2 \\ V_3 \end{matrix}$, given $V_1 = 1$

$$J(x^0) = \begin{bmatrix} 200 & -100 \\ -100 & 200 \end{bmatrix}$$

iteration 0:-

Plug in (A)

$$\begin{bmatrix} V_2^1 \\ V_3^1 \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \end{bmatrix} - \begin{bmatrix} 200 & -100 \\ -100 & 200 \end{bmatrix}^{-1} \begin{bmatrix} 1 \\ 0.5 \end{bmatrix}$$

$$= \begin{bmatrix} 0.991667 \\ 0.993333 \end{bmatrix}$$

iteration 1:- x^{n+1}

$$\begin{bmatrix} V_2^2 \\ V_3^2 \end{bmatrix} = \begin{bmatrix} 0.991667 \\ 0.993333 \end{bmatrix} - \begin{bmatrix} 197.333 & -99.1667 \\ -99.333 & 198.1667 \end{bmatrix}^{-1} \begin{bmatrix} 0.00843 \\ 0.00322 \end{bmatrix}$$

$$= \begin{bmatrix} 0.991599 \\ 0.993283 \end{bmatrix}$$

mismatch

this term is approaching zero

thus the difference between x^{n+1} & x^n is approaching zero.

now, not only D.C.

for actual R system:

$$S_i = V_i \sum_{k=1}^n Y_{ik}^* V_k^* \quad i=2, \dots, n$$

, solve for V_2, V_3, \dots, V_n then find S_i .

$$V_i = |V_i| e^{j\theta_i}$$

$$V_k = |V_k| e^{j\theta_k}$$

$$Y_{ik} = (g_{ik} + jb_{ik})$$

conductance

susceptance.

$$S_i = \sum_{k=1}^n |V_i| e^{j\theta_i} |V_k| e^{-j\theta_k} Y_{ik}^*$$

$$= \sum_{k=1}^n |V_i| |V_k| e^{j(\theta_i - \theta_k)} Y_{ik}^*$$

$$S_i = \sum_{k=1}^n |V_i| |V_k| [\cos(\theta_i - \theta_k) + j \sin(\theta_i - \theta_k)] (g_{ik} - j b_{ik})$$

also, $S_i = P_i + jQ_i$

$$\therefore P_i = \sum_{k=1}^n |V_i| |V_k| [g_{ik} \cos(\theta_i - \theta_k) + b_{ik} \sin(\theta_i - \theta_k)] \quad \text{--- (1)}$$

$$Q_i = \sum_{k=1}^n |V_i| |V_k| [g_{ik} \sin(\theta_i - \theta_k) - b_{ik} \cos(\theta_i - \theta_k)] \quad \text{--- (2)}$$

our variables:-

$$X = \begin{bmatrix} \theta_2 \\ \theta_3 \\ \vdots \\ \theta_n \\ \hline |V_2| \\ |V_3| \\ \vdots \\ |V_n| \end{bmatrix} \equiv \begin{bmatrix} \theta \\ \hline |V| \end{bmatrix}$$

ترتيبهم ما يقتر كل بيوتنا
هنا الترتيب لأننا نريد افتر
عن علامه أن يسطر اكل نظام

What about $F(x)$?

P_i, Q_i given. From (1) & (2):-

$$F_1(x) = P_2(x) - P_1 = 0$$

$$F_2(x) = Q_2(x) - Q_1 = 0$$

$$\therefore F(x) = \begin{bmatrix} P_2(x) - P_2 \\ P_3(x) - P_3 \\ \vdots \\ P_n(x) - P_n \\ \hline Q_2(x) - Q_2 \\ \vdots \\ Q_n(x) - Q_n \end{bmatrix}$$

دالة P مرتبة θ_2 و
دالة Q مرتبة θ_2 و $|V|$

We won't write it for simplicity

$$J(x) =$$


$\frac{\partial P_2(x)}{\partial \theta_2}$	$\frac{\partial P_2}{\partial \theta_3}$...	$\frac{\partial P_2}{\partial \theta_n}$	$\frac{\partial P_2}{\partial v_2 }$	$\frac{\partial P_2}{\partial v_3 }$...	$\frac{\partial P_2}{\partial v_n }$
$\frac{\partial P_3}{\partial \theta_2}$	$\frac{\partial P_3}{\partial \theta_3}$...	$\frac{\partial P_3}{\partial \theta_n}$	$\frac{\partial P_3}{\partial v_2 }$	$\frac{\partial P_3}{\partial v_3 }$...	$\frac{\partial P_3}{\partial v_n }$
\vdots	\vdots		\vdots	\vdots	\vdots		\vdots
$\frac{\partial P_n}{\partial \theta_2}$	$\frac{\partial P_n}{\partial \theta_3}$...	$\frac{\partial P_n}{\partial \theta_n}$	$\frac{\partial P_n}{\partial v_2 }$	$\frac{\partial P_n}{\partial v_3 }$...	$\frac{\partial P_n}{\partial v_n }$
$\frac{\partial Q_2}{\partial \theta_2}$	$\frac{\partial Q_2}{\partial \theta_3}$...	$\frac{\partial Q_2}{\partial \theta_n}$	$\frac{\partial Q_2}{\partial v_2 }$	$\frac{\partial Q_2}{\partial v_3 }$...	$\frac{\partial Q_2}{\partial v_n }$
$\frac{\partial Q_3}{\partial \theta_2}$	$\frac{\partial Q_3}{\partial \theta_3}$...	$\frac{\partial Q_3}{\partial \theta_n}$	$\frac{\partial Q_3}{\partial v_2 }$	$\frac{\partial Q_3}{\partial v_3 }$...	$\frac{\partial Q_3}{\partial v_n }$
\vdots	\vdots		\vdots	\vdots	\vdots		\vdots
$\frac{\partial Q_n}{\partial \theta_2}$	$\frac{\partial Q_n}{\partial \theta_3}$...	$\frac{\partial Q_n}{\partial \theta_n}$	$\frac{\partial Q_n}{\partial v_2 }$	$\frac{\partial Q_n}{\partial v_3 }$...	$\frac{\partial Q_n}{\partial v_n }$

J_{11}

J_{12}

J_{21}

J_{22}

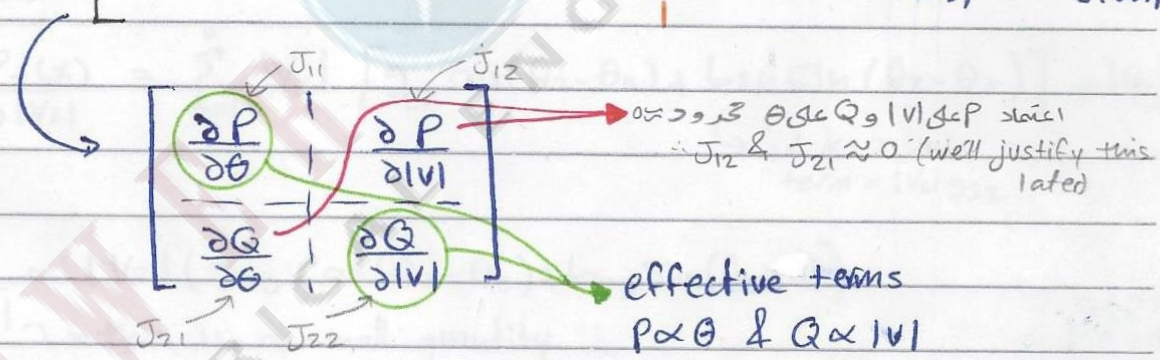


$$X^{V+1} - X^V = \Delta X^V = -j(X^V)^{-1} F(X)$$

$$P_2(x) = \sum_{k=1}^n |V_2| |V_k| \left[g_{2k} \cos(\theta_2 - \theta_k) + b_{2k} \sin(\theta_2 - \theta_k) \right]$$

$$\frac{\partial P_2}{\partial \theta_2} = \sum_{\substack{k=1 \\ k \neq 2}}^n |V_2| |V_k| \left[g_{2k} (-\sin(\theta_2 - \theta_k)) + b_{2k} \cos(\theta_2 - \theta_k) \right] \dots \textcircled{1}$$

* الفرق بين الزوايا صغير \Rightarrow إذا $\theta_{ik} \approx 24^\circ$ $\sin(\theta_{ik}) \approx \theta_{ik}$ و $\cos(\theta_{ik}) \approx 1$ و g (المقاومة) \gg b (السعة) \Rightarrow وبإسقاط $\frac{\partial P}{\partial \theta}$ كبيرة (أيها حجم). *

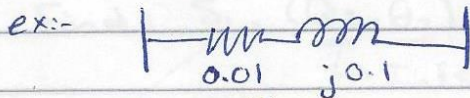**** Note:** in power systems usually $b > g$



$$y = \left[\frac{1}{0.01 + j0.1} \right] \times \frac{0.01 - j0.1}{0.01 - j0.1} = \frac{1 - j10}{g < b}$$

θ_3 only shows up at $k=3$.

$$\frac{\partial P_2(x)}{\partial \theta_3} = |V_2| |V_3| \left[g_{23} \sin(\theta_2 - \theta_3) - b_{23} \cos(\theta_2 - \theta_3) \right]$$

$$\frac{\partial P_2(x)}{\partial |V_2|} = \sum_{k=1}^n |V_k| \left[g_{2k} \cos(\theta_2 - \theta_k) + b_{2k} \sin(\theta_2 - \theta_k) \right] + |V_2| g_{22}$$

\hookrightarrow at $k=2$ this term = $|V_2| g_{22}$

10/4/2014

$$\frac{\partial P_2}{\partial |V_3|} \rightarrow \text{this is a small quantity}$$

"بتقدير مع مجهولنا: تقدير $|V_1|$ \times تقدير θ_1 على P_1 "

$$\begin{aligned} & \uparrow \\ & 2|V_2| g_{22} \\ & \text{Since at } k=2 \\ & \text{it } \frac{\partial (|V_2|^2 g_{22})}{\partial |V_2|} \end{aligned}$$

$$Q_2(x) = \sum_{k=1}^n |V_2| |V_k| \left(g_{2k} \sin(\theta_2 - \theta_k) - b_{2k} \cos(\theta_2 - \theta_k) \right)$$

$$\frac{\partial Q_2}{\partial \theta_2} = \sum_{\substack{k=1 \\ k \neq 2}}^n |V_2| |V_k| \left[g_{2k} \cos(\theta_2 - \theta_k) + b_{2k} \sin(\theta_2 - \theta_k) \right]$$

$$\frac{\partial Q_2}{\partial \theta_3} = |V_2| |V_3| \left[-g_{23} \cos(\theta_2 - \theta_3) - b_{23} \sin(\theta_2 - \theta_3) \right]$$

$$\frac{\partial Q_2}{\partial |V_2|} = \sum_{k=1}^n \left(g_{2k} \sin(\theta_2 - \theta_k) - b_{2k} \cos(\theta_2 - \theta_k) \right) - b_{22} |V_2|$$

to adjust the value of the sum at $k=2$.

$$\frac{\partial Q_2}{\partial |V_3|} = |V_2| \left(g_{23} \sin(\theta_2 - \theta_3) - b_{23} \cos(\theta_2 - \theta_3) \right)$$

$$x^{u+1} = x^u - \frac{F(x^u)}{J(x^u)}$$

$$-F(x^u) = (x^{u+1} - x^u) J(x^u) \\ = \Delta(x^u) J(x^u)$$

Case I:-

given: $V_1, (P_2, |V_2|), \dots, (P_m, |V_m|), S_{m+1}, \dots, S_n$

Find: $S_1, (Q_2, \theta_2), \dots, (Q_m, \theta_m), |V_{m+1}|, \dots, |V_n|$

\rightarrow $\sum_{k=1}^n V_k^* Y_{ik}^*$
 $S_i = V_i \sum_{k=1}^n V_k^* Y_{ik}^*$

" V_1 و Q_2 و θ_2 جيب ال V_1 وال Q_2 "

We'll derive the matrices for case II from those of case I.

$$J(x^u) (\Delta x^u) = -F(x^u)$$

$\frac{\partial P_2}{\partial \theta_2}$	$\frac{\partial P_2}{\partial \theta_3}$	\dots	$\frac{\partial P_2}{\partial \theta_n}$	$\frac{\partial P_2}{\partial V_2 }$	$\frac{\partial P_2}{\partial V_3 }$	\dots	$\frac{\partial P_2}{\partial V_n }$	$\theta_2^{u+1} - \theta_2^u$	$P_2(x) - P_2$
$\frac{\partial P_3}{\partial \theta_2}$	$\frac{\partial P_3}{\partial \theta_3}$	\dots	$\frac{\partial P_3}{\partial \theta_n}$	$\frac{\partial P_3}{\partial V_2 }$	$\frac{\partial P_3}{\partial V_3 }$	\dots	$\frac{\partial P_3}{\partial V_n }$	$\theta_3^{u+1} - \theta_3^u$	$P_3(x) - P_3$
\vdots	\vdots	\vdots	\vdots	\vdots	\vdots	\vdots	\vdots	\vdots	\vdots
$\frac{\partial P_n}{\partial \theta_2}$	$\frac{\partial P_n}{\partial \theta_3}$	\dots	$\frac{\partial P_n}{\partial \theta_n}$	$\frac{\partial P_n}{\partial V_2 }$	$\frac{\partial P_n}{\partial V_3 }$	\dots	$\frac{\partial P_n}{\partial V_n }$	$\theta_n^{u+1} - \theta_n^u$	$P_n(x) - P_n$
$\frac{\partial Q_2}{\partial \theta_2}$	$\frac{\partial Q_2}{\partial \theta_3}$	\dots	$\frac{\partial Q_2}{\partial \theta_n}$	$\frac{\partial Q_2}{\partial V_2 }$	$\frac{\partial Q_2}{\partial V_3 }$	\dots	$\frac{\partial Q_2}{\partial V_n }$	$V_2 ^{u+1} - V_2 ^u$	$Q_2(x) - Q_2$
$\frac{\partial Q_3}{\partial \theta_2}$	$\frac{\partial Q_3}{\partial \theta_3}$	\dots	$\frac{\partial Q_3}{\partial \theta_n}$	$\frac{\partial Q_3}{\partial V_2 }$	$\frac{\partial Q_3}{\partial V_3 }$	\dots	$\frac{\partial Q_3}{\partial V_n }$	$ V_3 ^{u+1} - V_3 ^u$	$Q_3(x) - Q_3$
\vdots	\vdots	\vdots	\vdots	\vdots	\vdots	\vdots	\vdots	\vdots	\vdots
$\frac{\partial Q_n}{\partial \theta_2}$	$\frac{\partial Q_n}{\partial \theta_3}$	\dots	$\frac{\partial Q_n}{\partial \theta_n}$	$\frac{\partial Q_n}{\partial V_2 }$	$\frac{\partial Q_n}{\partial V_3 }$	\dots	$\frac{\partial Q_n}{\partial V_n }$	$ V_n ^{u+1} - V_n ^u$	$Q_n(x) - Q_n$


if bus 2 was a PV bus (case I) (more than 1 gen).

\rightarrow (1 col & 1 row) \rightarrow Nil. \rightarrow PV buses \rightarrow dc

\rightarrow because V_2 is known

* in newton-raphson: increasing the # of generator buses (PV buses) decreases the dimensionality (complexity) of the problem, while in gauss it complicates the problem. (adds extra steps to it).

ex:-

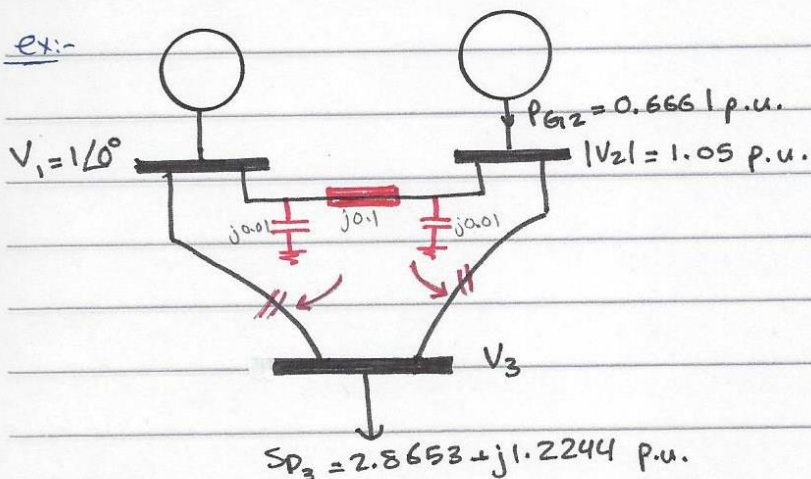

, apply N-R method to solve for variables:

Solution:-

Case II:-

Given:- V_1 , $(P_2, |V_2|)$, S_3
 $P_{G2} - P_{D2} = P_{G2} = 0.6661$
 1.05 p.u.
 $S_3 = -S_{D3} = -2.8653 - j1.2244$

find:- S_1 , (Q_2, θ_2) , $V_3 \rightarrow (|V_3|, \theta_3)$

$$X = \begin{bmatrix} \theta_2 \\ \theta_3 \\ |V_3| \end{bmatrix} \rightarrow \begin{matrix} \propto P_2 \\ \propto P_3 \\ \propto Q_3 \end{matrix}$$

$$Y_{\text{matrix}} = \begin{bmatrix} -j19.98 & j10 & j10 \\ j10 & -j19.98 & j10 \\ j10 & j10 & -j19.98 \end{bmatrix}$$

$$P_2(x) = \sum_{k=1}^n |V_2| |V_k| \left[\cancel{a_{2k}} \cos(\theta_2 - \theta_k) + b_{2k} \sin(\theta_2 - \theta_k) \right] = 0, \text{ since } Y \text{ doesn't have real part.}$$

$$= |V_2| |V_1| \times 10 \sin(\theta_2 - \theta_1) + |V_2|^2 \times \text{zero} + |V_2| |V_3| \times 10 \sin(\theta_2 - \theta_3)$$

→ be careful it's not $j10$ ($b = \text{real value equals the imaginary part of } Y \text{ (without "j")}$).

$$\therefore P_2(x) = 10.5 \sin(\theta_2) + 10.5 |V_3| \sin(\theta_2 - \theta_3) \dots (1)$$

$$P_3(x) = |V_3| |V_1| \times 10 \sin(\theta_3 - \theta_1) + |V_3| |V_2| \times 10 \sin(\theta_3 - \theta_2) + 0$$

$$P_3(x) = 10 |V_3| \sin(\theta_3) + 10.5 |V_3| \sin(\theta_3 - \theta_2) \dots (2)$$

$$Q_3(x) = \sum_{k=1}^n |V_3| |V_k| \left[\cancel{a_{3k}} \sin(\theta_3 - \theta_k) - b_{3k} \cos(\theta_3 - \theta_k) \right]$$

$$= -|V_3| |V_1| (10 \cos(\theta_3)) - |V_3| |V_2| \times 10 \cos(\theta_3 - \theta_2) + |V_3|^2 \times 19.98 \times 1$$

$$Q_3(x) = -10 |V_3| \cos(\theta_3) - 10.5 |V_3| \cos(\theta_3 - \theta_2) + 19.98 |V_3|^2 \dots (3)$$

13/4/2014

lecture #26

cont.

$$x = \begin{bmatrix} \theta_2 \\ \theta_3 \\ |V_3| \end{bmatrix} \quad J(x)?$$

$$\rightarrow \frac{\partial P_2(x)}{\partial \theta_2} = 10.5 \cos(\theta_2) + 10.5 |V_3| \cos(\theta_2 - \theta_3) \quad \dots (11)$$

$$\frac{\partial P_2(x)}{\partial \theta_3} = -10.5 |V_3| \cos(\theta_2 - \theta_3) \quad \dots (12)$$

إذا طالعش بالسالب لازم آتسك
كلية 86 نه 4 آزبه θ_3 بدعا تبه P_3 و بالكي P_2 بدعا نقل

$$\frac{\partial P_2(x)}{\partial |V_3|} = 10.5 \sin(\theta_2 - \theta_3) \quad \dots (13)$$

$$\rightarrow \frac{\partial P_3(x)}{\partial \theta_2} = -10.5 |V_3| \cos(\theta_3 - \theta_2) \quad \dots (21)$$

$$\frac{\partial P_3(x)}{\partial \theta_3} = 10 |V_3| \cos \theta_3 + 10.5 |V_3| \cos(\theta_3 - \theta_2) \quad \dots (22)$$

$$\frac{\partial P_3(x)}{\partial |V_3|} = 10 \sin(\theta_3) + 10.5 \sin(\theta_3 - \theta_2) \quad \dots (23)$$

$$\rightarrow \frac{\partial Q_3}{\partial \theta_2} = -10.5 |V_3| \sin(\theta_3 - \theta_2) \quad \dots (31)$$

$$\frac{\partial Q_3}{\partial \theta_3} = 10 |V_3| \sin \theta_3 + 10.5 |V_3| \sin(\theta_2 - \theta_3) \quad \dots (32)$$

$$\frac{\partial Q_3}{\partial |V_3|} = -10 \cos(\theta_3) - 10.5 \cos(\theta_3 - \theta_2) + 2 \times 19.98 |V_3| \quad \dots 33$$

$$\begin{aligned} \rightarrow F_1(x) &= P_2(x) - P_2^0 \leftarrow 0.6661 \text{ p.u.} \\ F_2(x) &= P_3(x) - P_3^0 \leftarrow -2.8653 \text{ p.u.} \\ F_3(x) &= Q_3(x) - Q_3^0 \leftarrow -1.2244 \text{ p.u.} \\ &\quad -0.52 \end{aligned}$$

$x^0 = \begin{bmatrix} 0 \\ 0 \\ 1 \end{bmatrix}$ flat start
depends on the value of Stack bus voltage $|V_1|$ here = 1 p.u.

$$F(x^0) = \begin{bmatrix} -0.6661 \\ 2.8653 \\ 0.7044 \end{bmatrix}$$

$$J(x^0) = \begin{bmatrix} 21 & -10.5 & 0 \\ -10.5 & 20.5 & 0 \\ 0 & 0 & 19.96 \end{bmatrix}$$

→ the inverse of this matrix can be found by inverting each individual sub matrix

$$\Delta(x^0) = J(x^0)^{-1} F(x^0)$$

$$\begin{bmatrix} \theta_2' - \theta_2^0 \\ \theta_3' - \theta_3^0 \\ |V_3'| - |V_3|^0 \end{bmatrix} = - \begin{bmatrix} 21 & -10.5 & 0 \\ -10.5 & 20.5 & 0 \\ 0 & 0 & 19.96 \end{bmatrix}^{-1} \begin{bmatrix} -0.6661 \\ 2.8653 \\ 0.7044 \end{bmatrix}$$

$$= \begin{bmatrix} -0.0513 & \text{rad} \\ -0.166 & \text{rad} \\ -0.0169 & \text{p.u.} \end{bmatrix} = \begin{bmatrix} -3.9396^\circ \\ -9.5139^\circ \\ -0.0619 \text{ p.u.} \end{bmatrix}$$

$$\therefore \theta_2' = -3.9396^\circ$$

$$\theta_3' = -9.5139^\circ$$

$$|V_3'| = 1 - 0.0619 = 0.9389$$

then calculate $S_1' = V_1' \sum Y_{1k}^* V_k^*$

& $Q_2' = \text{Im} \{ S_2' \}$...

$$V_1' = 1 \angle 0^\circ, V_2' = 1.05 \angle -3.9396^\circ$$

$$V_3' = 0.9389 \angle -9.5139^\circ$$


CHAPTER #10: Balanced 3-phase faults:

• What is a fault?


→ Any failure or condition in the system that results in the generated current (or part of it) not reaching the load (except the charging current).

• Types of fault:-

1. Balanced 3-phase fault.

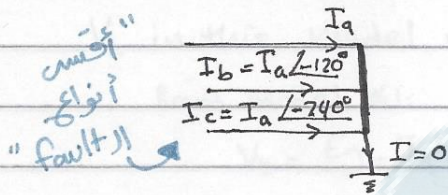


2. 1-phase to earth fault (1-P-E)

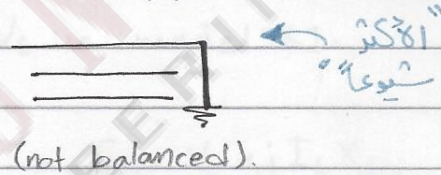

3. Phase to phase (P-P) fault.




4. Phase to phase to Earth fault (P-P-E)

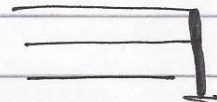

In this chapter we'll study the balanced 3-ph fault...

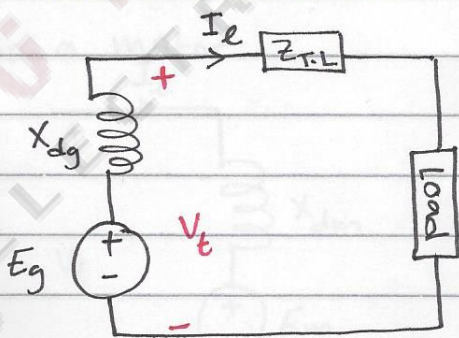
model #1: for calculations of Load current (I_L):



$$V_t = E_g - jX_{dg} I_e$$

model #2: for calculation of short ckt current of

Unloaded machine.

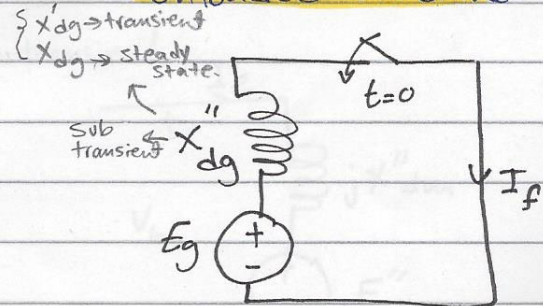


↳ before the fault there was no Armature reaction ($I_L = 0$) "No-load".

* model #1 is used to find I_L only, model #2 for I_f only but what about a loaded machine that has suddenly encountered a fault? (we'll use model #3) ...

model #3: for calculations of both I_L & I_f .

↳ Internal Voltages Method.

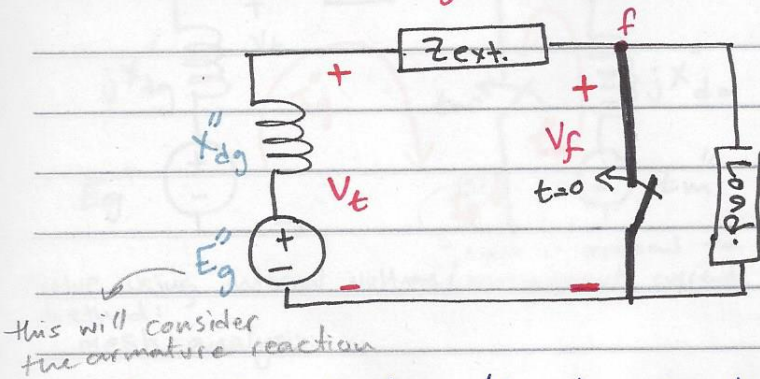

before the fault I want to use X_{dg} , but when $t=0$ (fault happens), I must use X''_{dg} (since armature reaction will change)
 ↳ $E_{AR} = -j I X_{ar}$

In order to be able to use this model to calculate I_L
 V_t in this model must equal V_t in model #1.

from model #1:

$$V_t = E_g - I_L \times jX_{dg} \quad \rightarrow \quad E_g = V_t + jI_L X_{dg} \quad \text{--- (1)}$$

from model #3:

$$V_t = E_g'' - jI_L X''_{dg} \quad \rightarrow \quad E_g'' = V_t + jI_L X''_{dg} \quad \text{--- (2)}$$

↳ (before fault).

(1) - (2)


$$\hookrightarrow E_g - E_g'' = jI_L (X_{dg} - X''_{dg})$$

↳ or at I_L

→ $E_g'' \equiv$ internal voltage. (mathematical representation, can't be measured practically).


⇒ for transient calculation use X'_{dg} , E_g' . "just replace (") with (")"

→ for a motor:

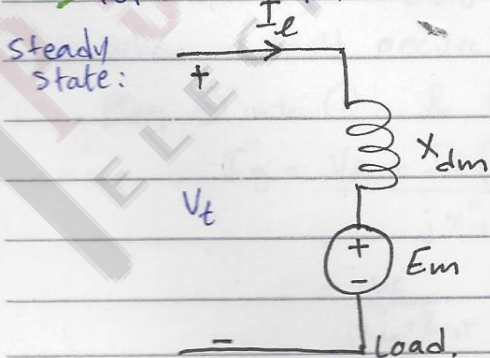

$$E_m = V_t - I_L jX_{dm}$$

Sub-transient:

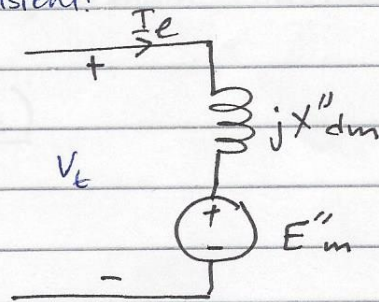


$$E''_m = V_t - jI_L X''_{dm}$$

For transient: $E'_m = V_t - jI_L X'_{dm}$

15/4/2014

Lecture #27

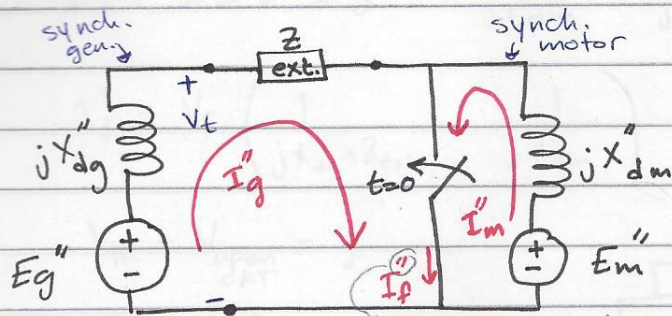

before the fault happens we can find I_L, E_g'', E_m''
 After the fault we can compute I_f'' .


Solve using internal voltage/subtransient current method:

mesh analysis:-

$$I_g'' = \frac{E_g''}{jX_{dg}'' + Z_{ext}} \quad \dots (1)$$

$$I_m'' = \frac{E_m''}{jX_{dm}''} \quad \dots (2)$$

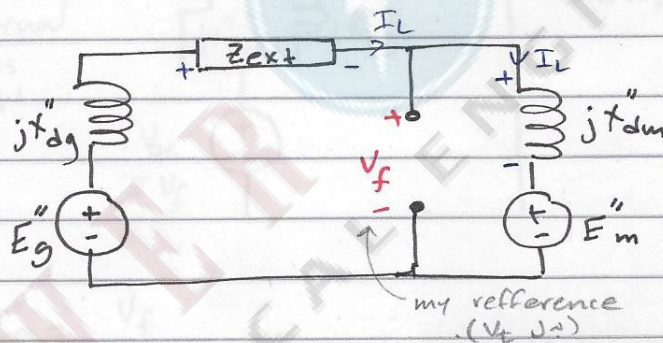$E_m'' ? E_g'' ?$ use the CKT before the fault:



$$E_g'' = V_f + I_L (Z_{ext} + jX_{dg}'') \quad \dots (a)$$

$$E_m'' = V_f - I_L (jX_{dm}'') \quad \dots (b)$$

When a fault occurs E_m'', E_g'', V_f remain constant.

Plug (a) into (1) & (b) into (2)

$$I_g'' = \frac{V_f + I_L (jX_{dg}'' + Z_{ext})}{jX_{dg}'' + Z_{ext}}$$

$$= \frac{V_f}{jX_{dg}'' + Z_{ext}} + I_L$$

$$I_m'' = \frac{V_f - jI_L X_{dm}''}{jX_{dm}''}$$


$$= \frac{V_f}{jX_{dm}''} - I_L$$

$$I_f'' = I_m'' + I_g'' = \frac{V_f}{jX_{dm}''} + \frac{V_f}{jX_{dg}'' + Z_{ext}}$$


$$I_f'' = V_f \left(\frac{1}{jX_{dg}'' + Z_{ext}} + \frac{1}{jX_{dm}''} \right) \Leftarrow \text{Thevenin!}$$

$$V_{th} = V_{open\ CKT} = V_f$$
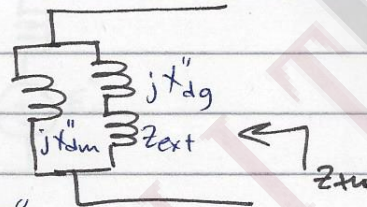
$$\frac{1}{Z_{th}} = \frac{1}{jX_{dg}'' + Z_{ext}} + \frac{1}{jX_{dm}''}$$


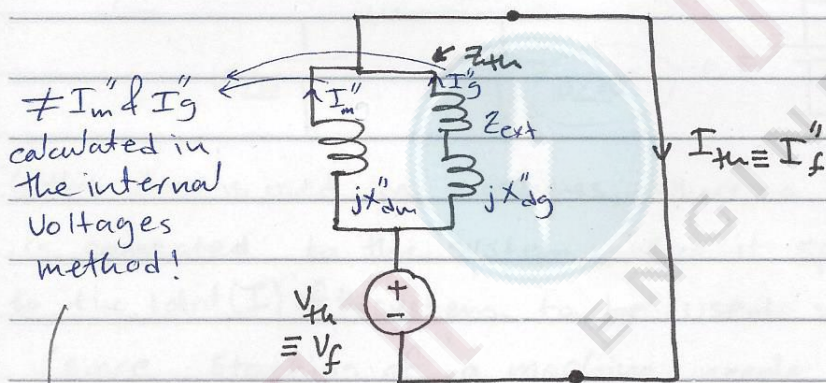
$$I_{slc} = V_f \times \frac{1}{Z_{th}} = I_{th}'' = I_f''$$




$$I_g'' = \frac{V_f}{Z_{ext} + jX_{dg}''}$$

$$I_m'' = \frac{V_f}{jX_{dm}''}$$

(We can use thevenin method for the external ckt (load) only, we can't use it for the internal ckt values).

\therefore thevenin is a very fast method to find I_f'' , but what about I_m'' & I_g'' ?


let's do some ckt modifications:

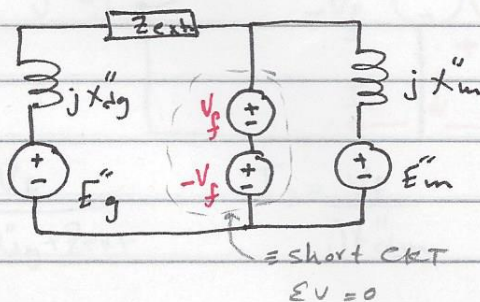


now, by super position :-

↳ Solution #1:

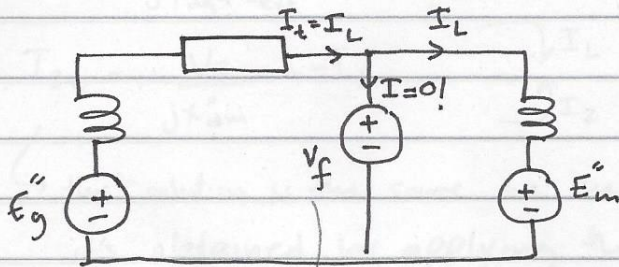let $[E_g'', E_m'', V_f]^{bc}$ ON & $[-V_f]$ OFF (short CKT).



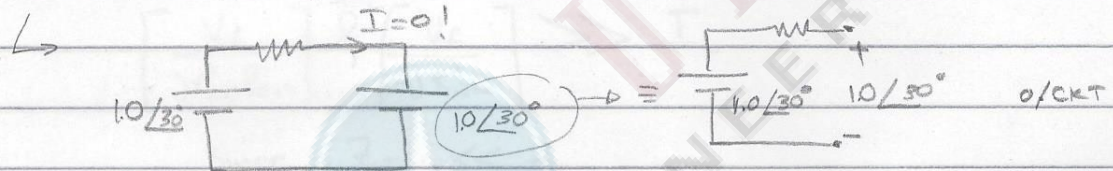
"مبدأ Voltage source"
 "قوة V قوة إيجابية (V_f)
 source (إيجابية)"



↳ this idea is used in machines, where a "spinning reserved" machine is connected to the system, where it spins but doesn't contribute to the total (I) of the system. to be used when an error occurs. (since starting of a machine needs long time due to its huge inertia). $V_L = V$ before inserting it.

↳ solution #2:

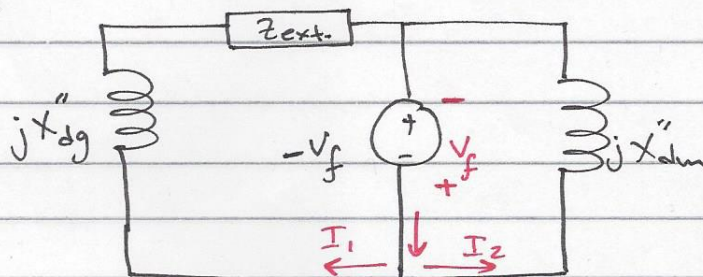let $(-V_f)^{bc}$ ON, (E_g'', E_m'', V_f) OFF




$$I_1 = \frac{V_f}{jX''_{dg} + Z_{ext}}$$

$$I_2 = \frac{V_f}{jX''_{dm}}$$

↳ the total solution (add sol. #① & ②).

$$I_{1t} = \frac{V_f}{jX''_{dg} + Z_{ext}} + I_L$$
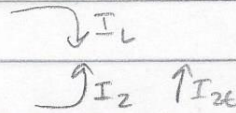
$$I_{2t} = \frac{V_f}{jX''_{dm}} + -I_L$$



↳ this solution is the same as the internal voltages method's sol. it's obtained by applying theorem then add loading condition.

$$\left[\frac{V_f}{jX''_{dg} + Z_{ext}} \right] \& \left[\frac{V_f}{jX''_{dm}} \right] \gg I_L$$

Since $Z_{TL} \ll Z_L$



~ "شاه صيک بقیه حل" اکل الثاني و باقي داعي الاول (I_L)

بالاحسان اذا ما صد طريقة اكل و حل كالتالي و اعمل I_L .

17/4/2015

Lecture #28

ex:

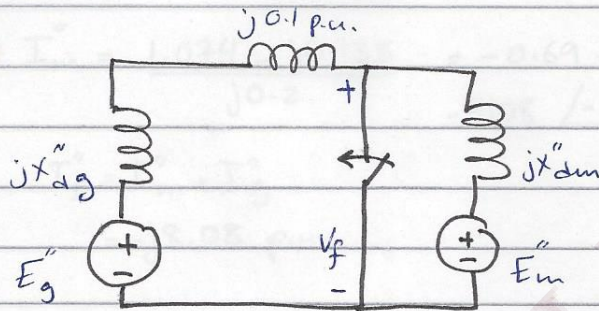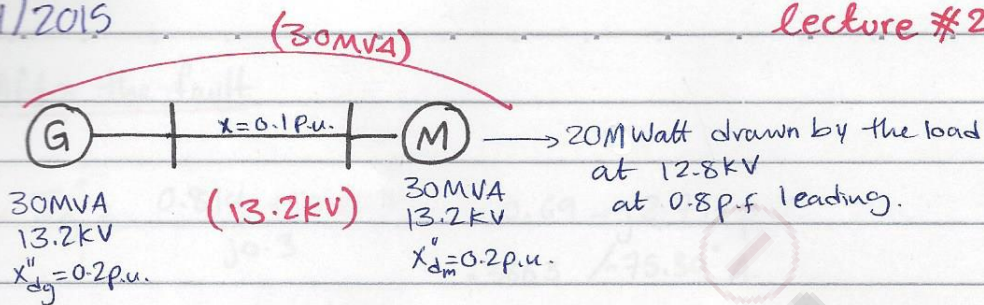

1. Internal Voltages Method:

- before fault:

$$V_f = \frac{12.8}{13.2} = 0.97 \angle 0^\circ \text{ pu.}$$

$$E''_g = 0.97 \angle 0^\circ + I (jX''_{dg} + jX_{TL}) \quad \dots (1)$$

@ the terminals of the motor:- $V = 0.97 \angle 0^\circ \text{ pu.}$

$$S = \frac{20 / 0.8}{30} \angle -36.87^\circ \text{ pu.}$$

$$I = \frac{S^*}{V^*} = \frac{20 / 0.8 \angle +36.87^\circ}{0.97 \angle 0^\circ} = 0.86 \angle 36.87^\circ \text{ pu.}$$

$$= 0.69 + j0.52 \text{ pu.}$$

back to (1):

$$* E''_g = 0.97 \angle 0^\circ + 0.86 \angle 36.87^\circ (j0.3)$$

$$= 0.814 + j0.207$$

$$* E''_m = V_f - jX''_{dm} I_L$$

$$= 0.97 \angle 0^\circ - j0.2 \times 0.86 \angle 36.87^\circ$$

$$= 1.075 - j0.138$$

$$\text{base current} = \frac{30 \times 10^6}{\sqrt{3} \times 13.2 \times 10^3} = 1312 \text{ A}$$

• After the fault

$$* I_g'' = \frac{0.814 + j0.207}{j0.3} = 0.69 - j2.71 \text{ p.u.} \\ = 3663 \angle -75.30^\circ \text{ A}$$

$$* I_m'' = \frac{1.074 - j0.138}{j0.2} = -0.69 - j5.37 \text{ p.u.} \\ = 7108 \angle -87.3^\circ \text{ A}$$

$$I_f'' = I_m'' + I_g'' \\ = -j8.08 \text{ p.u.}$$


2. Thevenin Method:

$$V_{th} = V_f = 0.97 \angle 0^\circ \text{ p.u.}$$

$$Z_{th} = j0.3 \parallel j0.2 = j0.12 \text{ p.u.}$$


$$I_f'' = \frac{0.97 \angle 0^\circ}{j0.12} = -j8.08 \text{ p.u.}$$
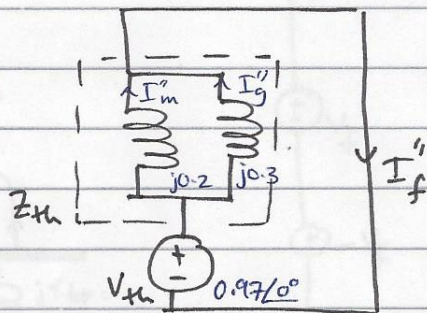
$$\begin{cases} I_m'' = -j3.23 \neq I_m \text{ in the previous meth.} \\ I_g'' = -j4.84 \neq I_g \text{ } \end{cases}$$




↳ solution? use superposition:

3. Super Position:

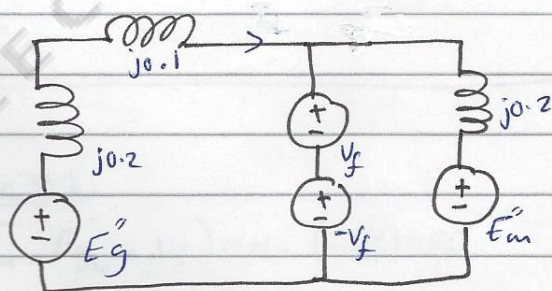

① $-V_f$ off, others ON

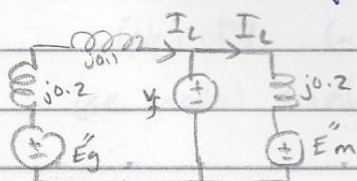
$$I_L = 0.86 \angle 36.87^\circ \text{ p.u.}$$



② $-V_f$ ON, others OFF

$$I_1 = \frac{0.97 \angle 0^\circ}{j0.3} = -j3.23$$
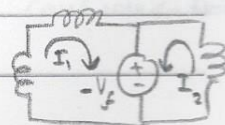
$$I_2 = \frac{0.97 \angle 0^\circ}{j0.2} = -j4.85 \text{ p.u.}$$



③ total solution:-

$$I_g'' = -j3.23 + 0.69 + j0.52 = 0.69 - j2.71 \text{ p.u.} = 3660 \angle -75.3^\circ \text{ A}$$

$$I_m'' = -j4.85 - 0.69 - j0.52 = -0.69 - j5.37 \text{ p.u.} = 7108 \angle -87.3^\circ \text{ A}$$

$$I_f'' = -j10600 \text{ A} \quad (\text{base current} = 1312 \text{ A})$$

in thevenin's method:-

$$I_m'' = -j6360 \text{ A}$$

$$I_g'' = -j4240 \text{ A}$$


$$4240 - 3660 \approx 800 \text{ A}$$

Therminin's method في الجهد في نقطة fault current في نقطة fault

والجهد في نقطة fault في نقطة fault

now, we'll focus on the 2nd sol. ($I_L = 0$)

ex2:

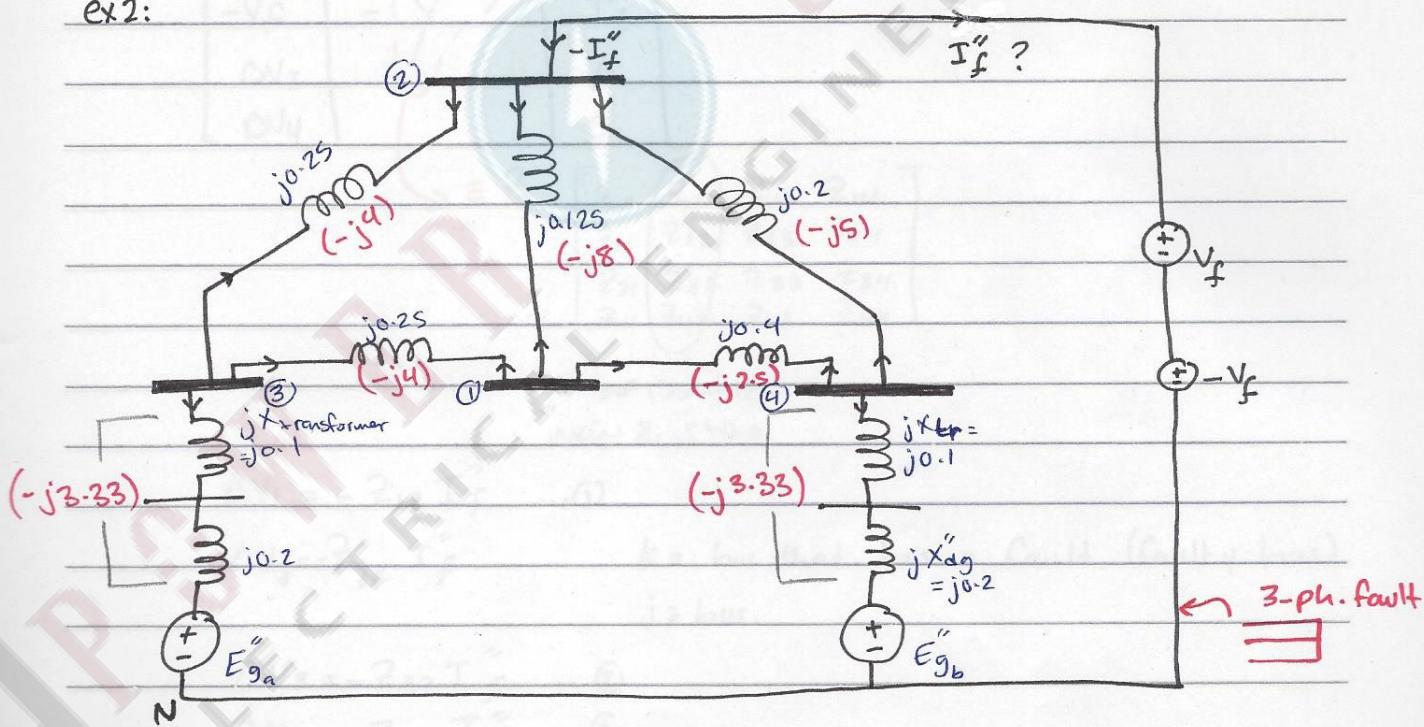

Solution #1:

$$(E_{g_a}'', E_{g_b}'', V_f) \text{ ON, } (-V_f) \text{ OFF}$$

assume I_L in all branches = 0 (don't take it into consideration).

$$\therefore V_1 = V_2 = V_3 = V_4 = E_{g_a}'' = E_{g_b}'' = V_f$$


\therefore go to solution #2:

$$(-V_f) \text{ ON, } (+V_f, E_{g_a}'', E_{g_b}'') \text{ OFF}$$

use nodal analysis. in p.s.s. \rightarrow bus \equiv node

entering I
leaving I

$$I = (YV)$$

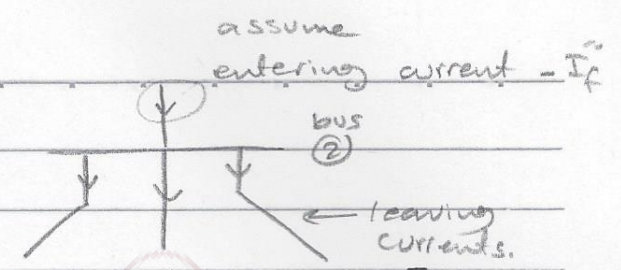

لكل row افترج = 0 اذا كان في اسي بيده bus و

$$\begin{bmatrix} 0 \\ -I_f'' \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -j14.5 & j8 & j4 & j2.5 \\ j8 & -j17 & j4 & j5 \\ j4 & j4 & -j11.33 & 0 \\ j2.5 & j5 & 0 & -j10.83 \end{bmatrix} \begin{bmatrix} \Delta V_1 \\ \Delta V_2 = -V_f \\ \Delta V_3 \\ \Delta V_4 \end{bmatrix}$$

$\Sigma \neq 0$

السؤال في ال Super position

neutral gen في بيده و

$$\begin{bmatrix} \Delta V_1 \\ -V_f \\ \Delta V_3 \\ \Delta V_4 \end{bmatrix} = Y^{-1} \begin{bmatrix} 0 \\ -I_f'' \\ 0 \\ 0 \end{bmatrix}$$

$$\equiv Z = \begin{bmatrix} z_{11} & z_{12} & z_{13} & z_{14} \\ z_{21} & z_{22} & z_{23} & z_{24} \\ z_{31} & z_{32} & z_{33} & z_{34} \\ z_{41} & z_{42} & z_{43} & z_{44} \end{bmatrix}$$

سؤال في ال Super position

$$\Delta V_1 = -z_{12} I_f'' \quad \dots (1)$$

$$\Delta V_j = -z_{jk} I_f'' \quad k \equiv \text{bus that has a fault. (faulty bus)}$$


$$j \equiv \text{bus.}$$

$$\Delta V_3 = -z_{32} I_f'' \quad \dots (2)$$

$$\Delta V_4 = -z_{42} I_f'' \quad \dots (3)$$

$$-V_f = -I_f'' z_{22} \quad \dots (4)$$
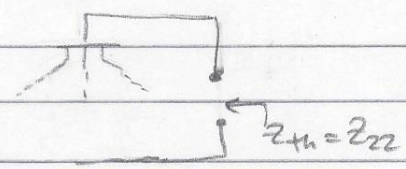
$$\hookrightarrow I_f'' = \frac{V_f}{z_{22}} \equiv z_{th}$$



Plug I_f'' in (2) & (3)

$$\Delta V_3 = -z_{32} \frac{V_f}{z_{22}} \quad , \quad \Delta V_4 = -z_{42} \frac{V_f}{z_{22}}$$

$$\Delta V_j = V_f - \frac{z_{jk}}{z_{kk}} V_f$$

cont. → now, add the 2 solutions:


$$V_1 = V_f - \frac{Z_{12}}{Z_{22}} V_f$$

$$V_2 = V_f - \frac{Z_{22}}{Z_{22}} V_f = 0$$

$$V_3 = V_f - \frac{Z_{32}}{Z_{22}} V_f$$

$$V_4 = V_f - \frac{Z_{42}}{Z_{22}} V_f$$

one-line diagram

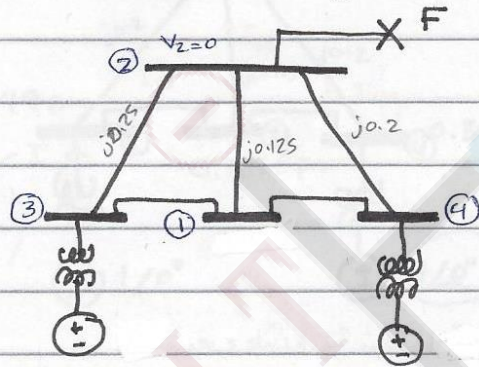

in general, $V_j = \underbrace{V_f}_{1^{st} \text{ sol.}} - \frac{Z_{jk}}{Z_{kk}} \underbrace{V_f}_{2^{nd} \text{ sol.}}$

given $V_f = 1.0 \angle 0^\circ$ p.u. "diff. do so" (col. 2)

$$Z_{bus} = \begin{bmatrix} - & j0.1938 & - & - \\ - & j0.2295 & - & - \\ - & j0.1494 & - & - \\ - & j0.1506 & - & - \end{bmatrix}$$

in two-port networks:-

$$Z_{ij} = \frac{V_i}{I_j} \Big|_{V_k=0, k \neq i} \neq 0$$

bus i is "looking in" (S/CKT) bus j, bus i is "looking in" (bus j, bus i)

$$I_f'' = \frac{V_f}{Z_{22}} = \frac{1.0 \angle 0^\circ}{j0.2295} = -j 4.3573 \text{ p.u.}$$

$$V_1 = 1.0 \angle 0^\circ - \frac{j0.1938}{j0.2295} 1.0 \angle 0^\circ = 0.1556 \text{ p.u.}$$

$$V_2 = 0$$

$$V_3 = 1.0 \angle 0^\circ - \frac{j0.1494}{j0.2295} 1.0 \angle 0^\circ = 0.349 \text{ p.u.}$$

$$V_4 = 1.0 \angle 0^\circ - \frac{j0.1506}{j0.2295} 1.0 \angle 0^\circ = 0.3438 \text{ p.u.}$$


fault at bus 2 → $V_2 = 0$ → @ other buses $|V|$ will decrease, the most affected bus (i) is the one that has the smallest impedance between its terminal & the faulty bus's $\equiv Z_{i2}$, in this example it's bus 1.

$$I_{12} = \frac{0.1556 - 0}{j0.125}$$


$$I_{32} = \frac{0.349 - 0}{j0.25}$$

$$I_{42} = \frac{0.3438 - 0}{j0.2}$$

$$I_f'' = I_{32} + I_{12} + I_{42}$$

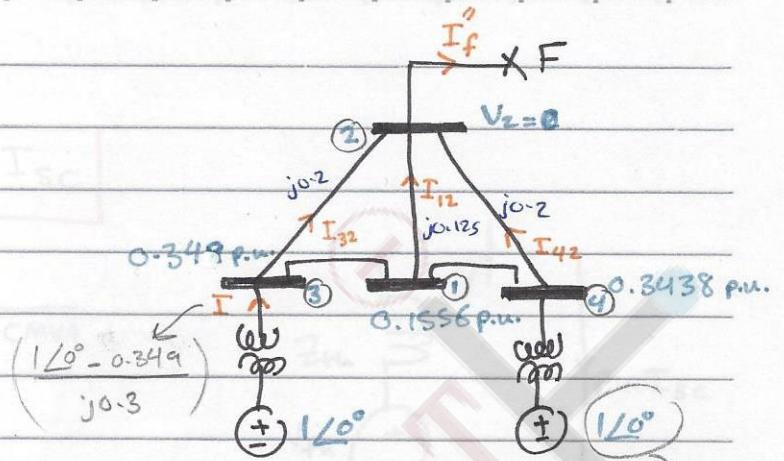

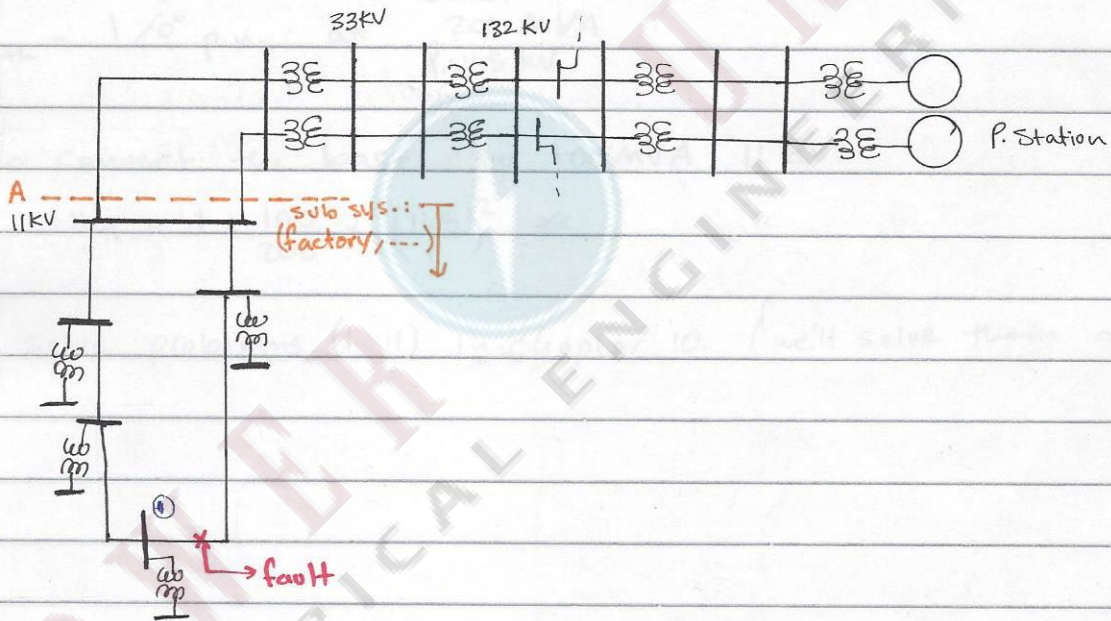تصنيف ثابت قبل و اثناء و بعد
 ~ fault
 $I_f = \text{const.}$ $I_L = 0$
 لا يوجد




for the sub-system calculations & analysis we just need to know V_{th} & Z_{th} at A, we don't need other details about the remaining P-system.

how to find thevenin equivalent?

usually, you'll be given (3-ph) Short CKT MVA (SCMVA) at A.

↳ at nominal voltage

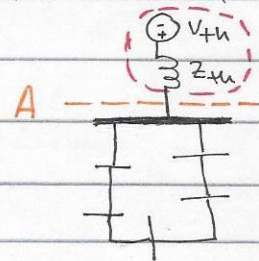

$$SCMVA = \sqrt{3} \times \text{Nominal Voltage (KV)} \times I_{sc} (A) \times 10^{-3} \quad \dots (1)$$

$$\text{Base MVA} = \sqrt{3} \times \text{base Voltage KV} \times I_{\text{base}} (A) \times 10^{-3} \quad \dots (2)$$

↳ let it equal nominal voltage.

divide (1) by (2):

$$SCMVA (p.u.) = p.u. I_{sc}$$

$$X_{th} (p.u.) = \frac{1}{p.u. I_{sc}} = \frac{1}{p.u. SCMVA}$$

another method?

consider a fault at bus 1

$$SCMVA = 200 \text{ MVA}$$


$$KV = 11.5 \text{ KV}$$

$$\rightarrow X_{th} = 1 \angle 0^\circ \text{ p.u. at } \begin{matrix} \text{base:} \\ 200 \text{ MVA} \\ \& 11.5 \text{ KV} \end{matrix}$$

to convert the base to 100 MVA, 11 KV


$$X'_{th} = 1 \times \frac{100}{200} \times \left(\frac{11.5}{11}\right)^2 \neq$$

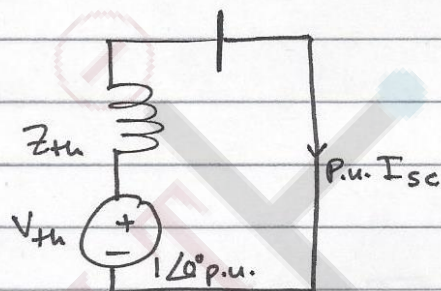solve problems (1-11) in chapter 10. (we'll solve them on sunday).




CHAPTER #11: Symmetrical Components:

- in CKTs: (review).

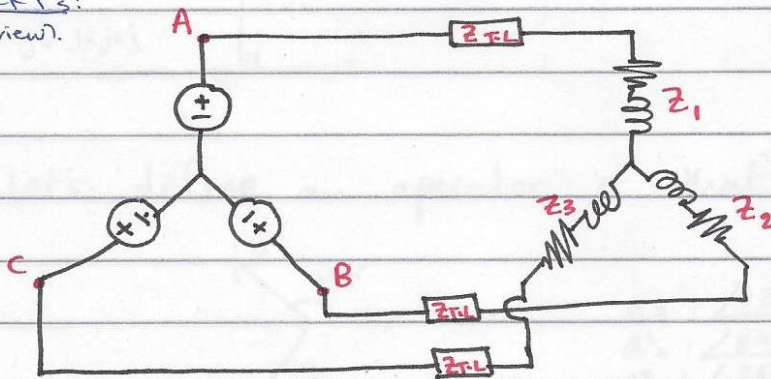


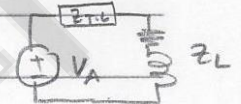if $Z_1 = Z_2 = Z_3$ (balanced): we use per phase CKT
 if $Z_1 \neq Z_2 \neq Z_3 \rightarrow$ we use mesh analysis.



- An unbalanced system of (n) related phasors. can be resolved into (n) balanced systems (we're here concerned about $n=3$). each containing ($n=3$) phasors equal in magnitude & equally displaced. (Fortescue's Thm.)

24/4
 lecture #30

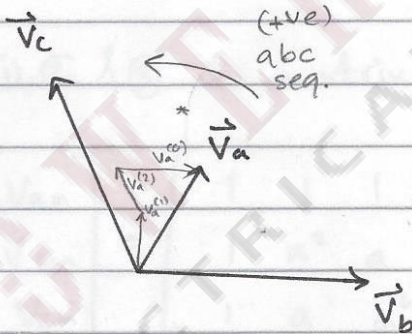


unbalanced system!


$$V_a = V_a^{(0)} + V_a^{(1)} + V_a^{(2)}$$

$$V_b = V_b^{(0)} + V_b^{(1)} + V_b^{(2)}$$

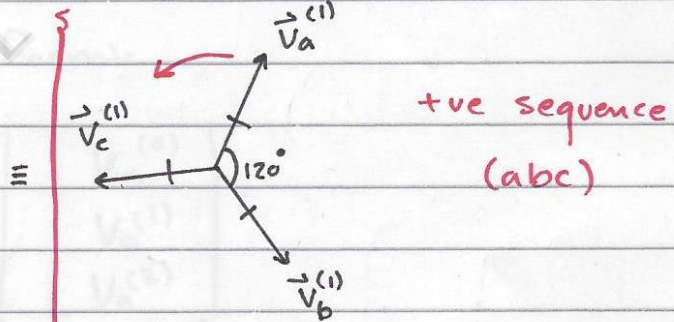
$$V_c = V_c^{(0)} + V_c^{(1)} + V_c^{(2)}$$



+ve sequence
 (abc)

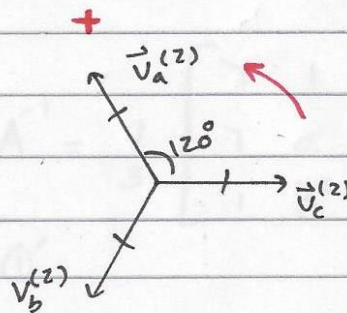


-ve seq.
 (acb)

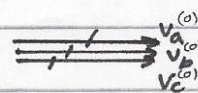


in-phase.
 Zero sequence.
 (balanced)

$$j = 1 \angle 90^\circ$$

(j) is used to shift any phasor by 90°

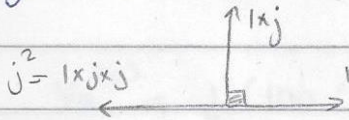

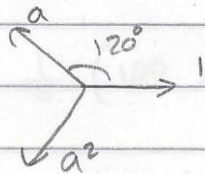Let's define an operator a that shifts the phasor 120°



$$a = 1 \angle 120^\circ$$

$$a^2 = 1 \angle 240^\circ$$

$$a^3 = 1 \angle 360^\circ$$

also: $a = -0.5 + j0.866$

back to the equations:-

$$V_{an} = V_a^{(0)} + V_a^{(1)} + V_a^{(2)} \quad \dots (1)$$

$$V_{bn} = V_b^{(0)} + V_b^{(1)} + V_b^{(2)} \quad \dots (2)$$

$$V_{cn} = V_c^{(0)} + V_c^{(1)} + V_c^{(2)} \quad \dots (3)$$

$$* V_b^{(1)} = V_a^{(1)} \angle_{-120^\circ}^{+240^\circ} = a^2 V_a^{(1)}$$

$$* V_c^{(1)} = V_a^{(1)} \angle_{+120^\circ}^{-240^\circ} = a V_a^{(1)}$$

$$* V_b^{(2)} = a V_a^{(2)}$$

$$* V_c^{(2)} = a^2 V_a^{(2)}$$

put (1), (2) & (3) in matrix form:-

$$\begin{bmatrix} V_{an} \\ V_{bn} \\ V_{cn} \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} V_a^{(0)} \\ V_a^{(1)} \\ V_a^{(2)} \end{bmatrix}$$

matrix A

$$\begin{bmatrix} V_a^{(0)} \\ V_a^{(1)} \\ V_a^{(2)} \end{bmatrix} = A^{-1} \begin{bmatrix} V_{an} \\ V_{bn} \\ V_{cn} \end{bmatrix}, \quad A^{-1} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix}$$

$$\therefore V_a^{(0)} = \frac{1}{3} (V_a + V_b + V_c) \quad \dots (1)'$$

$$V_a^{(1)} = \frac{1}{3} (V_a + a V_b + a^2 V_c) \quad \dots (2)'$$

$$V_a^{(2)} = \frac{1}{3} (V_a + a^2 V_b + a V_c) \quad \dots (3)'$$

in a case of a balanced system with (v) seq. : $|V_a| = |V_b| = |V_c| = 100$.

$$V_a^{(0)} = \frac{1}{3} (100 \angle 0^\circ + 100 \angle -120^\circ + 100 \angle -240^\circ) = 0$$

$$V_a^{(1)} = \frac{1}{3} (100 \angle 0^\circ + 100 \angle 0^\circ + 100 \angle 0^\circ) = 100 \angle 0^\circ$$


$$V_a^{(2)} = \frac{1}{3} (100 \angle 0^\circ + 100 \angle 120^\circ + 100 \angle -120^\circ) = 0$$

but is it applicable to 3 line to line voltages?
(V_{ab}, V_{bc}, V_{ca})? yes!

$$\begin{bmatrix} V_{ab}^{(0)} \\ V_{ab}^{(1)} \\ V_{ab}^{(2)} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} V_{ab} \\ V_{bc} \\ V_{ca} \end{bmatrix}$$

$$V_{ab}^{(0)} = \frac{1}{3} (V_{ab} + V_{bc} + V_{ca}) = 0 \text{ (closed loop } a \rightarrow b \rightarrow c \rightarrow a \text{)}$$

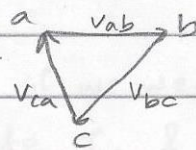also, $= V_{an}^{(0)} - V_{bn}^{(0)} = 0$




It's also applicable to currents, ... (any 3 phasors).

$$\begin{bmatrix} I_a^{(0)} \\ I_a^{(1)} \\ I_a^{(2)} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$$

for line currents:-

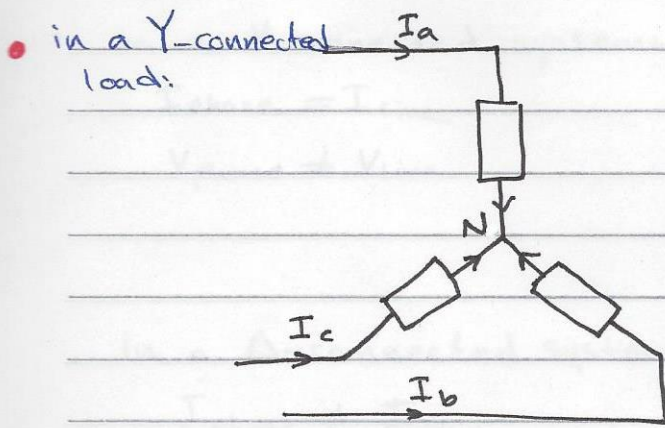
$$\begin{bmatrix} I_{ab}^{(0)} \\ I_{ab}^{(1)} \\ I_{ab}^{(2)} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_{ab} \\ I_{bc} \\ I_{ca} \end{bmatrix}$$




if the neutral (N) was isolated

$$I_a^{(0)} = 0$$

else: $I_a^{(0)}$ might not be zero.

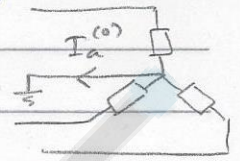


in a Δ -connected load:

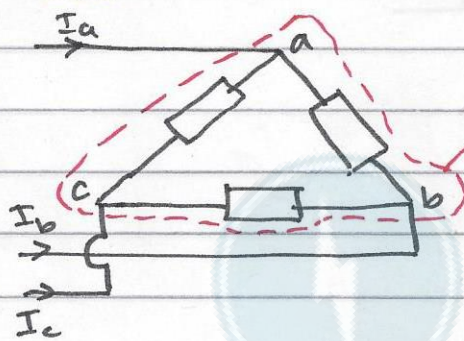

$(I_a + I_b + I_c)$ must equal zero.
 $\sum I = 0$

consider Δ as a super node. $\sum I = I_{\text{leaving the node}} = 0$.

ex:-

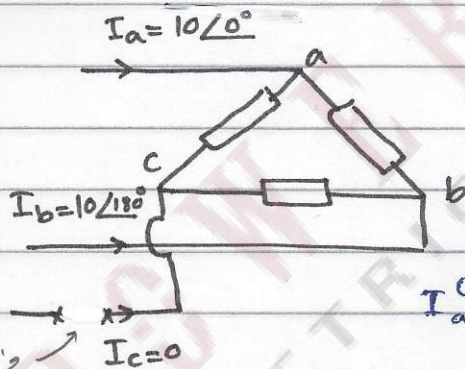

$\sum I = 0$ \therefore if we were give I_a we can calculate I_b & vice versa.

find $I_a^{(0)}$, $I_a^{(1)}$, $I_a^{(2)}$, \dots , $I_c^{(2)}$:

$$I_a^{(0)} = \frac{1}{3} (I_a + I_b + I_c) = \frac{1}{3} \sum I = 0.$$

$$I_a^{(1)} = \frac{1}{3} (10 \angle 0^\circ + 10 \angle 300^\circ + 0) = 5.78 \angle -30^\circ \text{ A}$$

$$I_a^{(2)} = \frac{1}{3} (10 \angle 0^\circ + 10 \angle 180^\circ \angle 240^\circ + 0) = 5.78 \angle +30^\circ \text{ A}$$


$$I_b^{(1)} = a^2 I_a^{(1)}, \quad I_c^{(1)} = a I_a^{(1)}$$

$$I_b^{(2)} = a I_a^{(2)}, \quad I_c^{(2)} = a^2 I_a^{(2)}$$

in a Y-connected system:-

$$I_{\text{phase}} = I_{\text{line}}$$

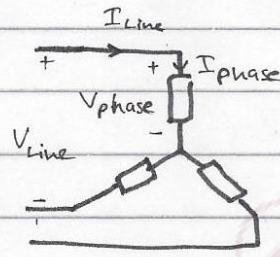
$$V_{\text{phase}} \neq V_{\text{line}}$$



in a Δ -connected system:-

$$I_{\text{phase}} \neq I_{\text{line}}$$

$$V_{\text{phase}} = V_{\text{line}}$$

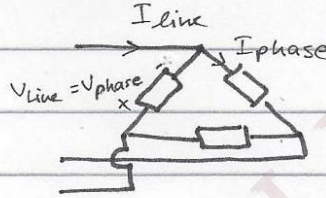


27/4/2014


Lecture #31

CHAPTER 10 problems:-

10.1

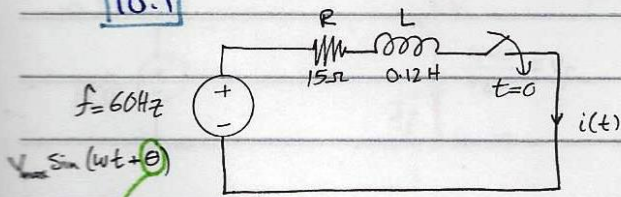

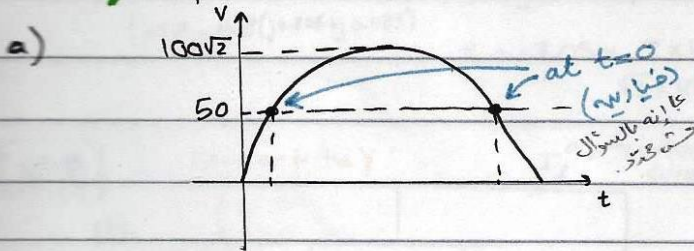θ : point on the waveform at which the switch closes



$$50 = 100\sqrt{2} \sin(\theta)$$


$$\theta = 20.7^\circ \text{ or } 159.3^\circ$$

$$i(t) = \underbrace{\frac{V_{max}}{Z} \sin(\omega t + \theta - \phi)}_{\text{Steady state component}} - \underbrace{\frac{V_{max}}{Z} \sin(\theta - \phi) e^{-\frac{R}{L}t}}_{\text{transient component}}$$

$$Z = 15 + j2\pi \times 60 \times 0.12 = 47.66 \angle 71.66^\circ \Omega$$

* max. value at $t=0$.

10.4

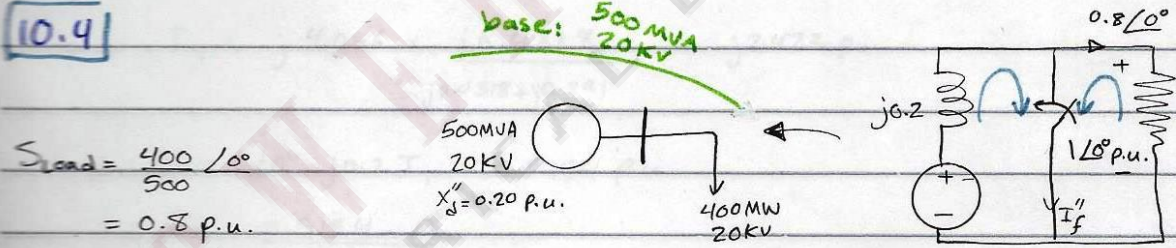


$$S_{load} = \frac{400}{500} \angle 0^\circ = 0.8 \text{ p.u.}$$

$$I_{load} = \frac{S_{load}}{V_{load}} = \frac{0.8}{1} = 0.8 \text{ p.u.}$$

$$E_g'' = 1 \angle 0^\circ + 0.8 \angle 0^\circ \times j0.2 = 1 + j0.16 \text{ p.u.}$$


$$I_g = \frac{1 + j0.16}{j0.2} = 0.8 - j5 \text{ p.u.}$$


10.6

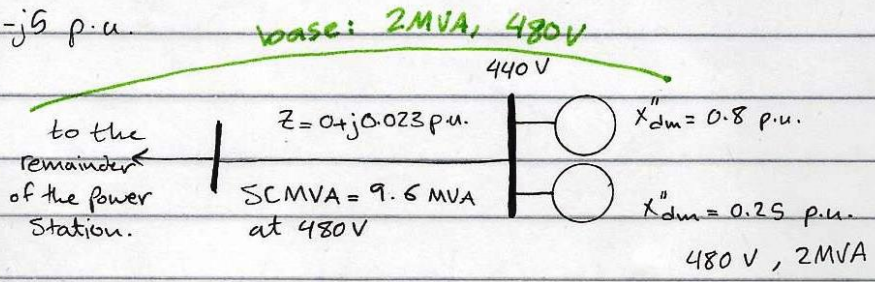

$$V_{base} = 480 \text{ V} \equiv 1 \angle 0^\circ \text{ p.u.}$$
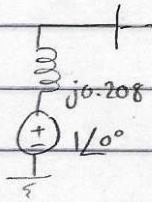
$$X_{line} = \frac{1}{9.6 \text{ MVA p.u.}} = \frac{1}{\frac{9.6}{2}} = j0.208 \text{ p.u.}$$




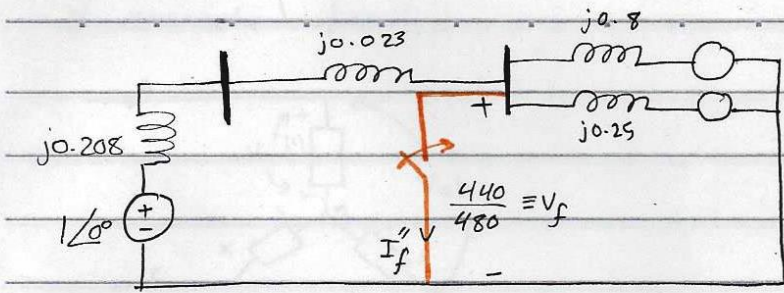

$$I_f'' = \frac{V_f}{(j0.8 // j0.25) // (j0.208 + j0.023)} = -j7.05 \text{ p.u.}$$

$$\equiv -j7.05 \times \frac{2 \times 10^6}{\sqrt{3} \times 480} \text{ A}$$

10.8

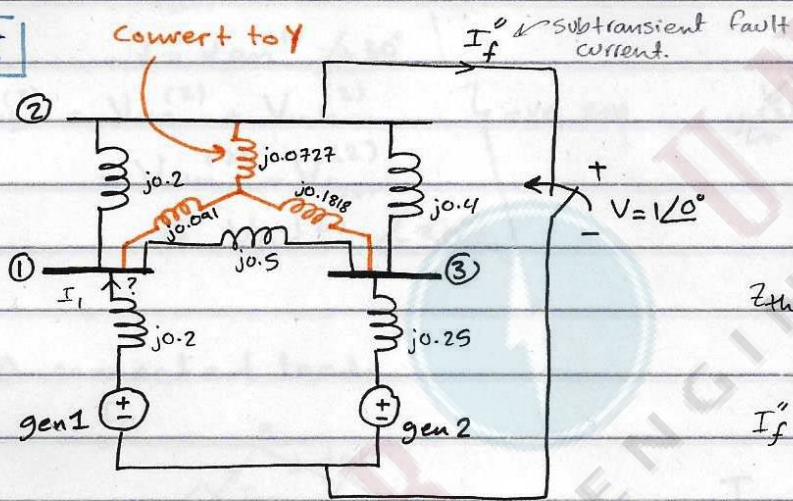

Use thevenin method (since load is not mentioned)...

$$Z_{th} = j0.0727 + (j0.1818 + j0.25) // (j0.2 + j0.2)$$

$$= j0.2465 \text{ p.u.}$$


$$I_f'' = \frac{V_f}{Z_{th}} = \frac{1 \angle 0^\circ}{j0.2465} = -j4.056 \text{ p.u.}$$

$$I_1 = -j4.056 \times \frac{j0.4318}{j0.4318 + j0.291} = -j2.423 \text{ p.u.}$$

$$V_1 = 1 \angle 0^\circ - j0.2 I_1 = 0.5154 \text{ p.u.}$$

$$I_{12} = \frac{0.5154 - 0 \angle 0^\circ}{j0.2}$$



* Y-connected load

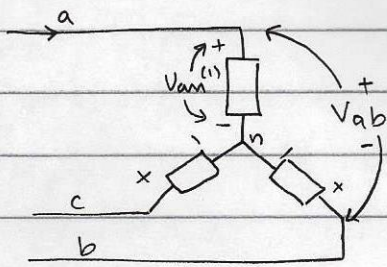


(+ve) sequence.

$$\begin{aligned} V_{ab}^{(1)} &= V_{an}^{(1)} + V_{nb}^{(1)} \\ &= V_{an}^{(1)} - V_{bn}^{(1)} \\ &= \sqrt{3} V_{an}^{(1)} \angle +30^\circ \end{aligned} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \text{+ve seq.}$$
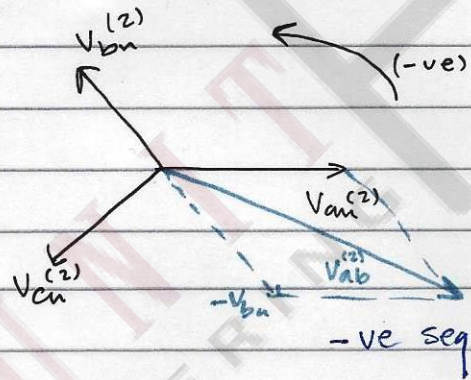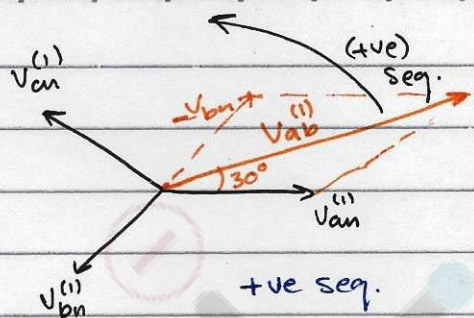
$$\begin{aligned} V_{ab}^{(2)} &= V_{an}^{(2)} + V_{nb}^{(2)} \\ &= V_{an}^{(2)} - V_{bn}^{(2)} \\ &= \sqrt{3} V_{an}^{(2)} \angle -30^\circ \end{aligned} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \text{-ve seq.}$$



* Δ-connected load:-

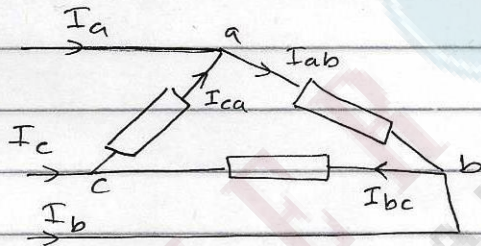


$$\begin{aligned} I_a + I_{ca} &= I_{ab} \\ \rightarrow I_a &= I_{ab} - I_{ca} \end{aligned}$$

for (+ve) seq.:

$$\begin{aligned} I_a^{(1)} &= I_{ab}^{(1)} - I_{ca}^{(1)} \\ I_a^{(1)} &= \sqrt{3} I_{ab}^{(1)} \angle -30^\circ \end{aligned}$$

for (-ve) seq.:
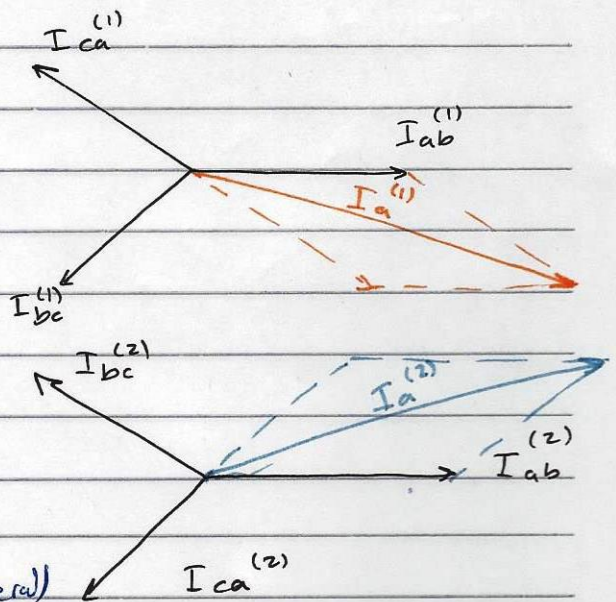
$$I_a^{(2)} = \sqrt{3} I_{ab}^{(2)} \angle +30^\circ$$



** $S = 3 V_a I_a^*$ (for a balanced sys.)

= $V_a I_a^* + V_b I_b^* + V_c I_c^*$ (in general)

eg:-

$V_a = 100 \angle 0^\circ$

$I_a = 10 \angle 60^\circ$

$S = 1000 \angle -60^\circ + 1000 \angle -60^\circ + 1000 \angle -60^\circ$

$V_b = 100 \angle -120^\circ$

$I_b = 10 \angle -60^\circ$

= $3 \times (1000 \angle -60^\circ)$

$V_c = 100 \angle -240^\circ$

$I_c = 10 \angle 180^\circ$

• 3-phase complex power:

→ for a balanced system:

$$S_{3\phi} = 3V_a I_a^*$$

→ for an unbalanced system:

$$S_{3\phi} = V_a I_a^* + V_b I_b^* + V_c I_c^*$$

in matrix form:

$$S_{3\phi} = \begin{bmatrix} V_a & V_b & V_c \end{bmatrix} \begin{bmatrix} I_a^* \\ I_b^* \\ I_c^* \end{bmatrix} \equiv \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix}^T \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}^* \quad \dots \textcircled{1}$$

→ transpose

remember:

$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} V_a^{(0)} \\ V_a^{(1)} \\ V_a^{(2)} \end{bmatrix} \\ \equiv [A] [V_{012}]$$

plug in $\textcircled{1}$

$$S_{3\phi} = \left([A] [V_{012}] \right)^T \left([A] [I_{012}] \right)^* \\ = \left([V_{012}]^T [A]^T \right) [A]^* [I_{012}]^* \quad \dots \textcircled{2}$$

$\rightarrow [A][B]^T \equiv [B]^T [A]^T$

$$\rightarrow [A]^T = [A]$$

$$\rightarrow [A]^* = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix}$$

$$\rightarrow A^T A^* = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \\ = \begin{bmatrix} 3 & 0 & 0 \\ 0 & 3 & 0 \\ 0 & 0 & 3 \end{bmatrix} \leftarrow 3A A^{-1} \\ \equiv 3I \leftarrow \text{Identity matrix}$$

$3A^{-1}$

plug in (2):

$$S_{3\phi} = 3 \begin{bmatrix} V_a^{(0)} & V_a^{(1)} & V_a^{(2)} \end{bmatrix} \begin{bmatrix} I_a^{*(0)} \\ I_a^{*(1)} \\ I_a^{*(2)} \end{bmatrix}$$

$$= \underbrace{3 V_a^{(0)} I_a^{*(0)}}_{\text{unit [VA]}} + 3 V_a^{(1)} I_a^{*(1)} + 3 V_a^{(2)} I_a^{*(2)} \quad \dots (3)$$

→ this term equals (0) when:-

1. it's a delta connected load.


2. it's a Y-connected load with an isolated neutral (not connected to earth).

each one of them is balanced, but the total system is unbalanced.

base: $3V_a I_a$

∴ in (3), p.u. $S_{3\phi}$:
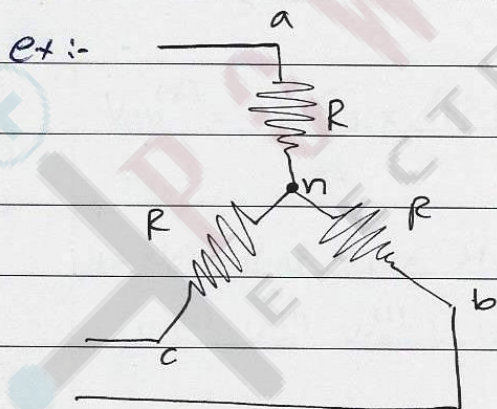
$$S_{3\phi} = V_a^{(0)} I_a^{*(0)} + V_a^{(1)} I_a^{*(1)} + V_a^{(2)} I_a^{*(2)} \quad [\text{p.u.}]$$



given: $|V_{ab}| = 1860V$ (+ve) sequence

$$|V_{bc}| = 2780V$$

$$|V_{ca}| = 2300V$$

find: $V_{an}^{(0)}$, $V_{an}^{(1)}$, $V_{an}^{(2)}$


Solution: $V_{ab}^{(0)} = 0$ (always) since $(V_{ab} + V_{bc} + V_{ca})$ forms a closed loop.

$$V_{ab}^{(1)} = \frac{1}{3}(V_{ab} + a V_{bc} + a^2 V_{ca})$$

I only have $|V|$, what to do?

1) first take a reference, let's say $V_{ca} = 2300 \angle 180^\circ$.

2)

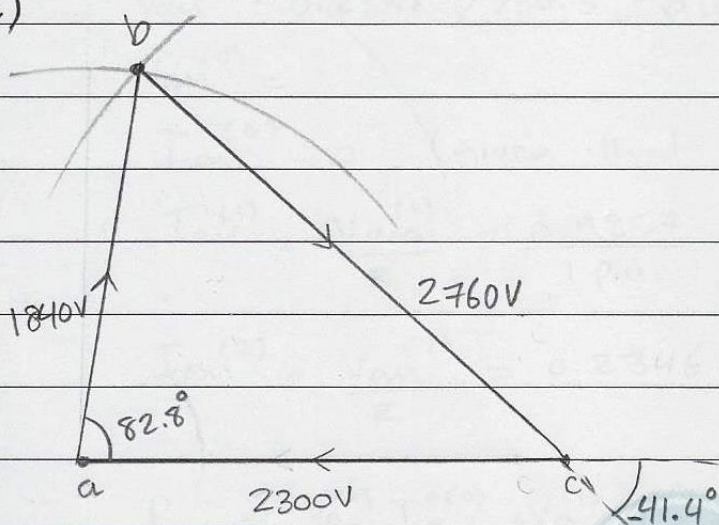

$$V_{ab} = 1840 \angle 82.8^\circ \text{ V}$$

$$V_{bc} = 2760 \angle -41.4^\circ \text{ V}$$

$$V_{ca} = 2300 \angle 180^\circ \text{ V}$$

$$400\text{V} : 1\text{cm}$$

→ choose base: 2300V, 300kVA

→ given that the ratings of the 3-ph load are: 2300V, 300kVA

$$\therefore R = 1.0 \text{ p.u.} \equiv \frac{(2300)^2}{500 \times 10^3} = 10.58 \Omega$$

$$V_{ab}^{(1)} = \frac{1}{3} (0.8 \angle 82.8^\circ + 1.2 \angle -41.4^\circ + 120^\circ + 1 \angle 180^\circ + 240^\circ) = 0.9857 \angle 73.6^\circ$$

$$V_{ab}^{(2)} = \frac{1}{3} (0.8 \angle 82.8^\circ + 1.2 \angle -41.4^\circ + 240^\circ + 1 \angle 180^\circ + 120^\circ) = 0.2346 \angle 220.3^\circ$$

** Note that since the system is (+ve) seq., the (+ve) seq component ($V_{ab}^{(1)}, V_{bc}^{(1)}, V_{ca}^{(1)}$) is stronger.

$$V_{ab}^{(1)} = \sqrt{3} V_{an}^{(1)} \angle +30^\circ$$

$$\therefore V_{an}^{(1)} = \frac{V_{ab}^{(1)}}{\sqrt{3}} \angle -30^\circ \text{ in Volts.}$$

$$V_{an}^{(1)} = V_{ab}^{(1)} \angle -30^\circ \text{ in p.u.}$$

$$\left(\begin{array}{l} \text{base: } 2300 \end{array} \right.$$

$$\rightarrow \text{base: } \frac{2300}{\sqrt{3}}$$

$$\therefore V_{an}^{(1)} = 0.9857 \angle 43.6^\circ \text{ p.u.} \quad (\text{base: } \frac{2300}{\sqrt{3}})$$

$$V_{an}^{(2)} = 0.2346 \angle 250.3^\circ \text{ p.u.} =$$

$$V_{an}^{(0)} = 0$$

$$I_{an}^{(0)} = 0 \quad (\text{given that neutral is isolated}).$$

$$I_{an}^{(1)} = \frac{V_{an}^{(1)}}{R} = \frac{0.9857}{1 \text{ p.u.}} \angle 43.6^\circ \text{ p.u.}$$

$$I_{an}^{(2)} = \frac{V_{an}^{(2)}}{R} = 0.2346 \angle 250.3^\circ \text{ p.u.}$$

$$P_{3\phi} = V_a^{(0)} I_a^{*(0)} + V_a^{(1)} I_a^{*(1)} + V_a^{(2)} I_a^{*(2)} \quad [\text{p.u.}]$$


↳ since it's a resistive load

$$= 0 + (0.9857)^2 + (0.2346)^2$$

$$= 1.02664 \text{ p.u.}$$


$$\equiv 1.02664 \times 500 \text{ kVA} = 513.32 \text{ kW}$$

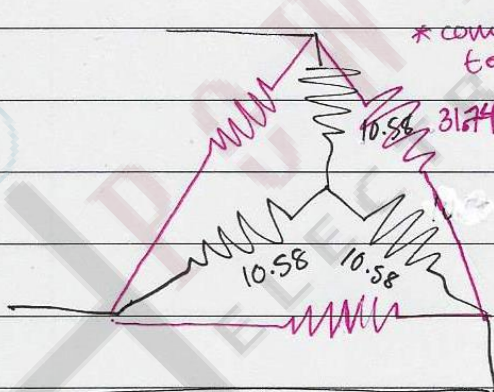We can solve this question using CKT I method!



$$P_{3\phi} = \frac{1840^2}{31.74} + \frac{2760^2}{31.74} + \frac{2300^2}{31.74} = 513.32 \text{ kW}$$

• now, consider a non-isolated neutral:

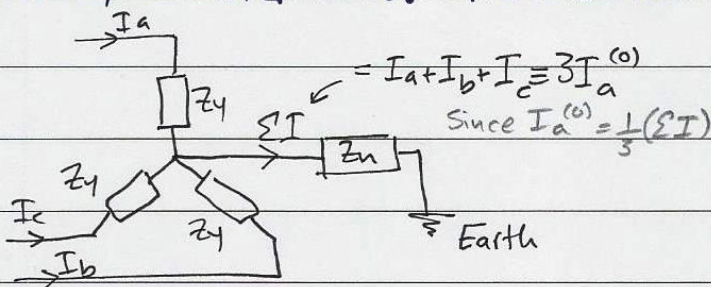

* the current flowing through (n) is a zero sequence current.

$$\begin{aligned} \Sigma I &= I_a^{(0)} + I_a^{(1)} + I_a^{(2)} \\ &+ I_b^{(0)} + I_b^{(1)} + I_b^{(2)} \\ &+ I_c^{(0)} + I_c^{(1)} + I_c^{(2)} \\ &= 3I_a^{(0)} + 0 + 0 \end{aligned}$$

* from now on $V_a \equiv V_{aE}$

"now E is my reference instead of n, where V_{nE} might not equal zero".

$$V_{nE} = 3I_a^{(0)} Z_n$$

$$\therefore V_{aE} = I_a Z_Y + (3I_a^{(0)} + Z_n)$$

$$V_{bE} = I_b Z_Y + (3I_a^{(0)} + Z_n)$$

$$V_{cE} = I_c Z_Y + (3I_a^{(0)} + Z_n)$$

even if it's not mentioned, it's there by default

$$(V_c \equiv V_{cE})$$

• for Y-connection:

$$[A]^{-1} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = Z_Y \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} + 3I_a^{(0)} Z_n \begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix}$$

$[A][V_{012}] \quad [A][I_{012}]$

$$[A]^{-1} [A] \begin{bmatrix} V_a^{(0)} \\ V_a^{(1)} \\ V_a^{(2)} \end{bmatrix} = Z_Y [A]^{-1} [A] \begin{bmatrix} I_a^{(0)} \\ I_a^{(1)} \\ I_a^{(2)} \end{bmatrix} + 3I_a^{(0)} Z_n \times \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix}$$



$$\begin{bmatrix} V_a^{(0)} \\ V_a^{(1)} \\ V_a^{(2)} \end{bmatrix} = Z_Y \begin{bmatrix} I_a^{(0)} \\ I_a^{(1)} \\ I_a^{(2)} \end{bmatrix} + 3I_a^{(0)} Z_n \begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix}$$

$$V_a^{(0)} = I_a^{(0)} [Z_Y + 3Z_n]$$



$$V_a^{(1)} = I_a^{(1)} Z_Y$$

$$V_a^{(2)} = I_a^{(2)} Z_Y$$


equivalent CKT:

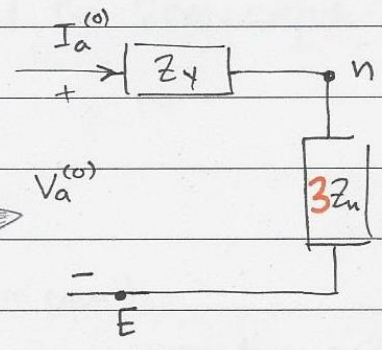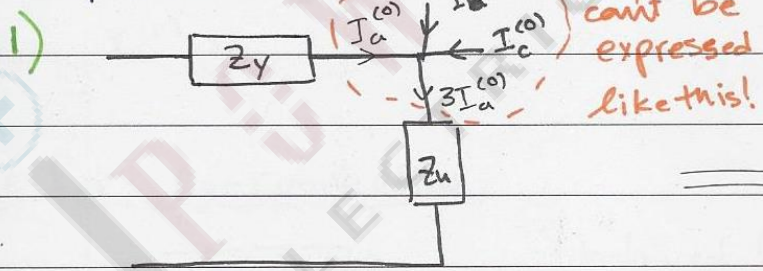

Zero sequence Network.


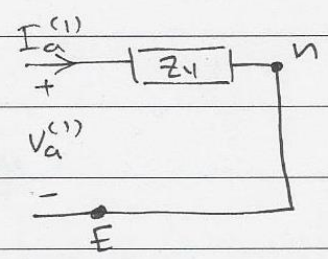
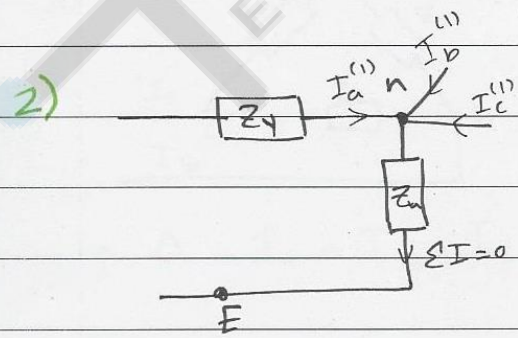


Positive sequence network.

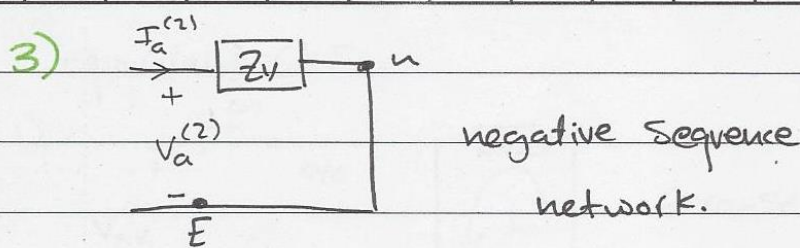

* the same is applied for phases B & C.

3-phase equivalent:

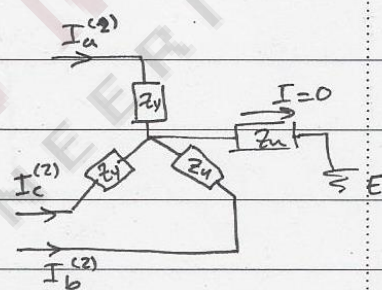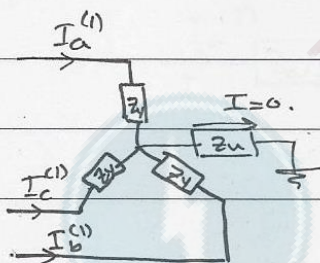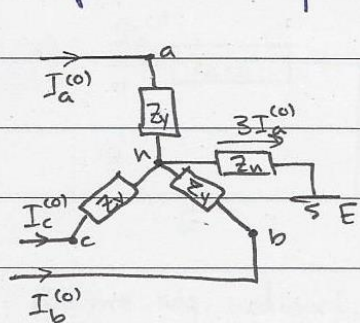

$$V_a^{(0)} = I_a^{(0)} [Z_y + 3Z_n]$$

Zero-seq.

$$V_a^{(1)} = I_a^{(1)} Z_y$$

+ve-seq.


$$V_a^{(2)} = I_a^{(2)} Z_y$$

-ve-seq.

** Isolating the neutral will affect the zero-sequence only

$$I_a^{(0)} = 0$$

• for Δ -connection:

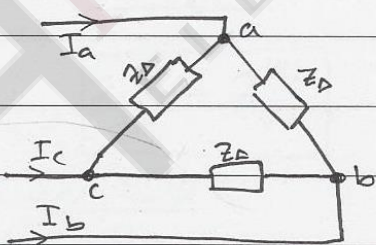


balanced (Z_s are equal).

V aren't balanced $\rightarrow \therefore$ currents aren't balanced also

in Δ , $I_a + I_b + I_c = 0$ always

equivalent CKT:

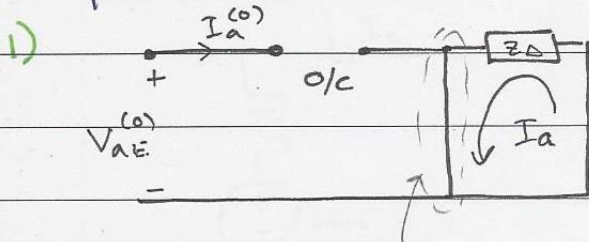


zero-seq. network.


بعض الحالات يكون

mutual inductance, في transformer, ...

بقدر بعضه فيه بين الـ phases

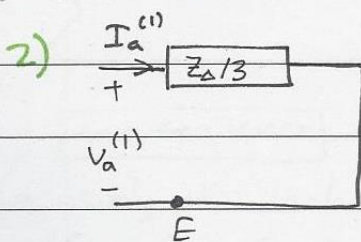


positive-seq. network.

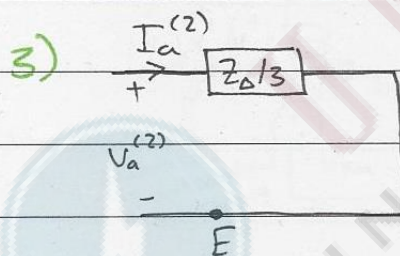

negative-seq. network.

$V_a^{(1)}, V_b^{(1)}, V_c^{(1)}$ are star connected
 $V_a^{(2)}, V_b^{(2)}, V_c^{(2)}$

for transmission line:

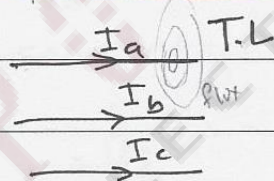

flux linkage

$$k_a^{(1)} = \frac{\Psi_a^{(1)}}{I_a^{(1)}}$$

$$Z_{T.L.}^{(1)} = Z_{T.L.}^{(2)}$$

$$X_1 = X_2$$

$$X_0 = (2 - 3.5) X_1$$




range.

$$\Psi_a = \sum \phi$$

for zero seq.:


+ve seq.

-ve seq.

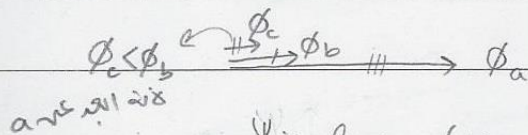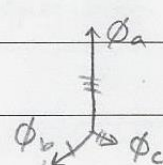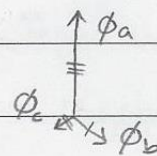

Ψ is higher (they add up)
 $\therefore l$ is higher


• for generator:

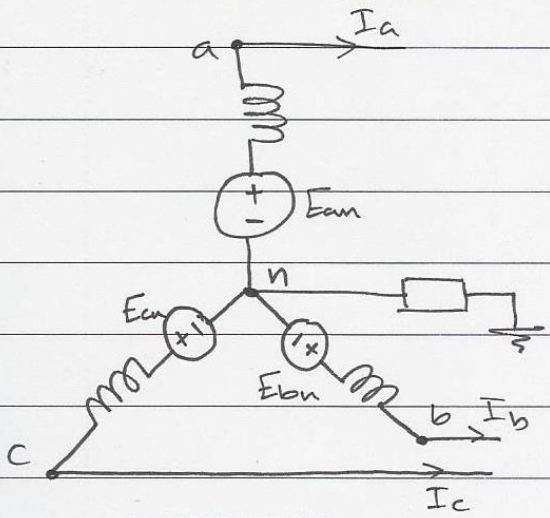


+ve sequence

usually it's balanced
 $(E_{an} = E_{bn} = E_{cn})$



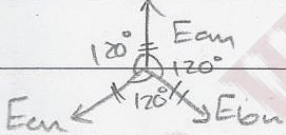
* a perfectly designed generator generates only +ve seq. V's with $\Delta\theta = 120^\circ$ between adjacent phases.



* the same CKTs apply for phases B & C.

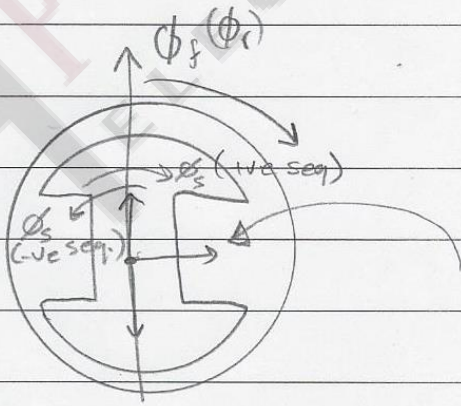

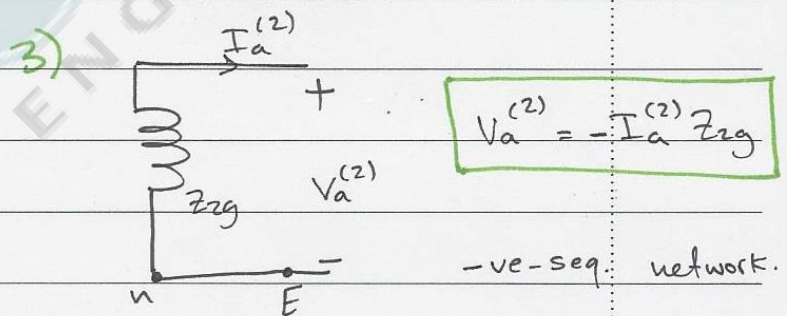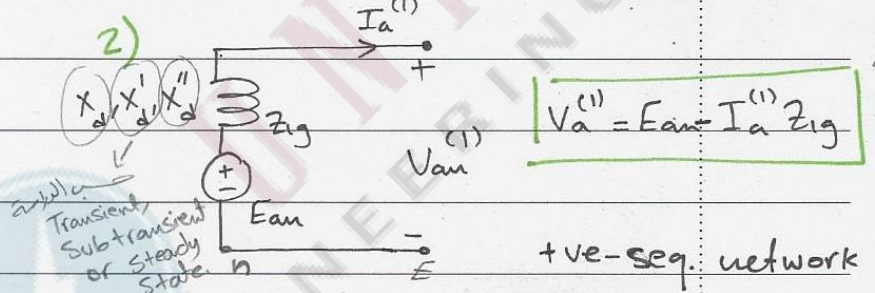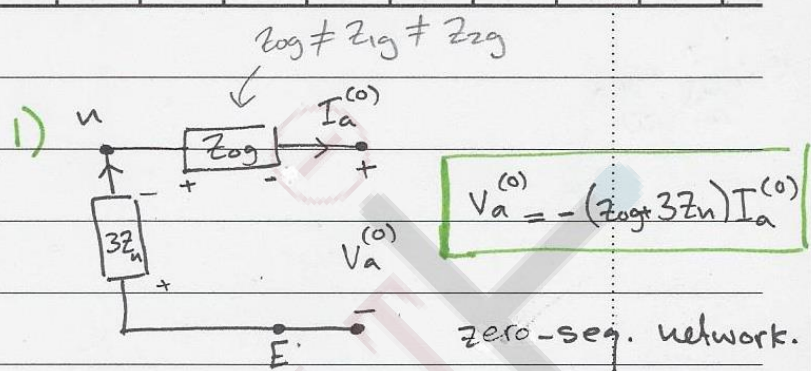ϕ_{ar} P.F. = 0 leading.
 ← magnetizing
 ϕ_{ar} (unity P.F.) cross magnetizing.
 ← demagnetizing
 ϕ_{ar} zero lagging P.F.



Lecture #34

Subject 6/5/2014

Date

No.




for +ve seq. current



for -ve seq. current
(Φ_s will flip).

- * for +ve seq: Φ_s is in the same direction of rotor's rotation (بشرفه ال rotor)
- * for -ve seq: Φ_s is in the opposite direction of rotor's rotation, \therefore its relative velocity is doubled. which will induce current in the field winding, damper winding, & rotor body. thus, rotor will heat up.

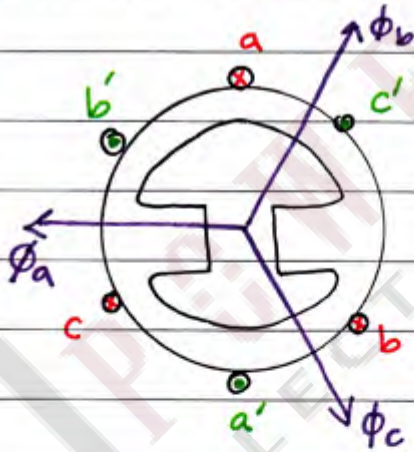• Armature reaction is weak for (-ve) seq. current, thus $Z_{2g} \approx X_d'' = X_L$



$$|\Phi_a| = |\Phi_b| = |\Phi_c| \text{ since } I_a^{(0)} = I_b^{(0)} = I_c^{(0)}$$

$$\therefore \Phi_a + \Phi_b + \Phi_c = 0$$


thus, zero-seq. current doesn't introduce any armature reaction.

(spacing between adjacent phases = 120°)

for zero-seq. current

$X_{2og} \approx X_d'$ (direct axis subtransient reactance).

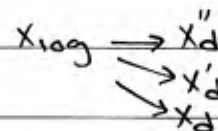$X_{og} = X_L$ (exactly). (no armature reaction).



* if we assumed no damper windings X_{2og} will increase.

** induced voltages E_{an}, E_{bn}, E_{cn} appears only in one sequence. (+ve or -ve)

↳ (مربط بالظلال في 30%) System

ex: 3-phase generator, without damper windings, Rated 20MVA, 13.8kV, $X_d'' = 0.25$ p.u., $E_{an} = 1 \angle 0^\circ$ p.u.

$X_{og} = 0.1$ p.u., $Z_n = 0$ (gen. is solidly grounded)

$X_{2g} = 0.35$ p.u. (since it's without damping $X_{2g} \approx X_d''$)

initially unloaded.


after fault:-

$V_{af} = 0$

$V_{bf} = 1.013 \angle -102.25^\circ$

$V_{cf} = 1.013 \angle 102.25^\circ$

$I_a = ?$

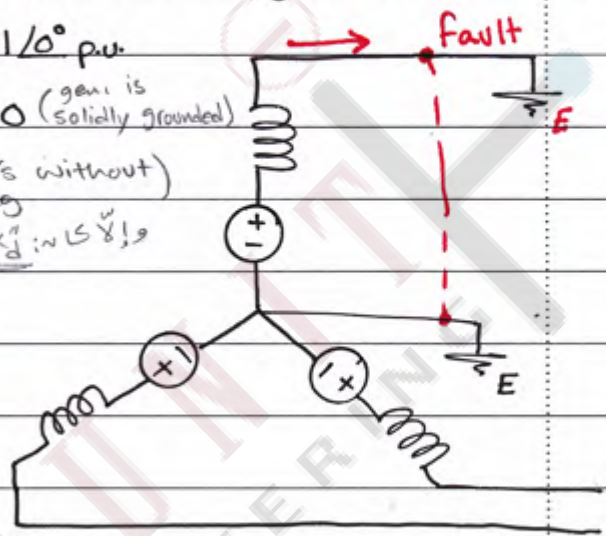

Solution:

$I_b = 0, I_c = 0$

$$\begin{bmatrix} V_a^{(0)} \\ V_a^{(1)} \\ V_a^{(2)} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix}$$

$V_b = 1.013 \angle -102.25^\circ$
 $V_c = 1.013 \angle 102.25^\circ$

$$= \begin{bmatrix} -0.143 \\ 0.643 \\ -0.5 \end{bmatrix} \leftarrow V_a^{(0)} + V_a^{(1)} + V_a^{(2)} = 0 \equiv V_a \neq$$

$V_a^{(0)} = -I_a^{(0)} * j0.1$

$I_a^{(0)} = -j1.43$ p.u.

$V_a^{(1)} = E_{an} - I_a^{(1)} Z_1$

$0.643 = 1 \angle 0^\circ - I_a^{(1)} * j0.25$

$I_a^{(1)} = -j1.43$ p.u.

$V_a^{(2)} = -I_a^{(2)} Z_2$

$I_a^{(2)} = -j1.43$ p.u.

* $I_a^{(0)} = I_a^{(1)} = I_a^{(2)}$

this always hold in a single phase to earth fault (we'll prove it later).




$$I_a = I_a^{(0)} + I_a^{(1)} + I_a^{(2)} = -j1.43 \times 3 = -j4.29 \text{ p.u.}$$

$$\text{base current} = \frac{20 \times 10^6}{\sqrt{3} \times 13.8 \times 10^3} \text{ A}$$


$$V_{ab} = V_{ac} - V_{bc} = 0 - 1.013 \angle -102.25^\circ = 1.013 \angle 77.75^\circ \text{ p.u.}$$

• Sequence CKTs of transformer:-

• Y-Y transformer:-

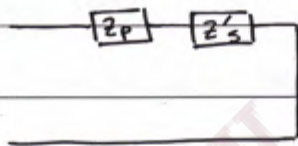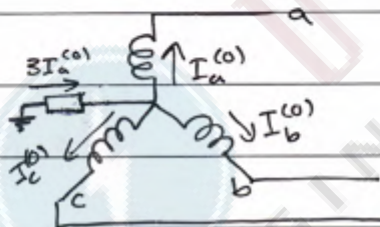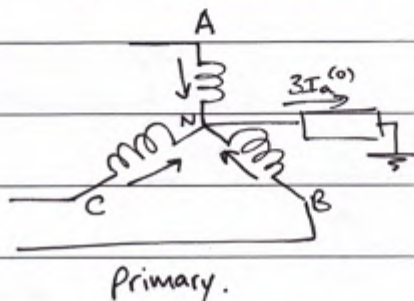

equivalent CKT for +ve & -ve seq.

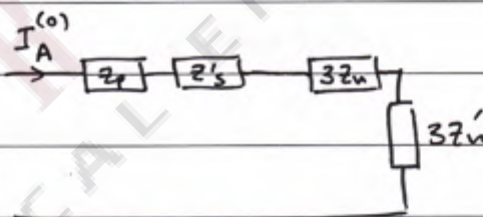


equ. CKT for zero. sequence.

• if neutral (N) is opened : $I_A^{(0)} = 0 \rightarrow \therefore I_a^{(0)} = 0$


• if $z_w = \infty$: $I_A^{(0)} = 0 \rightarrow \therefore I_a^{(0)} = 0$

Δ transformer sequence ckt's:

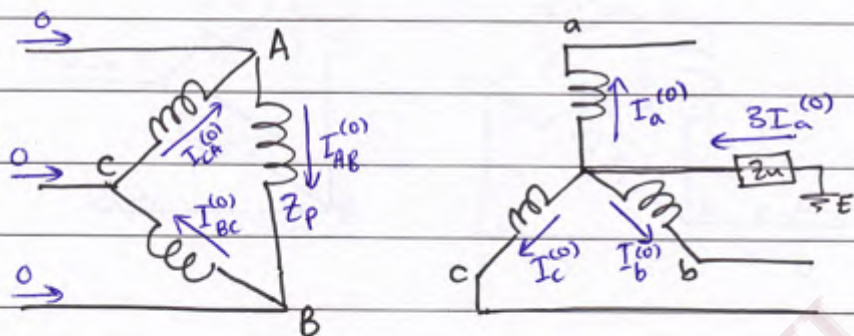
" zero-seq. لا يتركب من الاقسام الاثلاثية +ve seq. لا يتكون من اقل من اثنين فلا يتركب من الاقسام الاثلاثية "




* zero-seq equivalent ckt:

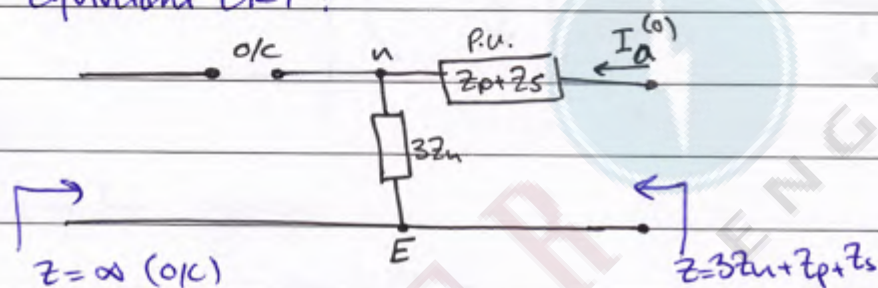



→ if (n) was short-circuited:

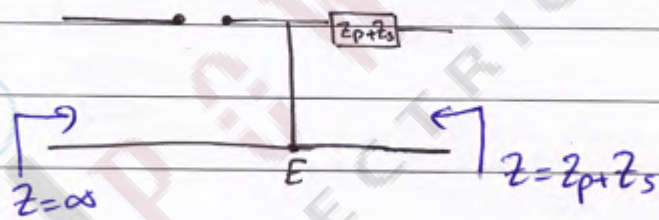

→ if (n) was isolated (o/c):

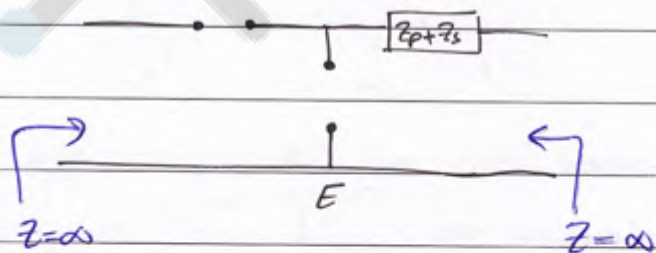


Δ-Δ transformer:-

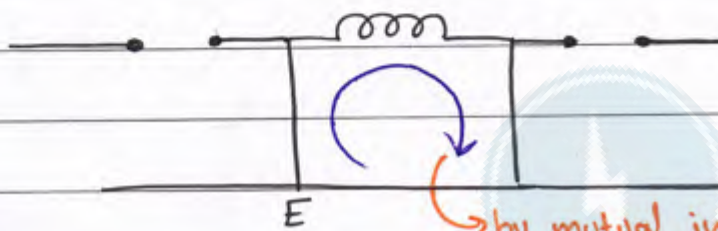
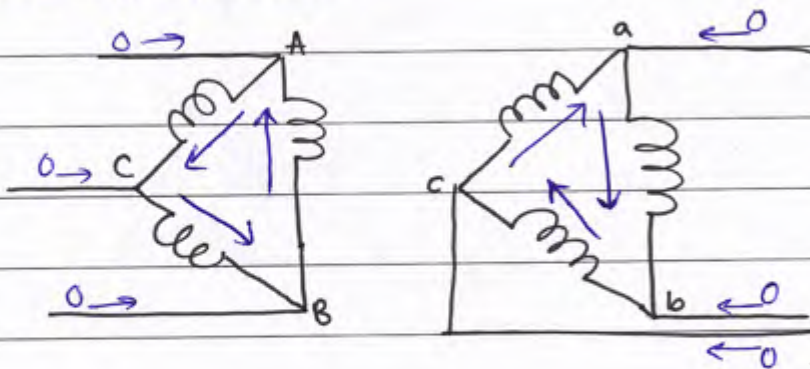


equ. CKT for zero seq. by mutual inductance.


Vector group

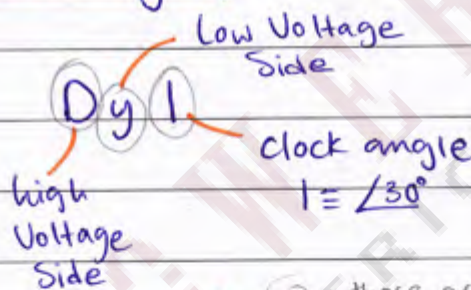

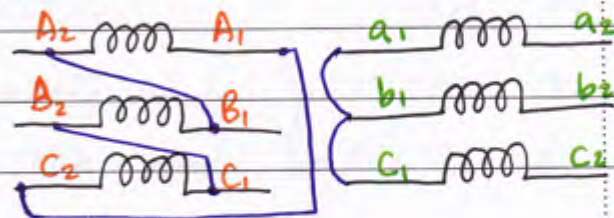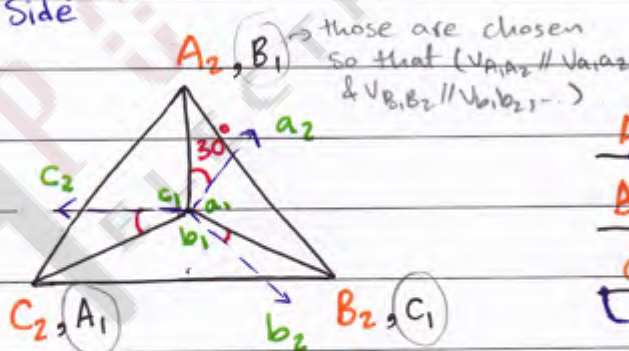this angle is between the equivalent Y for H.V side & the L.V side. (considering +ve sequence)
 • two seq. balancing



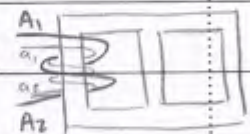• (a_1, a_2) & (A_1, A_2) are both wound on the same limb
 thus, $(V_{a_1 a_2} \text{ \& } V_{A_1 A_2})$ are in-phase.




"تلف ال L.V حوّل ال H.V"
 "لدى ال E حوّل ال E حوّل"
 "أطال ال (leakage flux)"

$V_{AN}^{(1)} = \underline{V_{an}^{(1)}} \angle +30^\circ \text{ p.u. (for +ve seq.)}$
 magnitude is the same in phase

but they have different bases.

for -ve seq:




الترتيب يكون عكس اتجاه عقارب الساعة

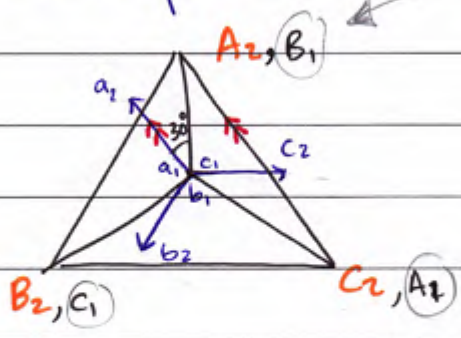

$$V_{AN}^{(2)} = V_{an}^{(2)} \angle -30^\circ \text{ p.u.}$$

Dy11

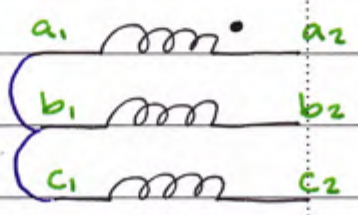
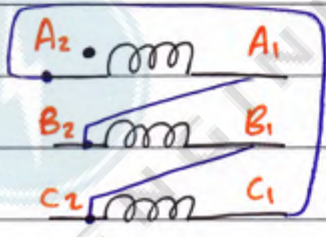
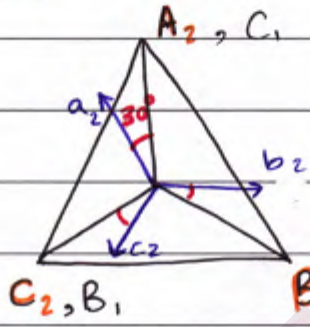
كل طور في secondary لا يتم كلهم نفس النوع و يكون Dy11 Dy1



$$V_{AN}^{(1)} = V_{an}^{(1)} \angle -30^\circ \text{ p.u. (for +ve)}$$



$$V_{AN}^{(2)} = V_{an}^{(2)} \angle +30^\circ \text{ p.u. (for -ve)}$$

Yy0

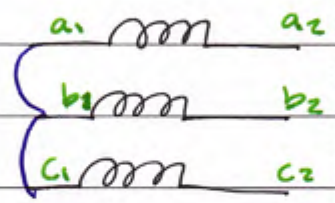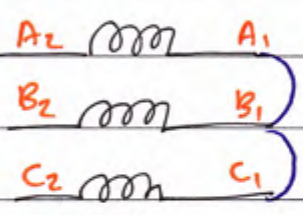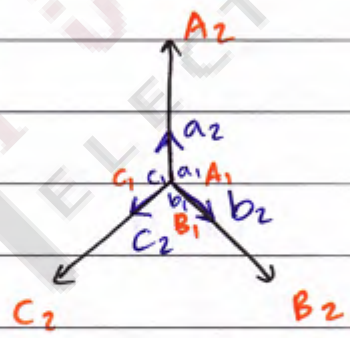

$$V_{AN}^{(1)} = V_{an}^{(1)} \text{ p.u.}$$

Yy6

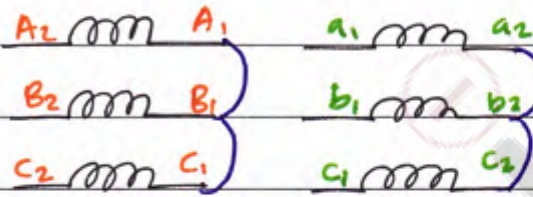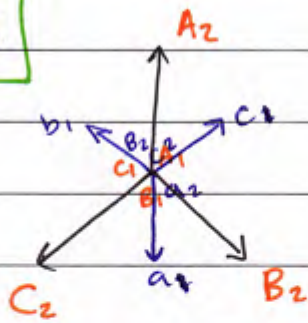

$$V_{AN}^{(1)} = V_{an}^{(1)} / 180^\circ \text{ p.u.}$$



$$V_{AN}^{(2)} = V_{an}^{(2)} / 180^\circ \text{ p.u.}$$

Yy9 → can't be made.

Dy5 → the same as Dy11 (just take the output from a₁, b₁, c₁ in secondary instead of a₂, b₂, c₂).

the same for Dy7 & Dy1


Yd11

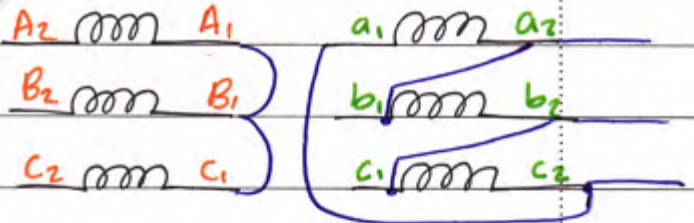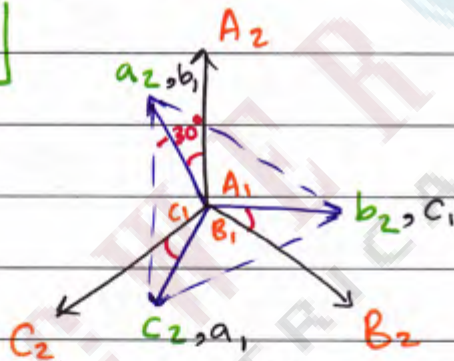

$$V_{AN}^{(1)} = V_{an}^{(1)} / -30^\circ \text{ p.u.}$$


$$V_{AN}^{(2)} = V_{an}^{(2)} / +30^\circ \text{ p.u.}$$

for -ve seq:

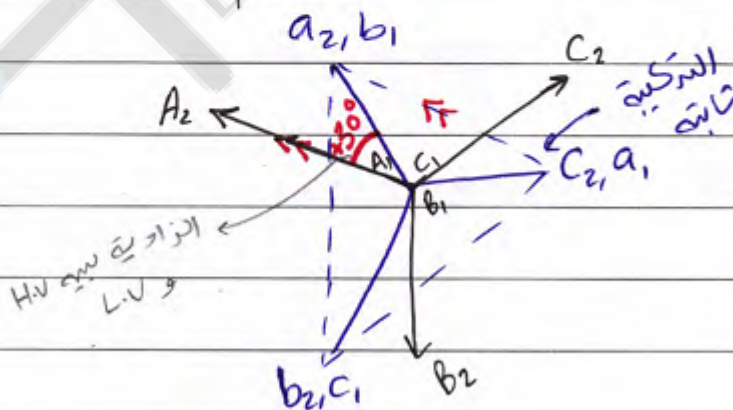

connected to diagram.

Previous ex:

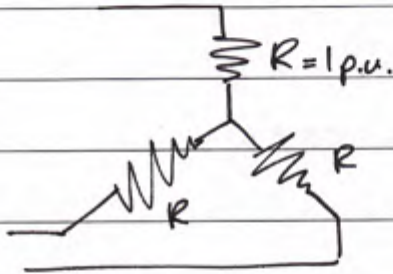

$$V_{ab} = 0.8 \angle 82.8^\circ \text{ p.u.}$$

$$V_{bc} = 1.2 \angle -41.4^\circ \text{ p.u.}$$



$$V_{ca} = 1 \angle 180^\circ \text{ p.u.}$$

$$I_{an}^{(1)} = \frac{V_{an}^{(1)}}{1 \text{ p.u.}} = 0.9856 \angle 43.6^\circ$$

$$\frac{V_{an}^{(2)}}{1 \text{ p.u.}} = I_{an}^{(2)} = 0.2346 \angle 250.3^\circ$$

if we add a Dy1 transformer

(13.2/2.3) kV

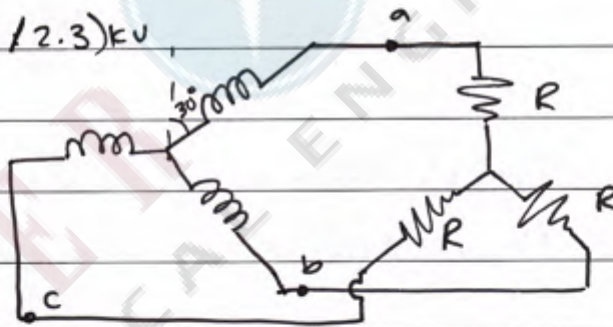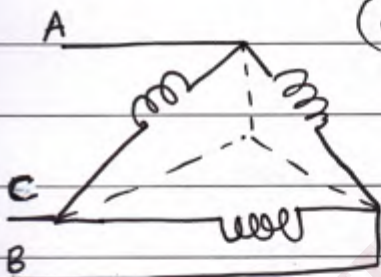


$$\text{Dy1 : } V_{AN}^{(2)} = V_{an}^{(2)} \angle -30^\circ \text{ p.u.}$$

$$V_{AN}^{(1)} = V_{an}^{(1)} \angle +30^\circ \text{ p.u.}$$

↳ reference $(\frac{2300}{\sqrt{3}})$

$$V_{AN}^{(1)} = 0.9856 \angle 43.6^\circ + 30^\circ \text{ p.u.}$$

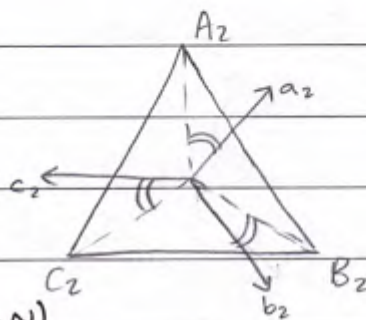↳ its base is $\frac{13200}{\sqrt{3}}$ (base L-N)



$$V_{AN}^{(2)} = 0.2346 \angle 250.3^\circ - 30^\circ \text{ (Base L-N)}$$

$$\text{↳ base} = \frac{13200}{\sqrt{3}}$$

$$V_{AN}^{(0)} = 0$$


$$V_{AN} = V_{AN}^{(0)} + V_{AN}^{(1)} + V_{AN}^{(2)} \equiv V_{AE} \quad \text{since in this ex. } V_{NC} = 0$$

$$= \boxed{0.8 \angle 82.8^\circ} \equiv V_{ab} \text{ (p.u.)}$$

$$V_B = V_B^{(1)} + V_B^{(2)} + V_B^{(0)}$$

$$= (0.9857 \angle 73.6^\circ) a^2 + (0.2346 \angle 220.3^\circ) a + 0$$
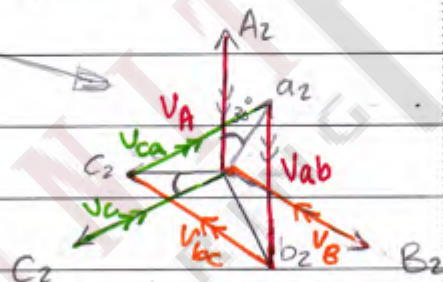
$$= \boxed{1.2 \angle -41.4^\circ} \equiv V_{bc} \text{ (p.u.)}$$



$$V_{AB} = V_{AE} - V_{BE}$$

$$= 0.8 \angle 82.8^\circ - 1.2 \angle -41.4^\circ$$

$$= 1.78 \angle 116.8^\circ \text{ (L-N, } \frac{13200}{\sqrt{3}})$$


also

$$\equiv \frac{1.78}{\sqrt{3}} \angle 116.8^\circ \text{ (L-L, } 13200)$$

$$V_{BC} = V_{BE} - V_{CE} = \dots = 2.09 \angle -27.7^\circ \text{ (L-N)}$$

$$V_{CA} = V_{CE} - V_{AE} = \dots = 1.356 \angle 215.8^\circ \text{ (L-N)}$$

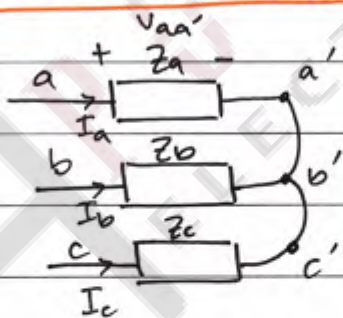• for an unbalanced load ($Z_a \neq Z_b \neq Z_c$) (general case).



$$\begin{pmatrix} V_{aa'} \\ V_{bb'} \\ V_{cc'} \end{pmatrix} = \begin{bmatrix} Z_a & 0 & 0 \\ 0 & Z_b & 0 \\ 0 & 0 & Z_c \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} \quad \text{pre-multiply by } [A]^{-1}$$

$$[A]^{-1} [A] \begin{bmatrix} V_{aa'}^{(0)} \\ V_{aa'}^{(1)} \\ V_{aa'}^{(2)} \end{bmatrix} = [A]^{-1} \begin{bmatrix} Z_a & 0 & 0 \\ 0 & Z_b & 0 \\ 0 & 0 & Z_c \end{bmatrix} [A] \begin{bmatrix} I_a^{(0)} \\ I_a^{(1)} \\ I_a^{(2)} \end{bmatrix}$$

unity matrix

$$\begin{bmatrix} V_{aa'}^{(0)} \\ V_{aa'}^{(1)} \\ V_{aa'}^{(2)} \end{bmatrix} = \mathbf{A}^{-1} \begin{bmatrix} Z_a & 0 & 0 \\ 0 & Z_b & 0 \\ 0 & 0 & Z_c \end{bmatrix} \begin{bmatrix} I_a^{(0)} \\ I_a^{(1)} \\ I_a^{(2)} \end{bmatrix}$$

$$V_{aa'}^{(0)} = \frac{1}{3} I_a^{(0)} (Z_a + Z_b + Z_c) + \frac{1}{3} I_a^{(1)} (Z_a + a^2 Z_b + a Z_c) + \frac{1}{3} I_a^{(2)} (Z_a + a Z_b + a^2 Z_c)$$

$$V_{aa'}^{(1)} = \frac{1}{3} I_a^{(0)} (Z_a + a Z_b + a^2 Z_c) + \frac{1}{3} I_a^{(1)} (Z_a + Z_b + Z_c) + \frac{1}{3} I_a^{(2)} (Z_a + a^2 Z_b + a Z_c)$$

$$V_{aa'}^{(2)} = \frac{1}{3} I_a^{(0)} (Z_a + a^2 Z_b + a Z_c) + \frac{1}{3} I_a^{(1)} (Z_a + a Z_b + a^2 Z_c) + \frac{1}{3} I_a^{(2)} (Z_a + Z_b + Z_c)$$

for a balanced load: $Z_a = Z_b = Z_c = Z_y$

$$\begin{aligned} V_{aa'}^{(0)} &= I_a^{(0)} Z_a \\ V_{aa'}^{(1)} &= I_a^{(1)} Z_a \\ V_{aa'}^{(2)} &= I_a^{(2)} Z_a \end{aligned}$$

→ in this case each voltage (+ve, -ve, zero) creates 3 seq. current (+ve, -ve, zero)! complicated!


∴ if $Z_a \approx Z_b \approx Z_c$ I neglect the difference & consider them equal.

Summary:




- for generator: $X_{1g} : X''_d \text{ or } X'_d \text{ or } X_d$
 $X_{2g} \approx X''_d$ (if no damper winding exists $\rightarrow X_{2og} \approx X''_d$)
 X_{og} is different.

- for T.L: $Z_1 = Z_2$
 Z_0 differs due to flux linkage difference = $(2 \sim 3.5) X_1$


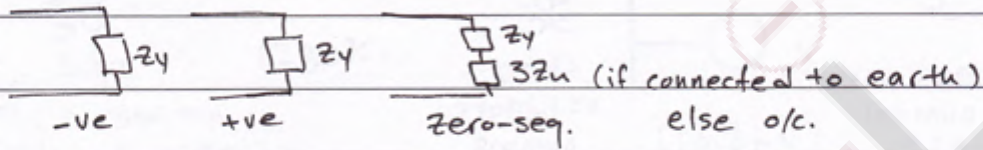
• for load: assume $Z_a = Z_b = Z_c = Z_Y$




ex:

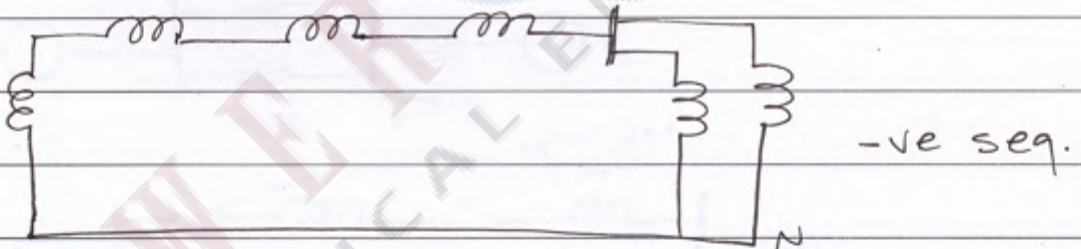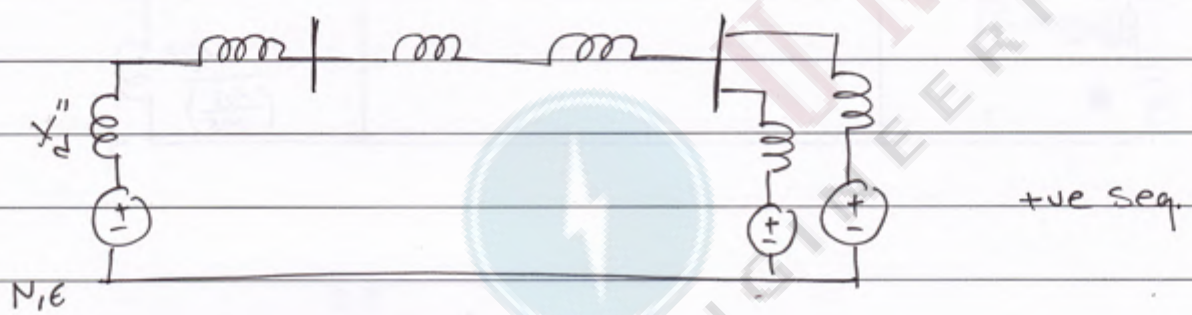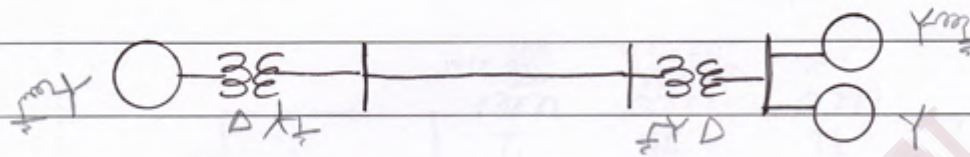


ex: (cont.)

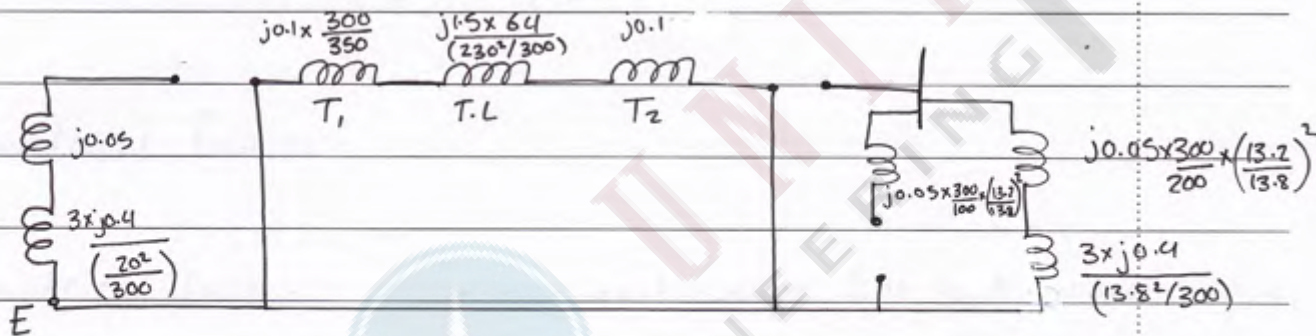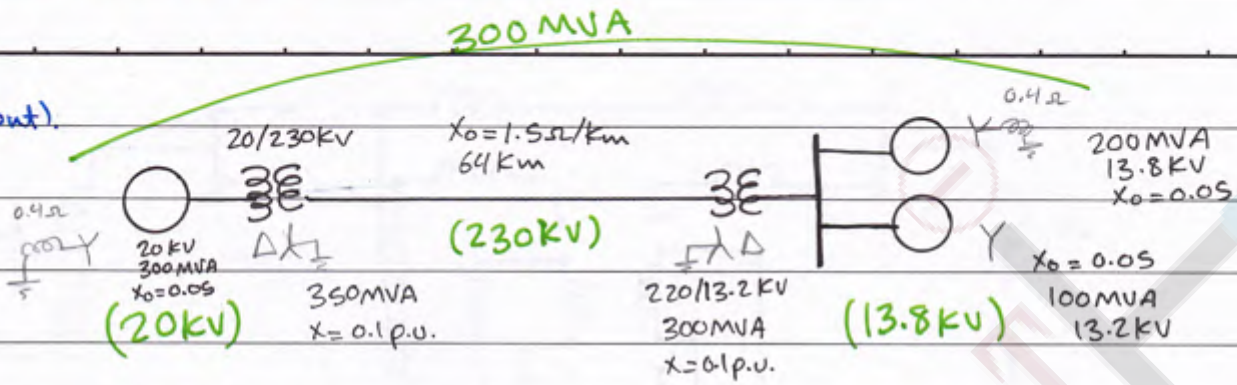


ex 2:

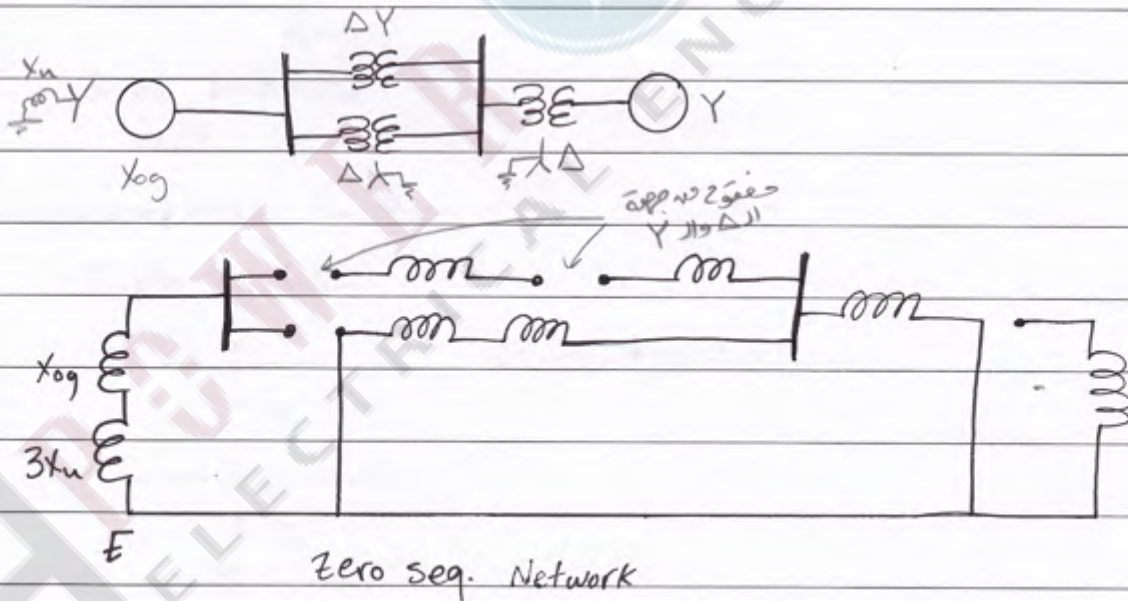

ex 3:

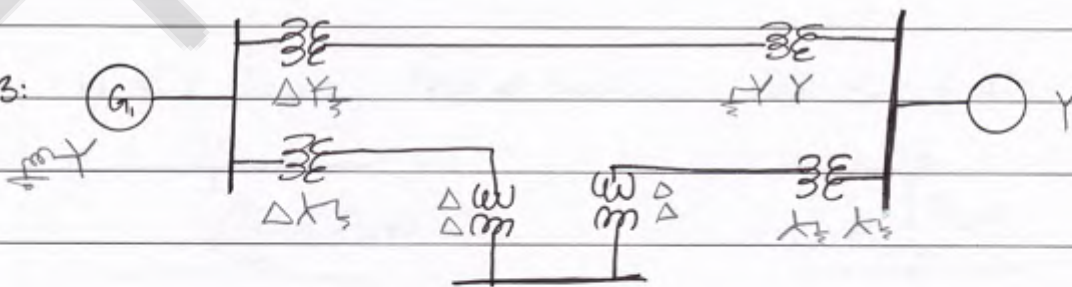


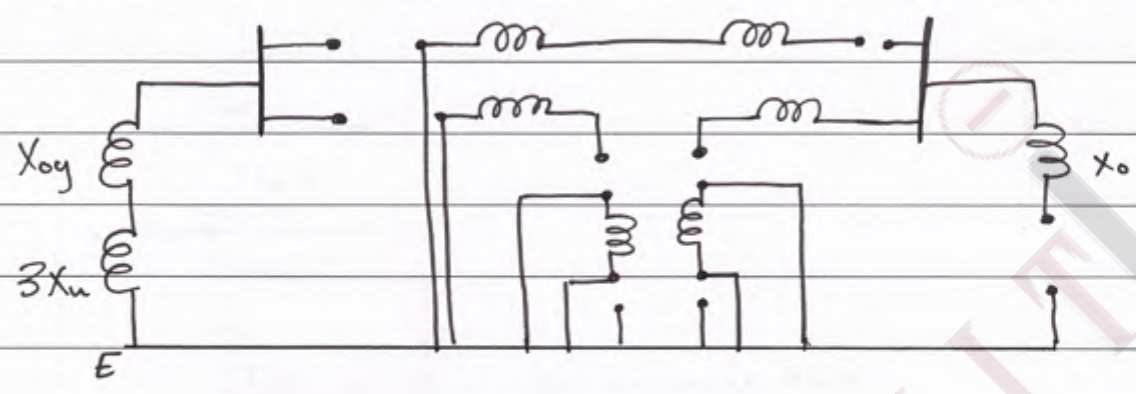

• Unsymmetrical faults:-

→ Symmetrical fault:-

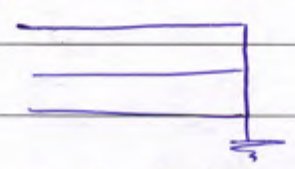* the most severe fault that might happen (worst case scenario).
 "إذا حدثت في النظام (System) أسوأ حالة، فيفضل أن تكون غير متماثلة".




3-ph balanced fault

* نادرا ما يحدث

→ Unsymmetrical faults:-



3-ph system:

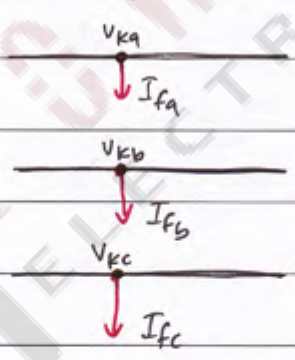


"عن الفولتية تقريبا 90%"

1) P-E fault: (85% of faults).

2) P-P fault

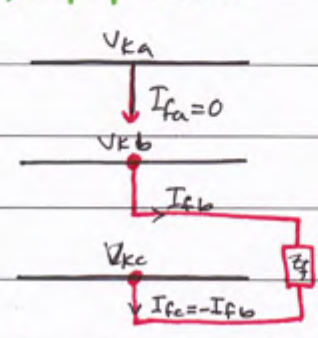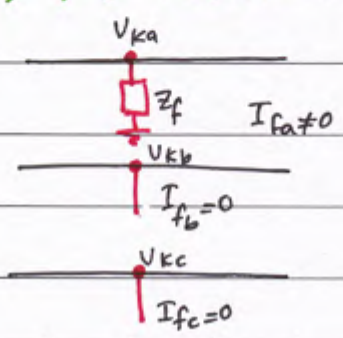


3) P-P-E Fault:

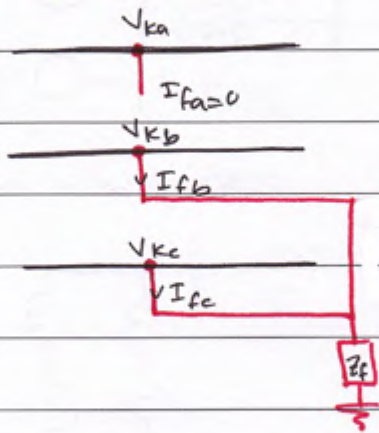

this impedance limits the current, so some times we assume it zero to consider the worst case scenario.

4) damaged jumper or fuse (open CT).

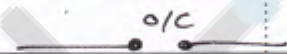

فستكون التيار صفر
فانتيقن ان
تيارات الخلف

لا حظ انه دائما اقلنا phase a
يكون هو المختلف

$$I_{fa} = I_{fa}^{(0)} + I_{fa}^{(1)} + I_{fa}^{(2)}$$

$$I_{fb} = I_{fb}^{(0)} + I_{fb}^{(1)} + I_{fb}^{(2)}$$

$$I_{fc} = I_{fc}^{(0)} + I_{fc}^{(1)} + I_{fc}^{(2)}$$


in symm. fault $V_j = V_f - \frac{Z_{jk}}{Z_{kk}} V_f$

now:


$$V_{ja} = V_{ja}^{(0)} + V_{ja}^{(1)} + V_{ja}^{(2)}$$

$$V_{jb} = V_{jb}^{(0)} + V_{jb}^{(1)} + V_{jb}^{(2)}$$


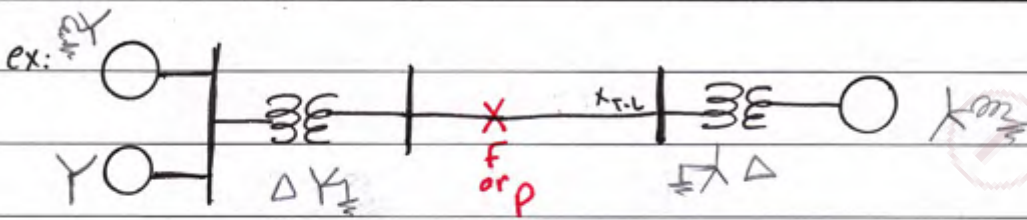
$$V_{jc} = V_{jc}^{(0)} + V_{jc}^{(1)} + V_{jc}^{(2)}$$



3 equivalent CKTs:

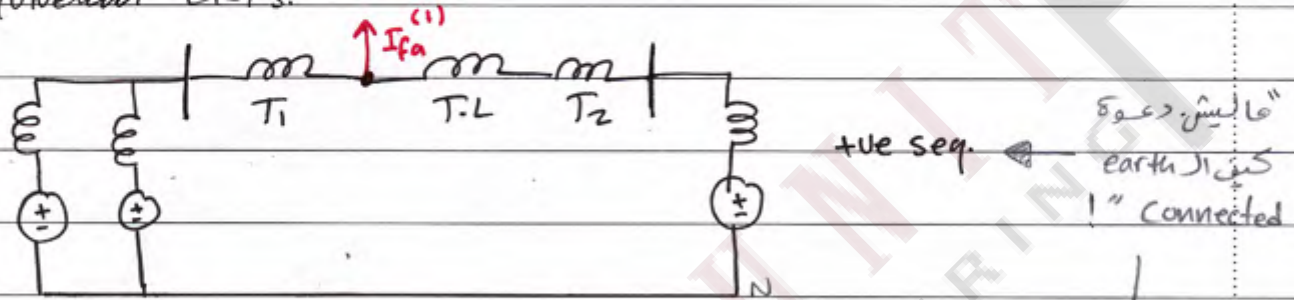

Sources are short-circuited

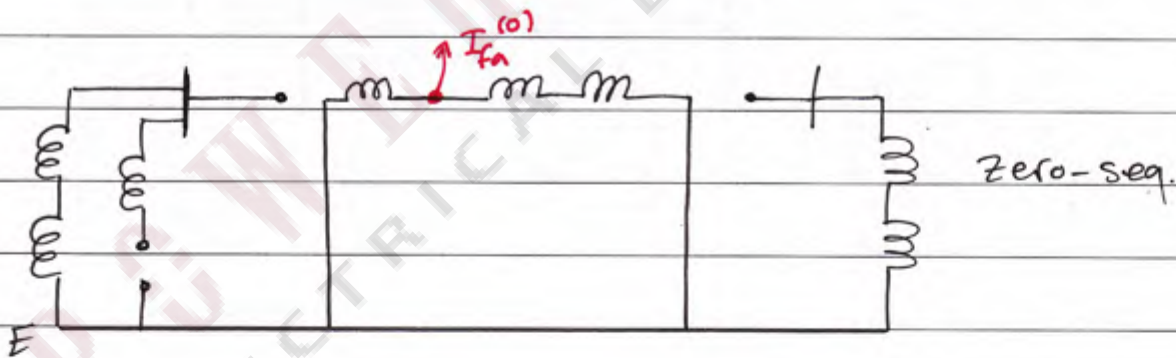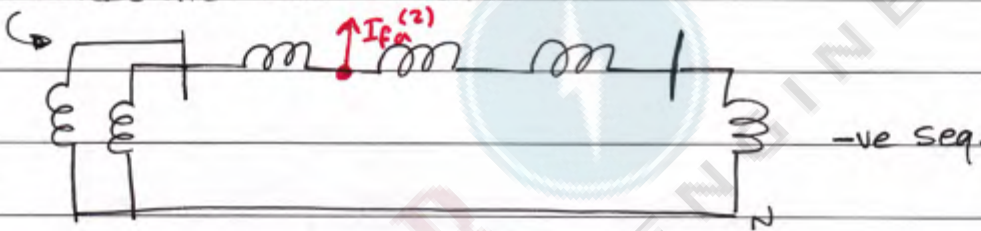

We'll use Z_{bus} method. ($3(Z_{bus})s$) $Z_{bus}^{(0)}$, $Z_{bus}^{(1)}$, $Z_{bus}^{(2)}$

$$Z_{bus}^{(1)} = \begin{bmatrix} Z_{11}^{(1)} & Z_{12}^{(1)} & \dots & Z_{1K}^{(1)} & \dots & Z_{1N}^{(1)} \\ Z_{21}^{(1)} & Z_{22}^{(1)} & \dots & Z_{2K}^{(1)} & \dots & Z_{2N}^{(1)} \\ \vdots & \vdots & \ddots & \vdots & \ddots & \vdots \\ Z_{K1}^{(1)} & Z_{K2}^{(1)} & \dots & Z_{KK}^{(1)} & \dots & Z_{KN}^{(1)} \\ \vdots & \vdots & \ddots & \vdots & \ddots & \vdots \\ Z_{N1}^{(1)} & Z_{N2}^{(1)} & \dots & Z_{NK}^{(1)} & \dots & Z_{NN}^{(1)} \end{bmatrix}$$

$$Z_{bus}^{(2)} = \begin{bmatrix} Z_{11}^{(2)} & Z_{12}^{(2)} & \dots & Z_{1K}^{(2)} & \dots & Z_{1N}^{(2)} \\ Z_{21}^{(2)} & Z_{22}^{(2)} & \dots & Z_{2K}^{(2)} & \dots & Z_{2N}^{(2)} \\ \vdots & \vdots & \ddots & \vdots & \ddots & \vdots \\ Z_{K1}^{(2)} & Z_{K2}^{(2)} & \dots & Z_{KK}^{(2)} & \dots & Z_{KN}^{(2)} \\ \vdots & \vdots & \ddots & \vdots & \ddots & \vdots \\ Z_{N1}^{(2)} & Z_{N2}^{(2)} & \dots & Z_{NK}^{(2)} & \dots & Z_{NN}^{(2)} \end{bmatrix}$$

from +ve seq. network.

from -ve seq. network.

$$Z_{bus}^{(0)} = \begin{bmatrix} Z_{11}^{(0)} & Z_{12}^{(0)} & \dots & Z_{1K}^{(0)} & \dots & Z_{1N}^{(0)} \\ Z_{21}^{(0)} & Z_{22}^{(0)} & \dots & Z_{2K}^{(0)} & \dots & Z_{2N}^{(0)} \\ \vdots & \vdots & \ddots & \vdots & \ddots & \vdots \\ Z_{K1}^{(0)} & Z_{K2}^{(0)} & \dots & Z_{KK}^{(0)} & \dots & Z_{KN}^{(0)} \\ \vdots & \vdots & \ddots & \vdots & \ddots & \vdots \\ Z_{M1}^{(0)} & Z_{M2}^{(0)} & \dots & Z_{MK}^{(0)} & \dots & Z_{MN}^{(0)} \end{bmatrix}$$

$V_{th} \rightarrow$ only in +ve seq.


\therefore first solution:-

$$V_{ja}^{(1)} = V_f, \quad V_{ja}^{(2)} = 0, \quad V_{ja}^{(0)} = 0$$


lecture #38

15/5/2014


Solution #1:

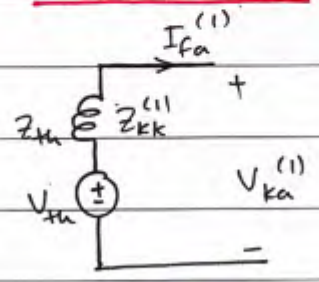

+ve seq.

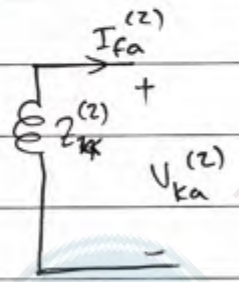

-ve seq.

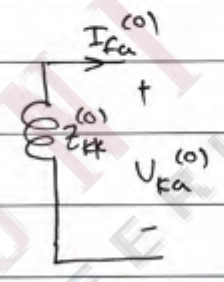

zero-seq.

$$\begin{bmatrix} V_{1a}^{(1)} \\ V_{2a}^{(1)} \\ \vdots \\ V_{ka}^{(1)} \\ \vdots \\ V_{Na}^{(1)} \end{bmatrix} = \begin{bmatrix} V_f \\ V_f \\ \vdots \\ V_f \\ \vdots \\ V_f \end{bmatrix}$$

here we didn't take I_L into consideration

$$\begin{bmatrix} V_{1a}^{(2)} \\ V_{2a}^{(2)} \\ \vdots \\ V_{ka}^{(2)} \\ \vdots \\ V_{Na}^{(2)} \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ \vdots \\ 0 \\ \vdots \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} V_{1a}^{(0)} \\ V_{2a}^{(0)} \\ \vdots \\ V_{ka}^{(0)} \\ \vdots \\ V_{Na}^{(0)} \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ \vdots \\ 0 \\ \vdots \\ 0 \end{bmatrix}$$

$$V_{ja}^{(1)} = V_f \dots \textcircled{1}$$

$$V_{ja}^{(2)} = 0 \dots \textcircled{2}$$

$$V_{ja}^{(0)} = 0 \dots \textcircled{3}$$

Solution #2:

$$\begin{bmatrix} \Delta V_{1a}^{(1)} \\ \Delta V_{2a}^{(1)} \\ \vdots \\ \Delta V_{ka}^{(1)} \\ \vdots \\ \Delta V_{Na}^{(1)} \end{bmatrix} = \begin{bmatrix} Z_{11}^{(1)} & Z_{12}^{(1)} & \dots & Z_{1K}^{(1)} & \dots & Z_{1N}^{(1)} \\ Z_{21}^{(1)} & Z_{22}^{(1)} & \dots & Z_{2K}^{(1)} & \dots & Z_{2N}^{(1)} \\ \vdots & \vdots & \ddots & \vdots & \ddots & \vdots \\ Z_{K1}^{(1)} & Z_{K2}^{(1)} & \dots & Z_{KK}^{(1)} & \dots & Z_{KN}^{(1)} \\ \vdots & \vdots & \ddots & \vdots & \ddots & \vdots \\ Z_{N1}^{(1)} & Z_{N2}^{(1)} & \dots & Z_{NK}^{(1)} & \dots & Z_{NN}^{(1)} \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ \vdots \\ -I_{fa}^{(1)} \\ \vdots \\ 0 \end{bmatrix}$$

$$\Delta V_{ja}^{(1)} = -Z_{jK}^{(1)} I_{fa}^{(1)} \dots \textcircled{1}'$$

$$\begin{bmatrix} \Delta V_{ja}^{(2)} \\ \Delta V_{za}^{(2)} \\ \vdots \\ \Delta V_{ka}^{(2)} \\ \vdots \\ \Delta V_{na}^{(2)} \end{bmatrix} = \begin{bmatrix} z_{11}^{(2)} & z_{12}^{(2)} & \dots & z_{1k}^{(2)} & z_{1n}^{(2)} \\ z_{21}^{(2)} & z_{22}^{(2)} & \dots & z_{2k}^{(2)} & z_{2n}^{(2)} \\ \vdots & \vdots & \vdots & \vdots & \vdots \\ z_{k1}^{(2)} & z_{k2}^{(2)} & \dots & z_{kk}^{(2)} & z_{kn}^{(2)} \\ \vdots & \vdots & \vdots & \vdots & \vdots \\ z_{n1}^{(2)} & z_{n2}^{(2)} & \dots & z_{nk}^{(2)} & z_{nn}^{(2)} \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ \vdots \\ -I_{fa}^{(2)} \\ \vdots \\ 0 \end{bmatrix}$$

$$\Delta V_{ja}^{(2)} = -z_{jk}^{(2)} I_{fa}^{(2)} \dots \textcircled{2}'$$

$$\begin{bmatrix} \Delta V_{ja}^{(0)} \\ \Delta V_{za}^{(0)} \\ \vdots \\ \Delta V_{ka}^{(0)} \\ \vdots \\ \Delta V_{na}^{(0)} \end{bmatrix} = \begin{bmatrix} z_{11}^{(0)} & z_{12}^{(0)} & \dots & z_{1k}^{(0)} & z_{1n}^{(0)} \\ z_{21}^{(0)} & z_{22}^{(0)} & \dots & z_{2k}^{(0)} & z_{2n}^{(0)} \\ \vdots & \vdots & \vdots & \vdots & \vdots \\ z_{k1}^{(0)} & z_{k2}^{(0)} & \dots & z_{kk}^{(0)} & z_{kn}^{(0)} \\ \vdots & \vdots & \vdots & \vdots & \vdots \\ z_{n1}^{(0)} & z_{n2}^{(0)} & \dots & z_{nk}^{(0)} & z_{nn}^{(0)} \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ \vdots \\ -I_{fa}^{(0)} \\ \vdots \\ 0 \end{bmatrix}$$

$$\Delta V_{ja}^{(0)} = -z_{jk}^{(0)} I_{fa}^{(0)} \dots \textcircled{3}'$$

total solution: $\textcircled{1} + \textcircled{1}' + \dots$

$$V_{ja}^{(1)} = V_f - z_{jk}^{(1)} I_{fa}^{(1)}$$

$$\hookrightarrow V_{ka}^{(1)} = V_f - z_{kk}^{(1)} I_{fa}^{(1)}$$


V at the faulty bus
not zero as before

$$V_{ja}^{(2)} = -z_{jk}^{(2)} I_{fa}^{(2)}$$

$$V_{ja}^{(0)} = -z_{jk}^{(0)} I_{fa}^{(0)}$$

$$I_{fa}^{(1)} = ? \rightarrow \left(\begin{array}{l} \text{فولتيج} \\ \text{fault} \end{array} \right)$$

P-E fault:

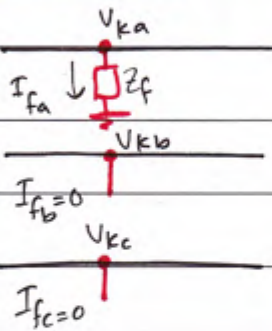

$$I_{fb} = I_{fc} = 0$$

$$Z_{ka} = I_{fa} Z_f$$

$$\begin{bmatrix} I_{fa}^{(0)} \\ I_{fa}^{(1)} \\ I_{fa}^{(2)} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_{fa} \\ I_{fb} \\ I_{fc} \end{bmatrix}$$


$$\therefore I_{fa}^{(0)} = I_{fa}^{(1)} = I_{fa}^{(2)} = \frac{1}{3} I_{fa}$$


$$V_{ka} = (V_{ka}^{(1)}) + V_{ka}^{(2)} + V_{ka}^{(0)} = I_{fa} Z_f$$

$$(V_f - I_{fa}^{(1)} Z_{kk}^{(1)}) - Z_{kk}^{(2)} I_{fa}^{(2)} - Z_{kk}^{(0)} I_{fa}^{(0)} = 3 I_{fa}^{(1)} Z_f$$

$$\therefore V_f = I_{fa}^{(1)} [Z_{kk}^{(1)} + Z_{kk}^{(2)} + Z_{kk}^{(0)} + 3Z_f]$$
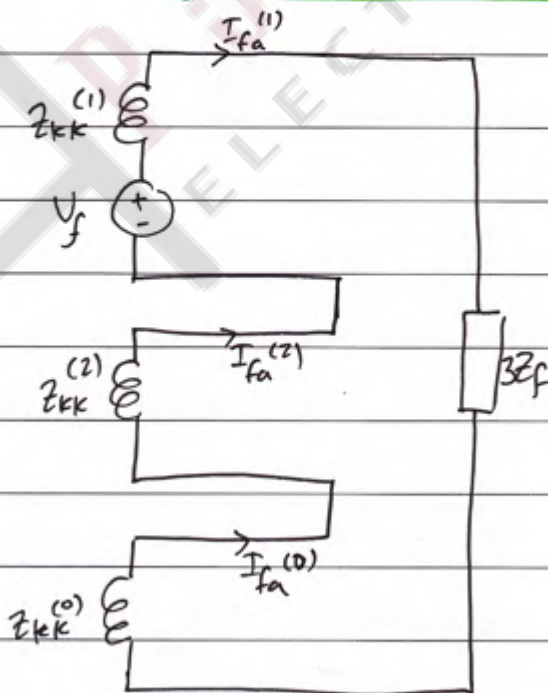
$$I_{fa}^{(1)} = \frac{V_f}{Z_{kk}^{(1)} + Z_{kk}^{(2)} + Z_{kk}^{(0)} + 3Z_f}$$




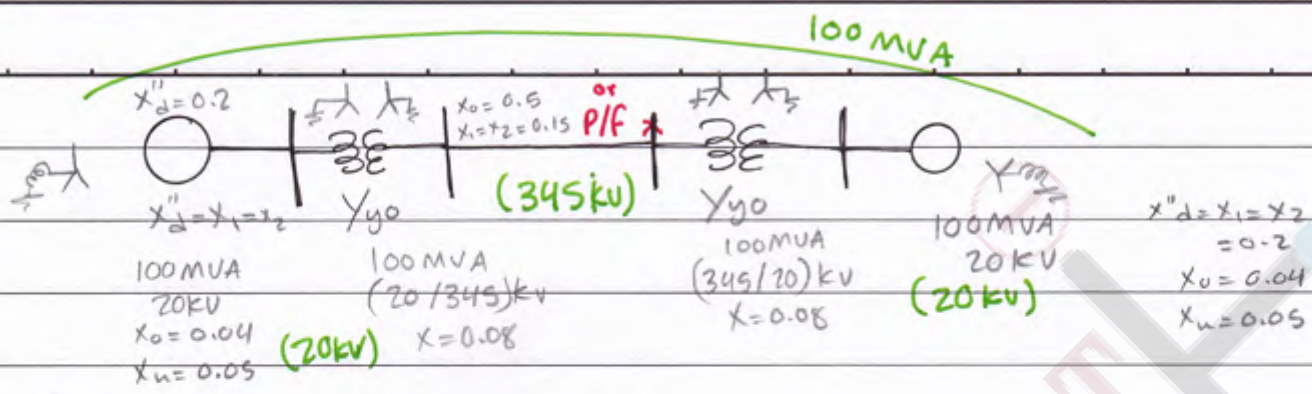

→ $I_L = 0$ before fault

* bolted fault $\Rightarrow Z_f = 0$

Solution:

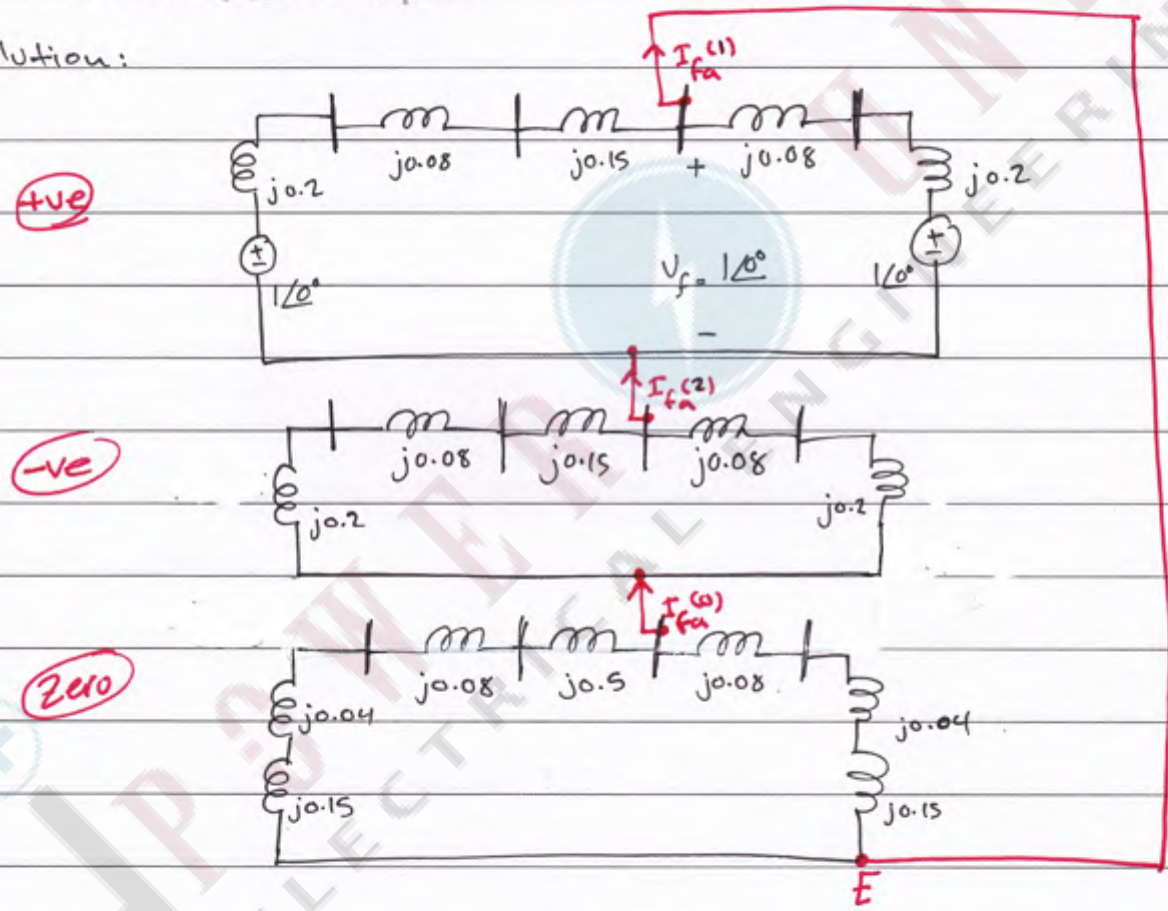

$$Z_{kk}^{(1)} = j0.28 // j0.48$$

$$Z_{kk}^{(2)} = Z_{kk}^{(1)} \text{ from symmetry}$$

$$Z_{kk}^{(0)} = j0.24 // j0.32$$

$$I_{fA}^{(1)} = \frac{1 \angle 0^\circ}{j0.1696 + j0.1696 + j0.1999} = -j1.8549$$

As fault is on H.V. side

$$I_{fA} = 3 I_{fA}^{(1)} = -j1.8549 \times 3 \text{ p.u.} \times \left(\frac{100 \times 10^6}{\sqrt{3} \times 345 \times 10^3} \right)$$

base current.

ex →
continued.

$$I_{fA}^{(1)} = I_{fA}^{(2)} = I_{fA}^{(0)} = -j1.8549 = \frac{I_{fA}}{3}$$

$$Z_{bus}^{(1)} = Z_{bus}^{(2)} = \begin{bmatrix} - & - & j0.0789 & - \\ - & - & j0.1104 & - \\ - & - & j0.1894 & - \\ - & - & j0.1211 & - \end{bmatrix}$$

↳ by symmetry

$$Z_{bus}^{(0)} = \begin{bmatrix} - & - & j0.443 & - \\ - & - & j0.0701 & - \\ - & - & j0.1999 & - \\ - & - & j0.1407 & - \end{bmatrix}$$

$$I_{fA} = 3I_{fA}^{(0)} = -j5.5647$$

find V_{4a}, V_{4b}, V_{4c} ?

$$Z_{bus} \text{ method: } V_{4a}^{(0)} = -Z_{43}^{(0)} I_{fA}^{(0)} = -j0.1407 \times -j1.8549 = -0.261 \text{ p.u.}$$


$$V_{4a}^{(1)} = 1 - Z_{43}^{(1)} I_{fA}^{(1)} = 1 - j0.1211 \times -j0.18549 = 0.7754 \text{ p.u.}$$

$$V_{4a}^{(2)} = -Z_{43}^{(2)} I_{fA}^{(2)} = -j0.1211 \times -j0.18549 = -0.2246 \text{ p.u.}$$

$$\begin{bmatrix} V_{4a} \\ V_{4b} \\ V_{4c} \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} V_{4a}^{(0)} \\ V_{4a}^{(1)} \\ V_{4a}^{(2)} \end{bmatrix} \quad \text{--- (1)}$$


if the transformer was $Yd1$:->

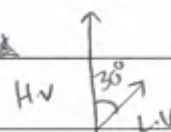* shift due to transformers
only appears in \pm ve sequences.



for +ve seq $\angle -30^\circ$
" -ve " $\angle +30^\circ$
Since V_{4a} is in the LV side.

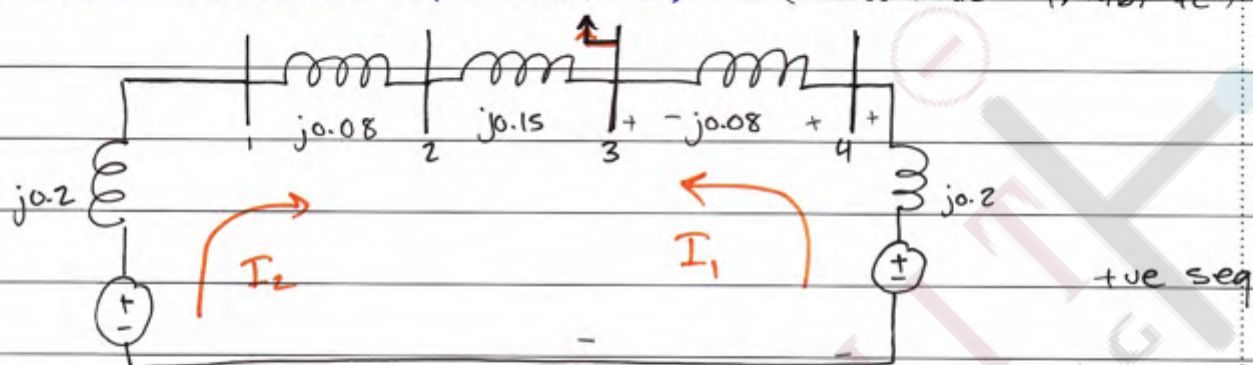- another method (CKT method) :- (to calculate V_{4a}, V_{4b}, V_{4c})



$$I_1 = -j1.8549 \times \frac{j0.43}{j0.71} \quad \text{current division.}$$

$$= -j1.3733$$

& it's the same for the -ve seq.

in the zero sequence:

$$I_1 = -j1.8549 \times \frac{0.77}{1.04} = -j1.2339$$

since the system was unloaded.

$$V_{4a}^{(1)} = 1 \angle 0^\circ - j0.2(-j1.3733) = 0.7753 \text{ p.u.}$$

$$V_{4a}^{(2)} = 0 - j0.2(-j1.3733) = -0.22546 \text{ p.u.}$$

$$V_{4a}^{(0)} = 0 - j0.19(-j1.233) = -0.261$$

- 3rd method:

$$V_{3A}^{(0)} = -Z_{kk}^{(0)} I_{fa}^{(0)} = -0.37079 \text{ p.u.}$$

$$V_{3A}^{(1)} = 1 - Z_{kk}^{(1)} I_{fa}^{(1)} = 0.6854 \text{ p.u.}$$

$$V_{3A}^{(2)} = -Z_{kk}^{(2)} I_{fa}^{(2)} = -0.3146 \text{ p.u.}$$


$$V_{3A} = 0$$

then $V_{4a}^{(1)} = V_{3A}^{(1)} + I^{(1)} \times j0.08$

$$V_{4a}^{(0)} = V_{3A}^{(0)} + (I^{(0)} \times j0.08)$$

⋮

P-P fault

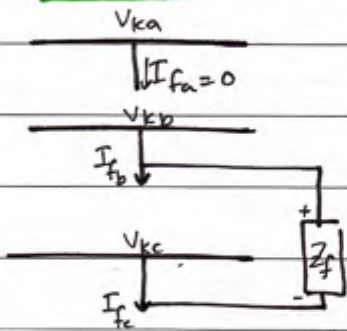

$$I_{fa} = 0$$

$$I_{fb} = -I_{fc}$$

$$V_{kb} - V_{kc} = I_{fb} Z_f$$

$$\begin{bmatrix} I_{fa}^{(0)} \\ I_{fa}^{(1)} \\ I_{fa}^{(2)} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} 0 \\ I_{fb} \\ -I_{fb} \end{bmatrix}$$

$I_{fa}^{(0)} = 0$... (1)

$$I_{fa}^{(1)} = \frac{1}{3} a I_{fb} - \frac{1}{3} a^2 I_{fb} = -I_{fa}^{(2)} \dots (2)$$

$I_{fa}^{(1)} = -I_{fa}^{(2)}$


zero seq. doesn't exist

$$V_{kb} = a^2 V_{ka}^{(1)} + a V_{ka}^{(2)} + 0$$


$$\begin{aligned} V_{kb} - V_{kc} &= (a^2 V_{ka}^{(1)} + a V_{ka}^{(2)}) - (a V_{ka}^{(1)} + a^2 V_{ka}^{(2)}) = I_{fb} Z_f \\ &= (a^2 - a) V_{ka}^{(1)} - (a^2 - a) V_{ka}^{(2)} = (a^2 - a) I_{fa}^{(1)} Z_f \end{aligned}$$

$V_{ka}^{(1)} - V_{ka}^{(2)} = I_{fa}^{(1)} Z_f \dots (3)$

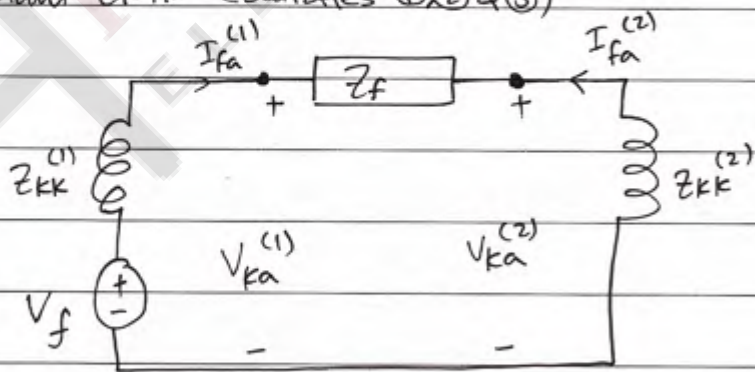• equivalent CKT:- (satisfies (1), (2) & (3))



P-P-E fault:

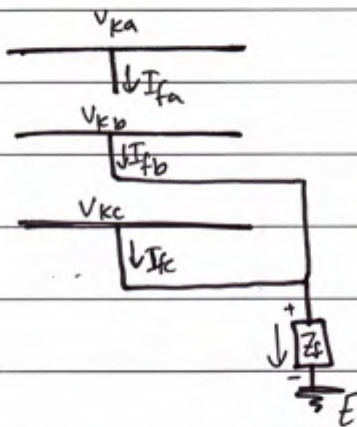

$$\rightarrow I_{fa} = 0$$

$$\rightarrow V_{kb} = V_{kc} = (I_{fb} + I_{fc}) Z_f$$

$$\begin{bmatrix} I_{fa}^{(0)} \\ I_{fa}^{(1)} \\ I_{fa}^{(2)} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_{fa} \\ I_{fb} \\ I_{fc} \end{bmatrix}$$

$$I_{fa}^{(0)} = \frac{1}{3} (I_{fb} + I_{fc}) \Rightarrow I_{fb} + I_{fc} = 3I_{fa}^{(0)}$$

$$\begin{bmatrix} V_{ka}^{(0)} \\ V_{ka}^{(1)} \\ V_{ka}^{(2)} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} V_{ka} \\ V_{kb} \\ V_{kc} \end{bmatrix}$$

$$V_{ka}^{(1)} = \frac{1}{3} (V_{ka} + aV_{kb} + a^2V_{kc})$$

$$V_{ka}^{(2)} = \frac{1}{3} (V_{ka} + a^2V_{kb} + aV_{kc})$$


$$V_{ka}^{(1)} = V_{ka}^{(2)}$$

$$3V_{ka}^{(0)} = V_{ka} + 2V_{kb}$$

$$\frac{2}{3}V_{ka}^{(0)} = (V_{ka}^{(0)} + V_{ka}^{(1)} + V_{ka}^{(2)}) + Z_f \times (3I_{fa}^{(0)}) Z_f$$

$$V_{ka}^{(0)} = V_{ka}^{(1)} + 3I_{fa}^{(0)} Z_f$$





equivalent ckt:

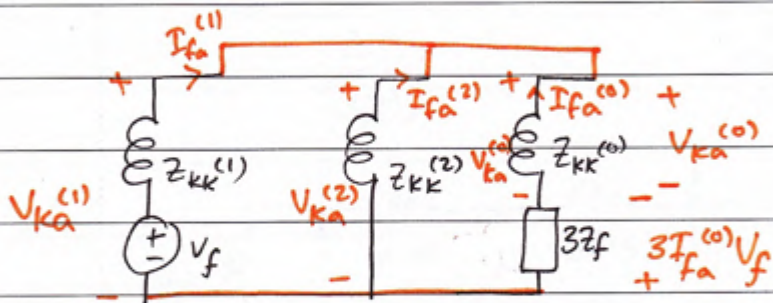


$$V_{kk}^{(1)} = V_{kk}^{(0)} = 3I_{fa}^{(0)} V_f$$

$$I_{fa}^{(2)} = -I_{fa}^{(1)} \left(\frac{Z_{kk}^{(0)} + 3Z_f}{Z_{kk}^{(2)} + Z_{kk}^{(0)} + 3Z_f} \right)$$
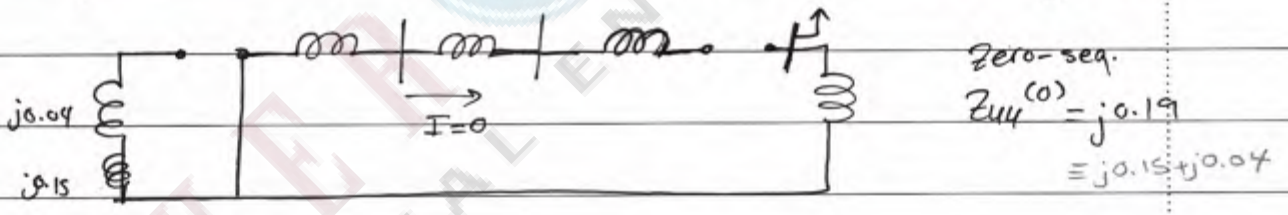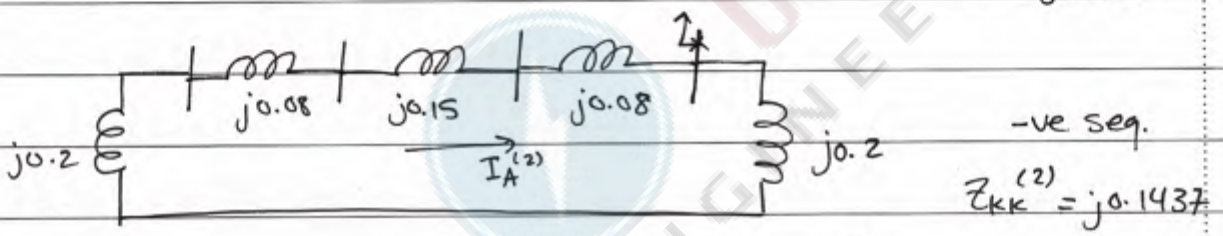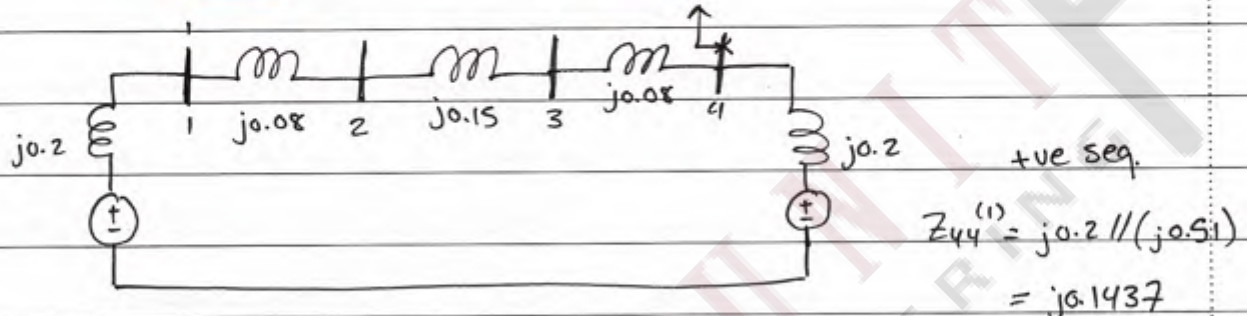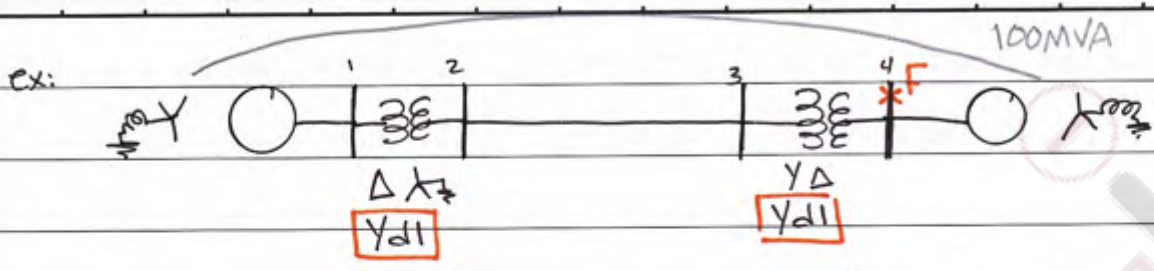
$$I_{fa}^{(0)} = -I_{fa}^{(1)} \left(\frac{Z_{kk}^{(2)}}{Z_{kk}^{(2)} + Z_{kk}^{(0)} + 3Z_f} \right)$$



L-L-E fault:

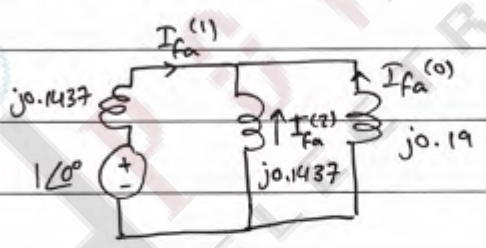

$$I_{fa}^{(1)} = \frac{1 \angle 0^\circ}{j0.1437 + (j0.19 \parallel j0.1437)} = -j4.4342 \text{ p.u.}$$

$$I_{fa}^{(2)} = -(-j4.4342) \times \frac{0.19}{0.19 + 0.1437} = j2.5247 \text{ p.u.}$$

$$I_{fa}^{(0)} = -(-j4.4342) \left(\frac{0.1437}{0.1437 + 0.19} \right) = j1.9095 \text{ p.u.}$$

$$\begin{bmatrix} I_{fa} \\ I_{fb} \\ I_{fc} \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} j1.9095 \\ -j4.4342 \\ j2.5247 \end{bmatrix}$$

→ $I_{fa} = 0$
 $I_{fb} = 6.6726 \angle 154.6^\circ \text{ p.u.}$
 $I_{fc} = 6.6726 \angle 25.4^\circ \text{ p.u.}$

base current = $\frac{100 \times 10^6}{\sqrt{3} \times 20 \times 10^3}$

$V_{4a}^{(1)} = V_{4a}^{(2)} = V_{4a}^{(0)}$ in parallel. (no Z_f is mentioned).

$V_{4a}^{(1)} = 1 - j0.1437 \times (-j4.4342) = 0.3628 \text{ pu.}$

$\rightarrow V_{4a}^{(2)} = V_{4a}^{(1)} = V_{4a}^{(0)}$

$\therefore V_{4a} = 3V_{4a}^{(1)} = 3 \times 0.3628 \text{ pu.}$

$V_{4b} = 0, V_{4c} = 0$ (Z_f isn't considered).


now find V_{2a} ?

① $I_A^{(2)} = j2.547 \times \frac{0.2}{0.71} = j0.7118$

+ phase shift

$I_A^{(2)} = j0.7118 \angle -30^\circ$

since it's a (-ve) seq.

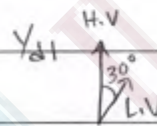

$I_A^{(1)} = -j4.434 \times \frac{0.2}{0.71} \angle +30^\circ = -j1.249 \angle 30^\circ$

$I_A^{(0)} = 0$

$I_A = I_A^{(1)} + I_A^{(2)}$

Vat bus 2: due to phase shift

$V_{2a}^{(1)} = \frac{1}{\sqrt{3}} - j0.28 \times (-j1.249 \angle 30^\circ)$
 $= 0.65028 \angle 30^\circ$

"بقدر العمل الكابتة سوكو با اعتر
 Phase shift
 با اعتر!"

$V_{2a}^{(2)} = (0 - j0.28 \times j0.7118) \angle -30^\circ$
 $= 0.19913 \angle -30^\circ$

$V_{2a}^{(0)} = 0$

base = $\frac{345 \text{ kV}}{\sqrt{3}}$

② using Z_{bus} method:

$V_{2a}^{(0)} = 0,$

$V_{2a}^{(1)} = 1 - Z_{24}^{(1)} I_{fa}^{(1)}$

$= 1 \angle 0^\circ - j0.0784 \times -j4.4342$
 $= (0.65236) \angle +30^\circ$

add it in

$$Z_{bus}^{(1)} = \begin{bmatrix} - & - & - & j0.0563 \\ - & - & - & j0.0784 \\ - & - & - & j0.1211 \\ - & - & - & j0.1437 \end{bmatrix}$$

$V_{2a}^{(0)} = 0$ what does it mean?

$$V_{2a}^{(0)} = -Z_{24}^{(0)} I_{fa}^{(0)}$$

$R \neq 0$

$\therefore Z_{24}^{(0)} = 0$; \therefore no connection between 2 & 4.

$$Z_{bus}^{(0)} = \begin{bmatrix} \dots & 0 \\ \dots & 0 \\ \dots & 0 \\ \dots & -j0.19 \end{bmatrix}$$


remember, $Z_{24} \neq Z$ between bus 2 & 4
that

at bus 1: 2 shifts will occur $+30$ then -30

(phase voltage) V_{2a} \rightarrow $1/\sqrt{3}$ \rightarrow transformed $1 \angle 30^\circ$ side
 " bus 2 \angle 30° و fault on bus \angle

• Chapter #11 Problems:-

11.2:

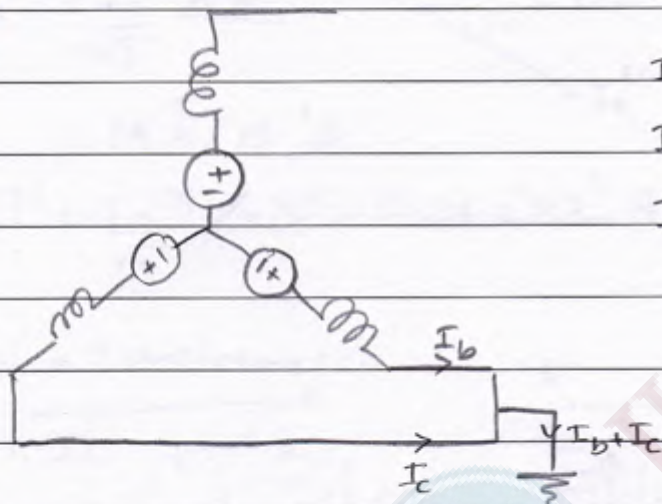

$$I_a^{(1)} = 600 \angle -90^\circ \text{ A}$$

$$I_a^{(2)} = 250 \angle 90^\circ \text{ A}$$

$$I_a^{(0)} = 350 \angle 90^\circ \text{ A}$$

$$I_a = 0$$

$$I_b^{(1)} = 600 \angle -90 + 240^\circ$$

$$I_b^{(2)} = 250 \angle 90 + 120^\circ$$

$$I_b^{(0)} = I_a^{(0)} = 350 \angle 90^\circ$$

$$* I_b = 904.1 \angle 144.5^\circ$$

$$I_c^{(1)} = 600 \angle -90 + 120^\circ$$

$$I_c^{(2)} = 250 \angle 90 + 240^\circ$$


$$I_c^{(0)} = 350 \angle 90^\circ$$

$$* I_c = 904.1 \angle 35.5^\circ$$

$$I_b + I_c = j1050 \text{ A} \equiv 3I_a^{(0)}$$

you can solve it directly.

11.4 & 11.14

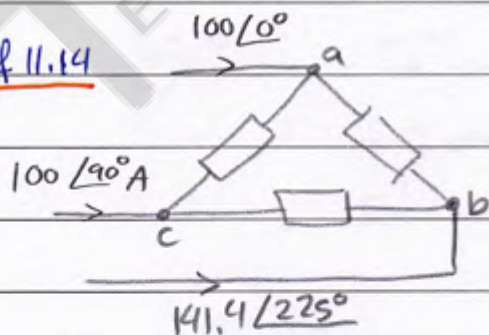

$$I_a^{(0)} = 0 \text{ (}\Delta\text{-load)}$$

$$I_a^{(1)} = \frac{1}{3} (100 \angle 0^\circ + 141.4 \angle 225 + 120 + 100 \angle 90 + 240)$$

$$= 111.5 \angle -15^\circ$$

$$I_a^{(2)} = \frac{1}{3} (100 \angle 0^\circ + 141.4 \angle 225 + 240 + 100 \angle 90 + 120)$$

$$= 29.9 \angle 105^\circ$$


→ then solve for $I_b^{(1)}, I_b^{(2)}, \dots, I_c^{(1)}, I_c^{(2)}, \dots$

$$I_{ab}^{(1)} = \frac{I_a^{(1)}}{\sqrt{3}} \angle +30^\circ$$

$$= 64.4 \angle 15^\circ \text{ A}$$

$$I_{ab}^{(2)} = \frac{I_a^{(2)}}{\sqrt{3}} \angle -30^\circ = 17.36 \angle 75^\circ \text{ A}$$

114 → add a transformer:

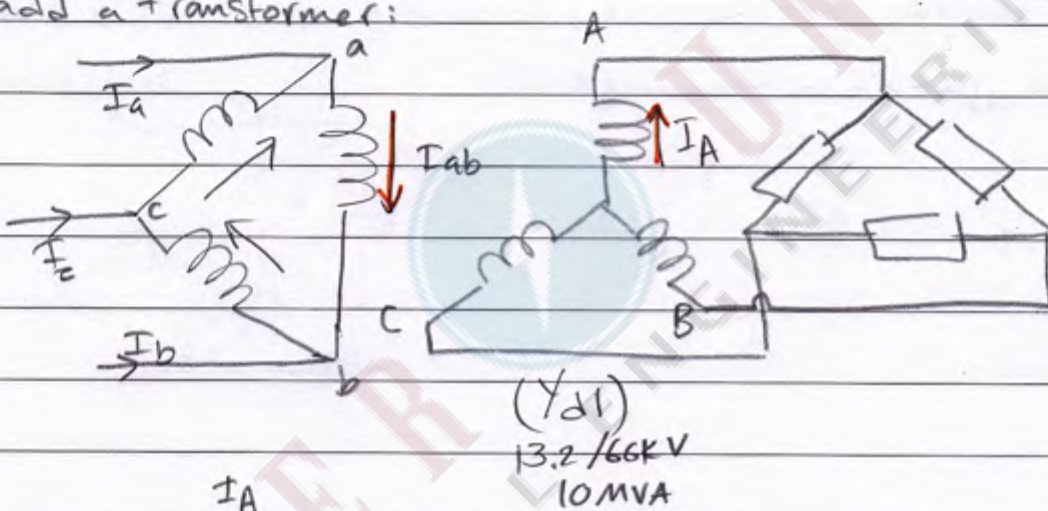


$$I_{ab} = 100 \angle 0^\circ \times \left(\frac{66}{\frac{13.2}{\sqrt{3}}} \right) \left(\frac{1}{13.2} \right) \quad \left(\text{since } I_{ab} \text{ is a phase current} \right)$$

← turns ratio. = 2.89

by symm. components

$$I_{ca} = 100 \angle 90^\circ \times 2.89 \quad I_a = I_{ab} - I_{ca} = 408.48 \angle -45^\circ$$

now, since it's a Yd1 transformer

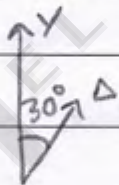

$$I_a^{(1)} = I_a^{(1)} \angle -30^\circ \text{ p.u.}$$

if I want it in Amperes

$$I_a^{(1)} = I_a^{(1)} \times (\text{transformation ratio}) \angle -30^\circ \text{ A}$$

since I_a & I_A are line to line currents.

in p.u. $I_a^{(1)} = I_a^{(1)} \angle -30^\circ = \frac{111.5 \angle -15^\circ}{\left(\frac{10 \times 10^6}{\sqrt{3} \times 66 \times 10^3} \right)} \angle -30^\circ = 1.274 \angle -45^\circ \text{ p.u.}$

base: $\frac{10 \times 10^6}{\sqrt{3} \times 13.2 \times 10^3} \text{ L-LKV}$


$$I_a^{(2)} = \frac{29.9 \angle 105^\circ}{\text{base current}} \angle 30^\circ \leftarrow \text{-ve seq.}$$

$$= 0.342 \angle 135^\circ \text{ p.u.}$$

$$I_a = I_a^{(1)} + I_a^{(2)} = 0.932 \angle -45^\circ \text{ p.u.}$$


$$= 408 \angle -45^\circ \text{ A} = I_b = I_c$$

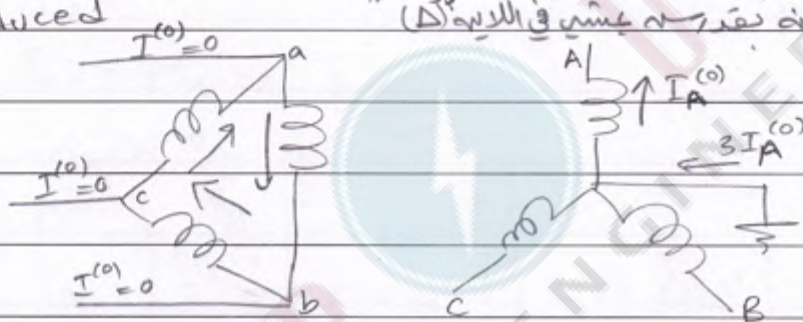if the Y side was grounded a zero seq. current will be introduced
 "(D) $\frac{I_a^{(0)}}{I_a^{(1)}} = \frac{Z_{Y0}}{Z_{Y0} + Z_{\Delta 0}}$ turns ratio" $\frac{I_a^{(0)}}{I_a^{(1)}}$






$I_{ab}^{(2)}$ from $I_a^{(2)}$
 $I_{ab}^{(1)}$ from $I_a^{(1)}$
 $I_{ab}^{(0)}$ from $I_a^{(0)}$
 (turns ratio)


11.9

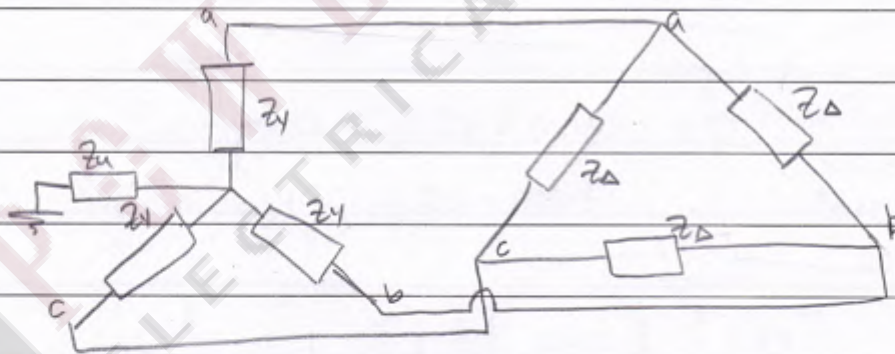

Sequence networks:

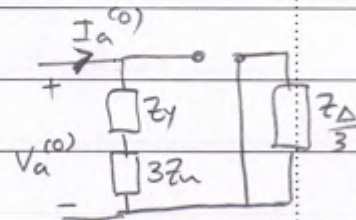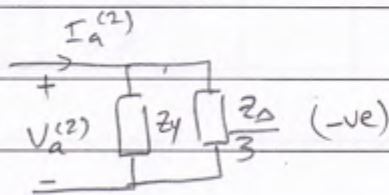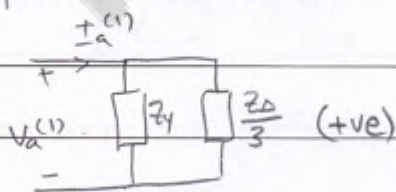

11.12

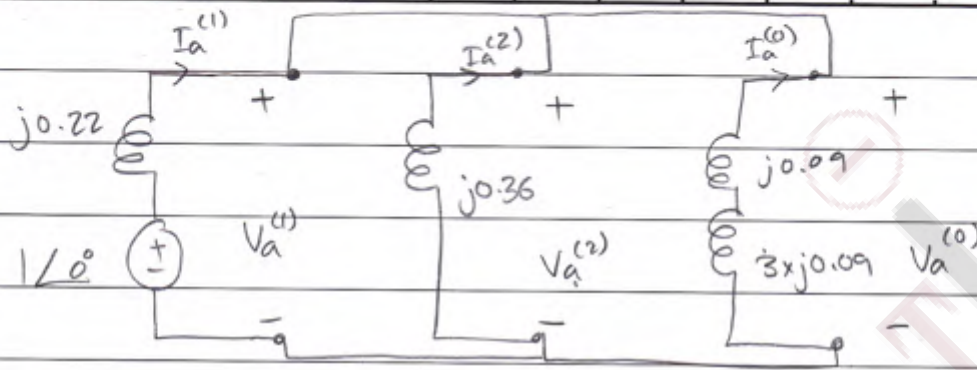

rated terminal voltage $\equiv 1\angle 0^\circ$

Fault currents:-

$$I_a = 0$$

$$I_c = 3.75 / 30^\circ \text{ p.u.}$$

$$I_b = 3.75 / 150^\circ \text{ p.u.}$$

V_a, V_b, V_c ?

$$\begin{bmatrix} I_a^{(0)} \\ I_a^{(1)} \\ I_a^{(2)} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} 0 \\ 3.75 / 150^\circ \\ 3.75 / 30^\circ \end{bmatrix} = \begin{bmatrix} j1.25 \\ -j2.5 \\ j1.25 \end{bmatrix}$$

من صفر جزف
فالتى اى
" b-c-E

$$V_a^{(1)} = 1\angle 0^\circ - j0.22 \times -j2.5$$

$$= 0.45$$

$$V_a^{(2)} = -j0.36 \times j1.25 = 0.45$$

$$V_a^{(0)} = -j0.36 \times j1.25 = 0.45$$

$$\rightarrow V_a^{(0)} = V_a^{(1)} = V_a^{(2)}$$


Since they're in parallel (V_f was not mentioned)

$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 0.45 \\ 0.45 \\ 0.45 \end{bmatrix} = \begin{bmatrix} 1.35 \\ 0 \\ 0 \end{bmatrix}$$

p.u.

Since $V_f = 0$

11.16

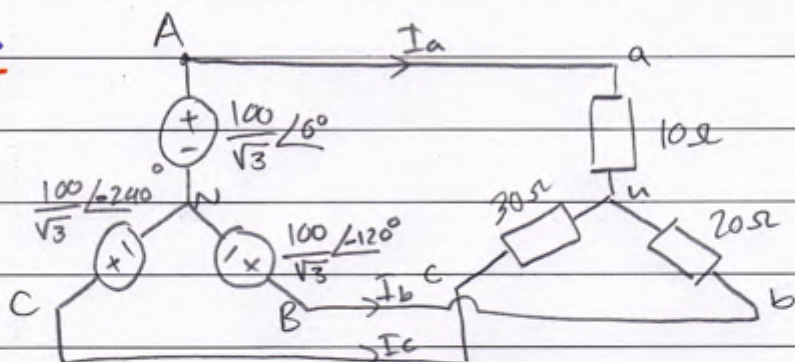

* CKT method (3 meshes the solve for currents).

* Symmetrical components

$$\underline{V_{AN}} = \underline{V_{An}} + \underline{V_{nN}}$$

\downarrow +ve seq. only \rightarrow zero-seq. only
 since it's a balanced source most contain zero & +ve seq. only \rightarrow to cancel the zero seq. from V_{nN}

$\therefore V_{An}^{(0)} = 0$

$V_{An}^{(1)} = \frac{100}{\sqrt{3}} \angle 0^\circ$

$V_{An}^{(2)} = 0$

$I_a^{(0)} = 0$

$V_{An}^{(1)} = \frac{100}{\sqrt{3}} \angle 0^\circ = \frac{1}{3} I_a^{(1)} (Z_a + Z_b + Z_c) + \frac{1}{3} I_a^{(2)} (Z_a + a^2 Z_b + a Z_c)$

$V_{An}^{(2)} = 0 = \frac{1}{3} I_a^{(1)} (Z_a + a Z_b + a^2 Z_c) + \frac{1}{3} I_a^{(2)} (Z_a + Z_b + Z_c)$

$I_a^{(0)} = 0$

$I_a^{(1)} = 3.147$

$I_a^{(2)} = 0.908 \angle 30^\circ$

$I_a = 3.959 \angle 6.35^\circ$