

17  
22

Q	Mark
1	9/15
2	30/30
3	11/15
SUM	50/60

University of Jordan  
Electrical Eng. Dept



EE 0933481 Power Systems (1)

First Exam.  
6-3-2016

الاسم: [redacted] رقم التفقد (61) الرقم الجامعي: [redacted]

Q1) The values shown on the system of Fig. 1 are pu reactance;

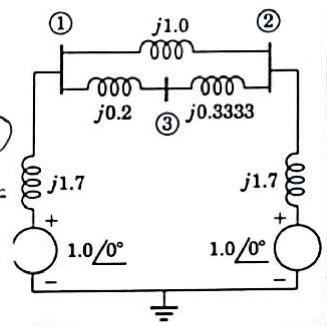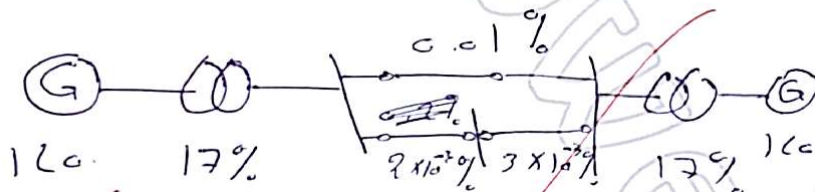1.1-If the value  $j1.7$  represent reactance of a transformer and the other values represent transmission lines, draw the single line diagram of the system. [6]



1.2-By performing any necessary redrawing for the system, evaluate:

a-The elements of the second row of its  $Y_{bus}$  matrix. [5]

b-The first nodal equation. [4]

$Z = \frac{1}{\sigma + jX}$

$$\begin{bmatrix} \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot \end{bmatrix}_{3 \times 3} = \begin{bmatrix} \frac{1}{j} + \frac{1}{j0.2} + \frac{1}{j1.7} & -\frac{1}{j} & -\frac{1}{j0.2} \\ -\frac{1}{j} & \frac{1}{j} + \frac{1}{j0.33} + \frac{1}{j1.7} & -\frac{1}{j0.33} \\ -\frac{1}{j0.2} & -\frac{1}{j0.33} & \frac{1}{j0.2} + \frac{1}{j0.33} \end{bmatrix}$$

(b)

$$\frac{V_1 - 1}{j1.7} + \frac{V_1 - V_2}{j} + \frac{V_1 - V_3}{j0.2} \quad \dots \quad (1)$$

$$\left( \frac{1}{j} + \frac{1}{j0.2} + \frac{1}{j1.7} \right) V_1 - \left( \frac{1}{j} \right) V_2 - \left( \frac{1}{j0.2} \right) V_3$$

(a)

$$\frac{-1}{j}, \quad \frac{1}{j} + \frac{1}{j0.33} + \frac{1}{j1.7}, \quad -\frac{1}{j0.33}$$

Q2) For the system shown in Fig. 2:

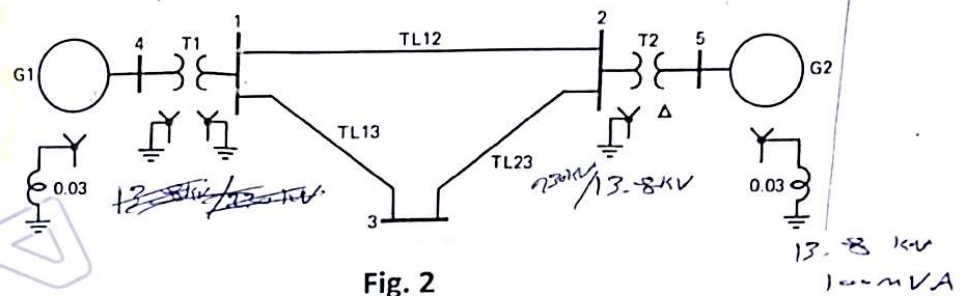


Fig. 2

2.1 If transformer T2 is rated at (13.8 kV Δ/230 kV Y) and  $N_1$  of Y=100 turns, evaluate  $N_2$  of Δ. [6]

6

$$\frac{V_{LL}}{V_{\Delta\Delta}} \equiv \frac{230 \text{ k}}{13.8 \text{ k}} = 16.6667 = \frac{N_1}{\frac{N_2}{\sqrt{3}}} = \frac{N_1 \sqrt{3}}{N_2}$$

$$\Rightarrow 16.6667 = \frac{100 \sqrt{3}}{N_2} \Rightarrow N_2 \equiv 10.4 \text{ turns}$$

2.2 If the ratings of G2 are 13.8 kV, 100 MVA are used as base values for the system, find the pu reactance of TL12 if it has 0.5 Ω/km and Length 80 km, knowing that T2 has the same rating above. [6]

6


$S_b = 100 \text{ MVA}$   
 $V_{bL} = 13.8 \text{ kV}$

$$X_{TL12} \equiv 80 (0.5) = 40 \Omega$$

$$Z_b = \frac{V_b^2}{S_b} \equiv \frac{230^2}{100} = 529$$

$$X(\text{pu}) = \frac{X}{X_b} \equiv \frac{40}{529} = 0.0756 \text{ pu}$$

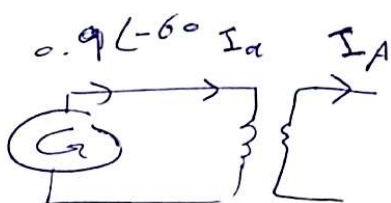2.3 If the current supplied by G2 is  $0.9 \angle -60^\circ$  pu, then find the current Entering bus 2 in Amperes by using negative sequence & base values Of (2.2) and the above ratings of T2. [8]



$$I_A = I_a \angle -30$$

$$I_{G2} = I_a = 0.9 \angle -60 \text{ pu}$$

$$I_A \equiv 0.9 \angle -90 \text{ pu}$$

$$I_b \equiv \frac{100 \text{ M}}{\sqrt{3} \cdot 230 \text{ k}} \equiv 251 \text{ A}$$

$$I = I_b I_{\text{pu}} = 251 (0.9) \angle -90 = 225.9 \angle -90 \text{ A}$$



2.4 If G1 is rated at 100 MVA, 25 kV and the values of its various reactance are  $0.8 \Omega$ ,  $0.4 \Omega$  and  $0.1 \Omega$ . Evaluate the expression for the magnitude of its symmetrical current when a balanced 3-ph fault is applied at its open circuit terminals. [10]

$$i(t) = \frac{E}{X} + E \left( \frac{1}{X'} - \frac{1}{X} \right) e^{-\frac{t}{T'}} + E \left( \frac{1}{X''} - \frac{1}{X'} \right) e^{-\frac{t}{T''}}$$

$$E = \frac{25}{\sqrt{3}} \text{ kV}; i(t) \approx 18042 + 14433 \left( \frac{1}{0.4} - \frac{1}{0.8} \right) e^{-\frac{t}{T'}}$$

$$+ 14433 \left( \frac{1}{0.1} - \frac{1}{0.4} \right) e^{-\frac{t}{T''}}$$

$$\approx 18042 + 18041 e^{-\frac{t}{T'}} + 108247.5 e^{-\frac{t}{T''}}$$

Q3) A transmission line has the following constants:  $A=D=1$ ,  $B=4+j7$  and  $C=0$ . When the line supplies a given load, the voltage regulation is 20%. Find the PF of the load if the angle of the sending voltage is  $5^\circ$  With respect to the Zero angle the receiving voltage. [15]

short line



$$V_R \quad \text{PF} \quad VR\% = \frac{|V_s| - |V_{RFL}|}{|V_{RFL}|} = 0.2$$

$$|V_s| \angle 5^\circ \quad |V_R| \angle 0^\circ \quad |V_s| - |V_{RFL}| = 0.2 |V_{RFL}|$$

$$V_s = V_R + I_R Z \quad \text{--- (1)}$$

$$|V_s| \approx 1.2 |V_{RFL}|$$

$$I_s = 0 + I_R \quad \text{--- (2)}$$

$$\theta_z = \theta_v - \theta_i$$

$$I_R = \frac{V_s - V_R}{Z} = \frac{1.2 |V_{RFL}| \angle 5^\circ - |V_R| \angle 0^\circ}{4 + j7} = \frac{0.2 |V_{RFL}| \angle 60^\circ}{4 + j7}$$

$$\Rightarrow \theta_{I_R} = -60^\circ \Rightarrow \theta_z = \theta_v - \theta_i = \boxed{60^\circ}$$

PF ??