

G	Mark
1	7/10
2	12/20
3	14/14
4	8/14
5	11/12
6	13/20
T	65/90

University of Jordan

Electrical Eng. Dept

EE 0933481 Power Systems (1)



2nd Exam.

13-12-2015

رقم التفاصي (٤٧) [الاسم:]

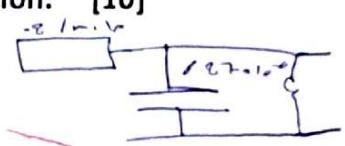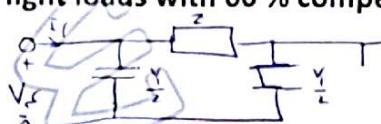Q1) The shunt admittance of a 300 mile transmission line is $(j6.87 \cdot 10^{-6})$ S/mile. Its series reactance is $0.8 \Omega/\text{mile}$. Determine the ABCD constants of the compensation network which should be connected at the receiving end at light loads with 60 % compensation. [10]

$$Y_{\text{tot}} = (6.87 \cdot 10^{-6} + j300) \text{ S} \\ = 2.061 \cdot 10^{-3} \text{ S}$$



$$60 \% \text{ compensation} = C \frac{B_c}{B_L} \Rightarrow \frac{B_{\text{compensation}}}{1.0305 \cdot 10^{-3} \text{ S}} = .6$$

Q2) A 200 mile, 100 kV transmission line has the following parameters at 60 Hz: $z = 0.8 \angle 75^\circ \Omega/\text{mile}$ and $y = j5.4 \cdot 10^{-6} \text{ S}/\text{mile}$.

a- Evaluate the incident voltage at the sending end when the line is open-circuited and the receiving voltage is maintained at a line voltage of 100 kV. [10]

$$V(x) = \frac{V_R}{Z_c} e^{jx} + I_R \frac{e^{-jx}}{Z_c}$$

$$I_R = 0$$

$$V_R = 100 \text{ kV}$$

$$\frac{V_R}{Z_c} + I_R e^{-jx}$$

$$x = 200 \text{ miles}$$

$$V_R = (100 + j\sqrt{2}) \text{ kV}$$

$$Z = 160 \angle 75^\circ$$

$$Y_c = 1.08 \cdot 10^{-3}$$

$$Z_{SIL} = 373.666$$

b- Evaluate SIL the line. [10]

$$Z_f = \sqrt{L/C} = \sqrt{\frac{w_0 m}{2.8648 \cdot 10^{-6}}} = 207 + j772.74 \Omega$$

$$P = \sqrt{3} \cdot V \cdot I = \frac{V^2}{Z_{SIL}} = \frac{100^2}{286.6} = 2 \text{ MW}$$

$$1.08 \cdot 10^{-3} \text{ S} = Y \Rightarrow w_c = 1.08 \cdot 10^{-3}$$

$$C = 2.8648 \cdot 10^{-6} \text{ F}$$

$$Z_{SIL} = \sqrt{L/C} = 2 \text{ mH} = 200 \text{ mH}$$


Q1)

$$\cdot 6 = \frac{B_{\text{comp}}}{B_L} \Rightarrow \cdot 6 = \left(\frac{1}{2}\right) = B_{\text{comp}}$$

$$B_{\text{comp.}} = -61.83 \cdot 10^{-3} \text{ A}$$

$$J = 5 \text{ A}$$
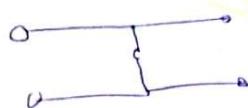
$$Y_{\text{comp}} = -61.83 \cdot 10^{-3} \text{ S}$$



$$V_f = V_R + 0$$

$$[s] = L Y_R V_R (1) - I_R$$
$$Y_c = -J B_c$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & \\ -61.83 \cdot 10^{-3} & 1 \end{bmatrix}$$

POLYTECHNIC
CIRCUIT

Q3) The Third Column in the Z_{bus} matrix of a 4-bus system in pu is as follows:

j 0.04	z_{13}
j 0.06	z_{23}
j 0.13	z_{33}
j 0.05	z_{43}

For a balanced 3-ph fault on Bus 3:

- a- Evaluate subtransient current in the line between buses 2 and 4 if it has pu impedance of $j2$. $v_f = 1 \angle 0^\circ$ [8]

$$I_{2-4} = \frac{v_2 - v_u}{z_{23}}$$

$$v_2 = v_f - \frac{v_f}{z_{33}} \cdot z_{23}$$

$$\frac{.53846 - .61538}{2j} = .03846 \angle -90^\circ$$


$$= 1 \angle 0^\circ - \frac{1 \angle 0^\circ}{.13j} + .06j = .53846 \angle -90^\circ$$

or

$$v_u = 1 - \frac{1}{.13j} \cdot .06j = .61538 \angle -90^\circ$$

$$.03846 \angle -90^\circ \text{ From } 4 \rightarrow 2$$

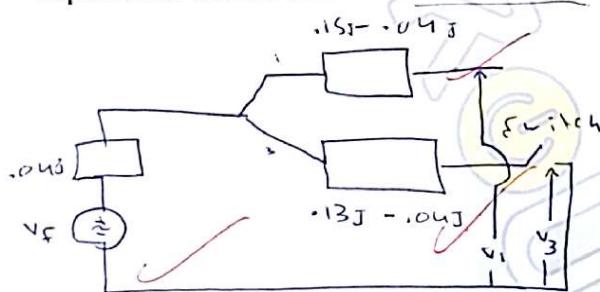- b- If the element Z_{11} of the Z_{bus} matrix is $j0.15$, draw the thevenin equivalent circuit between buses 1 and 3. [6]



$$\sum I^{(1)}_a = 0$$

Q4) The pu 3-ph complex power supplied to Y-connected load is $1.03 \angle 0^\circ$.

Given that : $V_{an}^{(1)} = 0.99 \angle 44^\circ$, $V_{an}^{(2)} = 0.23 \angle 250^\circ$, $I_a^{(1)} = 0.99 \angle 44^\circ$

By using the concept of symmetrical components, evaluate the other sequence currents. [14]

$$I_a^{(1)} = 0.99 \angle 44^\circ$$

$$V_{an}^{(1)} = 0.99 \angle 44^\circ$$

$$V_{an}^{(2)} = 0.23 \angle 250^\circ$$

$$\text{So } \begin{bmatrix} I_a^{(1)} \\ I_a^{(0)} \\ I_a^{(-1)} \end{bmatrix} = \begin{bmatrix} 0 \\ 0.99 \angle 44^\circ \\ 2.7685 \angle 70^\circ \end{bmatrix}$$

$$\sum I_{tot} = 3(V_{an}^{(1)} I_a^{(1)} + V_{an}^{(0)} I_a^{(0)} + V_{an}^{(-1)} I_a^{(-1)})$$

$$1.03 = 3(0.99 \angle 44^\circ + 0.99 \angle -44^\circ + 0.23 \angle 250^\circ + I_a^{(2)})$$

$$0.34333 = 0.9801 + 0.23 \angle 250^\circ + I_a^{(2)} \Rightarrow I_a^{(2)} = (2.7685 \angle 70^\circ)$$

$$Z_F + 2Z_m$$

$$Z_{aa} = Z_{ab}$$

11
12

Q5) Evaluate the followings

a- Z_2 of a 3-ph generator having at 50 Hz:

$$R = 2 \Omega, L_s = 2.8 \text{ mH}, M_s = 1.4 \text{ mH}$$

[5]

$$Z_2 = R + j\omega (L_s - M_s)$$

$$= 2 + (100\pi) (1.4) \rightarrow j$$

$$= 2.0478 \angle 12.4026^\circ \Omega$$

b- Z_0 of a 3-ph transmission line having at 50 Hz:

For each phase conductor: $R = 40 \Omega, L = 0.5 \text{ H}$

$$40 + j50 \Omega$$

For neutral conductor: $R = 20 \Omega, L = 0.2 \text{ H}$

Mutual inductance between two phase conductors = 0.3 H

Mutual inductance between phase conductor and neutral = 0.1 H

7
7

$$Z_{aa} = 40 + 0.5 + j(2\pi 50) \rightarrow j = 162.1 \angle 75.7134^\circ \Omega$$

$$Z_{nn} = 20 + 0.2 - j0 - j\pi 3 = 65.94 \angle 72.3432^\circ \Omega$$

$$Z_{ab} = 0.3 + j\pi - j0 = 94.247 \Omega$$

$$Z_{an} = 31.4159 \Omega$$

$$Z_0 = Z_F + 2Z_m \Rightarrow (Z_{aa} + 2Z_{ab} + Z_{nn}) + 2(Z_{ab})$$

$$(Z_{aa} + 2Z_{ab} + Z_{nn}) + (Z_{nn} + 2Z_{ab}) \rightarrow \text{خلف اورنی}$$

Q6) A generator is rated at 100 MVA, 20 kV, $X_1 = 20\%$ and $X_0 = 5\%$.



Its neutral is grounded through a reactor of 0.32Ω . The generator is operating at rated voltage without load when a single-line-to-ground fault occurs at its terminals.

a-Evaluate the fault current in pu.

[11]

b-Evaluate the corresponding sequence voltages.

[9]

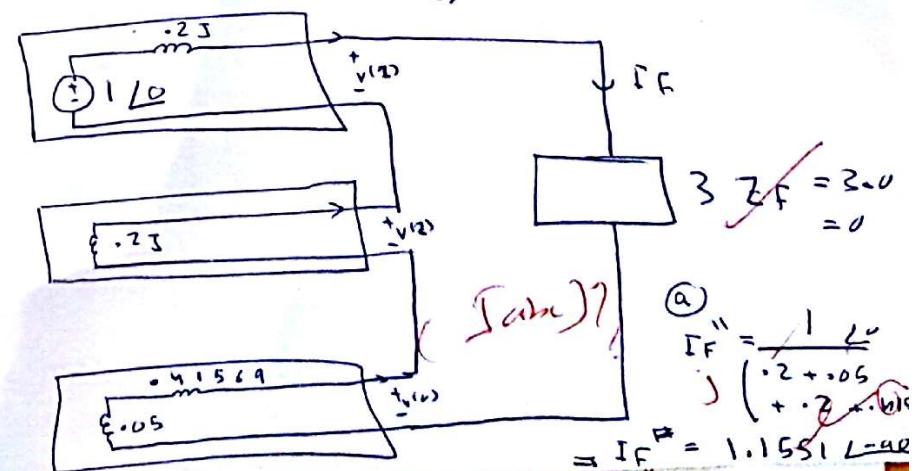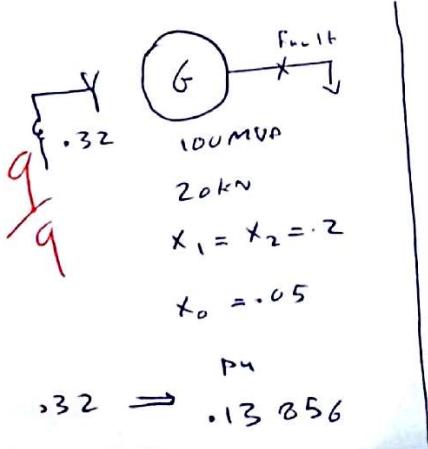


Part (B) / Q. 6

$$I_F = \frac{1 \text{ kV}}{0.2 + 0.2 + 0.5 + 0.1569} =$$

$$V^{(0)} = - I_F \cdot (0.05 + 0.1569) \text{ J} = - 53794 \text{ V} \quad \boxed{1.1551 - 90^\circ}$$

$$V^{(1)} = 1 - (-0.2 \text{ J}) \cdot I_F \Rightarrow 764 \text{ V}$$
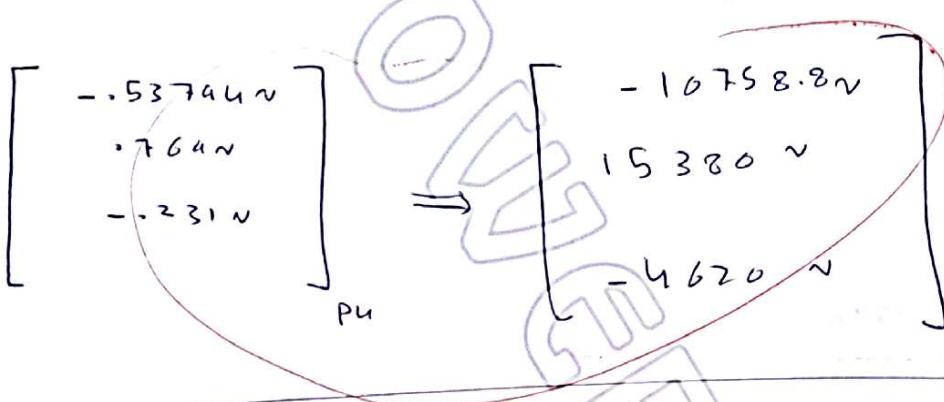
$$V^{(2)} = - I_F \cdot 0.2 \text{ J} \Rightarrow - 231 \text{ V}$$



Part (B) / Q. 5

$$V_{aa'} = I_a (Z_{aa} - Z_{an}) + (I_b + I_c) (Z_{ab} - Z_{an}) -$$

$$V_{aa'} = I_a Z_{aa} + (I_b + I_c) Z_{ab} + I_n (Z_{an}) -$$

 ~~$I_a (Z_{aa} - Z_{an})$~~
 $(I_n Z_{an} + I_a Z_{an}) + (I_b + I_c) Z_{an}$

$$I_a (Z_{aa} - Z_{an}) + (I_b + I_c) (Z_{ab} - Z_{an}) + I_n (Z_{an} - Z_{nn})$$

$$I_n = -I_a - (I_b + I_c)$$

$$\underbrace{I_a (Z_{aa} - Z_{an} + Z_{nn})}_{Z_s} + \underbrace{(I_b + I_c) (Z_{ab} - Z_{nn} + Z_{nn})}_{Z_n}$$

$$Z_o = Z_s + 2Z_m = Z_{aa} - 6Z_{an} + 3Z_{nn} + 2Z_{ab}$$

$$\Rightarrow Z_o = 359.76454 \quad \boxed{73.861}$$