

20 Jan 2019

* Power System Components:

It consists of 3 components:

- ① Generation
- ② Transmission
- ③ Distribution

- Generation:

Electrical energy is generated at power stations or plants, can be ~~etc~~ classified to:

- Thermal
- Hydro
- Renewable

- Thermal Plants: ^(non-salient) (cylindrical) (3000 rpm)

Can be classified according to:

- 1) Fuel: fossil (oil, coal, gas), Nuclear, geothermal
- 2) Prime mover: steam turbine, gas turbine, combined, internal combustion engine, cycle

- Hydro Plants: ^(non-cylindrical) (salient) (1000 - 1400 rpm)

Kinetic ~~energy~~ energy of water can be used to drive hydro turbine

• Renewable Plants:

- 1) Wind (induction generator)
- 2) Solar
- 3) Tidal

- Transmission:

→ Power stations generate voltages in the range (11-25) kV, in order to transfer this energy, the voltage is stepped-up through step-up transformers located at the power station substations.

→ In Jordan there are two transmission level 132 and 400 kV.

→ Since $p = vi$, - $v \equiv$ is set by the required insulation level between conductors
 - $i \equiv$ is set by the thermal capacity of the conductors

→ Usually transmission lines are double circuit

- Distribution:

→ At the receiving ends of the transmission lines there are substations which include step-down transformers in order to step-down the transmitted voltages to distribution levels

→ Although ~~the~~ distribution system is passive, but now it became Active, because generating ~~units~~ units are connected directly to this system



⊕ Power System Representation :


In order to perform analysis on a power system, then it should be represented as follows:-

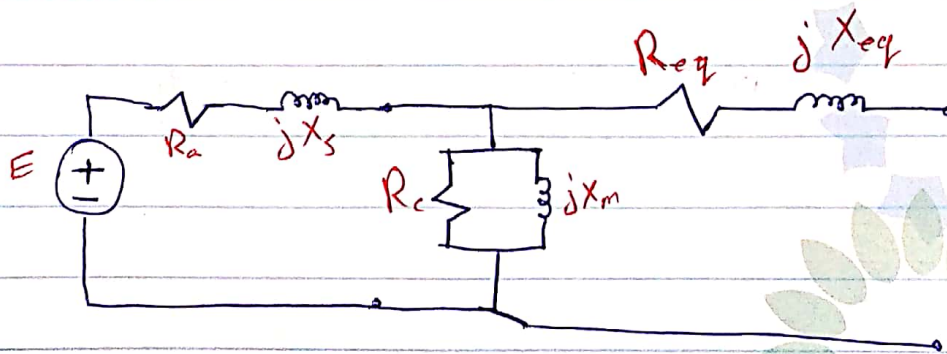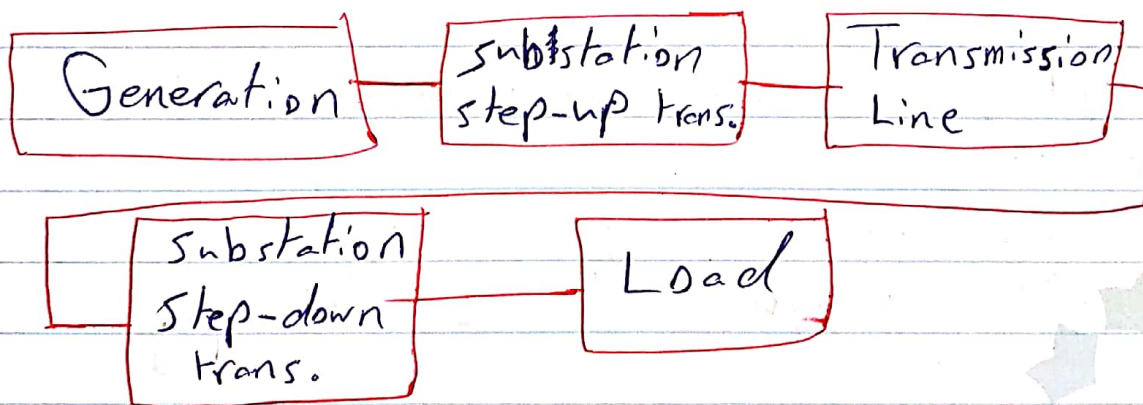- 1) Graphical representation
- 2) Mathematical representation


→ Graphical:

It per phase circuit. This is used for balanced systems. Here each component is represented by its equivalent circuit, illustrated as follows:-




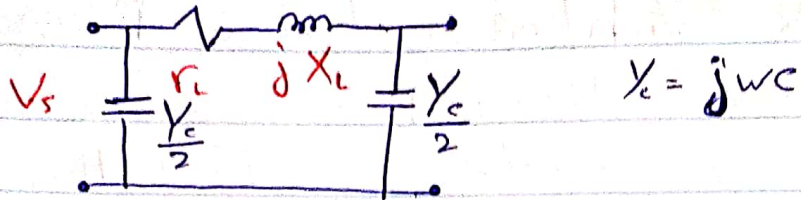

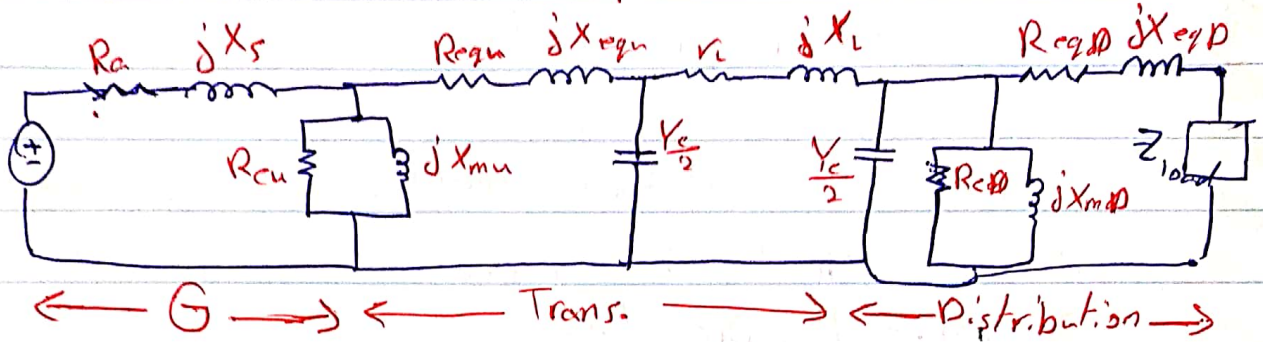this is called π -Representation of the line




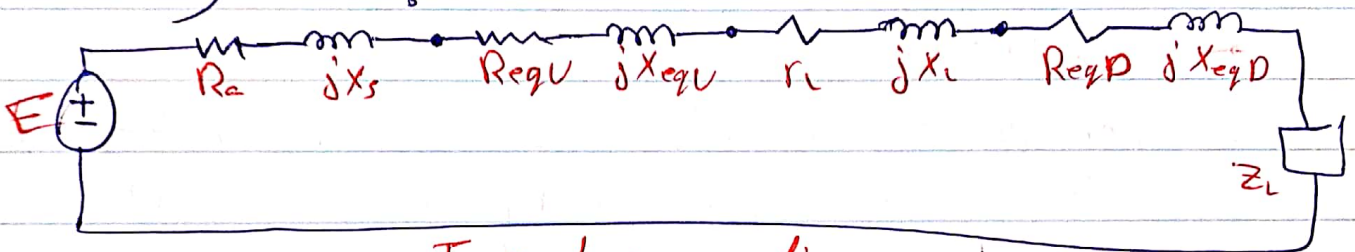- To simplify the analysis, shunt elements are neglected:



Impedance diagram

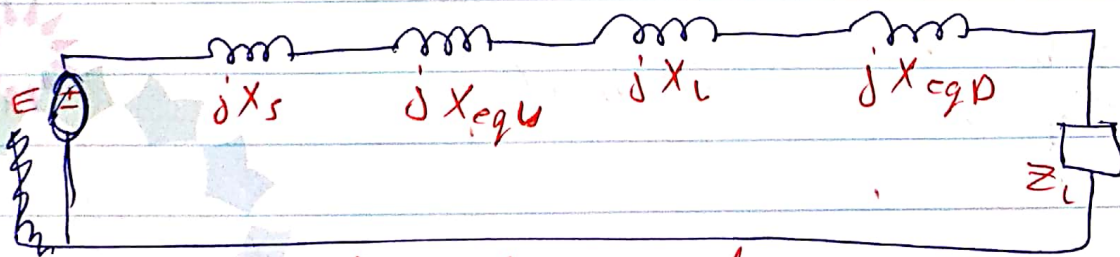- To simplify more, one may neglect resistive elements:



Reactance diagram



24 Jan 2019

• Single-line or ONE-line diagram:

- This diagram is used to show how the components of a given power system are connected to each other, by using only one-line.
- Consequently each component is ~~represented~~ represented by a standard symbol as follows:-

<u>Component</u>	<u>Symbol</u>
Generator	
Motor	
Transformer	
Busbar	
Transmission line	
Circuit breaker	
Current trans.	
Load	

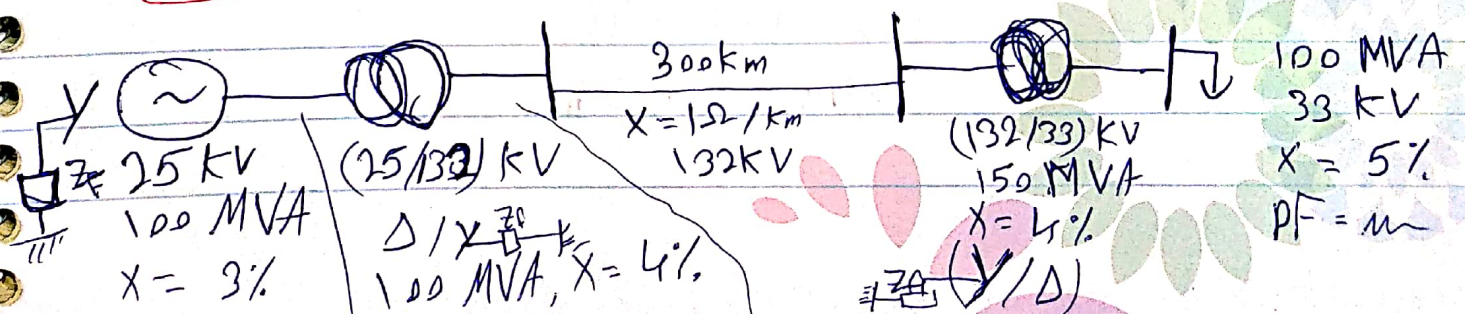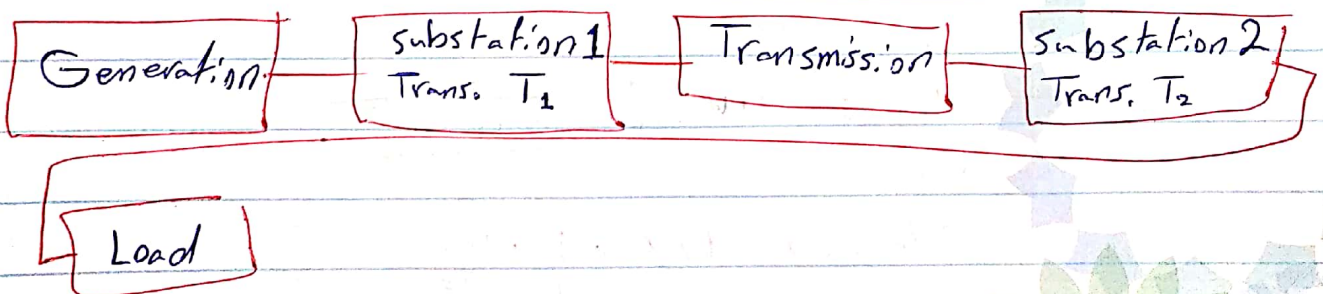→ To illustrate consider the previous system as follows single line diagram



Type of Data given on the diagram depends on the required application (e.g. load flow, fault analysis, ... etc)

$Z_f \equiv$ earthing impedance

Note: The give PU reactance of each component, its base values equals the rating of the component

To solve a given system, you should select a common base for all components.

Then update the given X_{pu} by using

$$X_{new} = X_{old} \times \left(\frac{V_{old}}{V_{new}} \right)^2 \times \frac{S_{new}}{S_{old}}$$

Ex: If common base values are selected at the gen. $V_B = 25 \text{ KV}$, $S_B = 100 \text{ MVA}$

at gen: 3%

at first trans: 4%

at ~~second trans~~ trans line: $X_{pu} = \frac{X}{Z_B} = \frac{300}{\frac{(25 \sqrt{3} \times 10^3)^2}{100 \times 10^6}}$

at second trans: $X = 4\% \times 1 \times \frac{100}{150}$

load: $Z_L = |Z_L| \cos^{-1} \text{PF}$

$$Z_L(\text{PU}) = Z_L / Z_B$$

— Mathematical :

• Bus Admittance Matrix:

This is based on the node equation, and illustrated as follows:

Apply node analysis:


$$\textcircled{1} \rightarrow V_1(-j0.8) + (V_1 - V_2)(-j4) = \bar{I}_1$$

$$-j4 \cdot 8 V_1 + j4 V_2 = \bar{I}_1 \quad \text{--- } \textcircled{1}$$

$$\textcircled{2} \rightarrow (V_2 - V_1)(-j4) + (V_2 - V_3)(-j2.5) = 0$$

$$j4 V_1 - j6.5 V_2 + j2.5 V_3 = 0 \quad \text{--- } \textcircled{2}$$
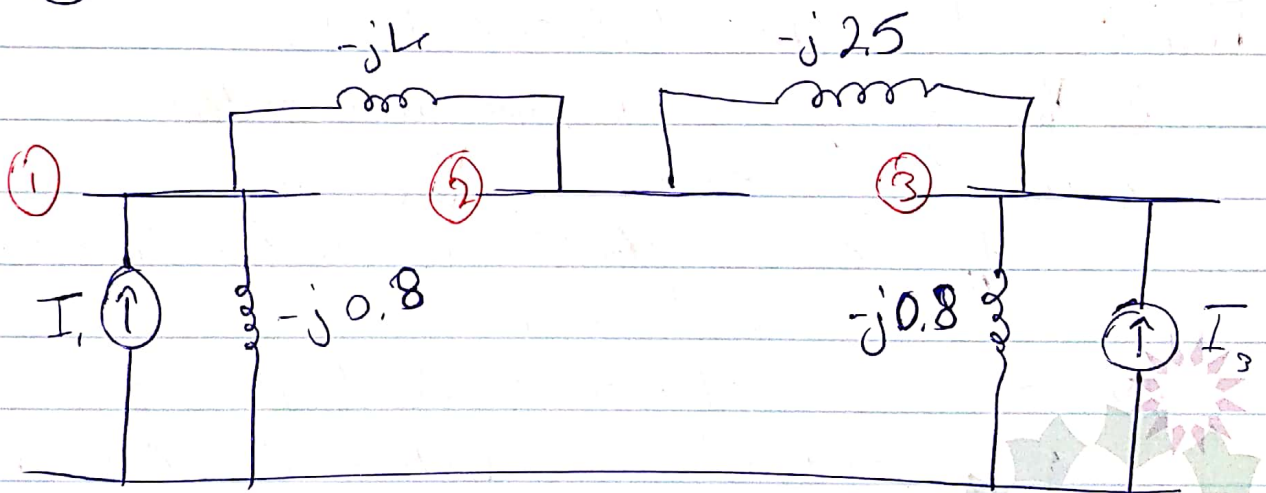
$$\textcircled{3} \rightarrow V_3(-j0.8) + (V_3 - V_2)(-j2.5) = \bar{I}_3$$



The given values are
PU admittances

$$j2.5 V_2 - j3.3 V_3 = \bar{I}_3 \quad \text{--- } \textcircled{3}$$

Now, rewrite the equations in a matrix form

$$\begin{bmatrix} -j4.8 & j4 & 0 \\ j4 & -j6.5 & j2.5 \\ 0 & j2.5 & -j3.3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} I_1 \\ 0 \\ I_3 \end{bmatrix}$$

$$[Y] [V] = [I] \quad \text{--- (1)}$$

Bus Admittance Matrix

Y_{Bus}

From (1), it can be deduced that:-

(1) Y_{Bus} is square and symmetrical matrix

(2) the diagonal element of Y_{Bus} , say

Y_{ii} = sum of admittances connected directly to the i^{th} bus

(3) the non-diagonal elements of Y_{Bus} , say

Y_{ij} = -1 x admittance between i^{th} and j^{th} buses

So, for given system Y_{Bus} can be written directly.

It will be seen that Y_{Bus} will be used in the load flow analysis.

If ① is multiplied by $[Y]^{-1}$

$$[Y][Y]^{-1}[V] = [I][Y]^{-1}$$

$$\therefore [V] = [Y]^{-1}[I]$$

\downarrow
- Z_{Bus} Matrix

$$\therefore [V] = Z_{Bus}[I]$$

Z_{Bus} will be used in fault analysis

• Evaluation of Z_{Bus} :

1) by finding $[Y_{Bus}]^{-1}$

2) by direct method

→ Direct method:

The buses are considered one at a time:

① consider Bus ① $V_1 = Z_a I_1$, $[V_1] = [Z_a][I_1]$

② Add or consider the next bus (i.e. connected to ref or connected to Bus ①)

\therefore for the 2 buses together \rightarrow

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_a & 0 \\ 0 & Z_b \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$\underbrace{\hspace{10em}}_{\text{Evolving } Z_{Bus}}$

③ Then one proceed to modify evolving Z_{Bus} by adding other branches or buses, as follows :-

③.1 adding Z_b from a new bus, say P, to the ref. node

$$\rightarrow \begin{bmatrix} V_1 \\ \vdots \\ V_N \\ V_P \end{bmatrix} = \begin{bmatrix} Z_{org} & 0 \\ \hline 0 \dots 0 & Z_b \end{bmatrix} \begin{bmatrix} I_1 \\ \vdots \\ I_N \\ I_P \end{bmatrix} \quad \text{③.1}$$

③.2 adding Z_b from a new bus, say P, to existing bus K

$$\rightarrow \begin{bmatrix} V_1 \\ \vdots \\ V_N \\ V_P \end{bmatrix} = \begin{bmatrix} Z_{original} & Z_{1k} \\ \vdots & \vdots \\ Z_{k1} \dots Z_{kN} & Z_{kk} \\ \hline & Z_{kk} + Z_b \end{bmatrix} \begin{bmatrix} I_1 \\ \vdots \\ I_k \\ I_p \end{bmatrix} \quad \text{③.2}$$

③.3 adding Z_b from existing bus K to the ref.

(a) create a new row and a column as in ③.2

(b) eliminate the produced $(N+1)$ row and the $(N+1)$ column, to find each element in Z_{hi} (new) in the new matrix as follows:

$$\text{③.3} \rightarrow Z_{hi} \text{ (new)} = Z_{hi} \text{ (old)} - \frac{Z_{h(N+1)} + Z_{(N+1)i}}{Z_{kk} + Z_b}$$

\uparrow row
 \uparrow column
 \downarrow added row
 \downarrow added column


29 Jan 2019

3.4 Z_b is added between two existing buses, say bus j and bus k

$$Z_{bus} = \begin{bmatrix} Z_{org} & | & \begin{matrix} \text{col } j \\ \text{col } k \end{matrix} \\ \hline \text{row } j - \text{row } k & | & Z_{bb} \end{bmatrix} \quad \text{where } Z_{bb} = Z_{jj} + Z_{kk} - 2Z_{jk} + Z_b$$

Eliminate the introduced new row and new column by using $Z_{hi}(\text{new}) = Z_{hi}(\text{old}) - \frac{Z_{h(N+1)} Z_{(N+1)i}}{Z_{bb}}$

Example:

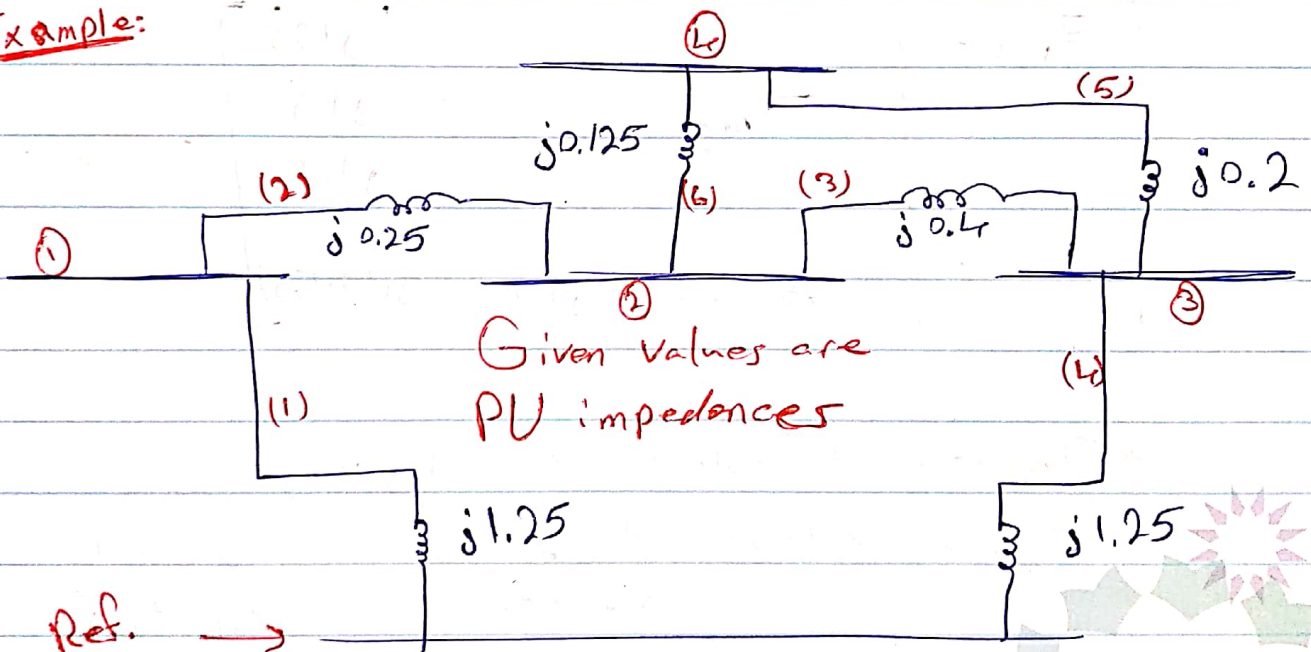

For the given system find Z_{bus} by using Build-up algorithm:



Procedure: start by adding branches sequentially according to their number.

$$1) Z_{bus 1} = [j1.25]$$

$$2) Z_{bus 2} = \begin{bmatrix} j1.25 & j1.25 \\ j1.25 & j(1.25+0.25) \end{bmatrix}$$

$$3) Z_{bus 3} = \begin{bmatrix} j1.25 & j1.25 & j1.25 \\ j1.25 & j1.5 & j1.5 \\ j1.25 & j1.5 & j(1.5+0.4) \end{bmatrix} \leftarrow Z_{org.}$$

$$4) Z_{bus 4} = \begin{array}{c} \begin{array}{c} Z_{org.} \\ \begin{bmatrix} j1.25 \\ j1.5 \\ j1.9 \\ j(1.9+1.25) \end{bmatrix} \end{array} \\ \begin{array}{c} \leftarrow \text{New Column} \\ \leftarrow \text{New Row} \end{array} \end{array}$$

→ Eliminate the L^{th} column and row, by using:-

$$Z_{ni}(\text{new}) = Z_{ni}(\text{old}) - \frac{Z_{n(L)} Z_{(L+i)}}{Z_{LL} + Z_b}, \quad N+1 = L$$

$$Z_{LL} + Z_b = j(1.9+1.25) = j3.15$$

→ Illustration, consider Z_{11} .

$$Z_{11}(\text{new}) = Z_{11}(\text{old}) - \frac{Z_{1L} Z_{L1}}{Z_{LL} + Z_b} = j1.25 - \frac{j1.25 \times j1.25}{j1.9 + j1.25}$$

$$= j0.75397$$

→ Repeat for $Z_{12}, Z_{13}, \dots, Z_{32}, Z_{33}$

$$5) Z_{bus 5} = \begin{bmatrix} j0.75397 & - & j0.49603 \\ - & - & - \\ j0.49603 & - & j0.75397 \end{bmatrix}$$

$$6) Z_{bus 6} = \begin{bmatrix} Z_{bus 5} & \begin{array}{l} 3^{rd} \\ \text{columns} \\ \text{of } Z_{bus 5} \end{array} \\ \hline \begin{array}{l} 3^{rd} \text{ row of } Z_{bus 5} \\ + 0.2 \end{array} & \begin{array}{l} j(0.75397 \\ + 0.2) \end{array} \end{bmatrix}$$

between bus ② and ④

$$7) Z_{bus 7} = \begin{bmatrix} Z_{bus 6} & \begin{array}{l} \text{col 2 of} \\ Z_{bus 6} - \\ \text{col 4 of} \\ Z_{bus 6} \end{array} \\ \hline \begin{array}{l} \text{row 2 of } Z_{bus 6} - \text{row 4 of } Z_{bus 6} \\ + Z_{55} \end{array} & Z_{55} \end{bmatrix}$$

where $Z_{55} = \underbrace{Z_{22} + Z_{44} - 2Z_{24}}_{\text{elements in } Z_{bus 6}} + Z_b (= j1.25)$

8) Finally eliminate the 5th column and row:


$$Z_{n_i} (\text{New}) = Z_{n_i} (\text{old}) - \frac{Z_{N(N+1)} Z_{(N+1)i}}{Z_{55}}, \quad N+1 = 5$$

→ It can be found that

$$Z_{bus 8} = \begin{bmatrix} j0.7166 & - & - & j0.5855 \\ j0.6094 & - & - & j0.6966 \\ j0.5394 & - & - & j0.6695 \\ j0.5805 & - & - & j0.7631 \end{bmatrix}$$

* Revision of PU Systems:

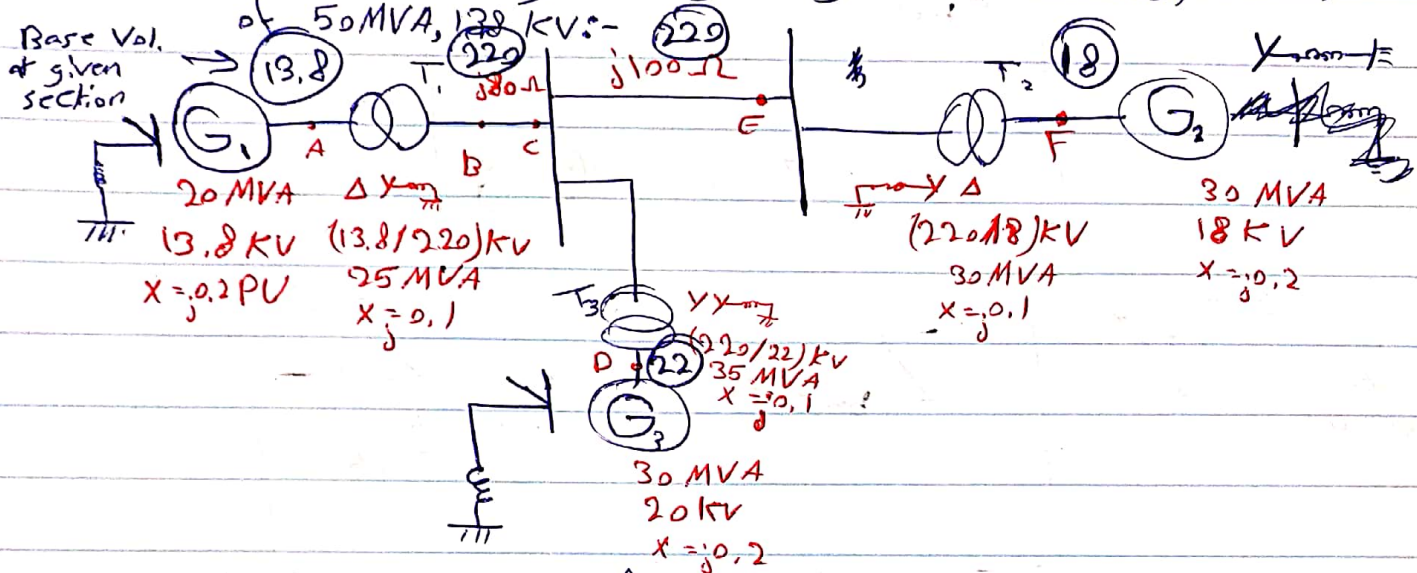Example: For the given single line diagram, evaluate its reactance diagram, by using a common Base at (G₁) location



- The given X PU of a given component is Based on the Rating of that component.

- Modify the given PU X according to the system


base values using $X_{new} = X_{old} \times \left(\frac{V_{old}}{V_{new}}\right)^2 \times \left(\frac{S_{new}}{S_{old}}\right)$

$S_{new} = 50 \text{ MVA}$, $V_{new} = 13.8 \text{ kV}$, S , $V_{old} = \text{Rating of the given component}$

- Identify the base voltage for each section of the system

Component	X_{new}
G ₁	$0.2 \times \left(\frac{13.8}{13.8}\right)^2 \times \frac{50}{20} = 0.5$
T ₁	$0.1 \times 1 \times \frac{50}{25} = 0.2$
line B-C	$Z_b = V_b^2 / S_b = \frac{220^2}{50} = 968$, $X = \frac{80}{968} = 0.083$
line C-E	$\frac{100}{968} = 0.103$

T_2	$0.1 \times 1 \times \frac{50}{30} = 0.17$
T_3	$0.1 \times 1 \times \frac{50}{35} = 0.14$
G_3	$0.2 \times \left(\frac{20}{22}\right)^2 \times \frac{50}{30} = 0.28$
G_2	$0.2 \times 1 \times \frac{50}{30} = 0.33$

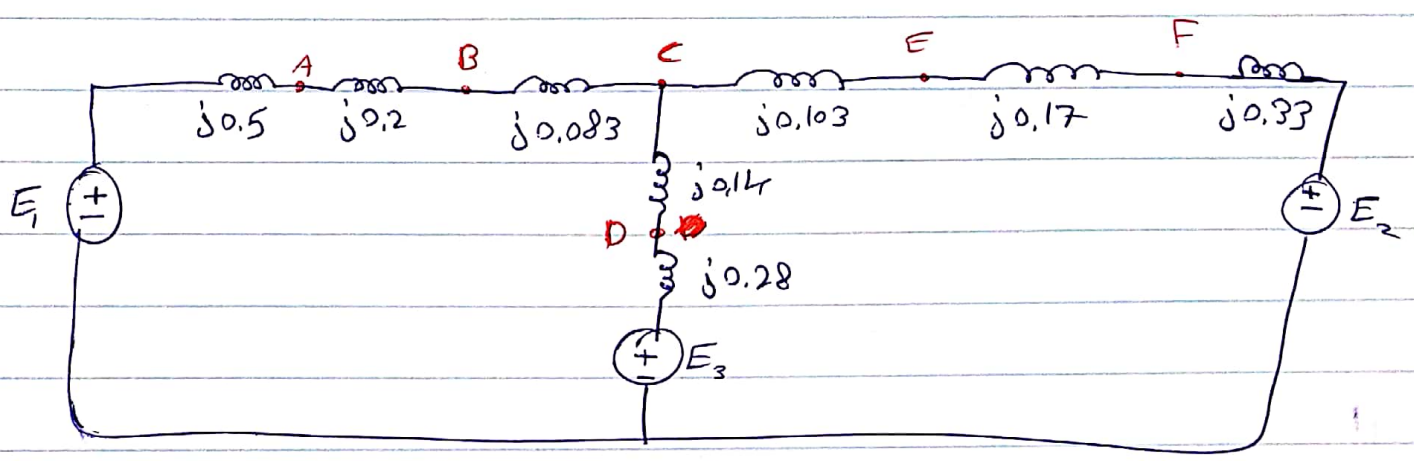

PU Reactance Diagram

- Comment:
- ① Knowing E_1, E_2, E_3 , we can solve the ckt. to find PU current and/or voltage at any point.
 - ② Knowing base values, we can find actual current and voltage values

* Equivalent ckt. of Power system component:

- 3Ph Sync. gen.:

- ① steady state

