

20/1/2019

Sunday

absent - D

22/1/2019

Tuesday

absent - D



24/1/2019

Thursday

AC sources

Types of AC = Sine, Cos, Square, Triangle, DC

$$V = 5 \sin \alpha$$

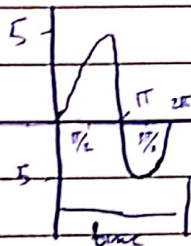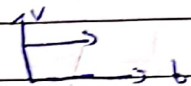

Periodic = Square / cos / sin AC Functions

Period = 2π → VCA angle

Assume $\alpha = (\text{constant}) \times t$

$$\text{Angle} = \alpha = \omega t$$


$$\text{So } 2\pi = \omega t \rightarrow \omega = \frac{2\pi}{T} \text{ rad/sec}$$

angular velocity

Frequency → # of periods / 1 sec

$$f = \frac{1}{T} = \frac{1}{3} = \text{Hz (Hertz)}$$

Example

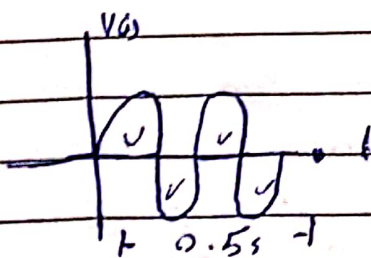


2 periods so $f = 2\text{Hz}$

$$\omega = \frac{2\pi}{T} = 2\pi f = 4\pi \text{ is the angular velocity (angular frequency)}$$

24/1/2019

Thursday

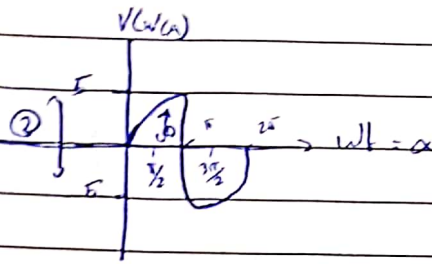

① Peak \rightarrow zero to max = 5

② Peak to peak \rightarrow min to max = 10

③ amplitude \rightarrow Distance between avg and max

• Avg for periodic function

$$is = \frac{1}{T} \int_0^T V(t) dt$$


to find amplitude

$$\rightarrow \frac{1}{T} \int_0^T 5 \sin wt dt = \frac{1}{T} \cdot 5 \left[\frac{T}{2\pi} [\cos \alpha - \cos(\frac{2\pi \alpha}{T})] \right] = 0$$

so $A = Avg = 5$

DC value

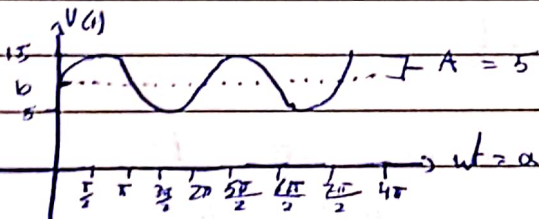
Ex: $V(t) = 10 + 5 \sin wt$, find P to P, A



Peak = 15V

Peak to Peak = 10V

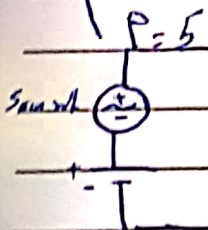to find A, $V_{avg} = \frac{1}{T} \int_0^T 10 + 5 \sin wt dt = \frac{1}{T} \cdot 10T + 0 = 10$
 $A = 5V$



for example 1: find $V(t)$ where Peak = 5

$F = 50 \text{ Hz}$

$$V(t) = 2 \sin(2\pi \times 50t) = 5 \sin(100\pi t)$$

2.1 if $P = 5, A = 3, F = 50 \text{ Hz}$

$$\therefore V(t) = 2 + 3 \sin wt$$

Thursday

24/1/2019

Example: A Generator rotates at speed of $300^\circ/\text{sec}$, how long does it take to complete 360° ?

↳ find T

$$\begin{array}{l} 300 \rightarrow \text{ls} \\ 360 \rightarrow \text{xs} \end{array} \quad \text{xs} = \frac{360}{300} = 1.2 \text{ seconds} = T$$

$$f = \frac{1}{T} = \frac{5}{6} \text{ Hz}$$

$$\omega = 2\pi f = \frac{10\pi}{6}$$

Example: sinusoidal current with an A of 10A, and $T = 0.12$. Determine the time at which $i = 5A$.

Solution:

$$i(t) = 10 \sin \omega t + \phi \quad \leftarrow \text{assume no outside DC source}$$

$$\omega = \frac{2\pi}{T} = \frac{2\pi}{0.12} \text{ rad/s}$$

$$5 = 10 \sin \left(\frac{2\pi t}{0.12} \right), \quad t = \frac{0.12}{2\pi} \cdot \sin^{-1}(0.5)$$

$$t = 0.01 \text{ sec}$$

thus when $t = 10 \text{ ms}$

no H.W

sunday 2)


27/1/2019

Ex: if a Gen is rotating at speed $300^\circ/\text{sec}$, how long does it take to complete 360° .

↳ phase shift

$$v(t) = A \cdot \sin(\omega t + \phi) + B, \quad \phi \text{ phase shift}$$


$$V(t) = A \sin(\omega t + \phi) + B$$

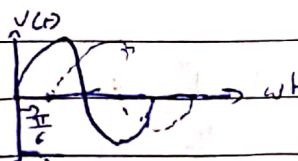

phase shift ϕ

Sunday

27/1/2019

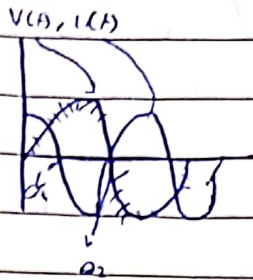

① cross zero

② \rightarrow \leftarrow

to Differentiate

① same Freq


② same ω

$$\phi = \text{Phase} = \phi_2 - \phi_1$$

\rightarrow i leads v

\leftarrow v lags i

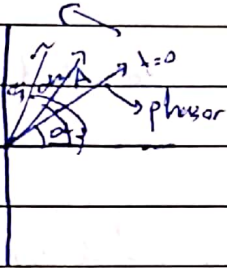phasors: forget rid of time domain
make them all frequency domain



$\omega = \text{constant}$

$$\alpha = \omega t$$

$$x\text{-axis} = A \cos \alpha = A \cos \omega t$$


$$y\text{-axis} = A \sin \alpha = A \sin \omega t$$

$$A \cos(\omega t + \phi) = A \angle \phi$$

t.D


P.D

Polar form

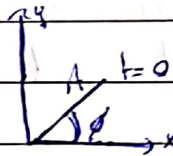

cosine

always proj
on x axis
cos

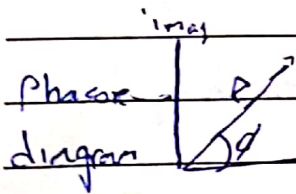

$$= A \cos \phi + j A \sin \phi$$

$$\text{so if } \phi = 30^\circ, A = 5$$

$$= 5(\cos 30) + j 5 \sin 30 = 2.5\sqrt{3} + j 2.5$$

to go from Rec to Polar

$$\text{Real } a + jb$$

Rectangular
form

$$|A| = \sqrt{a^2 + b^2}$$

$$\phi = \tan^{-1} \frac{b}{a}$$

tuesday - D

Thursday

31 / 1 / 2019

circuits 102

Ex :-


Determine phase angle between

$$v(t) = 30 \cos(\omega t - 20^\circ)$$

$$i(t) = 25 \sin(\omega t - 70^\circ)$$

for AC phasor

$$\cos(\omega t - 70 - 10)$$

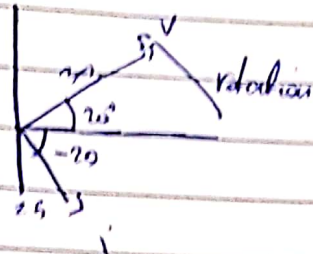

$$V(t) = 30 \angle 20^\circ$$

$$i(t) = 25 \angle -70^\circ$$

V leads i by 40°

AC \Rightarrow sinusoidal signal

to get rid of differential

we go to phasor

source \Rightarrow to phasor

$$V_L = L \frac{di}{dt}$$

$$i_C = C \frac{dv}{dt}$$

R
 C
 L

\rightarrow impedance (Z) can

$$Z_L = Z = \frac{V}{I}$$


$$\int di = \int \frac{1}{L} v_L dt$$

$$i = \frac{1}{L} \int_0^t v_L(t) dt = \frac{A}{\omega L} \sin \omega t = \frac{A}{\omega L} \angle -90$$

$A \cos \omega t \Rightarrow A \angle 0$

$$Z_L = \frac{A \angle 0}{\frac{A}{\omega L} \angle -90} = \omega L \angle 90 = j \omega L$$

same for C

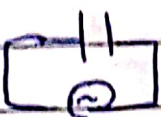

$$i_C = \frac{1}{C} \frac{dv}{dt} = \frac{1}{C} A \omega \cos \omega t = \frac{A \omega}{C} \angle 90$$

$$= \frac{A \omega}{C} \angle +90$$

$A \cos(\omega t) \Rightarrow A \angle 0$

Thursday


21/1/2019

Circuits 102

to graph C and L
For L

$$V = A \angle 0$$
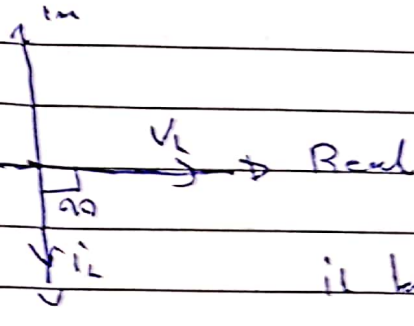
$$i = \frac{A}{\omega L} \angle -90^\circ$$




i_L lags V_L by 90°

For C

$$V_C = A \angle 90^\circ$$

$$i_C = A \omega C \angle -40^\circ$$

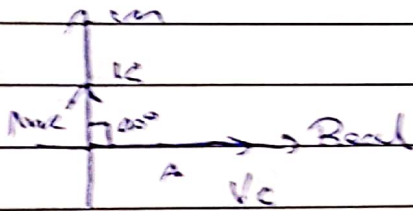


i_C leads V_C by 90°

Series impedance

$$Z = Z_1 + Z_2 \Omega$$

parallel impedance

$$Z = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

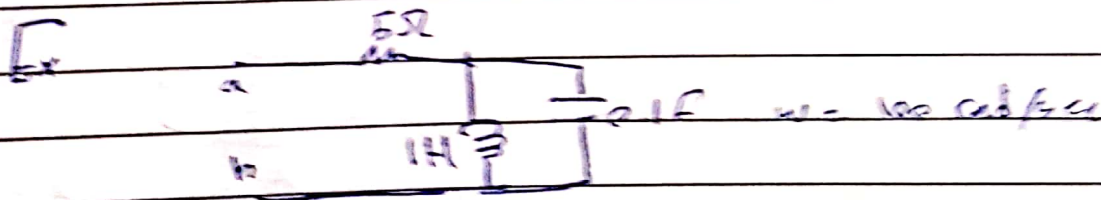

$Z_{eq} = ?$

$$Z_L = j\omega L \Rightarrow j(100)(1) = j100 \Omega$$

$$Z_C = \frac{1}{j\omega C} \Rightarrow \frac{1}{j(100)(0.1)} = -j1 \Omega$$

$$Z_{eq} = (Z_L \parallel Z_C) + Z_R$$

$$\frac{j100 \cdot (-j1)}{j100 - j1} = \frac{100}{j99} = -j1.01 \Omega + 5 = 5 - j1.01 \Omega$$

$$= 5 \angle -11.5^\circ$$

21/1/2019

Thursday

1- Real part in impedance is called Resistive part

2- Imaginary part // // // // Reactant part (Reactance)

$$Z = R \pm jX = |Z| \angle \theta$$

If + then Z is an inductive load (V leads I)

If - then Z is an capacitive load (I leads V)

$$\text{Power factor } \frac{V}{I} = \frac{|V| \angle \theta_1}{|I| \angle \theta_2} = \frac{|V|}{|I|} \angle \theta_1 - \theta_2$$

$$\frac{1}{R} \Rightarrow \sigma \text{ (conductivity) } (\Omega^{-1})$$

$$\frac{1}{Z} \Rightarrow Y \text{ (admittance) } (\Omega^{-1})$$

$$\text{If } Z = R + jX$$

$$Y = \frac{1}{R + jX} = \frac{R - jX}{R^2 + X^2} = \frac{R}{R^2 + X^2} - j \frac{X}{R^2 + X^2}$$

Real part (Conductance) Imag part (Susceptance)

$$\text{So } Y = G + jB$$

the + sign is conductance
Capacitive

ad - sign inductive

5/2/2019

Lucas Jones

ch 11

phasor


AC, sinusoidal source

$|I| \angle \theta_i$

$|V| \angle \theta_v$

$Z = |z| \angle \theta_z$

AC Power

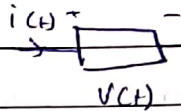

$P(t) = v(t)i(t) \rightarrow$ watt
 ↪ instantaneous power

$v(t) = V_m \cos(\omega t + \theta_v)$

$i(t) = I_m \cos(\omega t + \theta_i)$

$P(t) = V_m I_m \cos(\omega t + \theta_v) \cdot \cos(\omega t + \theta_i)$

trig id

$\cos x \cdot \cos y = \frac{1}{2} [\cos(x-y) + \cos(x+y)]$

$$P(t) = \frac{V_m I_m}{2} \left[\underbrace{\cos(2\omega t + \theta_v + \theta_i)}_{\text{freq}} + \underbrace{\cos(\theta_v - \theta_i)}_{\text{constant (Real power)}} \right]$$

so $\frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = P_{avg}$


$$P_{avg} = \frac{1}{T} \int_0^T P(t) \cdot dt = \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \left[\cancel{\cos(2\omega t + \theta_v + \theta_i)} + \cos(\theta_v - \theta_i) \right] dt$$

$$= \frac{1}{T} \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \cdot T = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

5/3/2019

Tuesday

$p(t)$ if $\theta_V = 0$

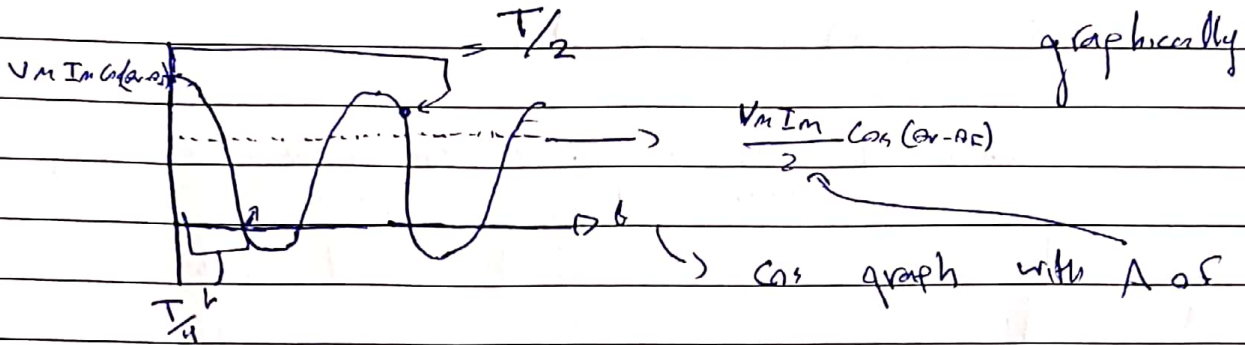

$$P(t) = \frac{V_m I_m}{2} \cos(2\omega t + \theta_1) + \frac{V_m I_m}{2} \cos(\theta_1)$$

at $\omega t = 0 \Rightarrow P(0) = V_m I_m \cos(\theta_1)$

to find P_{max} when $2\omega t + \theta_1 = \pi$

$$t = \frac{2\pi - \theta_1}{2 \times \frac{2\pi}{T}} = T - \frac{\theta_1}{2T}$$


to find P_{min} when $\cos(2\omega t + \theta_1) = -\cos(\theta_1)$

$$\cos(2\omega t + \theta_1) = \cos(\theta_1 + 180^\circ)$$

$$\therefore 2\omega t + \theta_1 = \theta_1 + \pi$$

$$t = \frac{\pi}{2\omega} = \frac{\pi \cdot T}{2 \cdot 2\pi}$$

$$t = \frac{T}{4}$$

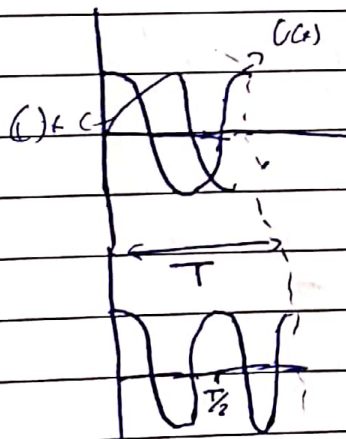

P takes half the time to (of the $V \cos I$) complete

5/2/2019

Tuesday

$$P = \frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i) + \cos(\theta_v - \theta_i)$$

$$\cos(2\omega t + \theta_v + \theta_i + \theta_v - \theta_v) = \cos(2\omega t + 2\theta_v - (\theta_v - \theta_i))$$

apply trig idc

$$\cos(x-y) = \cos x \cos y + \sin x \sin y$$

$$\cos(2(\omega t + \theta_v)) \cos(\theta_v - \theta_i) + \sin(2(\omega t + \theta_v)) \sin(\theta_v - \theta_i)$$

$$P(t) = \frac{V_m I_m}{2} \left[\cos(\theta_v - \theta_i) + (\cos(\theta_v - \theta_i) \cos 2(\omega t + \theta_v) + \sin(\theta_v - \theta_i) \sin 2(\omega t + \theta_i)) \right]$$

$$P_1(t) = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \left[1 + \cos 2(\omega t + \theta_v) \right]$$



$1 + (-1 \rightarrow 1) \Rightarrow 0$
 $-90 < \theta_v - \theta_i < 90$

$P_1(t) \geq 0$ = real power active power

$$P_2(t) = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \sin 2(\omega t + \theta_v)$$

$90 < \theta_v - \theta_i < 180$
 reactive power

$Q \Rightarrow \text{VAR reactive}$

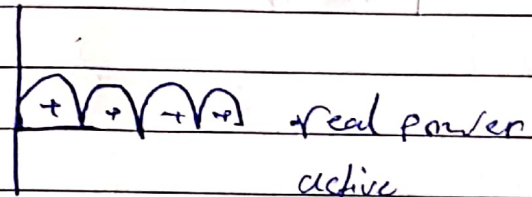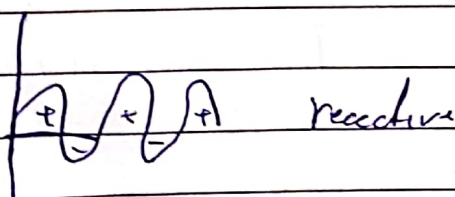

Thursday


7/2 / 2019

Circuit 102

A.C. Power

$$① P(t) = \frac{V_m I_m}{2} \left[\cos(\omega t - \theta_i) + \cos(2\omega t + \omega t + \theta_i) \right]$$


$P_1(t)$:- Real power

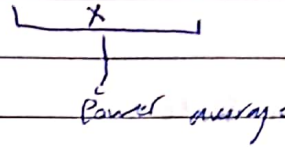

$$② P(t) = P_1(t) + P_2(t)$$

$$P_1(t) = R.P = \frac{V_m I_m}{2} \cos(\omega t - \theta_i) \left[1 + \cos 2(\omega t + \theta_i) \right]$$
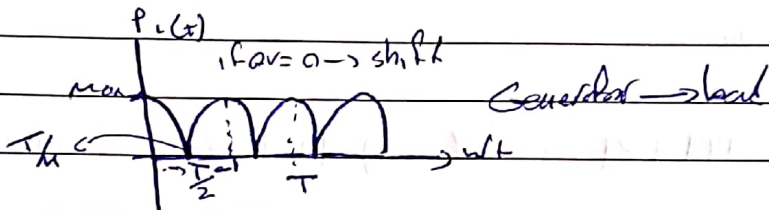
$$-90^\circ \leq \theta_v - \theta_i \leq 90^\circ \Rightarrow P_1(t) \geq 0$$



$$P_{1, \text{max}} = V_m I_m \cos(\theta_v - \theta_i)$$

Power happens when

$$\cos(2\omega t + 2\theta_i) = -1$$

$$2(\omega t + \theta_i) = \pi$$

$$t = \frac{\pi}{2\omega} - \frac{\theta_i}{\omega} = \frac{T}{4}$$


$P_2(t)$ = reactive power $\Rightarrow VAr$

$$= \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \sin 2(\omega t + \theta_i)$$

$90^\circ \leq \theta_v - \theta_i \leq 40^\circ$

$$\text{if } 0 \leq \theta_v - \theta_i \leq 90$$
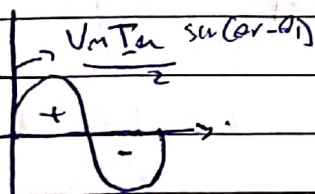
$$P_2(t) = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \geq 0 \quad (\text{inductive load})$$



+ Generator \rightarrow load
 - load \rightarrow Generator

because
 i lags V
 $\text{if } (\theta_v - \theta_i) > 0$
 $Q > 0$


$Q_{avg} = 0$
 (no power consumption)

2/2/2019

Phasors

$$P_{avg} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$|Q| = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i)$$

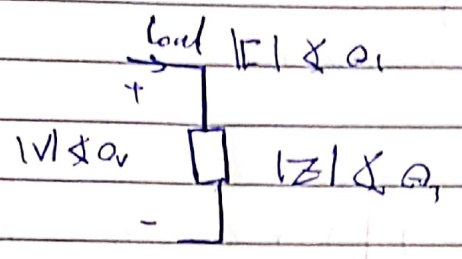

$$\text{so } |Z| = \frac{|V|}{|I|} = \frac{V_m}{I_m}$$

$$\theta_z = \theta_v - \theta_i$$

$$\vec{V}_z = I Z = (|I| \angle \theta_i) (|Z| \angle \theta_z) \quad \theta_z = \theta_v - \theta_i$$

$$= |I| |Z| \angle \theta_v$$

$$P_2(t) = v(t) i(t) = |I| |Z| \cos(\omega t + \theta_v) |I| \cos(\omega t + \theta_i)$$

$$= \frac{|I|^2 |Z|}{2} [\cos(2\omega t + \theta_v + \theta_i) + \cos(\theta_v - \theta_i)]$$

$$P_{avg} = \frac{I_m^2}{2} |Z| \cos(\theta_v - \theta_i)$$

$$|Z| \cos(\theta_z) = R$$

$$Z = R + jX$$

$$P_{avg} = \frac{I_m^2}{2} R \quad \rightarrow \text{on ahead (use on circuits) component}$$

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \quad \therefore, V_m = I_m |Z|$$

$$|Q| = \frac{I_m^2 |Z|}{2} \sin(\theta_z) = \frac{I_m^2}{2} X \quad \begin{matrix} \times \text{ inductive w/ } |Z| \\ \text{or } X = \frac{1}{\omega C} \\ \text{if capacitor} \end{matrix}$$


$X_L = \frac{1}{\omega C}$	Z = R + jX → inductor i lags v, Q > 0
$X_C = \omega L$	
	Z = R - jX → capacitor i leads v, Q < 0

2/2/2010

Thursday

Circuits 102

Ex

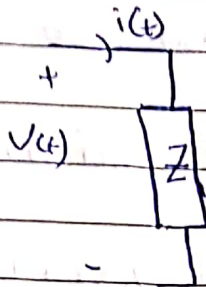

$$V(t) = 100\sqrt{2} \cos(\omega t)$$

$$i(t) = \sqrt{2} \cos(\omega t - \phi_1)$$

- (a) Avg. Real Power 3 cases
- (b) Reactive Power $\phi_1 = 0$
- (c) Peak to Peak Power $\phi_1 = 60$
 $\phi_1 = 80$

1-case $\phi_1 = 0$ (Resistive)

$$(a) P_{avg} = \frac{1}{2} V_m I_m \cos(\phi_1)$$

$$= \frac{1}{2} \cdot 100 \cdot \sqrt{2} \cdot \sqrt{2} = 100 \text{ watt}$$

$$(b) \text{Reactive } P = 0 \text{ (Resistive Load)}$$

$$(c) \text{Peak to Peak } P_{max} = V_m I_m \frac{1}{2} (\cos(\phi_1 - \phi_1) + \cos(2\omega t))$$

$$= 200$$


$$= V_m I_m \cdot 2 \cdot \frac{1}{2} = 200 \text{ watt}$$

$$P_{avg} = P_{in} - P_{L} = 200 - 0 = 200 \text{ watt}$$

$$P_{avg} = \frac{V_m I_m}{2} [\cos(\phi_1 - \phi_1) + \cos(2\omega t - \phi_1)]$$

$$= 0$$

Case 2 $\phi_1 = 60$

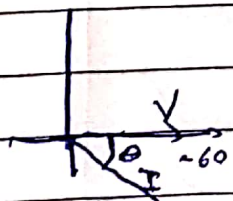

$i \text{ lag } V$

$$(a) P_{avg} = \frac{1}{2} V_m I_m \cos(\phi_1 - \phi_1)$$

$$= \frac{1}{2} \cdot 100 \cdot \sqrt{2} \cdot \sqrt{2} \cdot \cos 60$$

$$= 50 \text{ watt}$$

$$(b) P_{power} = Q(t) = \frac{V_m I_m}{2} \sin(\phi_1 - \phi_1) \sin(2\omega t)$$

$$= \frac{100 \cdot \sqrt{2} \cdot \sqrt{2}}{2} \sin(60) \sin(2\omega t)$$

Five Apple

Thursday

7/2/2019

② AC Power

$$P(t) = 50 + 100 \cos(2\omega t - 60^\circ)$$

$$P_{avg} = 50 - 100 = -50$$

AC Power

$$P(t) = v(t) i(t)$$

$$P_{avg} = 50 + 100 = 150$$

$$① P(t) = \frac{V_m I_m \cos(\omega t - \theta_i)}{2}$$

$$P_{tot} = 150 - (-50) = 200 \text{ watt}$$

Pavg

$$+ \frac{V_m I_m \cos(2\omega t + \theta_v + \theta_i)}{2}$$

P_{tot} Power Does not
Depend on phase
shift

$$\frac{P_{avg}}{2} = \frac{1}{2} I_{rms}^2 \cdot R$$

$$② P(t) = \frac{V_m I_m \cos(\omega t - \theta_i) [1 + \cos 2(\omega t + \theta_v)]}{2}$$

Real Power

$$+ \frac{V_m I_m \sin(\omega t - \theta_i) \sin 2(\omega t + \theta_v)}{2}$$

Reactive, $Q(t)$

$$Ex: \therefore v(t) = 80 \cos(\omega t + 20^\circ)$$

$$i(t) = 15 \sin(\omega t + 60^\circ) = 15 \cos(\omega t - 30^\circ)$$

① Instantaneous Power $P(t)$

② Avg Power

③ Reactive

$$② P(t) = \frac{80 \times 15}{2} \cos(20 - (-30)) + \frac{80 \times 15}{2} \cos(2 \times \omega t + 20^\circ - 30^\circ)$$

$$= \frac{600 \cos(50)}{2} + \frac{600 \cos(2\omega t - 10^\circ)}{2}$$

$$\text{Avg Power} = 385.52 \text{ W}$$

12/1 2015

Sunday


(c) Reactive Power (Q(t))

$$Z = \frac{V}{I} = \frac{60 \angle 20}{15 \angle -30}$$


$$= 600 \sin(20) \sin 2(60t + 20)$$

$$= \frac{80}{15} \angle +10$$

+ so it's an inductive

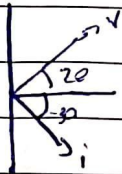

(I lags V) inductive

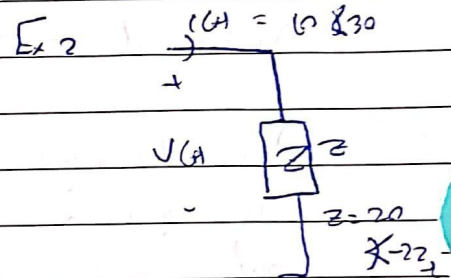

Power consumed by Z

(1) $P_{avg} = \frac{1}{2} I_m V_m \cos(\theta_v - \theta_i)$

$\theta_2 = \theta_v - \theta_i$

(2) $P_{avg} = \frac{1}{2} I_m^2 R$ or (3) $\frac{1}{2} V_m^2 / R$

to get R

$$Z = 20 \cos(-22) + j 20 \sin(-22)$$

R → Capacitive

$$R = |Z| \cos \theta_2$$

(1) $V = IZ = (10 \angle 30)(20 \angle -22)$
 sol $= 200 \angle 8^\circ$

$$P_{avg} = \frac{1}{2} (200) \times 10 \cos(8 - 30) = 1000 \cos(-22) = 927 \text{ W}$$


(2) $P_{avg} = \frac{1}{2} (10)^2 \times 20 \cos(-22) =$

find Q(t) → $\frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) \sin 2(\omega t + \theta_v)$
 Amp of Q(t)

$$\frac{1}{2} I_m^2 X, X = |Z| \sin \theta_2 = 20 \sin(22) = 7.49213$$

10/2/2019

Sunday

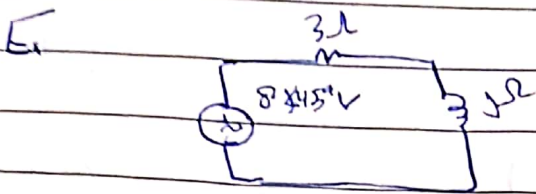

- (a) Find Avg power on R_L
- (b) // // // by the source
- (c) Find reactive power Q
- (d) Find $P(t)$ source

(a) 1- $P_{avg\ source} = 0$, 2- $P_{avg\ R} = \frac{1}{2} I_m^2 R$

(b) It's the same as $P_{avg\ R}$ but

$$I = \frac{8 \angle 45}{3 + j}$$

$$= \frac{1}{2} (2.53)^2 (3) = 9.6 \text{ watt}$$

$$= 2.53 \angle 26.8$$

$$P_{avg} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} (8)(2.53) \cos(45 - 26.5) = 9.6 \text{ watt}$$

(c) $Q(t) = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) \sin(2\omega t + 2\theta_v)$

$$= \frac{1}{2} (8)(2.53) \sin(45 - 26.56^\circ) \sin(\omega t + 45)$$

$Q_R = 0$

$$Q = \frac{1}{2} I_m^2 X$$

$$= \frac{1}{2} (2.53)^2 \times j = j$$


(d) $P(t) = P_1(t) + P_2(t)$

$$P_1(t) = 9.6 [1 + \cos 2(\omega t + 45)]$$

$$P_2(t) = Q(t)$$

10/2/2019

Sunday

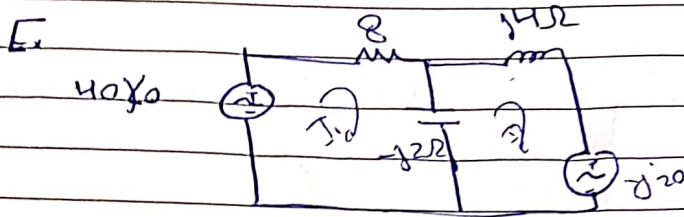

- (a) Find avg power on each element
- (b) Find Q(t) on each element

(a) Power on each $I = 0$ | mesh analysis

$$P_{avg} = \frac{1}{2} I_m V_m \cos(\theta) \\ = \frac{1}{2} I_m^2 R \\ = \frac{1}{2} 5^2 \cdot 8 = 100 \text{ watt}$$

$$(8 - j2) I_1 - I_2 (-j2) = 40 \angle 0 \\ -I_1 (-j2) + I_2 (-j2 + j4) = -j20$$

$$P_{avg} = Q(t) = \frac{1}{2} I_m^2 X \cdot \sin(2\omega t + \theta)$$

$$I_1 (8 - j2) + I_2 (j2) = 40 \angle 0 \dots \textcircled{1} \\ I_1 (j2) + I_2 (j2) = -j20 \dots \textcircled{2}$$

using Kronecker

$$A X = B$$

$$A = \begin{bmatrix} 8 - j2 & j2 \\ j2 & j2 \end{bmatrix}$$

$$X = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = A^{-1} B \quad B = \begin{bmatrix} 40 \\ -j20 \end{bmatrix}$$

~~$I_1 = \dots$~~
 ~~$I_2 = \dots$~~

$$I_1 = \frac{1}{8 + j16} [(-8 + j2) 40 + j2(-j20)]$$

$$A^{-1} = \frac{1}{\Delta} \begin{bmatrix} - & - \\ - & - \end{bmatrix}$$

$$\Delta = (8 - j2)(j2) - j2(j2)$$

$$I_2 = \frac{1}{8 + j16} [j2(40) - j2(-j20)]$$

$$= 16j + 4 + 4 - 8 + j16$$


$$X = A^{-1} B = \frac{1}{8 + j16} \begin{bmatrix} -8 + j2 & j2 \\ j2 & j2 \end{bmatrix} \begin{bmatrix} 40 \\ -j20 \end{bmatrix}$$

$$A^{-1} = \frac{1}{8 + j16} \begin{bmatrix} -8 + j2 & j2 \\ j2 & -j2 \end{bmatrix}$$

14/2/2019

Thursday

E. continue previous

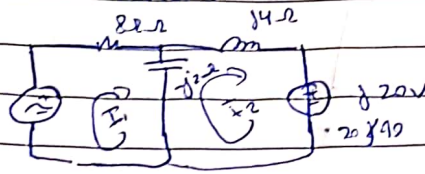

$$40 = I_1(8 - j2) + j2I_2$$

$$-j20 = j2I_1 + j2I_2$$

$$I_1 = 5 \angle 53.14^\circ$$

$$I_2 = 13.6 \angle -163^\circ$$

$$P_{avg} L = 0$$

$$P_{avg} R = \frac{1}{2} (5^2) \times 8 = \frac{400}{4} \text{ watt}$$

Calc

$$P_{avg} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$= -\frac{1}{2} (40)(5) \cos(0 - 53.14) = -60 \text{ watt}$$

$$P_{avg} = \frac{1}{2} (13.6)(20) \cos(90 - (-163))$$

$$= -40 \text{ watt}$$

$$b) P_{40V} = -\frac{1}{2} (40)(6) \sin(0 - 53)$$

$$P_{12} = \frac{1}{2} I^2 R = \frac{1}{2} (I_1 - I_2)^2 (-2)$$

$$P_{20} = +\frac{1}{2} (20)(13.6) \sin(90 - 162)$$



$$P_{14} = \frac{1}{2} (13.6)^2 \times 4$$

Power Avg

can be 2 cases

Case 1

Case 2

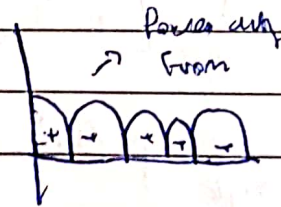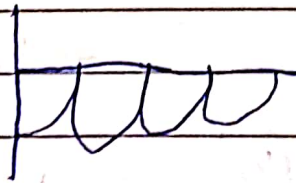


14/7/2019

Thursday

Circuits 102

Differential (P) H₂

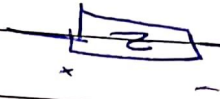

$$V(t) = 3 \cos(10t) + 5 \cos(20t)$$

$$P_{avg} = P_{avg_1} + P_{avg_2} + \dots$$

$$= \frac{1}{2R} [V_{m1}^2 + V_{m2}^2 + \dots]$$

$R = 4$

$$P_{avg} = \frac{1}{2 \times 4} [6^2 + 5^2]$$

$$E_{\infty} V(t) = 3 \cos(10t) + 4 \cos(10t - 20^\circ) + 5 \cos(20t)$$

$$= 3 \angle 0 + 4 \angle -20$$

$$= 6.7 \angle -17$$

$$P_{avg} = \frac{1}{2 \times 4} [(6.7)^2 + (5)^2] \checkmark$$