

10 marks) Q(1):

(a) (10 marks) For the circuit shown in Fig.1.a, find the equivalent capacitance between terminals a and b.

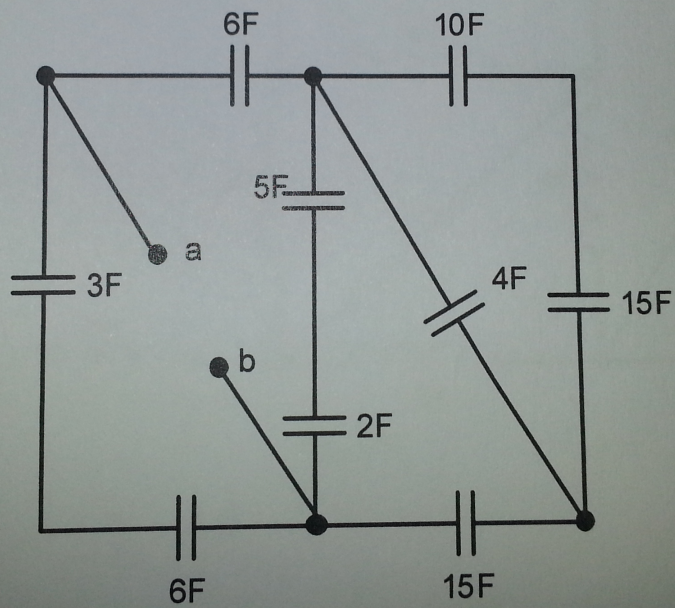


Fig. 1.a

10, 15 are in series.

Second exam
course


Fig. 1.a

Second exam
Summer course
2014-2015

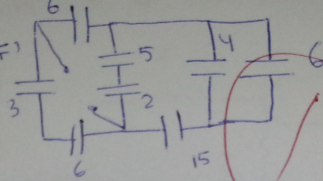Q1) Part a.

10, 15 are in series

$$\frac{10 \times 15}{10 + 15} = 6 \text{ (F)}$$




4, 6 are in parallel

$$4 + 6 = 10 \text{ (F)}$$

10, 15 in series
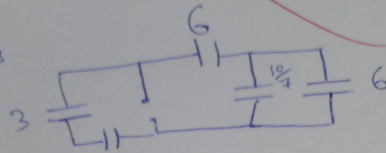
$$\frac{10 \times 15}{10 + 15} = 6 \text{ (F)}$$




5, 2 are in series

$$\frac{5 \times 2}{5 + 2} = \frac{10}{7} \text{ (F)}$$

$\frac{10}{7}$, 6 are in parallel

$$\frac{10}{7} + 6 = \frac{52}{7} \text{ (F)}$$


$\frac{52}{7}$, 6 are in series

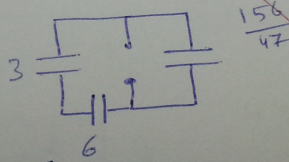

$$\frac{\frac{52}{7} \times 6}{\frac{52}{7} + 6} = \frac{156}{47} \text{ (F)}$$

3, 6 are in series
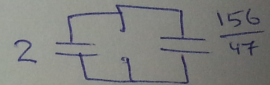
$$\frac{3 \times 6}{3 + 6} = 2 \text{ (F)}$$



2, $\frac{156}{47}$ are in parallel

$$2 + \frac{156}{47} = \frac{250}{47} \text{ (F)}$$

$$= 5.319 \text{ (F)}$$

(10 marks) For the circuit shown in Fig.1.b, find the equivalent inductance between terminals a and b.

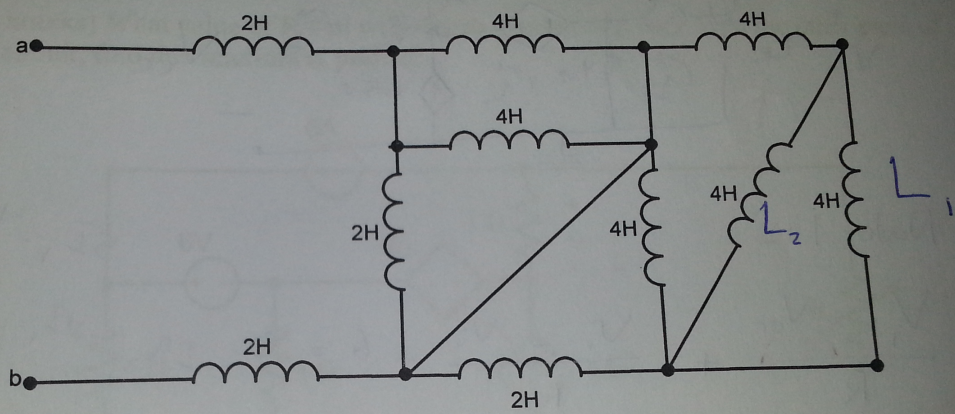


Fig.1.b


In the right: -

L_1 & L_2 are in parallel.

$$L_{eq} = 2H$$

L_{eq} is in series with the 4H inductor at the top.

$4+2=6H$

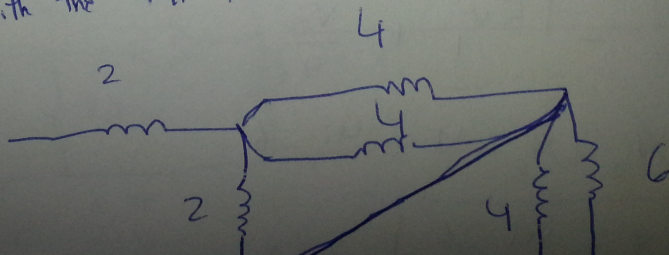

Q1) Part b
Summer
2014-2015

Q1) Part b

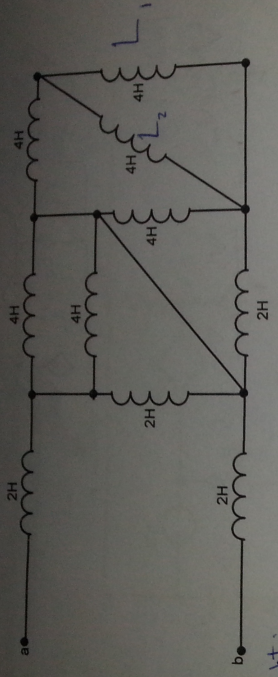


Fig. 1.b

In the right:-

As L_1 & L_2 are in parallel.

$L_{eq} = 2H$

L_{eq} is in series with the 4H inductor at the top.

$4+2=6H$

$4 || 4 = 2H$





$6 || 4 = 2.4H$

$2.4 + 2 = 4.4H$

$2 || 2 = 1H$

All are in series


~~$2+2+1=5H$~~

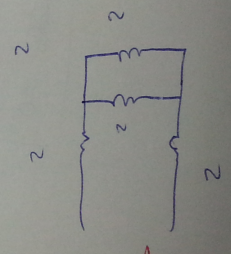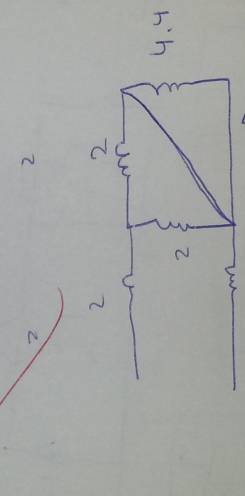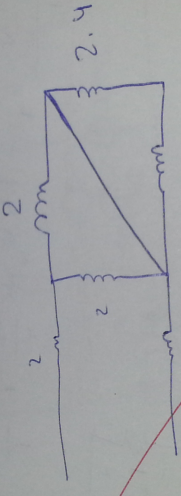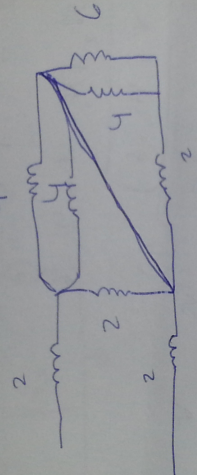


4.4 is cancelled where it's connected into short circuit.

(25 marks) Q(2): For the circuit shown in Fig. 2.

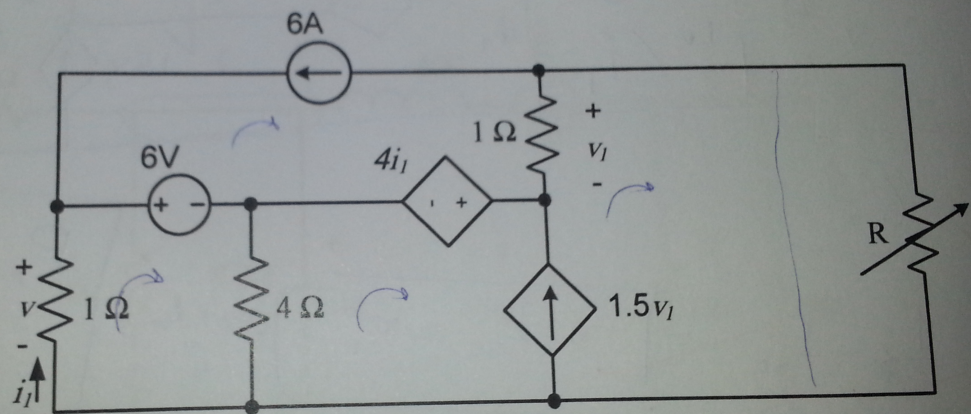
- (a) (15 marks) Find the Thévenin equivalent circuit for the circuit seen by the variable resistor R .
- (b) (10 marks) What value of R that will absorb maximum power from the other parts of the circuit, find this maximum power?



Open CKI 3-

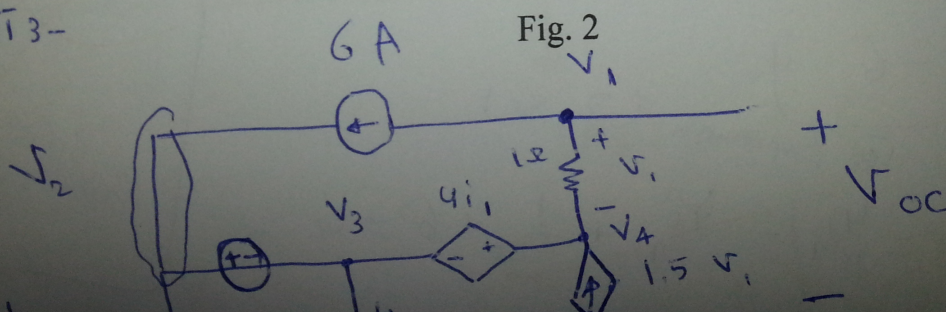

Q2 Second Exam
Summer 2016
2014-2016

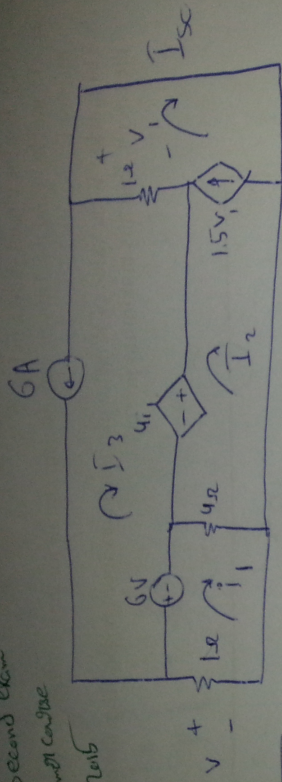

Mesh 3

$$I_2 = -6$$

$$V_1 = 1 - I_{sc} = -6 - I_{sc} = V_1 \quad \text{Ohm's Law}$$

$$\text{Mesh 1} \quad 5i_1 - 4i_2 = -6 \quad \text{Supermesh (2, sc)}$$

$$4I_2 - 4i_1 = 4i_1 + I_{sc} + 6 = 0$$

$$I_{sc} - I_2 = 1.5V_1$$

$$I_{sc} - I_2 = -1.5(-6 + I_{sc})$$

$$I_{sc} + 1.5I_{sc} - I_2 = -9$$


$$2.5I_{sc} - I_2 = -9$$

$$I_{sc} = -6.5V_1 + 4i_1 + I_1$$

$$I_{sc} = -1.5(-6 - I_{sc}) + 5i_1$$

$$P_M = \frac{(0.65V)}{4(\frac{4}{9})}$$

$$= 1.533$$

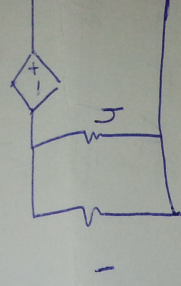

$$1 \parallel 4 = \frac{4}{5}$$


$$\frac{4}{5} \parallel 1$$

$$\frac{4}{5} \parallel \frac{4}{9} = R$$

$$\frac{4}{5} \parallel \frac{4}{9}$$

$$V = I_{sc} R_{th}$$

$$+6=0$$

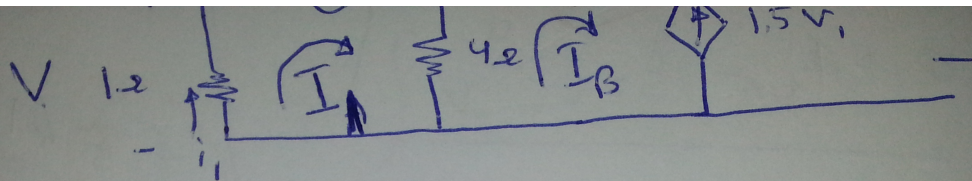

$$\frac{4}{1}$$

The max. power is when $R = R_{th}$
and is $P_{Max} = \frac{V_{th}^2}{4R_{th}}$
8.5

(30 marks) Q(3): For the circuit shown in Fig. 3.

1. (8 marks) Write the required Nodal equations.
2. (7 marks) Draw the dual circuit, show the numerical values of the different elements.
3. (15 marks) If the circuit is in steady-state where $v(t) = 5V$ and $i(t) = 2A$, then find V_c , i_L , and i_x .

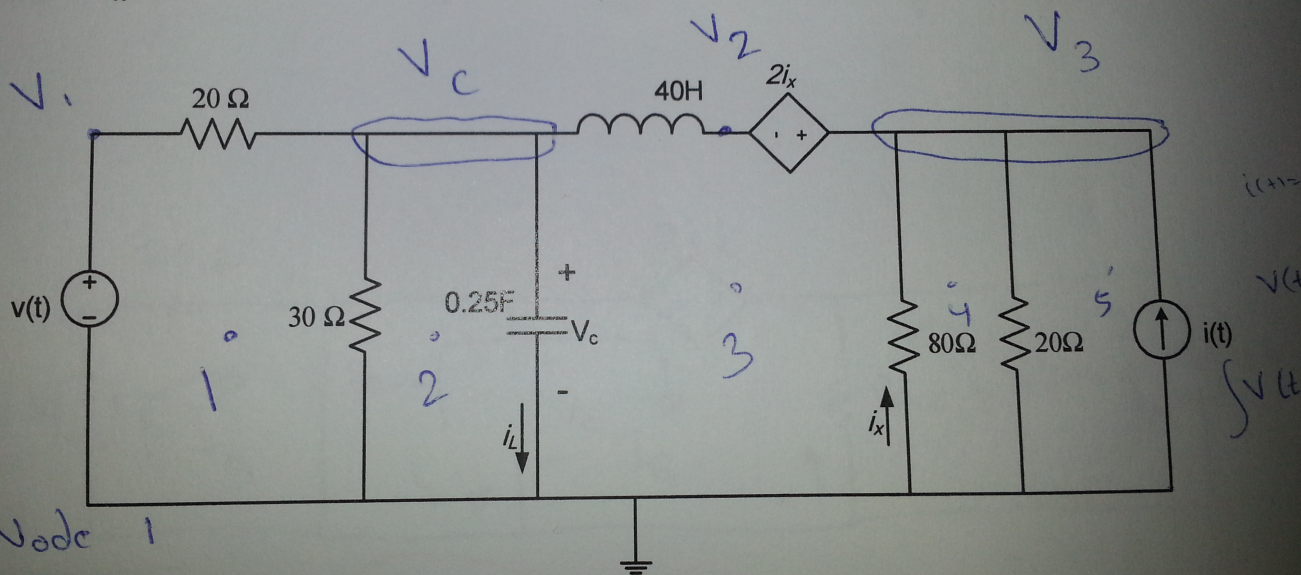


Fig. 3

@ Node 1

$$V_1 = v(t)$$

@ Node C :-

$$V_c - v(t)$$

$$V_c - 0.25 \frac{dv_c(t)}{dt}$$

$$+ \int (V_c - V_2) dt + i(t)$$

Fig. 3

@ Node 1

$$V_1 = v(t)$$

@ Node C :-

$$\frac{V_c - v(t)}{20} + \frac{V_c}{30} + 0.25 \frac{dV_c(t)}{dt} + \int \frac{V_c - v_2 dt + i_1(t_0)}{L} = 0$$

@ Supernode (C-2) :-


@ Supernode (2,3)

$$\frac{1}{L} \int (v_2 - v_c) dt + i(t_0) + \frac{v_3}{20} = i(t)$$

$$\frac{v_c - v(t)}{20} + \frac{v_c}{30} + \frac{1}{L} \int v_c - v_2 dt + i(t_0) = 0$$

$$v_3 - v_2 = 2 \text{ V}$$


4 5?

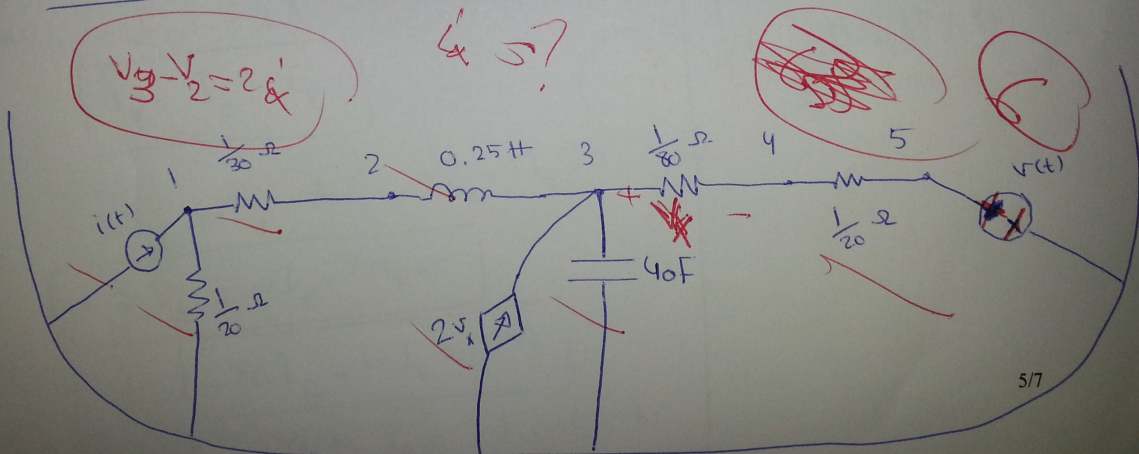

③ In steady state :-

Every capacitor is represented by an open CRT.
and every inductor is represented by short CRT.

①

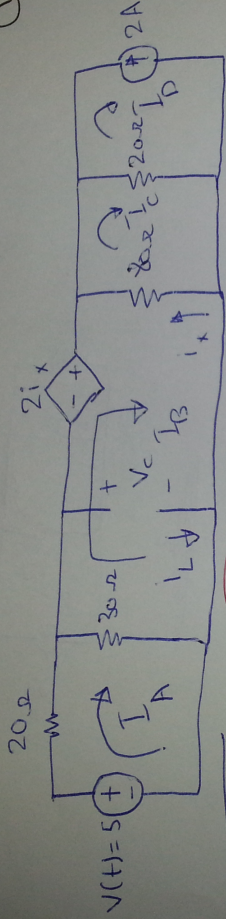

$i_L = 2A$ where it's open CRT.

@ Mesh A :-

$$-5 + 50I_A - 30I_B = 0$$

@ Mesh B :-

$$-30I_A + 110I_B - 80I_C = 2i_x$$

@ Mesh C :-

$$-80I_B + 100I_C - 20I_D = 0$$

$$I_D = -2A$$

$$i_x = I_C - I_B$$

$$-30I_A + 110I_B - 80I_C - 2I_C + 2I_B = 0$$

$$-20I_A + 112I_B - 82I_C = 0$$

$$V_C = (I_A - I_B)(30) = (-0.5296 + 1.0493)(30)$$

$$V_C = 15.291 \text{ (Volts)}$$

$$i_x = I_C - I_B$$

$$i_x = -1.239 + 1.0493$$

$$i_x = -0.1897 \text{ (A)}$$

$$\boxed{-5 + 50\bar{I}_A - 30\bar{I}_B = 0 \dots}$$

@ Mesh B :-

$$-30\bar{I}_A + 110\bar{I}_B - 80\bar{I}_C = 2i_x$$

@ Mesh C :-

$$-80\bar{I}_B + 100\bar{I}_C - 20\bar{I}_D = 0$$

@ Mesh D :- $\bar{I}_D = -2A$

$$\boxed{i_x = \bar{I}_C - \bar{I}_B}$$

$$-30\bar{I}_A + 110\bar{I}_B - 80\bar{I}_C - 2\bar{I}_C + 2\bar{I}_B = 0$$

$$\boxed{-30\bar{I}_A + 112\bar{I}_B - 82\bar{I}_C = 0 \dots}$$

$$\boxed{-80\bar{I}_B + 100\bar{I}_C = -40}$$

$$\bar{I}_A = -0.5296(A) \quad \bar{I}_B = -1.0493(A)$$

$$\bar{I}_C = -1.239(A)$$

$$V_C = (\bar{I}_A - \bar{I}_B)(30)$$

$$= (-0.5296 + 1.0493)(30)$$

$$\boxed{V_C = 15.291 \text{ (V)}} \quad \textcircled{5}$$

$$i_x = \bar{I}_C - \bar{I}_B \quad \textcircled{2}$$

$$i_x = -1.239 + 1.0493$$

$$\boxed{i_x = -0.1897(A)} \quad \textcircled{5}$$

(25 marks) Q(4): The variable dc voltage source V_s in the circuit shown in Fig.4 is adjusted so that i is zero, find the value of V_s .


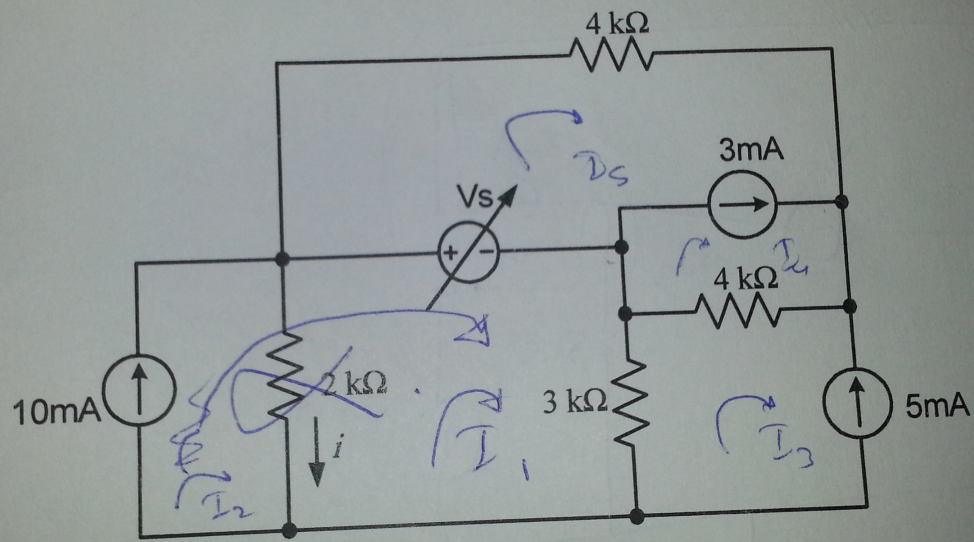


Fig. 4

when $i = 0$, then the CKT will be .

4kΩ

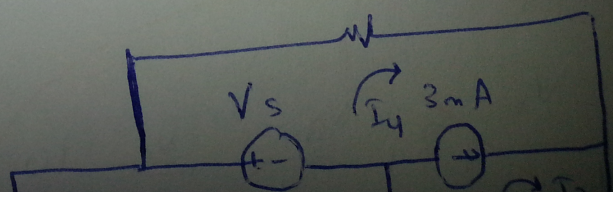Applying superposition
 Mesh 1 @ Mesh 2:-





① Super Mesh (3-4)

$$4(10)^3 I_3 - 4(10)^3 (5)(10)^{-3} - V_s + 4(10)^3$$

$$\frac{I_3}{3} - I_4 = 3 \text{ mA}$$

Applying superposition -
killing all the ~~current~~ voltage sources.

2

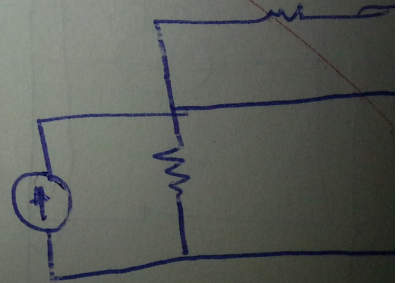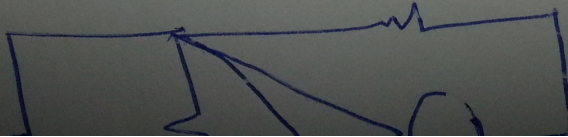

4