

$$S_{tot} = S_1 + S_2 + S_3$$

$$= (P_1 + jQ_1) + (P_2 + jQ_2) + (P_3 + jQ_3)$$

$$S_{tot} = (P_1 + P_2 + P_3) + j(Q_1 + Q_2 + Q_3)$$

$$Pf_{total} = \cos^{-1} \frac{Q_{tot}}{P_{tot}}$$

$$Q_1 = 80.2 \text{ KVAR.}$$

$$Q_2 = 150 \text{ KVAR}$$

$$Q_3 = 93 \text{ KVAR.}$$

$$\Rightarrow P_{tot} = 450 \text{ KW}$$



$$Q_{tot} = 323.2 \text{ KVAR.}$$

\* Tutorial (2) Solutions :

$$1 \text{ hp} = 746 \text{ W.}$$

Q1

Equivalent cct:

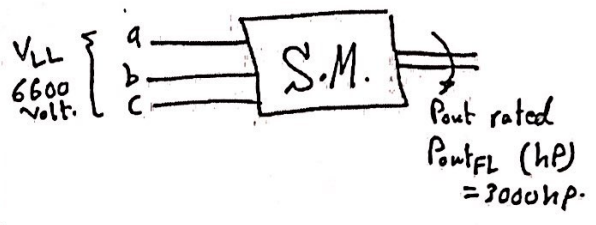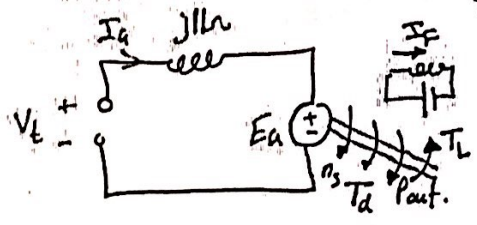

$$\Rightarrow S_{3\phi} = \frac{0.3 \text{ M}}{0.8} \Rightarrow S_{3\phi} = 3.75 \text{ MVA}$$

kVA

$$S_{3\phi} = \frac{P_{3\phi in}}{Pf}$$

$$\Rightarrow P_{3\phi in} = \frac{P_{out FL}}{Pf}$$

$$= \frac{3000 \times 746}{0.746}$$

$$P_{3\phi in} = 3 \text{ MW}$$

$$S_{3\phi} = 3 V_{\phi} I_{\phi} = \sqrt{3} V_L I_L$$


$$S_{\phi} = V_{ph} \cdot I_{ph} = 2.5 \text{ MVA}$$

in Y-con.  $(I_L) = |I_{ph}|$

$$|I_L| = \frac{S_{3\phi}}{\sqrt{3} V_L} = \frac{3.75 \text{ M}}{\sqrt{3} \times 6600} = |I_{ph}| = 328$$

$$\text{so } I_a = 328 \angle +36.87^\circ \text{ A}$$

⇒ phasor diagram:

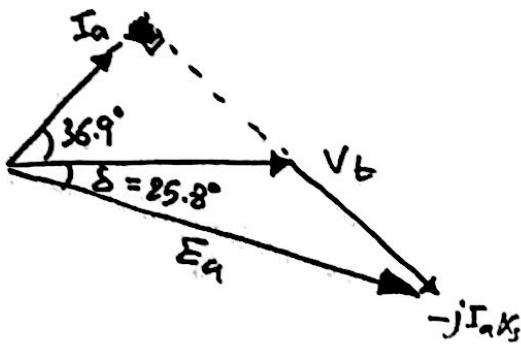

$$E_a = \frac{6600}{\sqrt{3}} \angle 0^\circ - 528 \angle 36.9^\circ \times 11 \angle 90^\circ$$

$$E_{ph} = 6636.8 \angle -25.8^\circ \text{ volt.}$$



$$|E_{aLL}| = 11493.7 \text{ volt.}$$

$$E_{aph} = 4037.3 \angle -4.1^\circ$$

$$|E_{aLL}| = 6992 \text{ V over excited supply}$$

Q2 | P=4, f=60Hz, Y-conn, |Vt|LL = 3980 volt.

Eqn. cct:

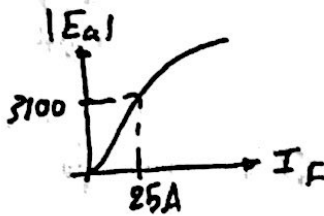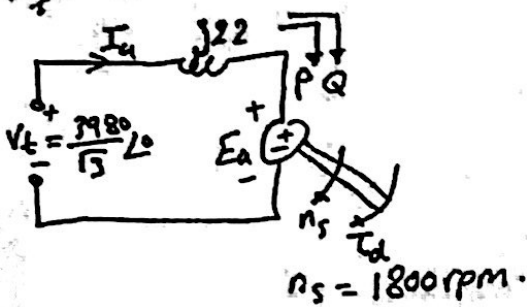

a)  $I_{ph} = I_L = \frac{V_t - E_a}{jX_s} = \frac{\frac{3980}{\sqrt{3}} \angle 0^\circ - \frac{3100}{\sqrt{3}} \angle 30^\circ}{22 \angle 90^\circ}$

⇒  $I_L = 53 \angle -40^\circ \text{ A.}$

b)  $PF = \cos(40^\circ) \Rightarrow PF = 0.766 / \text{lagging.}$

c)  $\omega_s = \frac{2\pi n_s}{60} = 188.5 \text{ rad/sec.}$

$P_d = P_{in} = \sqrt{3} I_L V_t \cos\theta = \frac{3 E_a V_t \sin\delta}{X_s}$

$R_a = 0 \quad P_d = 280.4 \text{ KW.}$


$T_d = \frac{P_d}{\omega_s} = \frac{280.4 \times 10^3}{188.5} \Rightarrow T_d = 1487 \text{ N.m.}$

\*phasor diagram:



$P_{in} = P_{out} + \sum \text{losses} = 12 \times 746 + 1200 = 10152 \text{ W.}$

Q3 |

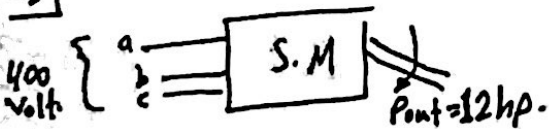


$\eta = \frac{P_{out}}{P_{in}} = \frac{12 \times 746}{10152} \Rightarrow \eta = 88\%$

$\sum P_{loss} = 1200 \text{ W.}$


\* Remember the following relation:

24

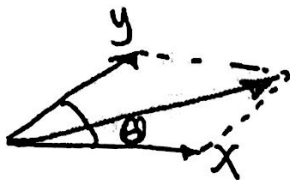


$$|x+y| = \sqrt{x^2 + y^2 + 2xy \cos \theta}$$

Q4

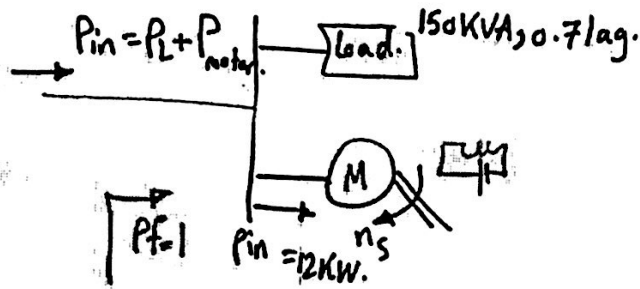

over excited:

$\Rightarrow$  Leading Pf.  
&  $|E_a| > V_t$ .

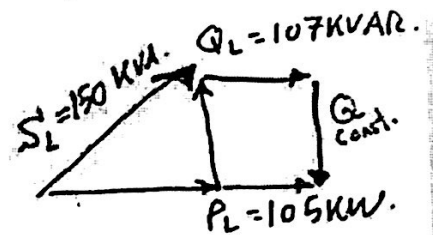

$$Q_m = Q_L = 107 \text{ KVAR.}$$


$$|S_m| = \sqrt{P_m^2 + Q_m^2} = \sqrt{12^2 + 107^2} \Rightarrow |S_m| = 107.6 \text{ KVA.}$$

$$P_{fm} = \cos \left[ \tan^{-1} \frac{Q_m}{P_m} \right] = \cos \left[ \tan^{-1} \frac{107}{12} \right] \Rightarrow \boxed{Pf = 0.111} \text{ leading.}$$

$$P_{in} = \frac{100 \times 746}{0.9} = \underline{\underline{82.9 \text{ KW.}}}$$

$$S_m = \sqrt{(82.9)^2 + (107)^2} = \underline{\underline{135.4 \text{ KVA.}}}$$

Q5

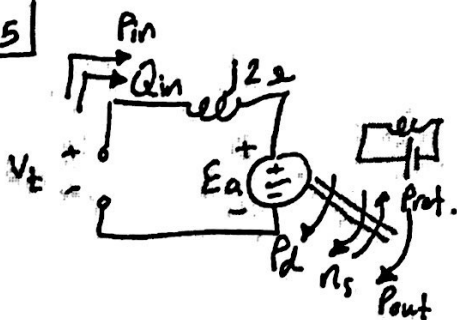

I. a)  $P_{in} = \sqrt{3} V_t I_L \cos \theta$

$$\Rightarrow 400 \text{ K} = \sqrt{3} \times 6.6 \text{ K} \times I_L \times 0.8$$

$$\Rightarrow |I_L| = |I_a| = 43.7 \text{ A}$$

$$\text{so } \boxed{I_a = 43.7 \angle -36.9^\circ \text{ A}}$$

b)  $E_a = V_t - j I_a X_s$

$$= \frac{6600}{\sqrt{3}} \angle 0 - 43.7 \angle -36.9^\circ \times 2 \angle 90^\circ$$

$$\Rightarrow \boxed{E_a = 3758.6 \angle -1^\circ \text{ volt.}}$$


$$\boxed{|E_a|_{LL} = 6510 \text{ volt.}}$$

c)  $T_{max} = \frac{P_{dmax}}{\omega_s}$

$$P_{dmax} = \frac{3 V_t E_a}{X_s} = \underline{\underline{21.4 \text{ MW.}}}$$

$$T_{dmax} = \frac{9.55 P_{dmax}}{n_s} = \frac{9.55 \times 21.4 \times 10^6}{1000}$$
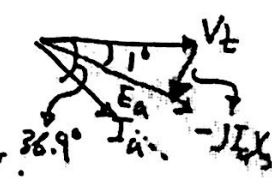
$$\boxed{T_{dmax} = 205.2 \text{ KN.m.}}$$



II.  $I_{f2} = 1.25 I_{f1} \Rightarrow E_{a2} = 1.25 E_{a1} = 1.25 * 3758.6$

$E_{a2} = 4698.25 \text{ volt.}$

a)  $P_{d1} = P_{d2}$

$\frac{\sqrt{3} V_L E_{a1} \sin \delta_1}{X_s} = \frac{\sqrt{3} V_L E_{a2} \sin \delta_2}{X_s} \Rightarrow E_{a1} \sin \delta_1 = 1.25 E_{a1} \sin \delta_2$


$\sin \delta_2 = \frac{\sin \delta_1}{1.25} = \frac{\sin(1)}{1.25} \Rightarrow \delta_2 = 0.8^\circ$

b)  $I_{a2} = \frac{V_L - E_{a2}}{jX_s} = \frac{3810.5 \angle 0 - 4698.25 \angle -0.8}{2 \angle 90} \Rightarrow I_{a2} = 445 \angle +85.8^\circ \text{ A}$

c)  $Pf = \cos \theta_2 = \cos(85.8) \Rightarrow Pf = 0.073 \text{ leading.}$

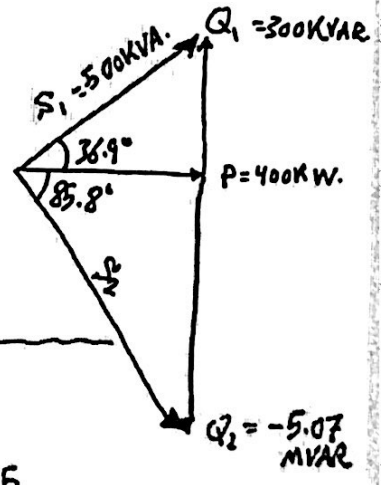d)  $P_{max2} = 1.25 P_{max1} = 1.25 * 21.4 \text{ MW} \Rightarrow P_{max2} = 26.7 \text{ MW.}$



$P_1 = 400 \text{ kW.}$   
 $Q_1 = \frac{P}{Pf} \sin \theta = \frac{400 \text{ K}}{0.8} * 0.6 = 300 \text{ KVAR.}$   
 $Q_2 = \sqrt{3} I_a V_L \sin \theta_2 = \sqrt{3} (6600) (445) \sin(-85.8)$   
 $= -5.07 \text{ MVAR.}$



Q6 3.3KV, 50Hz, P=2, Y-con.,  $X_s = 15 \Omega$   
 $|E_a| = |V_L| = 3.3 \text{ K volt.}$

a)  $P_{max} |_{\delta=90} = \frac{3.3 \text{ K} * 3.3 \text{ K}}{15} = 726 \text{ KW.}$

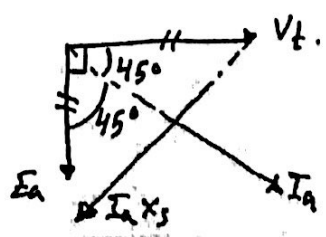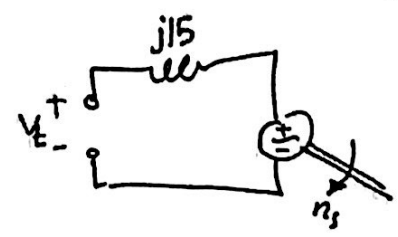$T_{max} = \frac{P_{max}}{\omega_s} = \frac{726 \text{ K}}{314} = 2310.9 \text{ N.m.}$



b)  $I_a = \frac{V_t - E_a}{jX_s} = \frac{\frac{3300}{\sqrt{3}} \angle 0^\circ - \frac{3300}{\sqrt{3}} \angle -90^\circ}{15 \angle 90^\circ} \Rightarrow I_a = 179.6 \angle -45^\circ \text{ A.}$

$Pf = \cos \theta \Rightarrow Pf = \cos 45 \Rightarrow Pf = 0.707$  lagging.

$Q = \sqrt{3} V_L I_L \sin \theta$  (absorbed).  $= \sqrt{3} * 3.3K * 179.6 * 0.707$   
 $\Rightarrow Q = 726 \text{ KVAR.}$


c)  $E_{a2} = 1.2 E_{a1} = 1.2 * \frac{3300}{\sqrt{3}} \Rightarrow E_{a2} = 2286 \text{ volt.}$

$\delta_2 = \sin^{-1} \left( \frac{\sin \delta_1}{1.2} \right) = \sin^{-1} \left( \frac{\sin 90}{1.2} \right) \Rightarrow \delta_2 = 56.4^\circ$

$I_{a2} = \frac{\frac{3300}{\sqrt{3}} \angle 0^\circ - 2286 \angle -56.4^\circ}{15 \angle 90^\circ} \Rightarrow I_a = 134 \angle -18.6^\circ \text{ A.}$

$Pf = 0.948$   
lagging

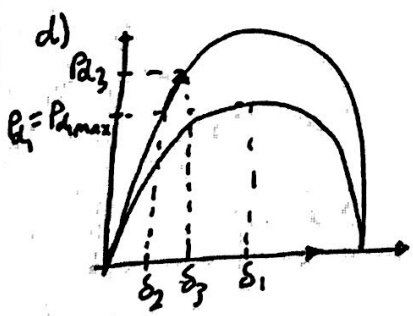$Q_2 = \sqrt{3} * 3300 * 134 \sin(18.6) \Rightarrow Q_2 = 244.3 \text{ KVAR.}$



$P_{d3} = 1.1 P_{d_{max}} = 1.1 * 726K = 798.6 \text{ KW.}$


$P_{d3} = 3 \frac{V_t E_{a3}}{X_s} \sin \delta_3$

$798.6 * 10^3 = 3 * \frac{3300}{\sqrt{3}} * 2286 \sin \delta_3$

$\Rightarrow \delta_3 = 66.5^\circ$

$I_a = 154.7 \angle -25.4^\circ \text{ A}$ ,  $Pf = 0.908$  lagging,  $Q_3 = 379.3 \text{ KVAR.}$

Q7 |  $V_t = 208 \text{ volt, } 45 \text{ KVA.}$   
 0.8 pf lead.  
 Δ-connected.  
 $f = 60 \text{ HZ}$  &  $X_s = 2.5 \Omega$   
 $P_{FRW} = 1.5 \text{ KW}$ ,  $P_{core} = 1 \text{ KW.}$   
 $P_{out} = 15 \text{ hp.}$

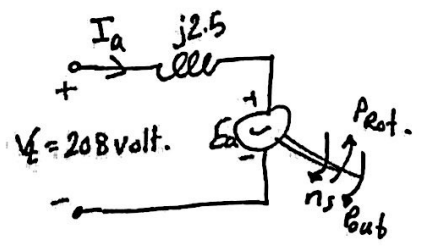




$$\Rightarrow P_{in} = P_d = P_{rot} + P_{out} = (1.5 + 1 + 11.2) \text{ kW} = \underline{13.7 \text{ kW}}$$

27
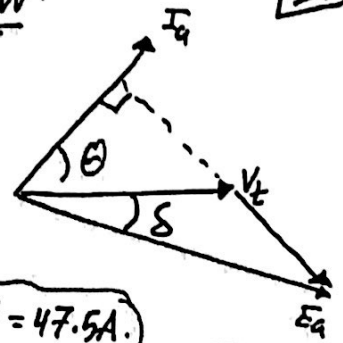
$$I_d = \frac{P_{in}}{3 V_{ph} \cos \theta} = \frac{13.7 \times 10^3}{3 \times 208 \times 0.8} = 27.4 \text{ A}$$



$$\Rightarrow I_a = 27.4 \angle 36.9^\circ \text{ A} \Rightarrow |I_L| = \sqrt{3} |I_{ph}| \Rightarrow |I_L| = 47.5 \text{ A}$$

$$E_a = 255 \angle -12.4^\circ \text{ volt}$$

$$P_{in2} = P_{out2} + P_{rot} = 22.4 + 2.5 = \underline{24.9 \text{ kW}}$$

$$P_{in2} = \frac{3 V_t E_{a2} \sin \delta_2}{X_s} \Rightarrow I_{a2} = \frac{V_t - E_{a2} \angle \delta}{j X_s}$$

$$\Rightarrow \delta_2 = 23^\circ$$

Pf = 0.966 leading

$$I_{a2} = 41.3 \angle 15^\circ \text{ A}$$

$$|I_L| = 71.5 \text{ A}$$


Q8

$$a) n_s = \frac{120}{p} * f = \frac{120}{2} * 60 \Rightarrow n_s = 900 \text{ rpm}$$

$$b) P_{in} = P_{out} = 400 * 746 \Rightarrow P_{in} = 298.4 \text{ kW}$$

$$P_{in} = 3 V_t I_a \text{ pf} \Rightarrow I_a = \frac{298.4 \text{ kW}}{3 * 480 * 0.8} \Rightarrow I_a = 259 \angle -36.9^\circ \text{ A}$$
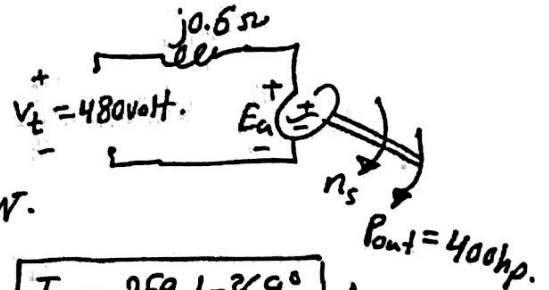
$$E_a = V_t - I_a (j X_s) = 480 \angle 0^\circ - (259 \angle -36.9^\circ) * 0.6j \Rightarrow E_a = 406.2 \angle -17.8^\circ \text{ volt}$$



$$c) \delta = 17.8^\circ \quad \tau = \frac{P_{in}}{\omega_s} = \frac{298.4 \text{ kW}}{2\pi * \frac{900}{60}} \Rightarrow \tau \approx 3166 \text{ N.m}$$

$$P_{in \text{ max}} = \frac{3 V_t E_g}{X_s} = \frac{3 * 480 * 406.2}{0.6} = 974.88 \text{ kW}$$

$$\tau_{\text{max}} = \frac{P_{\text{max}}}{\omega_s} \Rightarrow \tau_{\text{max}} \approx 10344 \text{ N.m}$$

$\tau$  is 30.6% of  $\tau_{\text{max}}$ .

$$d) E_{a2} = 1.3 E_{a1} \Rightarrow |E_{a2}| = 528 \text{ volt}$$

$$\sin \delta_2 = \frac{\sin \delta_1}{1.3} = \frac{\sin 17.8}{1.3} \Rightarrow \delta_2 = 13.6^\circ$$

$$I_a = \frac{V_t - E_a \angle -\delta}{j X_s} \Rightarrow I_a = 214.2 \angle 15^\circ \text{ A}$$

Pf = 0.966 leading

