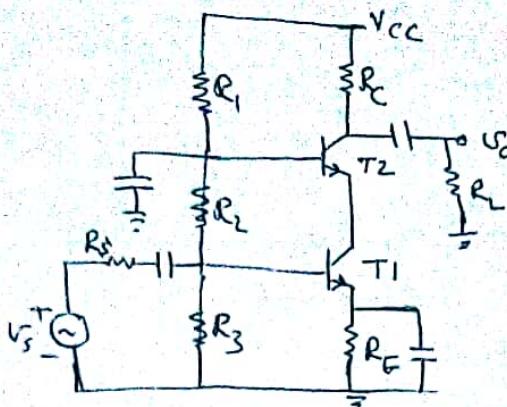


Q1) a) Draw the electronic circuit diagram of the cascode amplifier.



Write down its ac voltage gain.

$$A_V = -g_m R_C \parallel R_L$$


b) Draw the small signal low frequency circuit model of a common drain n-channel MOSFET, and use it to calculate the voltage gain when $R_1 \parallel R_2 = \infty \Omega$, R_S , R_{SD} , and R_D are finite.

$$V_o = g_m v_{gs} (R_s \parallel r_o)$$

$$V_S = v_{gs} + g_m (R_s \parallel r_o) v_{gs}$$

$$\therefore V_{BS} = \frac{1}{1 + g_m (R_s \parallel r_o)} V_S$$
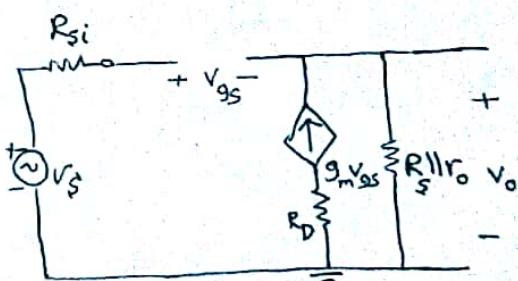
$$\therefore A_V = \frac{V_o}{V_S} = \frac{g_m (R_s \parallel r_o)}{1 + g_m (R_s \parallel r_o)}$$



(4)

Q2 Given the two-stage amplifier shown opposite with the following information: $I_{BQ1} = 3.2 \mu A$,

$I_{BQ2} = 20 \mu A$. Furthermore, for both transistors, $\beta_{dc} = \beta_{ac} = \beta = 99$, $V_T = 25 \text{ mV}$ and $V_A = \infty V$.

Calculate the overall voltage gain.

$$r_{pi} = \frac{V_T}{I_{BQ1}} = \frac{25}{3.2} k\Omega = 7.8125 k\Omega$$

$$r_{pi2} = \frac{25}{20} k\Omega = 1.25 k\Omega$$

$$r_o = \frac{V_A}{I_{Co}} = \frac{\infty}{I_{Co}} = \infty \Omega$$

Stage 1 is CE

$$R_{cbo1} = r_{pi} + (1+\beta)R_E = 1 \\ = 7.8125 + 100 \times 2 \\ = 207.8125 k\Omega$$


$$R_{i1} = R_1 || R_2 || R_{cbo1} = 67.3 || 12.7 || 207.8125 \\ = 0.884 || 207.8125 = 10.16 k\Omega$$

$$A'_{v1} = -\frac{\beta R_C}{R_{cbo1}} = -\frac{990}{207.8125} = -4.764$$

$$R_{o1} = R_{C1} = 10 k\Omega$$

$$V_o = \frac{R_L}{R_L + R_{o2}} A'_{v2} \frac{R_{i2}}{R_{i2} + R_{o1}} A'_{v1} \frac{R_{i1}}{R_{i1} + R_s} V_S$$

$$= \frac{V_o}{V_S} = \frac{0.25}{0.2504112} \times 0.99255 \frac{10.5}{10.5 + 10} \times -4.764 \frac{10.16}{10.16 + 0} \\ = \frac{0.25}{0.362} \times 0.99255 \frac{10.5}{20.5} \times -4.764 \times 1 \\ = -1.6729$$

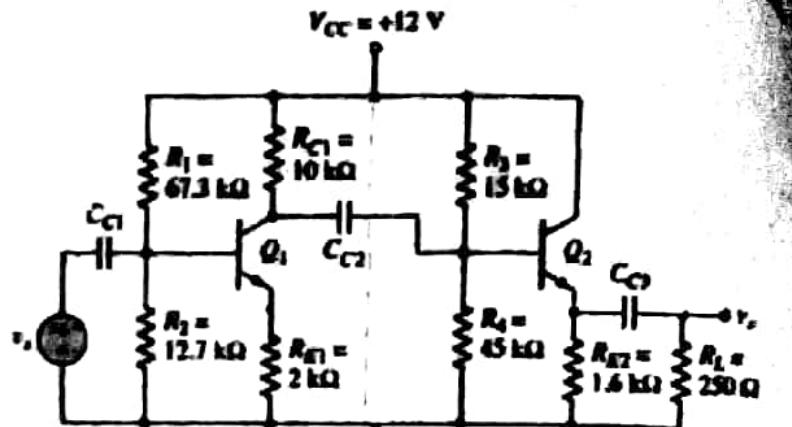

Stage 1

Stage 2

$$r_{o1} || R_E = R_G \\ \infty || R_E = R_G$$

(1)

Stage 2 is CC

$$R_{cbo2} = r_{pi2} + (1+\beta)(r_{o1} || R_E) \\ = 1.25 + 160 = 161.25 k\Omega$$

$$R_{i2} = R_1 || R_2 || R_{cbo2} \\ = 15 || 45 || 161.25 \\ = 11.25 k\Omega \quad 161.25 \\ = 10.5164 k\Omega \quad (4)$$

$$A'_{v2} = \frac{(1+\beta)(r_{o1} || R_E)}{R_{cbo2}} \\ = \frac{160}{161.25} = 0.99225$$


$$R_{o2} = \frac{r_{pi2} + R_{o1}}{1+\beta} \\ = \frac{11.25}{100} k\Omega = 112.5 \quad (5)$$

(3)

Q3) a) Given the circuit shown.

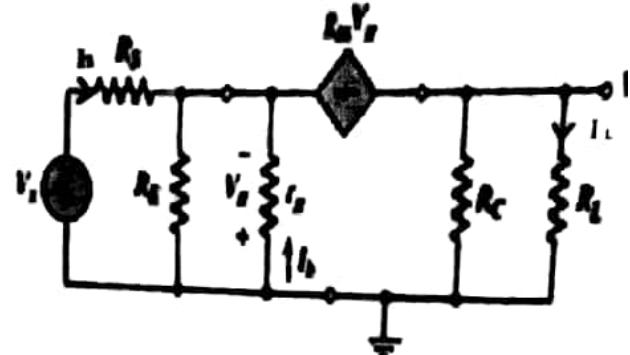- i) Classify the circuit using the following words and abbreviations which fit the circuit.

pMOSFET, nMOSFET, pnp, npn, CE, CC, CB, CS, CD, CG, loaded, unloaded.



This circuit represent

a loaded, low frequency, npn, common base (CB) amplifier

- ii) Derive the relationship which gives the current gain defined as $A_i = \frac{I_L}{I_s}$.

(2)

$$I_L = -\frac{R_C}{R_C + R_L} g_m V_{RE}$$

$$-I_s = \frac{V_T}{R_E \parallel r_n} + g_m V_{RE} = \left(\frac{1}{R_E \parallel r_n} + g_m \right) V_T$$

$$\begin{aligned} \therefore A_i &= \frac{I_L}{I_s} = \frac{-I_L}{-I_s} = \frac{\frac{R_C}{R_C + R_L} g_m}{g_m + \frac{1}{R_E \parallel r_n}} \\ &= \frac{R_C}{R_C + R_L} \frac{g_m (R_E \parallel r_n)}{1 + g_m (R_E \parallel r_n)} < 1 \end{aligned}$$

(3)

- b) In an npn transistor amplifier circuit involving coupling and bypass capacitors, and operated at high frequency.

- i) What capacitances account for the high frequency response?

The internal capacitances of the transistor: C_{ce} and C_{cb}


- ii) What capacitors account for the low frequency response?

(2)



Q4

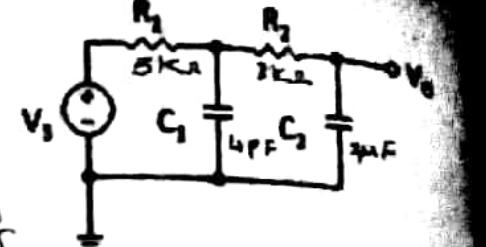- a) consider the circuit shown, where $R_1 = 5K\Omega$, $R_2 = 3K\Omega$, $C_1 = 4pF$, $C_2 = 2\mu F$. If the method of approximate time constants applies, use it to calculate f_L and f_H . Hence, or otherwise, calculate the midband gain.



since the resistances R_1 and R_2 are of the same order and C_1 and C_2 are order of magnitude different, then the time constants are well far apart. Hence, the method applies.

$$\tau_L = (R_1 + R_2)C_2 = 8 \times 10^3 \times 2 \times 10^{-6} = 16 \text{ ms}$$

$$\Rightarrow f_L = \frac{1}{2\pi\tau_L} = \frac{10^3}{2\pi \times 16} = 9.947 \text{ Hz}$$

$$\tau_F = (R_1 || R_2)C_1 = (3k || 5k)C_1 = 1.875 \times 10^3 \times 4 \times 10^{-12} = 7.5 \times 10^{-9} \text{ s} \\ = 7.5 \text{ ns}$$

$$\Rightarrow f_H = \frac{1}{2\pi\tau_F} = \frac{10^9}{2\pi \times 7.5} = \frac{1000}{15\pi} \text{ MHz} = 21.221 \text{ MHz}$$

Mid-band gain is obtained when $Z_{C_1} = \infty$ & $Z_{C_2} = 0\Omega$

Hence equals to zero volt



- b) A particular transistor short circuit current gain is given by $A_i = \frac{0.05 - j 10^{-12}f}{0.0005 + j 10^{-11}f}$

Represent A_i in the form $A_i = \frac{K(1-j\frac{f}{f_z})}{(1+j\frac{f}{f_p})}$. What are the values of K , f_z , and f_p .

$$A_i = \frac{0.05 \left(1 - j \frac{10^{-12}f}{0.05}\right)}{0.0005 \left(1 + j \frac{10^{-11}f}{0.0005}\right)} = 100 \frac{1 - j \frac{f}{50 \times 10^9}}{1 + j \frac{f}{50 \times 10^6}}$$


$$\Rightarrow K = 100$$

$$f_z = 50 \times 10^9 = 50 \text{ GHz}$$

$$f_p = 50 \times 10^6 = 50 \text{ MHz}$$

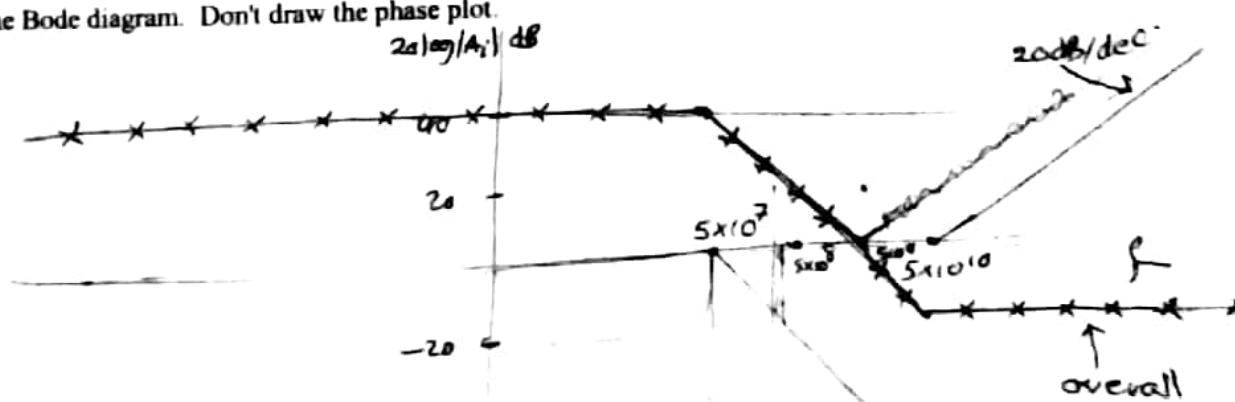(4)

Draw the Bode diagram. Don't draw the phase plot.



POWER UNIT

