

Chapter 6

* i_B, v_{BE} : total instantaneous values

* I_B, V_{BE} : DC values

* i_b, v_{be} : instantaneous AC values

* I_b, v_{be} : phasor values

$$* r_{\pi} = \frac{V_T}{I_{BQ}} = \frac{\beta V_T}{I_{CQ}}$$

$$* g_m = \frac{I_{CQ}}{V_T}$$

$$* \beta = g_m r_{\pi}$$

$$* r_o = \frac{V_A}{I_{CQ}}$$

① common-emitter Amplifier

* without R_E :

$$A_v = -g_m (r_o \parallel R_c) \cdot \left(\frac{R_1 \parallel R_2 \parallel r_{\pi}}{R_1 \parallel R_2 \parallel r_{\pi} + R_s} \right)$$

* with R_E :


$$A_v = \frac{-\beta R_c}{r_{\pi} + (1+\beta)R_E} \cdot \left(\frac{R_i}{R_i + R_s} \right)$$

$$* R_{ib} = r_{\pi} + (1+\beta)R_E$$


$$* R_i = R_1 \parallel R_2 \parallel R_{ib}$$

* active load :

$$A_v = -g_m (r_o \parallel R_c)$$

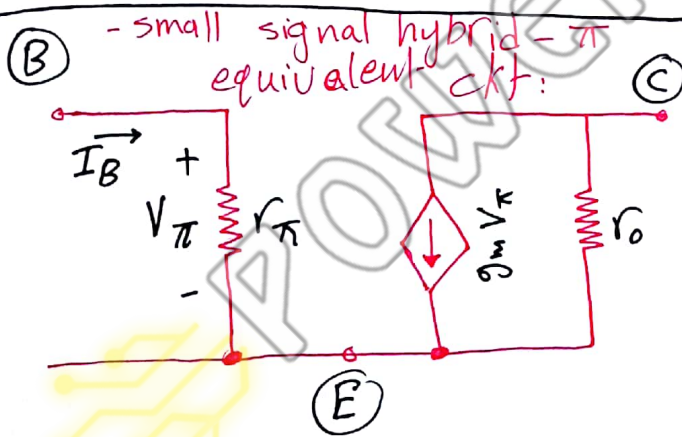

* AC & DC load line:

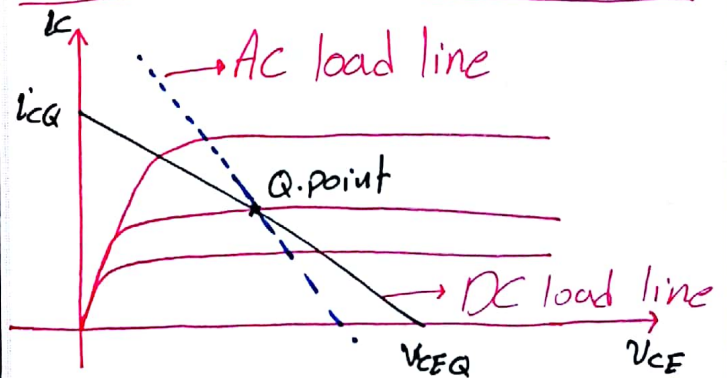

$$* DC: \text{slope} = \frac{-1}{R_c + R_{E1} + R_{E2}}$$

$$* AC: \text{slope} = \frac{-1}{R_c + R_{E1}}$$

Chapter 6

② common-collector:

$$A_v = \frac{(1+\beta)(r_o \parallel R_E)}{r_\pi + (1+\beta)(r_o \parallel R_E)} \cdot \left(\frac{R_i}{R_i + R_s} \right)$$

$$* R_{ib} = r_\pi + (1+\beta)(r_o \parallel R_E)$$

$$* R_o = \frac{r_\pi}{1+\beta} \parallel R_E \parallel r_o \quad * \text{without } R_s$$

$$* R_o = \left(\frac{r_\pi + R_1 \parallel R_2 \parallel R_s}{1+\beta} \right) \parallel R_E \parallel r_o \quad \text{with } R_s$$

$$* A_i = (1+\beta) \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{ib}} \right) \left(\frac{r_o}{r_o + R_E} \right)$$

$$- A_i \approx (1+\beta)$$

③ common-Base Amplifier

$$A_v = g_m (R_c \parallel R_L)$$

$$A_i = \frac{g_m r_\pi}{1+\beta} = \frac{\beta}{1+\beta} = \alpha$$


$$R_{ie} = \frac{r_\pi}{1+\beta} = r_e$$

$$* R_{eq} = R_s \parallel R_E \parallel r_\pi$$

$$R_{oc} = r_o (1 + g_m R_{eq}) + R_{eq}$$

by omar abu serrieh


* Darlington pair Configuration

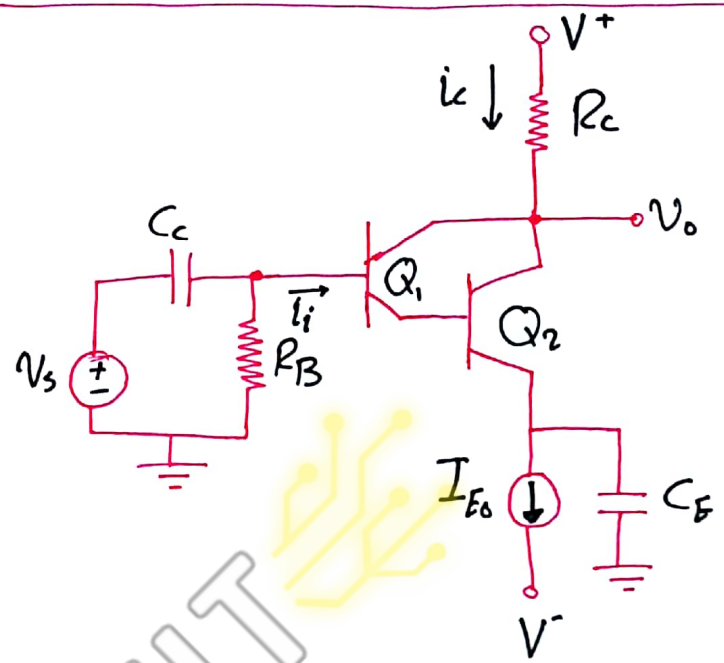

$$A_i = \beta_1 + \beta_2 (1 + \beta_1) \approx \beta_1 \beta_2$$

$$R_i \approx 2\beta_1 r_{\pi 2}$$

* Cascode Configuration:

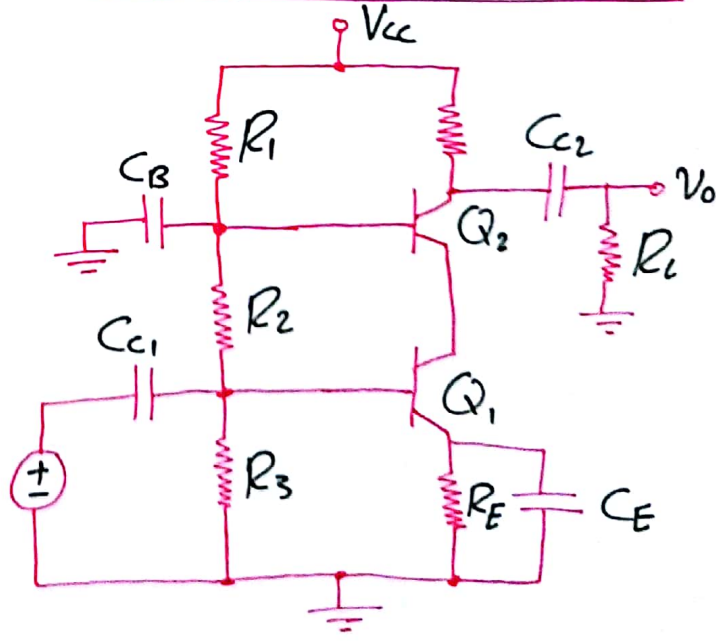

$$A_v \approx -g_{m1} (R_c \parallel R_L)$$

Chapter 4

$$* I_D = K_n (V_{GS} - V_{TN})^2$$

* D: Drain

$$* g_m = 2K_n (V_{GS} - V_{TN})$$

* S: Source

$$= 2\sqrt{K_n I_{DQ}}$$

* G: gate

$$* r_o = \frac{1}{\lambda I_{DQ}}$$

* $I_G = 0$

① Common-source Amplifier

$$A_v = -g_m (r_o \parallel R_D) \cdot \left(\frac{R_i}{R_i + R_{Si}} \right)$$

$$\# R_i = R_1 \parallel R_2 \quad \# \text{ without } R_s \rightarrow$$

$$A_v = \frac{-g_m R_D}{1 + g_m R_s} \cdot \frac{R_i}{R_i + R_{Si}} \quad \# \text{ with } R_s$$

$$A_v \approx \frac{-g_m R_D}{1 + g_m R_s} \approx \frac{-R_D}{R_s}$$

② Common-Drain Amplifier:

$$A_v = \frac{g_m (R_s \parallel r_o)}{1 + g_m (R_s \parallel r_o)} \cdot \left(\frac{R_i}{R_i + R_{Si}} \right)$$

$$* R_o = \frac{1}{g_m} \parallel R_s \parallel r_o$$

③ Common-gate


$$A_v = \frac{g_m (R_D \parallel R_L)}{1 + g_m R_{Si}}$$

$$A_i = \left(\frac{R_D}{R_D + R_L} \right) \cdot \left(\frac{g_m R_{Si}}{1 + g_m R_{Si}} \right)$$


$$* R_i = \frac{1}{g_m}$$

$$* R_o = R_D$$


① common-source:

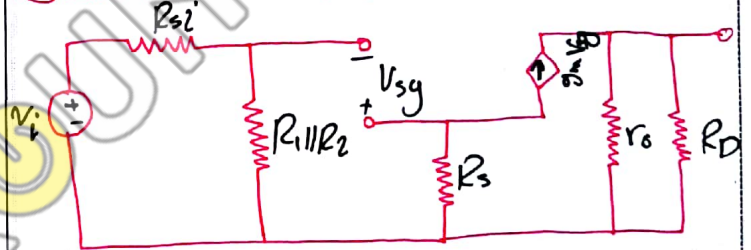


② common-Drain:

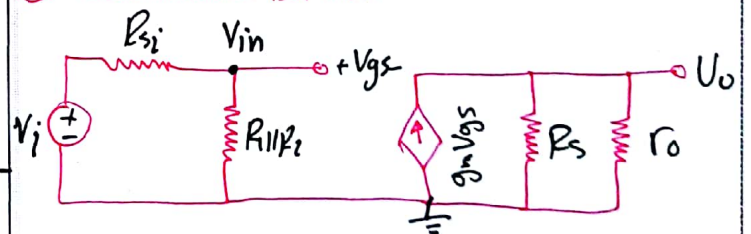

③ common-gate:

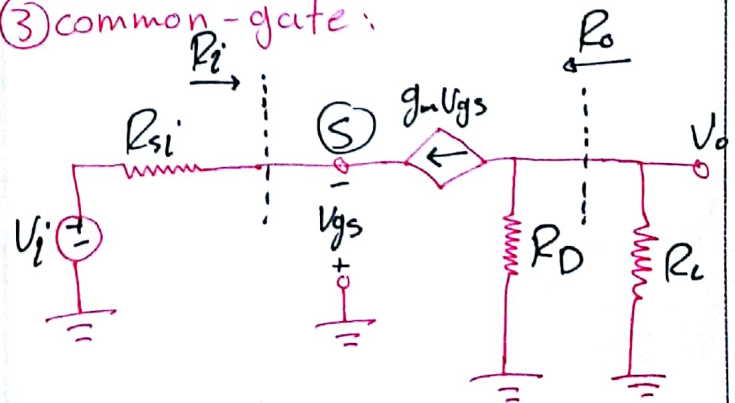

Chapter 7

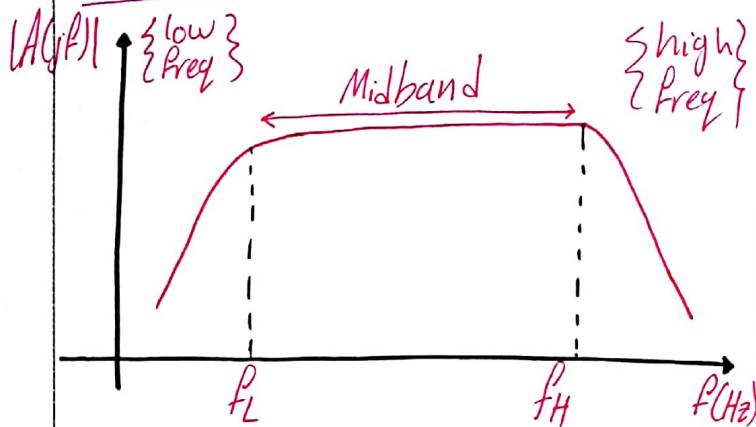


* in low frequency: external capacitances (bypass & coupling)

* in high frequency: internal capacitors (C_{μ} & C_{π})

* in midband range:
external \rightarrow short circuit
internal \rightarrow open circuit
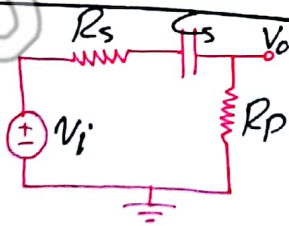
$$\frac{V_o(s)}{V_i(s)} = k \left(\frac{sT_s}{1+sT_s} \right)$$




where:

$$k = \frac{R_p}{R_s + R_p}$$

$$T_s = (R_s + R_p) C_s$$

\hookrightarrow time constant.

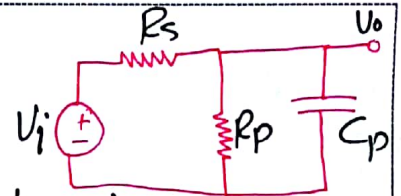

$$\frac{V_o(s)}{V_i(s)} = k \left(\frac{1}{1+sT_p} \right)$$

where: $* f_L = \frac{1}{2\pi T_s}$


$$k = \frac{R_p}{R_p + R_s} \quad * f_H = \frac{1}{2\pi T_p}$$

$$T_p = (R_s \parallel R_p) C_p$$

\hookrightarrow time constant

* Bipolar transistor:

short ckt current gain:

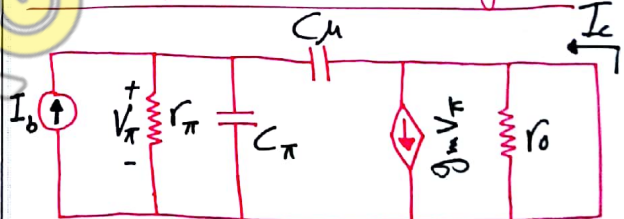

$$A_i = h_{fe} = \frac{(g_m - j\omega C_{\mu})}{\left[\frac{1}{r_{\pi}} + j\omega(C_{\pi} + C_{\mu}) \right]}$$



$$h_{fe} \approx \frac{g_m r_{\pi}}{1 + j\omega r_{\pi}(C_{\pi} + C_{\mu})}$$

$$f_{\beta} = \frac{1}{2\pi r_{\pi}(C_{\mu} + C_{\pi})} \quad * \text{beta cutoff freq.}$$


$$h_{fe} = \frac{\beta_0}{1 + j\left(\frac{f}{f_{\beta}}\right)}$$

$$f_T = \beta_0 f_{\beta} = \frac{g_m}{2\pi(C_{\pi} + C_{\mu})} \quad * \text{unity-gain bandwidth.}$$

Chapter 9

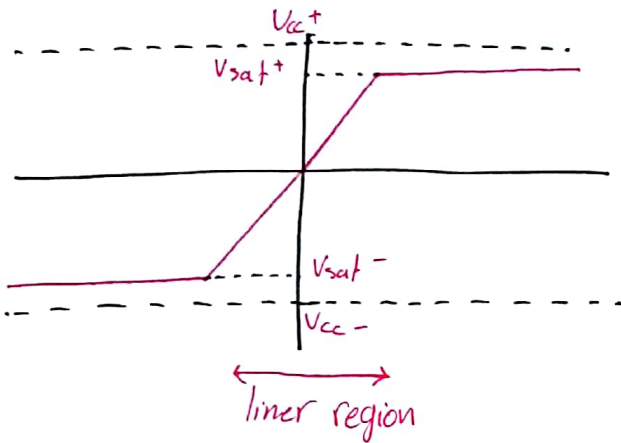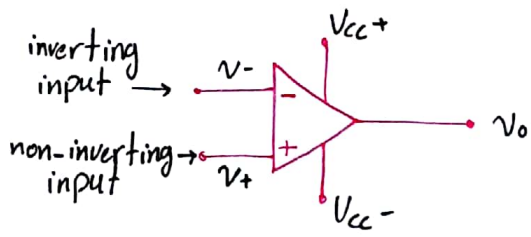


① The Inverting Amplifier

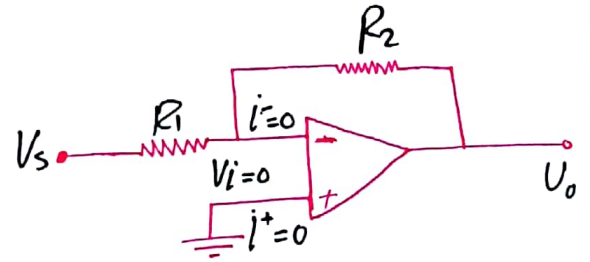


$$\begin{aligned} v^+ - v^- &= 0 \\ I^- = I^+ &= 0 \end{aligned} \quad \text{always}$$

$$\frac{V_o}{V_s} = -\frac{R_2}{R_1}$$


② the T-Network Amplifier

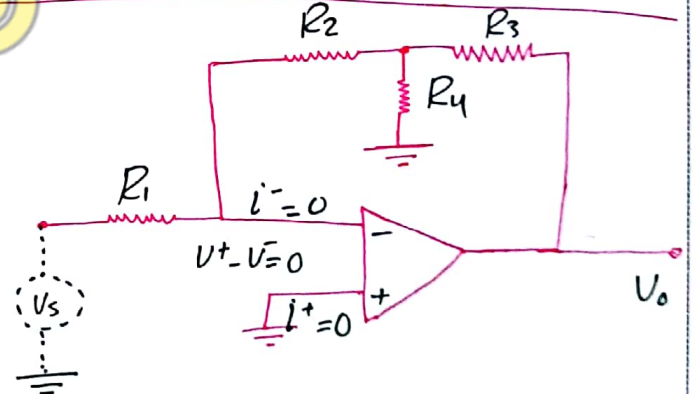
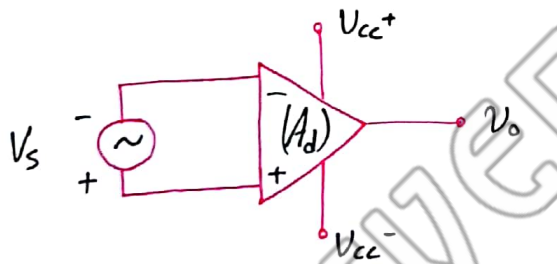
$$\frac{V_o}{V_s} = -\frac{R_2}{R_1} \cdot \left[1 + \frac{R_3}{R_2} + \frac{R_3}{R_4} \right]$$




$$V_o = A_d (v^+ - v^-) = A_d V_s$$

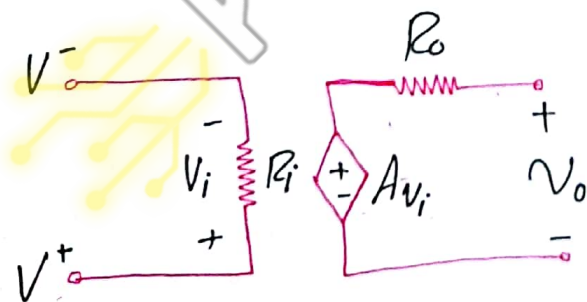

(practical op-amp model)


chapter 9

③ The non-inverting Amplifier

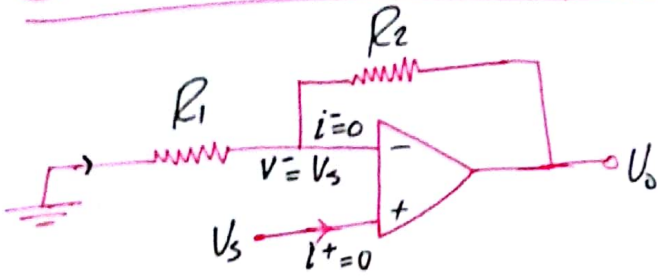


$$\frac{V_o}{V_s} = \left(1 + \frac{R_2}{R_1}\right) = \frac{R_1 + R_2}{R_1}$$

④ The summing Amplifier

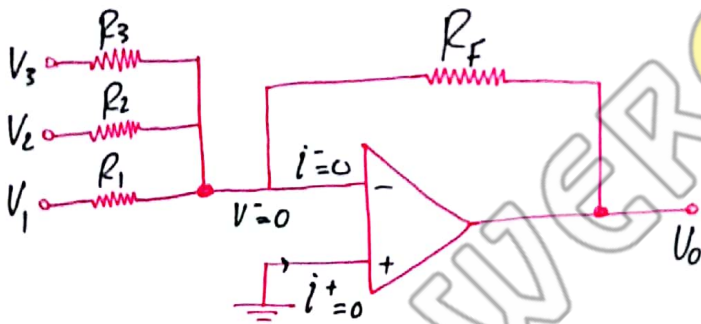

$$\frac{V_o}{V_i} = - \left[\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 + \frac{R_F}{R_3} V_3 \right]$$


⑤ the Difference Amplifier

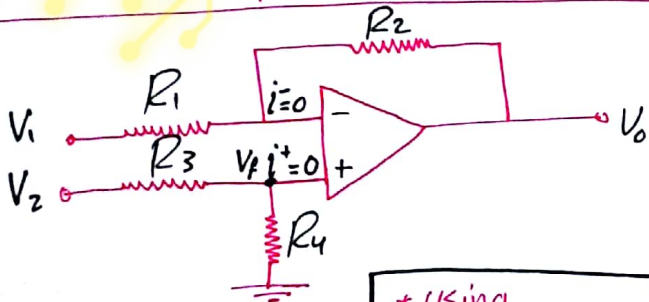

$$V_o = \frac{R_2}{R_1} (V_2 - V_1)$$


* using superposition

⑥ The Differentiator circuit

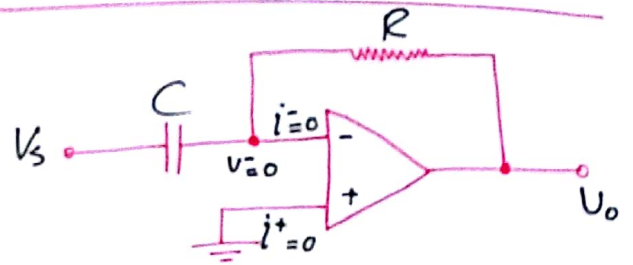


$$U_o = -Rc \frac{d}{dt} V_s$$

⑦ the integrator circuit

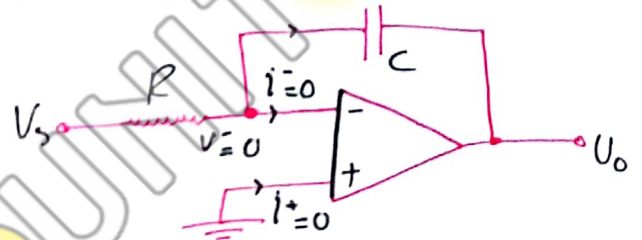

$$V_o = \frac{-1}{Rc} \int V_s dt$$


⑧ Reference voltage source

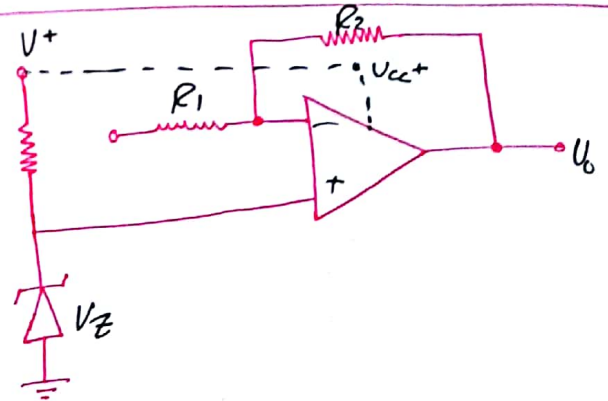

- Assuming the Zener is in Breakdown

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_Z$$


Chapter 12

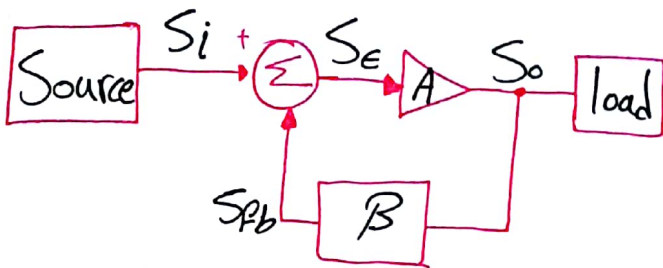

closed-loop transfer function:

$$A_f = \frac{S_o}{S_i} = \frac{A}{(1+BA)}$$

① series - shunt:

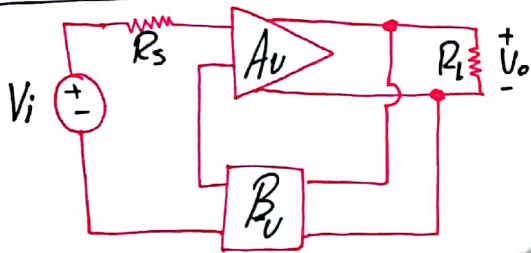


$$* A_{vzf} = \frac{A_v}{(1+B_v A_v)}$$

Voltage Amplifier

$$* R_{if} = R_i (1+B_v A_v)$$

$$* R_{of} = \frac{R_o}{(1+B_v A_v)}$$

② shunt - series:

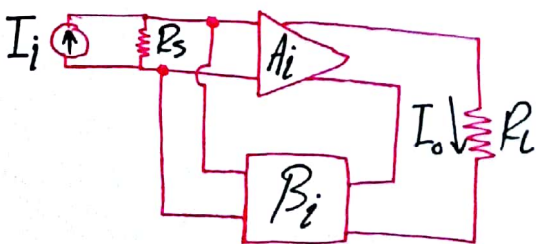


$$* A_{if} = \frac{A_i}{(1+B_i A_i)}$$

$$* R_{if} = \frac{R_i}{(1+B_i A_i)}$$

$$* R_{of} = R_o (1+B_i A_i)$$

current Amplifier

③ series - series:

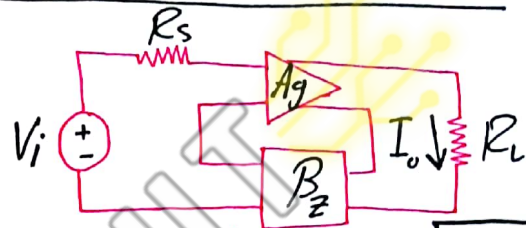


$$* A_{gf} = \frac{A_g}{(1+B_z A_g)}$$

$$* R_{if} = R_i (1+B_z A_g)$$

$$* R_{of} = R_o (1+B_z A_g)$$

transconductance Amplifier

④ shunt - shunt:

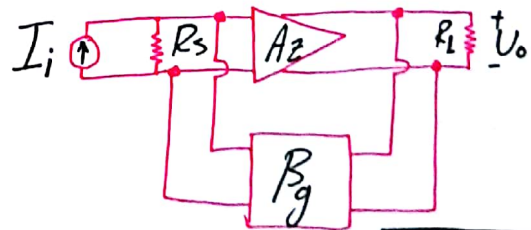

$$* A_{zf} = \frac{A_z}{(1+B_g A_z)}$$

$$* R_{if} = \frac{R_i}{(1+B_g A_z)}$$

$$* R_{of} = \frac{R_o}{(1+B_g A_z)}$$

transresistance Amplifier