

# **AMPLIFIERS NOTEBOOK**

**( ELECTRONICS II )**



**DR. RA'ED AL-ZOBIE  
SPRING - 2014**

**BY. HASAN ABU AL-RUZ**




\* Transistor:

→ BJT

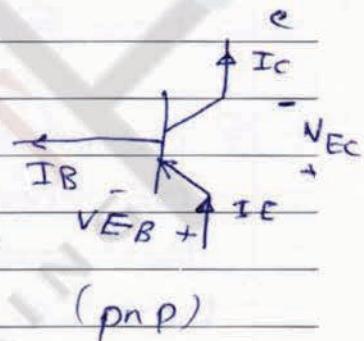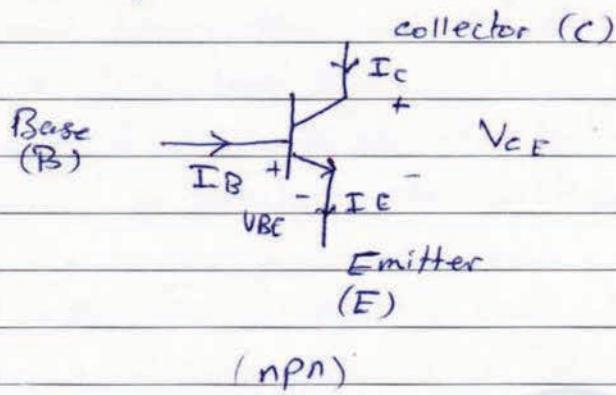
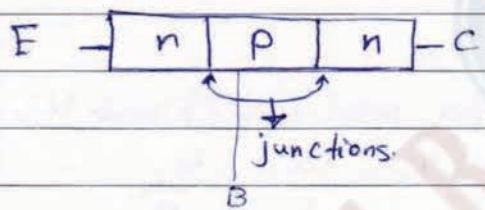
$$I_E = I_C + I_B ; I_C = \beta I_B ; I_E = (1 + \beta) I_B ; I_E = \frac{1}{\alpha} I_C$$



\* Modes of operations:- for BJT

① forward active mode (or active region) [Default Mode]

BE: Forward-biased

BC: Reverse-biased

BJT is used as amplifier

$$V_{BE} = V_{BE(on)} = 0.7V ; V_{CE} > V_{CE(sat.)} = 0.2 \text{ or } 0.3V$$

② Saturation mode

BE: Forward

BC: Forward

BJT is used as a switch.

$$V_{BE} = 0.7V$$

$$V_{CE} = V_{CE(sat.)}$$

$$I_C < \beta I_B$$

## (3) inverse - active mode:

BE : reverse - biased.


Bc : Forward - biased.

## (4) cut off Mode:

BE : reverse - biased

Bc : reverse - biased.

$$I_C = I_B = I_E = \text{Zero.}$$

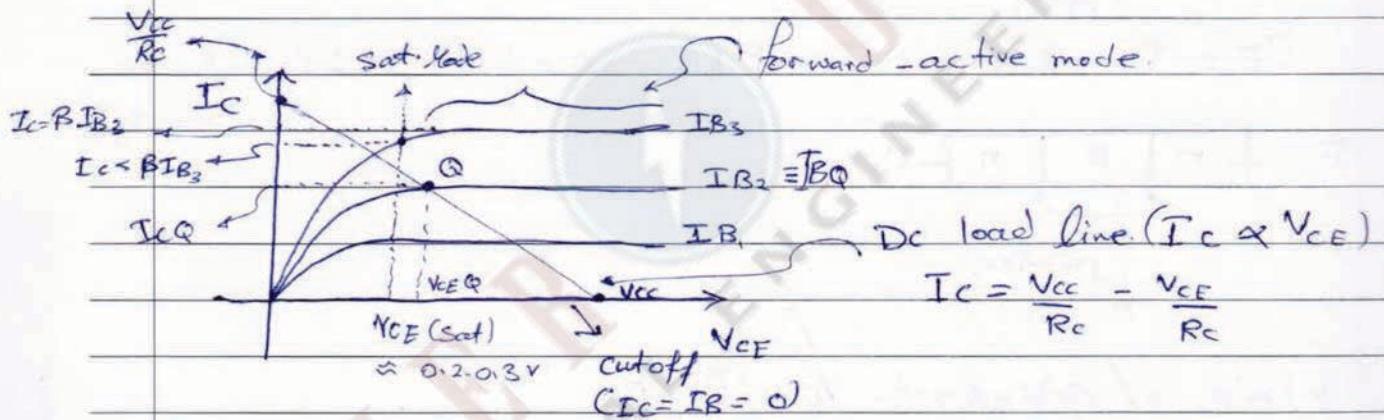

We control DC load line by changing  $R_C$  or  $R_B$ ; raising the ~~ex~~  $R_B$  will move the Q point into the forward active mode.

\*  $V_T$  : Thermal Voltage ( $V_T = 0.026$  V at room temp. 300K)

\*  $50 < \beta < 300$

\*  $\alpha \approx 0.999 \approx 1$

\*  $I_S$ : reverse-bias Saturation Current

$$\approx 10^{-15} - 10^{-12} A$$

$$\alpha = \frac{\beta}{1+\beta}$$

(2)

\* Dc analysis of BJT: We will study the following:

⇒ Finding the mode of operation.

⇒ Dc load line.

⇒ Finding the relation between  $V_o$  and  $V_i$ .

⇒ Dc analysis of multi stage circuit.

\* Steps for finding the mode of operation:-

1) assume forward active mode:-

$$\Rightarrow V_{BE} = 0.7 \text{ V}$$

$$\Rightarrow I_C = \beta I_B$$

2) check your assumption.

$$\Rightarrow I_B > 0 \text{ & } V_{CE} > V_{CE}(\text{sat}).$$

if yes : stop, otherwise:-

3) assume saturation:-

$$\Rightarrow V_{BE} = 0.7 \text{ V}$$

$$\Rightarrow V_{CE} = V_{CE}(\text{sat.})$$

$$\Rightarrow I_C \neq \beta I_B$$

⇒ check your assumption in 3

$$\Rightarrow I_C < \beta I_B$$

if yes, stop ; otherwise:-

5 Cut off Mode.

## lecture 2:

Ex: Consider the following circuit:


Given  $\beta = 100$ ,  $V_{BE(on)} = 0.7 \text{ V}$

$$V_{CE(\text{sat})} = 0.2 \text{ V}$$

[1] Find the mode of operation.

[2] Find the Q-point values.

[3] Draw the DC load line.

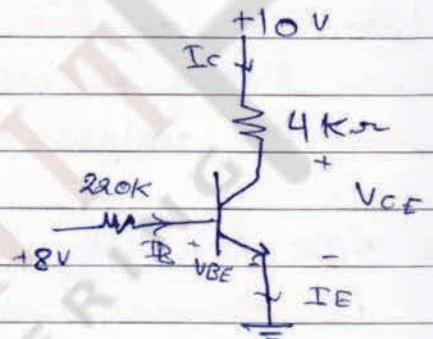

② Assume forward active mode.

$$V_{BE} = 0.7$$

$$I_C = \beta I_B$$

$$\Rightarrow \text{Input loop: } -8 + 220 I_B + 0.7 = \text{Zero?}$$

$$I_B = \frac{8 - 0.7}{220} = 33.2 \times 10^{-3} \text{ A} = 33.2 \text{ mA} > 0 \text{ Yes}$$

$$I_C = \beta I_B = 3.32 \text{ mA}$$

$\Rightarrow$  Output loop:-

$$-10 + 4 \times 3.32 + V_{CE} = 0$$

$$V_{CE} = 10 - 4 \times 3.32 = 3.28 \text{ V} > V_{CE(\text{sat})}, \text{ No}$$

So it is wrong assumption.

$\Rightarrow$  assume saturation mode:-

$$V_{BE} = 0.7, V_{CE} = V_{CE(\text{sat})} = 0.2 \text{ V}$$

$\Rightarrow$  Input loop

$$I_B = 33.2 \text{ mA}$$

$\Rightarrow$  Output loop:

$$-10 + 4 I_C + 0.2 = 0$$

$$I_C = 2.45 \text{ mA}$$

$\Rightarrow$  check  $I_C < \beta I_B$

$$2.45 < 3.32 \text{ mA}$$

Yes in Saturation mode.

b. Q-point values

$$I_{BQ} = 33.2 \mu\text{A}$$


$$I_{CQ} = 2.45 \text{ mA}$$

$$V_{CEQ} = 0.2 \text{ V}$$

c.

$$-10 + 4I_C + V_{CE} = 0$$
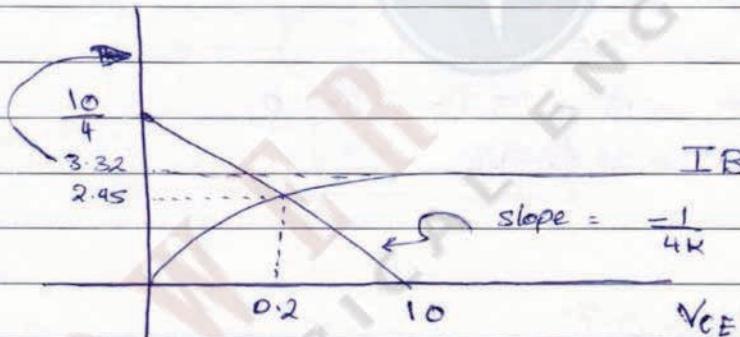
$$I_C = \frac{10}{4} - \frac{V_{CE}}{4} \quad \text{Dc load line.}$$




Ex: Draw the Voltage transfer curves ( $V_o \propto V_I$ ) for the following circuit

Given  $V_{BE(on)} = 0.7 \text{ V}$

$V_{CE(\text{Sat})} = 0.2 \text{ V}$

$\beta = 120$

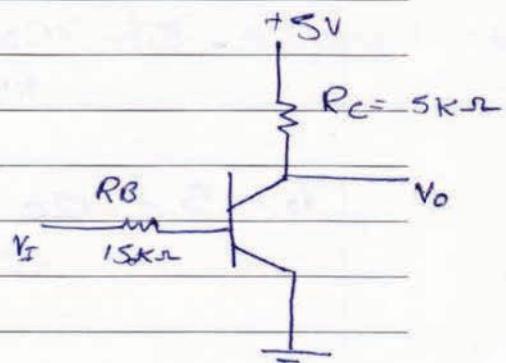

\* cut off

$$I_C = I_B = I_E = 0 \Rightarrow V_o = 5V$$

\* saturation

$$V_{CE(\text{sat})} = 0.2 \Rightarrow V_o = 0.2V$$

\* forward active mode:-

$$V_{BE} = 0.7$$

$$I_C = \beta I_B$$

$\Rightarrow$  input loop:

$$-V_I + 150 I_B + 0.7 = \text{Zero}$$

$$I_B = \frac{V_I - 0.7}{150}$$

$\Rightarrow$  Output Loop  $\Rightarrow -5 + 5 I_C + V_o = 0$

$$I_C = \frac{5 - V_o}{5}$$


$\Rightarrow I_C = \beta I_B$

$$\frac{5 - V_o}{5} = 120 \frac{V_I - 0.7}{150}$$


$$V_o = 5 - 120 \frac{(V_I - 0.7) R_C}{R_B}$$

$$= 5 - \frac{120 R_C V_I}{R_B} + \frac{120 R_C + 0.7}{R_B}$$

$$V_o = 5 + \frac{120 R_C \times 0.7}{R_B} - \frac{120 R_C}{R_B} V_I$$

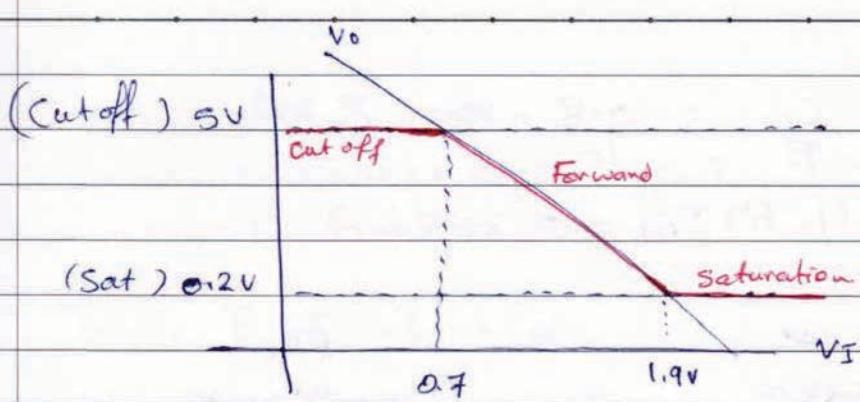

Lecture 3:

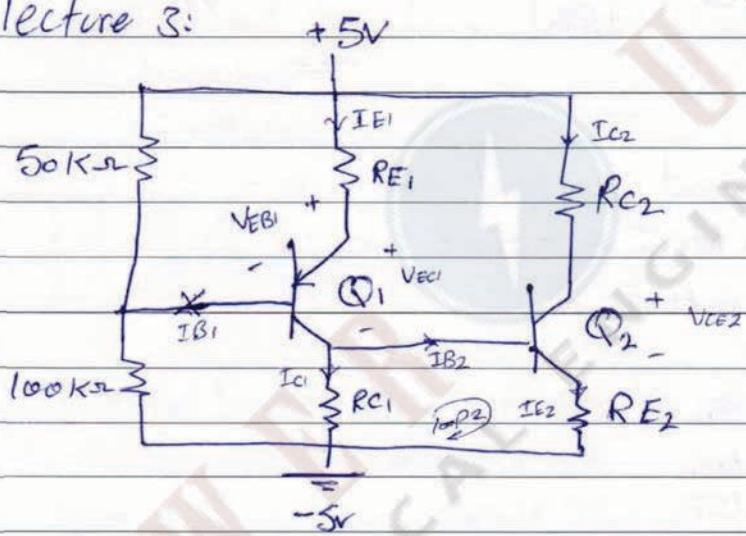

Given:

$$\beta = 100 \text{ for both } Q_1 \text{ and } Q_2$$

$$I_{C1} = I_{C2} = 0.8 \text{ mA}$$

$$V_{EB1} = V_{BE2} = 0.7 \text{ V}$$

$$V_{CE1} = 3.5 \text{ V}, V_{CE2} = 4 \text{ V} \Rightarrow Q_1 \text{ & } Q_2 \text{ are forward mode}$$


Find  $R_{E1}, R_C1, R_{E2}, R_{C2}$

$Q_1: pnp$

$Q_2: npn$

$$I_{B1} = I_{B2} = \frac{I_{C1}}{\beta} = \frac{0.8}{100} = 8 \mu A$$
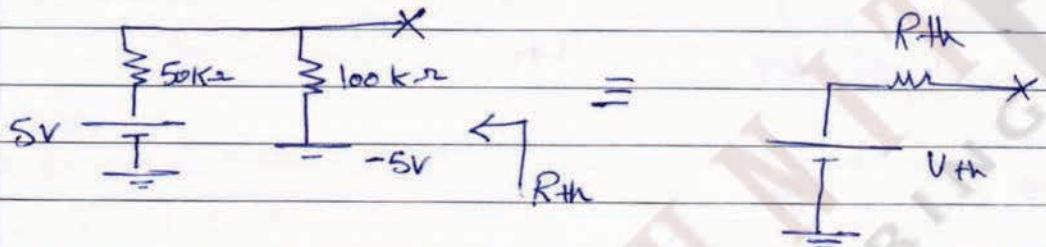
$$I_{E1} = I_{E2} = (1 + \beta) I_{B1} = 0.808 mA$$



$$R_{th} = 33.3 k\Omega$$

Calculate the current

$$-5 + 50I + 100I + -5 = 0$$

$$I = \frac{10}{150} mA$$

$$-V_{th} + I \cdot 100 - 5 = 0$$

$$V_{th} = -5 + \frac{1000}{150}$$

input loop 1

$$-5 + I_{E1} R_{E1} + 0.7 + I_{B1} R_{th} + V_{th} = 0$$

$$R_{E1} = 2.93 k\Omega$$

$$\text{output loop 1: } -5 + I_{E1} R_{E1} + V_{E1} + R_{C1} (I_{C1} - I_{B2}) - 5 = 0$$

$$R_{C1} = 5.215 k\Omega$$

$$\text{input loop 2: } -(-5) - R_{C1} (I_{C1} - I_{B2}) + V_{BE2} + I_{E2} R_{E2} - 5 = 0$$

$$R_{E2} = 4.25 k\Omega$$

Output loop 2:


$$-S + I_{C2} R_{C2} + V_{CE2} + R_{E2} I_{E2} - S = 0$$

$$R_{C2} = 3.215 \text{ k}\Omega$$

Basic BJT Amplifiers :-

Dc voltage source

used for biasing


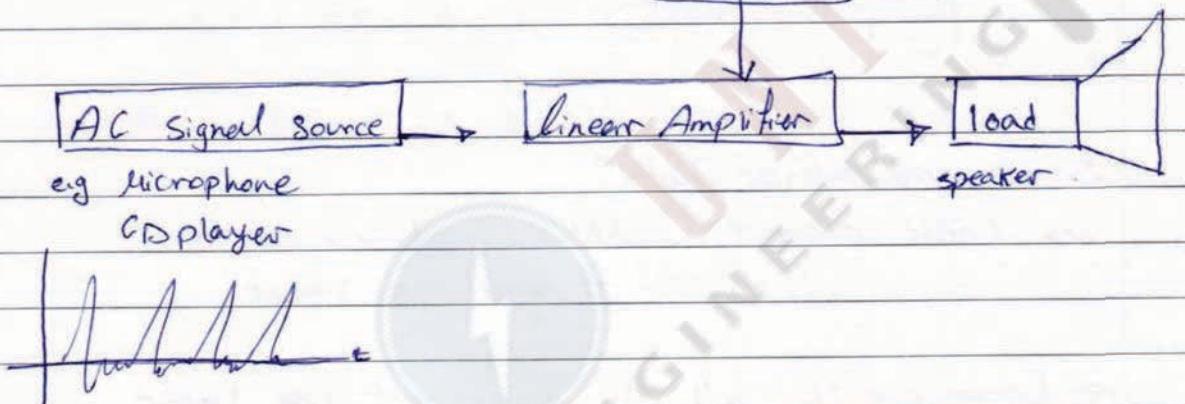


Dc voltage Source: to set the Q-point in the forward active mode.

Ac signal source: it should be small Ac signal.


Linear Amp.: it must be linear

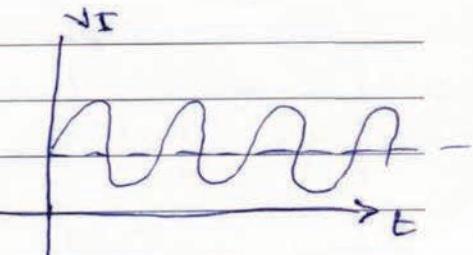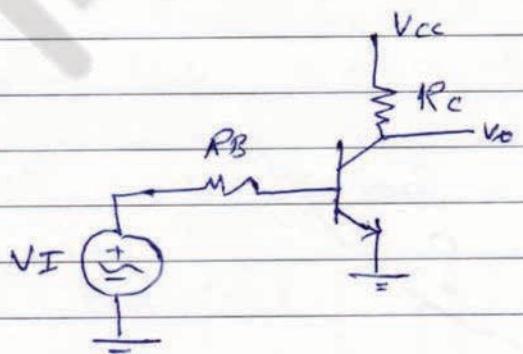\* the transistor in amplifier circuit should be in the forward active region. why?



$$V_I = 3 + 2 \sin \omega t$$

(a)

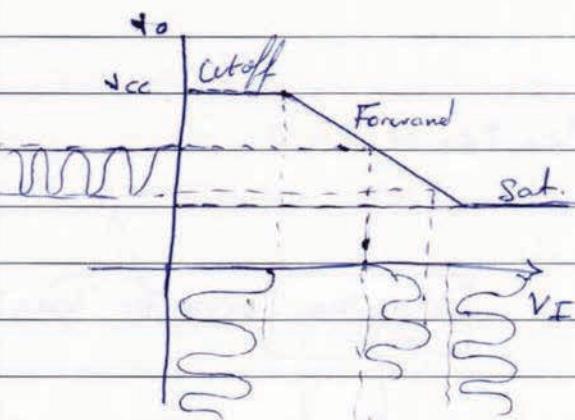

2. we need a linear, why?

→ linear element  $\text{---M---, ---H---, } \text{---O---}$   
 $I \propto V$  is linear

→ linear circuit: all its component are linear


→ linear amplifier: means that the relationship between  $V_I$  &  $V_O$  is linear.

→ to get linear amplifier, we need all it's component to be linear

→ Amplifier consist of  $\text{---M---, ---H---, } \text{---K---}$   
 linear, linear, non-linear!

③ we need a small AC signal to get a linear Transistor  
 How?

→ graphically:

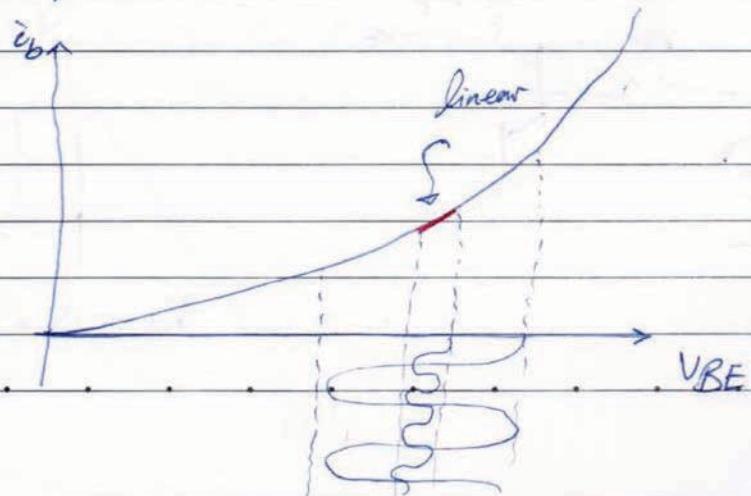

\* Mathematically:-

Note:  $I_B$  : Dc Current ;  $I_B = 3A$

$i_b$  : Ac current ;  $i_b = 2S \sin(\omega t)$

$i_B$  : Ac + Dc current ,  $i_B = 5 + 3 \sin(\omega t)$ .

$I_B$  : phasor form ,  $I_B = 3 \angle 30^\circ$

$$\text{we know that: } i_B = \frac{I_s}{1+\beta} \exp\left(\frac{V_{BE}}{V_T}\right)$$

$$= \frac{I_s}{1+\beta} \exp\left(\frac{V_{BEQ} + V_{be}}{V_T}\right)$$

Dc      Ac

$$i_B = \underbrace{\frac{I_s}{1+\beta} \exp\left(\frac{V_{BEQ}}{V_T}\right)}_{IBQ} \cdot \exp\left(\frac{V_{be}}{V_T}\right)$$

$$i_B = I_{BQ} \exp\left(\frac{V_{be}}{V_T}\right)$$

Note: Taylor Series :  $e^\theta = \frac{\theta^0}{0!} + \frac{\theta^1}{1!} + \frac{\theta^2}{2!} + \dots$


$\Rightarrow$  if  $\theta \ll 1$

$$e^\theta \approx 1 + \theta \quad [\text{exponential relationship will be linear}]$$

$$\Rightarrow e^{\frac{V_{be}}{V_T}} \approx 1 + \frac{V_{be}}{V_T}$$

$$\text{if } \frac{V_{be}}{V_T} \ll 1$$

$$\Rightarrow V_{be} \ll V_T$$

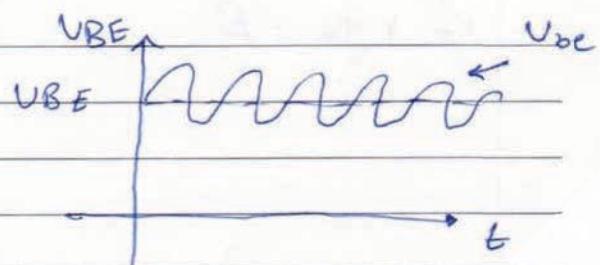

if  $V_{be}$  is small value:

$$i_B \approx I_{BQ} \left(1 + \frac{V_{be}}{V_T}\right)$$


$$I_{BQ} + i_b \approx I_{BQ} + \frac{I_{BQ}}{V_T} V_{be}$$

$$i_b \approx \frac{I_{BQ}}{V_T} V_{be}$$

constant

So, Linear relationship between  $i_b$  &  $V_{be}$ . It can be implemented as ( $r_\pi$ )

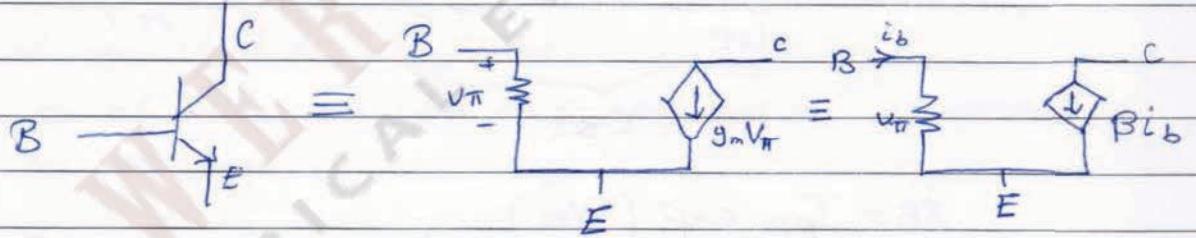Small Signal Hybrid- $\pi$  equivalent circuit



$r_\pi = V_T$   $\approx$  diffusion resistance.  
 $I_{BQ}$

$g_m = \frac{I_{CQ}}{V_T}$   $A/V$  (-ve) trans conductance.

$$r_\pi \times g_m = \beta$$

\* General steps to solve an amplifier circuit

I Dc analysis

⇒ Draw Dc equivalent circuit

1. Kill all Ac Sources
2. replace all capacitors by open circuit
3. Keep all Dc Sources.

⇒ Find  $I_{BQ}$ ,  $I_{CQ}$ ,  $I_{CEQ}$

II Ac analysis:

⇒ Draw the Ac equivalent circuit

1. replace the transistor by Hybrid- $\pi$  equivalent circuit.
2. Kill all Dc sources
3. replace all capacitors by short-circuit

⇒ Find Voltage gain  $A_v = \frac{V_o}{V_i}$

$i_b$ ,  $i_c$ ,  $V_{ce}$ ,  $R_i$ ,  $R_o$

III by Using Superposition:-

Find result = Ac + Dc

$$i_B = i_b + I_{BQ}$$

## lecture 4:

~~Ex:~~

$$\beta = 100, V_{BE(\text{on})} = 0.7 \text{ V}$$

find the voltage gain  $A_v = \frac{V_o}{V_s}$

Dc analysis



⇒ Dc equivalent circuit

⇒ input loop

$$-1.2 + I_B Q \cdot 50 + 0.7 = 0$$


$$I_B Q = 10 \mu\text{A}$$
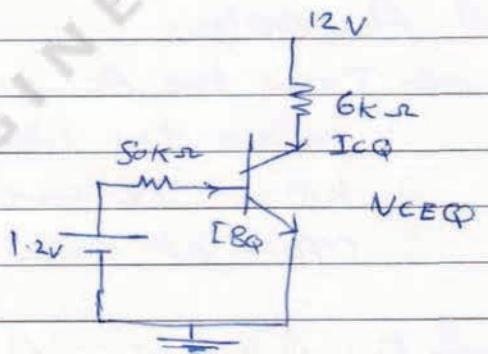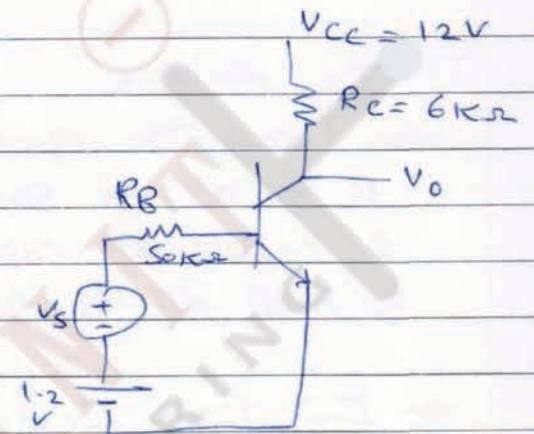
$$\Rightarrow I_C Q = \beta I_B Q \\ = 1 \text{ mA}$$



\* Ac analysis

⇒ Ac equivalent circuit:

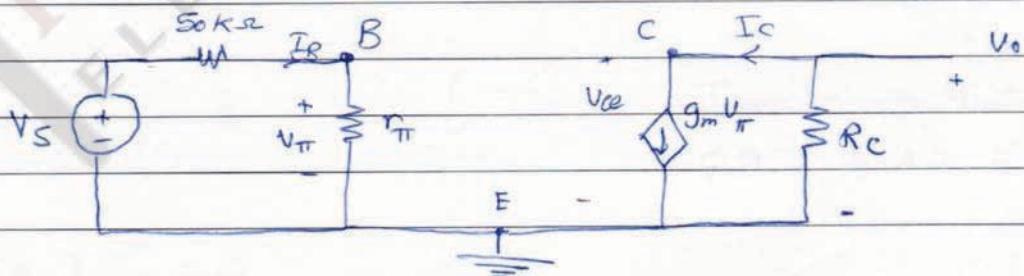

$$A_V = \frac{V_o}{V_s}$$

$$\Rightarrow V_o = -g_m V_{\pi} R_C \quad \text{Ans(1)}$$

$$V_{\pi} = \frac{V_s r_{\pi}}{V_{\pi} + R_B} \quad \text{Ans(2)}$$

$\Rightarrow$  Sub Q in (1)

$$V_o = -g_m R_C + \frac{V_s V_{\pi}}{V_{\pi} + R_B}$$

$$A_V = \frac{V_o}{V_s} = \frac{-g_m R_C V_{\pi}}{r_{\pi} + R_B}$$

$$r_{\pi} = \frac{V_I}{I_{BQ}} = \frac{0.026}{10 \times 10^{-6}} = 2.6 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_I} = 38.5 \times 10^{-5} \frac{A}{V}$$

$$A_V = -11.4 \quad * \text{ the minus sign makes a phase shift } 180^\circ$$

B] find and draw  $i_B$ ,  $i_C$ ,  $i_{CE}$  if  $V_S = 0.25 \sin \omega t$

$$i_B = i_b + I_{BQ}$$

$$= \frac{0.2 \sin \omega t}{50 + 2.6} + 10 \mu A$$

$$i_B = 4.75 \sin \omega t + 10 \mu A$$

Sol.

$$i_c = i_e + I_{CQ}$$





$$\beta I_b + 1 \text{ mA}$$

$$i_c = 0.475 \sin \omega t + 1 \text{ mA}$$

$$V_{CE} = V_{ce} + V_{CEQ}$$


$$-i_c R_C + 12 - I_{CQ} \times 6$$

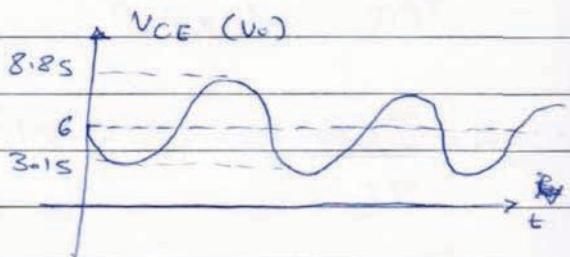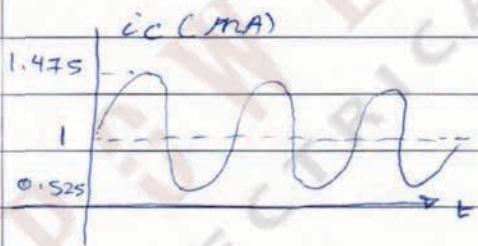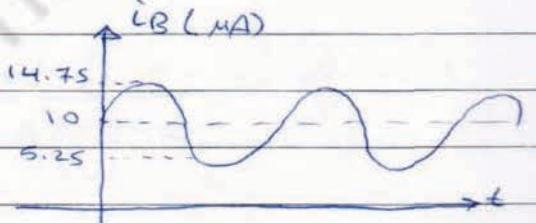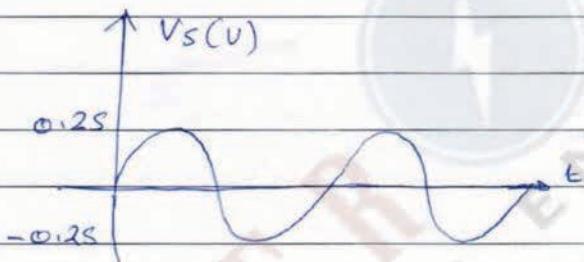
$$V_{CE} = -2.85 \sin \omega t + 6 \text{ V}$$



\* Hybrid- $\pi$  equivalent model including the Early Effect

Early effect

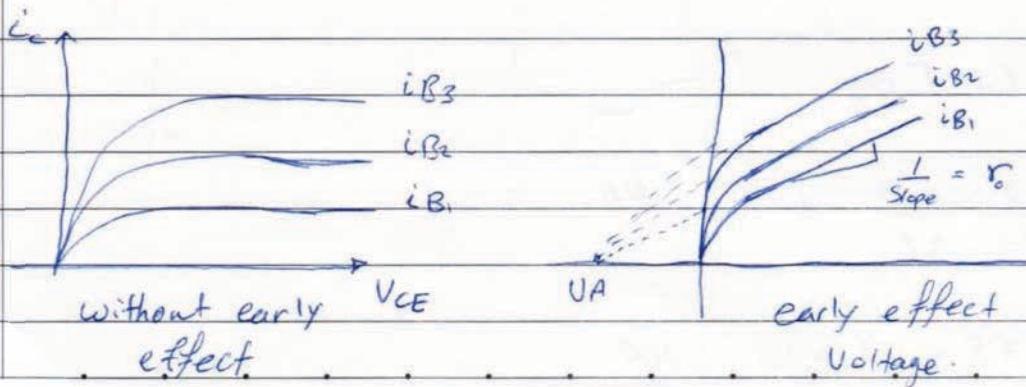

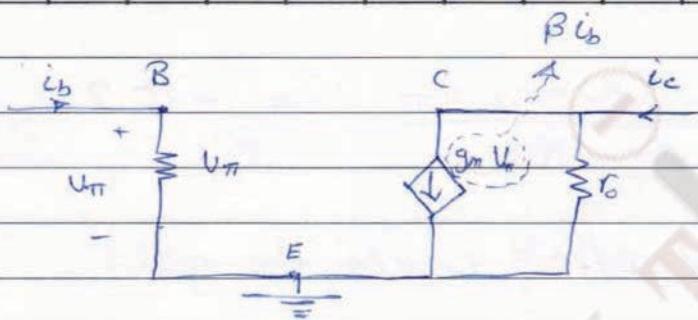


$$r_o = \frac{V_A}{I_{CQ}} \approx$$

Lecture 5:

Ex: consider the last example:-

$$\text{find } A_v = \frac{V_o}{V_s} , \text{ if } V_A = 50 \text{ V}$$
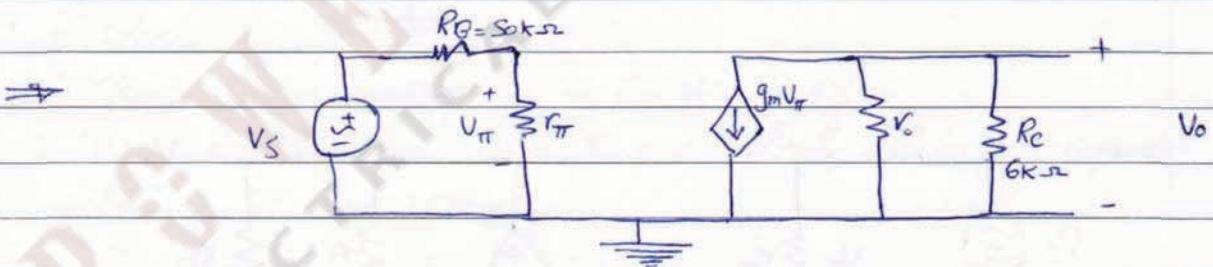
$$r_o = \frac{V_A}{I_{CQ}} = \frac{50}{1 \text{ mA}} = 50 \text{ k}\Omega$$



$$A_v = \frac{V_o}{V_s}$$

$$V_o = -g_m V_{\pi} (R_C // r_o) \rightsquigarrow (1)$$

$$V_{\pi} = V_s \frac{r_{\pi}}{r_{\pi} + R_B} \rightsquigarrow (2)$$



Sub 2 in 1

$$V_o = -g_m (R_C // V_o) V_s \frac{r_{\pi}}{r_{\pi} + R_B}$$

$$\Delta V = -\frac{g_m (R_C \parallel r_o) r_{\pi}}{r_{\pi} + R_B} = -10.2$$

$\Rightarrow$  Early effect reduces the gain


\* PNP transistor

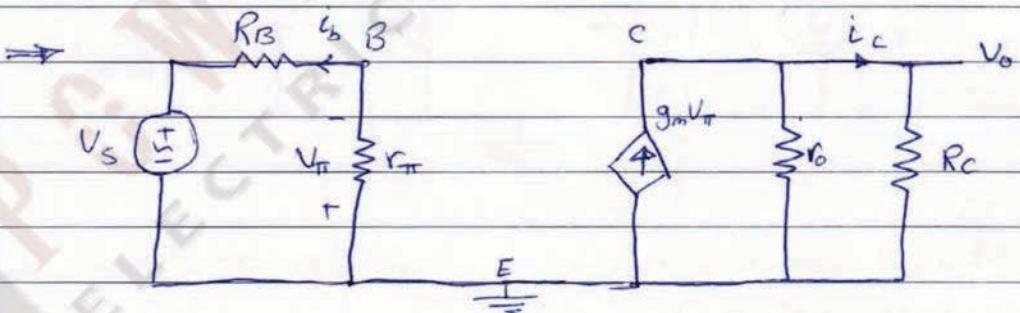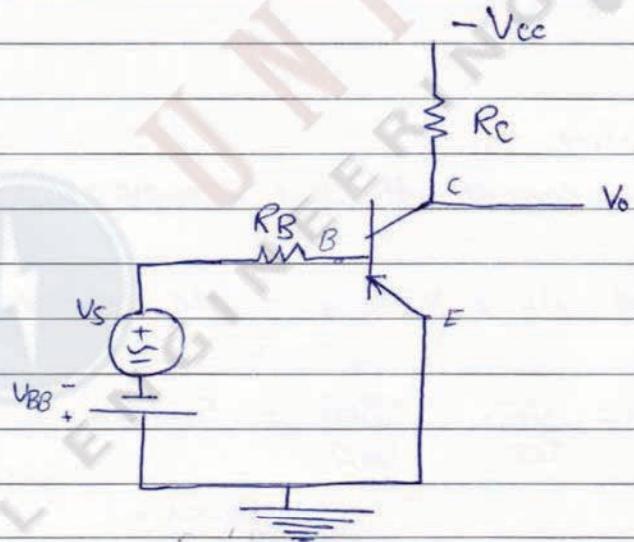

$$\Delta V = g_m V_{\pi} (r_o \parallel R_C)$$

$$V_{\pi} = -\frac{V_s r_{\pi}}{r_{\pi} + R_B}$$

Note:

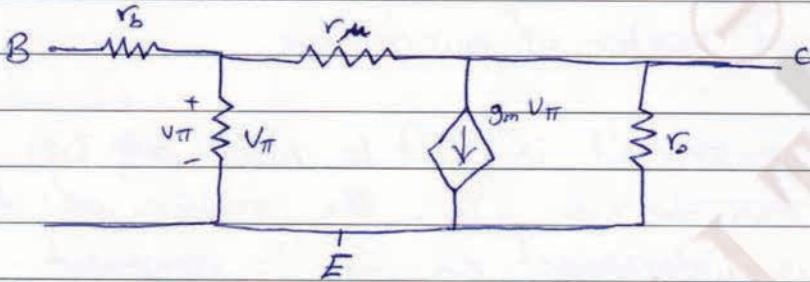


\* Basic Transistor Amplifier Configuration:-

- 1) Common Emitter Amplifier (CE)
- 2) Common Base Amplifier (CB)
- 3) Common Collector Amplifier (CC)

\* CE amplifier:-

- 1) Basic CE amplifier
- 2) Basic CE amplifier with Emitter resistor
- 3) Basic CE amplifier with Emitter resistor and By pass capacitor
- 4) Advanced CE amplifier.

\* Basic CE amplifier.

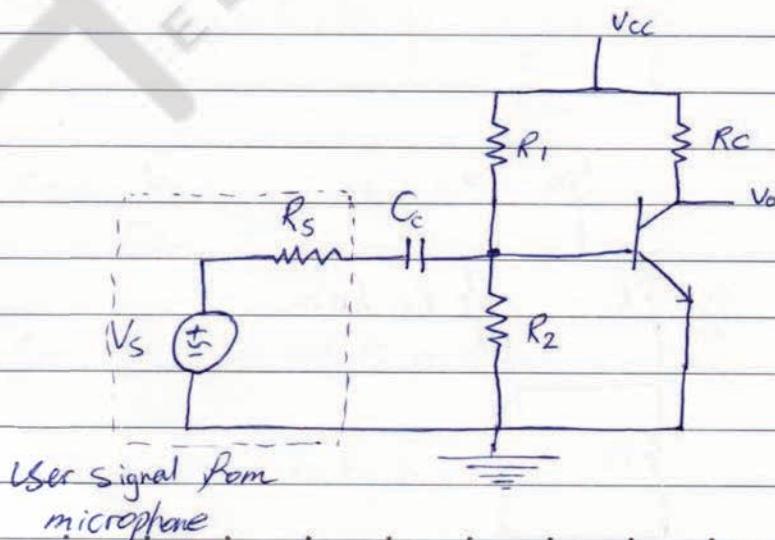

$C_c$ : Coupling capacitor

$R_s$ : internal resistor of microphone.

Coupling Capacitor: it is used to block any DC component from the user. So, the position of the Q-point is independent on the dc component from the user

lecture 5:

6/3/2014


1) Basic CE amplifier:-

Ex:-

$$\beta = 100, V_{BE(\text{on})} = 0.7 \text{ V}, V_A = 100$$


Find :-

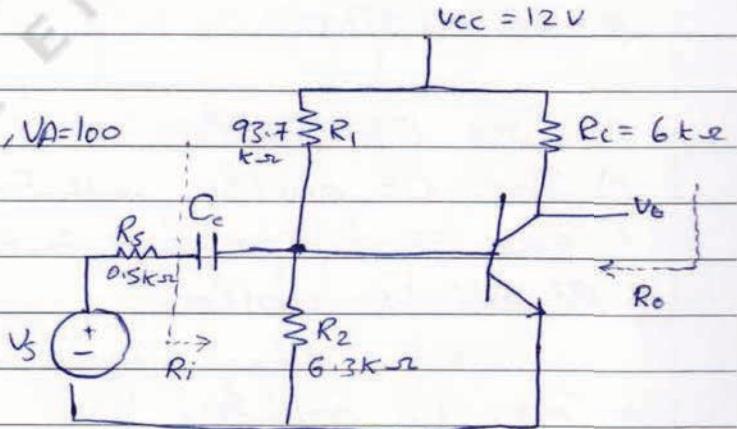- 1) the Voltage gain  $A_V$
- 2)  $R_i$  (input impedance)
- 3)  $R_o$  (output impedance)



Dc analysis:-

Dc eq. circuit

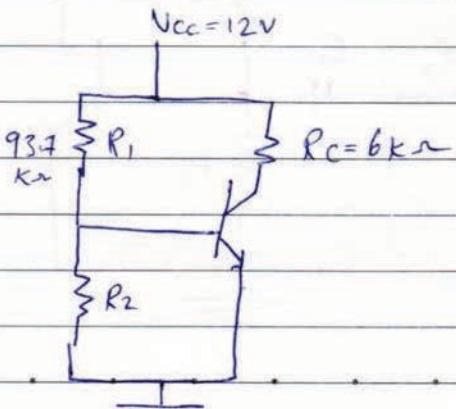


(Q20)

this circuit can be represented in thevenin circuit :-

$$R_{th} = R_1 \parallel R_2$$
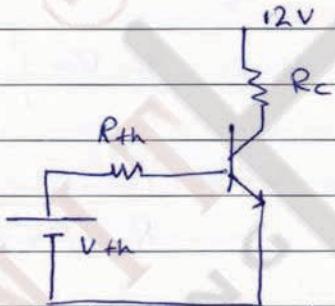
$$V_{th} = \frac{12 \cdot R_2}{R_2 + R_1}$$




$$\Rightarrow -V_{th} + R_{th} I_{BQ} + 0.7 = 0$$

$$I_{BQ} = 9.5 \text{ mA}$$


$$I_{CQ} = \beta I_{BQ} = 0.95 \text{ mA}$$
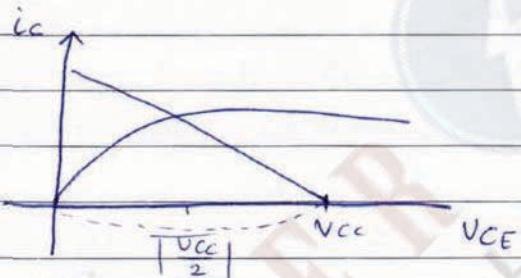
$$V_{CEQ} = 12 - I_{CQ} R_C = 6.31 \text{ V}$$



\* Ac analysis

Ac eq. circuit

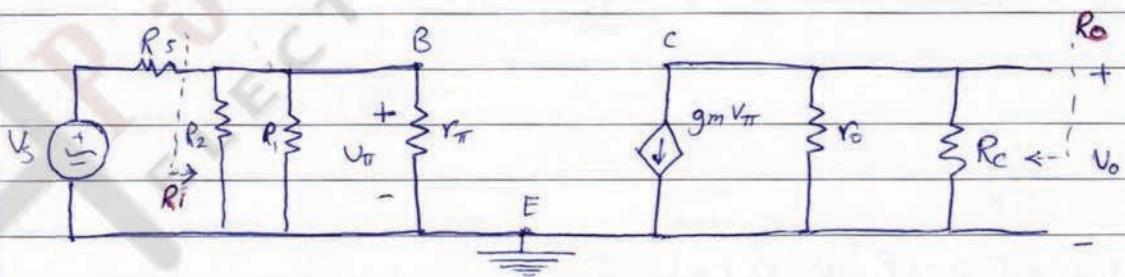

$$r_\pi = \frac{V_T}{I_{BQ}} = 2.74 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = 36.5 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_{CQ}} = 105 \text{ k}\Omega$$

$$AV = \frac{V_o}{V_s}$$

$$\Rightarrow V_o = -g_m V_T (R_C // R_o) \quad \rightarrow (1)$$

$$\Rightarrow V_T = \frac{N_S (R_1 // R_2 // r_{\pi})}{R_1 // R_2 // r_{\pi} + R_S} \quad \rightarrow (2)$$


Sub 2 in 1 :-

$$AV = \frac{V_o}{V_s} = -g_m (R_C // r_o) (R_1 // R_2 // r_{\pi})$$

$$R_1 // R_2 // r_{\pi} + R_S$$

$$= -163$$

(2) Back to the AC eq. circuit.

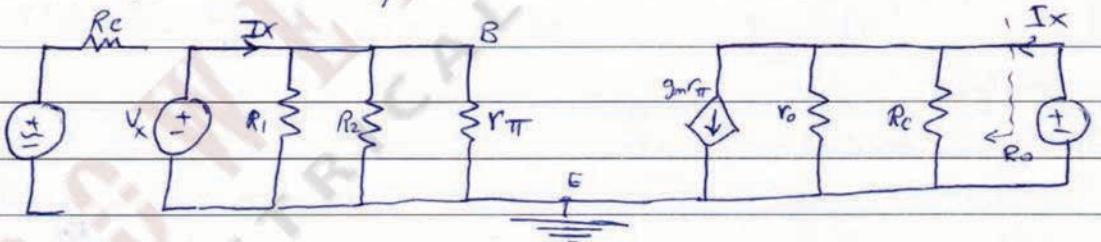

$$R_i = \frac{V_x}{I_x}$$

$$-V_x + I_x (R_1 // R_2 // r_{\pi}) = 0$$

$$R_i = \frac{V_x}{I_x} = R_1 // R_2 // r_{\pi}$$

$$= 1.87 k\Omega$$

to find  $R_o$  reconnect  $V_s$  &  $R_s$  & delete  $V_x$

$$R_o = \frac{V_x}{I_x}$$

$$R_o = r_o \parallel R_C \\ = 5.68 \text{ k}\Omega.$$

\* Advantages:-  
high  $A_v$

\* Disadvantages:-

1. very sensitive to  $V_{BE(on)}$
2. unstable performance.


$\Rightarrow$  if  $V_{BE(on)} = 0.7 \text{ V}$

$$I_{BQ} \rightarrow I_{CQ} \rightarrow V_{CEQ} = 6.31 \text{ V} \text{ (forward)}$$


$\Rightarrow$  if  $V_{BE(on)} = 0.6 \text{ V}$

$$I_{BQ} \rightarrow I_{CQ} \rightarrow V_{CEQ} = -3.6 \text{ V} \text{ (it is not forward.)}$$

2] high loading effect:-

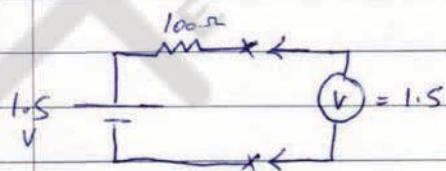

Source without  
load.

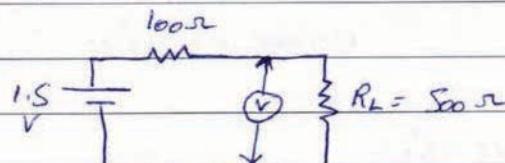

Source with load.  
 $V = 1.25 < 1.5$   
(loading effect)


To reduce the loading effect ( $V_o \approx V_s$ )

$R_L$  should be  $\gg R_s$

$\Rightarrow$  in our example

$$R_i = 1.87 \text{ k}\Omega \quad ? \quad R_s \ll R_i$$

$$R_s = 0.5 \text{ k}\Omega$$

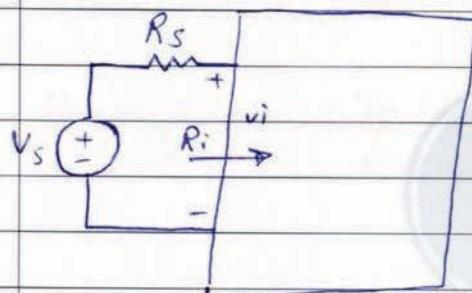


$$v_i = \frac{V_s R_i}{R_i + R_s}$$

$$v_i = 0.789 V_s$$

lecture 6

9/3/2014

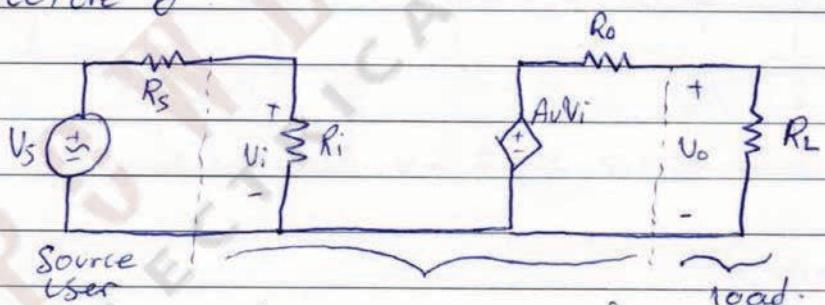

two-port eq. circuit for  
Voltage amplifier.

$$v_i = \frac{V_s R_i}{R_i + R_s}$$


$\Rightarrow$  to reduce the loading effect on the input circuit ( $v_i \approx V_s$ )  
we need high  $R_i$

$$V_o = A_v V_i + \frac{R_L}{R_L + R_o}$$

$\Rightarrow$  to reduce the loading effect on the circuit's output  
 $(v_o \approx A_v V_i)$  we need low  $R_o$

$\Rightarrow$  for current amplifier we need low  $R_i$  and high  $R_o$

## 2] CE amplifier with $R_E$

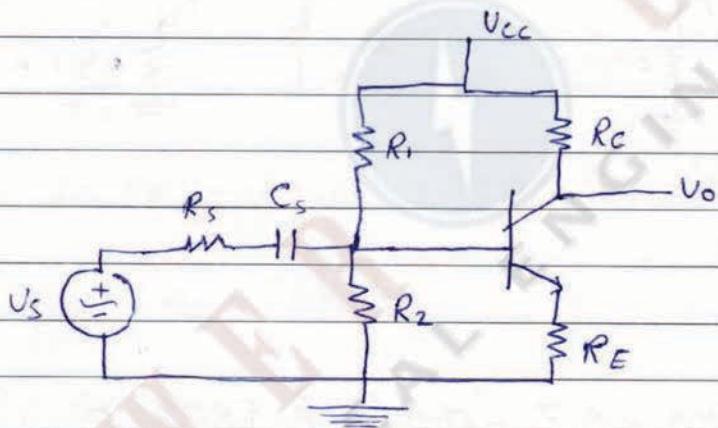


\* Disadvantages:-

Small Av

\* Advantages:-

1.  $A_v$  is less dependent on  $\beta$  (Stable gain)
2. Small loading effect.

Ex:-

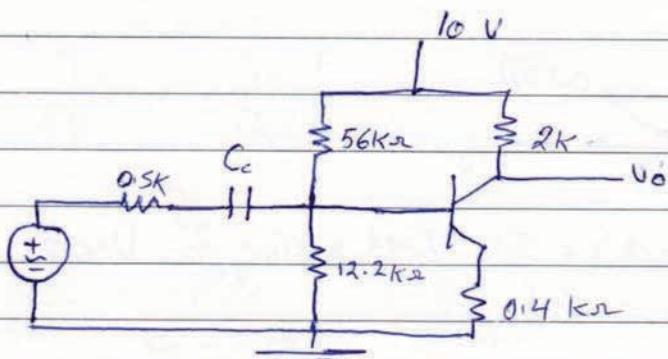


(25)

$B = 100$ ,  $U_A = \infty$ ,  $V_{BE(on)} = 0.7 \text{ V}$   
 $\Rightarrow r_o = \infty$  (no early effect).

Find : ①  $A_v$  ②  $R_i$  ③  $R_o$

Dc analysis :-

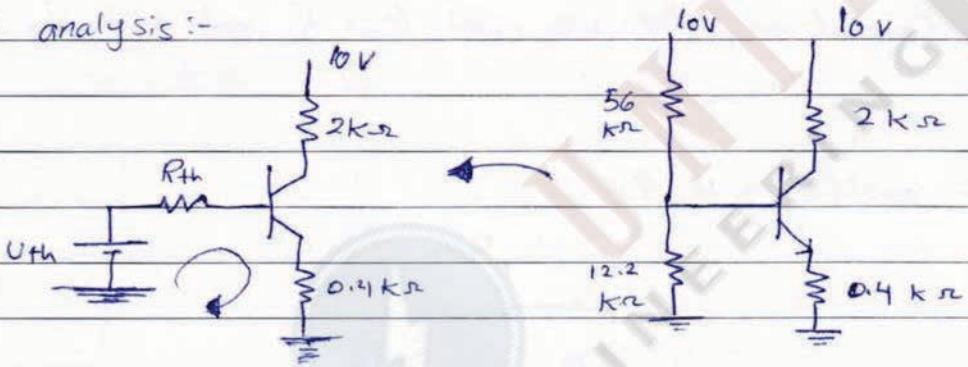

$$R_{th} = 56 // 12.2 = 10 \text{ k}\Omega$$

$$U_{th} = 1.78 \text{ V}$$


input loop

$$-U_{th} + R_{th} I_{BQ} + 0.7 + 0.4(1+B) I_{BQ} = 0$$

$$I_{BQ} = 0.0216 \text{ mA}$$


$$I_{CQ} = B I_{BQ} \\ = 2.16 \text{ mA}$$

$$V_{CEQ} = 4.81 \text{ V}$$

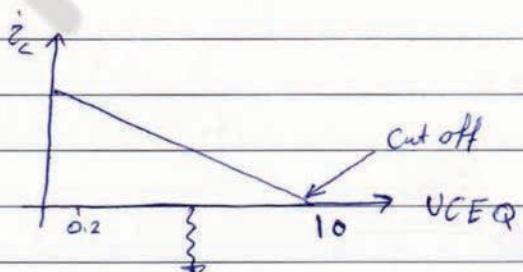

$$V_{CEQ} \left( \frac{10 + 0.2}{2} \right) = 5.1 \text{ best value for } V_{CEQ}$$

Ac analysis

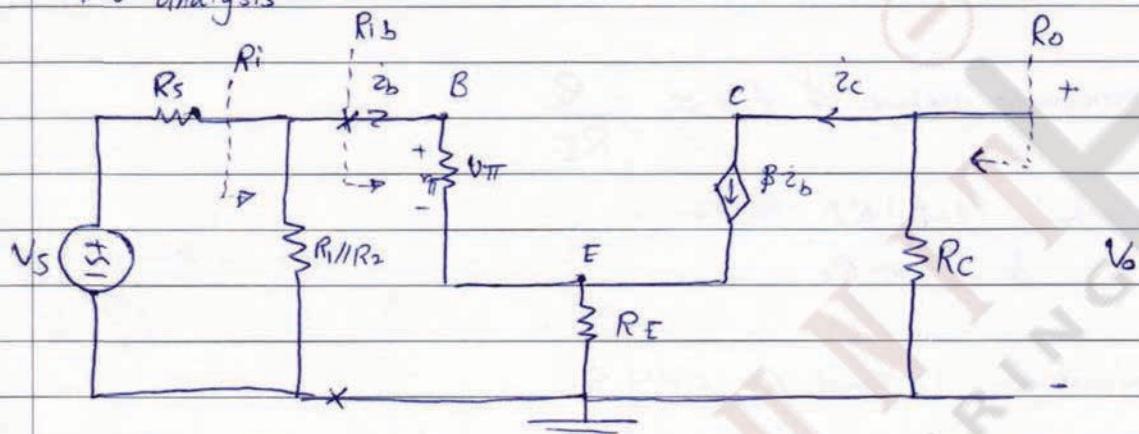


$$R_{ib} = \frac{V_x}{I_x}$$

$$-U_x + i_x r_\pi + (1+\beta) i_x R_E = 0$$

$$R_{ib} = \frac{V_x}{i_x} = r_\pi + (1+\beta) R_E$$
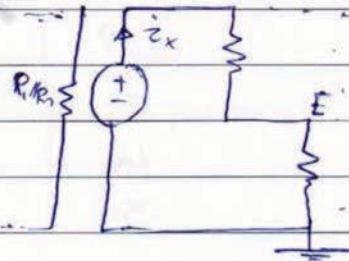
$$R_i = R_1 // R_2 // R_{ib} = 8.06 \text{ k}\Omega$$



$$A_V = \frac{V_o}{V_s}$$

$$\Rightarrow V_o = -\beta i_b R_c \quad \text{---(1)}$$

$$\Rightarrow V_i = \frac{V_s}{R_i + R_s}$$

$$\Rightarrow i_b = \frac{V_i}{R_{ib}} = \frac{V_s R_i}{R_{ib}(R_i + R_s)} \quad \text{---(2)}$$

from 1 & 2

$$A_V = \frac{V_o}{V_s} = \frac{-\beta R_c}{r_\pi + (1+\beta) R_E} \left( \frac{R_i}{R_i + R_s} \right) \Rightarrow A_V = -4.53$$

exact value.

lecture 6 :-

11/3/2014

$$\text{approximate value of } Av \approx -\frac{R_C}{R_E}$$

because:-  $(1+\beta)R_E \gg r_{\pi}$


&  $R_i \gg R_S$

disadvantage:- 1. Small  $Av = -4.53$

advantage: 1.  $Av$  is less dependant on  $\beta$

$\beta$	$Av$
50	-4.41
100	-4.53
150	-4.57


2. Small loading effect

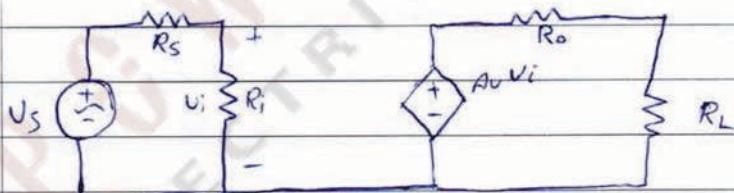

$$\Rightarrow V_i = \frac{V_s R_i}{R_i + R_S}$$

$$V_i = 0.942 V_s$$

### 3] CE with RE and Bypass Capacitor

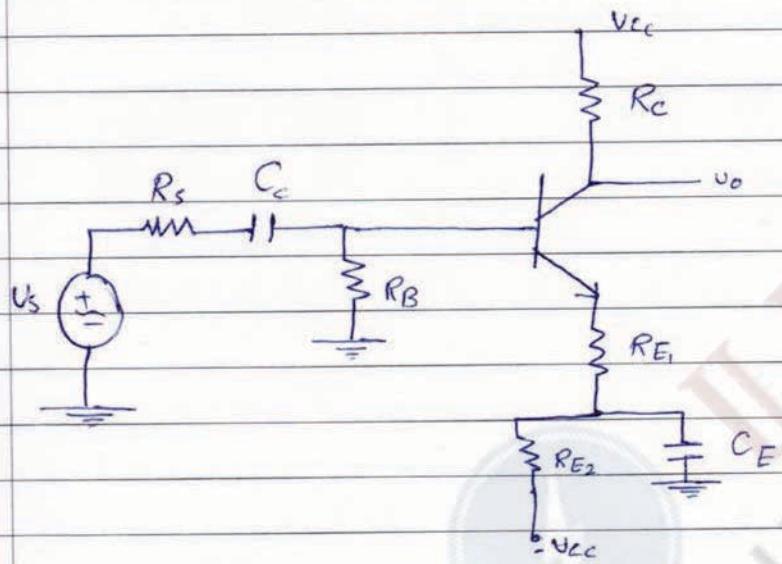

CE: Bypass capacitor. to satisfy AC & DC requirement

lecture 7:

16/3/2014


Consider a CE amplifier with  $R_E$ . use the approximate gain  $A_v = -\frac{R_C}{R_E}$ . assume that  $I_{CQ} = 1mA = I_{EQ}$

$V_{CEQ} = 5V$ ,  $\beta = 99$ ,  $V_{CC} = 9V$ , find  $R_C$  &  $R_E$  such that :

(1)  $A_v = -8$

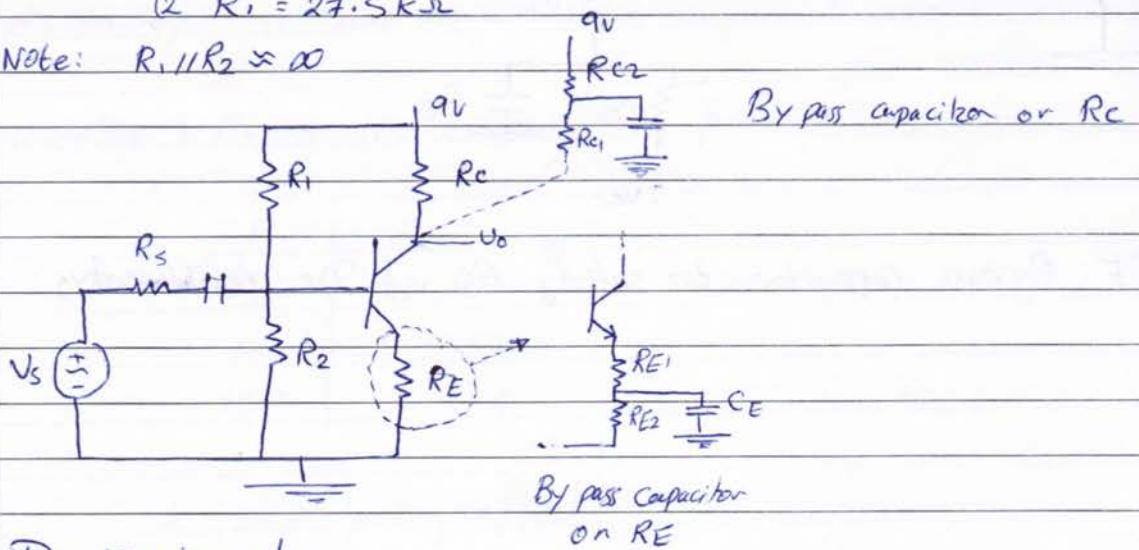(2)  $R_i = 27.5k\Omega$

Note:  $R_1 \parallel R_2 \approx \infty$



and Dc requirements:

④  $I_{CQ} = 1mA$

④  $V_{CEQ} = 5V$

and Ac requirements:-

④  $A_v = -8$

④  $R_i = 27.5k\Omega$ .

\* from Dc requirement take the output loop:

$$-9 + I_{CQ} R_C + V_{CEQ} + I_{EQ} R_E = 0$$

$$\boxed{R_C + R_E = 4 k\Omega} \text{ and } (1)$$

from AC requirements:-

$$\Rightarrow A_V = -\frac{R_C}{R_E} \Rightarrow R_C = 8R_E \quad \text{Ans(1)}$$

$$\Rightarrow R_i = R_1 \parallel R_2 \parallel R_{ib}$$

$$27.5 = r_\pi + (1+\beta)R_E$$

$$r_\pi = \frac{V_T}{I_{BQ}} = 2.574$$

$$\Rightarrow R_E = 0.25 \text{ k}\Omega$$

$$\text{from 1} \Rightarrow R_C = 3.75 \text{ k}\Omega$$

$$\text{from 2} \Rightarrow R_C = 2 \text{ k}\Omega$$

conflict !!

$\Rightarrow$  Solution : use Bypass Capacitor on  $R_E$  or  $R_C$

Bypass capacitor on  $R_E$  :-

DC

$$-9 + I_{CQ} R_C + V_{CEQ} + I_{EQ} (R_{E1} + R_{E2}) = 0 \quad \text{Ans(1)}$$

AC


$$-8 = \frac{-R_C}{R_{E1}} \Rightarrow R_C = 8R_{E1} \quad \text{Ans(2)}$$

$$R_i = r_\pi + (1+\beta)R_{E1} \Rightarrow R_{E1} = 0.25 \text{ k}\Omega$$

$$\Rightarrow \text{from (2)} \quad R_C = 2 \text{ k}\Omega$$

$$\text{from (1)} \quad R_{E2} = 1.75 \text{ k}\Omega$$


\* advanced CE amplifier:-

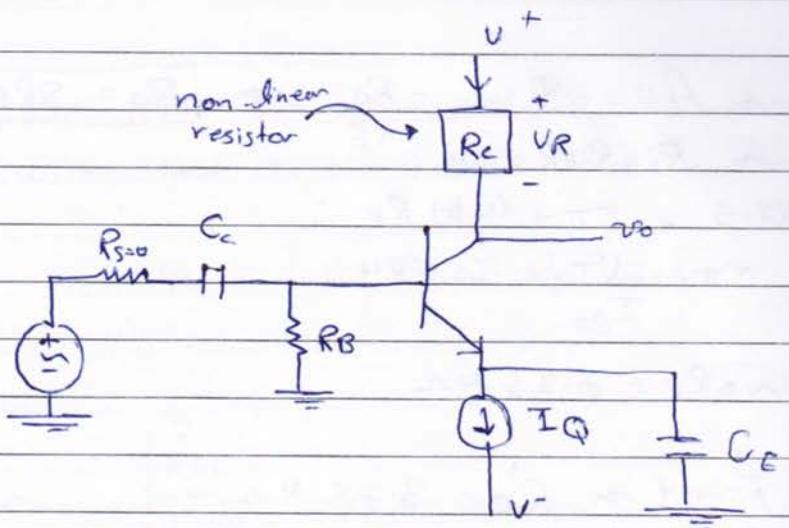

Advantages :-


very high  $A_v$

non-linear resistor:-

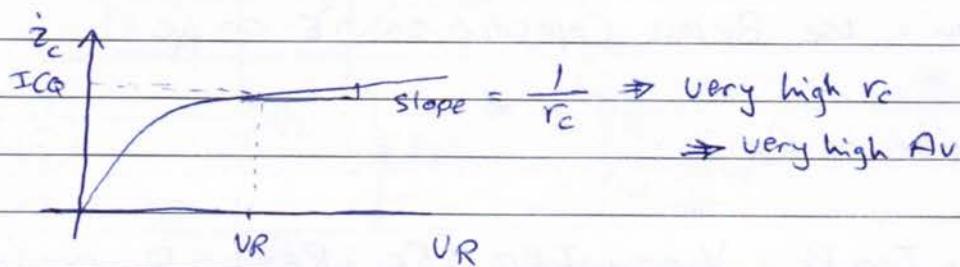

Ex: if  $I_Q = 0.5 \text{ mA}$ ,  $\beta = 120$ ,  $V_A = 80 \text{ V}$ ,  $R_C = 120 \text{ k}\Omega$   
 find  $A_v$ ?

AC analysis:-

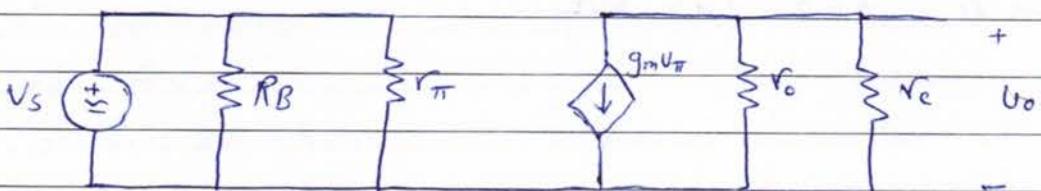

$$I_{EQ} = I_Q = 0.5 \text{ mA}$$

$$r_o = \frac{V_A}{I_{CQ}} = 160 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = 19.2 \text{ mA}$$

$$A_v = -g_m (r_o \parallel R_C) \\ = -1317 \rightarrow \text{very high gain}$$

lecture 8:


18/3/2014

\* Ac load Line :-

$\Rightarrow$  DC load Line :  $I_C \propto U_{CE}$  (DC circuit)

$\Rightarrow$  AC load Line :  $i_{ac} \propto U_{CE}$  (AC circuit).

Ex:-

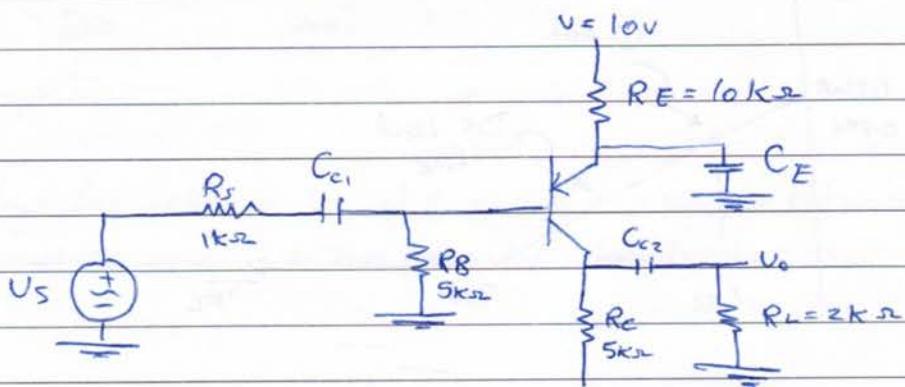

$$\beta = 150$$

$$V_{FB} = 0$$

$$U_{EB(\text{on})} = 0.7 \text{ V}$$

find & draw the DC and AC load line :-

[Common Emitter amplifier]

Dc analysis:-

input loop:

$$-I_0 + I_{EQ} - I_0 + 0.7 + 5I_{BQ} = 0 \\ \rightarrow (1+\beta) I_{BQ}$$


$$\Rightarrow I_{BQ} = 5.96 \text{ mA}$$

$$\Rightarrow I_{CQ} = \beta I_{BQ} = 0.894 \text{ mA}$$

output loop:-

$$-I_0 + I_{EQ} R_E + V_{EQ} + I_{CQ} R_C - I_0 = 0$$

$$\therefore V_{EQ} = 6.53 \text{ V}$$

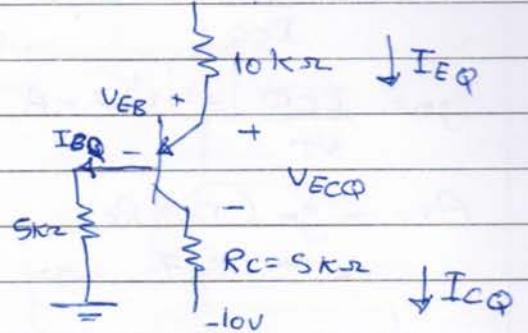


Dc load Line:-


$$-V^+ - I_C R_E \left( \frac{1+\beta}{\beta} \right) I_C + V_{EC} + I_C R_C = 0 \\ \rightarrow +V^-$$

$$I_C = \frac{(V^+ - V^-) - V_{EC}}{R_C + \frac{(1+\beta)}{\beta} R_E}$$
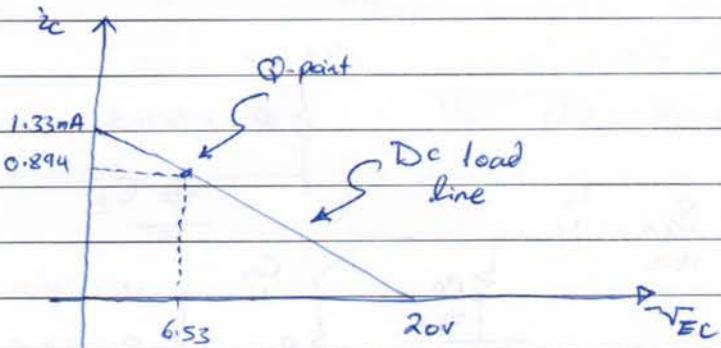
$$= \frac{R_C + \frac{(1+\beta)}{\beta} R_E}{R_C + (1+\beta) R_E}$$




Ac analysis:-

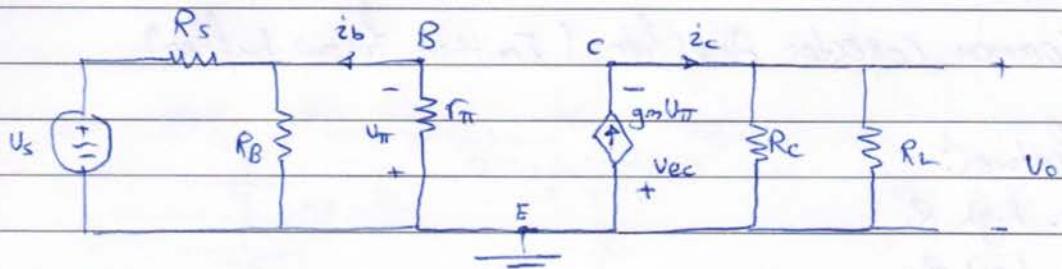

Ac Load Line:-

$$V_{EC} = -i_C (R_C \parallel R_L)$$
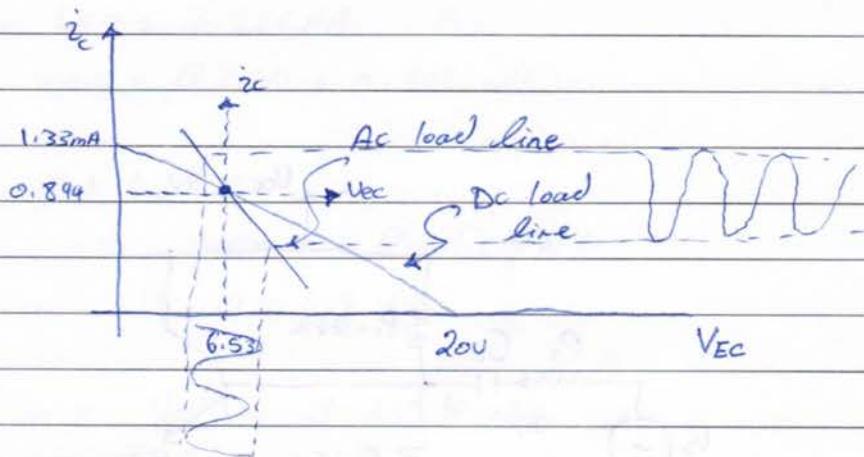
$$i_C = -\frac{1}{R_C \parallel R_L} V_{EC}$$



→ Ac load line helps in visualizing the relationship between the small signal response and the transistor characteristics.

lecture 9:

20/3/2014

## Common collector Amplifier (Emitter follow buffer)

features:-

1. High  $R_i$
2. Low  $R_o$
3.  $A_v \approx +1$
4.  $A_i = 1 + \beta \approx \beta$
5. it is used as a final stage in multi-stage amplifier.
6.  $R_1$  &  $R_2$  should be very large to take the advantage of high  $R_{ib}$

Ex:-

given :-


$$\beta = 100$$

$$V_A = 80 \text{ V}$$


find:-

$$AV = \frac{V_o}{V_s}$$

$$R_i, R_o, A_i = \frac{I_o}{I_i}$$

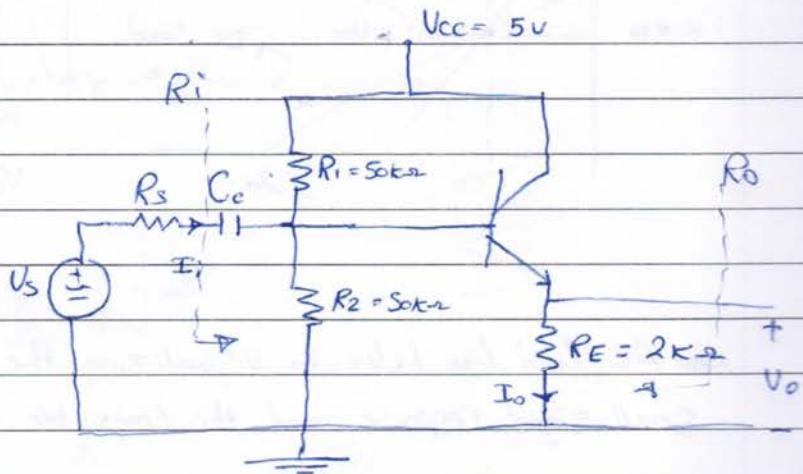

Dc analysis:-

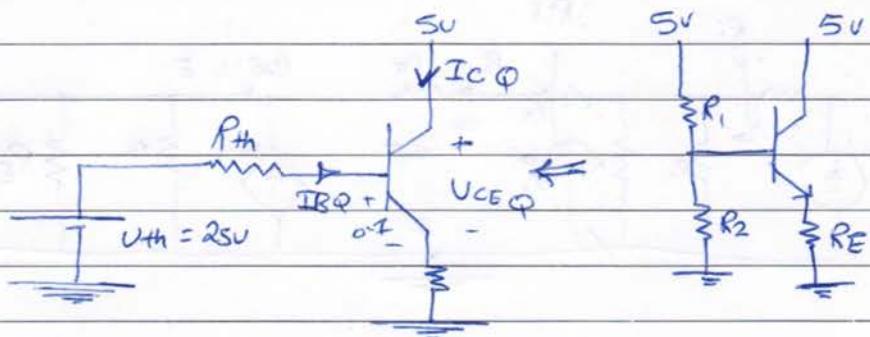

input loop:

$$-2.5 + I_{BQ} \cdot 2.5 + 0.7 + R_E (1 + \beta) I_{BQ} = 0$$

$$I_{BQ} = 7.929 \mu A$$

$$I_{CQ} = \beta I_{BQ} = 0.793 \text{ mA}$$

output loop:

$$-5 + V_{CEQ} + R_E I_{EQ} = 0$$


$$V_{CEQ} = 3.4 \text{ V}$$

$$V_T = \frac{U_T}{I_{BQ}} = 3.28 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = 30.5 \text{ mA/V}$$

$$r_o = \frac{U_A}{I_{CQ}} = 100 \text{ k}\Omega$$

Ac analysis :-

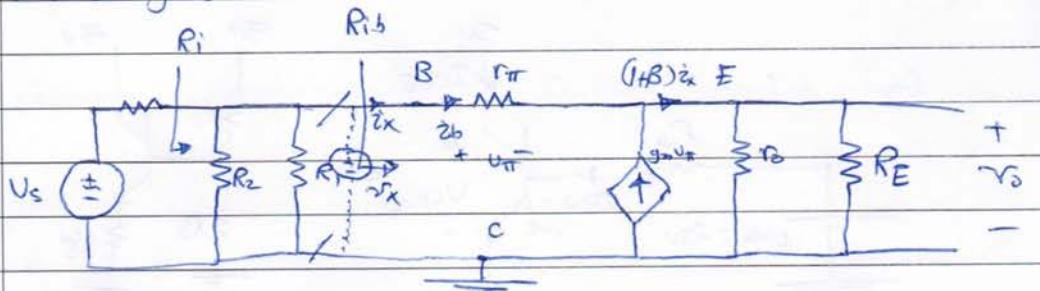

$$\Rightarrow R_i = R_1 \parallel R_2 \parallel R_{fb}$$

$$R_{fb} = \frac{V_x}{i_x}$$

$$-V_x + i_x r_{\pi} + (1+\beta)i_x (r_o \parallel R_E) = 0$$

$$\Rightarrow R_{fb} = \frac{V_x}{i_x} = r_{\pi} + (1+\beta)(r_o \parallel R_E)$$

$$= 201 \text{ k}\Omega$$

$$R_i = R_1 \parallel R_2 \parallel R_{fb} = 22 \cdot 2 \text{ k}\Omega \quad (\text{high value}) \text{ with respect to } R_s$$

$$\Rightarrow Av = \frac{V_o}{V_s}$$

Remove  $V_x$  & re-connect the lines back.

$$V_o = (1+\beta) i_b (r_o \parallel R_E) \quad \text{no(1)}$$

$$V_{in} = V_s \frac{R_i}{R_i + R_s}$$

$$i_b = \frac{V_{in}}{R_{fb}} \quad \text{no(2)}$$

$$Ar = \frac{r_o}{r_s} = \left( \frac{r_\pi + R_1 // R_2 // R_s}{1 + \beta} \right) // RE // r_o$$

$$= 0.962 \approx 1$$