

Solution second Exam.

HYVOS RATS

Q1 find f_T (unity Bandwidth) 60 dB

$$60 \text{ dB} = 20 \log_{10}(B)$$

~~$$B = 10^3$$~~
$$\Rightarrow B = 10^3$$

Figure (1)

$$f_T = B f_B = 10^3 \times 50 \text{ KHz} = 50 \text{ MHz}$$

Q2 $T(s) = K \frac{1}{1+s\tau}$


In figure (1) find The Transfer function

$$\Rightarrow \frac{10^3}{1+s4\mu\text{s}} = \frac{10^3}{1+s \frac{f}{f_{3dB}}} = \frac{10^3}{1+s \frac{f}{5 \times 10^4}}$$

Q3 if $B = 20 \text{ dB} \Rightarrow f_T = ??$

$$f_T = B f_B = \text{const.} = 50 \text{ MHz}$$

Q4

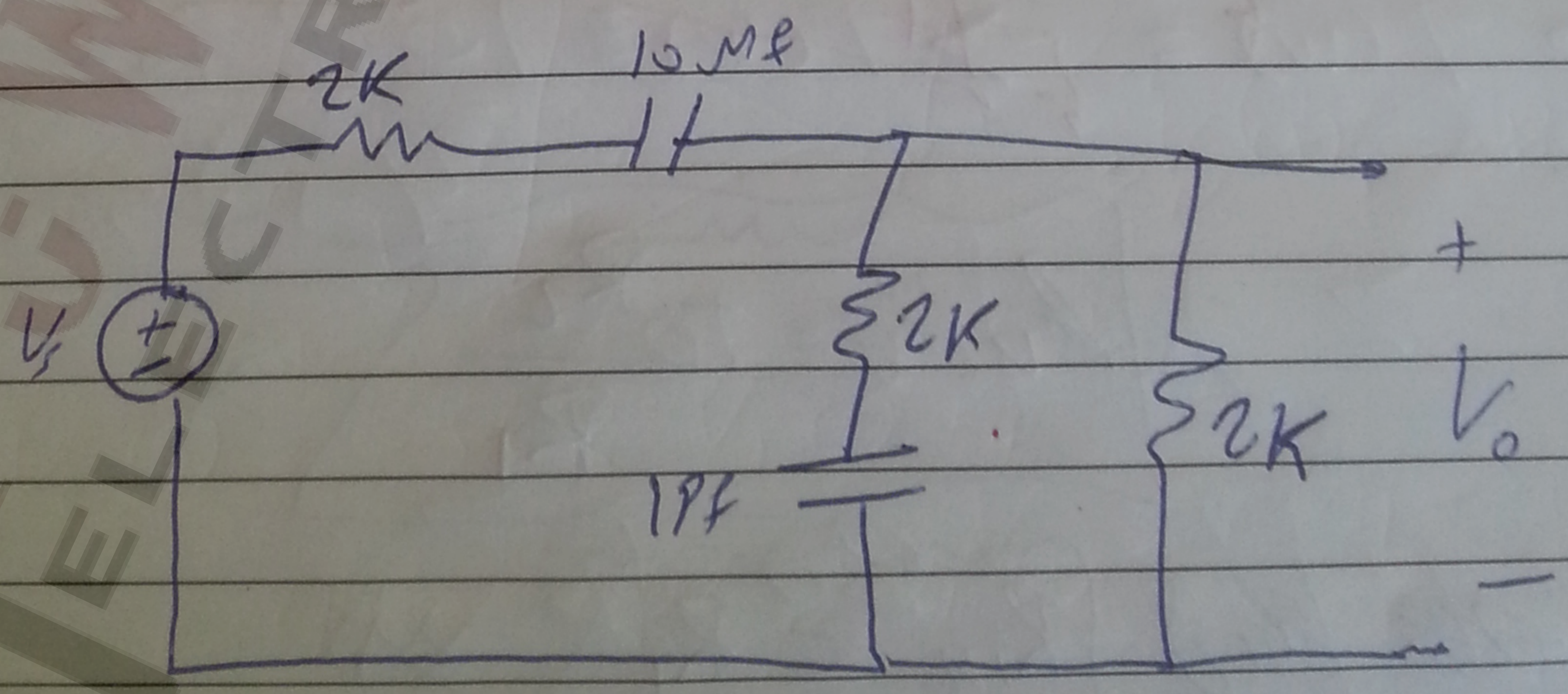


→ find f_L

$$f_c = \frac{1}{2\pi\tau} \Rightarrow \tau = R_{th} C$$

$$= 10 \times 10^{-6} (2+2) \times 10^3$$

$$\Rightarrow f_c = \frac{100}{8\pi} \text{ Hz}$$


Q6 $V_o = 9.5 \text{ V}$

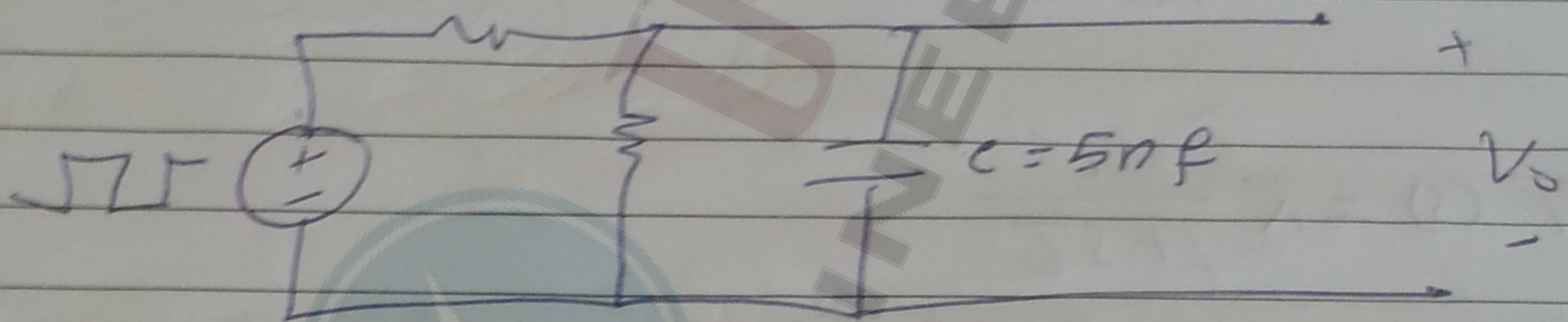

$f_s = ??$


$$\tau \leq \frac{1}{10 f_s}$$
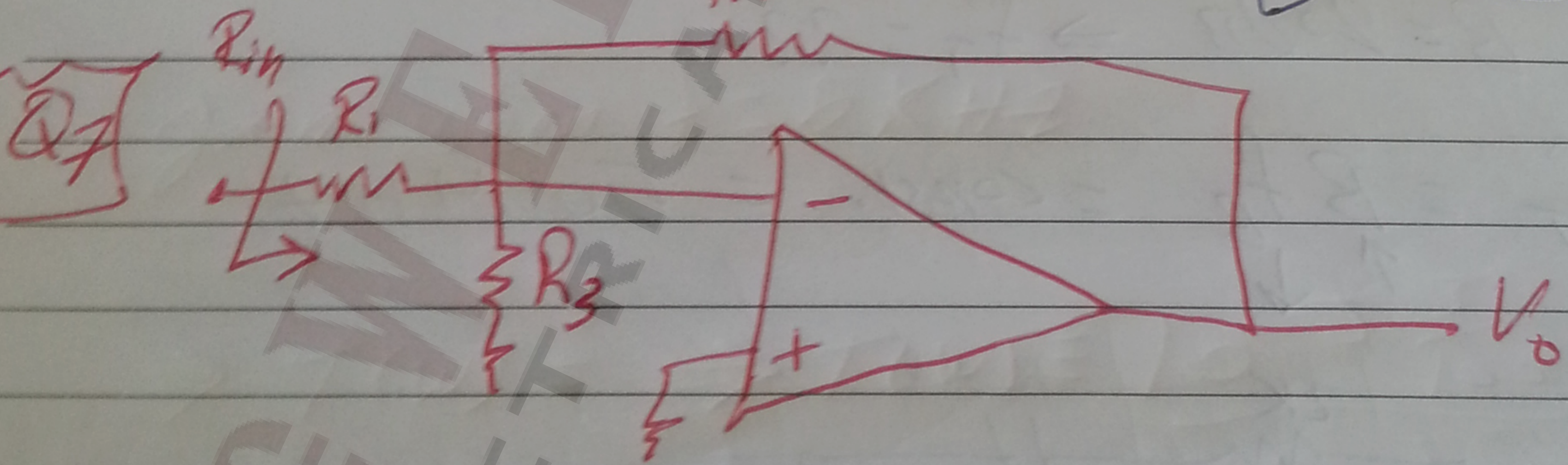
$$2\text{K} * 5 \times 10^{-9} \leq \frac{1}{10} \times \frac{1}{f_s} \Rightarrow f_s \leq 5 \text{ kHz}$$



$$A_v = -\frac{R_2}{R_1}$$


Q8 ~~and~~ $R_{in} = R_1$

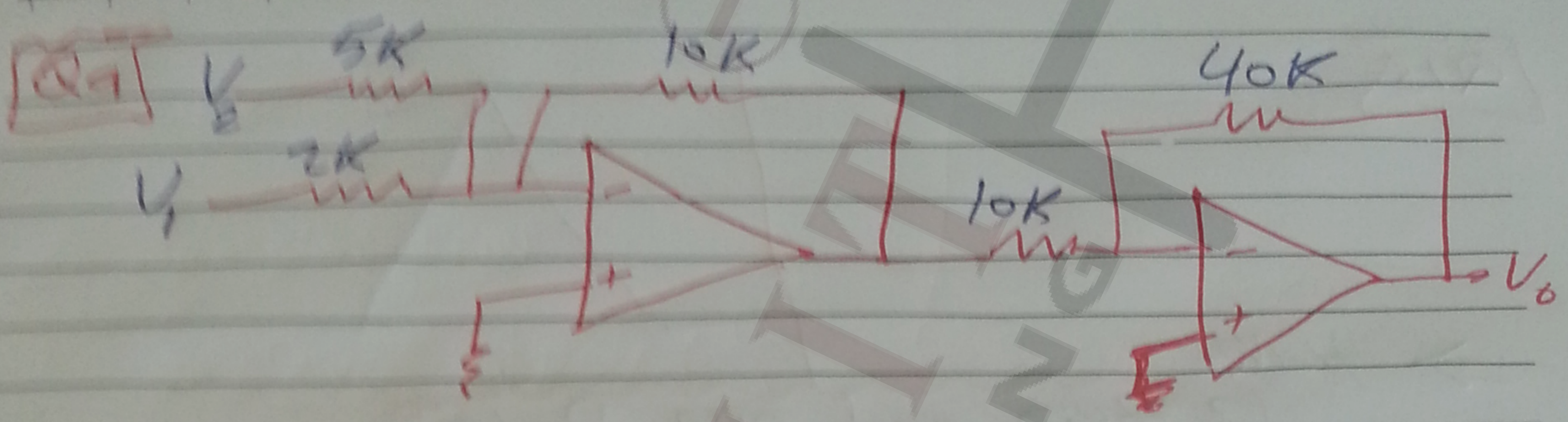

$$V_{out} = -5V_1 - 2V_2$$

$$V_o = -4(-5V_1 - 2V_2)$$


$$= 20V_1 + 8V_2 \quad \#$$

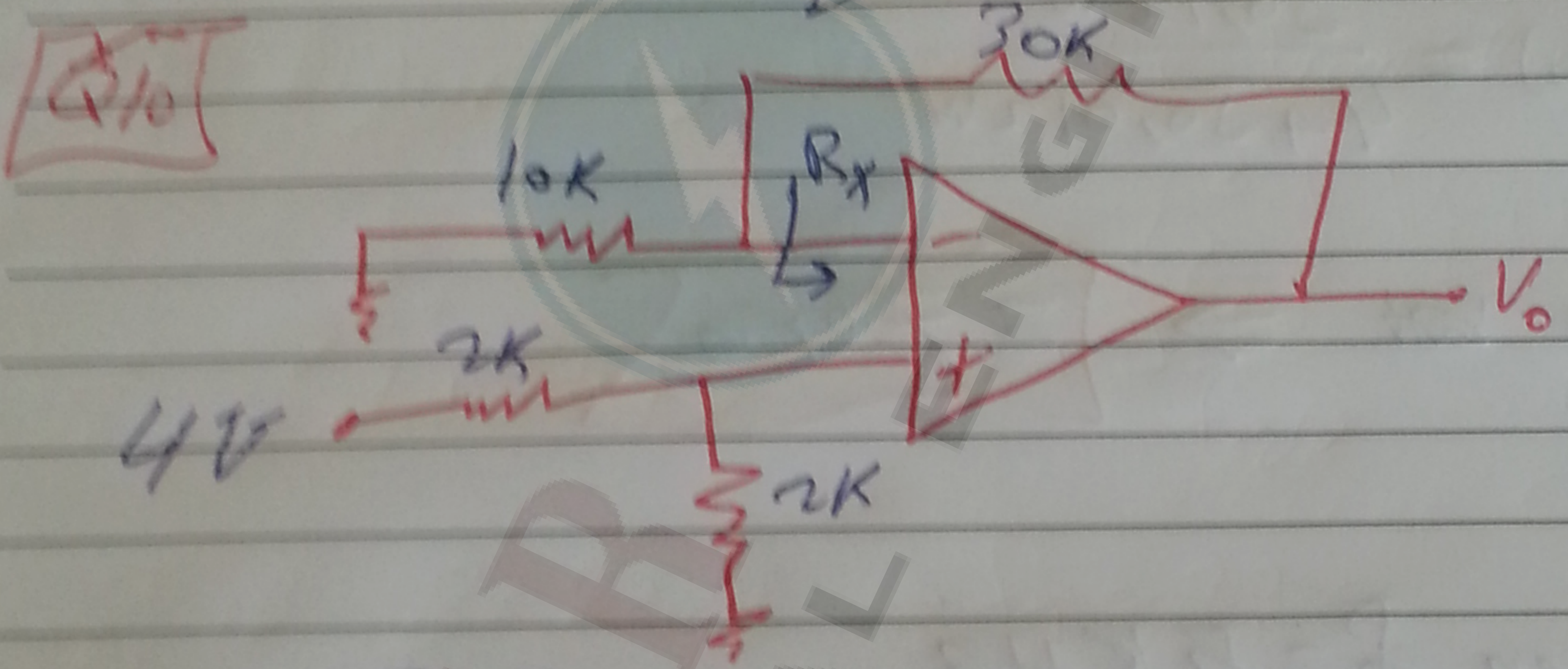

$$V_o = 8V \quad \#$$

Q11 $R_x = \infty$


Q12

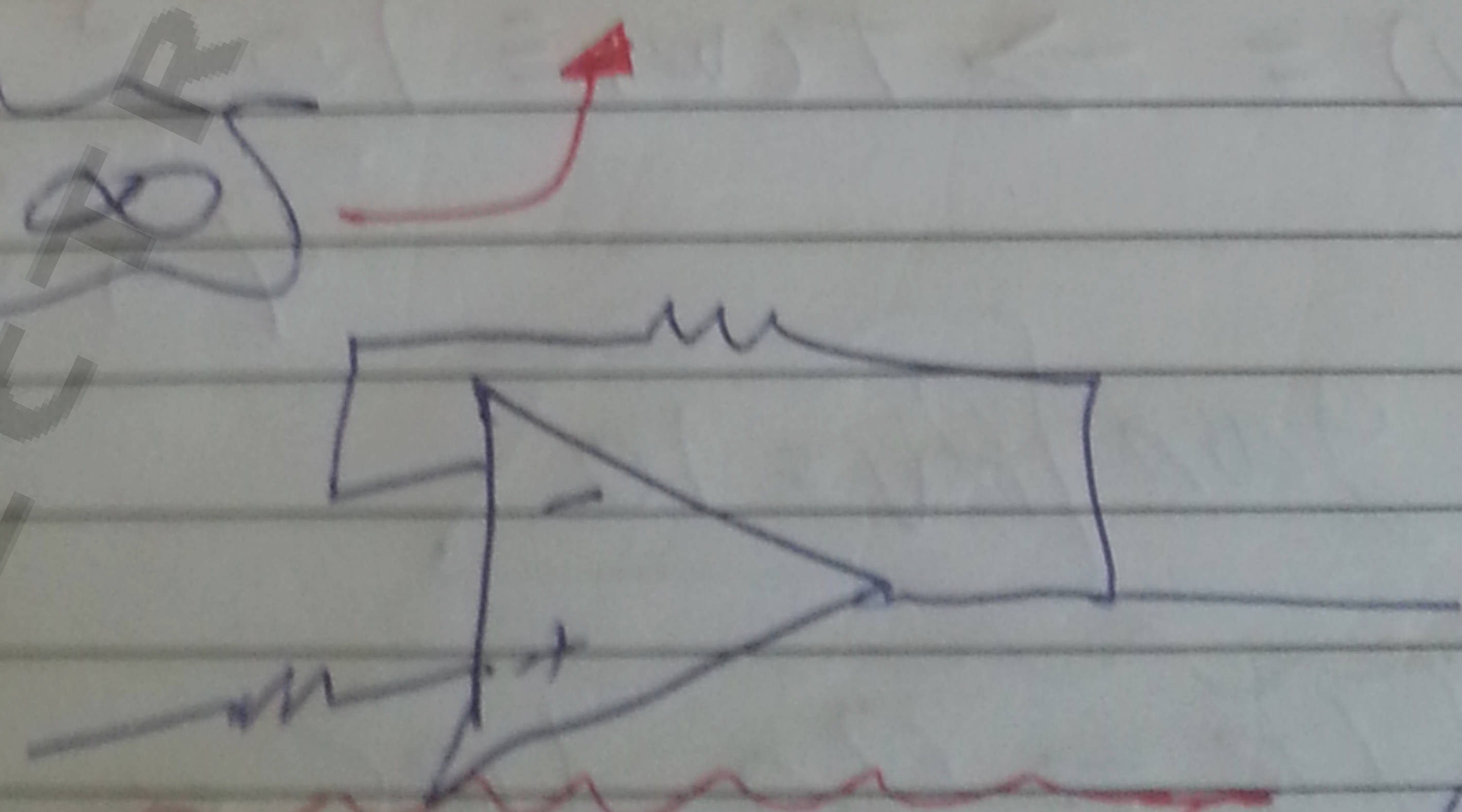

« Buffer » and $AV = 1$

ANALYSIS


Q9

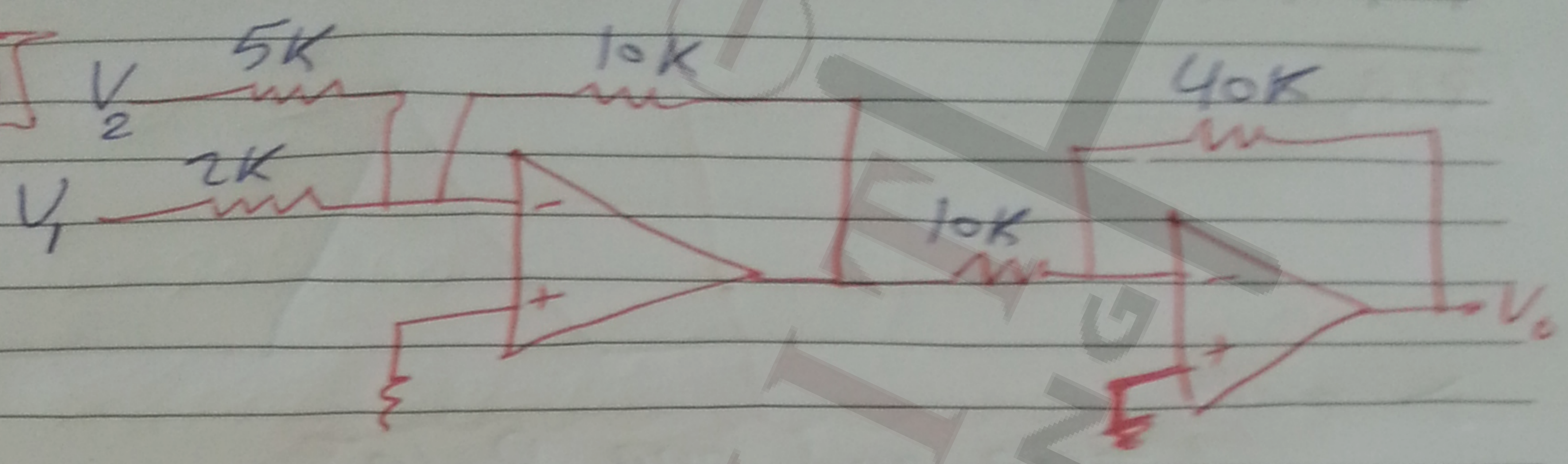

$$V_{out} = -5V_1 - 2V_2$$

$$V_o = 4(-5V_1 - 2V_2) = 20V_1 + 8V_2 \quad \#$$

Q10

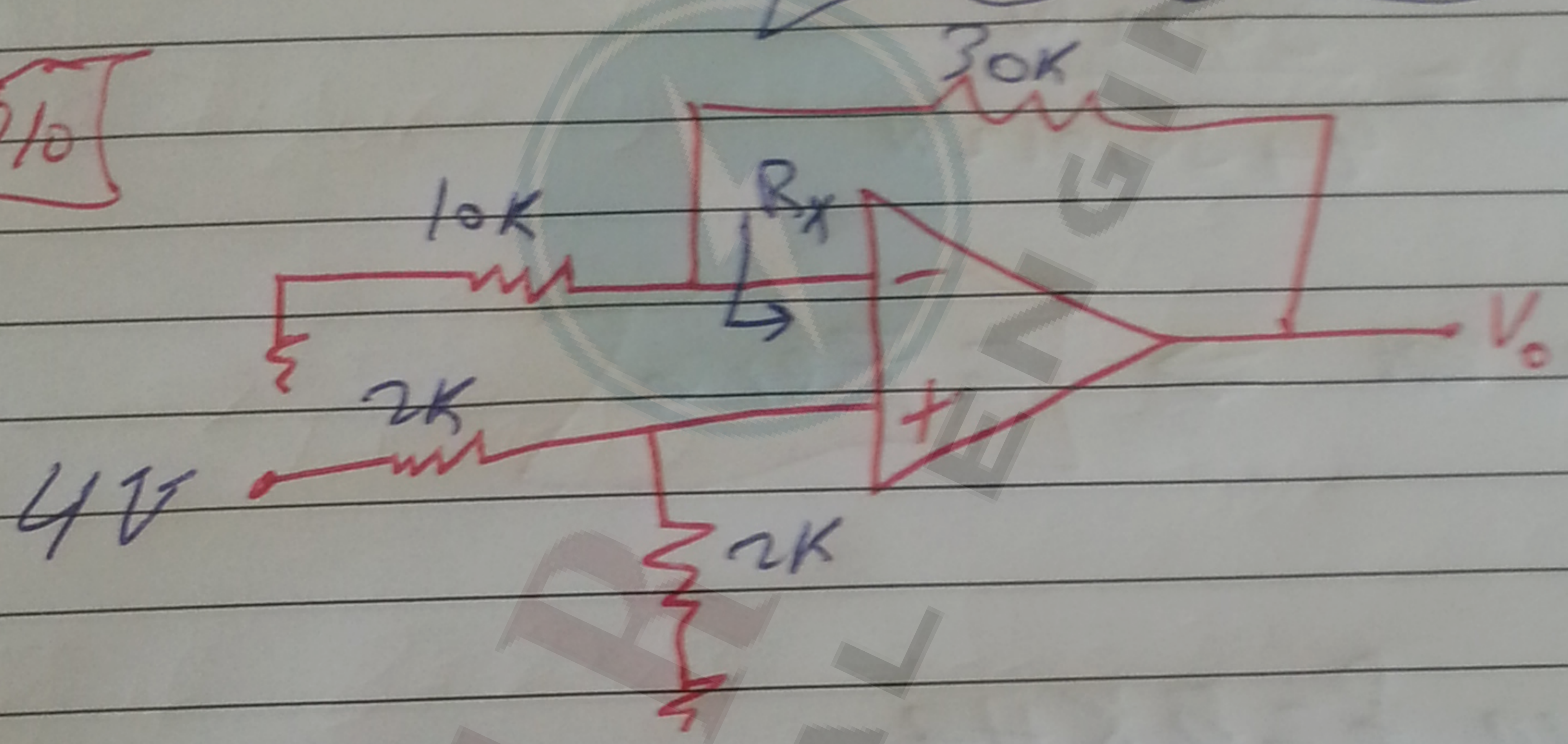


$$V_o = 8V \quad \#$$

Q11


$$R_x = \infty$$

12

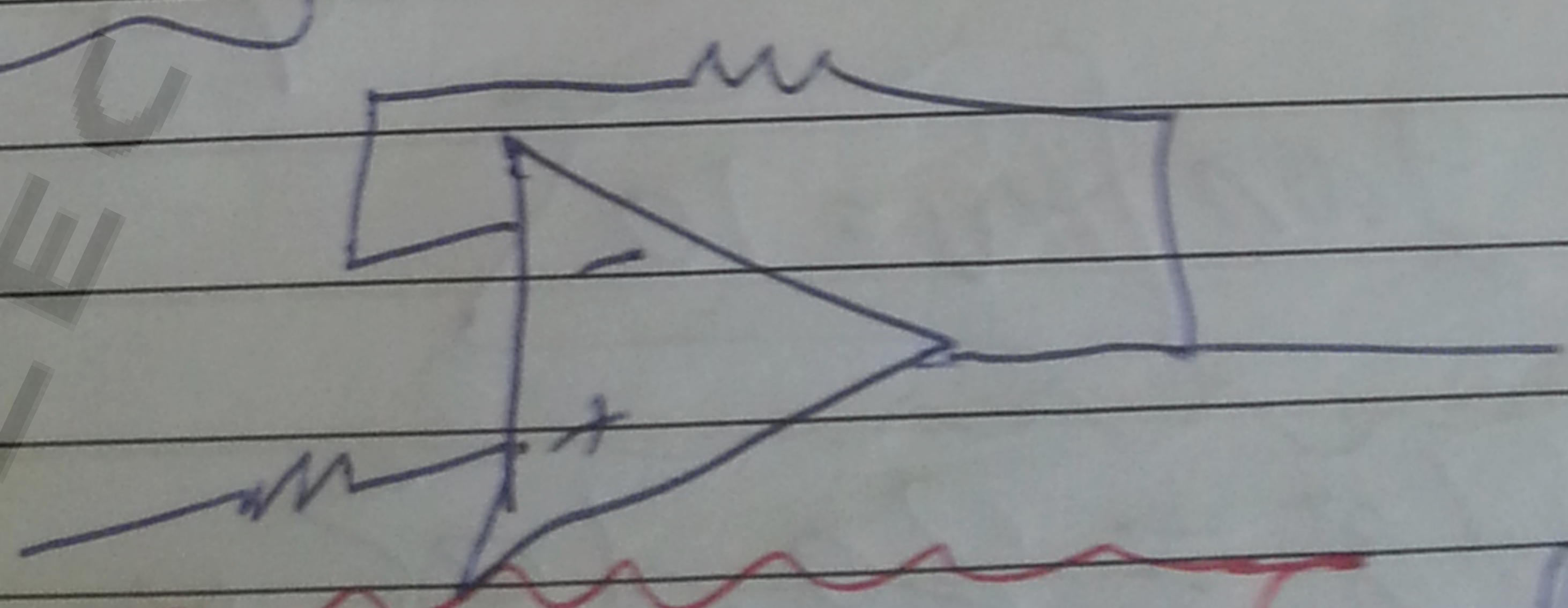

« Buffer » and $AV = 1$

Q13

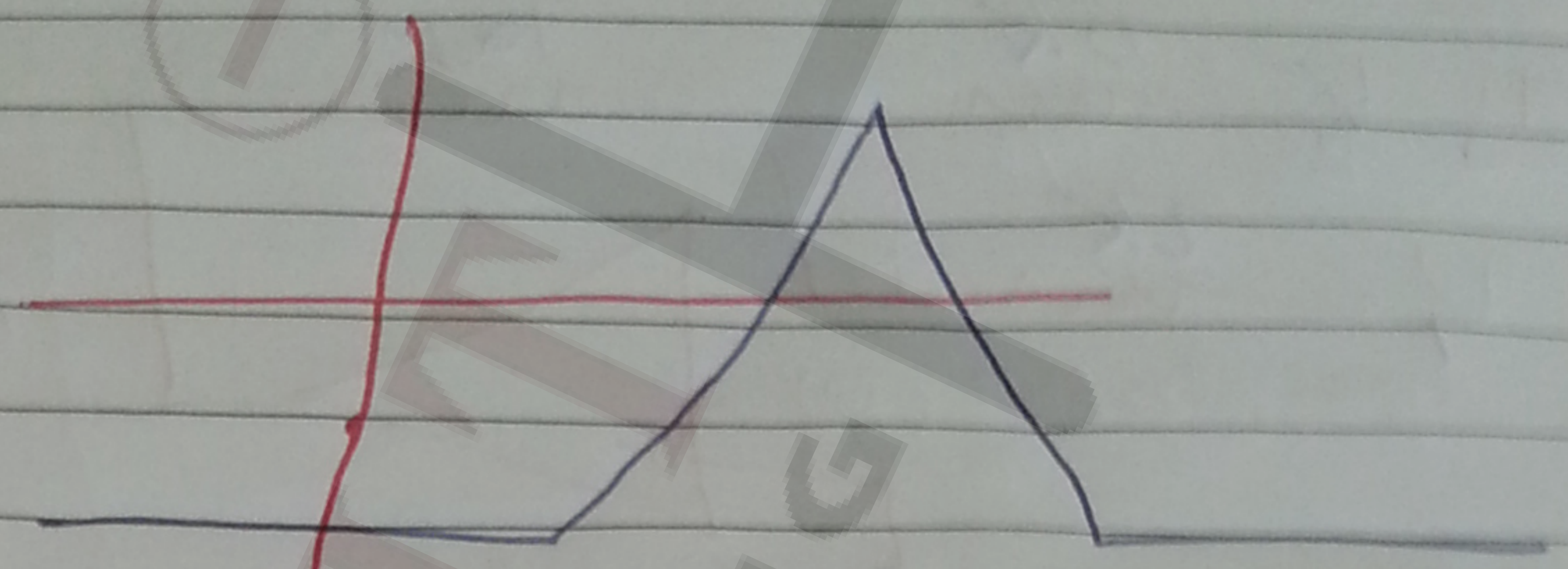

→ Have

2 Zero and one Pole

Q14

$$T = 35 \mu s$$

Q15

$$T(\omega) = \frac{50,12 \omega}{4 + j0,012 \omega}$$

DC gain ~~is~~ ⇒ = Zero

gain when $f = 5 \text{ kHz}$

$$\Rightarrow T(\omega) = \Rightarrow T(\omega) = \frac{10 \cdot j \frac{3}{100}}{4 + j \frac{3}{100}}$$

⇒ gain $A_v = 10$

gain in $dB = 20 \text{ dB}$ #