

Amplifiers

NoteBook

Dr: Ra'ed Al Zoubi


By: Rana Al Akhras




Tue

* Transistor: BJT & FET


- BJT: (C) collector

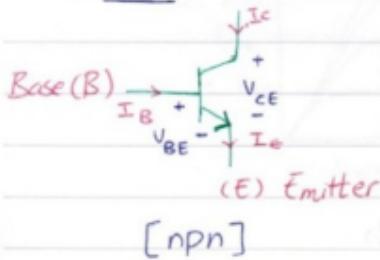

[npn]

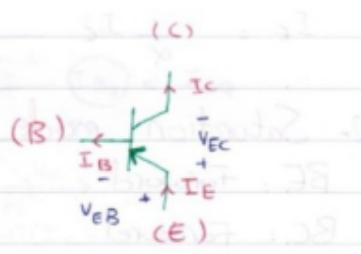

[pnp]

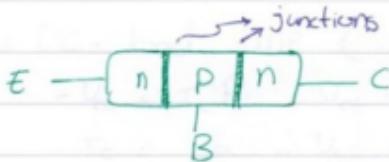

* Mode of operation for BJT:-

1. Forward-active mode (or active region)

BE: Forward-biased

BC: Reverse-biased

→ BJT is used as Amplifier.

$$\bullet V_{BE} = V_{BE(on)} = 0.7V$$

$$\bullet V_{CE} > V_{CE(sat)}, \text{ where } V_{CE(sat)} \approx 0.2V \text{ or } 0.3V$$

$\bullet I_C = \beta I_B$, β : Gain [unit less] → at a certain temperature, characteristic of the transistor

- $50 < \beta < 300$
- $I_C = (\alpha + \beta) I_B$
- $I_C = \frac{1}{\alpha} I_C$

2. Saturation mode :-

BE : Forward

BC : Forward

BJT is used as a switch.

- $V_{BE} = 0.7 V$
- $V_{CE} = V_{CE}(\text{sat})$
- $I_C < \beta I_B$

3. Inverse-active mode:

BE : reversed - biased

BC : forward - biased


4. Cutoff mode:

BE : reverse

BC : reverse

$$I_C = I_B = I_C = 0$$


18-2-2014 / Tue

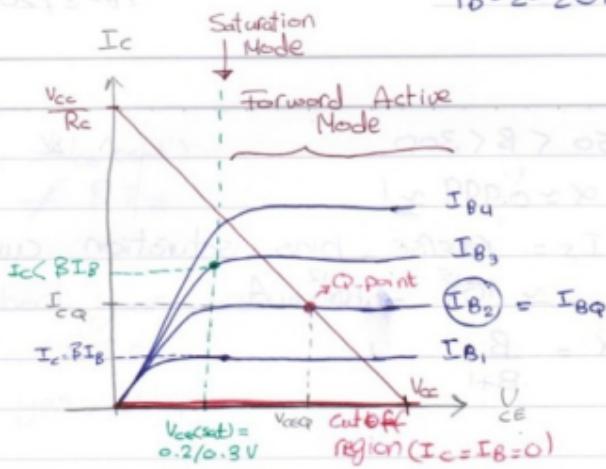

* DC- load line ($I_c \propto V_{ce}$)

$$-V_{ce} + I_c R_c + V_{ce} = 0$$
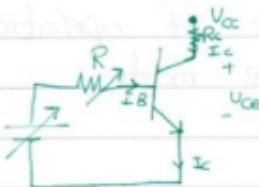
$$I_c = \frac{V_{ce}}{R_c} - \frac{V_{ce}}{R_c}$$



* V_T : Thermal voltage ($V_T = 0.026$) at room temperature 300K

- $50 \leq \beta \leq 300$
- $\alpha \approx 0.999 \approx 1$
- $I_s = \text{reverse-bias saturation current}$
 $\approx 10^{-15} - 10^{-12} \text{ A}$
- $\alpha = \frac{\beta}{\beta + 1}$

* DC analysis of BJT :-

- Finding the mode of operation.
- DC load line.
- Finding the relation between V_o & V_i .
- DC analysis of multi-stage circuit.

• Steps for finding the mode of operation.

① Assume Forward-active mode

$$\rightarrow V_{BE} = 0.7$$

$$\rightarrow I_C = \beta I_B$$

② Check your assumption

$$\rightarrow I_B > 0 \text{ and } V_{CE} > V_E (\text{sat}), \text{ if yes stop}$$

③ otherwise assume saturation mode

$$\rightarrow V_{BE} = 0.7$$

$$\rightarrow V_{CE} = V_{CE(\text{sat})}$$

$$I_C \neq \beta I_B$$

④ check your assumption

$$I_C < \beta I_B$$

if yes, stop

⑤ otherwise, cut off mode.

Ex:- consider the following cct:-

Given: $\beta = 100$, $V_{BE(on)} = 0.7 \text{ V}$

$V_{CE(\text{sat})} = 0.2 \text{ V}$

1. Find the mode of operation

- assume F.A.M. $\rightarrow I_C < 30 \text{ mA}$

$$V_{BE} = 0.7$$

$$I_C = \beta I_B$$

\rightarrow input loop:

$$-8 + 220 I_B + 0.7 = 0$$

$$I_B = \frac{-8 - 0.7}{220} = 33.2 \text{ mA} > 0 \text{ V}$$

$$I_C = \beta I_B = 100 * 33.2 \text{ mA} = 3.32 \text{ mA}$$

\rightarrow output loop:

$$-10 + 4 * 3.32 + V_{CE} = 0$$

$$V_{CE} = 10 - 4 * 3.32 = -3.28 \text{ V} > V_{CE(\text{sat})}$$


No, incorrect assumption.

- assume saturation mode

$$V_{BE} = 0.7 \text{ V}$$

$$V_{CE} = V_{CE(\text{sat})} = 0.2 \text{ V}$$

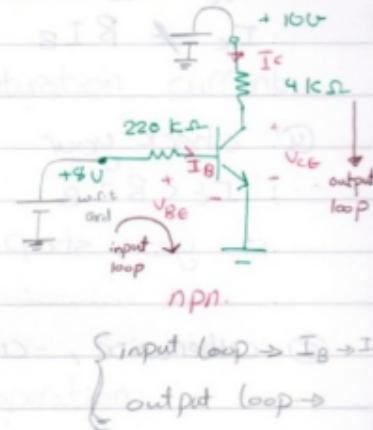\rightarrow input loop $\rightarrow I_B = 33.2 \text{ mA}$



→ output loop:-

$$-10 + 4 I_c + 0.2 = 0$$

$$I_c = 2.45 \text{ mA}$$

check : $I_c < \beta I_B$

$$2.45 < 3.32 \quad \checkmark$$

yes, saturation mode

2. Find Q-point values:-

Q-point values: $I_{BQ} = 3.32 \text{ mA}$


$$I_{CQ} = 2.45 \text{ mA}$$

$$V_{CEQ} = 0.2 \text{ V}$$

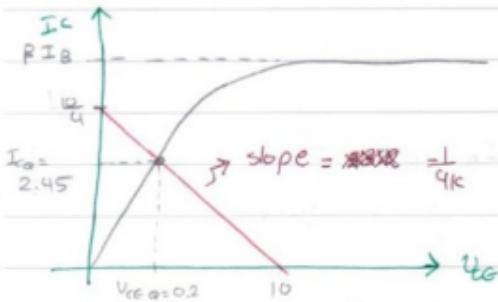3. Find and draw the DC load line:-

$$-10 + 4 I_c + V_{CE} = 0$$

$$I_c = \frac{10 - V_{CE}}{4} \quad [\text{mA}] \rightarrow \text{DC-load line.}$$



$$I_B = 3.32 \text{ mA}$$

* we can't use it
as amplifier.

Ex Draw the voltage transfer curves ($V_o \propto V_i$) for the following cct :-

Given:

$$V_{BE(\text{ON})} = 0.7 \text{ V}$$

$$V_{CE(\text{sat})} = 0.2 \text{ V}$$

$$\beta = 120$$

• cutoff :-

$$I_C = I_B = I_c = 0$$

$$\rightarrow V_o = 5 \text{ V} \quad (\text{V}_i \text{ ڈیجیٹیل ہے})$$

• saturation :-

$$V_{CE(\text{sat})} = 0.2 \text{ V}$$

$$\rightarrow V_o = 0.2 \text{ V}$$

• forward active mode :-


$$V_{BE} = 0.7$$

$$I_C = \beta I_B$$

$$\rightarrow \text{input loop: } -V_i + 150 I_B + 0.7 = 0$$

$$I_B = \frac{V_i - 0.7}{150}$$
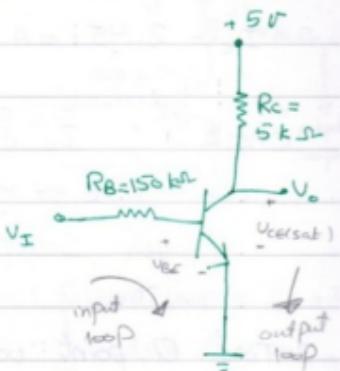
$$\rightarrow \text{output loop: } -5 + 5 I_C + V_o = 0$$




$$I_C = \frac{5 - U_o}{5}$$

$$\Rightarrow I_C = \beta I_B$$

$$\frac{5 - U_o}{5} = 120 \left(\frac{V_I - 0.7}{150} \right)$$

$$U_o = 5 - 120 \frac{R_c}{R_B} V_I + \frac{120 R_c + 0.7}{R_B}$$
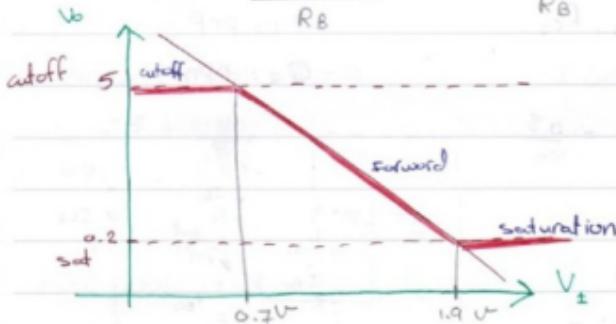
$$V_o = 5 + \frac{120 R_c + 0.7}{R_B} - \frac{120 R_c}{R_B} V_I \quad \text{"negative slope"}$$



when pnp used
slope: β vs α

1

- Example :- - input loop then output loop
with load in coils $\approx 1\Omega$


Given:-

$$\beta = 100 \text{ for both } Q_1 \text{ & } Q_2$$

$$I_{C1} = I_{C2} = 0.8 \text{ mA}$$

$$V_{EB1} = V_{BE2} = 0.7 \text{ V}$$

$$V_{EC1} = 3.5 \text{ V}, V_{EE2} = 4 \text{ V} \Rightarrow Q_1 \text{ & } Q_2 \text{ are in F.A.N}$$

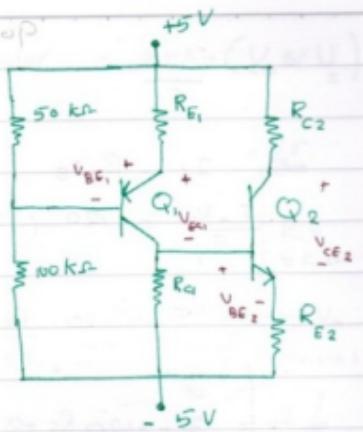
Find R_E , R_B , R_{E2} , R_C Q_1 : pnp Q_2 : npn

$$\Rightarrow I_{B1} = I_{B2} = \frac{I_{C1}}{\beta} = \frac{0.8}{100}$$



$$I_{B1,2} = 8 \text{ mA}$$

$$\Rightarrow I_{E1} = I_{E2} = (1 + \beta) I_{B1}$$

$$I_{E1,2} = 0.808 \text{ mA}$$

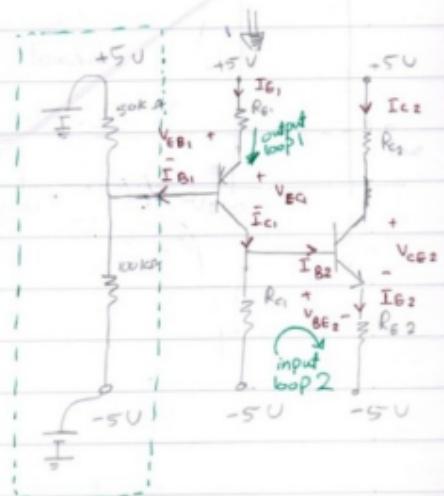


2

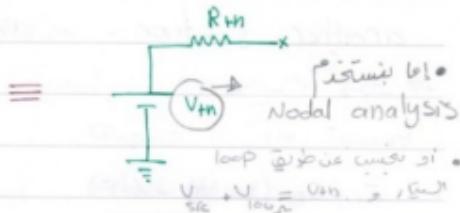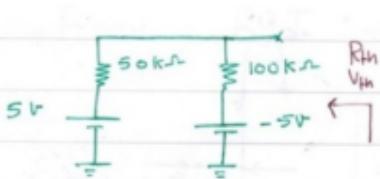

$$R_{Th} = 50 \parallel 100 = \frac{5000}{150} = 33.3 \text{ k}\Omega$$

$$-5 + 50I + 100I + -5 = 0$$

$$I = \frac{10}{150} \text{ mA}$$

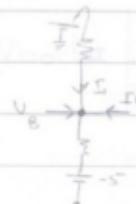

$$\rightarrow -V_{Th} + I(100) - 5 = 0$$

$$V_{Th} = -5 + \frac{1000}{150}$$

لـ V_{Th} ، جذر جـ



$$\text{input loop 1} : -5 + \tilde{I}_{E1} R_{E1} + 0.7 + \tilde{I}_{B1} R_{Th} + V_{Th} = 0 \Rightarrow R_{E1} = 2.9 \text{ k}\Omega$$

$$\text{output loop 1} : -5 + \tilde{I}_{E1} \tilde{R}_{E1} + \tilde{V}_{CE1} + R_{C1} (\tilde{I}_{C1} - \tilde{I}_{B2}) - 5 = 0 \Rightarrow R_{C1} = 52.5 \text{ k}\Omega$$

$$\text{input loop 2} : -(5) - R_{C1} (\tilde{I}_{C1} - \tilde{I}_{B2}) + V_{BE2} + \tilde{I}_{E2} R_{E2} - 5 = 0 \Rightarrow R_{E2} = 4.25 \text{ k}\Omega$$

$$\text{output loop 2} : -5 + I_C R_{C2} + V_{CE2} + R_{E2} \tilde{I}_{E2} - 5 = 0 \Rightarrow R_{C2} = 3.215 \text{ k}\Omega$$

B


another solution:- "without V_{th} "

$$I_1 = \frac{5 - V_B}{50}$$

$$I_1 + I_{B1} = \frac{V_B - (-5)}{100}$$

$$\frac{V - V_B}{50} + I_{B1} = \frac{V_B + 5}{100}$$

$$\rightarrow V_B = \dots$$

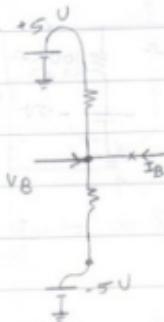

input loop:-


$$-5 + I_E R_{E1} + V_{EB} + V_B = 0$$

out. HOS → control the
Biasing → control the Q-point position

25-2/2014 Tue.

[4]

• Basic BJT Amplifier:-

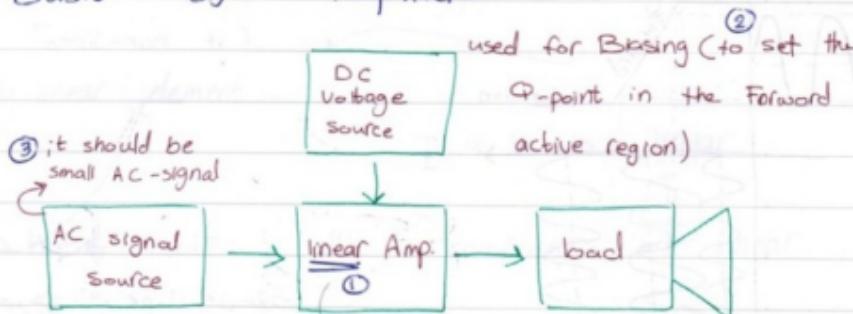


e.g.: microphone
CD player
CD writer

we can apply superposition.

→ DC-analysis \Rightarrow AC-analysis \Rightarrow (kill to AC-sigs. جاء) ونفس المنهج المكمل

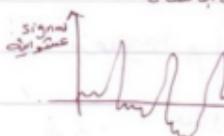
random \rightarrow Design as a fin. وتأسیس علی الترتیب Random signal \rightarrow sin $-$ + sin $+$ (b) (عائمه)



linear amp \rightarrow output = const + Input


O/I علی الترتیب
Input = const

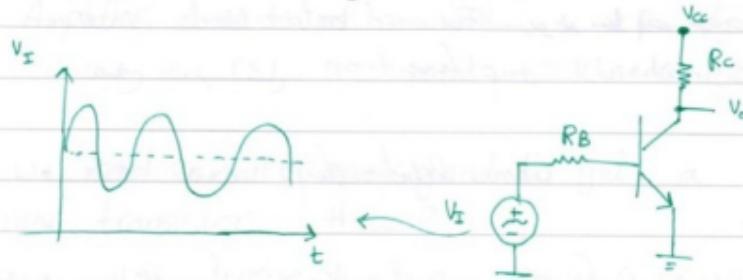1. The transistor in Amplifier circuit should be in the forward-active Region. why?!




$$V_I = 3 + 2 \sin \omega t$$


(5)

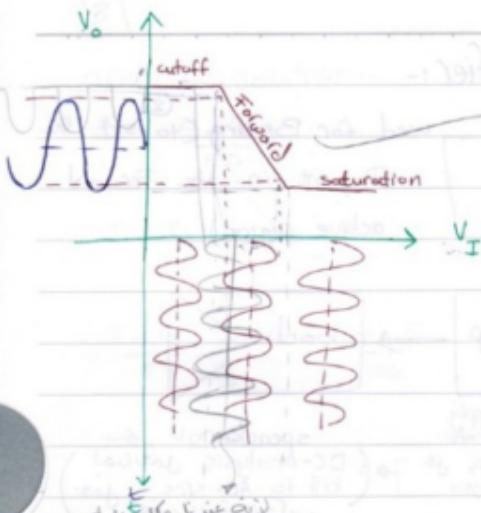

if it non-linear

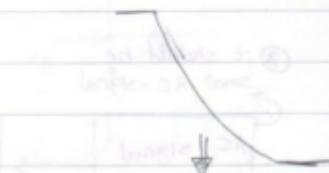

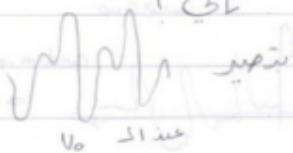عمره هي بيغير عباره من
ومن يجيء الماسن بيتكلم بختار
نادي !



ذات عيار عالي اذ
عيار من اذ
اعطى من عيار
الحال عالي
عمره اذ
عمره اذ

in ad blanda tenuis vides a restant ut al


• في حالة الـ saturation يكون يكون يكون يكون

و ويزيد على ذلك Forward active Node

اف في signal لا amplification يحصل بقدر اعلى

• Linear Relationship تكون تكون تكون .

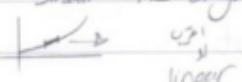Linear relationship تكون تكون تكون small - AC - signal يحيى .




1

2. we need a linear amplifier, why?


\Rightarrow linear element :- m , $+t$, $-m$
 $I \propto V$ is linear.

\Rightarrow linear circuit :- all its components are linear.

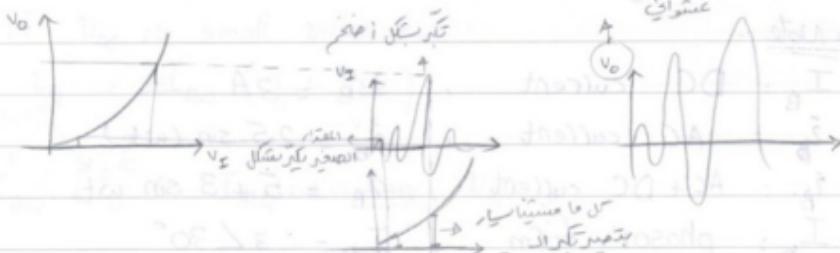\Rightarrow linear Amplifier :- means that the Relation between V_I and V_o is linear. "to get linear amplifier we need all its components to be linear."



- Amplifier consists of : m , $+t$,


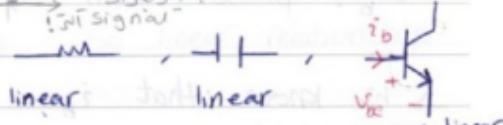


- 3. we need small AC-signal to get a linear transistor. How?



(2)

* Graphically :-

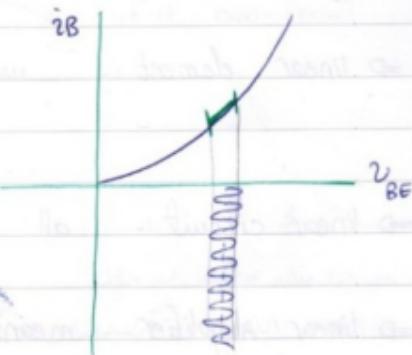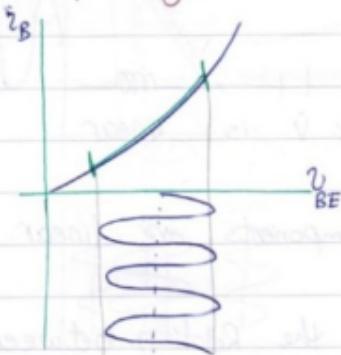

* Mathematically :-

* Note :-

$$I_B: \text{DC current}, \quad I_B = 3A$$

$$i_B: \text{AC current}, \quad i_B = 2.5 \sin(\omega t)$$

$$i_B: \text{AC+DC current}, \quad i_B = 5 + 3 \sin \omega t$$

$$I_B: \text{phasor form}, \quad I_B = 3\angle 30^\circ$$

Reverse saturation current i_{BQ}

$$\rightarrow \text{We know that } i_B = \frac{I_s \exp\left(\frac{V_{BE}}{V_T}\right)}{1+\beta} = \frac{I_s}{1+\beta} \exp\left(\frac{V_{BEQ} + V_{be}}{V_T}\right)$$

$$\rightarrow i_B = \left[\frac{I_s}{1+\beta} \exp\left(\frac{V_{BEQ}}{V_T}\right) \right] \cdot \exp\left(\frac{V_{be}}{V_T}\right)$$

(3)

$$\therefore i_B = I_{BQ} \cdot \exp\left(\frac{V_{be}}{V_T}\right)$$

Note:-

$$\text{Taylor Series: } e^{\theta} = \frac{\theta}{0!} + \frac{\theta^1}{1!} + \frac{\theta^2}{2!} + \frac{\theta^3}{3!} + \dots$$

$$\text{if } \theta \ll 1 \Rightarrow e^{\theta} \approx 1 + \theta \quad \begin{matrix} \text{linear relationship} \\ \text{exponential relationship} \end{matrix}$$

$$\Rightarrow e^{\frac{V_{be}}{V_T}} \approx 1 + \frac{V_{be}}{V_T} \quad \text{if } \frac{V_{be}}{V_T} \ll 1$$

$$V_{be} \ll V_T \quad 0.026$$


if V_{be} is small value :-

$$i_B = I_{BQ} \left(1 + \frac{V_{be}}{V_T} \right)$$

$$I_{BQ} + i_b \approx I_{BQ} + \frac{I_{BQ}}{V_T} V_{be}$$

$$i_b = \frac{I_{BQ}}{V_T} V_{be} \quad \Rightarrow \text{So linear relationship}$$

[Const]


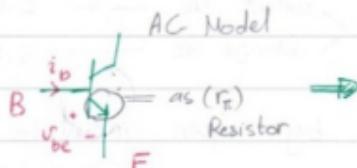


→ transistor JFET
linear circuit

∴ small signal Hybrid - π eqivalent cct.



[4]

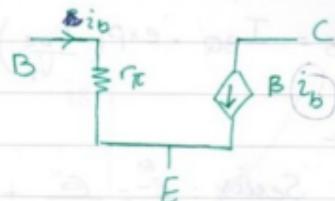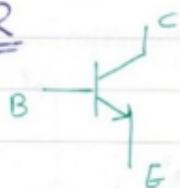OR

$$\cdot r_{\pi} = \frac{V_T}{I_{BQ}} \quad \text{"diffusion resistance"} \quad [\Omega]$$

$$\cdot g_m = \frac{I_{CQ}}{V_T} \quad \text{"transconductance"} \quad [A/V] \quad [\sim]$$

$$\cdot r_{\pi} \times g_m = B$$

* procedure: DC-analysis then AC-analysis *

H-parameter Model: $\begin{pmatrix} A & B \\ C & D \end{pmatrix}$

* General steps to Solve an Amplifier circuit :-

① DC-analysis:-

- Draw DC-equivalent cct

- kill all AC-sources current src \rightarrow o.c
voltage src \rightarrow s.c

- replace all capacitors by open circuit bal. w.r.t. m.s.

- keep all DC-sources l.e. w.r.t. S.C. \Rightarrow

- then find I_{BQ} , I_{CQ} , V_{CEQ}



(2) AC-analysis:-

- Draw the AC-equivalent ckt..
- Replace the transistor by the Hybrid- π equivalent
- Kill all DC-sources
- Replace all capacitor by short-circuit

• Find voltage gain $A_v = \frac{V_o}{V_i}$

$i_b, i_c, V_{cc}, R_i, R_o$

4-then by using super position:-

find result = AC + DC

$$i_B = i_b + I_{BQ}$$

* Ex 6.1

$$\beta = 100, V_{BE(\text{ON})} = 0.7 \text{ V}$$

Find the voltage gain

$$A_v = \frac{V_o}{V_s}$$

$$V_s = 0.25 \sin \omega t$$

• DC-analysis :-



→ DC equivalent circuit :-

- input loop :-

$$-1.2 + I_B (50) + 0.7 = 0$$

$$I_{BQ} = 10 \text{ mA}$$

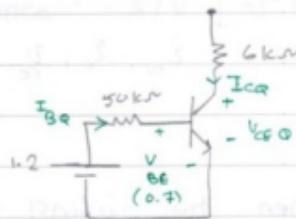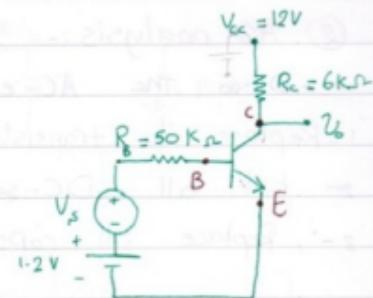
$$\therefore I_{cQ} = \beta I_{BQ} = 1 \text{ mA.}$$



• AC-analysis :-

→ AC-equivalent circuit :-

$$A_v = \frac{V_o}{V_s}$$

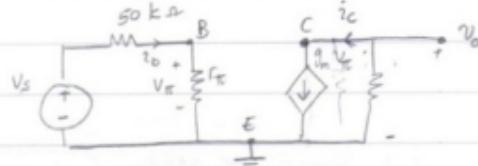

$$\rightarrow V_o = -g_m V_{be} R_C \rightarrow [1]$$

$$V_{be} = V_s \frac{r_\pi}{r_\pi + R_B} \rightarrow [2]$$

Sub (2) in (1):

$$v_o = -g_m R_C + \frac{v_s r_\pi}{r_\pi + R_B}$$

$$\therefore A_v = \frac{v_o}{v_s} = -\frac{g_m R_C r_\pi}{r_\pi + R_B}$$

$$\cdot r_\pi = \frac{V_T}{I_{BQ}} = \frac{0.026}{10 \times 10^{-6}} = 2.6 \text{ k}\Omega$$

$$\rightarrow g_m = \frac{I_{CQ}}{V_T} = 38.5 \text{ mA/V}$$

$$A_v = -11.4$$

-ve sign: phase shift = 180° between v_s and v_o

Find and Draw i_B^1, i_C, v_{CE} if $v_s = 0.25 \sin \omega t$
from AC-cct

$$i_B^1 = i_b + I_{BQ}$$

$$i_B^1 = \frac{v_s}{50 + r_E} + 10 \text{ mA}$$

$$i_B^1 = \frac{0.25 \sin \omega t}{50 + 2.6} + 10 \text{ mA}$$

$$i_B^1 = 4.75 \sin \omega t \text{ mA} + 10 \text{ mA}$$

$$\dot{i}_c = \dot{i}_e + I_{cq}$$

$$\dot{i}_c = \beta i_b + I_{cq}$$


$$i_c = 0.475 \sin \omega t + 1 \text{ mA}$$

$$V_{ce} = V_{ee} + V_{ceq}$$

$$V_{ce} = -i_c R_c + 12 - I_{cq} \times 6$$

$$V_{ce} = -2.85 \sin \omega t + 6 \text{ V}$$




where $V_{ce} = V_0$

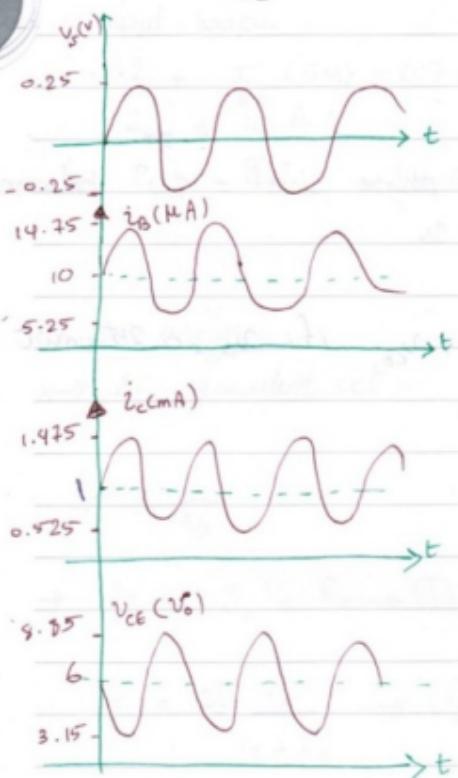

Because there's different units

- * Hybrid π - equivalent model including the Early Effect:

Early Effect:-

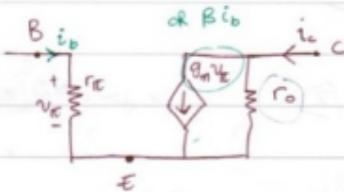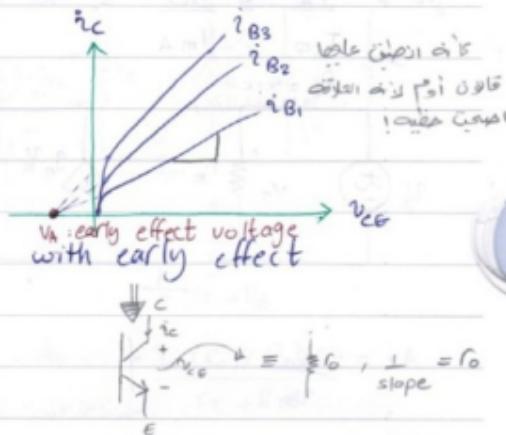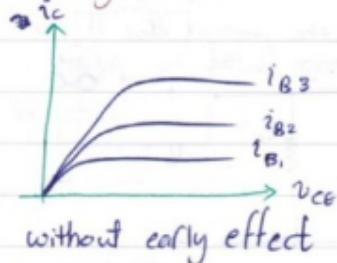

→ the AC-equivalent with early effect.

- * early effect $\Rightarrow r_o$ parallel to

$$r_o = \frac{V_A}{I_{CQ}}$$

- * the early effect reduce the gain voltage.


Ex :- consider the last example:-

Find $A_v = \frac{V_o}{V_I}$, if $V_A = 50V$.

$$r_0 = \frac{V_A}{I_{cq}} = \frac{50}{1mA} = 50k\Omega$$

I_{cq} $I_m A$

$$R_B = 50k\Omega$$

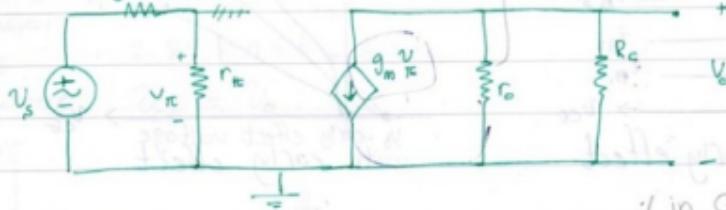

the typical for it
high value to assume
O.C.

(in General)

$$A_v = \frac{V_o}{V_s}$$

early effect

reduce / decrease the

$$V_o = -g_m V_{BE} (R_C // r_0) \quad \dots \text{ (1)}$$

Gain

$$V_{BE} = V_s - \frac{r_\pi}{r_\pi + R_B}$$

$$\dots \text{ (2)}$$

* for early effect

Sub (2) in (1).

$$V_o = -g_m (R_C // r_0) V_s \frac{r_\pi}{r_\pi + R_B}$$

$$A_v = -g_m (R_C // r_0) \frac{r_\pi}{r_\pi + R_B}$$


$A_v = -10 \cdot 2$ The early effect reduces the Gain.

npn \rightarrow pnp : Biasing
 - Alternating voltage V_{BE} is applied to the base-emitter junction.
 - The collector current i_C is controlled by the collector voltage $-V_{CC}$.

4-3-2014 Tue

* PnP -transistor :-

Accet (conf) is early effect

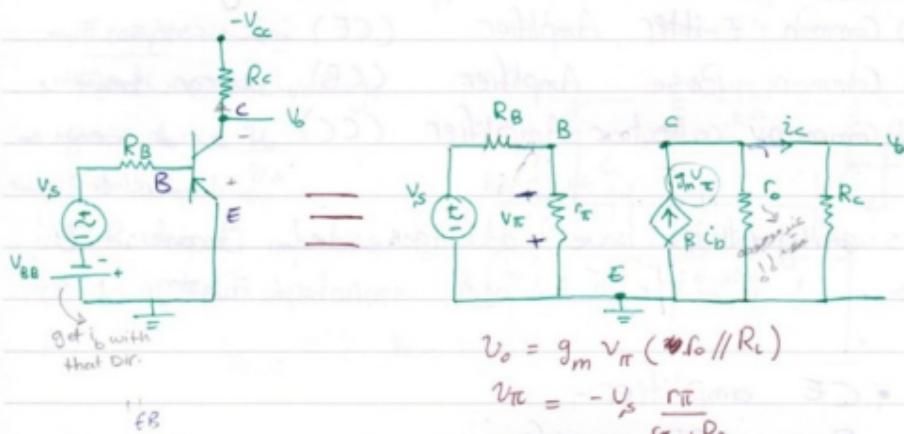


Same as npn

$$\leftarrow A_v = -g_m (r_o \parallel R_C) r_E$$

use the Both input is positive, i.e., $v_s > 0$

* Note *

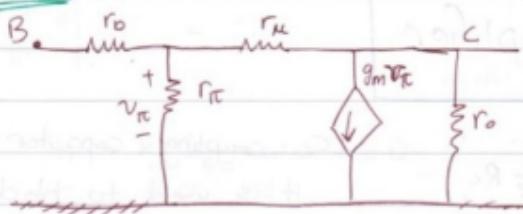

$r_B \approx 0 \rightarrow$ very small value $\rightarrow S.C$

$r_{RE} \approx \infty \rightarrow$ very high value $\rightarrow O.S$

we can negligible if.

* Basic Transistor Amplifier configuration:-

- ① Common Emitter Amplifier (CE) متوافق مع المعايير
- ② Common Base Amplifier (CB) متوافق مع المعايير
- ③ Common collector Amplifier (CC) متوافق مع المعايير


this configurations have advantages and Disadvantages

→ ! التقطع متعدد (multistage)

• CE amplifier:-

- 1 - Basic CE amplifier
- 2 - Basic CE amplifier with Emitter resistor
- 3 - Basic CE amplifier with Emitter resistor and By-pass capacitor.
- 4 - Advanced CE amplifier

1. Basic CE Amplifier

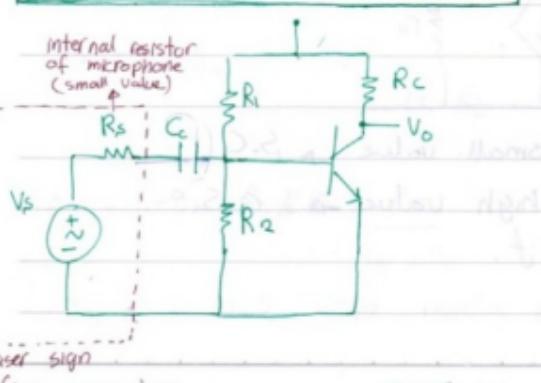

C_c : coupling capacitor
it is used to block any DC component from the user. SO, the position of Q-point is independent on the DC component from the user.

• Basic CE Amplifier :-

Example :-


Find : ① the voltage

$$\text{gain } A_v = \frac{V_o}{V_s}$$

Pin point to output stage


- ② R_i "input impedance"
- ③ R_o "output impedance"
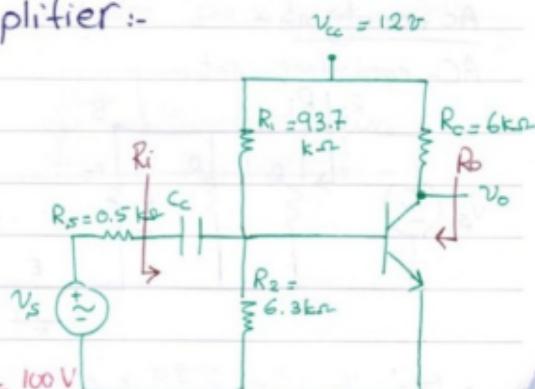
$$\beta = 100 \quad V_a = 0.7 \quad V_A = 100 \text{ V}$$



DC analysis :-

DC equivalent circuit :-

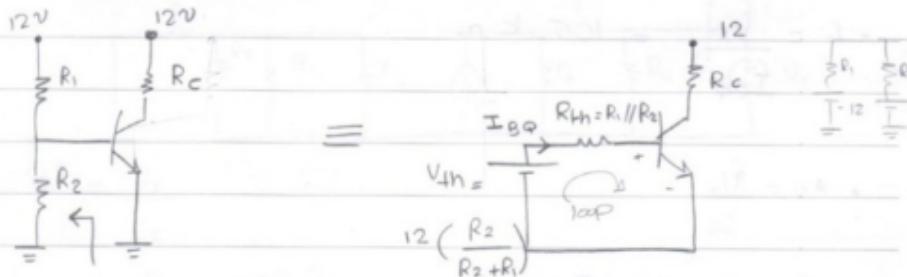

$$-V_{th} + R_{th} I_{BQ} + 0.7 = 0$$

$$I_{BQ} = 9.5 \text{ mA}$$

$$I_{CQ} = \beta I_{BQ} = 0.95 \text{ mA}$$

$$V_{CEQ} = 12 - I_{CQ} R_C = 6.31 \text{ V}$$

$\approx \frac{1}{2} (R)$ → Best value!



Given $R_C = 6 \text{ k}\Omega$

Best value to get
good amplification

$$\frac{12 - 12}{2} \rightarrow -12 \text{ V (O)}$$

Ac-analysis:-

AC equivalent cct:-

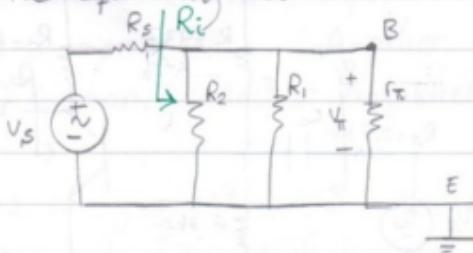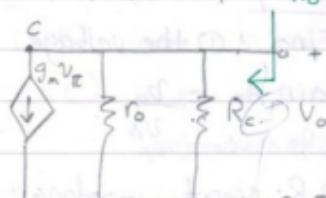s.c.i. — if R_o 

$$\cdot r_{\pi} = \frac{V_T}{I_{EQ}} = 2.74 \text{ k}\Omega$$

$$\cdot g_m = \frac{I_{EQ}}{V_T} = 36.5 \text{ mA/V}$$

$$\cdot r_o = \frac{V_A}{I_{CQ}} = 105 \text{ k}\Omega$$

$$\cdot A_v = \frac{V_o}{V_s}$$


$$\rightarrow V_o = -g_m v_{\pi} (R_o \parallel r_o) \quad \rightarrow (1)$$

$$\rightarrow v_{\pi} = V_s \left(\frac{R_1 \parallel R_2 \parallel r_{\pi}}{R_1 \parallel R_2 \parallel r_{\pi} + R_s} \right) \quad \rightarrow (2)$$

Sub (2) in (1)

$$A_v = \frac{V_o}{V_s} = \frac{-g_m (R_o \parallel r_o) (R_1 \parallel R_2 \parallel r_{\pi})}{(R_1 \parallel R_2 \parallel R_{\pi}) + R_s} = -163$$

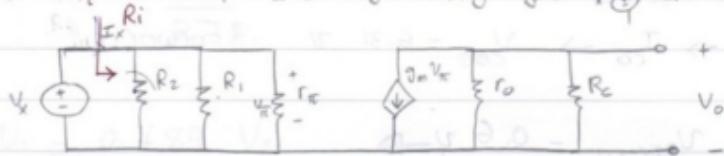to find R_i indep. sources short circuiting v_x \rightarrow src. v_x




$$R_i = \frac{v_x}{I_x} \text{ using } v_{th}$$

$$-v_x + I_x (R_i // R_2 // r_\pi) = 0$$

$$R_i = \frac{v_x}{I_x} = R_i // R_2 // r_\pi = 1.87 \text{ k}\Omega$$

to find R_o

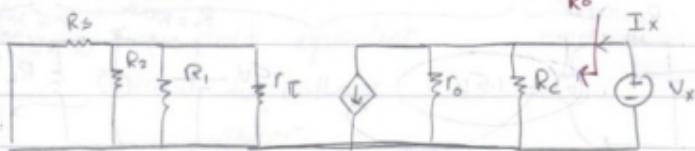

$$R_o = \frac{v_x}{I_x}$$

$$\Rightarrow R_o = r_\pi // R_C$$

$$= 5.68 \text{ k}\Omega$$

Advantage:- high A_v

Disadvantage:- 1. very sensitive to $v_{BE(on)}$ \rightarrow (unstable performance)

calculation

$$\text{if } V_{BE(\text{ON})} = 0.7 \text{ V} \Rightarrow$$


$$I_{BQ} \rightarrow I_{CQ} \rightarrow V_{CEQ} = 6.31 \text{ V} \quad \text{"Forward"}$$

$$\text{if } V_{BE(\text{ON})} = 0.6 \text{ V} \Rightarrow$$


$$I_{BQ} \rightarrow I_{CQ} \rightarrow V_{CEQ} = -3.62 \text{ V} \quad \text{"Not Forward"}$$

2. high loading effect:-

loading effect:

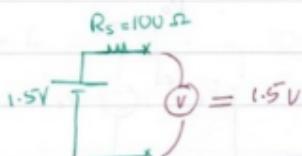

src without
load

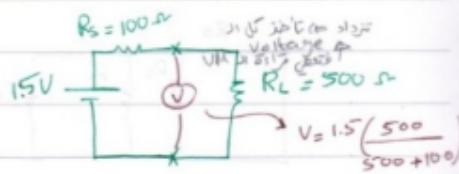

src with
load

$$= 1.25 \text{ V}$$

$$1.25 < 1.5$$

→ To reduce the loading effect ($V_o \approx V_s$)


R_L should be $\gg R_s$

→ in our example:

$$R_i = 1.87 \text{ k}\Omega$$


$$R_s = 0.5 \text{ k}\Omega$$

$$R_s \ll R_i$$

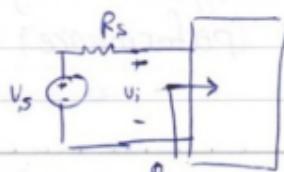

$$v_i = v_s \frac{R_i}{R_i + R_s}$$

$$v_i = 0.789 v_s$$

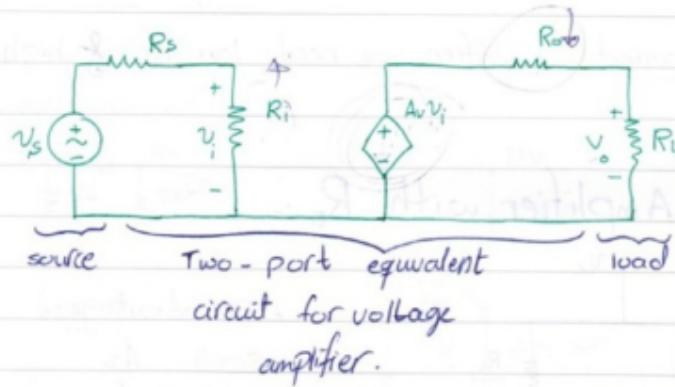

$$\cdot v_i = v_s \frac{R_i}{R_i + R_s}$$

To reduce the loading effect on the input circuit ($v_i \approx v_s$) we need high R_i

$$\cdot v_o = Av v_i \frac{R_L}{R_L + R_o}$$

To reduce the loading effect on the output

circuit ($V_o \approx A_v V_i$) we need low R_o $\rightarrow E R_o \text{ low}$
Voltage follower


- (High R_i and Low R_o) Good voltage amplifier

voltage Amp \rightarrow wide Good current \rightarrow narrow Amp



- For current amplifier we need low R_i & high R_o

- CE - Amplifier with R_E :-

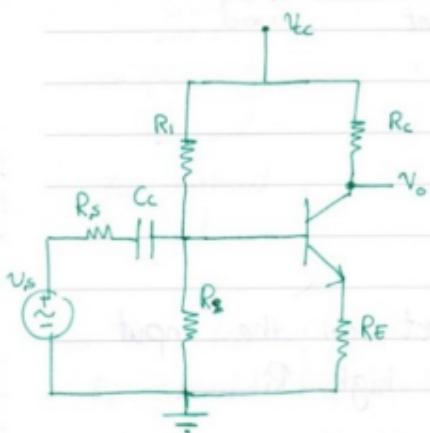

* Disadvantage:-

Small A_v

* Advantages:-

1. A_v is less dependent on β (stable gain)
2. small loading effect.


Example

$\beta = 100$, $V_A = \infty$ (no early effect, $r_o = \infty$ open circuit),

$$V_{BECON} = 0.7 \text{ V}$$



Find :-

- ① A_v
- ② R_i
- ③ R_o

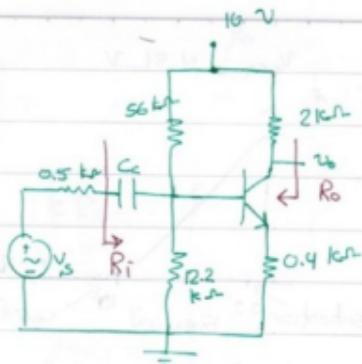

. DC analysis:-

DC-equivalent circuit:

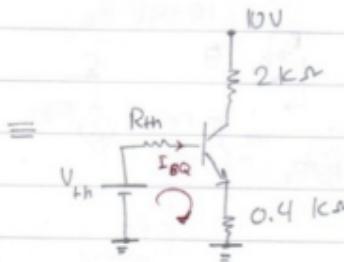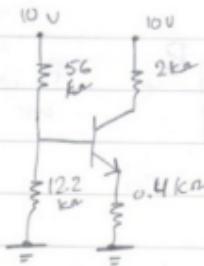

$$R_{in} = 56 // 12.2 \text{ k}\Omega$$

$$R_{in} = 10 \text{ k}\Omega$$

$$V_{in} = 1.78 \text{ V}$$


*input loop:-

$$-V_{in} + R_{in} I_{BQ} + 0.7 + 0.4(1 + \beta) I_{BQ} = 0$$


$$I_{BQ} = 0.0216 \text{ mA} = 21.6 \text{ mA}$$

$$I_{CQ} = \beta I_{BQ} = 100 \times 21.6 \text{ mA} = 2.16 \text{ mA}$$

$$V_{CEO} = 4.81 \text{ V}$$

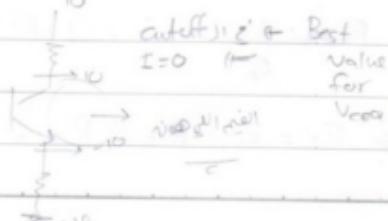


$$V_{CEQ} = 4.81 \text{ V}$$

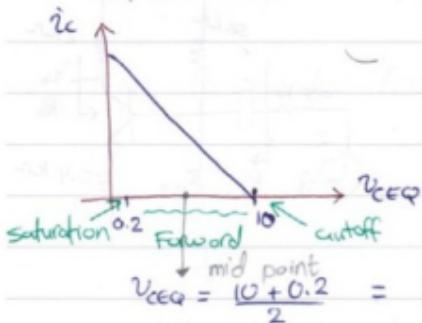

$$V_{CEQ} = \frac{10 + 0.2}{2} = 5.1$$

Best value for V_{CEQ}

AC-analysis:-

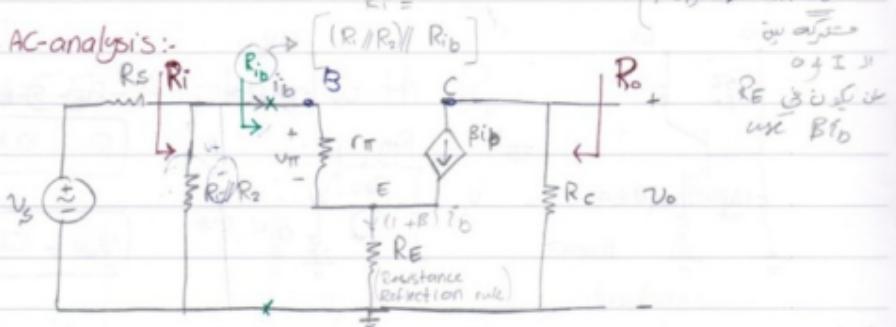



$$R_{B1} = \frac{V_S}{I_x}$$

$$-V_x + i_x r_x + (1+B) i_x R_E = 0$$

$$R_{B1} = \frac{V_S}{I_x} = r_x + (1+B) R_E = 41.6 \text{ k}\Omega$$
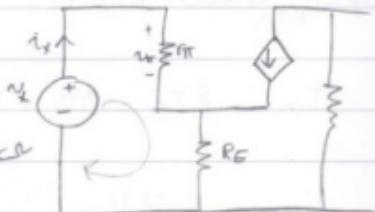
$$\rightarrow R_i = R_1 \parallel R_2 \parallel R_{B1} = 8.06 \text{ k}\Omega$$



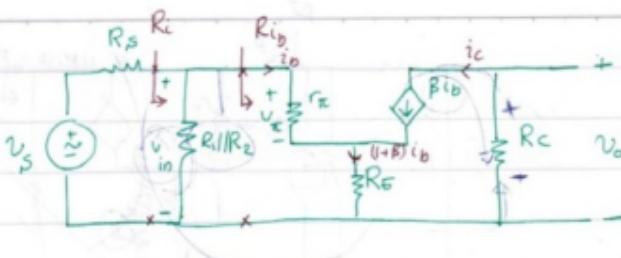

$$R_i = R_i \parallel R_2 \parallel R_{i_b}$$

$$R_{i_b} = r_x + (1 + \beta) R_E$$

$$A_v = \frac{v_o}{v_s}$$

$$\rightarrow v_o = -\beta i_b R_C \quad \boxed{1}$$

$$v_i = v_s \frac{R_i}{R_i + R_s}$$

$$i_b = \frac{v_i}{R_{i_b}} = \frac{v_s}{R_{i_b}} \frac{R_i}{R_{i_b}(R_i + R_s)} \quad \boxed{2}$$

use 1 & 2 :-

$$A_v = \frac{v_o}{v_s} = -\frac{\beta R_C}{r_x + (1 + \beta) R_E} \left(\frac{R_i}{R_i + R_s} \right)$$

$$A_v = -4.53 \quad \text{exact value.}$$

$$R_E = 1.2 k\Omega$$

~~EU + B > R_E~~

$$\frac{R_E}{R_I} \text{ del } R_S \text{ or } V_o = \text{if } R_E > R_I$$

approximate value of $A_v \approx -\frac{R_C}{R_E}$

inverted phase
but up this is exam

Because:-


1. $(1 + \beta)R_E \gg r_o$
2. $R_i \gg R_s$

Disadvantage:- small $A_v = -4.53$

Advantage :- 1. A_v is less dependent on β

	β	A_v
مقدار کمی β	50	-4.41
مقدار متوسط β	100	-4.53
A_v stable & remains constant.	150	-4.57

2. Small loading effect

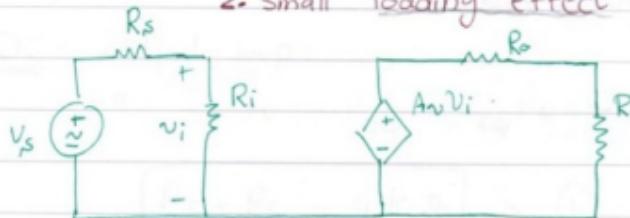

jeeli $\neq R_i$

no effect

loading effect \downarrow

$$V_i = V_s \quad R_i \approx 8.06$$

$$R_i + R_S \approx 0.5 k\Omega$$

$$V_i = 0.942 V_s$$


for stability use *
this design CE with R_E
but the gain \Rightarrow multistage

Design:

loading effect \rightarrow Buffer w/
zero input resistance
 R_L & R_o

11-3-2014 // TUE

3. CE with R_E and By pass Capacitor:-

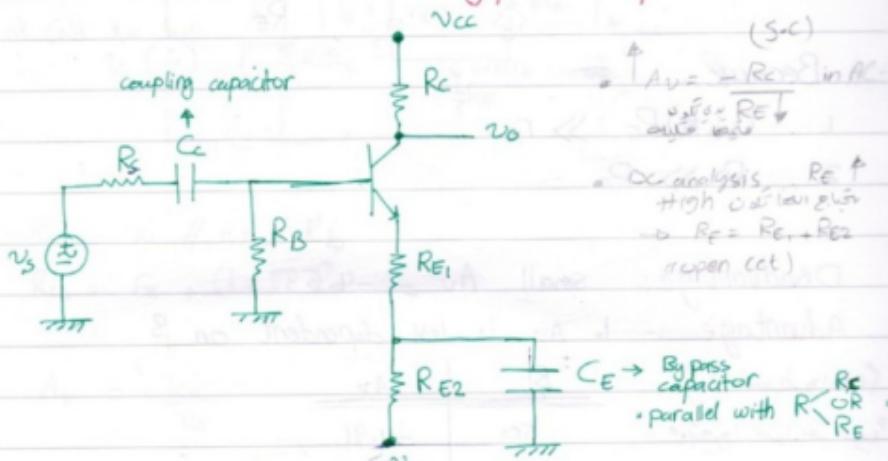

there's no S/C
to get i_b

C_E : ByPass capacitor \rightarrow To satisfy the AC and DC requirement.

simplify Design & Analysis

Example consider a CE amplifier with R_E . Use the approximate gain $A_s = -\frac{R_E}{R_C}$, Assume that $I_{CQ} = 1 \text{ mA} = I_{EQ}$.


$$V_E = 5 \text{ V} \quad V_{CE} = 9 \text{ V}$$

$$\beta = 99 \quad R_L \parallel R_2 \approx \infty$$

Find R_C & R_E such that:

$$\text{[1]} \quad A_v = -8$$
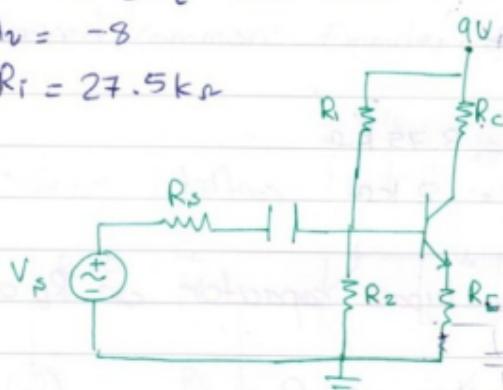
$$\text{[2]} \quad R_i = 27.5 \text{ k}\Omega$$



DC requirements:

$$I_{CQ} = 1 \text{ mA}$$

$$V_{CEQ} = 5 \text{ V}$$

AC requirements:

$$A_v = -8$$

$$R_i = 27.5 \text{ k}\Omega$$

DC: output loop: $-9 + I_{CQ} R_C + V_{CEQ} + I_{EQ} R_E = 0$

$$R_C + R_E = 4 \text{ k}\Omega \rightarrow \textcircled{1}$$

AC: $A_v = -8 = -\frac{R_C}{R_E} \rightarrow R_C = 8 R_E \rightarrow \textcircled{2}$

$$R_i = 2.75 \text{ k}\Omega$$

$$R_i = R_{\pi} \parallel R_2 \parallel R_{ib}$$

$$27.5 = R_{\pi} + (1+B)R_E$$

$$\frac{V_T}{I_{BQ}} = 2574$$

$$R_E = 0.25 \text{ k}\Omega$$

From ①: $R_C = 3.75 \text{ k}\Omega$

From ②: $R_E = 2 \text{ k}\Omega$ conflict.

Solution:- use bypass capacitor on R_E or R_C

Bypass capacitor on R_E :-

$$\underline{DC}: -V_{cc} + I_{CQ}R_C + V_{CEQ} + I_{EQ}(R_{E1} + R_{E2}) = 0$$



$$R_C + R_{E1} + R_{E2} = 4 \text{ k}\Omega \quad \dots \textcircled{1}$$

$$\underline{AC}: A_V = 8 = \frac{-R_C}{R_E} \rightarrow R_C = 8 R_E \quad \dots \textcircled{2}$$


$$R_i = R_{\pi} + (1+B)R_E \rightarrow R_{E1} = 0.25 \text{ k}\Omega$$

from ②: $R_C = 2 \text{ k}\Omega$


from ①: $R_{E2} = 1.75 \text{ k}\Omega$

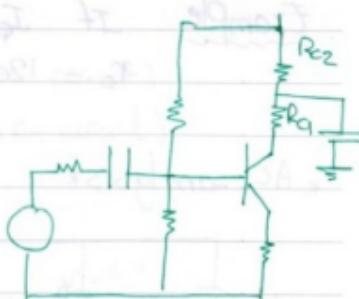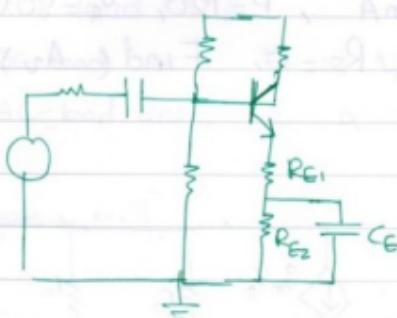

• Advanced common Emitter amplifier CE :

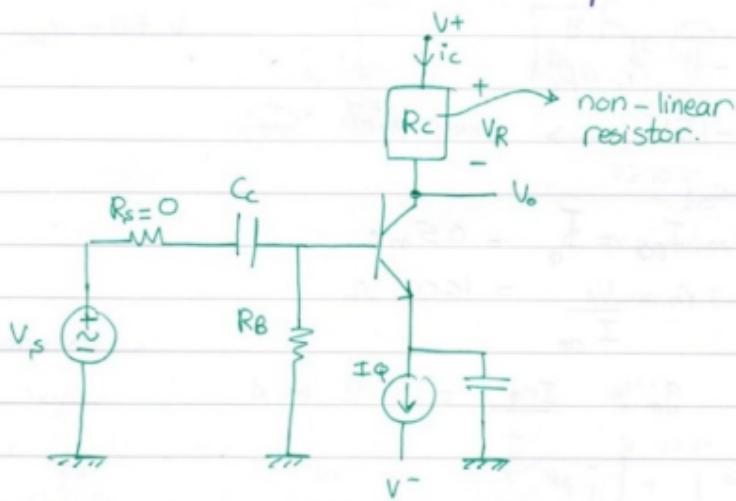


Advantage :- very high A_v

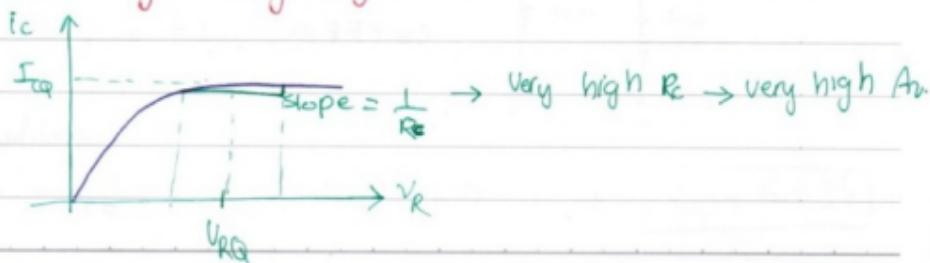

Example If $I_Q = 0.5 \text{ mA}$, $\beta = 120$, $V_A = 80 \text{ V}$
 $r_c = 120 \text{ k}\Omega$, $R_s = 0$, Find (A_v) :-

* AC analysis *

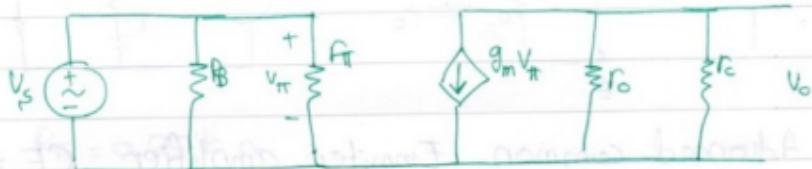

$$A_V = -g_m (r_o / R_c)$$

$$= -1317 \rightarrow \text{very high Gain.}$$

where $I_{EQ} = I_Q = 0.5 \text{ mA}$

$$r_o = \frac{V_A}{I_{EQ}} = 160 \text{ }\Omega$$

$$g_m = \frac{I_{EQ}}{V_T} = 19.2 \text{ mA}$$

- AC-load line:-

- DC-load line: $I_C \propto V_{CE}$ (DC-circuit)


- AC-load line: $i_c \propto v_e$ (AC-circuit)

* Example :- 6.9

$$\beta = 15G$$

$$V_A = \infty$$

$$V_{EB}(\text{con}) = 0.7 \text{ V}$$

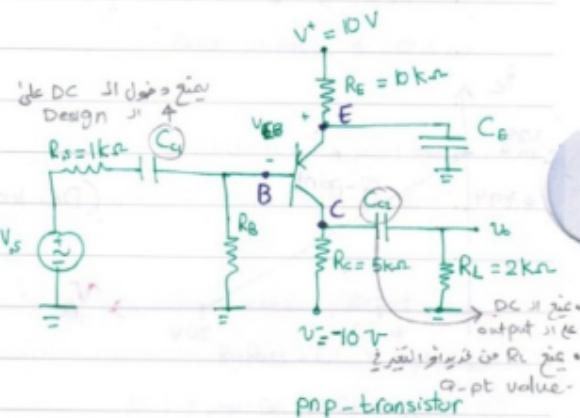

pnp-transistor
Q-pt value-

common Emitter Amp.

* DC-analysis *

input loop:

$$-10 + I_{EQ} \times 10 + 0.7 + 5I_{EQ} = 0$$


$$\rightarrow I_{EQ} = 5.96 \text{ mA}$$

$$I_{CO} = \beta I_{EQ} = 0.894 \text{ mA}$$

output loop:

$$-10 + I_{EQ} R_E + V_{ECQ} + I_{CO} R_C - 10 = 0 \rightarrow$$

$$V_{ECQ} = 6.53 \text{ V}$$

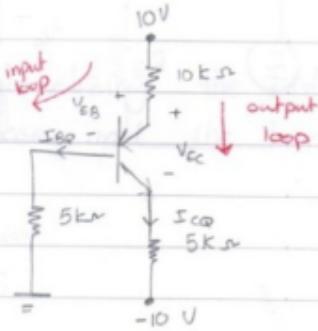


(Q23) DC load line:-


$$-V^+ + R_E \left(\frac{1+\beta}{\beta} I_C \right) + V_{EC} + I_C R_C + V^- = 0$$

$$I_C = \frac{V^+ - V^-}{R_C + \left(\frac{1+\beta}{\beta} \right) R_E}$$

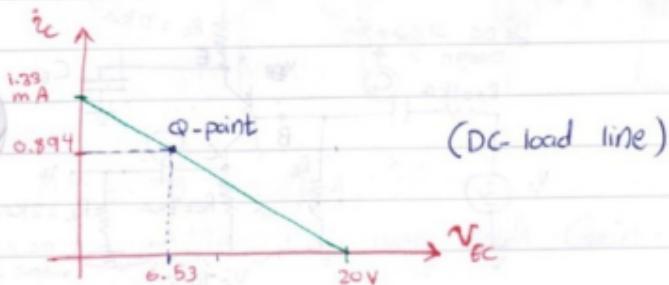Normal range of operation
By default (n. Forward)



* AC analysis *

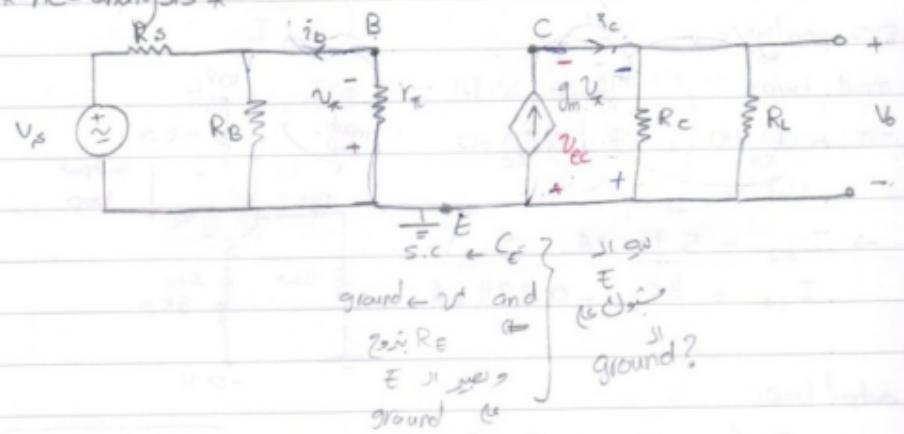


* AC load line :-

$$v_{ce} = -i_c (R_c // R_L)$$

$$i_c = -\frac{1}{R_c // R_L} v_{ce} \rightarrow \text{AC-load line eqn.}$$

zero bias & Q-pt

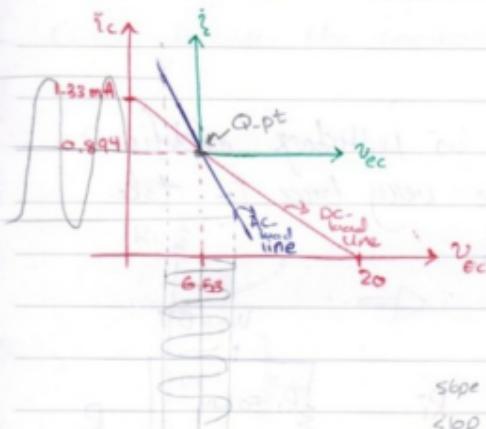

AC & DC load line

AC-load line.

Gain will be 100

op. in AC circuit

Bypass - C

AC stage = DC + RC load

slope AC

slope DC > slope AC

- AC load line helps in visualizing the relationship between the small signal response and the transistor characteristics.

* R_{in} should be high because $R_i = R_1 \parallel R_2 \parallel R_{in}$
 ~~R_i & R_{out} is high~~ \Rightarrow R_i & R_{out} \leftarrow High \rightarrow 20-3-2014
 parallel \Rightarrow R_i is very high

* Common Collector Amplifier:- (Emitter follower / buffer).

* Features:-

1. High $R_i \rightarrow$ loading effect is small in the input $\Rightarrow V_i = V_s$
2. Low $R_o \rightarrow$ as $S/C \Rightarrow$ small loading effect in the output
3. $A_v \approx +1$
4. $A_i \approx 1 + \beta$
5. It's used as a final stage in multistage amplifiers
6. R_1 & R_2 ~~should~~ should be very large to take the advantage of high R_{in} .

* Ex *

$$\beta = 100$$

$$V_A = 80V$$

$$\text{Find } A_v = \frac{V_o}{V_s},$$



$$R_i, R_o, A_i = \frac{I_o}{I_{in}}$$

load $\Rightarrow V_o \approx V_{oc}$ without drop


$$W = \frac{V_o}{R_i + R_o} \cdot R_o$$

$$V_i = V_s - \frac{V_s}{R_i + R_o} \cdot R_i$$

because R_i very high

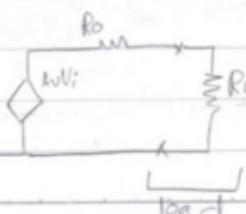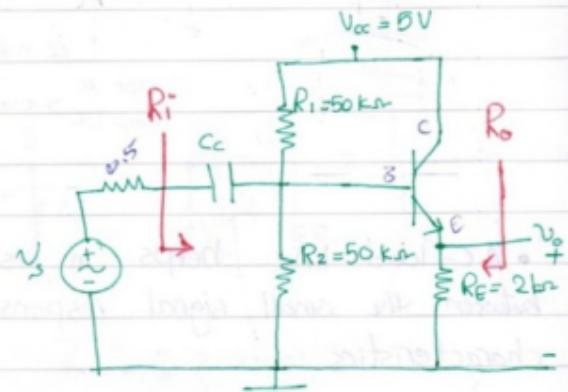


= open

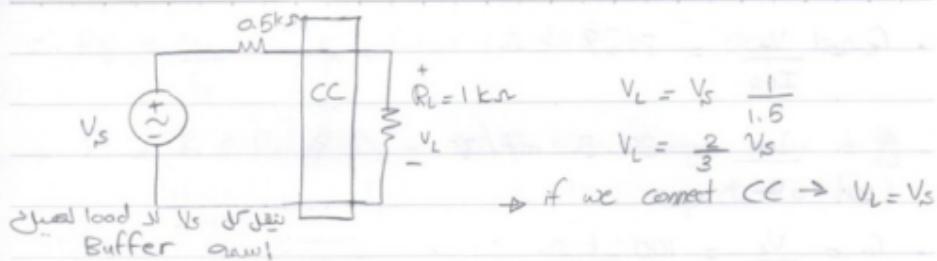

and the voltage in E follows the input voltage (in Mag & f phase)
 $\text{CC} \rightarrow$ because the common is collector.

- DC-analysis :-

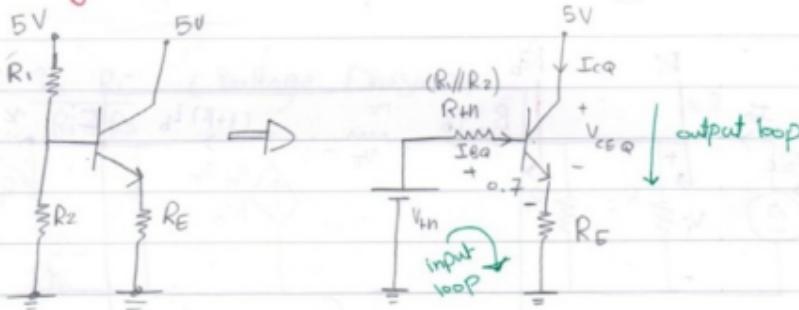

$$\text{input loop: } -2.5 + I_{BQ}(25) + 0.7 + R_E(1+\beta) I_{BQ} = 0$$

$$I_{BQ} = 7.929 \text{ mA}$$

$$I_{cQ} = \beta I_{BQ} = 0.793 \text{ mA}$$

$$\text{output loop: } -5 + V_{ceQ} + R_E I_{ceQ} = 0$$



$$V_{ceQ} = 3.5 \text{ V}$$

$$R_T = \frac{V_T}{I_{BQ}} = 3.28 \text{ k}\Omega$$

$$g_m = \frac{I_{DQ}}{V_T} = 30.5 \text{ mA/V}$$


$$r_o = \frac{V_A}{I_{CQ}} = 100 \text{ k}\Omega$$

AC-analysis:-

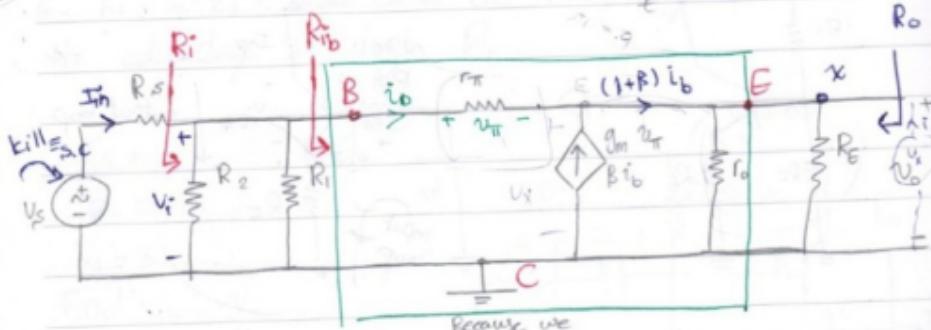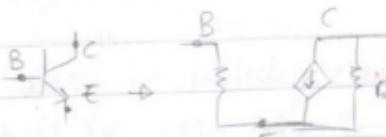

$$R_i = R_1 // R_2 // R_{ib} \rightarrow i_x \approx V_x \omega_n \text{ due to } R_{ib} \text{ pairing}$$

start w/ R_{ib} & R_E &

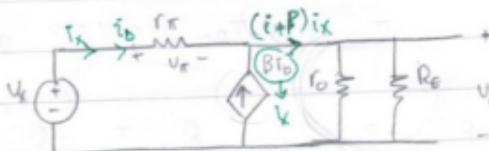

$$\text{loop} \rightarrow -U_x + i_x r_\pi + (1+B)i_x (R_o // R_E) = 0$$

$$\therefore R_{ib} = \frac{v_x}{i_x} = r_\pi + (1+\beta)(r_o \parallel R_E) = 201 \text{ k}\Omega$$

$$\rightarrow R_i = R_1 \parallel R_2 \parallel R_{ib} = 22.2 \text{ k}\Omega \quad (\text{High value with respect to } R_s)$$

should be ↑
 high high

$$A_v = \frac{v_o}{v_s} \quad v_s \text{ & } v_o \text{ in common}$$

$$v_o = (1+\beta) i_b (r_o \parallel R_E)$$

$$v_{in} = \frac{v_s R_i}{R_i + R_s} \quad (\text{Voltage Division})$$

$$i_b = \frac{v_{in}}{R_{ib}}$$

$$\rightarrow A_v = \frac{v_o}{v_s} \left(\frac{r_\pi + R_1 \parallel R_2 \parallel R_s}{1 + \beta} \right) \parallel R_E \parallel r_o$$

$$= +0.962 \approx 1$$

$$R_o = \frac{V_x}{i_x}$$

KCL at node X:-

$$I_x + g_m V_\pi = \frac{V_r}{R_E} + \frac{V_r}{r_o} + \frac{V_x}{r_\pi + R_S // R_1 // R_2} \rightarrow ①$$

$$V_\pi = -V_x \frac{r_\pi}{r_\pi + R_S // R_1 // R_2} \rightarrow ②$$

sub ② in ① :

$$R_o = \frac{V_x}{i_x}$$

$$= \left(\frac{r_\pi + (R_1 // R_2 // R_S)}{1 + B} \right) // R_E // r_o$$

it can give a difference

$R_o = 36.6 \approx \text{"very low value"}$

$$A_I = \frac{i_o}{i_{in}}$$

$$\approx i_o = (1 + B) i_b \frac{r_o}{r_o + R_E} \rightarrow ①$$

$$i_b = i_{in} \frac{R_1 // R_2}{R_1 // R_2 + R_{ib}} \rightarrow r_\pi + (1 + B)(r_o // R_E) \rightarrow ②$$

23-3/2014

use ① & ②:

$$A_i = \frac{i_o}{i_{in}} = (1+B) \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{ib}} \right) \left(\frac{R_o}{R_o + R_E} \right)$$

Typically/usually $R_o \gg R_E$

$$R_o = 100k\Omega$$


$$R_E = 2k\Omega$$

$R_1 \parallel R_2 \gg R_{ib}$ in this ex. isn't typical

$$\rightarrow A_i \approx 1+B \approx B$$

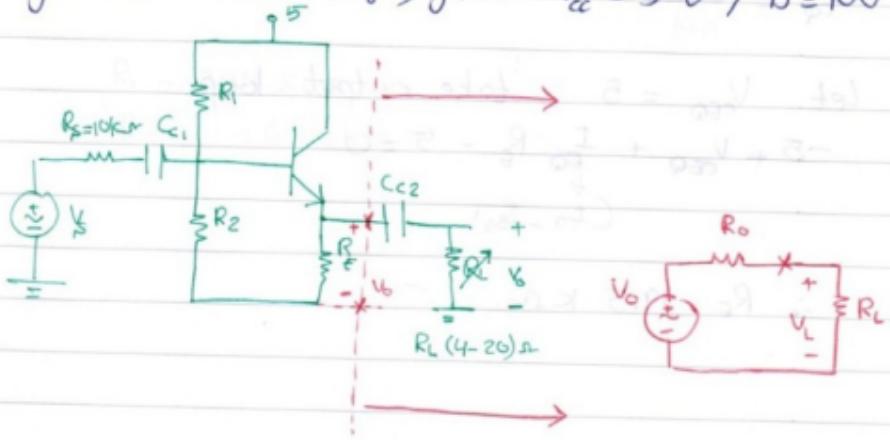Example:- Design a common collector amp.

(CC) that connects a voltage source (microphone) with $R_s = 10k\Omega$ with a load that has R_L changes from $4k\Omega$ to $20k\Omega$, we want to design CC amplifier such that the output voltage doesn't vary more than 5%, given $V_{cc} = 5V / B = 100$



$$0.95 V_o \leq V_L \leq V_o$$

$$0.95 V_o = V_o \frac{R_L}{R_L + R_o} \Rightarrow R_o = 200 \Omega$$

at $R_L = 4 k\Omega$ (cause it will give the least V_L)

For CC:

$$R_o = \left(\frac{r_\pi + R_1 // R_2 // R_s}{1 + \beta} \right) // R_E // r_o$$

usually $R_1 // R_2 \gg R_s$

$$\frac{r_\pi + R_1 // R_2 // R_s}{1 + \beta} \ll R_E // r_o$$

$$R_o \approx \frac{r_\pi + R_s}{1 + \beta}$$

$$r_\pi = 10.2 k\Omega$$

$$r_\pi \approx \frac{V_t}{I_{BQ}} \rightarrow I_{BQ} = \frac{0.076}{10.2k} \approx 2.55 \text{ mA}$$

$$I_{CQ} = 0.255 \text{ mA.}$$


Let $V_{CEQ} = 5$, take output loop:

$$-5 + V_{CEQ} + I_{CQ} R_E - 5 = 0$$

$$(I_{CQ} + I_{BQ})$$


$$\therefore R_E = 19.5 k\Omega.$$

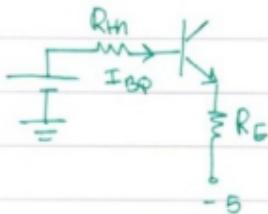→ For stability $R_{th} = 0.1(1+\beta)R_E$ "Rule"
 $R_{th}(= R_1 // R_2) = 198 \text{ k}\Omega$



$$-V_{th} + R_{th} \frac{I_{BQ}}{R_E} + 0.7 + \frac{I_{EQ}}{R_E} - 5 = 0$$

→ we can find V_{th} .

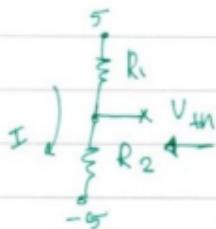

$$V_{th} = \left(\frac{R_2}{R_1 + R_2} \right) (10) - 5 + \frac{R_1}{R_1 + R_2} (10) - 5$$

$$= \frac{R_1}{R_1 + R_2} \left(\frac{R_2}{R_1 + R_2} (10) - 5 \right)$$

R_{th}


$$\therefore R_1 = 344 \text{ k}\Omega$$

$$R_2 = 467 \text{ k}\Omega$$


* Common Base Amplifier (CB) :-


* Features:-

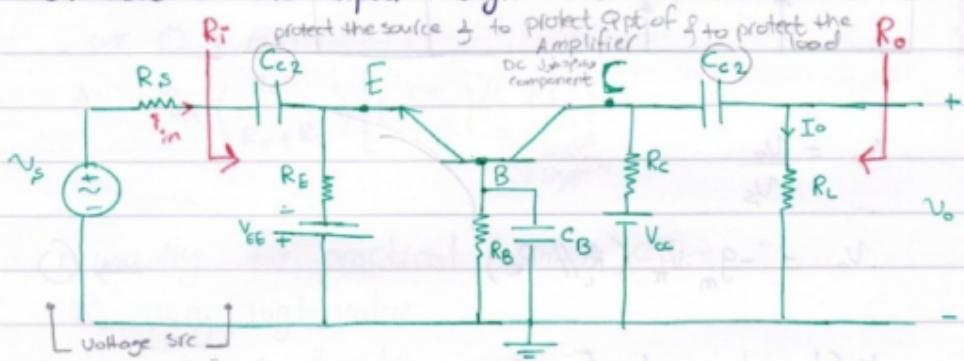1. $A_v > 1$
2. $A_i \approx 1$
3. small R_i
4. high R_o
5. CB - Amplifier \equiv Ideal current source. (without R_s)
6. used if the input signal is a current.



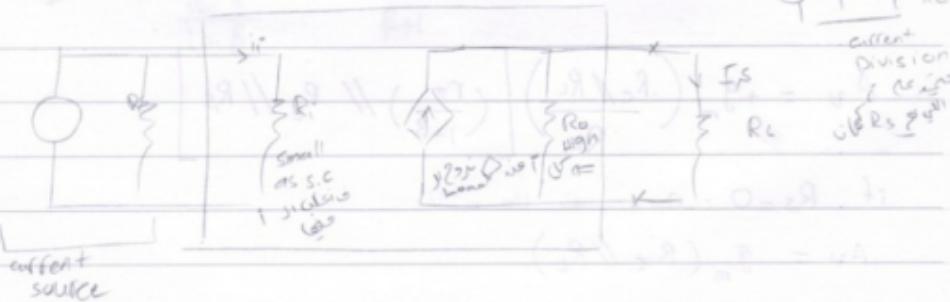Find : $A_v = \frac{V_o}{V_s}$, $A_i = \frac{I_o}{I_{in}}$, R_o, R_i



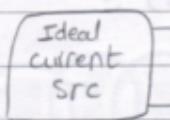


the Reading of Ameter

\rightarrow will still const!

* the equivalent:

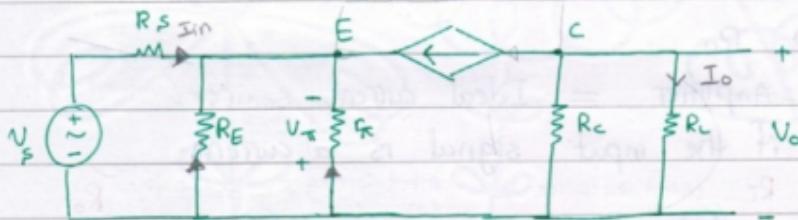$f_0 \rightarrow$ if there is early effect.



$$A_v = \frac{V_o}{V_s}$$

$$V_o = -g_m V_{pi} (R_L // R_C)$$

→ ①

at node E \Rightarrow

$$g_m V_{pi} + \frac{V_{pi}}{R_{pi}} + \frac{V_{pi}}{R_E} + \frac{V_s - (-V_{pi})}{R_s} = 0 \rightarrow ②$$

$$A_v = +g_m \left(\frac{R_C // R_L}{R_s} \right) \left[\left(\frac{r_{pi}}{1+\beta} \right) // R_E // R_s \right]$$

if $R_s = 0$ $\Rightarrow V_{pi} = -V_s$

$$A_v = g_m (R_C // R_L)$$

$$A_i = \frac{I_o}{I_{in}}$$

$$I_o = -g_m V_\pi \frac{R_c}{R_c + R_L} \quad (\text{current division}) \rightarrow ①$$

bCL at Emitter:-

$$I_{in} + g_m V_\pi + \frac{V_\pi}{R_E} + \frac{V_\pi}{r_\pi} = 0$$

$$V_\pi = -I_n \left[\left(\frac{r_\pi}{1+\beta} \right) // R_E \right] \rightarrow ②$$

. ux ① f ②:

$$A_i = g_m \left(\frac{R_c}{R_c + R_L} \right) \left[\left(\frac{r_\pi}{1+\beta} \right) // R_E \right]$$

ملاحظة
النهاية


* usually for practical common CB:-

R_c very high value.

R_L very small value.


$$\rightarrow A_i \approx \frac{g_m r_\pi}{1+\beta} = \frac{\beta}{\beta+1} = \alpha = 0.99 \approx 1$$

* CB - Amplifier:-

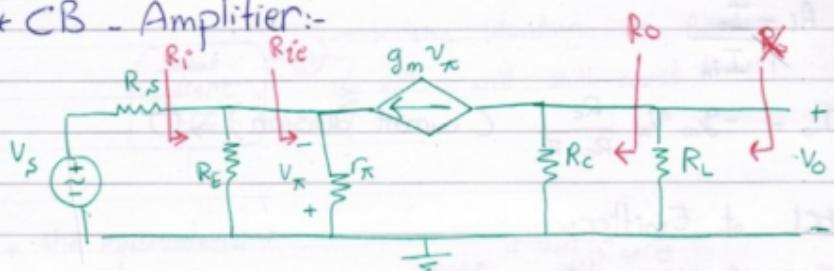

$$R_i = R_E // R_{ie}$$

loop P
current Division
Voltage Division

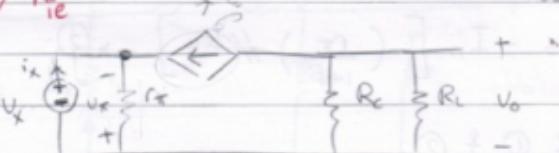

$$R_{ie} = \frac{V_x}{i_x}$$

* find R_{ie} in this

KCL at node E :-

$$i_x + \frac{V_x}{r_x} + g_m V_x = 0$$

cct. +


[AC-equivalent circuit
then gains ...]

$$\text{but } V_x = -V_{ix}$$

$$\Rightarrow i_x - \frac{V_x}{r_x} - g_m V_x = 0$$

$$R_{ie} = \frac{V_x}{i_x} = \frac{r_x}{1 + g_m r_x} = \frac{r_x}{1 + \beta} \rightarrow \text{small value.}$$

• $R_i = R_E // R_{ie}$ "small value"

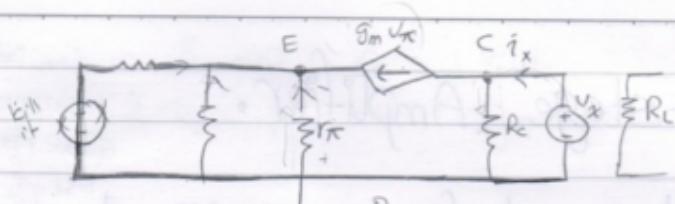

KCL at C:-

$$i_x - \frac{V_x}{R_C} - g_m V_x = 0 \rightarrow ①$$

KCL at E:-

$$g_m V_x + \frac{V_x}{R_E} + \frac{V_x}{R_F} + \frac{V_x}{R_S} = 0$$

$$\rightarrow V_x \left(g_m + \frac{1}{R_E} + \frac{1}{R_F} + \frac{1}{R_S} \right) = 0 \therefore V_x = 0$$

\therefore from ①: $R_o = \frac{V_x}{I_x} = R_C$.

* مراجعة الامتحان *

• Multi-stage Amplifier.


objectives
requirement
البيانات المطلوبة
1-stage.

it is used to satisfy some requirements
that can not be satisfied by single stage.

Example : * CE without R_E \rightarrow has a high A_v
but unstable.

* CE with R_E \rightarrow has low A_v
but stable.


* CC has $A_v = 1$ but high R_i and R_o

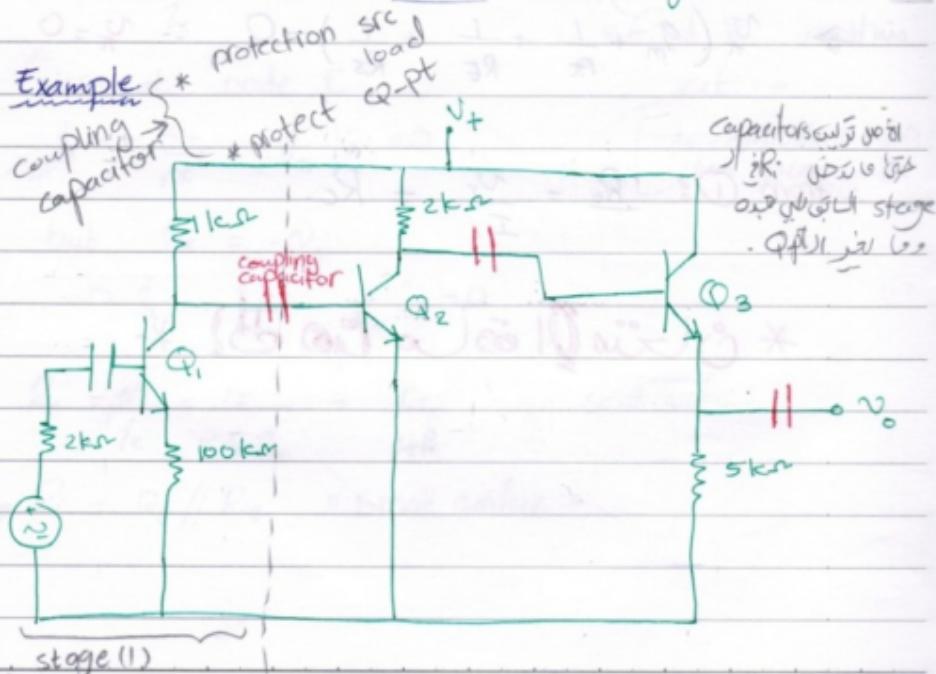


For Q_1 : $\beta = 100$, $r_e = 1 \text{ k}\Omega$

For $Q_2 \& Q_3$: $\beta = 100$, $r_e = 0.5 \text{ k}\Omega$

Find $A_v = \frac{V_o}{V_s}$:

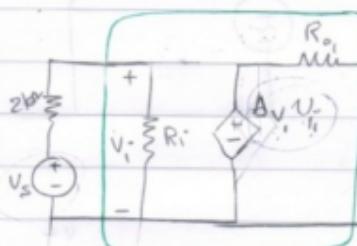

$$V_i = V_s \frac{R_i}{R_i + R_s}$$

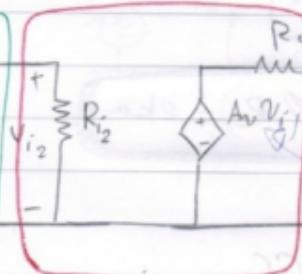

$$V_i = A_v V_m \frac{R_{i2}}{R_{i2} + R_{o1}}$$

$A_v \leftarrow$ الباقي من الـ stage \downarrow يعني ! الباقي من الـ stage \downarrow يعني !

$A_v \& R_o$
stage

* Solution :-

$$\text{stage 1: } A_{v1} = -\frac{\beta R_C}{R_i + (1+\beta)R_E} \left(\frac{R_i}{R_i + R_s} \right)$$


$$R_P = [R_i + (1+\beta)R_E] // \underbrace{R_i // R_2}_{\infty}$$

$$\therefore R_i = R_C + (1+\beta)R_E$$

Sub \rightarrow

$$A_{v1} = -7.63$$

$$R_{o1} = R_C = 1 \text{ k}\Omega$$

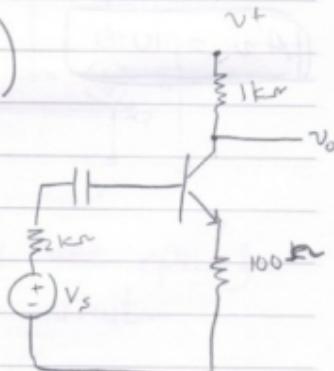


stage 2:- CE without R_E

$$A_{V2} = -g_m \left(\frac{R_1 // R_2 // r_\pi}{R_1 // R_2 // r_\pi + R_o} \right) \left(r_o // R_C \right)$$

R_o

$$A_{V2} = -133$$

$$R_{o2} = r_o // R_C = 2k\Omega$$

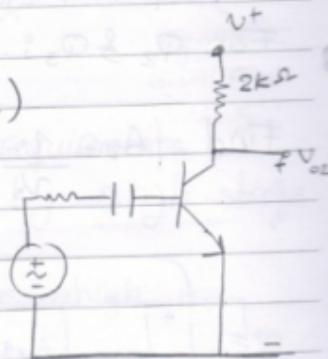


stage 3:- CC

$$V_o = V_s A_1 A_2 A_3$$

$$A_V = \frac{V_o}{V_s} = A_1 A_2 A_3$$

-2.63 2.5 1

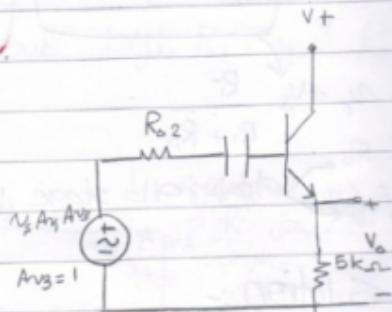

$$[A_V = 1010]$$


High gain $\approx 10^4$

* Active load :

advantage:-

high r_c , so

high A_v

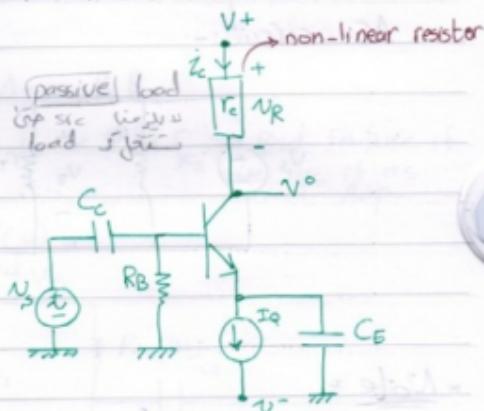

advantages:-

1. small size, so


can be used in

ICs..

2. r_c is high, so


high A_v .

3. we don't need
by pass capacitor.

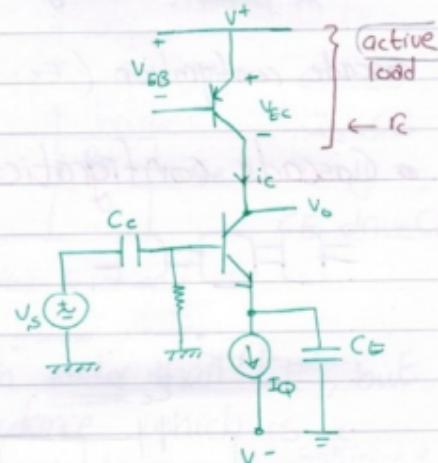

This is an example of using the nph & pnp transistors in the same circuit.

AC- circuit:-

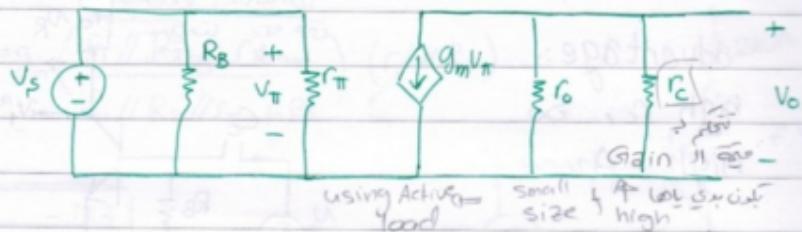


* Note *

Multistage Amplifier could be cascade configuration OR cascode configuration.

output of the first stage is input to the second stage (as series)

cascade configuration (Ex: Darlington pair circuit)


• Cascade configuration:-

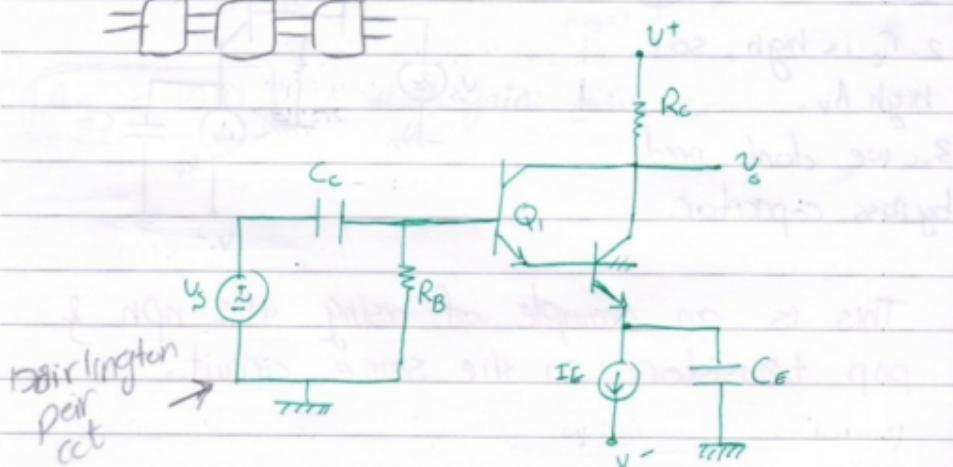

Features:-

1. High current gain : $A_i \approx B_1 B_2$
2. High input resistance: $R_i \approx 2B_1 r_{\pi_2} \rightarrow$ Bad Feature if we use it as current Amp.

* Cascade configuration:-

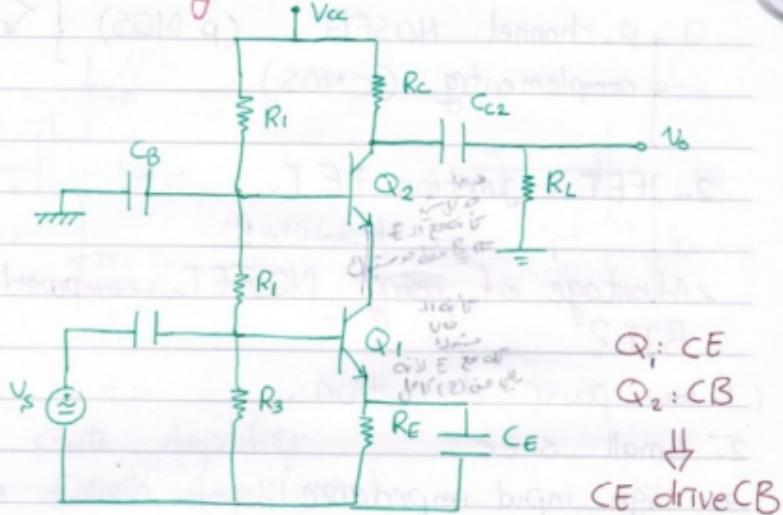

* Advantage :-

- CB stage has bandwidth wider than CE, but CB has low ^(Bad) input impedance which is a limitation in many application. _{CE \rightarrow high input Z}

But cascode configuration has a wide Bandwidth and high input impedance!

CB \rightarrow output is off \rightarrow CE \rightarrow wide input range

* Field Effect Transistor (FET) Amplifiers *

FET:-

1. MOSFET: metal - oxide - semiconductor FET.


- * n-channel MOSFET (n MOS)
 - * p-channel MOSFET (p MOS)
 - * complementary (CMOS)
- } Enhancement
} Depletion.

2. JFET: junction FET.

(for small Ohmic U)

Advantage of using MOSFET compared with BJT?

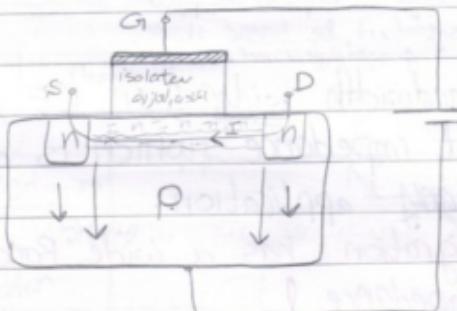1. low power dissipation.
2. small size.
3. High input impedance. \rightarrow because there is isolator.



holes will move with the direction of field \rightarrow majority of n-channel

$$\cdot I_G = 0, I_S = I_D$$

$(V_{GS} > V_{th}) \text{ good}$

\leftarrow loading effect


But: $g_m(\text{BJT}) \gg g_m(\text{FET})$

so that $A_{\text{v(BJT)}} \gg A_{\text{v(FET)}}$


Gain. \rightarrow ~~single stage~~

by using ~~single stage~~
Multistage.

n-channel MOSFET

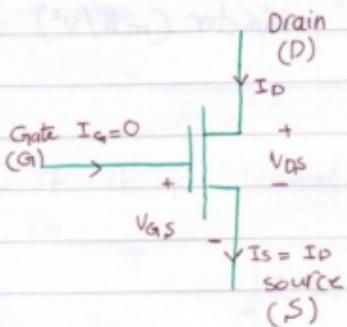

p - channel MOSFET

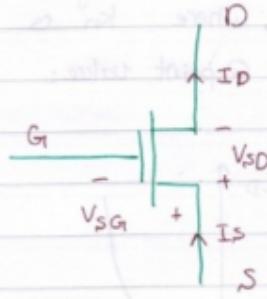

. we will have :-

- 1- common Gate Amplifier
- 2- Common Drain Amplifier
- 3- Common Source Amplifier


* The Transistor should be in **Saturation Mode** to work as Amplifier.

• DC-analysis :-

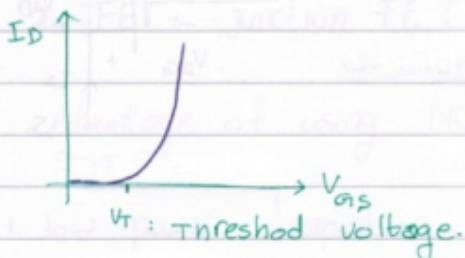1. Draw DC-equivalent cct, $-I-$: o.c
Finding it from input loop AC-src: S.C
↑ then use eqn
2. use $I_{DQ} = K_n \left(\frac{V_{GSQ}}{V_{TN}} - V_{TN} \right)^2$

where K_n is the conduction parameter (mA/V^2)


- Q-point value: I_{DQ} , $\frac{V_{GSQ}}{V_{DS}}$, $\frac{V_{DS}}{\text{controller}}$



→ if $V_{DSQ} > V_{DS(\text{sat})}$, then saturation Mode.

↳ Finding it from output loop.

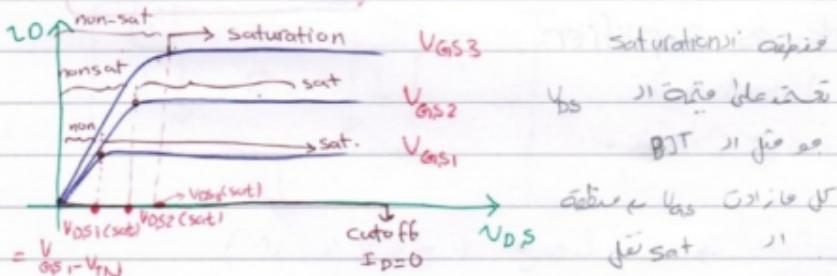
$$V_{DS(\text{sat})} = V_{GSQ} - V_{TN}$$




* AC-analysis *

- Draw Ac-equivalent cct:

- if it n-channel:-

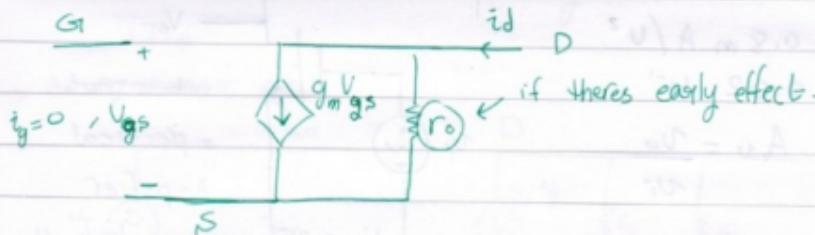

- if it p-channel:-

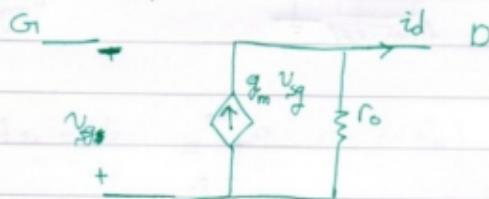

$$\rightarrow g_m = 2kn(V_{GSQ} - V_{TN}) \rightarrow \text{for n-channel}$$

but $g_m = 2kp(V_{SGQ} + V_{TP}) \rightarrow \text{p-channel}$

$$\rightarrow r_o = \frac{1}{\lambda I_{DS}}$$

• where λ is the channel length modulation parameter.
(+ve value)

$$\rightarrow i_d = g_m V_{gs} = 2kn(V_{GSQ} - V_{TN}) V_{gs}, \text{ if } r_o = \infty$$

* Example :-

Given :

$$V_{TN} = 1V$$

$$k_A = 0.8 \text{ mA/V}^2$$

$$\lambda = 0.02 \text{ V}^{-1}$$

$$\text{find } A_v = \frac{V_o}{V_i}$$

it is common source.

DC-analysis:-

$$V_{DSQ} = V_G = 2.12V$$



$$I_{DQ} = k_A \left(\frac{V_{GSQ} - V_{TN}}{2} \right)^2$$

$$I_{DQ} = 1 \text{ mA}$$

$$V_{DSQ} = V_{DD} - I_D R_D = 2.5V$$

$$V_{DSQ} > (V_{DS(sat)} = V_{GS} - V_{TN}) \quad \checkmark \text{ (saturation)}$$

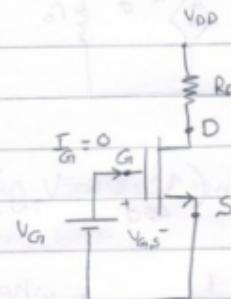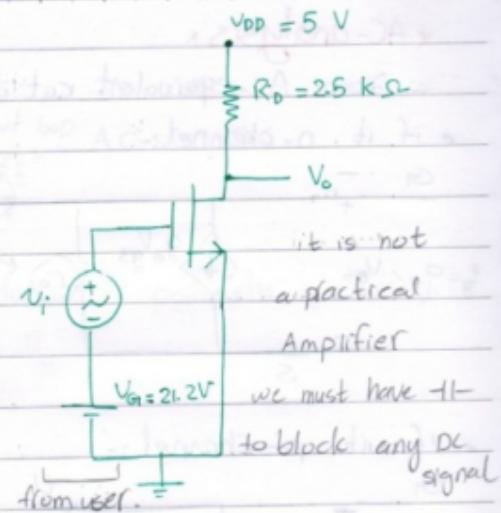so we can use the transistor as amplifier




AC-analysis:-

$$\cdot g_m = 2k_n(V_{GSSQ} - V_{TN}) = 1.79 \text{ mA/v}$$

$$\cdot r_o = \frac{1}{2I_D} = 50 \text{ k}\Omega \quad (\text{early effect})$$

→ AC-equivalent circuit:-

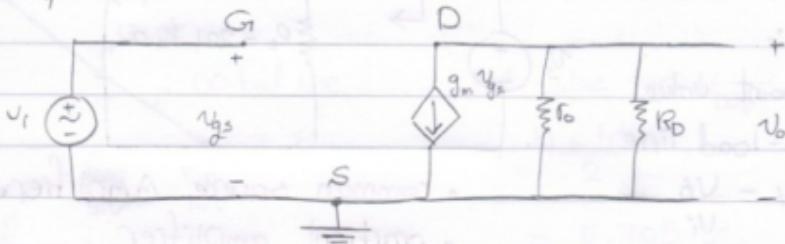

$$A_v = \frac{U_o}{U_i} = -g_m (r_o // R_o)$$

$$A_v = -4.26 \quad (\text{BJT } \text{is direct small value})$$

• use the same circuit in the previous example, but with p-channel MOSFET

$$\left\{ V_{DD} = -5 \text{ v} \right.$$

and $\left. + (2.12) \text{ OR } + (-2.12) \right.$

$$A_v = -g_m (r_o // R_o) \text{ & it is the same value.}$$



+ Example:-

$$V_{TN} = 1.5 \text{ V}$$

$$k_n = 0.5 \text{ mA/V}^2$$

$$\lambda = 0.01 \text{ V}^{-1}$$

Find :-


1. Q-point value

2. DC-load line

3. $A_v = \frac{V_o}{V_i}$

4. R_i

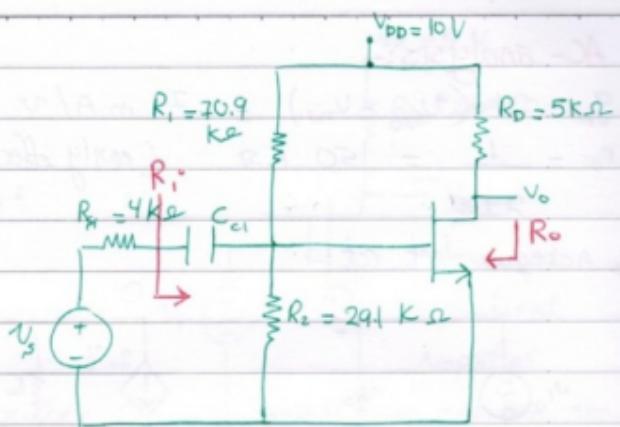5. R_o (~~Output~~ ~~current~~ ~~is~~ ~~in~~ ~~the~~ ~~out~~)




- common source Amplifier.
- practical amplifier.

Dc-analysis:-

voltage division

$$V_{GSO} = 10 \times \frac{R_2}{R_2 + R_1} = 2.91 \text{ V}$$
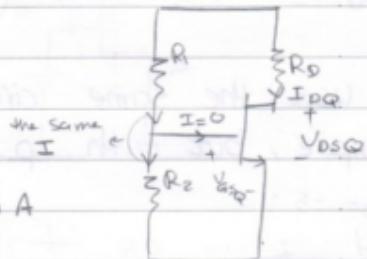
$$I_{DQ} = k_n (V_{GSO} - V_{TN})^2 = 1 \text{ mA}$$



$$V_{DSQ} = 10 - I_{DQ}R_D = 5 \text{ V}$$


$$V_{DSQ} >? (V_{DS(sat)} = V_{GSQ} - V_{TN}) \quad (\text{saturation})$$

DC-load line: $I_D \propto V_{DS}$

$$-V_{PD} + I_D R_D + V_{DS} = 0$$

$$I_D = \frac{V_{DD}}{R_D} - \frac{V_{DS}}{R_D}$$

slope: $-\frac{1}{R_D}$

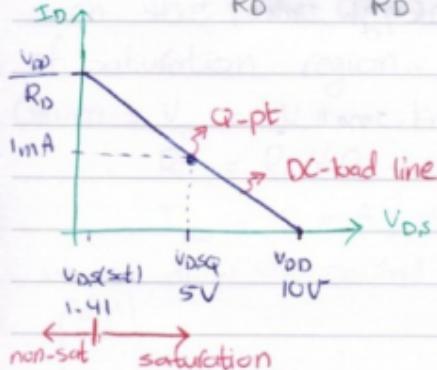


Best value for V_{DSQ} :

$$\frac{10 + 1.41}{2}$$

$$= 5.705 V$$

* AC analysis:-

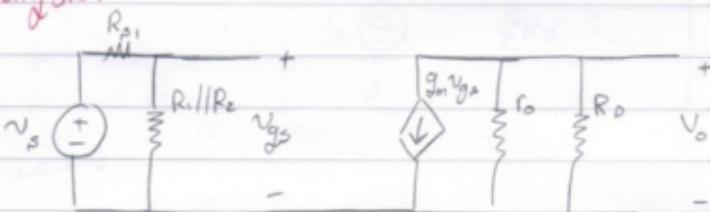

$$A_v = \frac{v_o}{v_i}$$

$$v_o = -g_m v_{gs} (R_L || R_D)$$

$$v_{gs} = v_s \frac{R_1 || R_2}{R_1 || R_2 + R_{S1}}$$

$$A_v = -g_m \left(r_o // R_D \right) \left(\frac{R_1 // R_2}{R_1 // R_2 + R_{S1}} \right) = -0.562.$$

$$R_i = R_1 // R_2 = 20.6 \text{ k}\Omega \quad (\text{high value})$$

$$R_o = r_o // R_D = 4.76 \text{ k}\Omega \quad (\text{small})$$

Design Example:-

Design the bias of MOSFET (common source) such that the Q-point is in the middle of saturation region:-



Given : $V_{TN} = 1V$, $k_n = 1 \text{ mA/V}^2$, $\lambda = 0.015 \text{ V}^2$

$$R_i = R_1 // R_2 = 100 \text{ k}\Omega$$

$$I_{DQ} = 2 \text{ mA}, V_{DD} = 12 \text{ V}$$

we will draw the DC-load line:

$I_D(\text{mA})$

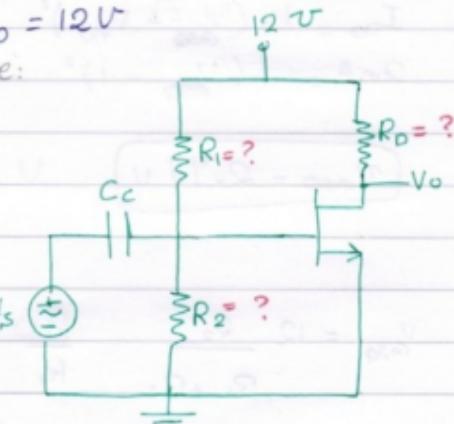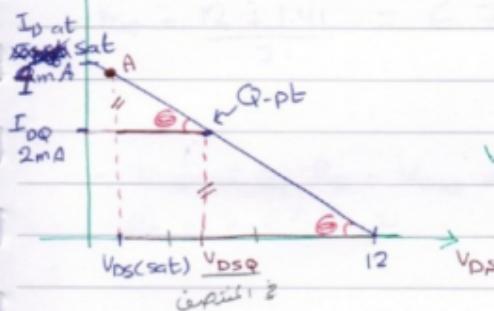

the same tan of G.

at point A: $I_D = 4 \text{ mA}$

$$I_{DA} = k_n (V_{GSA} - V_{TN})^2$$

$$\rightarrow V_{GSA} = 3 \text{ V}$$

$$\Rightarrow V_{DS(\text{sat})} = V_{GSA} - V_{TN} = 2 \text{ V}$$

[the same of at pt A]

$$V_{DSQ} = \frac{12 + 2}{2} = 7 \text{ V}$$

Best value.

$$-12 + I_{DQ} R_D + V_{DSQ} = 0$$

$$(R_D = 2.5 \text{ k}\Omega)$$

$$I_{DQ} = kn(V_{GSQ} - V_{TN})^2$$

$$2 \text{ mA} = i(V_{GSQ} - 1)^2$$

$$V_{GSQ} = 2.41 \text{ V}$$

$$V_{GSQ} = 12 \frac{R_2}{R_1 + R_2} \frac{R_1}{R_1}$$

$$V_{GSQ} = 12 \frac{R_1 R_2}{R_1 + R_2} \cdot \frac{1}{R_1}$$

$$2.41 = 12 \left(\frac{R_1}{R_1 + R_2} \right) \frac{1}{R_1}$$

$$\therefore (R_1 = 498 \text{ k}\Omega)$$

$$(R_2 = 125 \text{ k}\Omega)$$

Q another Solution:-

$$V_{GSG} = 12 \frac{R_i}{R_1} = \frac{1200}{R_1}$$

$$I_{DQ} = k_n (V_{GSG} - V_{TN})^2$$

$$2 = 1C \left(\frac{1200}{R_1} - 1 \right)^2$$

$$\sqrt{2} + 1 = \frac{1200}{R_1} \rightarrow R_1 = \frac{1200}{\sqrt{2} + 1}$$


$$V_{DS(sat)} = 1.41 \text{ V}$$

$$V_{DQ} = \frac{12 + 1.41}{2} = 6.7 \text{ V}$$

$$-12 + I_{DQ} R_D + V_{DSQ} = 0$$

$$R_D = 2.65 \text{ k}\Omega$$

$$V_{DS} = \frac{12}{2.65}$$

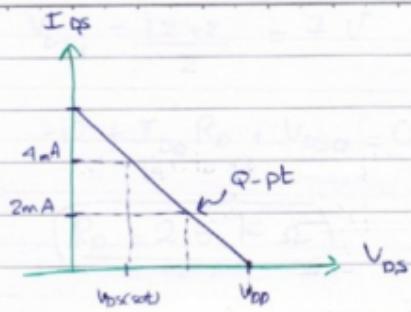

$$I_{D(sat)} = k_n (V_{G_S(sat)} - V_{T_N})^2$$

$$V_{G_S(sat)} = 3V$$

$$V_{DS(sat)} = V_{G_S(sat)} - V_{T_N} = 2V$$

$$V_{DSQ} = \frac{V_{D_D} + V_{DS(sat)}}{2} = 7$$

from the output loop:

$$-V_{DD} + \frac{I_D}{R_D} + \frac{V_{DSQ}}{7} = 0$$

$$\rightarrow R_D = 2.5 k\Omega$$


$$I_{DQ} = k_n (V_{G_SQ} - V_{T_N})^2$$

$$V_{G_SQ} = 2.41V$$

$$V_{GSQ} = V_{DD} * \frac{R_2}{R_1 + R_2} R_1 * \frac{1}{R_1}$$

$$\rightarrow R_1 = 498 \text{ k}\Omega$$


$$R_2 = 125 \text{ k}\Omega$$

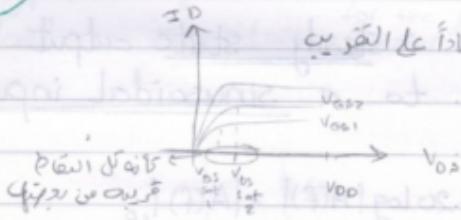

New Chapter

Frequency Response

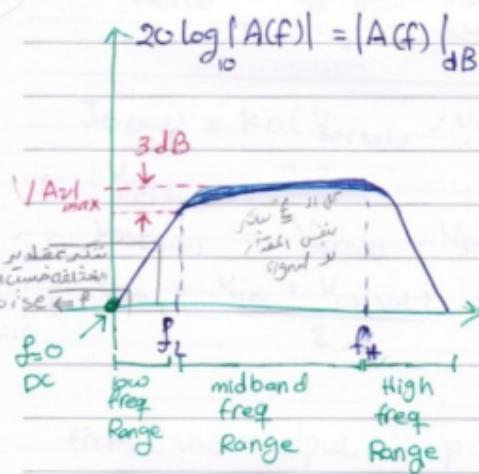
- it is steady state output of a linear sys. due to a sinusoidal input.



f_L : low corner - frequency
low 3dB frequency
~~break-point frequency~~

- Bandwidth (BW) = $f_H - f_L$ Gain indep. on freq
if it wide \Rightarrow Good Amplifier.

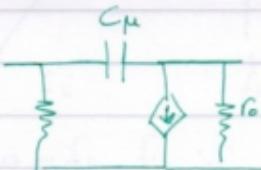- ^{W.P. & useful info}
^{3. Load} Types of capacitors:-
1. coupling and bypass Capacitors $\parallel R_C / \parallel R_E$ ^{Group(1)}
 2. Transistor and load capacitors ^{the same behavior for the both} $\parallel C_L$ ^{Group(2)}



Transistor capacitor



Load capacitor

Capacitor \leftarrow ^{o.c} _{s.c}
 have impedance -

- In DC ($f=0$) \rightarrow all capacitors are open cct.

$$Z_C = \frac{1}{j2\pi f C} = \infty \Omega$$

- In Low frequency range:

Group(1) : $Z_C = \frac{1}{j2\pi f C}$ ^{as balanced $\Rightarrow f \rightarrow j2\pi f C \uparrow$ rise}

Group(2) :  open cct

$$Z_C = \frac{1}{j2\pi f C} \Rightarrow Z_C: \text{high value} \\ \approx \infty \Omega$$

- In midband Range:

Group(1) : S.C

Group (2): open cct


Group (1): High value

Group (2): low "

High frequency range:

Group (1): short cct
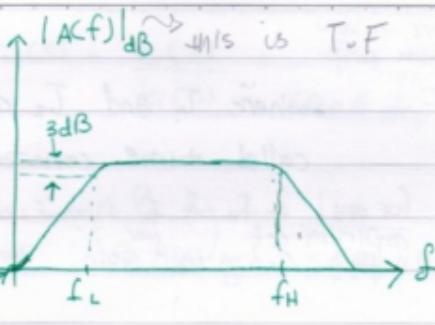
$$\text{Group (2): } Z_c = \frac{1}{j2\pi fC}$$



$$\text{BW} = f_H - f_L$$

Note: The values of capacitors in graph 1 \gg values of capacitors in graph 2.

Transfer Function: $A(f)$

\rightarrow S-Domain:

$$S = j\omega = j2\pi f \quad (\text{complex frequency})$$

$$Z_c = \frac{1}{j\omega C} = \frac{1}{SC}$$

$\frac{S}{+}$
From
Laplace

$$\text{In general, } \underbrace{T(s)}_{\substack{\text{Transfer} \\ \text{function}}} = \frac{k (s - z_1)(s - z_2) \dots (s - z_n)}{(s - p_1)(s - p_2) \dots (s - p_m)}$$

$z_1, z_2 \dots z_n$: Zeros of Transfer function

$p_1, p_2 \dots p_m$: poles of Transfer function.

K: constant.

\rightarrow To draw AF of amplifier, we will consider only two forms of $T(s)$.

$$\textcircled{1} \quad T_1(s) = k_1 \frac{1}{1 + 5T_1 s}$$

corner freq



where T_1 and T_2 are called time constant.

$$\textcircled{2} \quad T_2(s) = k_2 \frac{1}{1 + 5T_2 s}$$

corner freq

for any $f_n & f_c$ then draw amplifier circuit then finding the gain. then draw

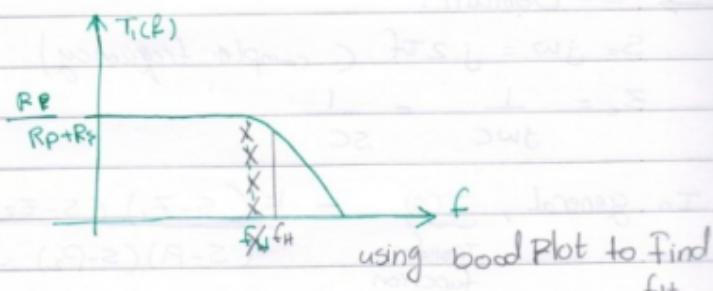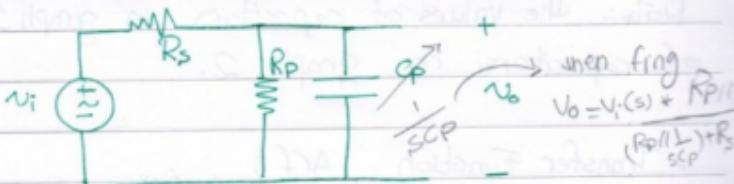• $T_1(s)$: This is transfer function of the following circuit:



$$T_1(s) = \frac{V_o(s)}{V_i(s)}$$

$$V_o(s) = V_i(s) * \frac{R_p // \frac{1}{sC_p}}{(R_p // \frac{1}{sC_p}) + R_s}$$



13-4/2014

$$T_1(s) = \frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{R_p // sC_p}}{(R_p // \frac{1}{sC_p}) + R_s}$$

$$= \left(\frac{R_p}{R_p + R_s} \right) \frac{1}{1 + s(R_p // R_s) C_p}$$

$$\rightarrow K_1 = \frac{R_p}{R_p + R_s} \quad \& \quad T_1 = (R_p // R_s) C_p$$

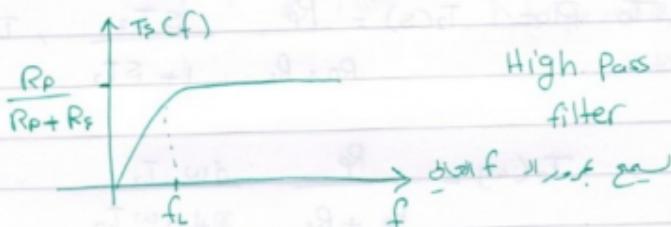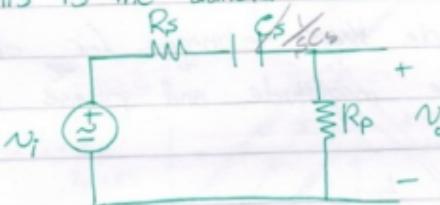- $T_2(s)$: This is the transfer function of this circuit.



$$T_2(s) = \frac{V_o(s)}{V_i(s)}$$

$$V_o(s) = V_i(s) * \frac{R_p}{R_p + R_s + \frac{1}{sC_s}}$$

$$T_2(s) = \frac{SC_s R_p}{1 + (R_p + R_s) C_s} = \frac{(2) V}{(2) + (2) \frac{V}{C_s}} = \frac{2V}{2 + \frac{V}{C_s}}$$

$$(T_2(s) = \left(\frac{R_p}{R_p + R_s} \right) \cdot \frac{s(R_s + R_p)C_s}{1 + (R_s + R_p)C_s s})$$

where $k = \frac{R_p}{R_p + R_s}$ & $T = (R_s + R_p)C_s$

* Bode Plot:-

it is a simple ~~technique~~ technique for obtaining approximate plots of the magnitude and phase of transfer function.


$$\text{To Plot } T_2(s) = \frac{R_p}{R_p + R_s} \frac{sT_2}{1 + sT_2}, \quad T_2 = (R_s + R_p)C_s$$

$$\rightarrow T_2(\omega) = \frac{R_p}{R_p + R_s} \frac{j\omega T_2}{1 + j\omega T_2}$$

$$|T_2(\omega)| = \frac{R_p}{R_p + R_s} \frac{\omega T_2}{\sqrt{1 + (\omega T_2)^2}}$$

$$|T_2(f)| = \frac{R_p}{R_p + R_s} \cdot \frac{2\pi f T_2}{\sqrt{1 + (2\pi f T_2)^2}}$$

$$\left|T_2(f)\right|_{dB} = 20 \log \frac{R_p}{R_p + R_s} + 20 \log 2\pi f T_2 - 20 \log \sqrt{1 + (2\pi f T_2)^2}$$

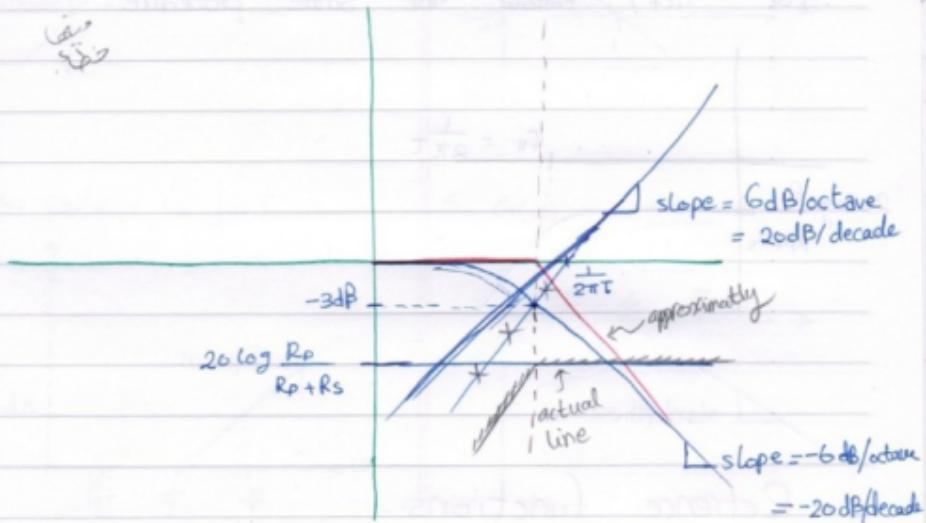

Octave:-

$$20 \log 2 = 6 \text{ dB}$$

$$20 \log 4 \times 2 = 12 \text{ dB} + 6 \text{ dB}$$

$$20 \log 8 \times 2 = 18 \text{ dB} + 6 \text{ dB}$$

$$20 \log 16 \times 2 = 24 \text{ dB} + 6 \text{ dB}$$


• decade:

$$20 \log 10 = 20 \text{ dB}$$

$$20 \log 100 \times 10 = 40 \text{ dB} + 20$$


$$20 \log 1000 \times 10 = 60 \text{ dB} + 20$$

For $T_1(f)$ follow the same procedure.

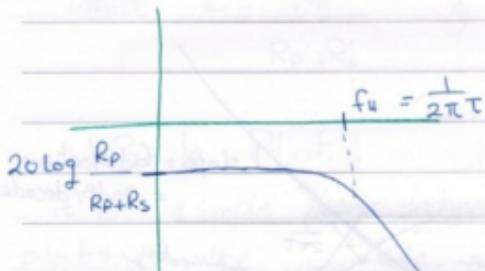


• Reference functions:-


$$\text{i. } T(\omega) = k$$

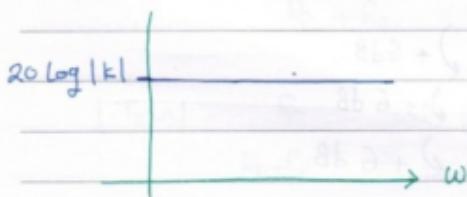

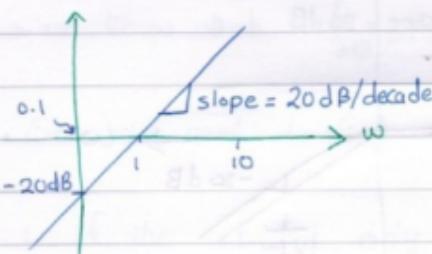
$$2. T(\omega) = \frac{j\omega}{j\omega}$$




$$3. T(\omega) = \frac{1}{j\omega}$$

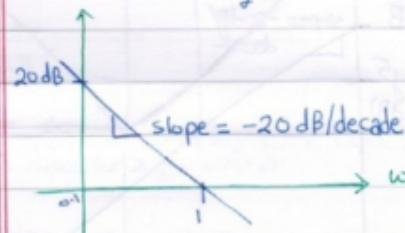

$$4. G(\omega) = 1 + j\omega T$$

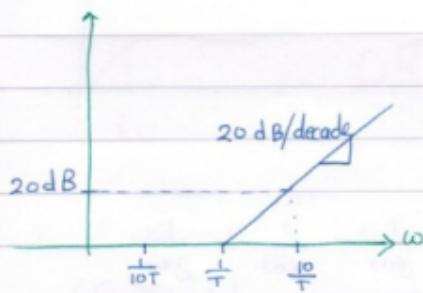

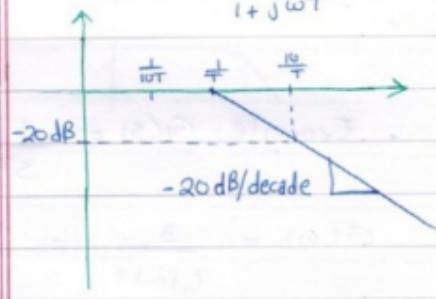
$$5. G(\omega) = \frac{1}{1 + j\omega T}$$



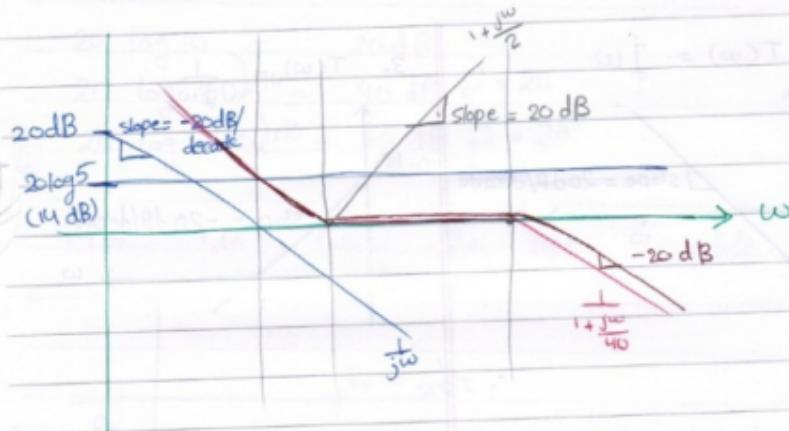• Example:- Plot the following : $G_1(s) = \frac{100(s+2)}{s(s+40)}$


$$G_1(j\omega) = \frac{100(j\omega+2)}{j\omega(j\omega+40)}$$

$$G_1(j\omega) = \frac{100 \times 2 \left(1 + \frac{j\omega}{2} \right)}{j\omega \times 40 \left(1 + \frac{j\omega}{40} \right)} = \frac{5 \left(1 + \frac{j\omega}{2} \right)}{\left(1 + \frac{j\omega}{40} \right)}$$



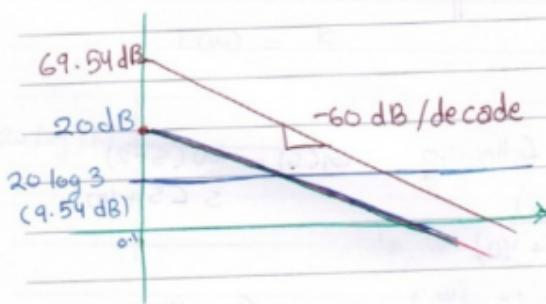Example: $G(s) = \frac{3}{s^3}$

$$G(j\omega) = \frac{3}{(j\omega)^3} = 3 \cdot \frac{1}{j\omega} = \frac{1}{j\omega} = \frac{1}{j\omega}$$



- Short circuit and Open circuit time const.

→ we know that $f_{\text{BP}} = \frac{1}{2\pi T}$


• So, we need to find T (Time constant), How?!

- capacitor \Rightarrow $\text{v} \propto \text{v}_0 e^{-\frac{t}{T}}$


1. if the cct has only one capacitor:

$$T = R_{\text{eq}} C$$

↳ seen by C .

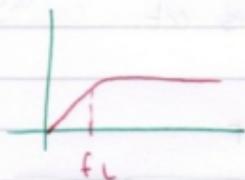


OR

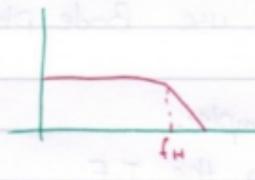

2. if the cct has two capacitors:-

$$(C_1 \gg C_2)$$

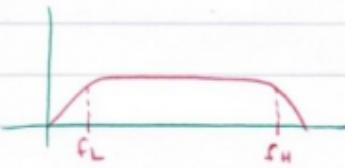

$$T_L = R_{\text{eq}} C_1, \quad Z_C = \frac{1}{j2\pi f C} \approx \infty$$

where C_2 will be open cct

$$\Rightarrow f_L = \frac{1}{2\pi T_L}$$

$$T_H = R_{eq} C_2 \rightarrow Z_C = \frac{1}{j2\pi f} \underset{f \rightarrow \infty}{\rightarrow} 0$$

3. if the cct has more than two capacitor.
or ($C_1 = C_2$)



→ we need to find the transfer function $\frac{V_o(s)}{V_s(s)}$
then use Bode plot to draw this cct.

- Example:-

Draw the T.F

$\frac{V_o(f)}{V_s(f)}$ and Find
the Band width

of the Given cct:

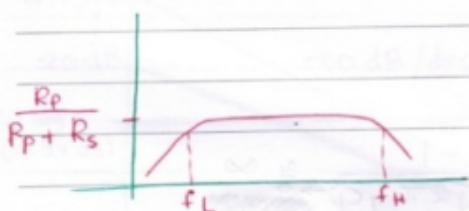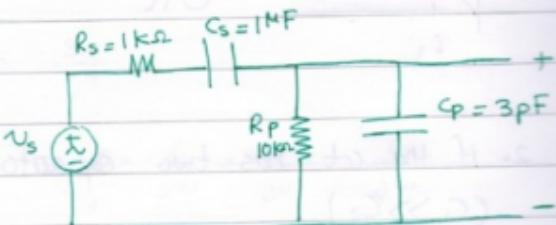

17-4/2014


$$\cdot f_L = \frac{1}{2\pi T_L} , \quad T_L = R_{eq} C_S \quad (C_P : O.C)$$
$$T_L = (R_S + R_P) C_S = 1.1 \times 10^{-2} \text{ sec}$$
$$f_L = 14.5 \text{ Hz}$$

$$\cdot f_H = \frac{1}{2\pi T_H} , \quad T_H = R_{eq} C_P \quad (C_S : S.C)$$
$$T_H = (R_S // R_P) C_P = 2.73 \times 10^9 \text{ sec}$$

$$f_H = 58.3 \text{ MHz}$$

$$\cdot BW = f_H - f_L = 58.3 - 14.5 \text{ MHz}$$


ناتج من محاجنة

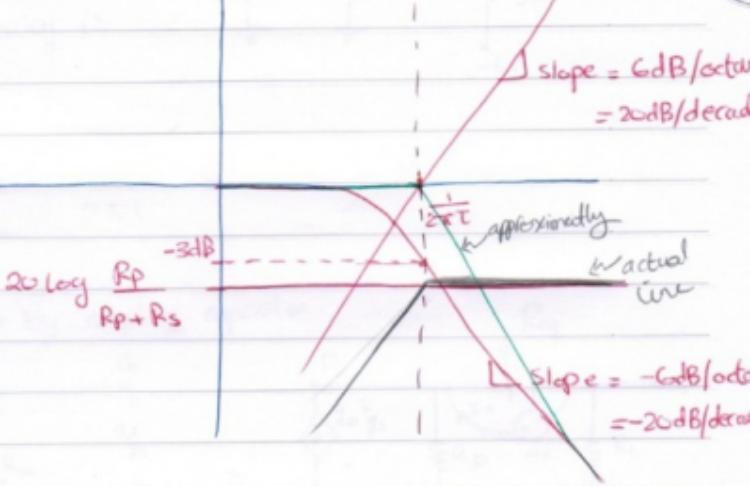

Lecture


20-4-2014

Ex:

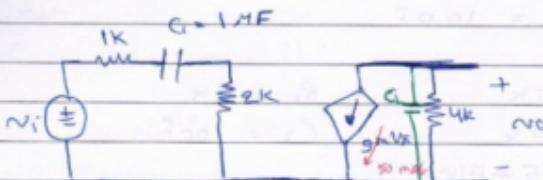

Sketch the bode plot of the transfer function magnitude.

Diagram of transfer function.

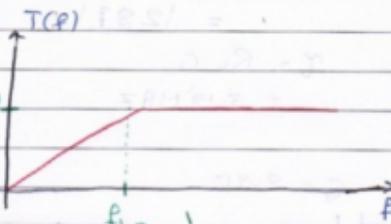

$$\Rightarrow T_{\max}(f) = T(f=f_L) = \frac{N_o}{N_i} = \frac{N_o}{N_i}$$

\downarrow
 C_1 is short circuit

$$N_o = -g_m N_A * 4$$

$$N_A = N_i \frac{2}{2+1}$$

$$\Rightarrow \frac{N_o}{N_i} = -g_m \times R_L \times \frac{2}{2+1} = -133$$

$$|T(f)|_{\max} = 133$$

$$\Rightarrow f_L = \frac{1}{2\pi C} \quad \tau = R_C C$$

$$= 53.1 \text{ Hz} \quad = (1+2) \times 1/4 \\ = 3 \text{ m sec}$$

Ex:- same example . without C_L , assume C_L parallel with $R_L = 10 \text{ pF}$

$$R_s = 0.5 \text{ k}$$

$$R_L = 5 \text{ k}$$

$$V_x = 1.5 \text{ V}$$

$$C_L = 10 \text{ pF}$$


$$g_m = 75 \text{ mA/V}$$

$$|T_{max}(f)| = |T(f_{po})| = g_m \times R_L \times \frac{1.5}{1.5 + 0.5} = 1281$$

$$f_H = \frac{1}{2\pi C}$$

$$\gamma = R_L C \\ = 3.18 \text{ MHz}$$

Ex 2.3

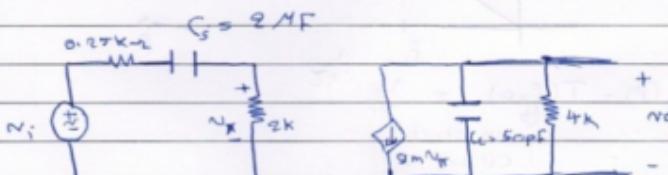

Sketch the Bode plot of the transfer function magnitude


$\Rightarrow C_s \gg C_L$

at low freq $\Rightarrow Z_C = \frac{1}{2\pi f C_L}$ C_L is open circuit
 C_s has an effect

$$P_L = \frac{1}{2\pi C_L}$$

$$T_L = R_{eq} C_s \quad (C_L \text{ open circ}) \\ = 2.25 \times 10^3 \times 2 \times 10^{-6} \\ = 4.5 \text{ msec}$$

$\therefore P_L = 35.4 \text{ Hz}$

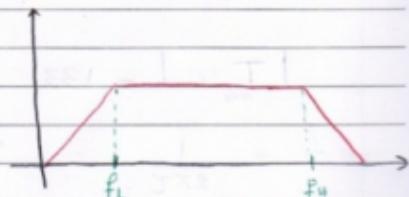

$$f_H = \frac{1}{2\pi L_H}$$


$$L_H = R_{eq} C_L \quad (s : \text{short ch-})$$

$$\begin{aligned} L_H &= 4\pi/8 * 50 \mu H^{-1/2} \\ &= 0.2 \text{ m sec} \end{aligned}$$

$$f_H = 0.796 \text{ MHz}$$

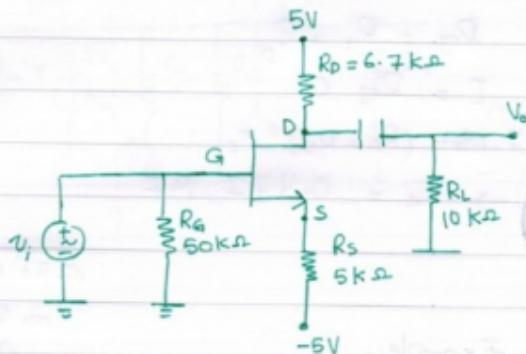Example:-


This circuit is used as audio amplifier, find the value of C_c such that the corner frequency is 20 Hz.



$$f_c = 20 \text{ Hz} = \frac{1}{2\pi T} \rightarrow T = 7.96 \text{ msec}$$

$$T = \frac{R_{eq}}{2\pi f_c}$$

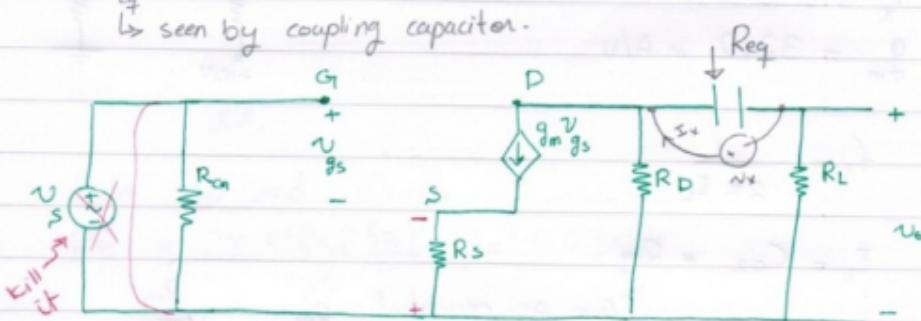\hookrightarrow seen by coupling capacitor -



$$v_{gs} = -R_S \cdot g_m v_{gs}$$

$$v_{gs} (1 + R_S g_m) = 0$$

$v_{gs} = 0$

$$R_{eq} = R_L + R_D$$

$$I = R_{eq} C_C$$

$$7.69 \text{ m} = (R_D + R_L) C_C$$

$$\rightarrow C_C = 0.477 \text{ nF}$$

\Rightarrow is Capacitor at corner

corner J

Example:-


$$B = 100$$

$$V_A = 120 \text{ V}$$

$$C_{C2} = 1 \text{ nF}$$

$$r_\pi = 3.10 \text{ k}\Omega$$


$$g_m = 32.2 \text{ mA/V}$$

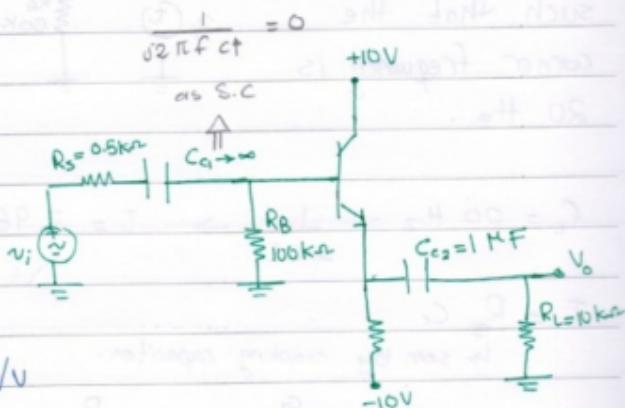


$$f_L = \frac{1}{2\pi R_L}$$

$$I_L = C_{C2} * R_{eq}$$

\hookrightarrow from AC equivalent

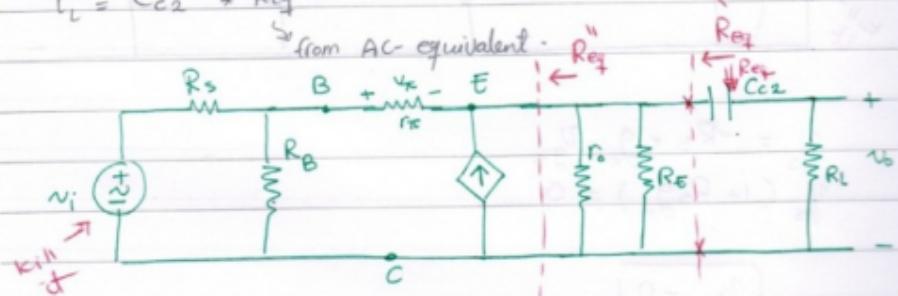

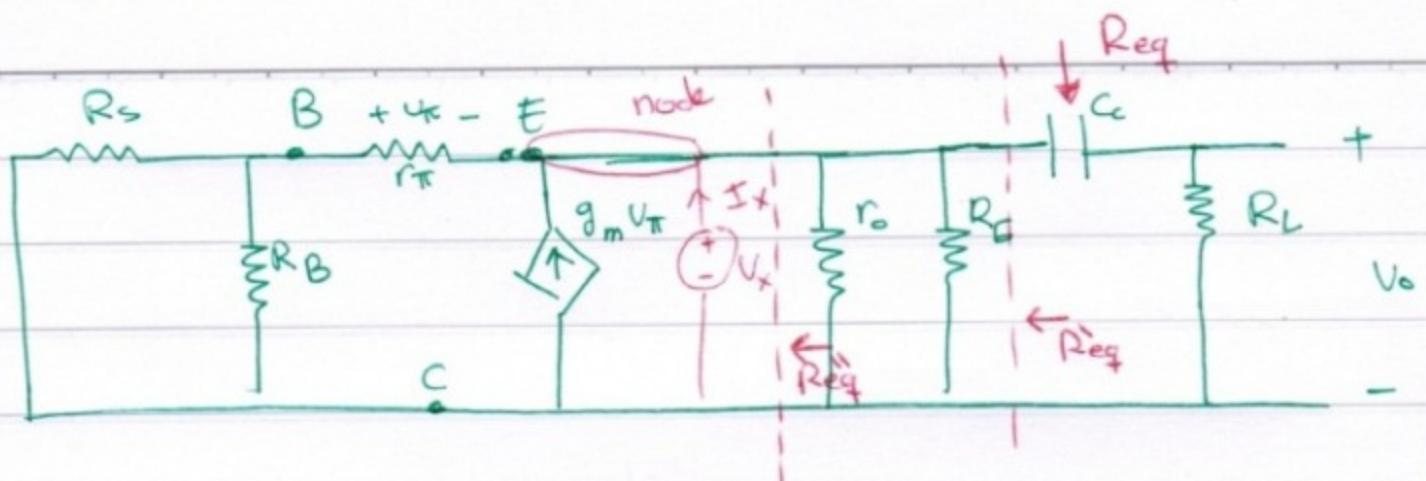

$$R_{\text{req}} = R_L + R_{\text{req}}$$

KCL at node E:

$$I_x + g_m V_\pi = - \frac{V_x}{r_\pi} \rightarrow (1)$$

$$V_\pi = - V_x \frac{r_\pi}{r_\pi + (R_B // R_s)} \rightarrow (2)$$


$$R_{\text{req}} = \frac{V_x}{I_x}$$

from (2) and (1) \rightarrow

$$R_{\text{req}} = \frac{V_\pi + (R_s // R_B)}{1 + \beta} = 0.0356$$

$$\rightarrow R_{\text{req}} = 35.6 \Omega$$
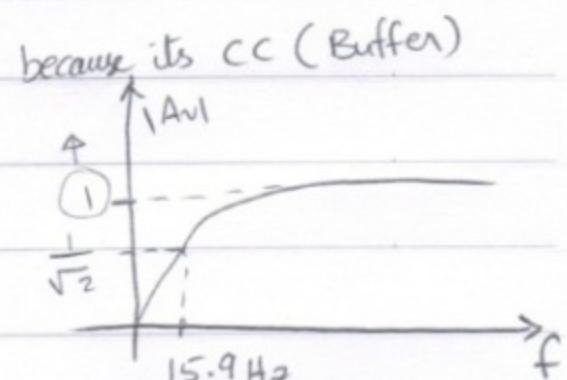
$$f_L = \frac{1}{2\pi T_L} = 15.9 \text{ Hz}$$





© Power Unit


Mo3ath A7MAD

24-4/2014

Time Response :-

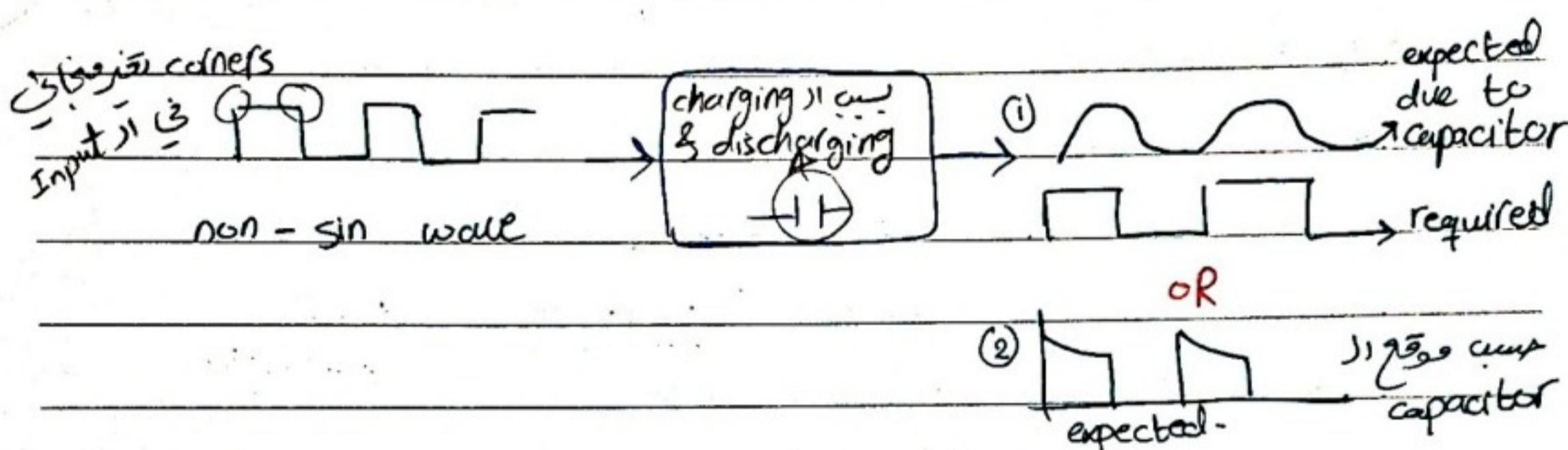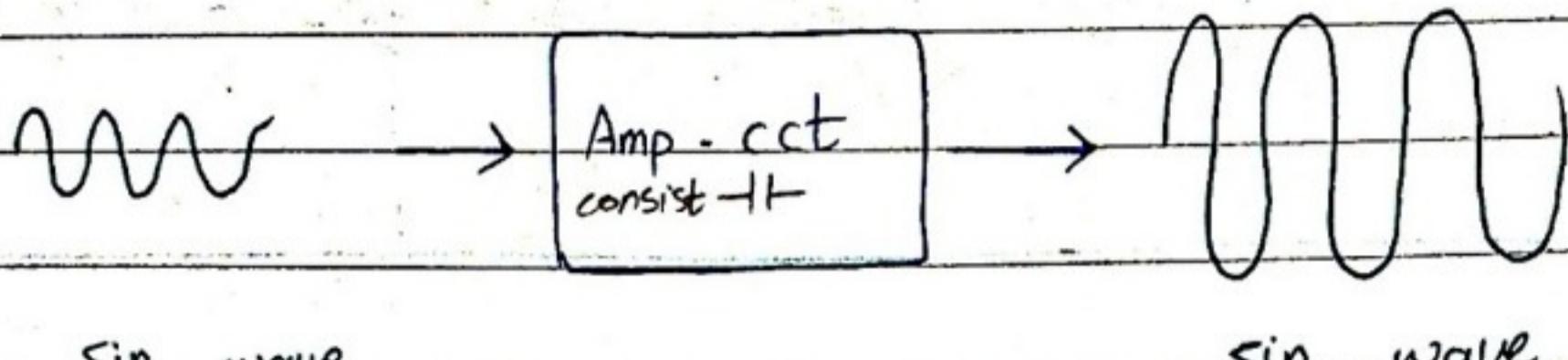

Consider the following cct :-

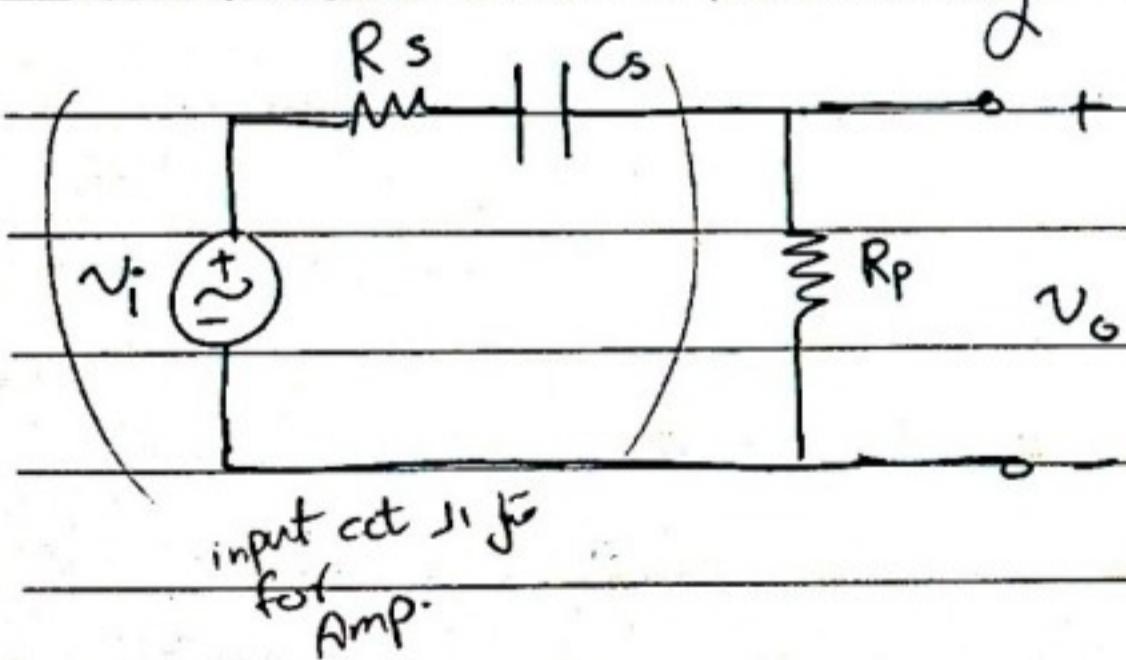


$$\frac{v_o(s)}{v_i(s)} = \frac{R_p}{R_p + R_s} = \frac{s(R_s + R_p)C_s}{1 + s(R_s + R_p)C_s}$$

$$T(s) = \frac{v_o(s)}{v_i(s)} = k_2 \frac{s T_2}{1 + s T_2}$$

24/4/2014 Thu.

if $V_i(t) = u(t)$: unit step function.

$$V_i(t)$$

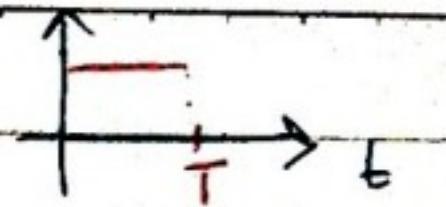

what is $V_o(t)$?!

$$V_o(s) = V_i(s) T(s)$$



$$V_o(s) = \frac{1}{s} \cdot k_2 \frac{sT_2}{sT_2}$$

by Laplace Transform $1 + sT_2$

$$V_o(s) = k_2 \frac{T_2}{1 + sT_2}$$

inverse
Laplace Transform

$$V_o(t) = k_2 e^{-\frac{t}{T_2}}$$

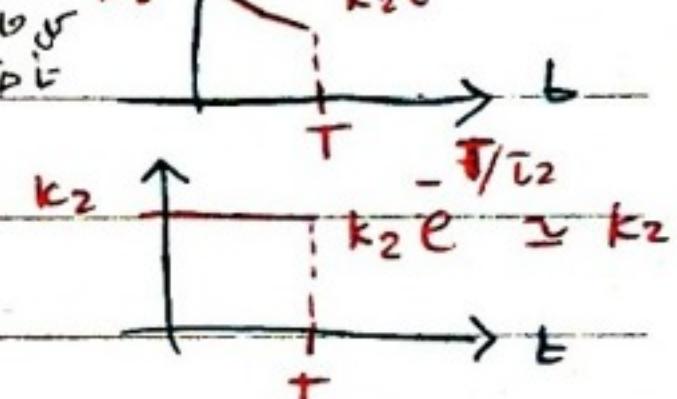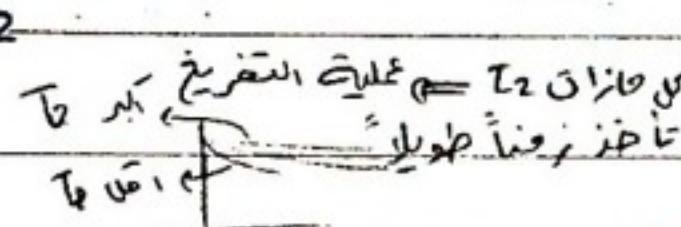

But the required $V_o(t)$: and

to get it \Rightarrow

$$k_2 \approx k_2 e^{-\frac{t}{T_2}}$$

$$-\frac{t}{T_2}$$

$$e^{-\frac{t}{T_2}} \approx 1$$

$\frac{t}{T_2}$ very small value.

min value to get

$$\Rightarrow T_2 \gg T$$

$$C_s$$


$$C_s(R_s + R_p) \gg T$$

$$T_2 = 10T$$


should be very large.

$$T_2 \geq 10T$$

$$f_{Vi} = \frac{1}{2T}$$

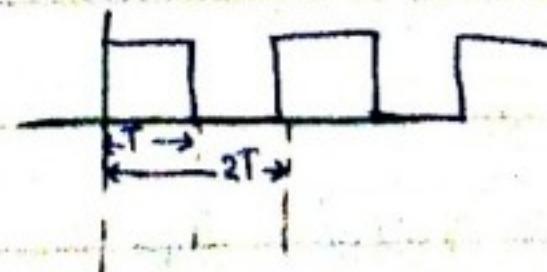

- consider the following cct:-

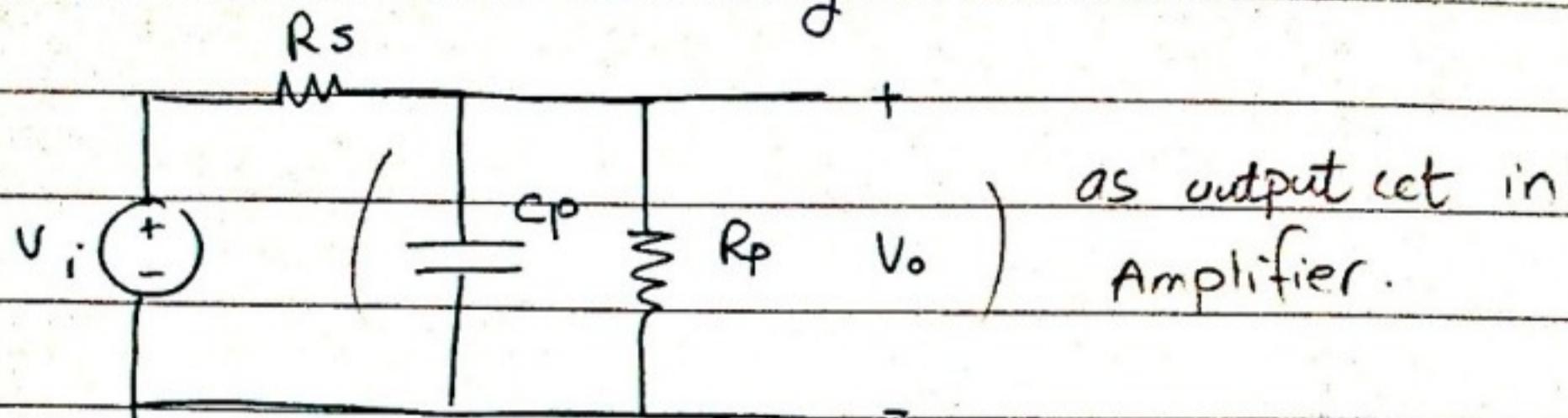

$$\frac{V_o(s)}{V_i(s)} = \frac{R_p}{R_p + R_s} \cdot \frac{1}{1 + s(R_s // R_p) C_p}$$

$$= K_1 \cdot \frac{1}{1 + sT_1}$$

→ if the input $v_i(t) = u(t)$
what is the output?

$$V_o(s) = V_i(s) \cdot T(s)$$

$$= \frac{1}{s} \cdot \frac{K_1}{1 + sT_1}$$


$$V_o(s) = \frac{K_1}{s} \cdot \frac{1}{1 + sT_1} \xrightarrow[\text{Transform } v_o(t)]{\text{inverse Laplace}} V_o(t) = K(1 - e^{-t/T})$$

- To get the required $V_o(t)$:

$$T_1 \ll T$$

$$C_p (R_p // R_s) \ll T$$

→ we need C_p to be very small value.

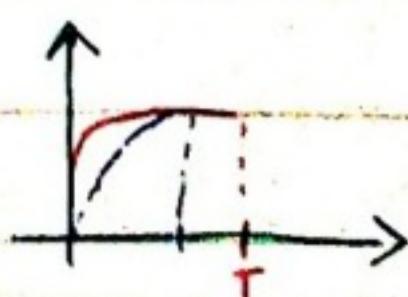


24/4/2014 Thu.

Time Response & frequency Response.


$$T \leftarrow \frac{T}{10}$$

Time-Response لـ $\frac{1}{10}$

T.F. انوار تـ $\frac{1}{10}$ اـ

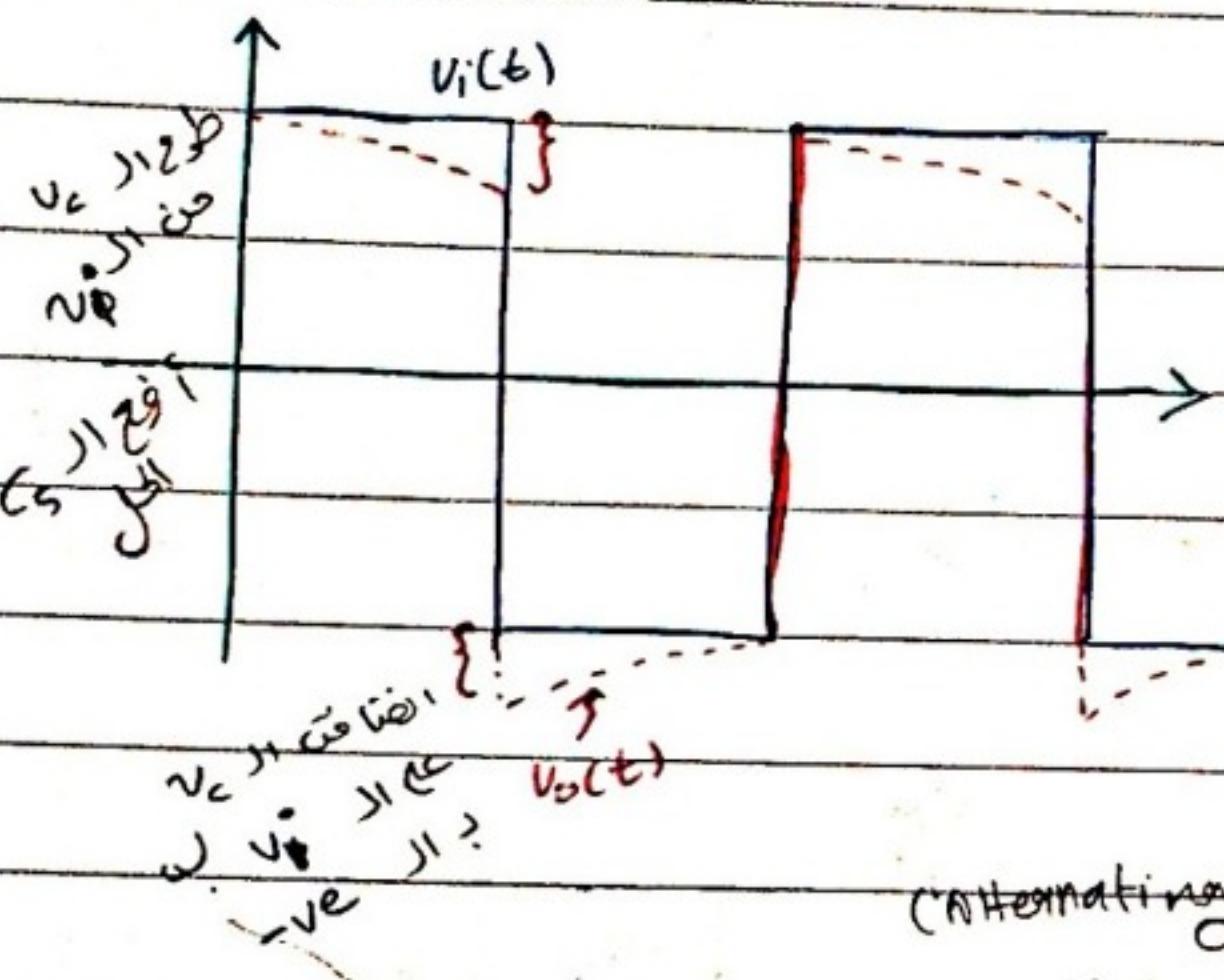



for the first cct:

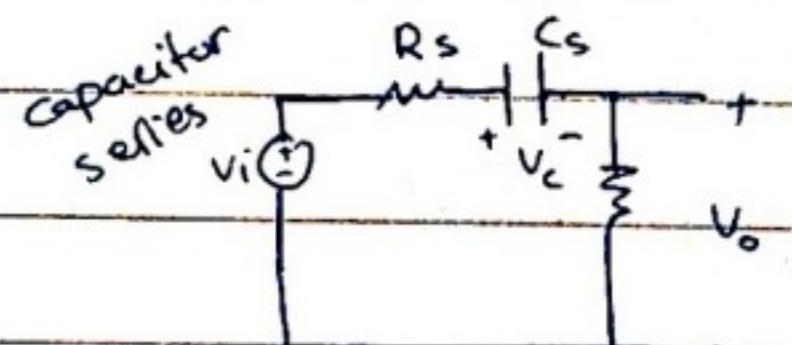

$$-v_i + v_c + v_o = 0$$

$$v_o = v_i - v_c$$

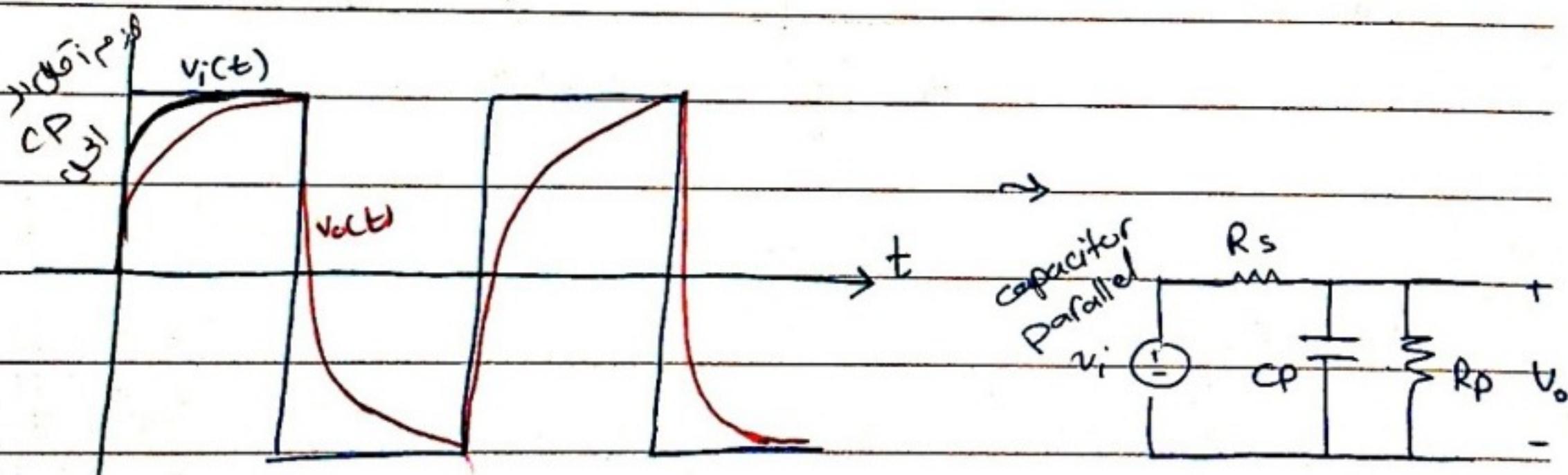


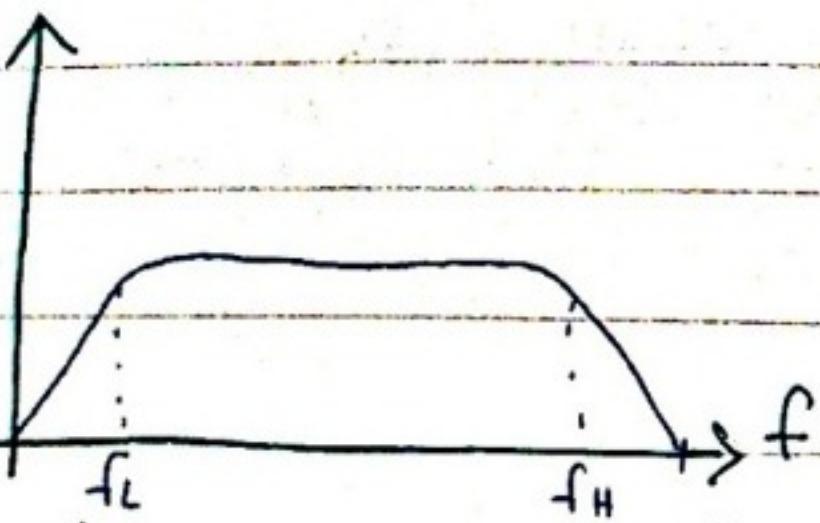


due to coupling
and bypass
capacitor

due to
transistor

and load capacitor parallel to R_L

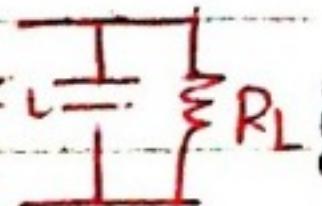

Transistor capacitor:

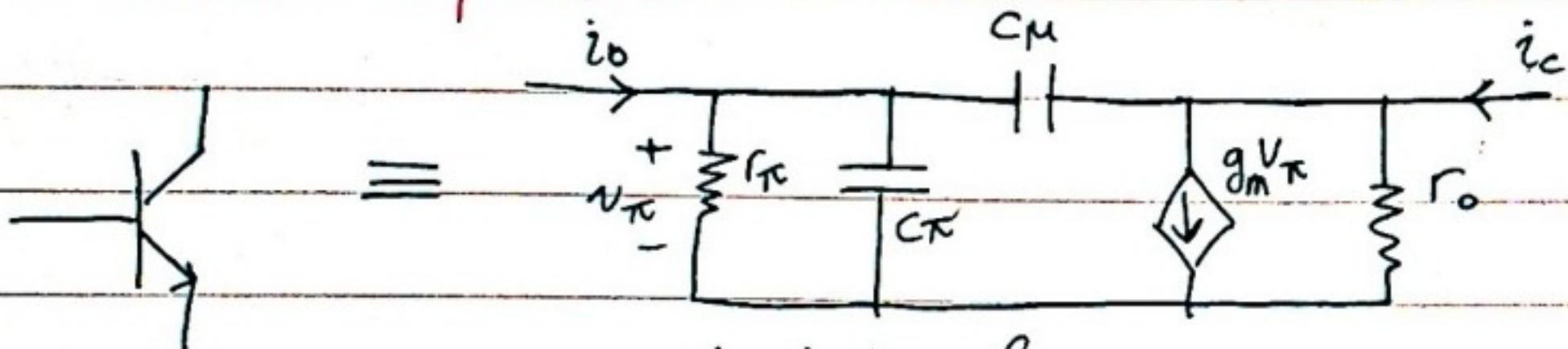

at high frequency.


→ DC, low, mid frequency ranges:

$$i_c = \beta i_b$$

$$\text{at high frequency: } i_c = h_{fe} i_b$$

where h_{fe} : small signal current gain.


or ~~or~~ short-cct. current gain

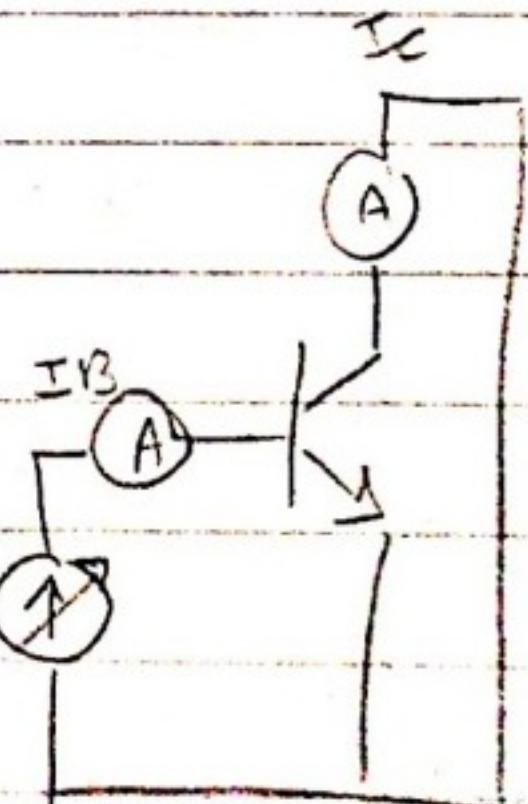

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

27-4/2014 Sun.

$$i_c = g_m v_{\pi} \sqrt{\kappa}$$

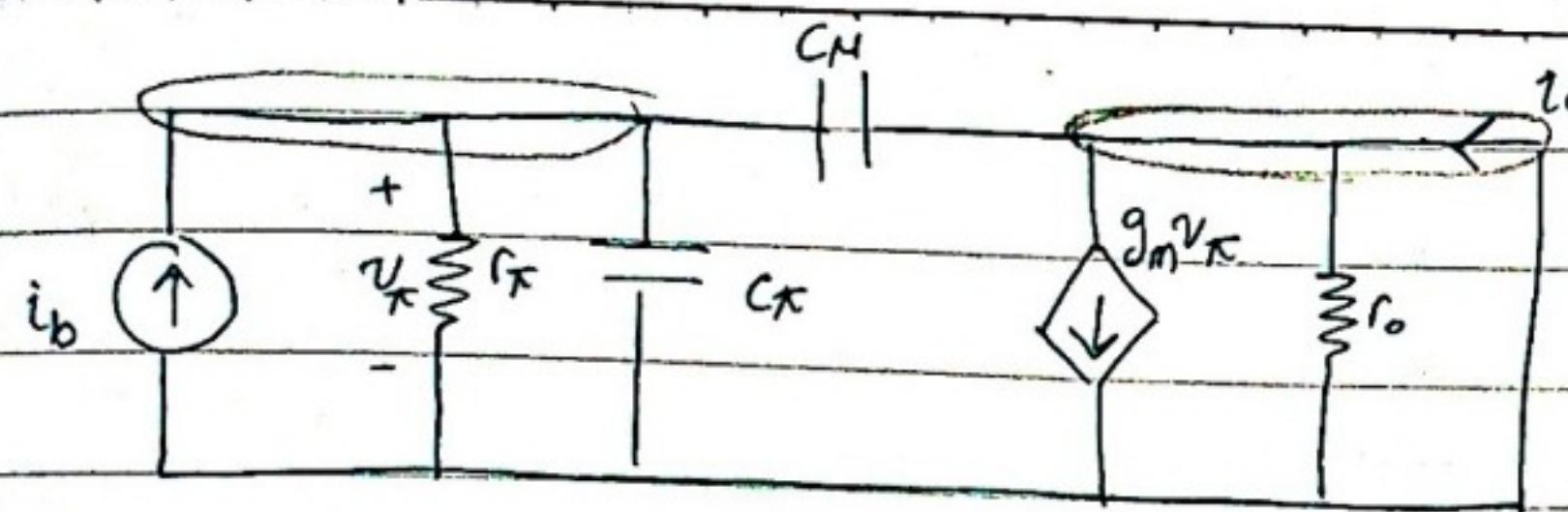

$$h_{fe} = \frac{i_c}{i_b}$$

• KCL at the input node:

$$i_b = \frac{v_{\pi}}{r_{\pi}} + \frac{v_{\pi}}{(1/j\omega C_{\pi})} + \frac{v_{\pi}}{(1/j\omega C_M)}$$

$$i_b = v_{\pi} \left(\frac{1}{r_{\pi}} + j\omega (C_{\pi} + C_M) \right) \rightarrow ①$$

• KCL at the output node:

$$g_m v_{\pi} = i_c + \frac{v_{\pi}}{(1/j\omega C_M)}$$

$$v_{\pi} = \frac{i_c}{(g_m - j\omega C_M)} \rightarrow ②$$

Sub ② in ①:

$$h_{fe} = \frac{g_m - j\omega C_M}{\frac{1}{r_{\pi}} + j\omega (C_{\pi} + C_M)} = \frac{i_c}{i_b}$$

for typical values :-


$$C_N = 0.2 \text{ pf}$$

$$g_m = 50 \text{ mA/V}$$

$$f_{\max} = 100 \text{ MHz}$$

$$\Rightarrow \omega C_N \ll g_m$$
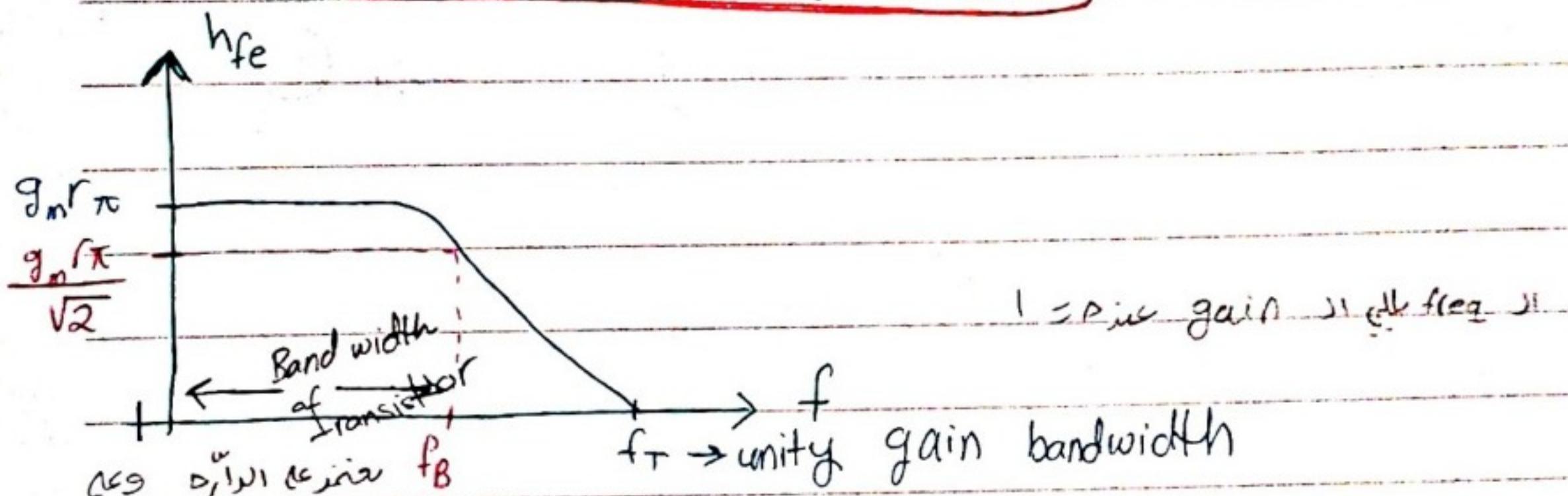
$$\text{So, } h_{fe} \approx \frac{g_m r_\pi}{1 + j\omega r_\pi(C_\pi + C_N)} \approx k \frac{1}{1 + ST}$$



DC-cct (f_B) \rightarrow beta cutoff frequency

$$f_B = \frac{1}{2\pi\tau} = \frac{1}{2\pi r_\pi (C_\pi + C_N)}$$

• f_T ?

$$|h_{fe}(f_T)| = 1$$

$$\left| \frac{g_m r_\pi}{1 + j \left(\frac{f_T}{f_B} \right)} \right| = 1$$

27-4/2014 Sun.

$$\frac{g_m f_T}{\sqrt{N_f + \left(\frac{f_T}{f_B}\right)^2}} = 1$$


$$\begin{aligned} \cdot \frac{j f_T}{f_B} &= j \frac{f_T}{\frac{1}{2\pi C_T (C_{\pi} + C_{\mu})}} \\ &= j 2\pi f_T (C_{\pi} + C_{\mu}) f_T \end{aligned}$$

$$\cdot \text{usually } f_T \gg f_B \Rightarrow$$

$$\frac{f_T}{f_B} = \beta$$

gain * Bandwidth = const.

$$\therefore f_T = \beta f_B$$

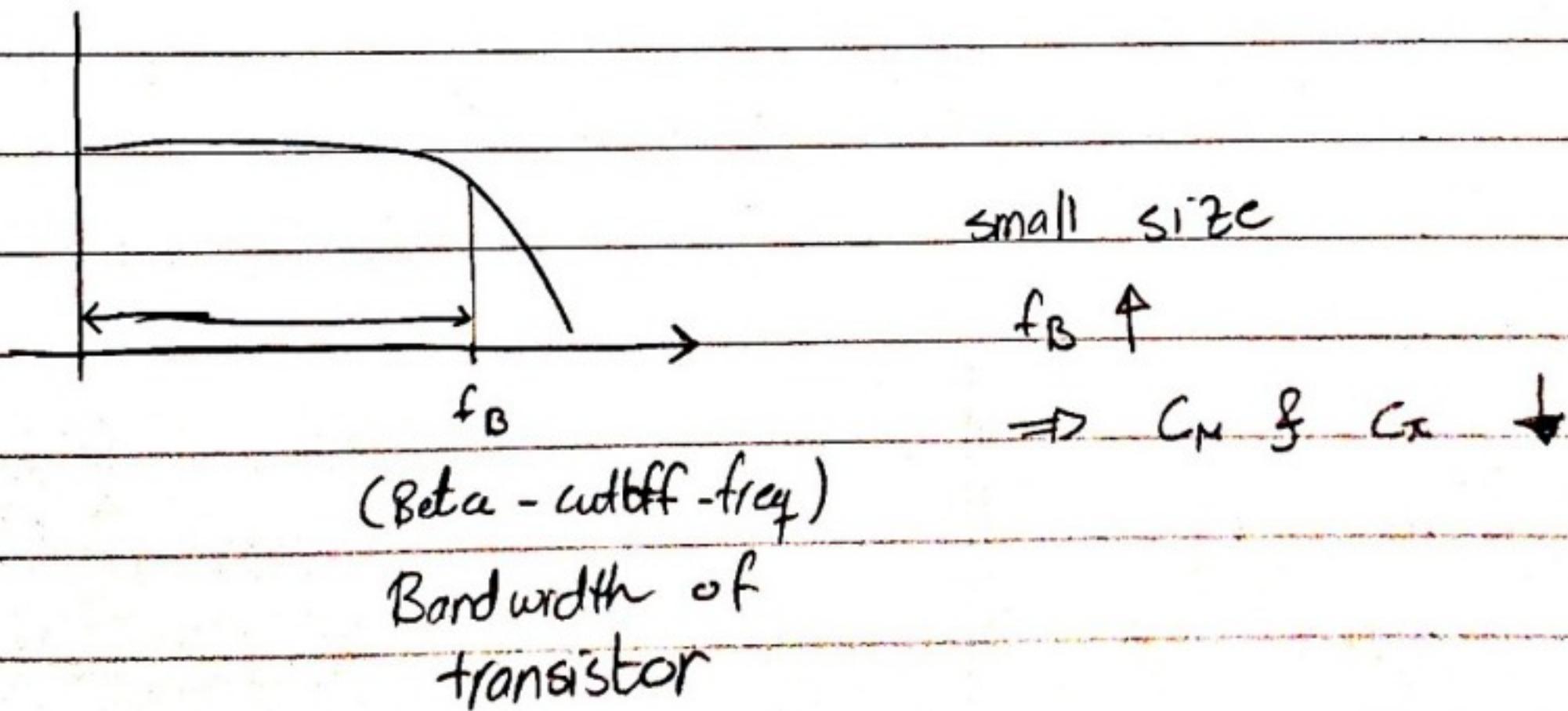

* Example Find the 3dB freq of the short cct
current gain of BJT with $r_\pi = 2.6 \Omega$, $C_\pi = 2 \text{ pF}$
 h_{fe}

$$C_N = 0.1 \text{ pF}$$

$$f_B = \frac{1}{2\pi r_\pi (G_\pi + C_N)} = 29.1 \text{ MHz}$$

* Example Find C_π for the BJT given that:

$$I_{CQ} = 1 \text{ mA}$$

$$f_T = 500 \text{ MHz}$$

$$\beta = 100$$

$$C_N = 0.3 \text{ pF}$$

$$f_T = \beta f_B \rightarrow f_B = 5 \text{ MHz}$$

$$f_B = \frac{1}{2\pi r_\pi (G_\pi + C_N)} \Rightarrow C_\pi = 11.9 \text{ pF}$$


$$\frac{\beta V_T}{I_{CQ}}, V_T = 0.026 \text{ V}$$

Note:-



$$1 - f_T \gg f_B$$

$$2 - C_N \ll C_\pi$$

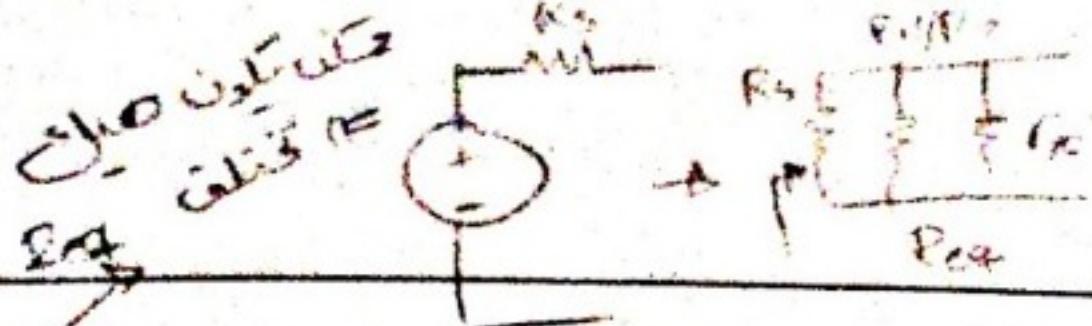* $C_N \ll C_\pi$, But we can't neglect C_N due to
Miller effect.



29-4/2014 Tue.

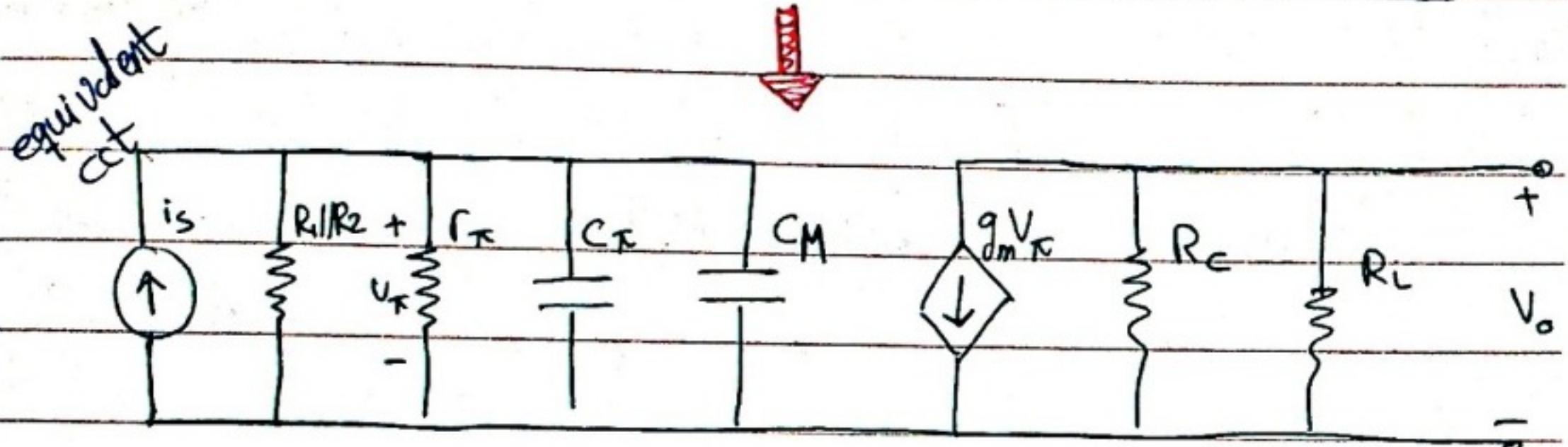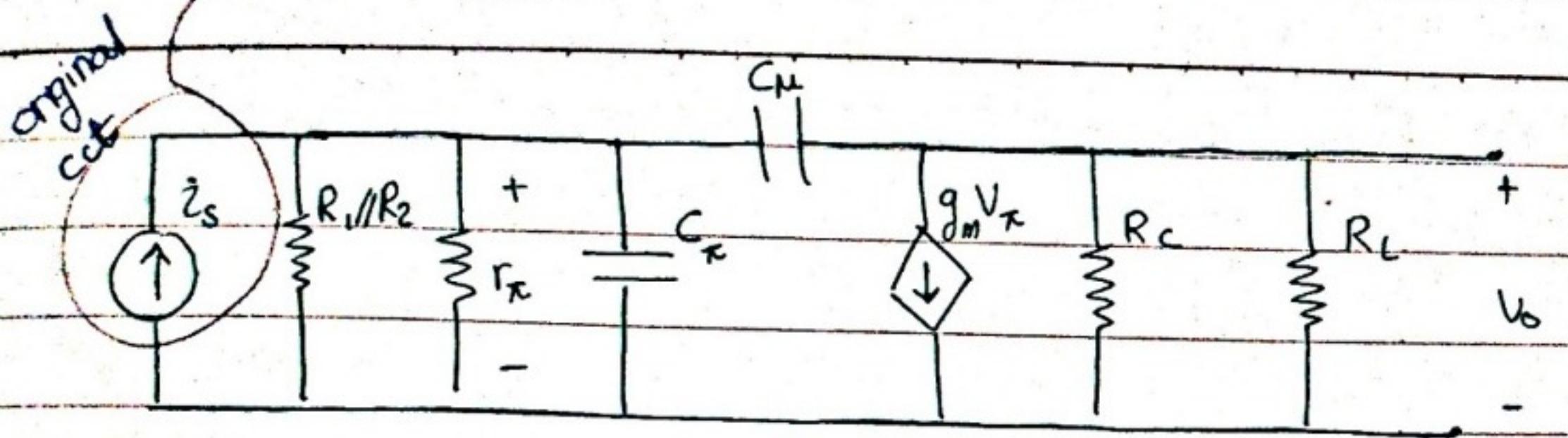

$$C_M = C_M \times \left[1 + g_m (R_C // R_L) \right]$$

→ Miller effect (OR feedback effect)

Miller Capacitance

$$f_{3dB} = \frac{1}{2\pi T}, \quad T = R_{eq} C_{eq}$$

Example If $R_C = R_L = 4 k\Omega$, $r_\pi = 2.6 k\Omega$

$R_1 // R_2 = 200 k\Omega$, $C_\pi = 4 \text{ pF}$, $C_M = 0.2 \text{ pF}$

$g_m = 38.5 \text{ mA/V}$, find: f_{3dB} for this cct.

① if we consider the Miller effect:

$$f_{3dB} = \frac{1}{2\pi T} = \frac{1}{2\pi R_{eq} C_{eq}}$$

$$= \frac{1}{2\pi (R_1 // R_2 // r_\pi) (C_\pi + C_M)} = 3.16 \text{ MHz}$$

$$\frac{1}{2\pi (R_1 // R_2 // r_\pi) (C_\pi + C_M)} \approx 15.6 \text{ pF}$$

29-4/2014

• f_{3dB} = $\frac{1}{2\pi(R_1 + R_2 + r_s)C_{\pi}}$

f_{3dB} \downarrow J. J. J.

do not


② if we consider the Miller effect ($C_H \neq 0$)

$$f_{3dB} = \frac{1}{2\pi(R_1 + R_2 + r_s + g_m C_H)C_{\pi}} = 15.5 \text{ MHz}$$

$C_H: \text{O.C}$
 $\rightarrow C_H = C_o * (\dots)$
 $\Rightarrow C_H = 0$

• f_{3dB} | $\ll f_{3dB}$ | without Miller ösl. & ögf.
 Miller * * * * * Mid ||

• FET at high frequency:

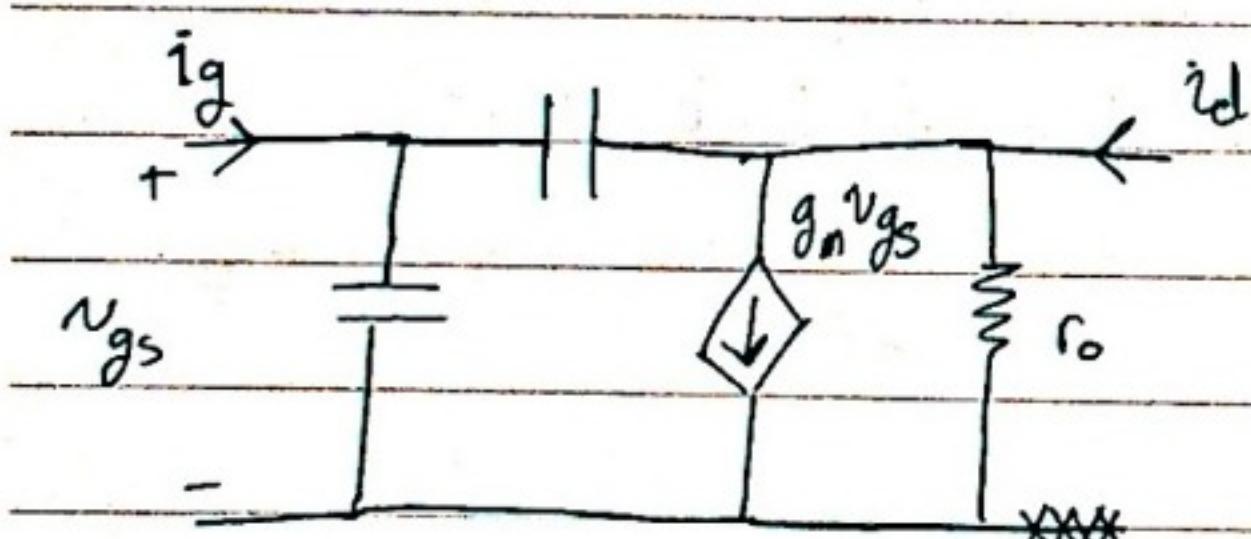


in DC $\rightarrow I_G = 0$

low f Midband $\rightarrow I_G = 0$

high frequency $\rightarrow ?!$

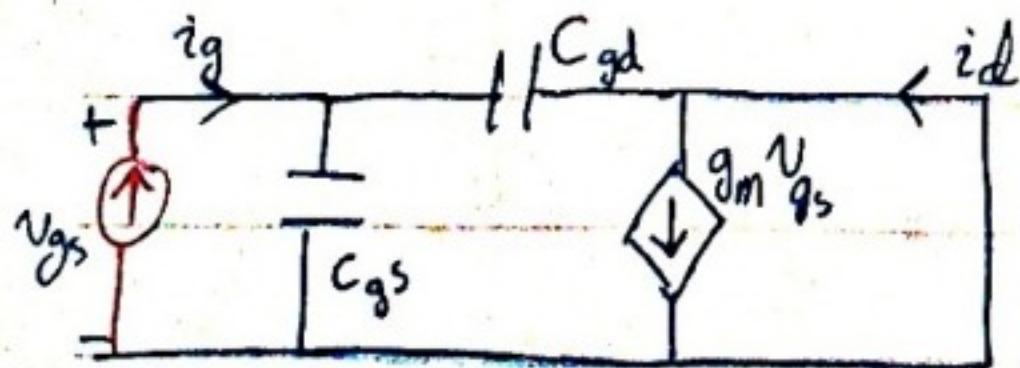* We calculate the short cct current gain:



$$A_i = \frac{i_d}{i_g}$$

29-4/2014 Tue

$$A_i = \frac{g_m - j\omega C_{gd}}{j\omega (C_{gs} + C_{gd})}$$

if we consider the typical values $C_{gd} = 0.05 \text{ pF}$
 $g_m = 1 \text{ m.A/V}$

$$\rightarrow g_m \gg \omega C_{gd}$$


$$A_i = \frac{g_m}{j\omega (C_{gs} + C_{gd})}$$

→ unity gain bandwidth :-

$$f_u = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

• Operational Amplifier (op-amp)

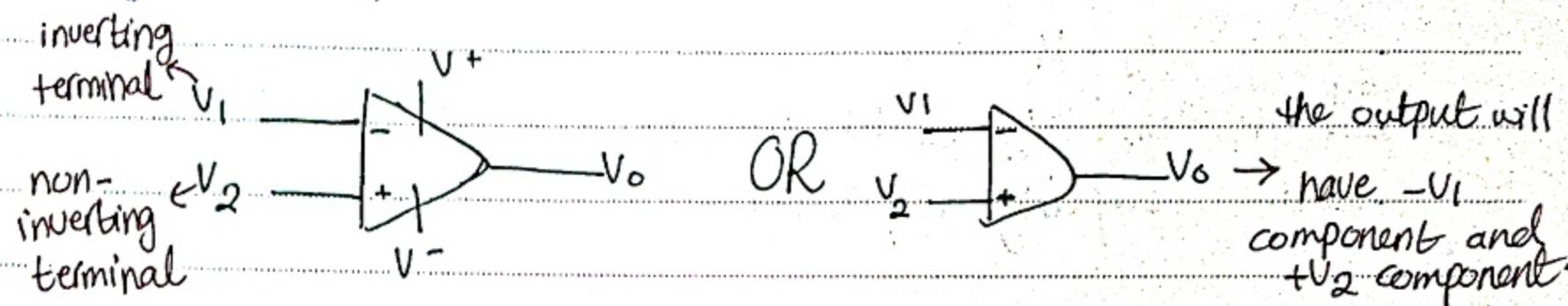it is an integrated cct (IC) that amplifies the difference between two input voltage produces a signal output.




• Name, why "operational"?

it was used in analog computers to perform mathematical operations to solve differential and integral equations.

* Ideal op-amp \rightarrow will be considered usually

* non-ideal op-amp

• Ideal op-amp:-

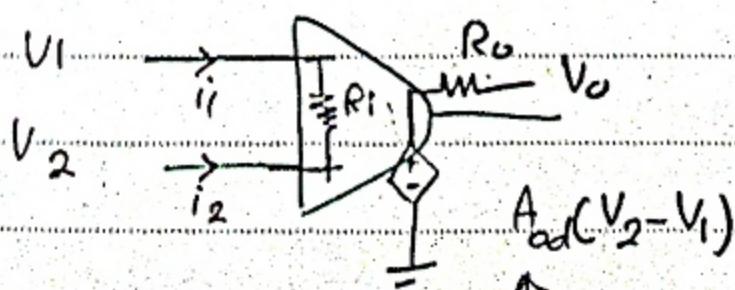

$$A_{od}(V_2 - V_1)$$

open loop
differential
voltage gain

$$\boxed{1} R_i = \infty \Omega$$

$$\boxed{2} R_o = 0 \Omega$$

$$\boxed{3} i_1 = i_2 = 0 A$$

$$\boxed{4} A_{od} = \infty$$


$$\Rightarrow V_2 - V_1 = 0$$

$$\therefore V_2 = V_1$$

$\boxed{5}$ V_1 and V_2 could be DC or AC, and we need coupling capacitor.

• OP-amp Applications-

1] inverting amplifier

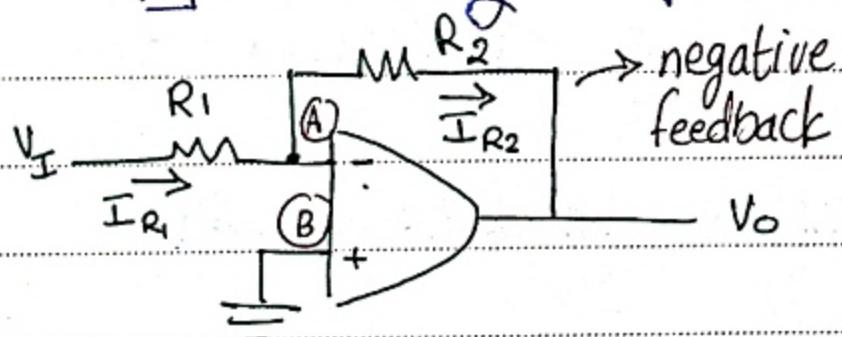

$$\text{at } A: V_A = 0$$

$$i_1 = 0$$

$$\text{at } B: V_B = V_I$$

$$I_2 = 0$$

$$I_{R_1} = I_{R_2}$$

$$\frac{V_I - 0}{R_1} = \frac{0 - V_O}{R_2}$$

$$\rightarrow \frac{V_O}{V_I} = -\frac{R_2}{R_1}$$

$$V_O = V_I \left(-\frac{R_2}{R_1} \right)$$

* Point (A) is:


an virtual ground
cause it gave $V_A = 0$
 $\& I_1 = 0$

• feedback:-

negative feedback: it result in stable circuit

positive feedback: it is used to produce oscillators.

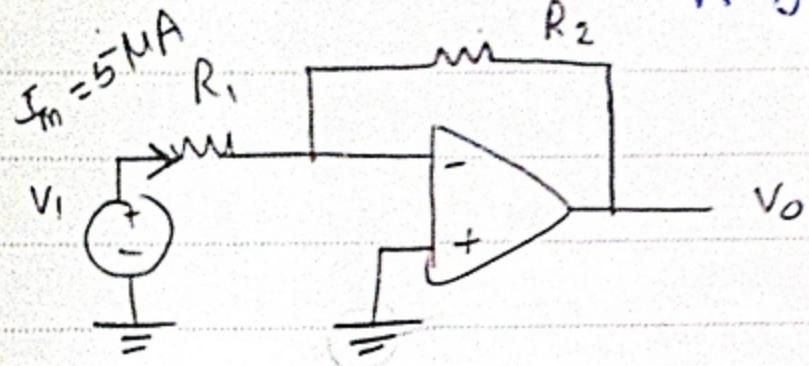Example:- Design an inverting amp. such that the voltage gain $A_v = -5$, knowing that this ~~is~~ cct is connected with a src that have $v_s = 0.18 \sin \omega t$ V and this src can supply maximum current of 5 mA.




$$A_v = -\frac{R_2}{R_1} = -5$$

$$R_2 = 5 R_1$$

$$I_m = \frac{V_{s(\max)} - 0}{R_1}$$

$$\rightarrow R_1 = 20 \text{ k}\Omega$$


$$\therefore R_2 = 100 \text{ k}\Omega$$

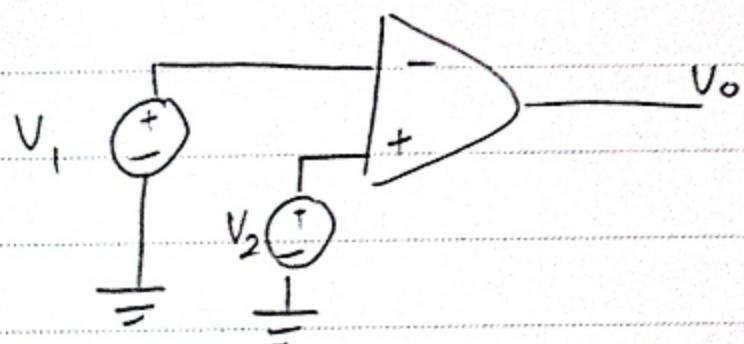


(comparator)

if $V_2 > V_1 \rightarrow V_o +ve$

if $V_2 < V_1 \rightarrow V_o -ve$


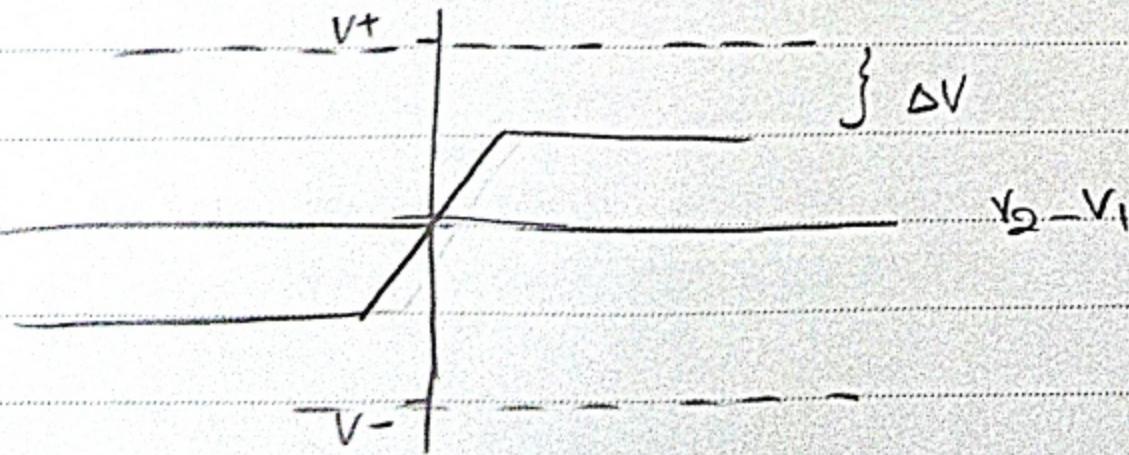


8 / 5 / 2014

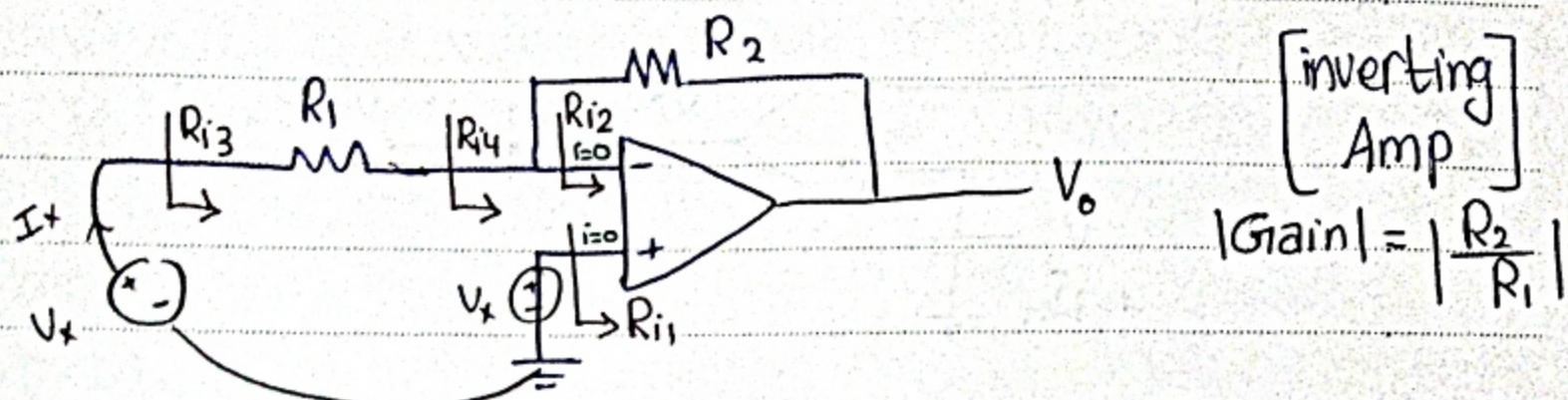



$$\frac{V_o}{V_i} = -\frac{R_2}{R_1}$$

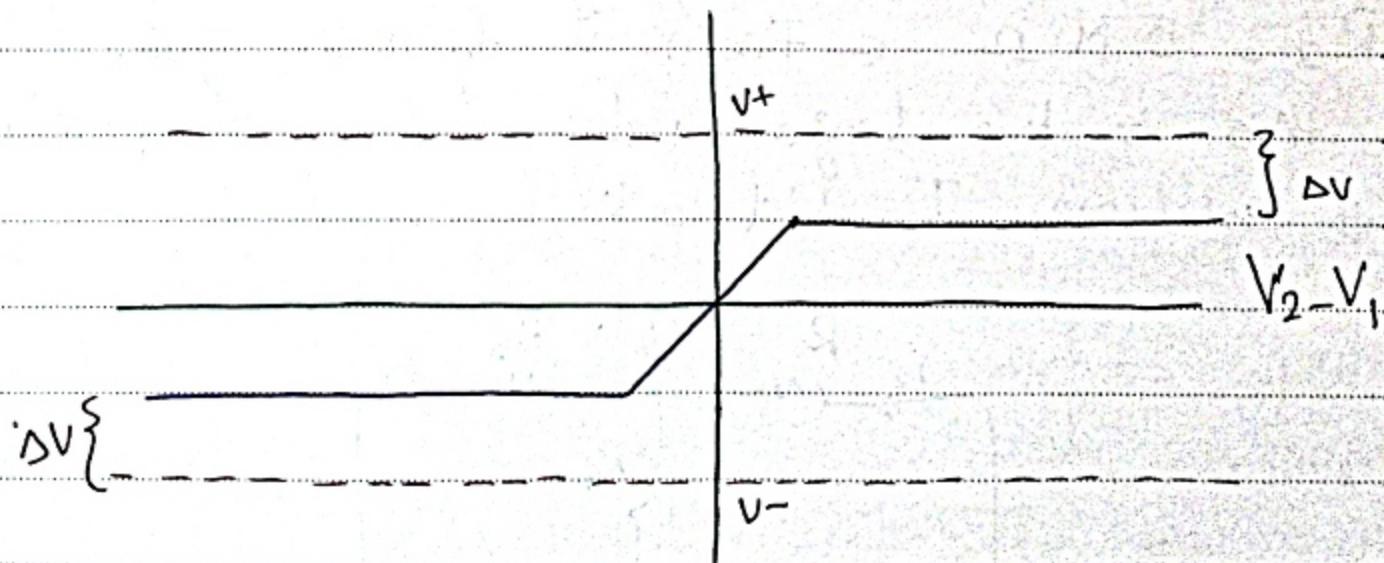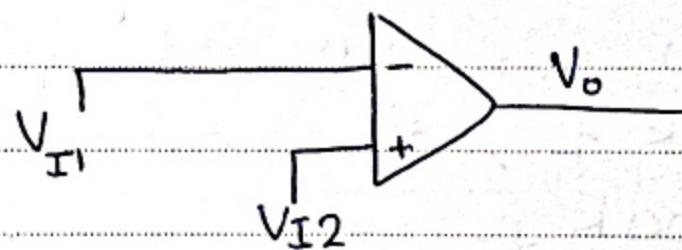- $R_{ii} = \infty$
- $R_{i2} = \infty$, $\frac{V_x}{I_x} = \frac{V_x}{0} = \infty$
- $R_{i3} = R_1$
- $R_{i4} = \frac{V_x}{I_x} = 0$



V_o of an op-amp cct is always between
 $V^- + \Delta V \leq V_o \leq V^+ - \Delta V$

* Compartor:-

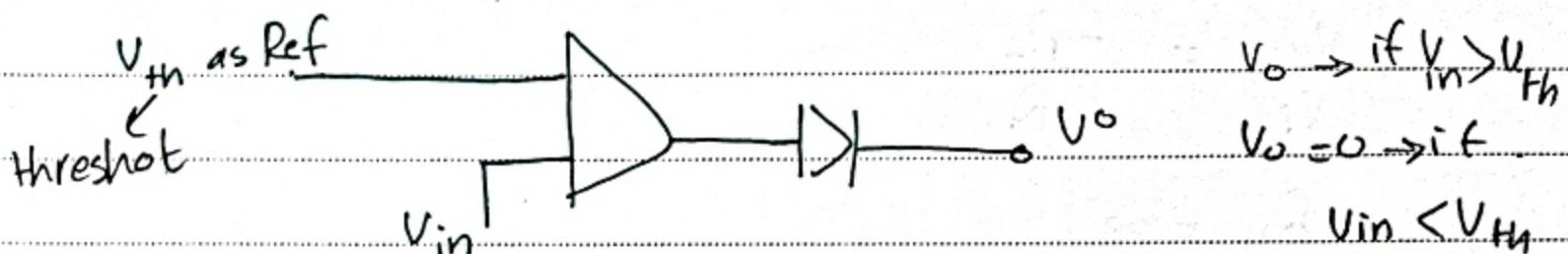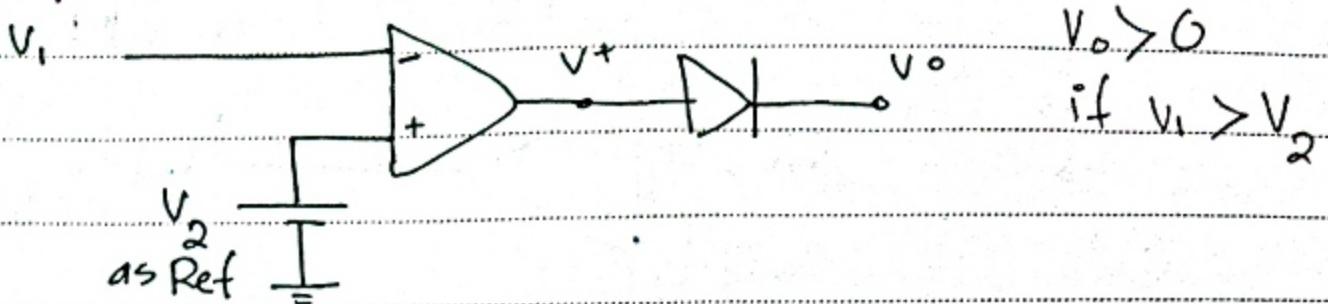

- Application:- Amplifier with T-Network.

why do we need T-Network?!


answer: if we want to design an inverting amplifier with $A_v = -100$ and input impedance of $R_i = 50 \text{ k}\Omega$, then we need:

$$R_1 = R_2 = 50 \text{ k}\Omega$$

$R_2 = 5 \text{ M}\Omega$ ← finding it from the gain.

→ this is too large value for most practical circuit.

⇒ Solution: T-Network

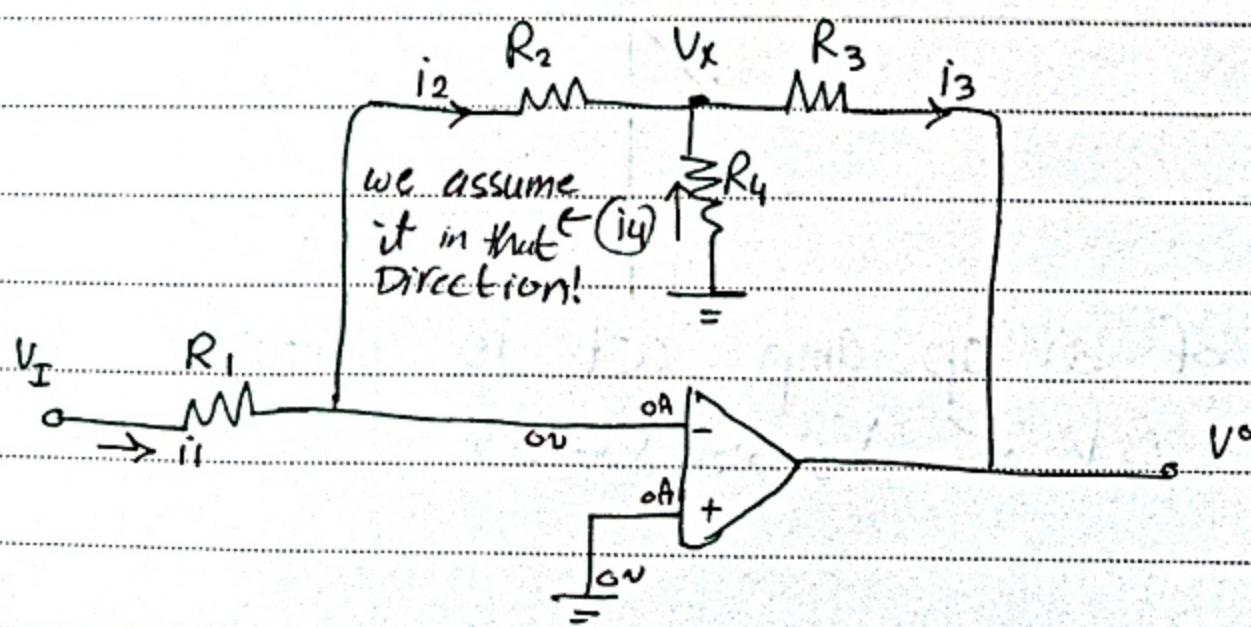

8/5/2014

$$i_2 = i_1$$

$$\frac{V_I}{R_1} = \frac{0 - V_x}{R_2}$$

requirements } Gain \uparrow \rightarrow loading effect \downarrow
 $R_i \uparrow$ $\therefore R_2$ will be \uparrow

$$\rightarrow V_x = \frac{-R_2}{R_1} V_i \rightarrow ①$$

@ node x:

$$i_2 + i_4 = i_3$$


$$-\frac{V_x}{R_2} - \frac{V_x}{R_4} = \frac{V_x - V_o}{R_3}$$

$$V_x = \left(\frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_3} \right) = \frac{V_o}{R_3} \rightarrow ②$$

sub ② in ①:

$$A_v = \frac{V_o}{V_i} = \frac{-R_2}{R_1} \left(1 + \frac{R_3}{R_4} + \frac{R_3}{R_2} \right)$$

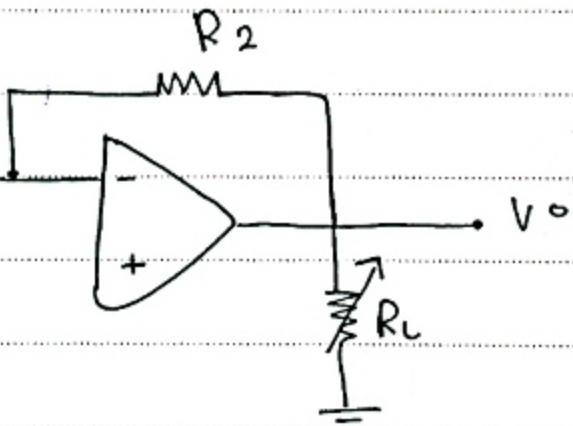inverting input signal on ve
 $\frac{1}{R_1} \parallel R_2$



$$A_v = -\frac{R_2}{R_1}$$

will not change
with R_L

non-ideal

$$A_{od} = \infty \quad R_i = \infty \quad R_o = 0$$

Ideal OP-amp:- if is assumed to simplify the analysis and design non-ideal op-amp but the final will be similar to the non-ideal op-amp.


J to C5 via
coupling capacitor
at input and output !!.

8/5/2014

- Example:- if we assume that $A_{od} \neq \infty$

$$\rightarrow V_2 \neq V_1 \quad R_i = \infty \quad R_o = 0$$

Find the gain of an inverting amp:-

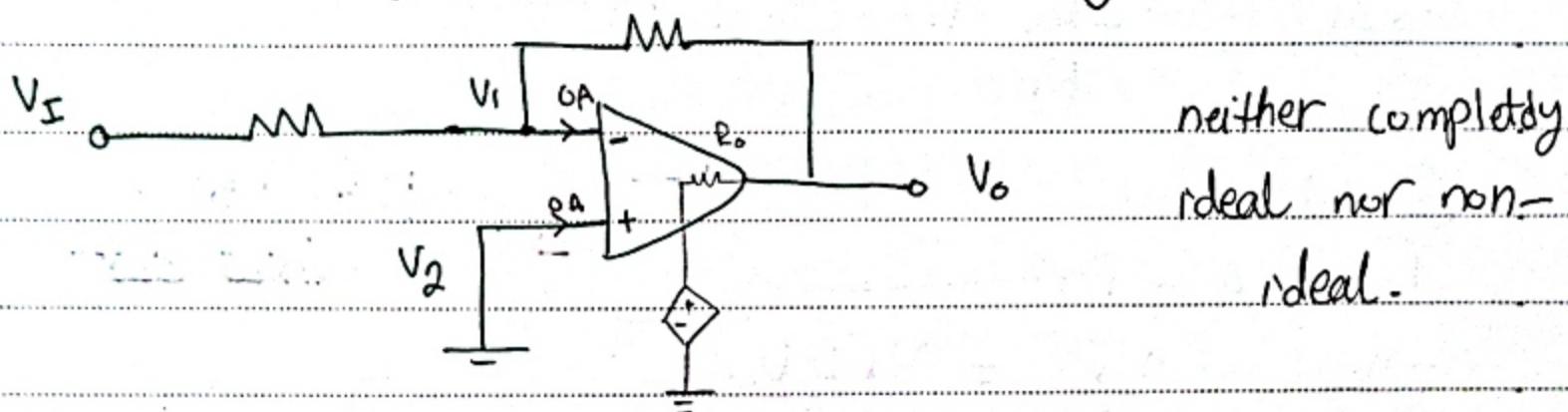

$$R_i = 0 \rightarrow i_1 = i_2 = 0$$

$$iR_1 = iR_2$$

$$\cdot \frac{V_I - V_1}{R_1} = \frac{V_1 - V_o}{R_2} \rightarrow \boxed{1}$$

$$\cdot V_o = A_{od} (V_2 - V_1) = -A_{od} V_1 \approx$$

$$\rightarrow V_1 = \frac{-V_o}{A_{od}}$$


Sub ② in ①

$$A_V = \frac{1}{-\frac{R_2}{R_1} \left(1 + \frac{1}{A_{od}} \left(1 + \frac{R_2}{R_1} \right) \right)}$$

$$\text{if } R_2 = 100 \text{ k}\Omega \quad R_1 = 10 \text{ k}\Omega$$


$\frac{A_{od}}{10^2}$	A_V	
10^3	-9.01	
10^4	-9.89	
10^5	-9.989	\rightarrow the same
10^6	-9.9999	result.

- summing amplifier:

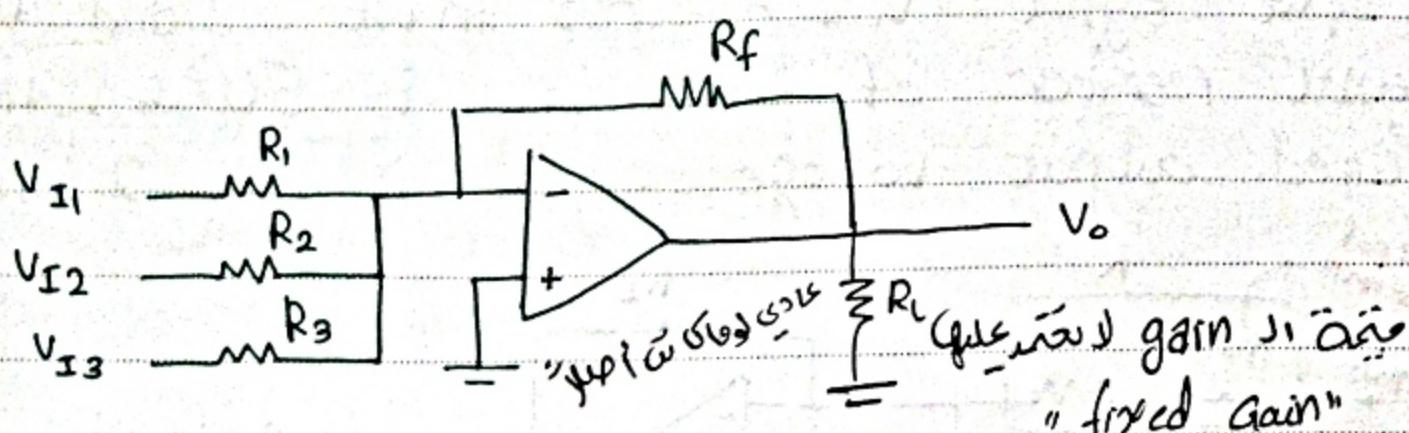

use super position technique :-

$V'_o = V_o$ due to V_{I1} only :-

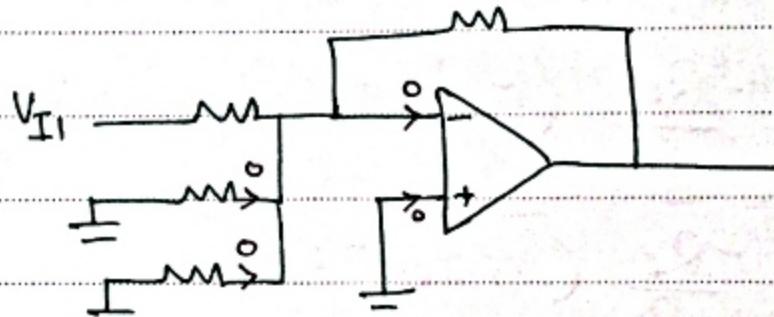

$$\therefore V'_o = -\frac{R_f}{R_1} * V_{I1}$$

$$V''_o = -\frac{R_f}{R_2} * V_{I2}$$

$$V'''_o = -\frac{R_f}{R_3} * V_{I3}$$


$$\therefore V_{\text{total}} = -R_f \left(\frac{V_{I1}}{R_1} + \frac{V_{I2}}{R_2} + \frac{V_{I3}}{R_3} \right)$$

if $R_1 = R_2 = R_3 = R$

$$\rightarrow V_o = -\frac{R_f}{R} (V_{I1} + V_{I2} + V_{I3})$$

$$V_o = -(V_{I1} + V_{I2} + V_{I3}) \quad : \text{just if all Resistors are equal to each other}$$

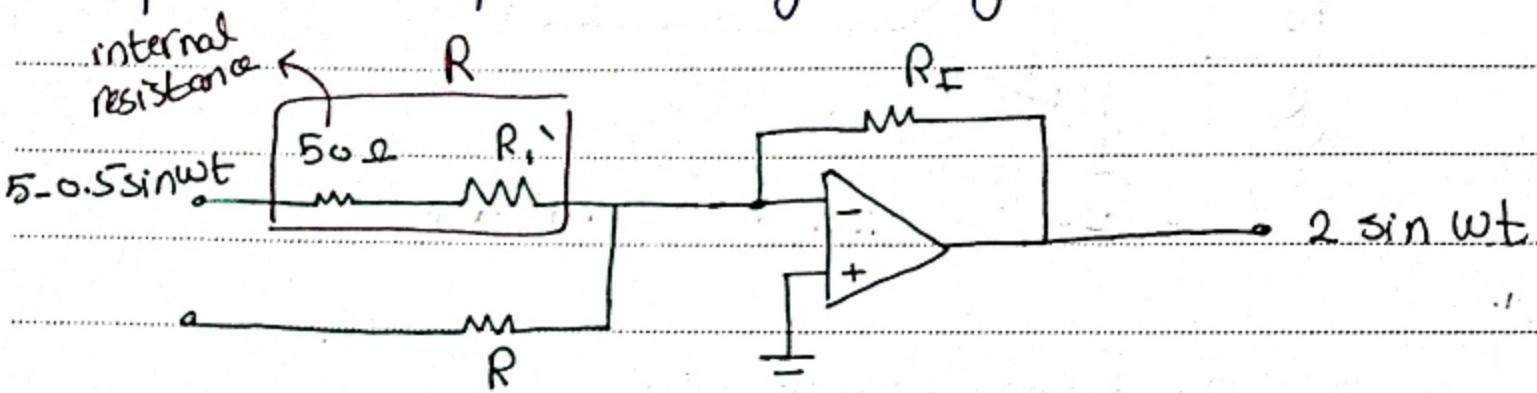- Example:- Design a summing Amplifier that has an input signal $V_i = 5 - 0.5 \sin \omega t$ and the internal resistor of the source is 50Ω , the required output voltage signal is $V_o = 2 \sin \omega t$



$$V_o = -\frac{R_f}{R} (V_{I1} + V_{I2})$$

$$2 \sin \omega t = -\frac{R_f}{R} (5 - 0.5 \sin \omega t + V_{I2})$$

$$2 \sin \omega t = -\frac{R_f}{R} (5 - 0.5 \sin \omega t + (-5))$$


$$2 = -\frac{R_f}{R} (-0.5)$$

$$\rightarrow \frac{R_f}{R} = 4 \Rightarrow R_f = 4R \quad \text{any two values verified this ratio.}$$

$$\text{Let } R_f = 120 \text{ k}\Omega \rightarrow R = 30 \text{ k}\Omega$$

$$R_1 = 30 \text{ k}\Omega - 50 \Omega$$

• Non-inverting amplifier:-

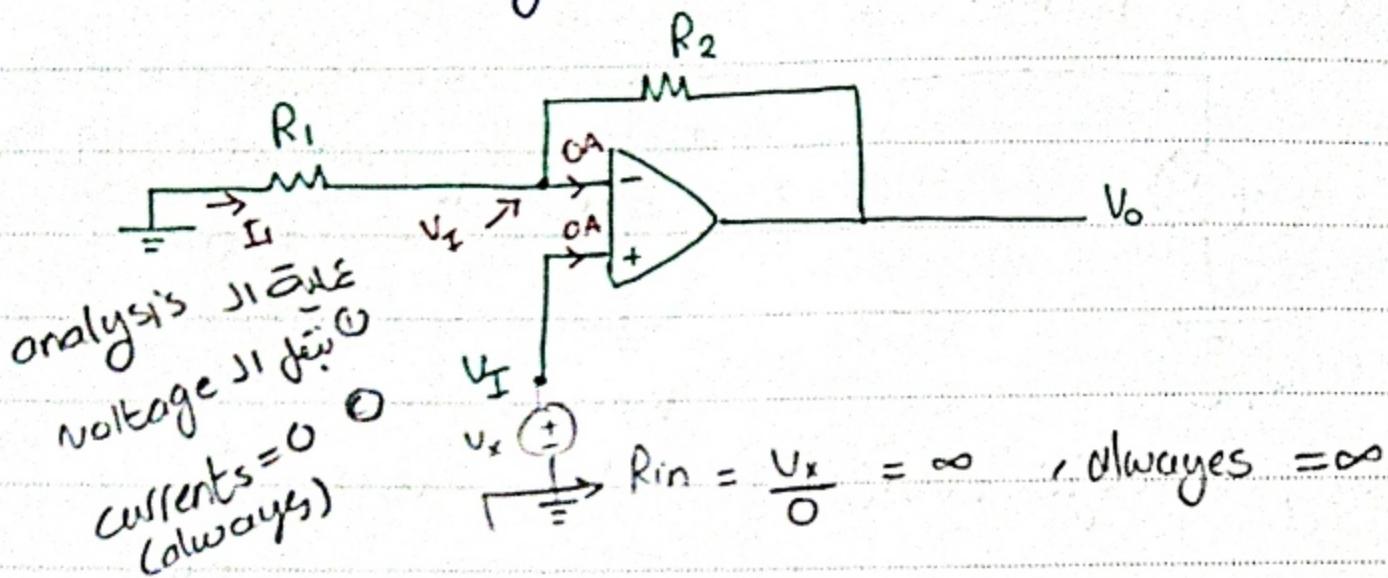


$$I_1 = I_2$$

$$\frac{0 - V_I}{R_1} = \frac{V_I - V_O}{R_2}$$

$$A_v = \frac{V_O}{V_I} = 1 + \frac{R_2}{R_1} \quad (\text{here } > 1)$$

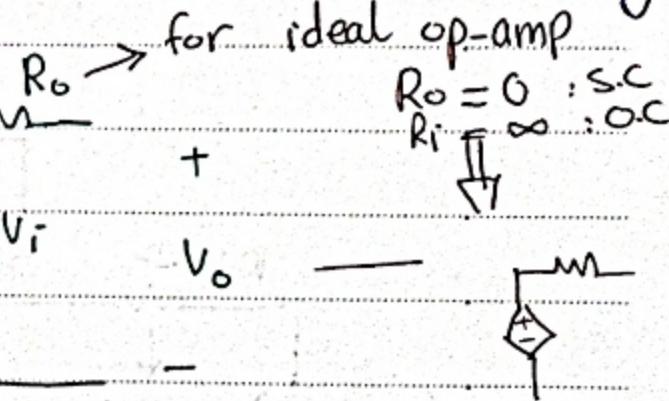• Equivalent two-port Network of non-inverting amplifier




$$A_v < 1 \text{ when } R_2 < R_1 !$$

loading effect
output follows V_I^{mag} phase.

• Voltage follower (Buffer / impedance transformer)

using in IC-s
"integrating cct"

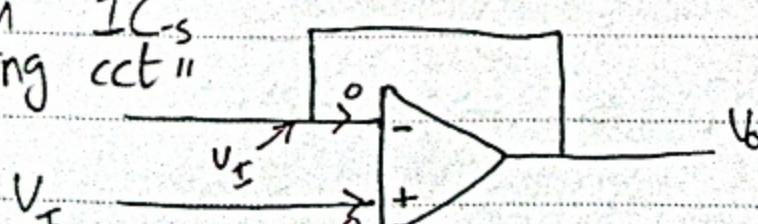


$$A_v = \frac{V_O}{V_I}$$

$$A_v = 1$$

• Example:-

$$R_s = 100 \text{ k}\Omega$$

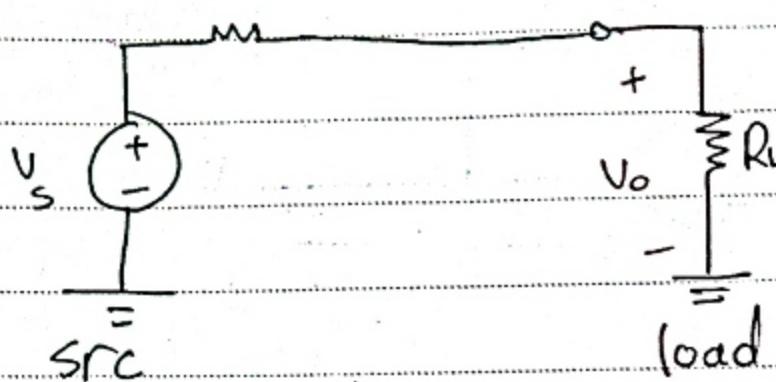

src \times Using load \times
without using
Buffer.

using voltage division: $V_o = V_s \times \frac{1}{1 + 100}$


→ High loading effect
problem.

But without loading effect (without load) →

$$V_o = V_s$$

⇒ with load V_o changed.



to solve this problem using Buffer

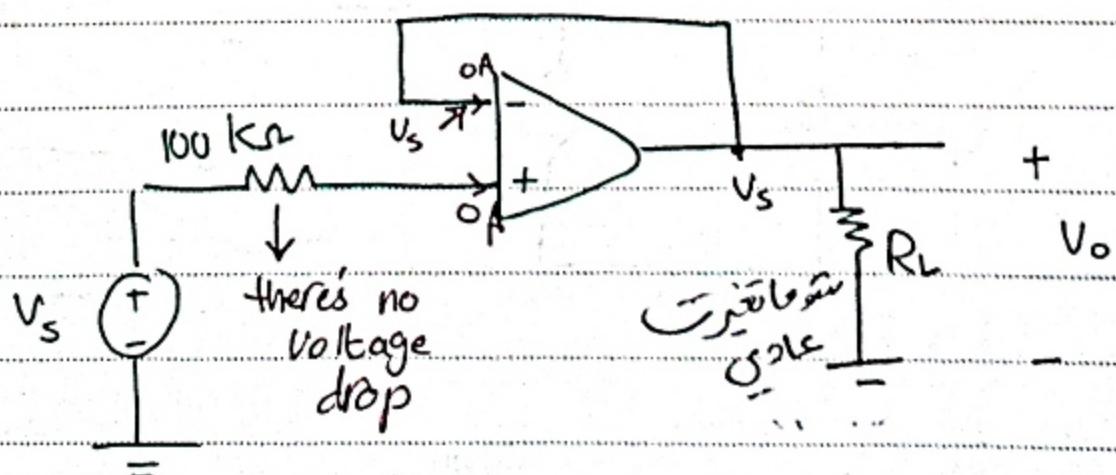

→ $V_o = V_s$ "no loading effect"


if $R_L : \infty \rightarrow V_o = 0$

- current - to - voltage converter:-

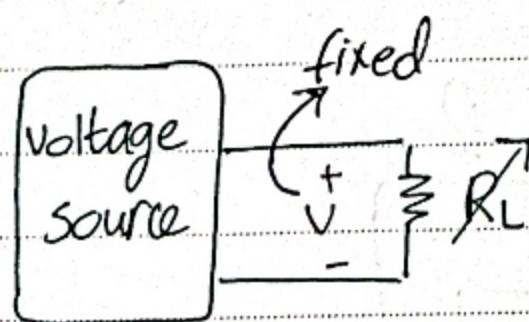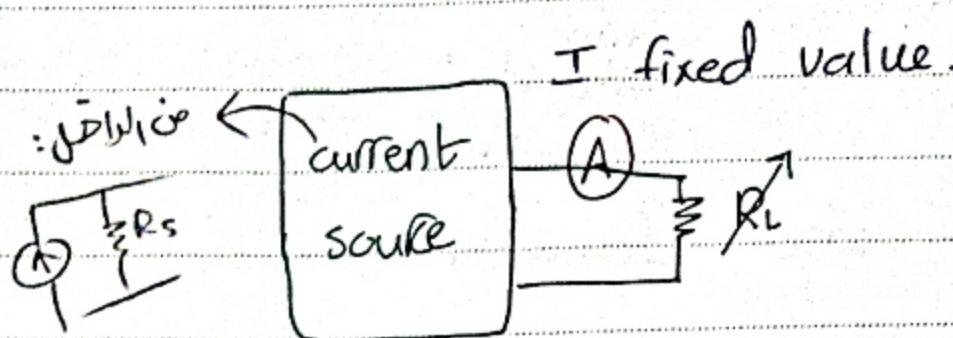

- current to voltage converter:-


* Method: use R .

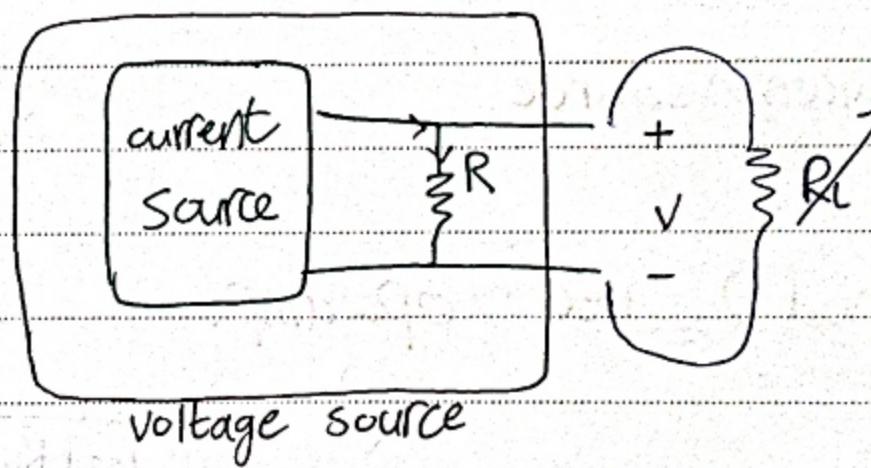

V will change with R_L so it is bad solution.

$i_s \rightarrow i_o \rightarrow V_o \propto R_s$

* Method: use OP-amp.

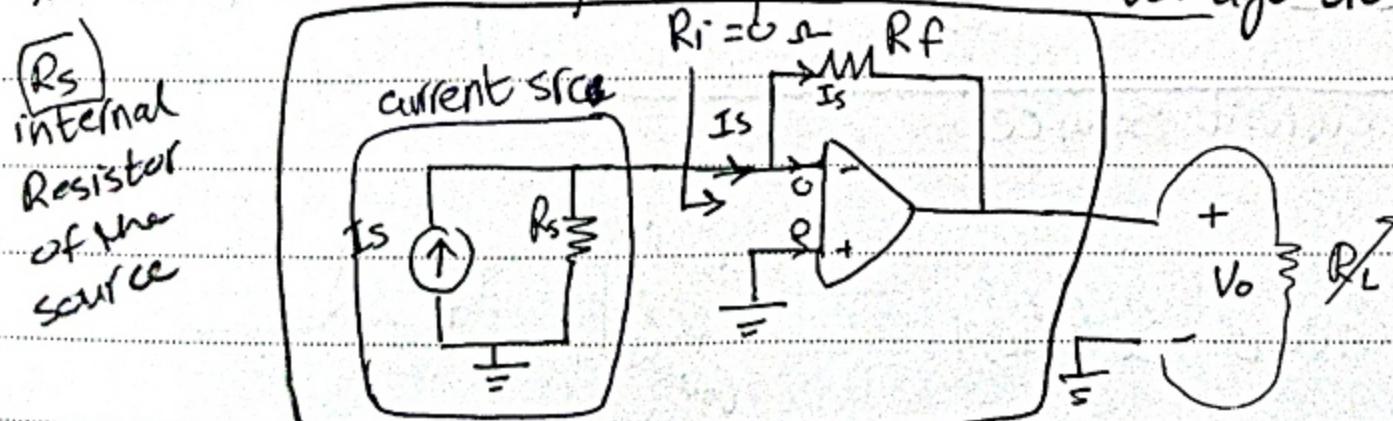


$$I_S = \frac{V_o - V_0}{R_f} \rightarrow V_o = -R_f I_S$$

fixed
independent
on R_L

→ Good Solution.


* Voltage-to-current inverter:-

- Method 1: use R :

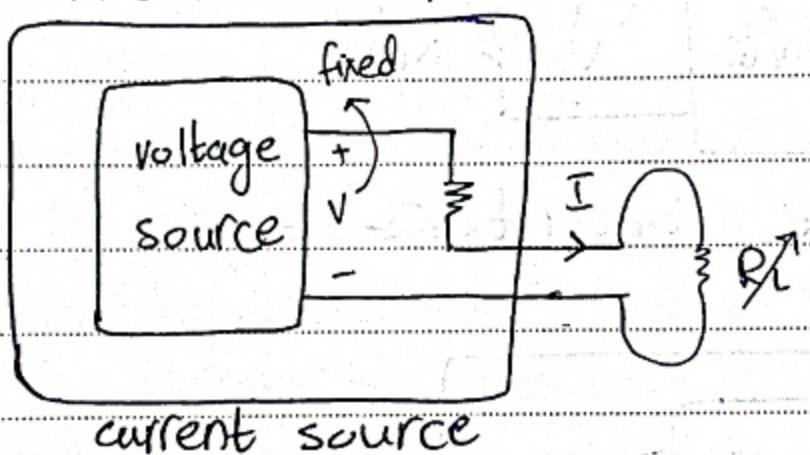

→ Bad solution since
 I changes with R_L

- Method 2: use op-amp:

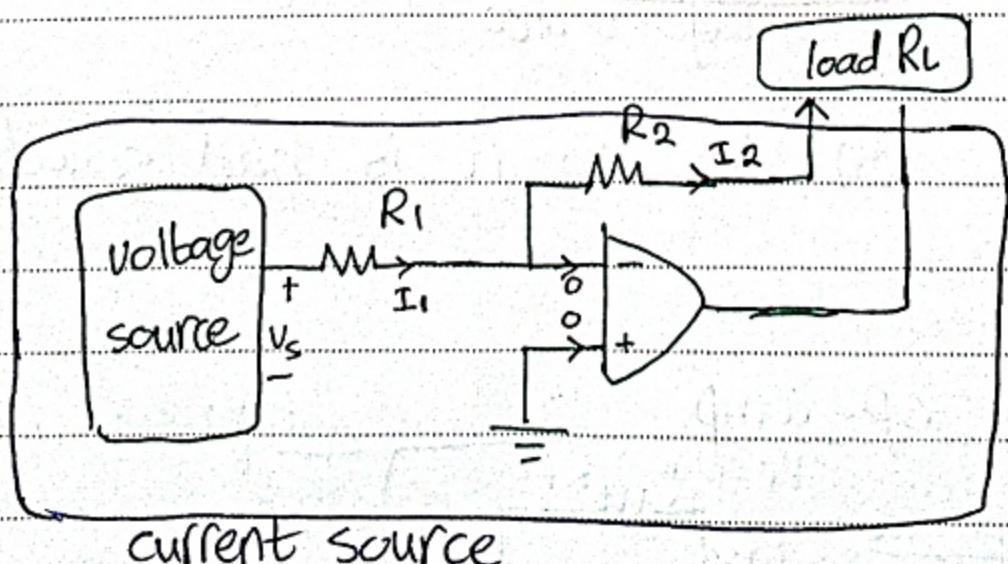


$$I_2 = I_1 = \frac{V_S}{R_1}$$


fixed
fixed

I_2 fixed, ind.
on R_2

→ Good Solution.

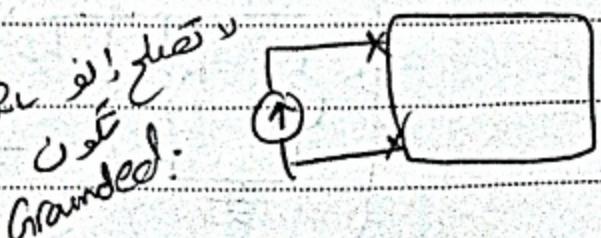


- But R_L should not be grounded

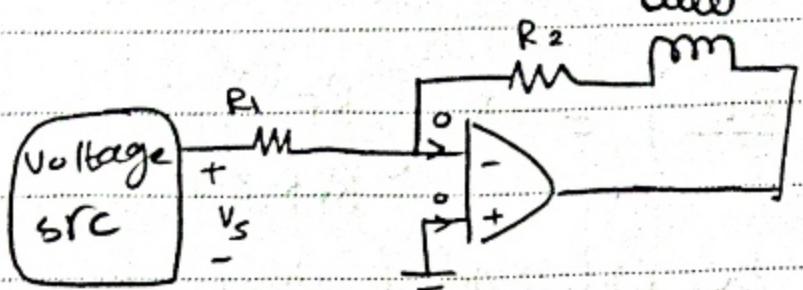

Disadvantage -

مما يغير صفة المضخم
ألا ينبع منه

Method 3:

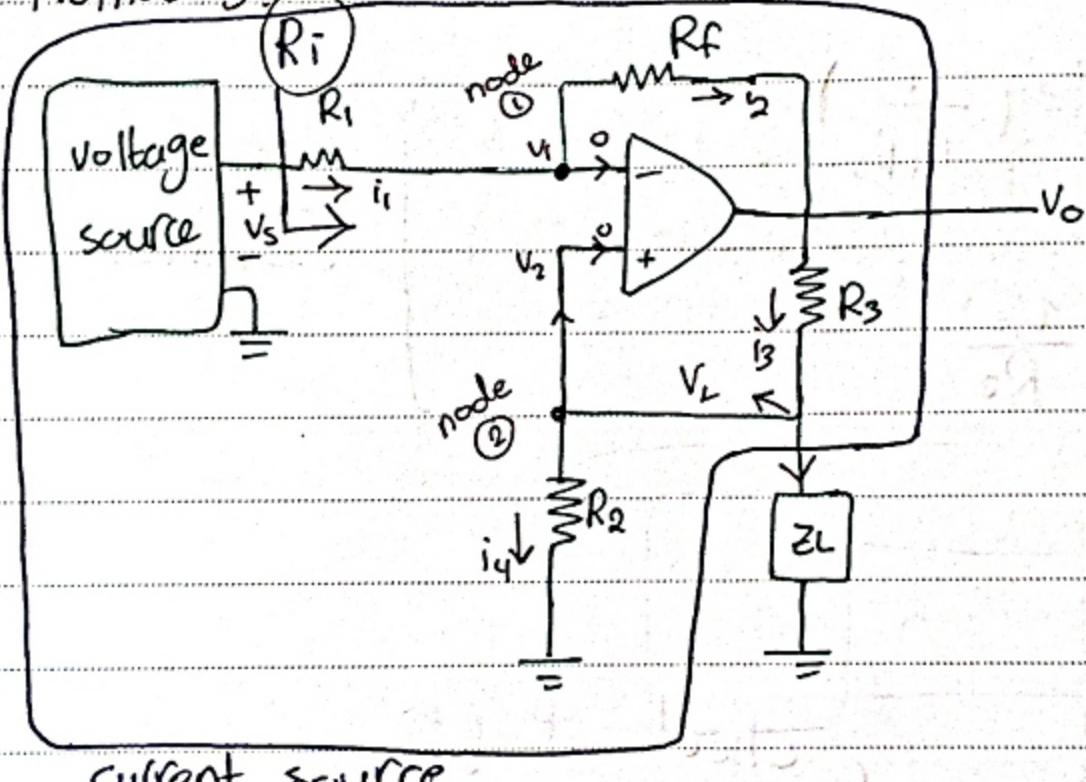

current source

$$\rightarrow V_1 = V_2 = V_L = i_L Z_L$$

$$\rightarrow i_1 = i_2 \quad \text{from node (1)}$$

$$\frac{V_s - i_1 Z_L}{R_1} = \frac{i_2 Z_L - V_o}{R_f} \rightarrow [1]$$

(i_L أولاً ثم i_2 ثم i_1)

$$\rightarrow i_3 = i_L + i_4 \quad \text{from node (2)}$$

$$\frac{V_o - i_L Z_L}{R_3} = i_L + \frac{i_L Z_L}{R_2} \rightarrow [2]$$

use [1] and [2]:

$$i_L \left(\frac{R_F Z_L}{R_1 R_3} - 1 - \frac{Z_L}{R_2} \right) = V_s \left(\frac{R_F}{R_1 R_3} \right)$$

→ we need i_L to be independent on $Z_L \rightarrow$

$$\boxed{\frac{R_F}{R_1 R_3} = \frac{1}{R_2}} \quad \text{لذلك يجب أن يكون} \frac{R_F}{R_1 R_3} = \frac{1}{R_2}$$

$$\rightarrow i_L = -V_s \left(\frac{R_F}{R_1 R_3} \right)$$

(current fixed, independent on Z_L)

Good Solution.

→ Finding R_i :

$$R_i = \frac{R_1 R_2}{R_2 + Z_L}, \text{ check if } !?$$

متوسط بين CCT تكون العدة

$$\text{op-amp: } V_o = A_{od}(V_2 - V_1)$$


هيون بعديم عيار

Difference Amplifier: → to take the difference between two voltages and amplify it.

$$V_o = A_{od}(V_2 - V_1)$$




V_{I_1} V_{I_2}

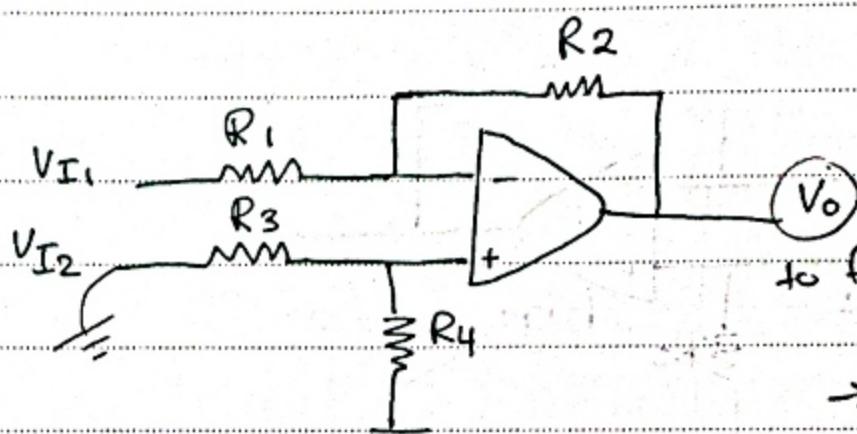

to find it with r.t.o
 V_I_1 & V_I_2
→ using super
position.


• By super position:-

$$V'_o = -\frac{R_2}{R_1} V_{I_1}$$

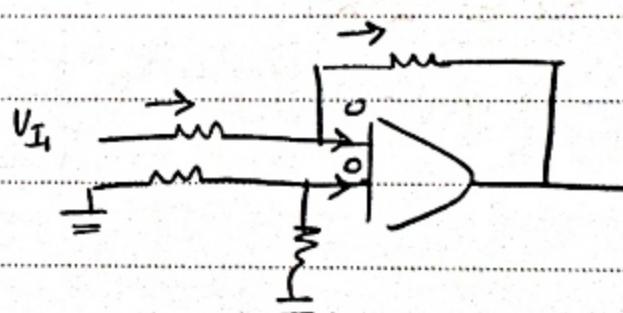

$$V''_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_4 + R_3}\right) V_{I_2}$$

inverting-amp.

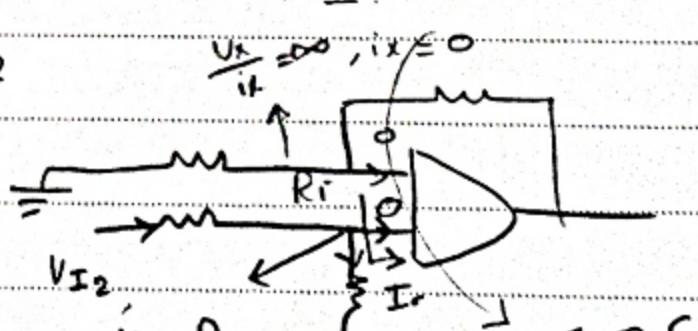

$$\frac{V_{I_2} R_4}{R_3 + R_4} \text{ as o.c}$$


$$\rightarrow V_o = -\frac{R_2}{R_1} V_{I_1} + \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_4 + R_3}\right) V_{I_2} \rightarrow \text{voltage division between } R_3 \text{ & } R_4$$

$$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right) V_{I_2} - \frac{R_2}{R_1} V_{I_1}$$

• if $V_{I_1} = V_{I_2}$ then V_o should be = zero

$$\text{So } \frac{R_2}{R_1} = \frac{R_4}{R_3}$$
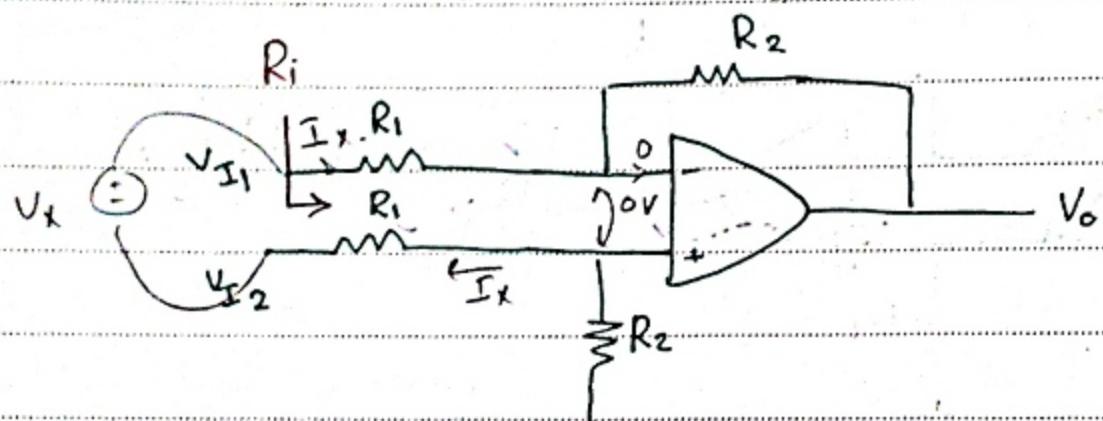
$$\therefore V_o = \frac{R_2}{R_1} (V_{I_2} - V_{I_1})$$



$$R_i = 2R_1$$

$$-V_x + R_1 I_x + R_1 I_x + 0 = 0$$

$$2R_1 = \frac{V_x}{I_x}$$

* Instrumentation Amplifier:-

we know that for difference amplifier:-

$$\cdot \text{Gain} = \frac{R_2}{R_1}$$

$$\cdot R_i = 2R_1$$


↓ loading effect \leftarrow due to R_i on effect

↓ of Gain

$$! \text{ Gain} \downarrow \Leftrightarrow \uparrow R_i \Leftrightarrow \uparrow R_i$$

→ problem:- Both R_i and gain are dependent on R_i

→ solution:- ① use Buffer.

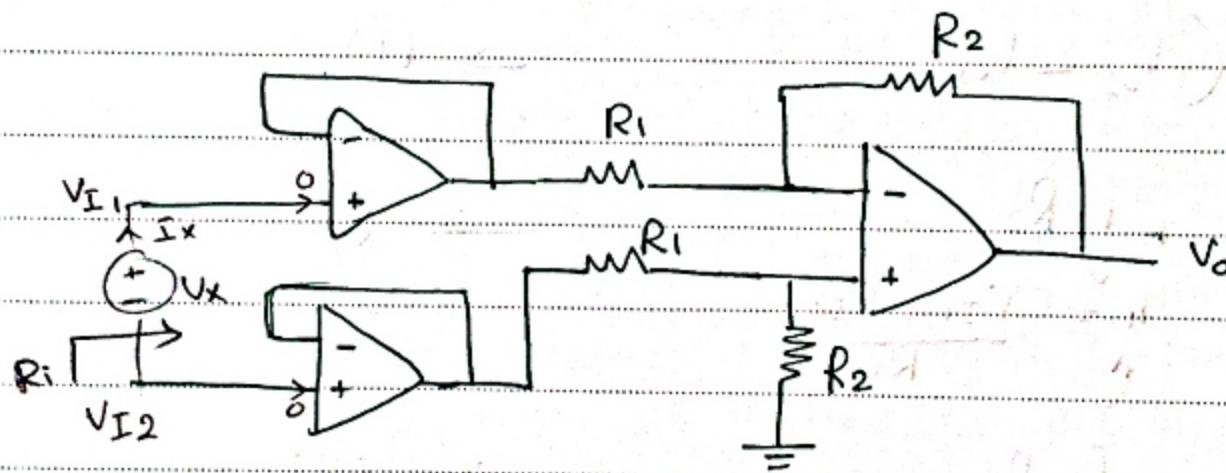

$$\Rightarrow R_i = \infty$$


\Rightarrow But there is another problem!

if we need to change the gain we have to change two resistor.

using potentiometer \leftarrow 2-resistor signal user will be cap

the change must be equally \rightarrow This is a practical problem.

②: using Instrumentation Amplifier.

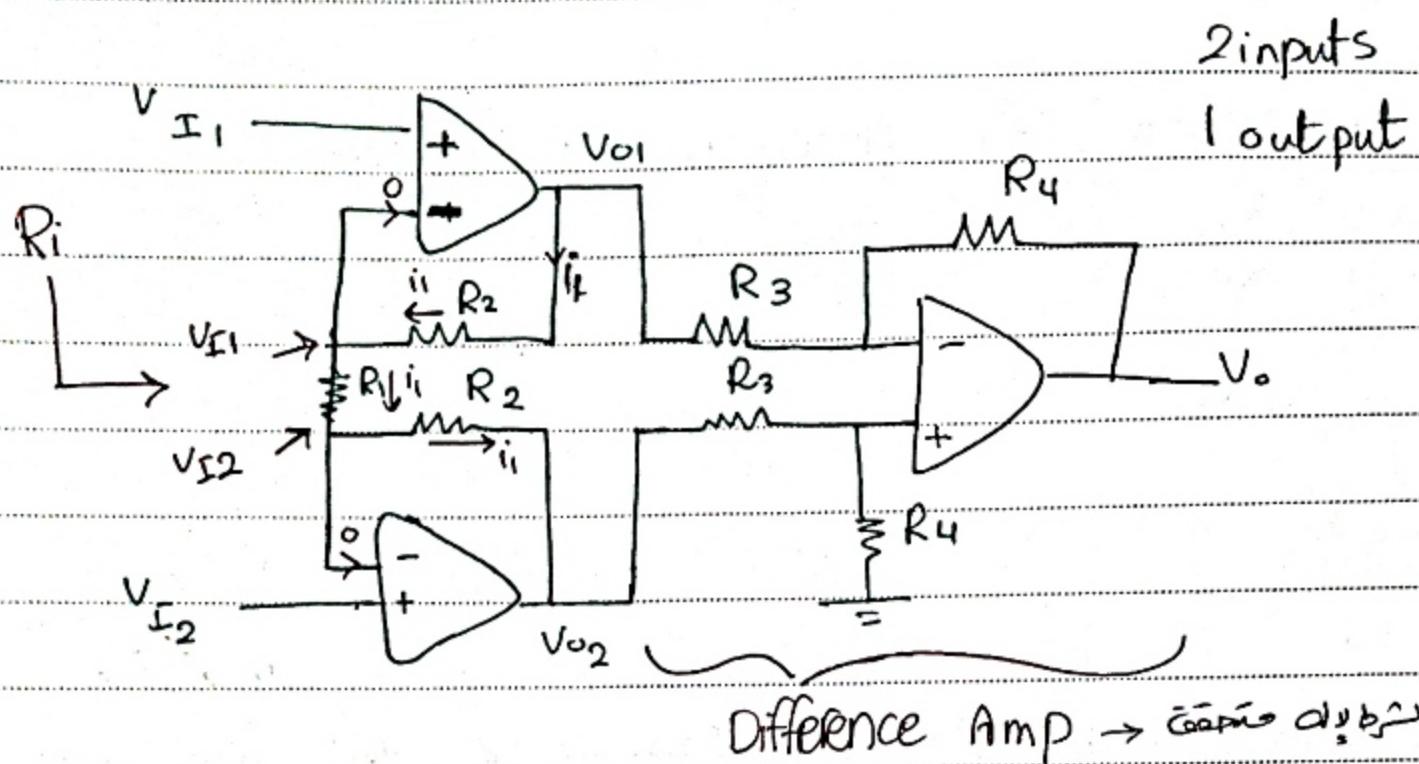

$$V_o = \frac{R_4}{R_3} (V_{o2} - V_{o1}) \rightarrow ①$$

$$V_{o1} = V_{I1} + i_1 R_2 \rightarrow ②$$

$$i_1 = \frac{V_{I1} - V_{I2}}{R_1}$$

$$V_{o2} = V_{I2} - i_1 R_2 \rightarrow ③$$

use ② and ③ in ①:-


$$V_o = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1} \right) (V_{I2} - V_{I1})$$

*fixed fixed
R1 R2
R3 Ri*

- advantages:-

1. $R_i = \infty$
2. The gain can be changed using one resistor (R_i)

- * Integrator:-

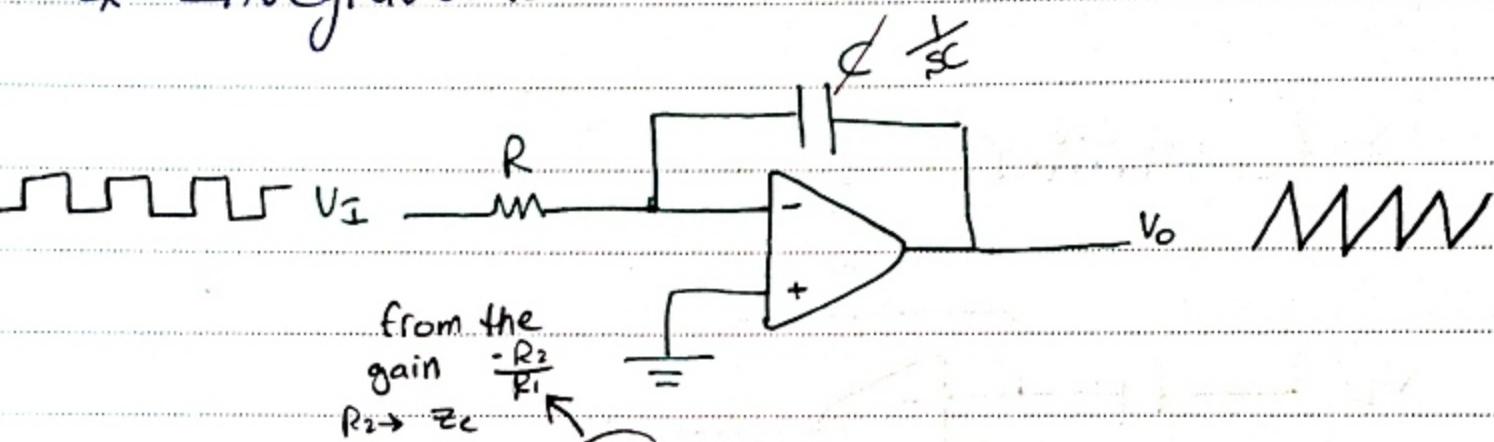


- $V_o(s) = V_I(s) * \frac{-Z_C}{R} = -\frac{1}{SRC} \cdot V_I(s)$ (S-domain)
output = input * T.F

T.F: Transfer function $\frac{1}{t}$ \rightarrow Gain

- $V_o(s) = V_c(0) - \frac{1}{RC} \int_0^t v_I(t) dt$ (time-domain)

- Example:-

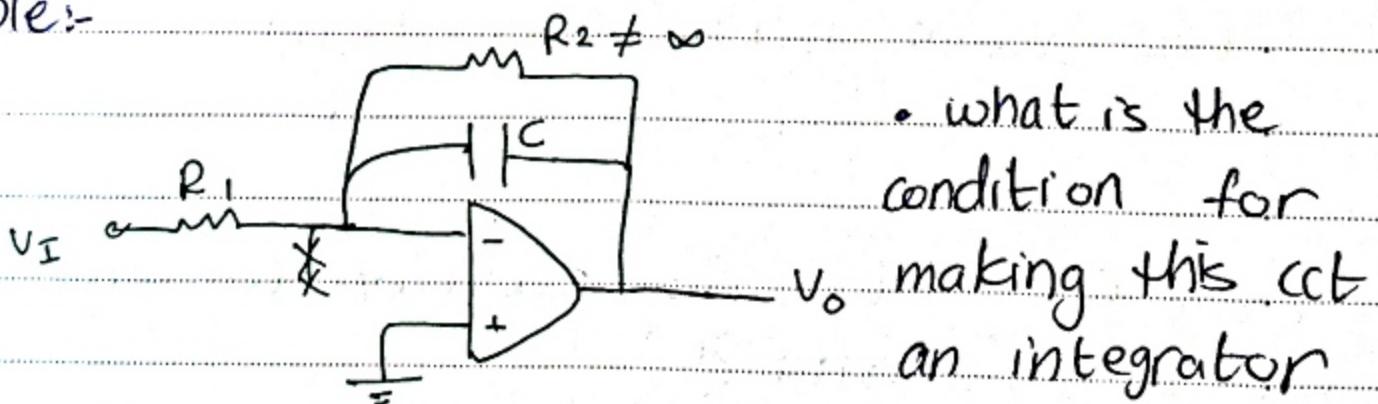

$$V_o(s) = -R_2 // \frac{1}{sC} \quad V_I(s) = -R_2 \cdot \frac{1}{R_1} V_I(s)$$


$$\left(-\frac{R_2}{R_1} \cdot \frac{1}{1+R_2 sC} \right) \approx \left(-\frac{1}{sRC} \right) \text{ (using 2-terms)}$$

→ the condition: $RCS \gg 1$

$$\rightarrow \frac{-R_2}{R_1} \cdot \frac{1}{RCS} = \frac{1}{R_{ICS}} \# \downarrow j\omega f$$

⇒ this cct can be used as integrator at high frequency.

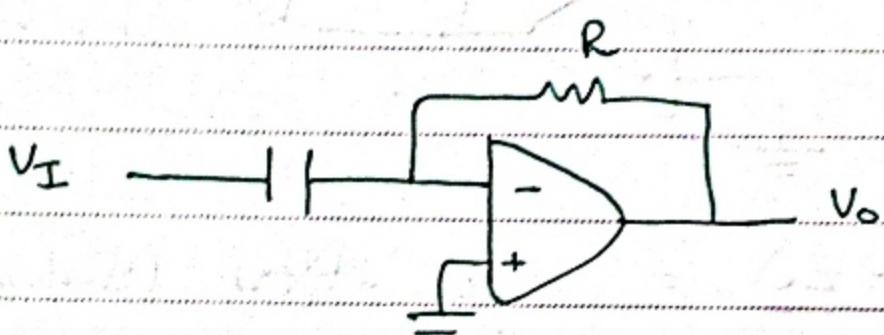* differentiator: - $C \ll R$ (use), $R \ll C$ (use)



S-Domain: $V_O(s) = \frac{-R}{(1/sC)} V_I(s)$

$$V_O(s) = -RCS V_I(s)$$


time-Domain: $V_O(t) = -RC \frac{dV_I(t)}{dt}$

Example:- what is the condition to make this cct a differentiator?

$$V_O = \frac{-R_2}{R_1 + \frac{1}{sC}} V_I(s)$$

$$V_O(s) = \frac{-R_2 sC}{sCR_1 + 1} V_I(s)$$


$$\rightarrow SCR_1 \ll 1$$

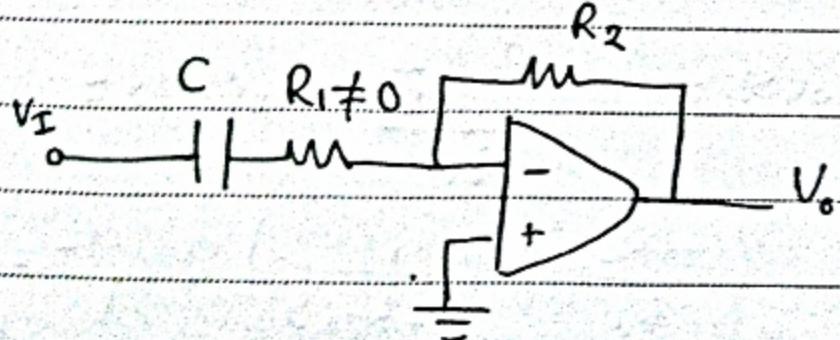


⇒ this cct can be used as differentiator at low frequency.

* Precision half-wave rectifier:-

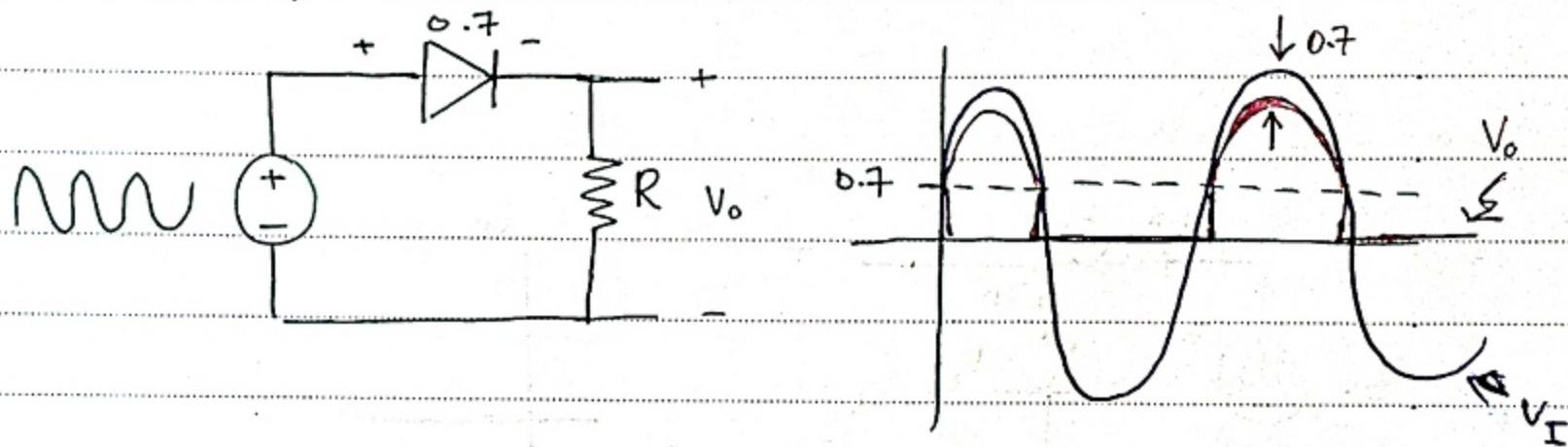→ we know that in the diode rectifier, the voltage should be > 0.7



• Precision half-wave rectifier:-

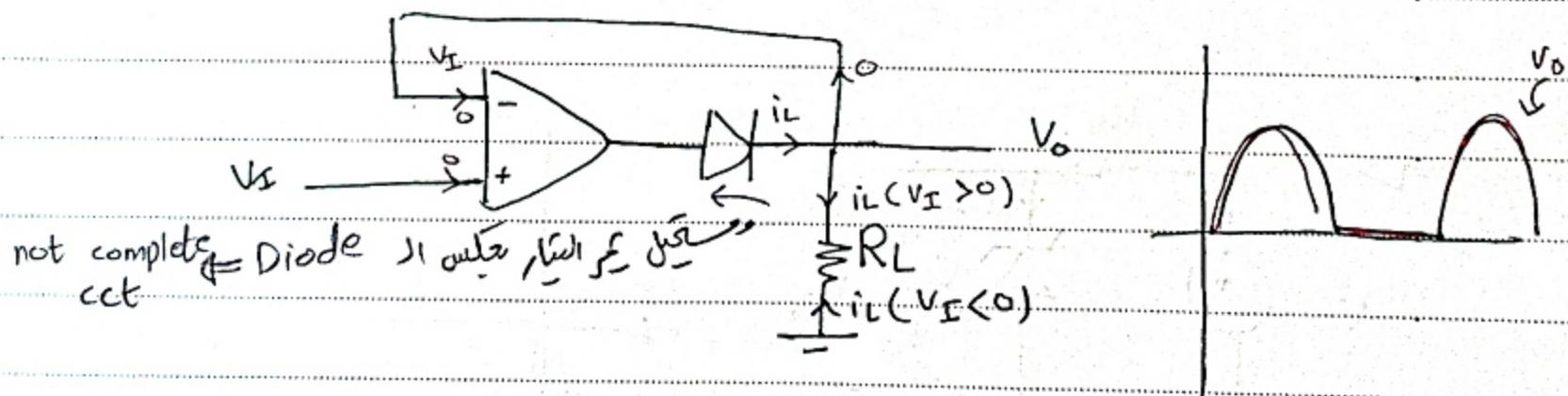

• if $V_I > 0 \Rightarrow V_o > 0 \Rightarrow i_L \downarrow$ (Down) ⇒ Diad is ON
• buffer cct


$$\therefore V_o = V_D$$

• if $V_I < 0 \Rightarrow V_o < 0 \Rightarrow i_L \uparrow$ (up) ⇒ Diode is off
• it is not



a complete cct

$$\therefore V_o = 0$$

* Reference voltage source design:-

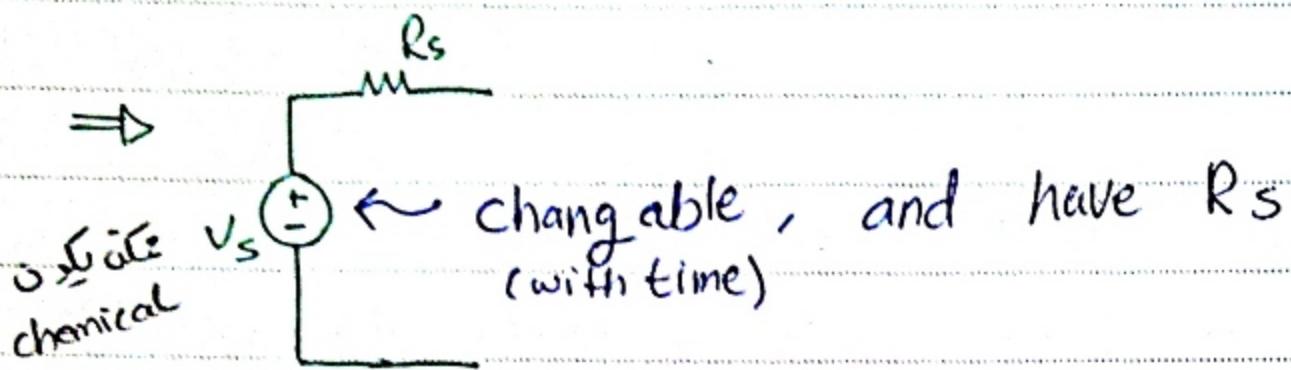

$V_o \Leftarrow I_S \Leftarrow V_s$

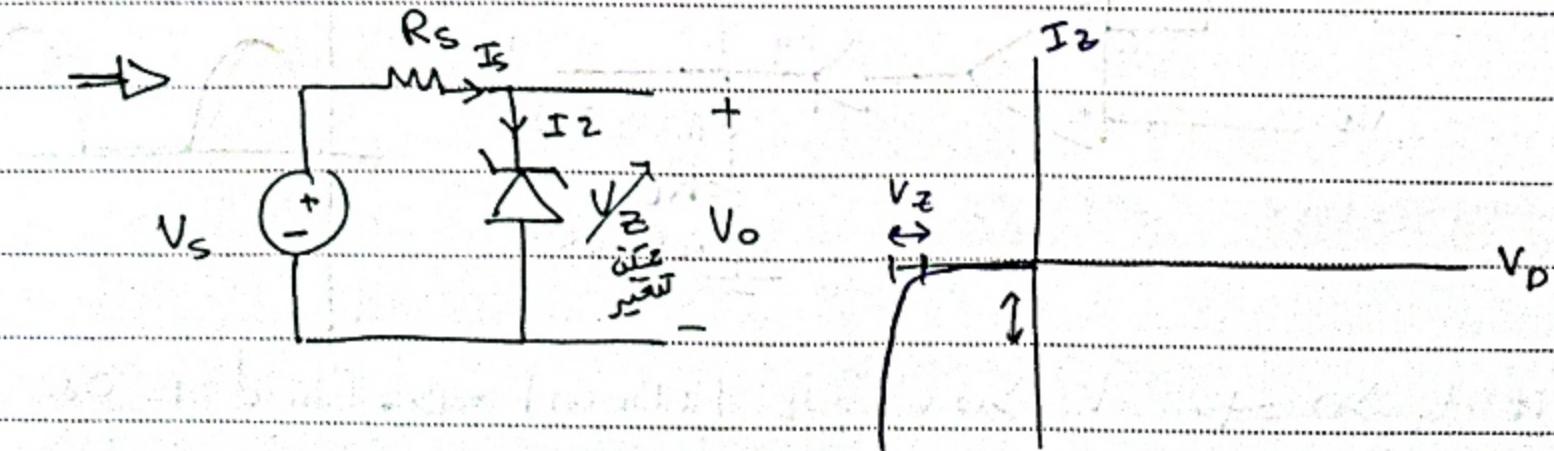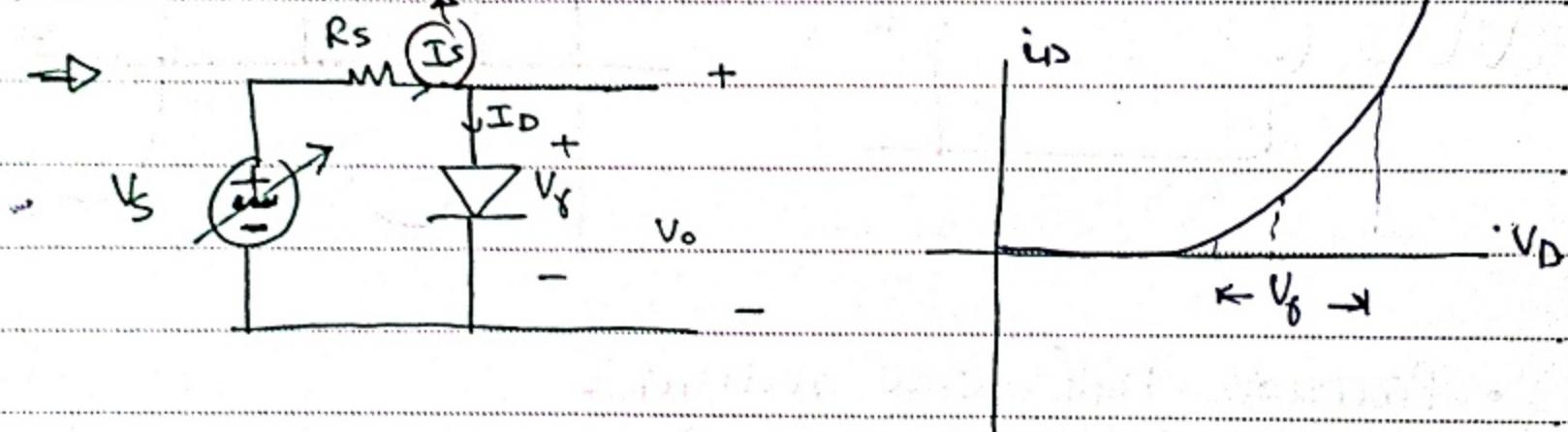


- * Problems:-
- ① V_o changes with V_s
- ② in some cases we need a reference voltage $\neq V_o$

$$V_s < V_2 \rightarrow i_z = 0$$

15 / 5 / 2014

$$V_s > V_2 \Rightarrow i_z \neq 0$$


\Rightarrow

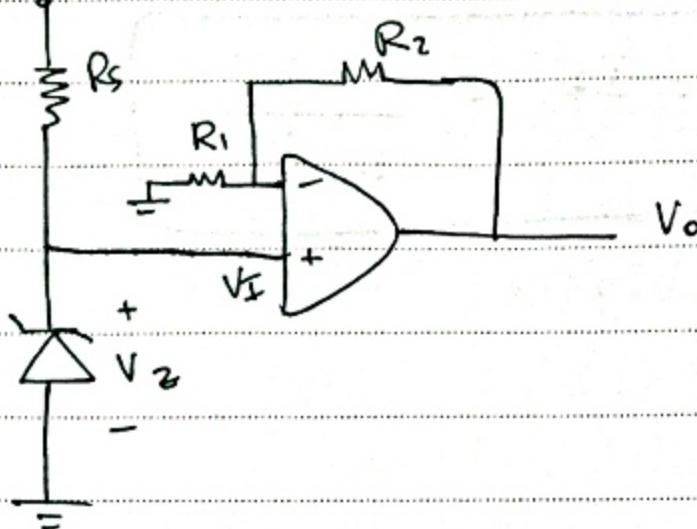

• if $V_s < V_2 \Rightarrow V_I = V_s$ problem

$V_s > V_2 \Rightarrow V_I = V_2 \rightarrow V_2 \uparrow$ as $V_s \uparrow$

\Rightarrow

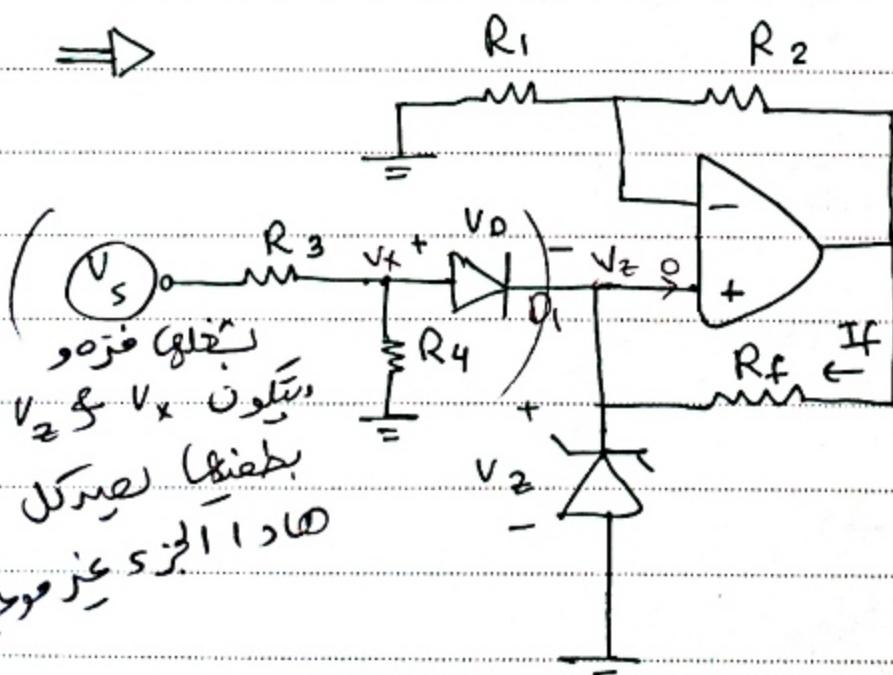

V_o "Reference voltage source design"

D_I is ON \Rightarrow if $V_x - V_2 > V_f$

$$\Rightarrow V_o = V_2 \left(1 + \frac{R_2}{R_1} \right)$$

$$I_f = \frac{V_o - V_2}{R_f} = \frac{R_2 V_2}{R_1 R_f}$$

$$I_F = I_2 = \frac{R_2 V_2}{R_1 R_F}$$

* feedback and stability:-

- Type:-
1. Positive feedback
 2. negative feedback. *


• negative feedback:-

Advantage:-

1. stable gain: the gain is independent on transistor parameter.

e.g.:-

(Fig. 1)

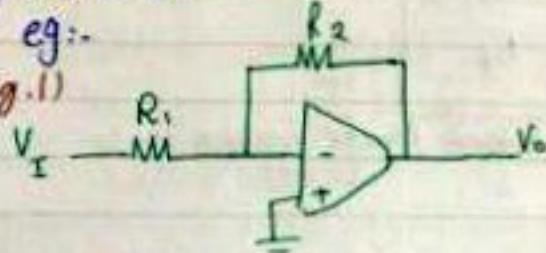

$$\text{Gain} = -\frac{R_2}{R_1}$$

* gain without feedback = A_{ad}

2. increases the bandwidth.

3. increases signal to noise ratio.

noise power

signal power

$\left(\frac{S}{N}\right) \uparrow$ increase Good

4. reduction of non-linear distortion.


↳ due to large signal. ↳ there's non-linear device or large signal to Amp

5. control of input and output impedance level

e.g.: in (Fig. 1) $R_i = R_1$.

- Disadvantages:-

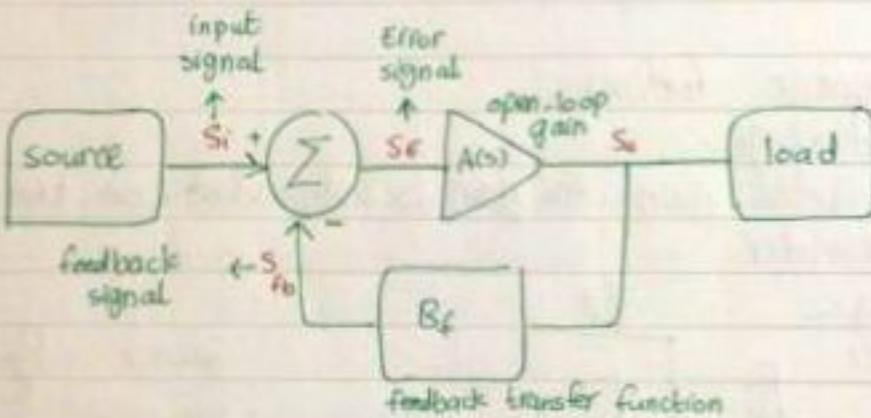1. reducing the gain.
2. the cct may become unstable (oscillate) at high frequencies.



$$S_o = A S_E$$

$$S_{fb} = S_o B_f$$

$$S_E = S_i - S_{fb}$$

$$\therefore S_o = A(S_i - S_o B_f)$$

$$A_f = \frac{S_o}{S_i} = \frac{A}{1 + BA}$$

the gain without feedback.

$$A_f = \frac{A}{1 + BA}$$

$A_f < A$ (Disadvantage)

$$\text{usually } BA \gg 1 \Rightarrow A_f = \frac{1}{B_f}$$


↓ depends on feedback
Stable Gain.

↳ independent on op-amp parameter

* Bandwidth extension:-

$$\text{let } A(s) = \frac{A_0}{1 + \frac{s}{\omega_n}}$$

gain without feedback

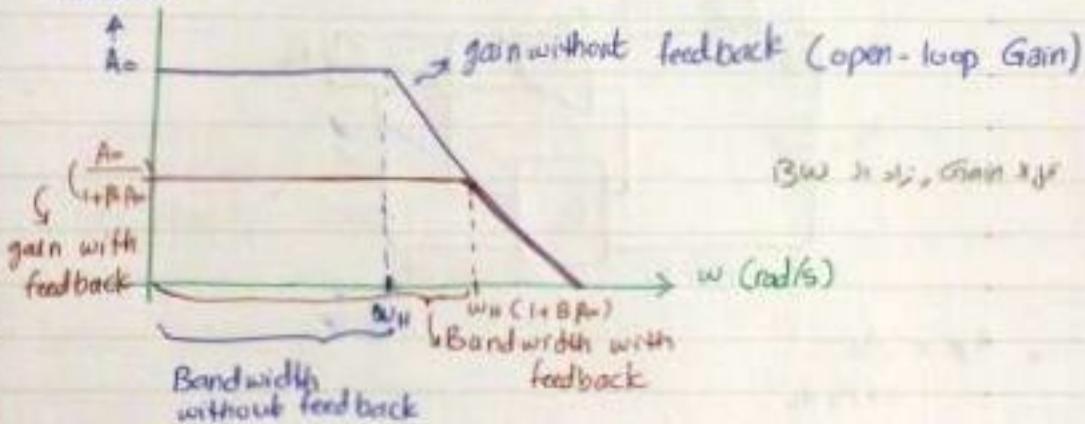

$B(w_n)$ \rightarrow Gain \propto w_n^2

$$A_f(s) = \frac{A(s)}{1 + BA(s)}$$


$$A_f(s) = \frac{A_0 / (1 + \frac{s}{\omega_n})}{1 + BA_0 / (1 + \frac{s}{\omega_n})}$$

$$A_f(s) = \frac{\frac{A_0}{1 + BA_0}}{1 + \frac{s}{\omega_n(1 + BA_0)}}$$

- Gain \downarrow \times Bandwidth \uparrow = constant

* Basic feedback configurations:-

③ series - shunt: as parallel

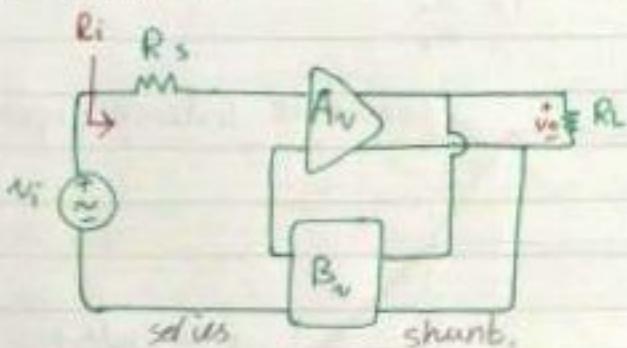


$$\cdot A_f = \frac{A_v}{1 + B_v A_v}$$

$$\cdot R_{if} = R_i (1 + B_v A_v), \quad R_i: \text{R input with feedback}$$


$$\cdot R_{of} = \frac{R_o}{1 + B_v A_v}, \quad R_o: \text{R input without feedback}$$

$(1 + B_v A_v) \rightarrow \text{enlarge!} \quad \leftarrow R_i \text{ enlarge!}$
 $\downarrow \leftarrow R_o$
 $\downarrow \leftarrow A$


④ shunt - series:

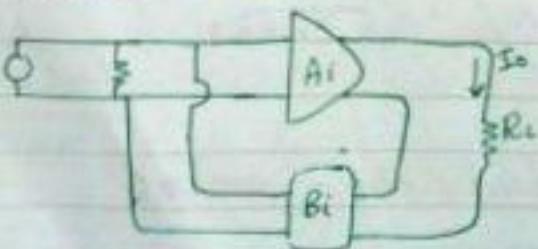

③ Series-series:-

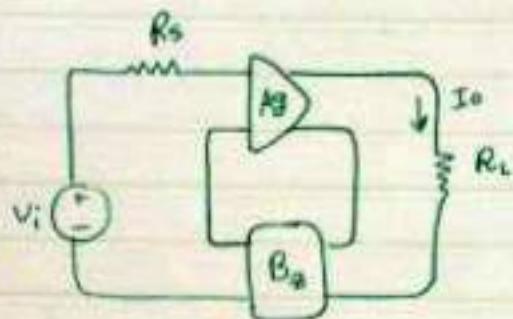

④ Shunt-shunt:-

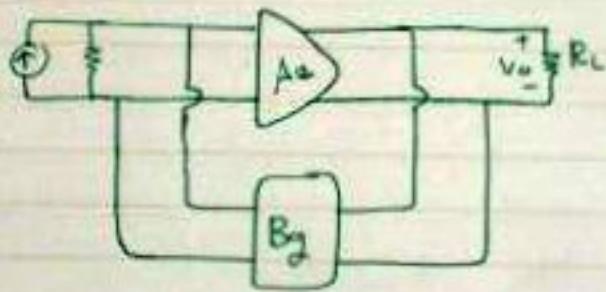

- Miller effect of Mosfet $\rightarrow C_m = ?$ ≈ 100