

$$A_v = \frac{v_o}{v_s} = \left( \frac{r_{\pi} + R_1 \parallel R_2 \parallel R_3}{1 + \beta} \right) \parallel R_E \parallel r_o$$

$$= 0.962 \approx 1$$

lecture 6:

23/5/2019

last example continues:

$$R_o = \frac{V_x}{i_x}$$

Kcl at node x:

$$i_x + g_m v_{\pi} = \frac{V_x}{R_E} + \frac{V_x}{r_o} + \frac{V_x}{r_o + r_s \parallel R_1 \parallel R_2} \quad \text{no(1)}$$

$v_{\pi} = -v_x \quad \checkmark$

$$v_{\pi} = -v_x \quad \checkmark$$

$$V_x = -v_x \frac{r_{\pi}}{r_{\pi} + R_s \parallel R_1 \parallel R_2} \quad \text{no(2)}$$

no Sub 2 in 1

$$R_o = \frac{V_x}{i_x} = \left( \frac{r_{\pi} + R_1 \parallel R_2 \parallel R_3}{1 + \beta} \right) \parallel R_E \parallel r_o$$

$$R_o = 36.6 \, \Omega \quad \text{no Very low value.}$$

no Current gain:

$$A_i = \frac{i_o}{i_b}$$

$$i_o = (1 + \beta) i_b \frac{r_o}{r_o + R_E}$$

$$z_{in} = z_{in} \frac{R_1 // R_2}{R_1 // R_2 + R_{ib}} \quad \text{--- eq 2}$$

$$\downarrow r_o + (1+\beta)(r_o // R_E)$$

Sub 2 in 1


$$A_i = \frac{z_o}{z_{in}} = (1+\beta) \left( \frac{R_1 // R_2}{R_1 // R_2 + R_{ib}} \right) \left( \frac{r_o}{r_o + R_E} \right)$$

typically,  $r_o \gg R_E$ So the term  $\frac{r_o}{r_o + R_E} \approx 1$ }  $R_1 // R_2 \gg R_{ib}$ also the term  $\frac{R_1 // R_2}{R_1 // R_2 + R_{ib}} \approx 1$ So  $A_i \approx (1+\beta) \approx \beta$ 

Ex: design a common collector amplifier that connects a Voltage Source (Microphone) with  $R_s = 10 \text{ k}\Omega$  with a load (speaker) that has  $R_L$  changes from  $4 \text{ k}\Omega$  to  $20 \text{ k}\Omega$ .


We want to design CC amplifier such that the output Voltage does not vary by more than 5%.

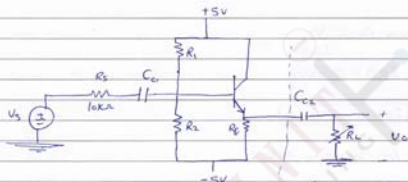given  $V_{CC} = 5 \text{ V}$  $\beta = 100$



We want to find  $R_1$ ,  $R_2$  &  $R_E$  that satisfied the requirement

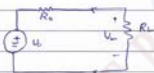$\Rightarrow$  5% means that  $95\% \leq V_o \leq V_o$



$$.95 V_o = V_o \frac{R_L}{R_L + R_o} \rightarrow R_o = 200 \Omega$$

for CC:

$$R_o = \left( \frac{r_\pi + R_1 \parallel R_2 \parallel R_s}{1 + \beta} \right) \parallel R_E \parallel r_o$$

Usually  $R_1 \parallel R_2 \gg R_s$

$$\Rightarrow \frac{r_\pi + R_1 \parallel R_2 \parallel R_s}{1 + \beta} \ll R_E \parallel r_o$$

$$\Rightarrow R_o \approx \frac{r_\pi + R_s}{1 + \beta}$$

$$\Rightarrow \boxed{R_o = 10.2 \text{ k}\Omega}$$

$$\rightarrow r_{\pi} = \frac{V_T}{I_{BQ}}$$

$$I_{BQ} = 2.55 \mu\text{A}$$

$$\rightarrow I_{CQ} = 0.255 \text{ mA}$$

$$\text{let } V_{CEQ} = 5 \text{ V}$$

output loop

$$-5 + V_{CEQ} + I_C R_E - 5 = 0$$

$$\rightarrow R_E = 19.6 \text{ k}\Omega$$

for stability -

$$R_{th} = 0.1 (4\beta) R_E$$

$$\text{So } R_{th} = 198 \text{ k}\Omega$$

$$R_1 \parallel R_2$$

$$-V_{th} + R_{th} I_{BQ} + I_C + I_{CQ} R_E - 5 = 0$$



we can find  $V_{th}$

$$V_{th} = \left( \frac{R_2}{R_1 + R_2} \right) (10) - 5$$

$$= \frac{R_1}{R_1} \left( \frac{R_2}{R_1 + R_2} \right) (10) - 5$$

$$R_1 = 344 \text{ k}\Omega$$

$$R_2 = 467 \text{ k}\Omega$$


## Lecture 10

25/3/2014


## \* Common Base Amplifier (C.B)

Features:-

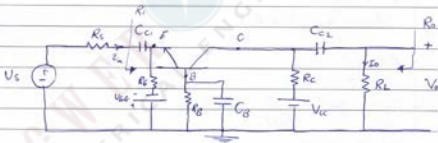1.  $A_v > 1$
2.  $A_i \approx 1$
3. Small  $R_i$
4. high  $R_o$
5. CB amplifier = Ideal current source.
6. used if the input signal is a current.


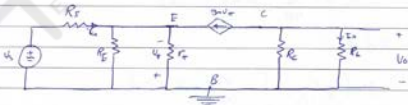
$$\text{find: } A_v = \frac{V_o}{V_s}, \quad A_i = \frac{i_o}{i_s}, \quad R_o, \quad R_i$$



\* Coupling Capacitor Features:-

1. protect load & the source.
2. protect the location of Q point

$$A_v = \frac{V_o}{V_s}$$

$$\Rightarrow V_o = -g_m V_{\pi} (R_L \parallel R_C)$$

$\Rightarrow$  KCL at node E

$$g_m V_{\pi} + \frac{V_{\pi}}{r_{\pi}} + \frac{V_{\pi}}{R_E} + \frac{V_s - (-V_{\pi})}{R_s} = 0 \quad \text{--- (2)}$$

use 1 & 2

$$A_v = g_m \left( \frac{R_C \parallel R_L}{R_s} \right) \left[ \left( \frac{V_{\pi}}{1+\beta} \right) \parallel R_E \parallel R_s \right]$$

if  $R_s = 0 \Omega$

$$A_v = g_m (R_C \parallel R_L)$$

$$A_i = \frac{i_o}{i_{in}}$$

$$\Rightarrow I_o = -g_m V_{\pi} \frac{R_C}{R_C + R_L} \quad \text{--- (1)}$$

KCL at Emitter

$$i_{in} + g_m V_{\pi} + \frac{V_{\pi}}{R_E} + \frac{V_{\pi}}{r_{\pi}} = 0$$

$$V_{\pi} = -i_{in} \left[ \left( \frac{r_{\pi}}{1+\beta} \right) \parallel R_E \right] \quad \text{--- (2)}$$


from 1 & 2

$$A_i = g_m \left( \frac{R_C}{R_C + R_L} \right) \left[ \left( \frac{r_{\pi}}{1+\beta} \right) \parallel R_E \right]$$

usually for practical CB,  $R_E$  very high value  
 $R_L$  very small value.

$$A_i \times \frac{g_m r_{\pi}}{1+\beta} = \frac{\beta}{1+\beta} = \alpha \approx 0.99 \approx 1$$

CB amplifier

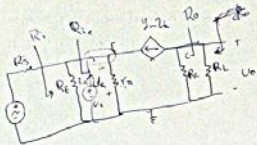

①

$R_i = R_E \parallel R_C$

$$R_E = \frac{V_E}{I_E}$$

KCL @ node E :-  $i_e + \frac{V_E}{R_s} + g_m V_e = 0$

but  $V_e = -V_E \Rightarrow i_e - \frac{V_E}{R_s} - g_m V_e = 0$

$$R_E = \frac{V_E}{I_E} = \frac{r_e}{1 + \beta} = \frac{r_e}{1 + \beta} \text{ small value}$$

$R_i = R_E \parallel R_C$  small value



KCL @ C :-  $i_x - \frac{V_x}{R_C} - g_m V_e = 0 \quad \text{--- (1)}$

KCL @ E :-  $g_m V_e + \frac{V_x}{R_C} + \frac{V_x}{R_L} = 0 \Rightarrow V_e \left( g_m + \frac{1}{R_C} + \frac{1}{R_L} + \frac{1}{R_L} \right) = 0$

From (1)  $\Rightarrow r_o = \frac{V_x}{I_x} = R_C$

$\therefore V_e = 0$


First



# \* Multi-stage Amplifier :-

It is used to satisfy some requirement, that can't be satisfied by single stage.

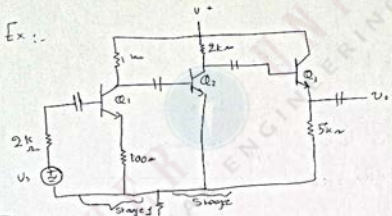- Example - CE without  $R_E$   
→ has high  $A_v$  but unstable
- CE with  $R_E$   
→ has low  $A_v$  but stable
- CC has  $A_v \approx 1$  but high  $R_i'$  and low  $R_o$



For  $Q_1$  :  $\beta = 100$  ,  $r_n = 1k\Omega$   
→  $Q_2$  &  $Q_3$  :  $\beta = 100$  ,  $r_n = 0.5k\Omega$

Final  $A_v = \frac{V_o}{V_s}$

Solution :-  
Stage 1 :- CE w/  $R_E$  >


$$A_{v1} = \frac{-\beta R_c}{r_n + (1+\beta)R_E} \left( \frac{R_i}{R_i + R_s} \right) \Rightarrow R_i = [r_n + (1+\beta)R_E] \parallel R_1 \parallel R_2$$

$$R_i = r_n + (1+\beta)R_E$$

$A_{v1} = -7.63$

$R_o = R_c = 8.1k\Omega$

Stage 2: CE without  $R_e$

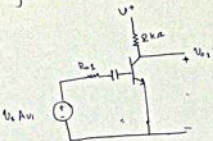


$$A_{V2} = -g_m \left( \frac{R_1 \parallel R_2 \parallel R_{cs}}{R_1 \parallel R_2 \parallel R_{cs} \parallel R_{bs}} \right) (R_{cs} \parallel R_c) \quad (8)$$

$$A_{V2} = -133$$

$$R_{cs} = R_c = 2k\Omega$$

Stage 3 :- CC

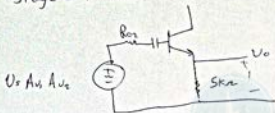

$V_o = A_{V1} A_{V2} A_{V3}$

$$A_{V3} = 1$$

$$V_o = V_i A_{V1} A_{V2} A_{V3}$$

$$A_{V1} = \frac{V_o}{V_i} = A_{V1} A_{V2} A_{V3}$$

$$= 1010$$