

$$A_v = \frac{v_o}{v_s} = \left(\frac{r_{\pi} + R_1 // R_2 // R_3}{1 + \beta} \right) // R_E // r_o$$

$$= 0.962 \approx 1$$

lecture 10:

23/3/2014

last example continues:-

$$R_o = \frac{v_x}{i_x}$$

Kcl at node x:

$$i_x + g_m v_{\pi} = \frac{v_x}{R_E} + \frac{v_x}{r_o} + \frac{v_x}{r_{\pi} + r_s // R_1 // R_2} \quad \text{--- (1)}$$

$$v_{\pi} = -v_x$$

$$v_{\pi} = -v_x \frac{r_{\pi}}{r_{\pi} + r_s // R_1 // R_2} \quad \text{--- (2)}$$

Sub 2 in 1


$$R_o = \frac{v_x}{i_x} = \left(\frac{r_{\pi} + R_1 // R_2 // R_3}{1 + \beta} \right) // R_E // r_o$$

$$R_o = 36.6 \Omega \quad \text{--- Very low value.}$$

Current gain:


$$A_i = \frac{i_o}{i_m}$$
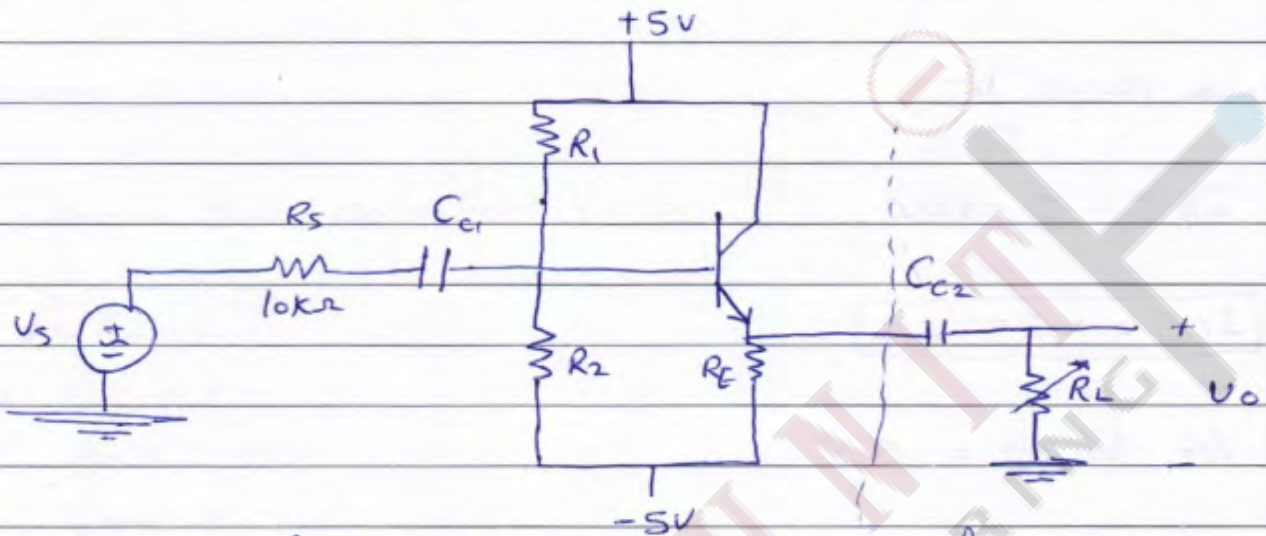
$$i_o = (1 + \beta) i_b \frac{r_o}{r_o + R_E}$$



We want to find R_1, R_2 & R_E that satisfied the requirement.

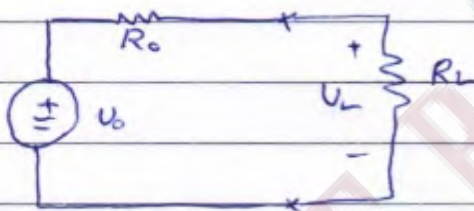\Rightarrow 5% means that $95\% \leq V_L \leq V_o$



$$.95 V_o = V_o \frac{R_L}{R_L + R_o} \Rightarrow R_o = 200 \Omega$$

for CC:

$$R_o = \left(\frac{r_{\pi} + R_1 // R_2 // R_s}{1 + \beta} \right) // R_E // r_o$$

Usually $R_1 // R_2 \gg R_s$

$$\Rightarrow \frac{r_{\pi} + R_1 // R_2 // R_s}{1 + \beta} \ll R_E // r_o$$

$$\Rightarrow R_o \approx \frac{r_{\pi} + R_s}{1 + \beta}$$

$$\Rightarrow \boxed{r_{\pi} = 10.2 \text{ k}\Omega}$$

$$\Rightarrow r_{\pi} = \frac{V_T}{I_{BQ}}$$

$$I_{BQ} = 2.55 \mu A$$

$$\Rightarrow I_{CQ} = 255 \mu A$$

$$\text{let } V_{CEQ} = 5 V$$

output loop:

$$-5 + V_{CEQ} + I_E R_E - 5 = 0$$

$$\Rightarrow R_E = 19.6 k\Omega$$


for stability:

$$R_{th} = 0.1 (1 + \beta) R_E$$

$$\text{So } R_{th} = 198 k\Omega$$

$$R_1 // R_2$$
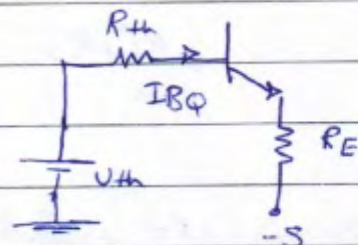
$$-U_{th} + R_{th} I_{BQ} + 7 + I_E R_E - 5 = 0$$



We can find U_{th}

$$U_{th} = \left(\frac{R_2}{R_1 + R_2} \right) (10) - 5$$

$$= \frac{R_1}{R_1} \left(\frac{R_2}{R_1 + R_2} \right) (10) - 5$$

$$R_1 = 344 k\Omega$$

$$R_2 = 467 k\Omega$$


Lecture 10

25/3/2014


* Common Base Amplifier (CB)

Features:-

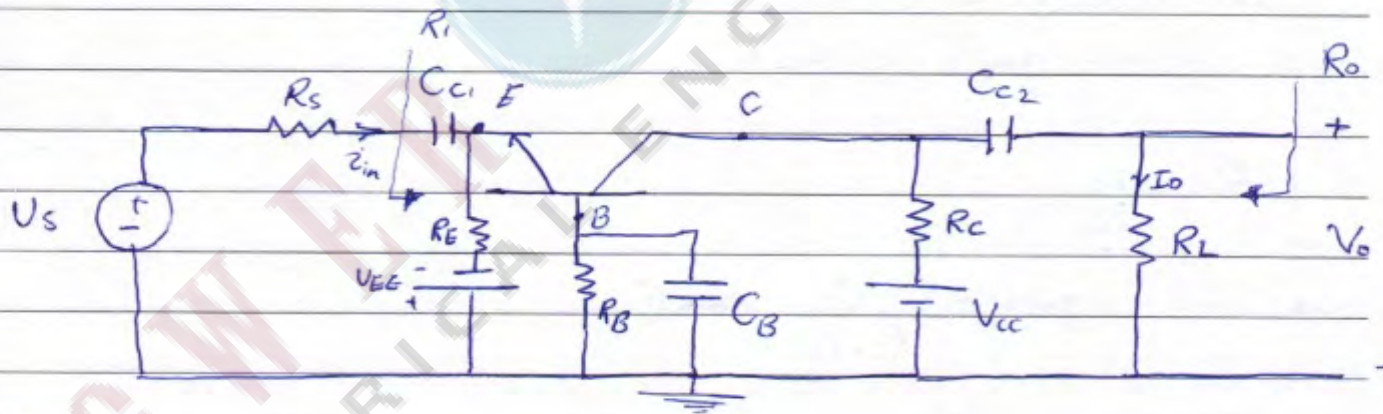1. $A_v > 1$
2. $A_i \approx 1$
3. Small R_i
4. High R_o
5. CB amplifier \equiv Ideal Current Source.
6. used if the input signal is a current.


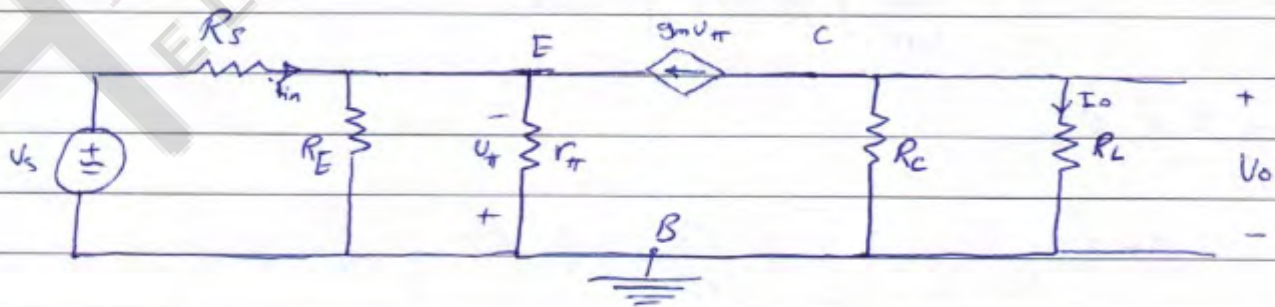
$$\text{find: } A_v = \frac{V_o}{V_s}, \quad A_i = \frac{i_o}{i_{in}}, \quad R_o, \quad R_i$$



* Coupling Capacitor Features:-

1. protect load & the source.
2. protect the location of Q point

$$A_v = \frac{V_o}{V_s} =$$

$$\Rightarrow V_o = -g_m U_{\pi} (R_c \parallel R_L)$$

\Rightarrow KCL at node E

$$g_m U_{\pi} + \frac{U_{\pi}}{r_{\pi}} + \frac{U_{\pi}}{R_E} + \frac{V_s - (-V_{\pi})}{R_s} = 0 \Rightarrow (2)$$

use 1 & 2.

$$A_v = g_m \left(\frac{R_c \parallel R_L}{R_s} \right) \left[\left(\frac{U_{\pi}}{1+\beta} \right) \parallel R_E \parallel R_s \right]$$

if $R_s = 0 \Omega$

$$A_v = g_m (R_c \parallel R_L)$$

$$A_i = \frac{i_o}{i_{in}}$$

$$\Rightarrow I_o = -g_m U_{\pi} \frac{R_c}{R_c + R_L} \Rightarrow (1)$$

KCL at Emitter

$$i_{in} + g_m U_{\pi} + \frac{U_{\pi}}{R_E} + \frac{U_{\pi}}{r_{\pi}} = 0$$

$$U_{\pi} = -i_{in} \left[\left(\frac{r_{\pi}}{1+\beta} \right) \parallel R_E \right] \Rightarrow (2)$$

from 1 & 2

$$A_i = g_m \left(\frac{R_c}{R_c + R_L} \right) \left[\left(\frac{r_{\pi}}{1+\beta} \right) \parallel R_E \right]$$


No. _____

usually for practical CB, R_E very high value
 R_L very small value.

$$A_i \times \frac{g_m r_{\pi}}{1+\beta} = \frac{\beta}{1+\beta} = \alpha = .99 \approx 1$$

CB amplifier

1

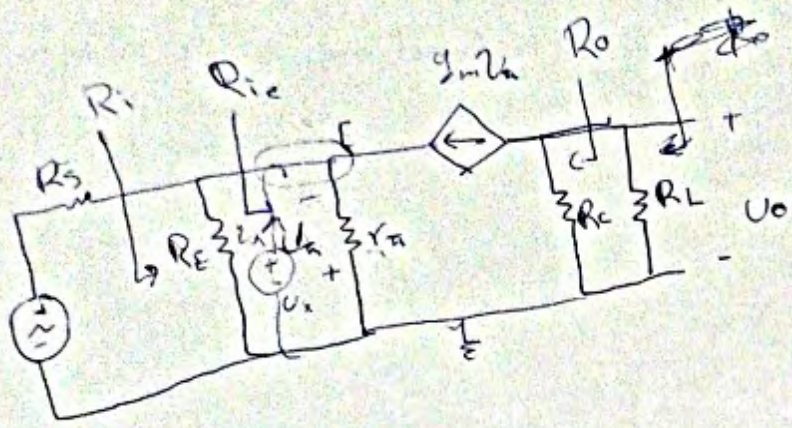

$R_i = R_E \parallel R_{Ee}$


$R_{Ee} = \frac{V_x}{i_x}$

KCL @ node E :- $i_x + \frac{V_{\pi}}{r_{\pi}} + g_m V_{\pi} = 0$

but $V_{\pi} = -V_x \Rightarrow i_x - \frac{V_x}{r_{\pi}} - g_m V_x = 0$

$R_{Ee} = \frac{V_x}{i_x} = \frac{r_{\pi}}{1 + g_m r_{\pi}} = \frac{r_{\pi}}{1 + \beta}$ small value

$R_i = R_E \parallel R_{Ee}$ small value

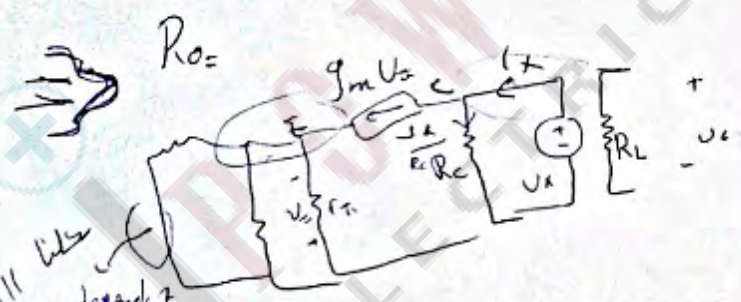

KCL @ c :- $i_x - \frac{V_x}{R_c} - g_m V_{\pi} = 0 \quad \text{--- (1)}$

KCL @ E :- $g_m V_{\pi} + \frac{V_{\pi}}{r_{\pi}} + \frac{V_{\pi}}{R_E} + \frac{V_x}{R_s} = 0 \Rightarrow V_{\pi} (g_m + \frac{1}{r_{\pi}} + \frac{1}{R_E} + \frac{1}{R_s}) = 0$

From (1) $\Rightarrow R_o = \frac{V_x}{i_x} = R_c$

$\therefore V_{\pi} = 0$

First



Multi-stage Amplifier :-

It is used to satisfy some requirements that can't be satisfied by single stage.

Example - CE without R_E


→ has high A_V but unstable

• CE with R_E

⇒ has low A_V but stable

• CC has $A_V = 1$ but high R_i and low R_o

Ex :-

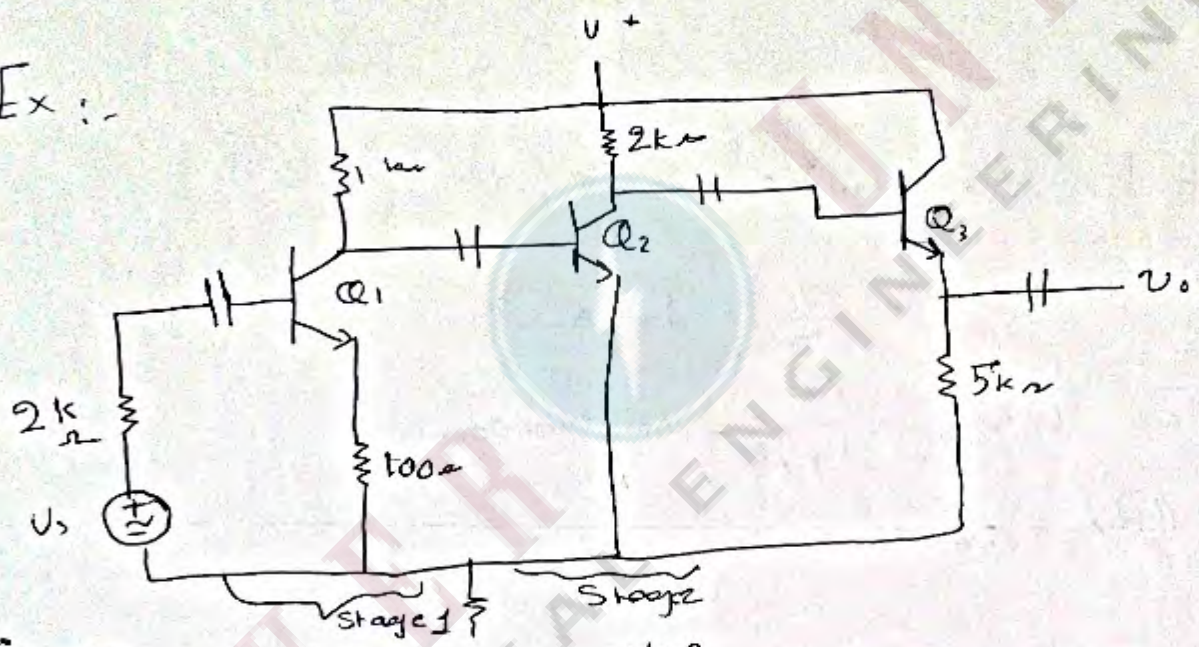

For Q_1 : $\beta = 100$, $r_{\pi} = 1k\Omega$

↳ Q_2 & $Q_3 = \beta = 100$, $r_{\pi} = 0.5k\Omega$

Final $A_V = \frac{V_o}{V_s}$

Solution :-
Stage 1 :- CE w/ R_E


$$A_{V1} = \frac{-\beta R_c}{r_{\pi} + (1+\beta)R_E} \left(\frac{R_i}{R_i + R_s} \right) \Rightarrow R_i = \frac{[r_{\pi} + (1+\beta)R_E] \parallel R_1 \parallel R_2}{\infty}$$

$$R_i = r_{\pi} + (1+\beta)R_E$$

$$A_{V1} = -7.63$$

$$R_o = R_c = 1k\Omega$$

stage 2: CE without RE

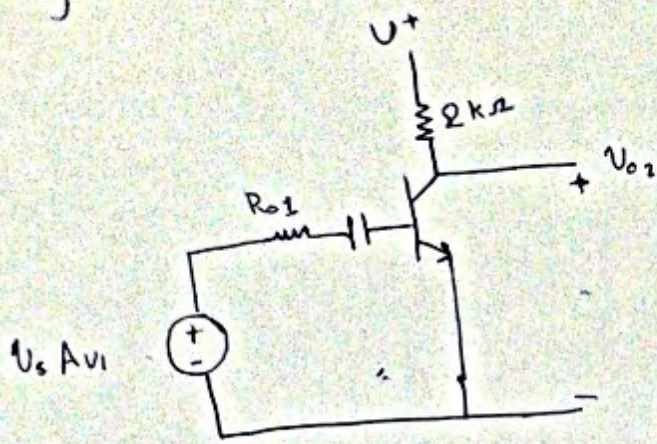


$$A_{V2} = -g_m \left(\frac{R_L \parallel R_C \parallel r_m}{R_L \parallel R_C \parallel r_m + R_{s1}} \right) (R_L \parallel R_C)$$

$$A_{V2} = -133$$

$$R_{o2} = R_C = 2k\Omega$$

Stage 3 :- CC

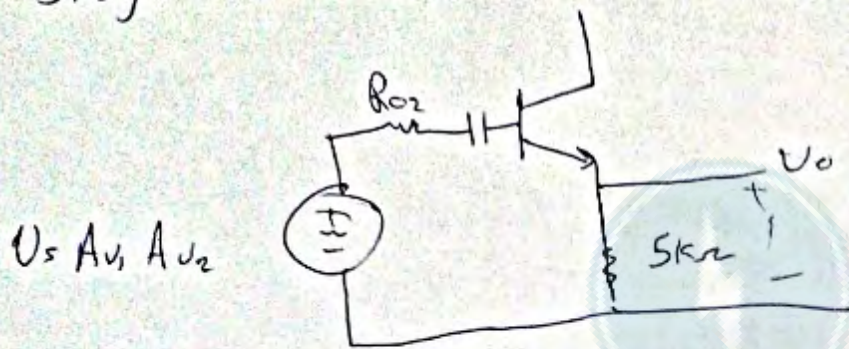

$$A_{V3} = 1$$

$$U_o = U_s A_{V1} A_{V2} A_{V3}$$

$$\therefore A_V = \frac{U_o}{U_s} = A_{V1} A_{V2} A_{V3} = 763 \times -13 \times 1 = -1010$$