
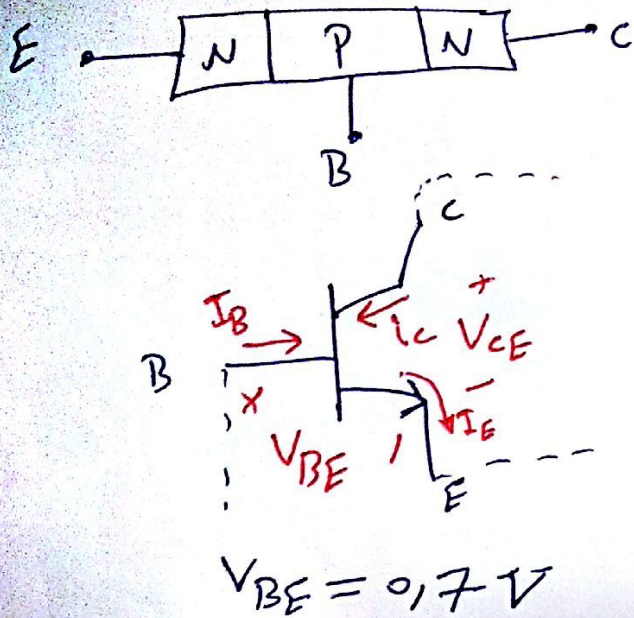


# Amplifier First Material

## NPN

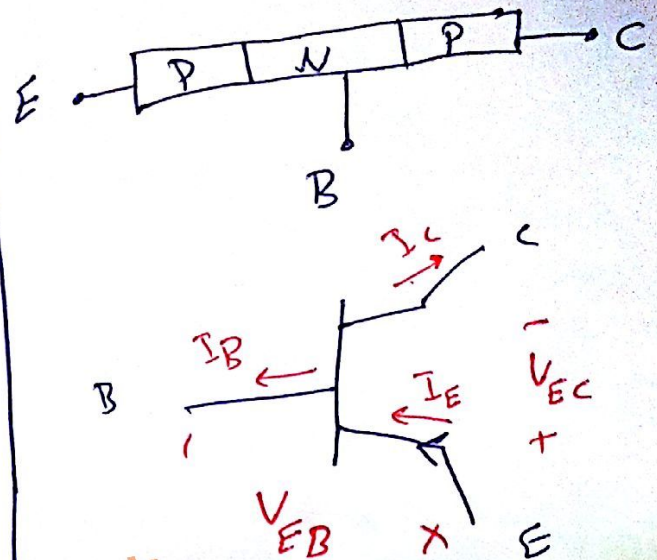

## PNP



Power Unit

$$I_c = \beta I_B$$

$$I_c = \alpha I_E \quad ; \quad \alpha = \frac{\beta}{1 + \beta}$$

$$I_E = I_c + I_B = \beta I_B + I_B = I_B (\beta + 1)$$

Thermal Voltage ( $V_T$ )





$$; \quad \boxed{V_T \approx 0.026}$$


\* **Amplifier** work in Forward active mode (BJT)

$\Rightarrow$  BE  $\Rightarrow$  forward-biased

BC  $\Rightarrow$  Reverse-biased

Note :-

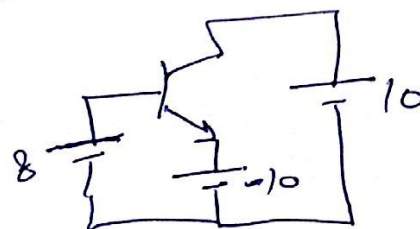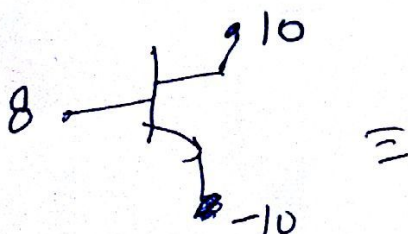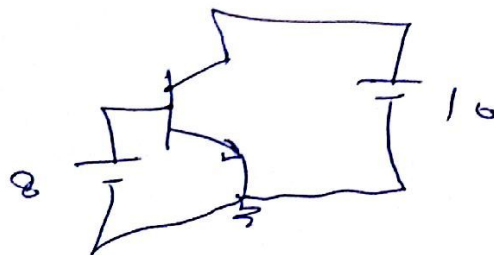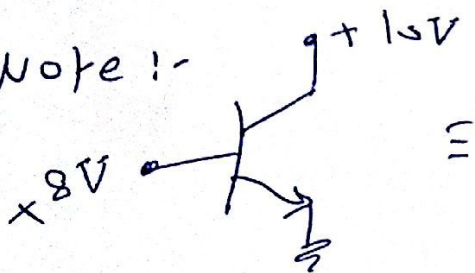

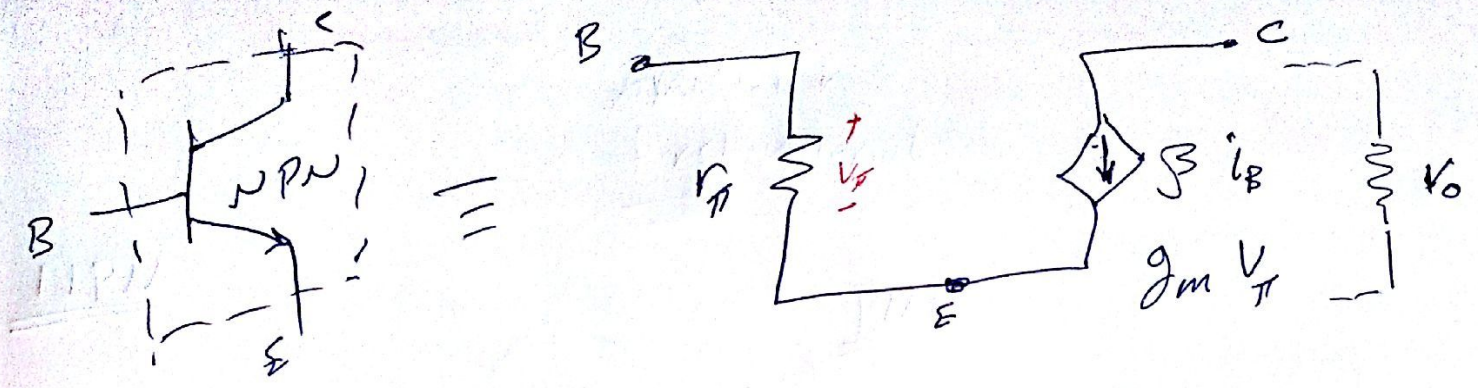

$$r_{\pi} = \frac{V_T}{I_{BQ}} \quad \sim \quad , \quad g_m = \frac{I_{CQ}}{V_T} \quad \sim$$


$$r_o = \frac{V_A \ll \text{given}}{I_{CQ}} \quad \sim$$

\* The steps to solve AMP. CKT

- ① solve the DC ANALYSIS. and find  $I_E, I_B, I_C, V_{CE}, V_{BE}$  and  $g_m$
- ② Draw the AC CKT and find the  $(A_v)$  or any  
 Think you want. ;  $A_v = \frac{V_o}{V_{in}} \equiv \frac{AC}{AC}$

Power Unit

Q. 1:-

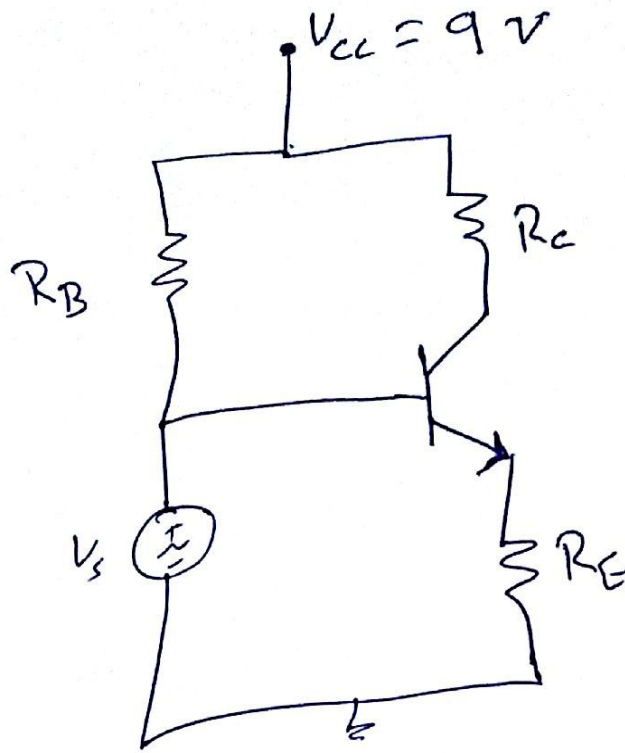

→ What the type of this CKT ??

⇒ we need to specify the output


→ Draw the AC CKT :-

→ find the exp. of  $V_{ce}$  ??

→ find the exp. of  $V_s$

→ find the exp. of  $R_{in}$

Power Unit

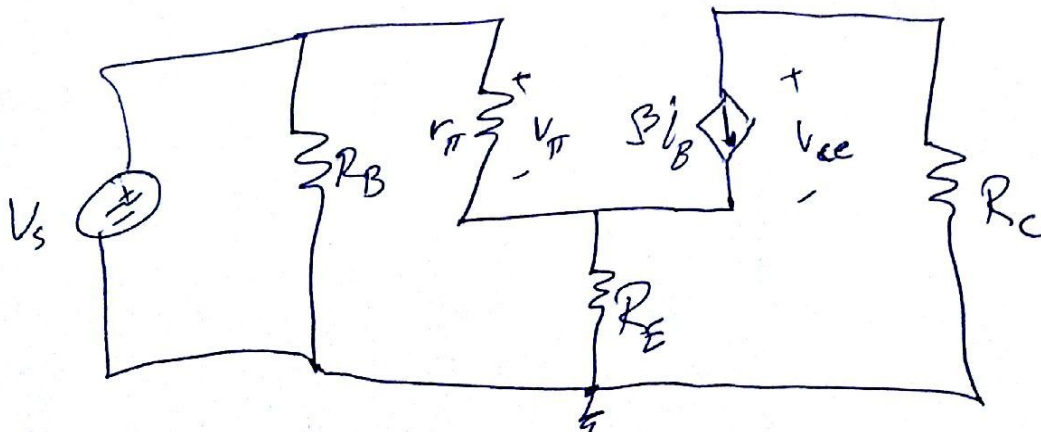

→  $V_{ce} = ?$


$$R_c i_c + V_{ce} + \frac{(1+\beta)}{\beta} i_c R_E = 0$$

② ⇒  $V_{ce} = - \left( R_c + \frac{(1+\beta)}{\beta} R_E \right) i_c$

③  $-V_s + i_b r_{\pi} + i_e R_E = 0$

⇒  $V_s = i_b r_{\pi} + i_e R_E$

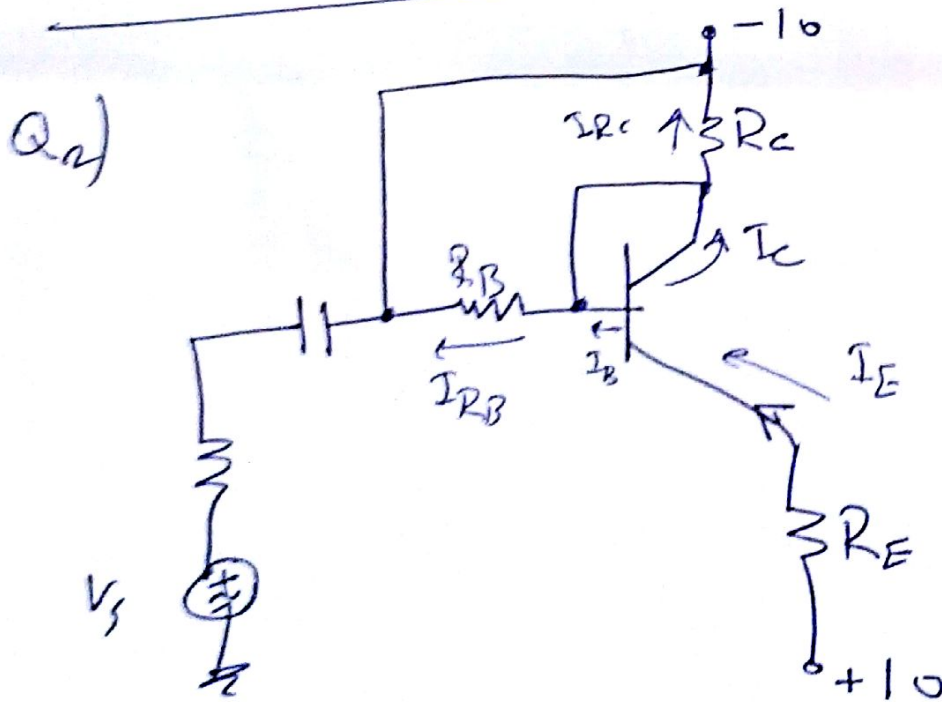④  $R_{in} = R_B \parallel (r_{\pi} + (1+\beta) R_E)$



Amas Kat3  
Power Unit

\* if  $I_E = 1mA$ ,  $\beta = 100$  find  $I_{Rc}$

$$I_{RB} = I_B + (I_C - I_{RC})$$

$$\Rightarrow -10 + I_E R_E + 0,7 + R_B I_{RB} - 10 = 0$$

$$\Rightarrow I_{RB} = \frac{19,3 - R_E}{R_B}$$

Aras kat 3  
Power Unit

$$\Rightarrow I_{RC} = I_C + (I_B - I_{RB})$$

$$= \frac{R_B + R_E - 19,3}{R_B}$$

② if  $R_E = \text{zero}$  find the DC Slope ??


~~DC Slope from output~~

$$\Rightarrow \begin{cases} -10 + V_{EC} + I_{RC} R_C - 10 = 0 \\ -10 + 0,7 + I_{RB} R_B - 10 = 0 \end{cases}$$

$$\text{slope} = \frac{-\beta}{(1+\beta)R_C}$$


Q3)

Power Unit  
Amas kat3

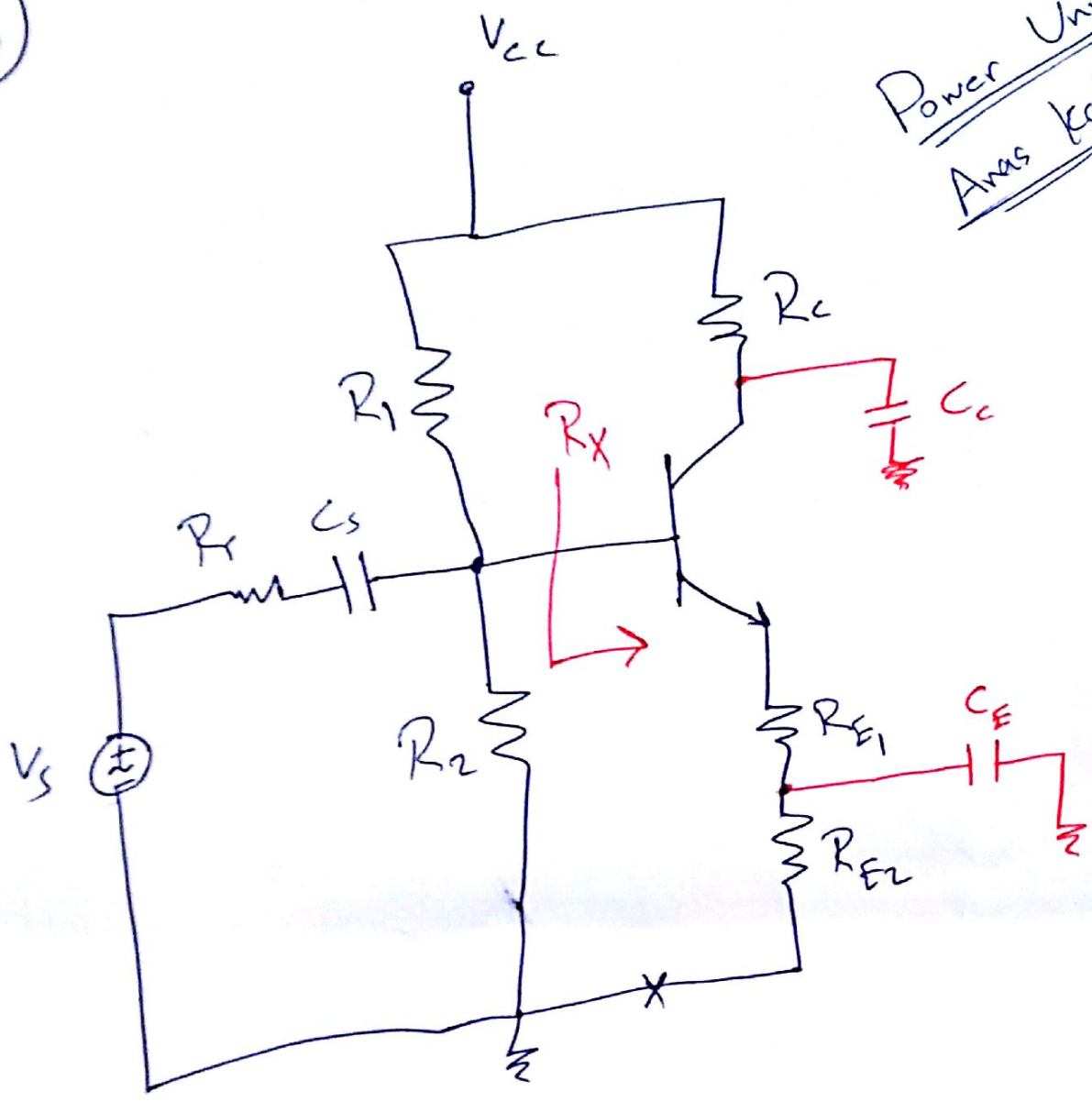

find  $R_o$ ,  $R_x$ ,  $A_v$  ??

Solu. :-

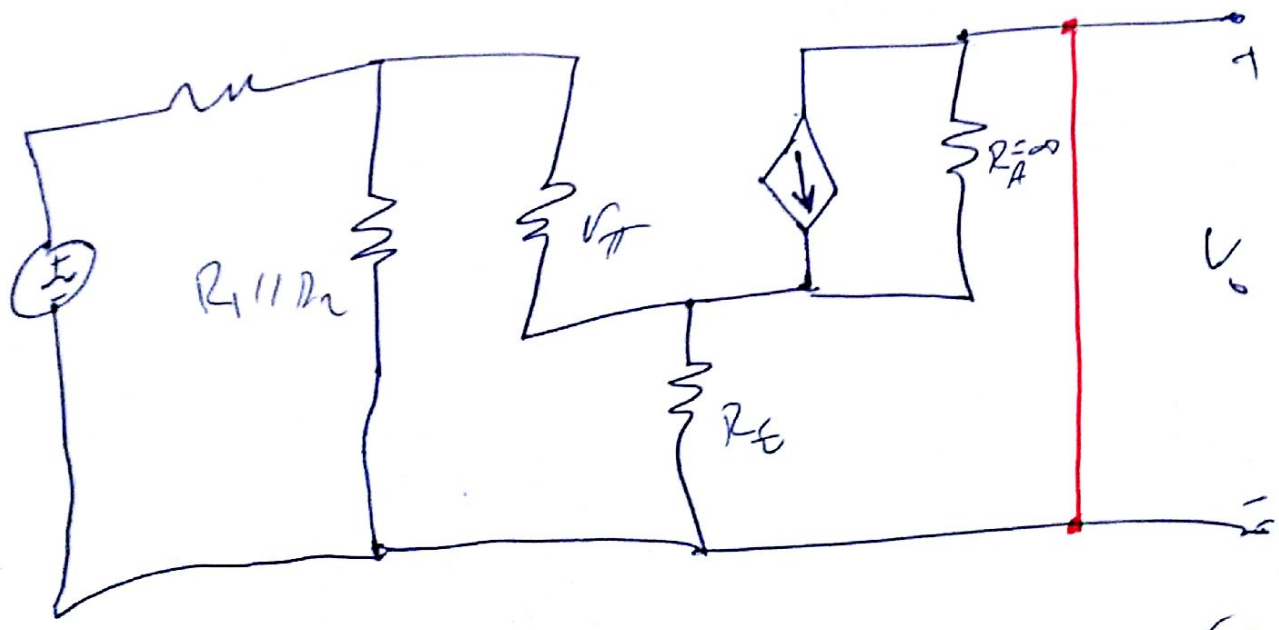

(6)

$$R_{out} = \text{zero}$$

$$A_v = \frac{V_o}{V_{in}} = \frac{\text{zero}}{V_{in}} = \text{zero}$$

$$R_x = r_{\pi} + (1 + \beta) R_{E1}$$

Power Unit  
Amas kat 3