
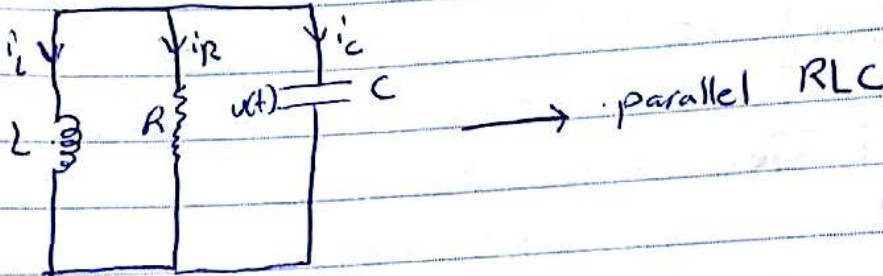


Chapter 8

RLC circuits

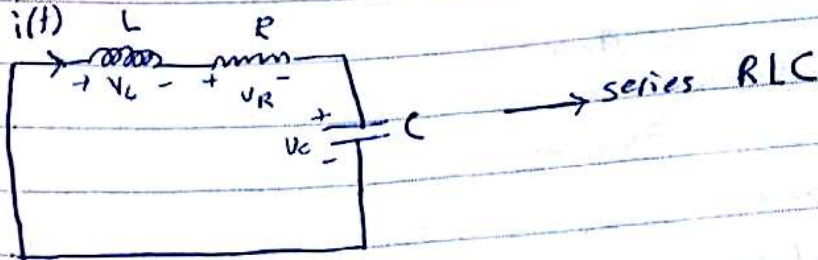

* parallel RLC :-

KCL at upper node :-

$$i_L + i_R + i_C = 0$$

$$\frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0) + \frac{v(t)}{R} + C \frac{dv(t)}{dt} = 0$$

$$C \frac{d^2 v(t)}{dt^2} + \frac{1}{R} \frac{dv(t)}{dt} + \frac{1}{L} v(t) = 0 \quad \text{--- (1)}$$

2nd order homogeneous Diff eq.

→ to solve this eq we need 2 initial conditions $i_L(t_0)$, $v_C(t_0)$


solution

$$v(t) = A e^{st} \rightarrow v = v_0 e^{-t/\tau} \quad \text{parallel RC} \quad \text{--- (2)}$$

Sub (2) in (1)

for $t > 0$

$$V(0) = 60, i_L(0) = -0.3 \text{ A}$$

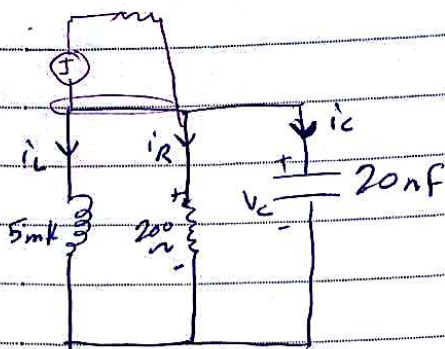

$$\alpha = \frac{1}{2RC} = 125000 \text{ s}^{-1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 100000 \text{ s}^{-1}$$

$\alpha > \omega_0$
overdamping

$$s_1 = -50000 \text{ s}^{-1}$$

$$s_2 = -200000 \text{ s}^{-1} \quad |k_2| > |s_1|$$

$$V(t) = A_1 e^{-50000t} + A_2 e^{-200000t} \quad V_c(t)$$

$$V(0) = 60$$

$$60 = A_1 + A_2 \quad \text{--- (1)}$$

$$\left. \frac{dV(t)}{dt} \right|_{t=0} = \frac{V_c(0)}{C}$$

$$i_C(0) \rightarrow \text{KCL}$$

$$i_C(0) + i_R(0) + i_L(0) = 0$$


$$i_C(0) = -i_R(0) - i_L(0)$$

$$= -\frac{60}{200} - (-0.3)$$

$$= -0.3 + 0.3$$


$$= \text{zero}$$

* Ex 2 Find $V_C(t)$ for $t > 0$

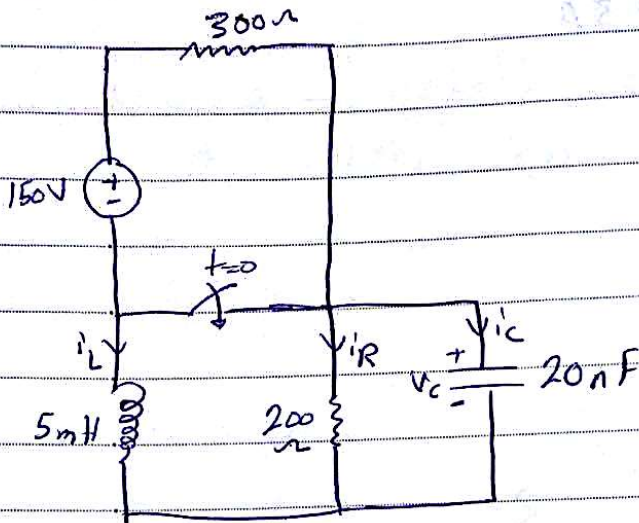

solution for

for $t < 0$

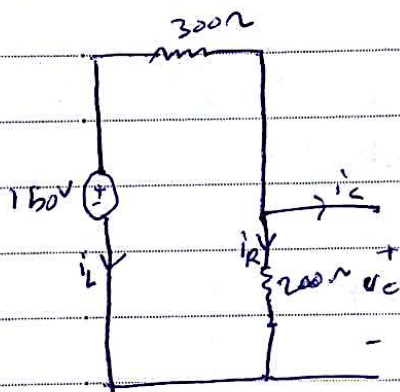

$$V_C(0^-) = V_C(0^+) = V_C(0)$$

$$i_L(0^-) = i_L(0^+) = i_L(0)$$

$$i_R(0^-) \neq i_R(0^+)$$

$$i_L(0^-) \neq i_C(0^+)$$

$$V_C(0^-) = 150 * \frac{200}{500} = 60 \text{ volt} = V_C(0^+)$$

$$V_C(0) = 60 \text{ V}$$

$$i_R(0^-) = \frac{150}{300} = 0.3 \text{ A} \neq i_R(0^+)$$

$$i_L(0^-) = -i_R(0^-) = -0.3 \text{ A} = i_L(0^+)$$

$$i_C(0^-) = 0 \neq i_C(0^+)$$

* Draw ~~Plot~~ $v(t)$

$$v(0) = 0$$

$$v(\infty) = 0$$

$$\frac{dv(t)}{dt} = 84(-e^{-t_m} + 6e^{-6t_m}) = 0 \quad \text{Time maximum time}$$

$$6e^{-6t_m} - e^{-t_m} = 0$$

$$e^{-5t_m} = \frac{1}{6}$$


$$-5t_m = \ln \frac{1}{6}$$

$$t_m = \frac{-1}{5} \ln \left(\frac{1}{6} \right) \text{ s}$$

$$t_m = 0.3528 \text{ s}$$

$$v(t_m) = 84(e^{-t_m} - e^{-6t_m})$$

$$V_m = 48.9 \text{ Volt}$$

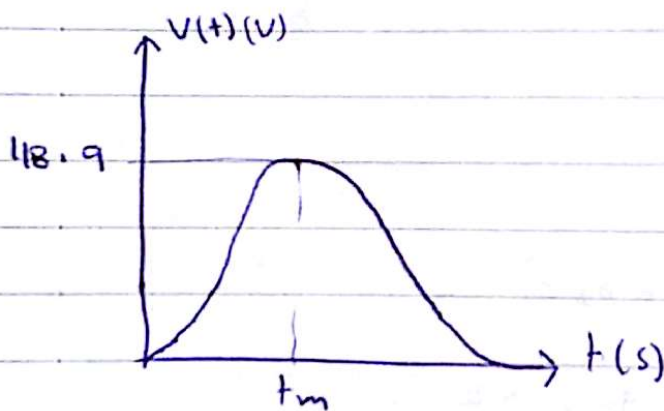

settling time occurs at v less 1% V_m
(t_s)

$$1\% V_m = 0.489 \text{ Volt}$$

→ to find t_s

$$v(t_s) = 84(e^{-t_s} - e^{-6t_s})$$

$$0.489 = 84e^{-t_s} - \cancel{e^{-6t_s}}$$

decay faster

$$t_s = 5.15 \text{ s}$$

capacitor (C), (L), $\omega = 0.315 \text{ rad/s}$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -1 \text{ s}^{-1}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -6 \text{ s}^{-1}$$

$$v(t) = A_1 e^{-t} + A_2 e^{-6t} \quad \text{volt}$$

to find A_1, A_2

$$v(0) = 0 \rightarrow A_1 + A_2 = 0$$

$$A_1 = -A_2$$

$$i(0) = 10 \rightarrow \text{for inductor}$$

* avoid the integral *

$$\text{KCL: } i_c(0) = i_L(0) + i_R(0)$$

$$i_c(0) = 10 + \text{zero} \quad v_L(0) = v_c(0) = \text{zero}$$

$$i_c(0) = 10$$

$$i_c = c \frac{dv(t)}{dt}$$

$$i_c(0) = c \left. \frac{dv}{dt} \right|_{t=0}$$

$$* \left. \frac{dv(t)}{dt} \right|_{t=0} = \frac{i_c(0)}{c}$$

$$\frac{dv(t)}{dt} = -A_1 e^{-t} - 6A_2 e^{-6t}$$

$$\left. \frac{dv(t)}{dt} \right|_{t=0} = -A_1 - 6A_2 = 420$$

$$\text{but } A_1 = -A_2$$

$$A_2 - 6A_2 = 420$$

$$A_2 = -84$$

$$A_1 = 84$$

$$v(t) = 84 \left(e^{-t} - e^{-6t} \right) \text{ volt}$$

* Ex 2

for parallel RLC if $L = 10 \text{ mH}$, $C = 100 \text{ nF}$. Find R to have over damped, under damped and critical damped?

Solution:

① for over damped

$$\alpha > \omega_0$$

$$\frac{1}{2RC} > \frac{1}{\sqrt{LC}}$$

$$2RC < \sqrt{LC}$$

$$R < \frac{\sqrt{LC}}{2C}$$

$$R < 5 \Omega$$

② $r > 5 \Omega$


under damped response

③ $R = 5 \Omega$

critical damped

⊠ The overdamped Response for parallel RLC :

Example 2

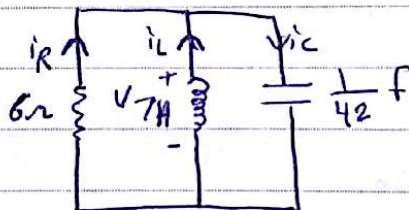

Find $v(t)$ if $v(0) = 0$, $i(0) = 10 \text{ A}$?

Solution:

$$\alpha = 3.5 \text{ s}^{-1}$$

$$\omega_0 = \sqrt{8} \text{ s}^{-1}$$

$\alpha > \omega_0 \rightarrow$ over damped response

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$A_1, A_2, s_1, s_2 \text{ ??}$$

$$s \rightarrow \frac{1}{s} \text{ Freq.}$$

$$\alpha = \frac{1}{2RC} = \text{Neper frequency}$$

$$\frac{1}{\sqrt{LC}} = \omega_0 = \text{Resonant frequency}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

base on α and ω_0

1) $\alpha^2 > \omega_0^2 \rightarrow$ real value for s_1, s_2

overdamped response

2) $\alpha^2 < \omega_0^2 \rightarrow s_1, s_2$ are complex

under damped response

3) $\alpha^2 = \omega_0^2 \rightarrow s_1 = s_2 = -\alpha$

critical damped Response

∴ Define :-

$$(\text{Zeta}) \zeta = \frac{\alpha}{\omega_0} \equiv \text{damping ratio.}$$

$$\zeta > 1 \text{ over damped } \alpha > \omega_0$$

$$\zeta < 1 \text{ under damped } \alpha < \omega_0$$

$$\zeta = 1 \text{ critical damped } \alpha = \omega_0$$

$$CA s^2 e^{st} + \frac{1}{R} A s e^{st} + \frac{1}{L} A e^{st} = 0$$

$$A e^{st} \left(Cs^2 + \frac{s}{R} + \frac{1}{L} \right) = 0$$

$$\cancel{A e^{st}} A e^{st} = 0 \begin{cases} \rightarrow A = 0 \\ \rightarrow s = -\infty \end{cases}$$

[A always zero
Trivial solution

OR

$$Cs^2 + \frac{s}{R} + \frac{1}{L} = 0$$

$$s = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$

$$A = C, \quad B = \frac{1}{R}, \quad C = \frac{1}{L}$$

$$s = \frac{-\frac{1}{R} \pm \sqrt{\left(\frac{1}{R}\right)^2 - 4\frac{1}{L}}}{2C}$$

$$s = \frac{-\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}}{1}$$

$$s_1 = \frac{-\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}}{1}$$

$$s_2 = \frac{-\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}}{1}$$

$$v_1 = A_1 e^{s_1 t} \rightarrow \text{soln}$$

$$v_2 = A_2 e^{s_2 t} \rightarrow \text{soln}$$

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \rightarrow \text{general solution}$$

$$\alpha = \omega_0 = \frac{1}{\sqrt{LC}} = 500 \text{ s}^{-1}$$

$$500 = \frac{1}{2RC}$$

$$R = \frac{1}{2C(500)} = 1 \text{ k}\Omega$$


$$R_1 = 1 \text{ k}\Omega$$

* diff eqn over damped, w/ 1/2 *

b) $v(0^-) = v(0^+) = v(0) = 100 \text{ V}$

if we apply +70, R_2 deleted

so we apply +50

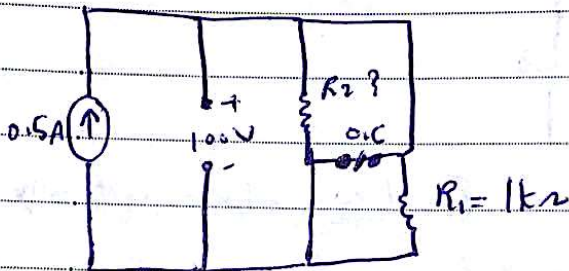


$$i_{R_2} = \frac{0.5 \times 1\text{k}}{1\text{k} + R_2}$$

$$V_{R_2} = i_{R_2} R_2 = 100$$


$$100 = \left(\frac{0.5(1000)}{1000 + R_2} \right) \times R_2$$

$$R_2 = 250 \Omega$$

$$i_L(0^-) = i_{R_2}(0^-) = \frac{0.5 \times 1000}{1250} = 0.4 \text{ A}$$

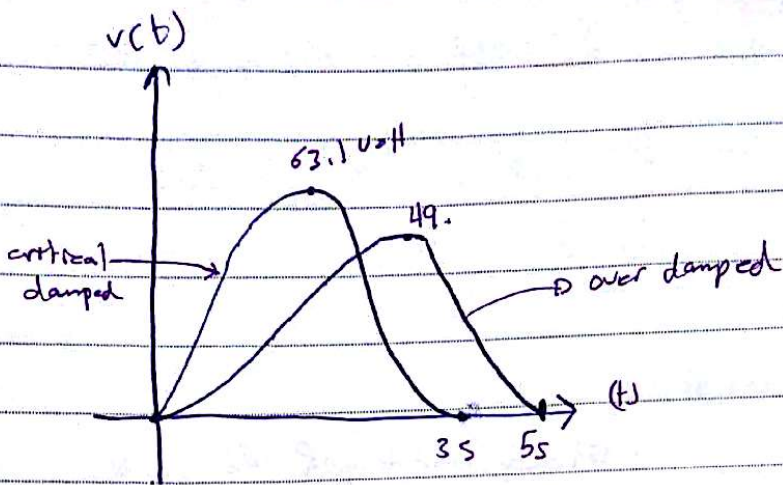

Example 3

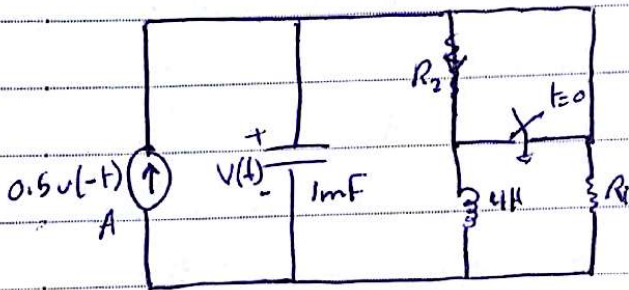


- choose R_1 so that the response for $t > 0$ will be critically damped
- select R_2 to obtain $v(0) = 100 \text{ V}$
- Find $v(t)$ at $t = 1 \text{ ms}$


solution 2

$$0.5 u(-t) = \begin{cases} 0.5, & t < 0 \\ 0, & t > 0 \end{cases}$$

a) for $t > 0$

* For $t < 0$ $v(0) = 100 \text{ V}$

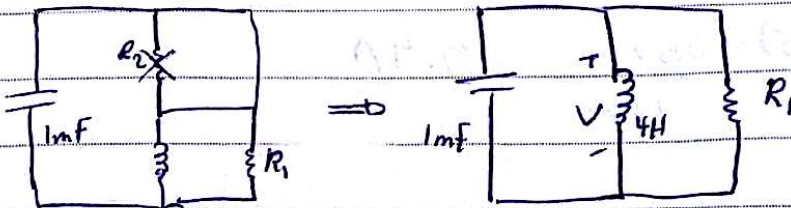

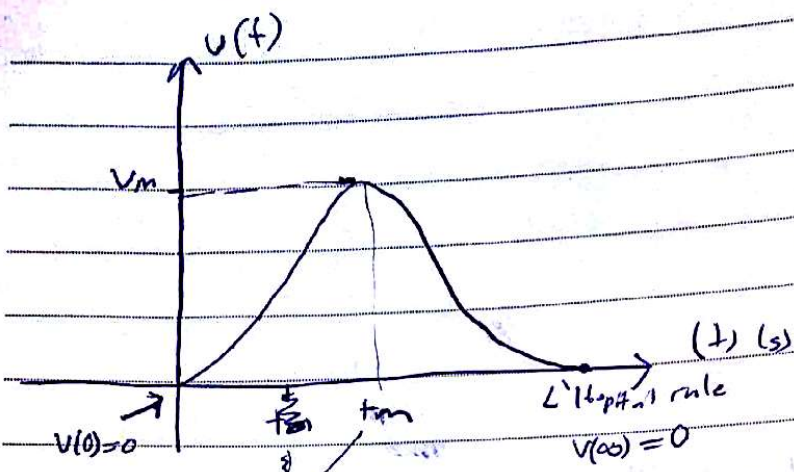

$$\frac{dv(t_m)}{dt_m} = 0$$

$$420 + (-\sqrt{6} e^{-\sqrt{6}t}) + 420 e^{-\sqrt{6}t} = 0$$

$$+\sqrt{6} + 420 t_m e^{-\sqrt{6}t_m} = 420 e^{-\sqrt{6}t_m}$$

$$\sqrt{6} t_m = 1$$

$$t_m = \frac{1}{\sqrt{6}} = 0.4085$$

t_m | t_m | overdamped
critical

$$V(t_m) = 63.1 \text{ Volt}$$

* $t_s \rightarrow V_m$ drop to 1% V_m


$$\frac{V_m}{100} = 0.631 \text{ V}$$

$$0.631 = 420 t_s e^{-\sqrt{6} t_s}$$

$$t_s = 3.12 \text{ s} < t_s$$

over damped
5.15 s

* Critical Damping:

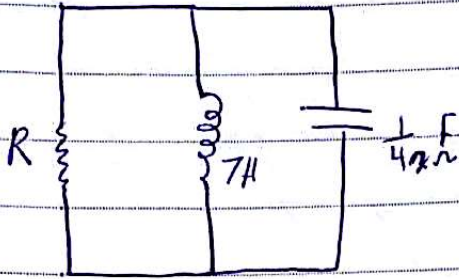

$v(0) = 0, i(0) = 10 \text{ A}$

R? to have critical damped?

$\alpha = \omega_0$

$\frac{1}{2RC} = \frac{1}{\sqrt{LC}} \Rightarrow 4R^2C^2 = LC$
 $L = 4R^2C$

$R = \pm \sqrt{\frac{L}{4C}}$

$R = \pm \sqrt{\frac{7}{4(\frac{1}{42})}}$

$R = 8.57 \Omega$

R under 7Ω is underdamped, 7Ω is critically damped, R over 7Ω is overdamped

$\alpha = \omega_0$ $\alpha > \omega_0$

$\alpha \downarrow R \uparrow$

$\alpha = \frac{1}{2RC} = \sqrt{6} \text{ s}^{-1}$

$\omega_0 = \sqrt{6} \text{ s}^{-1}$

$\alpha = \omega_0 = \sqrt{6} \text{ s}^{-1}$

$s_1 = s_2 = -\alpha = -\sqrt{6} \text{ s}^{-1}$

$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$

$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$

$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$
 $= A_1 e^{-\sqrt{6}t} + A_2 e^{-\sqrt{6}t} = (A_1 + A_2) e^{-\sqrt{6}t}$

solutions:

$v(t) = A_1 t e^{-\sqrt{6}t} + A_2 e^{-\sqrt{6}t}$

* only for identical roots

$v(0) = 0 + A_2 = 0$

$A_2 = 0$

$v(t) = A_1 t e^{-\sqrt{6}t} + 70$

$\frac{dv(t)}{dt} \Big|_{t=0} = \frac{ic(0)}{C} \quad ; \quad i_c = C \frac{dv}{dt}$

$ic(0) = 420 \text{ V/s}$


$A_1 t e^{-\sqrt{6}t} + e^{-\sqrt{6}t} \Big|_{t=0} = 420$
 $A_1 = 420$

$A_1 = 420$

$A_1 = 420 \text{ V}$

$v(t) = 420 t e^{-\sqrt{6}t} + 70$

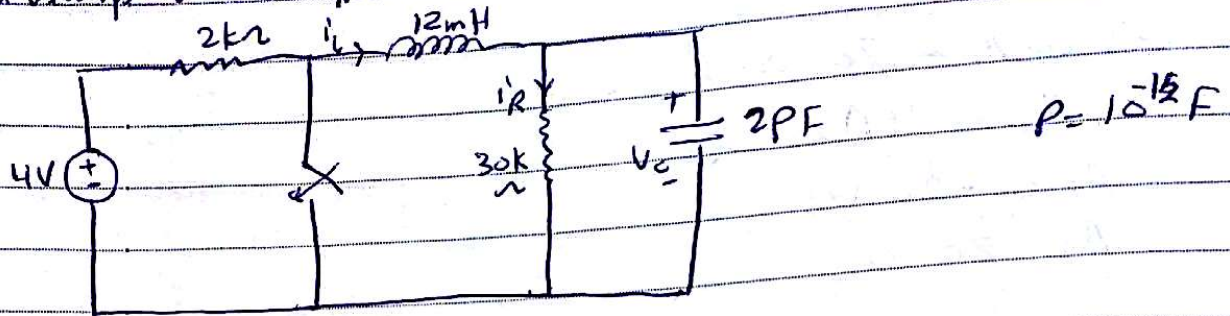* Example: Find $i_R(t)$ for All $t \geq 0$



solution:

$$i_R = \frac{V_C}{30000}$$

$$i_R(0^-) = 125 \mu A \neq i_R(0^+)$$

$$i_L(0^+) = i_L(0^-) = i_L(0) = 125 \text{ mA}$$

$$V_C(0^-) = V_C(0^+) = V_C(0) = 3.75 \text{ Volt}$$

→ over damped ($\alpha > \omega_0$)

$$i_R(t) = 161.3 e^{s_1 t} + 36.34 e^{s_2 t}$$

$$s_1 = -3.063 \times 10^6 \text{ s}^{-1}$$

$$s_2 = -13.6 \times 10^6 \text{ s}^{-1}$$

$$\left. \frac{dv(t)}{dt} \right|_{t=0} = 0$$


$$-50000 A_1 - 200000 A_2 = 0$$

$$A_1 = -4 A_2 \quad \text{--- (2)}$$


$$A_1 = -20 \text{ V}$$

$$A_2 = 80 \text{ V}$$
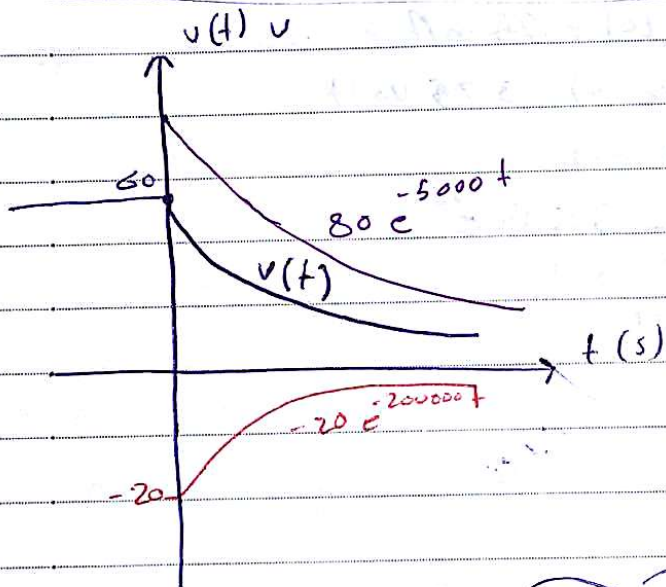
$$v(t) = 80 e^{-5000t} - 20 e^{-20000t} \quad v > 0 \quad t > 0$$



* Source free series RLC circuits :-

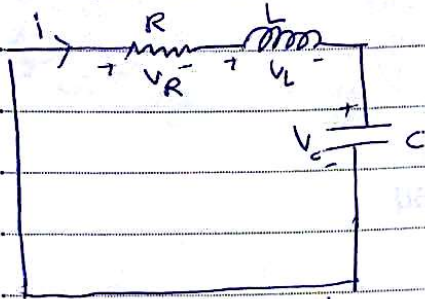

$$\text{KVL} \Rightarrow iR + L \frac{di}{dt} + \frac{1}{L} \int i(t) dt + v(t) = 0 \quad * \text{ 2nd order homog diff equation}$$

derive again :-

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{L} i(t) = 0$$

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad \text{for over damped}$$

$$i(t) = (A_1 t + A_2) e^{-\alpha t} \quad \text{for critical}$$

$$i(t) = e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t) \quad \text{for under damped.}$$

$$\alpha = \frac{R}{2L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 4.75 \text{ rad/s}$$

$$i_L(t) = e^{-1.2t} (B_1 \cos 4.75t + B_2 \sin 4.75t)$$

$$i_L(0) = 2.027$$

$$B_1 = 2.027 \text{ Ampere}$$

$$v(t) \Rightarrow \frac{di}{dt}$$

$$V = L \frac{di}{dt}$$


$$\frac{di}{dt} = \frac{V(t)}{L} = \frac{97.3}{10} = 9.73 \text{ A/s}$$

$$\frac{di(t)}{dt} = e^{-1.2t} (-4.75 B_1 \sin 4.75t + 4.75 B_2 \cos 4.75t) + 1.2 e^{-1.2t} (B_1 \cos 4.75t + 4.75 B_2 \sin 4.75t)$$


$$\left. \frac{di}{dt} \right|_{t=0} = 4.75 B_2 - 1.2(B_1) = 9.73 \text{ A/s}$$

$$B_2 = 2.561 \text{ A}$$
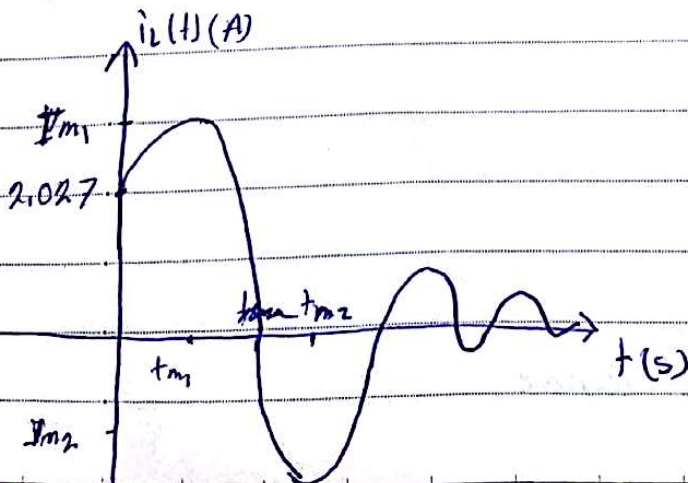
$$i_L(t) = e^{-1.2t} (2.027 \cos 4.75t + 2.561 \sin 4.75t) \text{ A}$$




* Ex 8 Find $i_L(t)$ and plot it

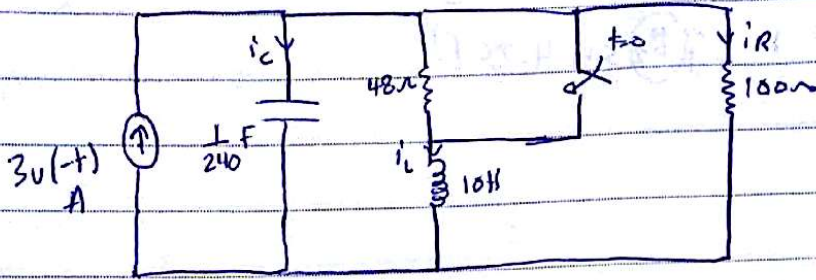

solutions

for $t < 0$

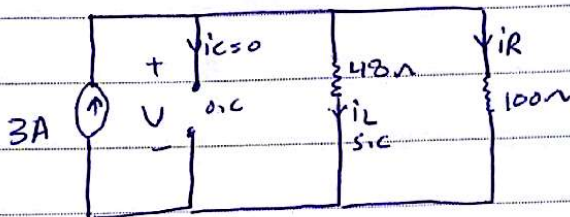

$$i_L(0) = \frac{3 \times 100}{148} = 2.027 \text{ A}$$


$$V(0) = 97.3 \text{ Volt}$$

$$i_L(0) = 2.027 \text{ Ampere}$$

$$V(0) = \left(\frac{300}{148}\right) \times 48 = 97.3 \text{ AV}$$

for $t > 0$

parallel RLC circuits

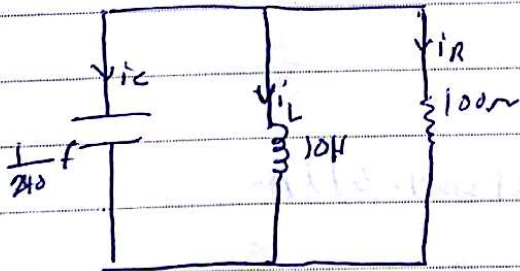


$$\alpha = \frac{1}{2RC} = 1.2 \text{ s}^{-1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 4.899 \text{ s}^{-1}$$

$\omega_0 > \alpha \rightarrow$ under damped response.
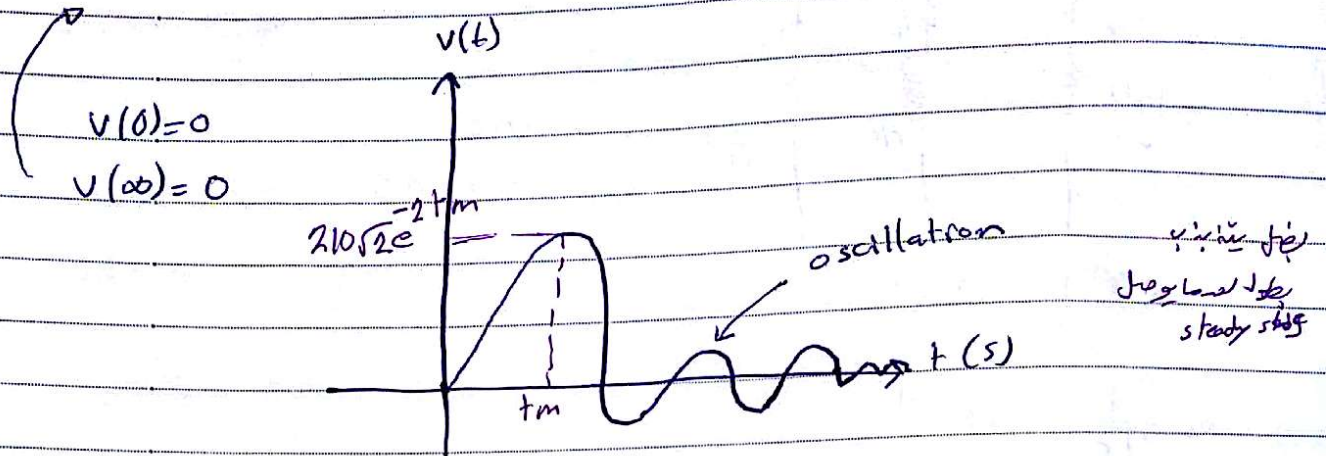
$$v(t) = e^{-2t} (210\sqrt{2} \sin \sqrt{2}t) \text{ V, for } t > 0 \quad \text{(real)}$$



To find maximum values:-

$$\frac{dv(t)}{dt} = 0$$

$$V_{m1} = 71.8 \text{ V} \rightarrow t_{m1} = 0.435 \text{ s}$$


→ Next minimum

$$V_{m2} = -0.845 \text{ V} \rightarrow t_{m2} = 2.66 \text{ s}$$

$$\text{settling time} \rightarrow \frac{V_m}{100} \Rightarrow 0.718 \text{ Volt}$$

$$t_s = 2.92 \text{ s} \quad \left\{ \begin{array}{l} t_s | \\ \text{critical} \end{array} \right. \quad \left\{ \begin{array}{l} t_s | \\ \text{over} \end{array} \right.$$

Example

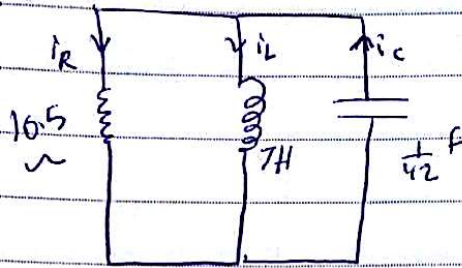

$$v(0) = 0$$

$$i(0) = 10 \text{ A}$$

$$\alpha = \frac{1}{2RC} = 2 \text{ s}^{-1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \sqrt{6} \text{ s}^{-1}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{2} \text{ rad/s}$$

$$v(t) = e^{-\alpha t} (B_1 \cos \omega_d t + j B_2 \sin \omega_d t)$$

$$v(0) = 0$$

$$0 = 1 \times B_1$$

$$\boxed{B_1 = 0}$$

$$\left. \frac{dv(t)}{dt} \right|_{t=0} = \frac{i_C(0)}{C}$$

$$i_R(0^+) = 0, \quad i_C(0^+) = 10$$

$$\left. \frac{dv(t)}{dt} \right|_{t=0} = 420 \text{ volt}$$

$$= e^{-\frac{1}{2}t} (-\sqrt{2} B_1 \sin \sqrt{2} t + j B_2 \sqrt{2} \cos \sqrt{2} t) \cdot (-\frac{1}{2}) + -2 e^{-\frac{1}{2}t} (B_1 \cos \sqrt{2} t + j B_2 \sin \sqrt{2} t)$$

$$420 = j B_2 \sqrt{2}$$

$$B_2 = \frac{-j 420}{\sqrt{2}}$$

$$\boxed{B_2 = -j 210 \sqrt{2} \text{ Volt}}$$

* The Under damped Response

For Parallel RLC circuits

$$\alpha < \omega_0, R \uparrow \alpha \downarrow, \zeta < 1$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$s_{1,2} = -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2}$$

$\omega_0 \rightarrow$ resonant freq
 $\alpha \rightarrow$ Neper freq

$\omega_d =$ Natural resonant frequency (rad/s)

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$s_1 = -\alpha + j\omega_d$ $s_2 = -\alpha - j\omega_d$	complex
---	---------

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \rightarrow \text{for overdamped}$$

$$= A_1 e^{-\alpha t} e^{j\omega_d t} + A_2 e^{-\alpha t} e^{-j\omega_d t}$$

$$\alpha = \frac{1}{2RC} \text{ (real)}$$

$$= e^{-\alpha t} \left[A_1 (\cos \omega_d t + j \sin \omega_d t) + A_2 (\cos \omega_d t - j \sin \omega_d t) \right]$$

$$= e^{-\alpha t} \left\{ (A_1 + A_2) \cos \omega_d t + j (A_1 - A_2) \sin \omega_d t \right\}$$

$$v(t) = e^{-\alpha t} (B_1 \cos \omega_d t + j B_2 \sin \omega_d t)$$

$$B_1 = A_1 + A_2$$

$$B_2 = A_1 - A_2$$

$$c) s_1 = s_2 = -\alpha = -500 \text{ s}^{-1}$$

$$v(t) = A_1 t e^{-500t} + A_2 e^{-500t}$$

$$v(0) = 100 \rightarrow \boxed{A_2 = 100 \text{ Volt}}$$

$$\left. \frac{dv(t)}{dt} \right|_{t=0} = \frac{i_c(0)}{C}$$

$$= 50000 \text{ V/s}$$

$$i_c(0) = i_L(0) + i_R(0)$$

$$= 0.4 + 0.1$$

$$= 0.5$$

$$\left. \begin{array}{l} \text{for } t > 0 \\ \text{for } t < 0 \end{array} \right\}$$

$$\left. \frac{dv(t)}{dt} \right|_{t=0} = A_1 t (-50000 e^{-500t}) + A_1 e^{-500t} - 50000 e^{-500t} = 500000$$

$$e^{-500t} (-500 A_1 t + A_1 - 50000) = 500000$$

$$e^{-500t} = 500000 \quad \times$$

$$-500 A_1 t + A_1 - 50000 = 500000$$

$$A_1 = 1150000 \text{ at } t=0$$

$$\boxed{v(t) = 1150t e^{-500t} + \frac{0.1}{500} e^{-500t} \text{ kV}} \quad t > 0$$

$$v(t) = \dots$$

$$i(t) = C \frac{dv(t)}{dt}$$

$$i(t) = 0.25 \left(\frac{1}{3} (16e^{-t} - 4e^{-4t}) \right)$$

$$= \frac{16}{3} e^{-t} - \frac{4}{3} e^{-4t} \quad \text{Ampere}$$

→ For $R = 4 \Omega$

$$i(0) = 4.8 \text{ A}$$

$$v(0) = 4.8 \text{ Volt}$$

$$\alpha = 2 \text{ s}^{-1}, \quad \omega_0 = 2 \text{ s}^{-1} \rightarrow \text{critical}$$

$$s_1 = s_2 = -\alpha = -2 \text{ s}^{-1}$$

$$v_f = 24 \text{ Volt}$$

$$v(t) = 24 + (A_1 t + A_2) e^{-2t} \text{ V}$$

$$v(t) = 24 - 19.2 (t+1) e^{-2t} \text{ Volt}$$

$$i(t) = (9.6t + 4.8) e^{-2t} \text{ Ampere}$$

→ For $R = 1 \Omega$

$$i(0) = 12 \text{ A}$$

$$v(0) = 12 \text{ V}$$

$$\alpha = 0.5 \text{ s}^{-1}, \quad \omega_0 = 2 \text{ s}^{-1} \rightarrow \text{under damped}$$

$$\omega_d = 1.936 \text{ rad/s}$$

$$v_f = 24 \text{ Volt}$$

$$v(t) = 24 + (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t} \text{ Volt}$$

$$A_1 = 21.694 \text{ Volt}$$


$$A_2 = -12 \text{ Volt}$$

$$i(t) = (3.15 \sin 1.936 t + 12 \cos 1.936 t) e^{-0.5t} \text{ Ampere}$$

$$s_1 = -2.5 - \sqrt{(2.5)^2 - (2)^2} = -1 \text{ s}^{-1}$$

$$s_2 = -2.5 + \sqrt{(2.5)^2 - (2)^2} = -4 \text{ s}^{-1}$$

at $t = \infty$

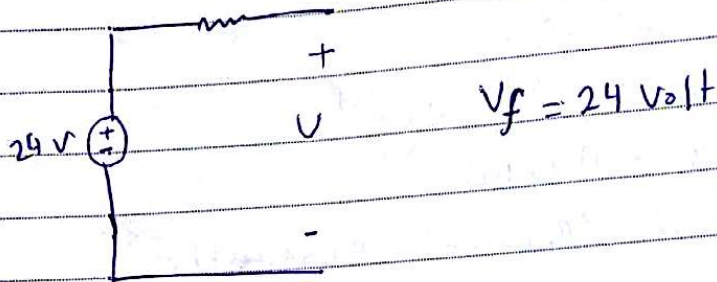

$$v(t) = 24 + A_1 e^{-t} + A_2 e^{-4t} \text{ V}, t > 0$$

from $t \rightarrow \infty \rightarrow v(\infty) = 4 \rightarrow \boxed{A_1 + A_2 = -20} \text{ --- (1)}$

$$\left. \frac{dv(t)}{dt} \right|_{t=0} = \frac{i_L(0)}{C} = \frac{4}{0.25} = 16 \text{ V/s}$$

$$\frac{dv(t)}{dt} = -A_1 e^{-t} - 4A_2 e^{-4t}$$

$$\boxed{-A_1 - 4A_2 = 16} \text{ --- (2)}$$

$$A_1 = -\frac{64}{3} \text{ V}, \quad A_2 = \frac{4}{3} \text{ V}$$

$$v(t) = \left(24 + -\frac{64}{3} e^{-t} + \frac{4}{3} e^{-4t} \right)$$

$$v(t) = 24 + \frac{4}{3} \left(-16 e^{-t} + e^{-4t} \right) \text{ volt}, t > 0$$

⊠ complete response for the RLC circuits

(Step Response)

$$v(t) = \overset{\text{forced}}{v_f} + v_n$$

$$= v_{ss} + v_n$$

Over damped :- $v(t) = v_f + A_1 e^{\alpha_1 t} + A_2 e^{\alpha_2 t}$


critical :- $v(t) = v_f + (A_1 t + A_2) e^{-\alpha t}$

under damped :- $v(t) = v_f + (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t}$

at $t \rightarrow \infty$
 $L \rightarrow \text{SC}$
 $C \rightarrow \text{OC}$

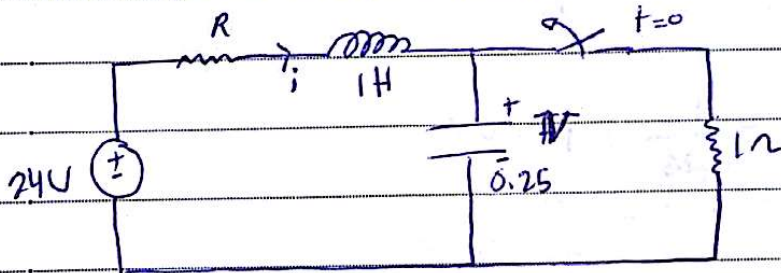
Example :-

Find $v(t)$ and $i(t)$ for $t > 0$, for $R = 5 \Omega$, $L = 1 \text{ H}$, $C = 1 \mu\text{F}$?




solution :-

→ for $R = 5 \Omega$

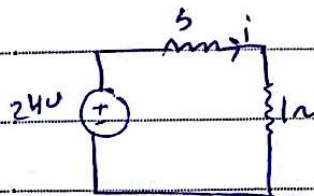

$i_L(0^-) = \frac{24}{5} = 4 \text{ A}$ for $t < 0$ } initial conditions
 $i_C(0) = 4 \text{ V}$

for $t > 0$

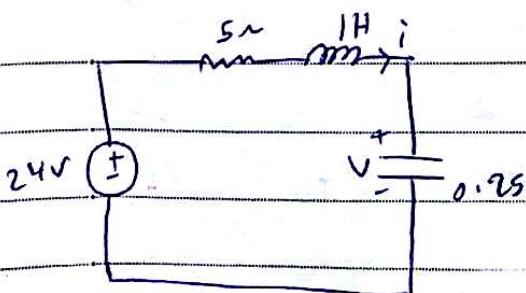



$$\alpha = \frac{R}{2L} = 2.5 \text{ s}^{-1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 2 \text{ s}^{-1}$$

$\alpha > \omega_0 \rightarrow$ over damped

Drum Series RLC
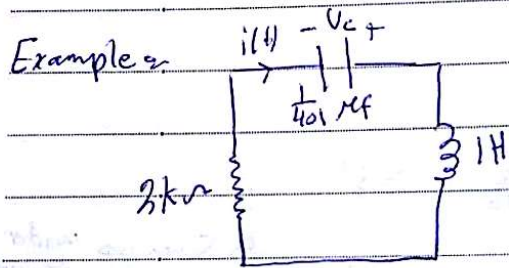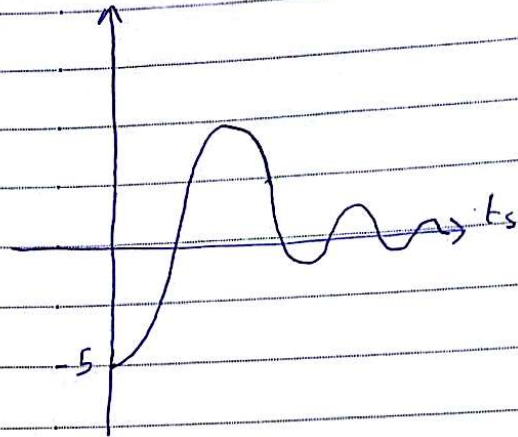
$$v_c(t) = e^{-0.97t} (-5 \cos 9.968t + 0.413 \sin 9.968t) \text{ V } t > 0$$



Find and sketch $i(t)$?

if $i(0) = 2 \text{ mA}$
 $v_c(0) = 2 \text{ V}$

Solution:

Series RLC


$$\alpha = 1000 \text{ s}^{-1}, \quad \omega_0 = 2025 \text{ s}^{-1} \rightarrow \text{under damped}$$


$$\omega_d = 2000 \text{ rad/s}$$

$$i(0) = 2 \text{ mA} = B_1$$

$$B_2 = 0$$
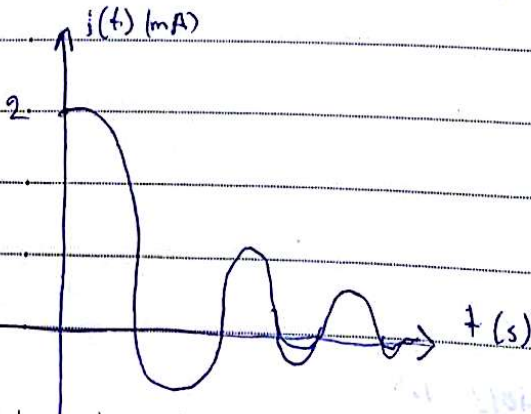
$$i(t) = 2e^{-1000t} (\cos 2000t) \text{ mA}$$



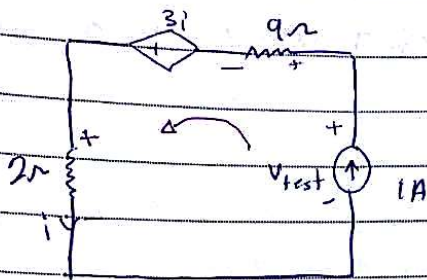


$$i = 1 \text{ A}$$

KVL eqn

$$+2i + -3i + -9i + V_{\text{test}}$$

$$V_{\text{test}} = 8 \text{ Volt}$$
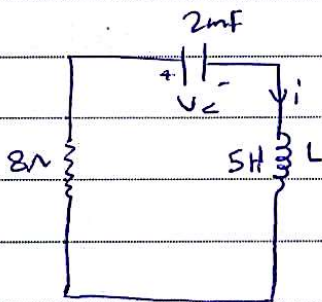
$$R_{th} = \frac{V_{\text{test}}}{I_{\text{test}}} = \frac{8}{1} = 8 \Omega$$



$$\alpha = \frac{R}{2L} = \frac{8}{10} = 0.8 \text{ s}^{-1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 10 \text{ rad/s}$$

$\alpha < \omega_0 \Rightarrow$ under damped

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 9.968 \text{ rad/s}$$

$$V_c(t) = e^{-0.8t} (B_1 \cos 9.968t + B_2 \sin 9.968t) \text{ Volt}$$

$$V_c(0) = -5 \quad \boxed{B_1 = -5 \text{ Volt}}$$

$$\frac{dV_c(t)}{dt} \Big|_{t=0} = \frac{i_c(0)}{C}$$


$$i_c(0) = i_L(0) = 0$$

$$\frac{dV_c(t)}{dt} = \dots$$

$$\boxed{B_2 = -0.4013 \text{ Volt}}$$


* Example 2

find $v(t)$ for $t > 0$

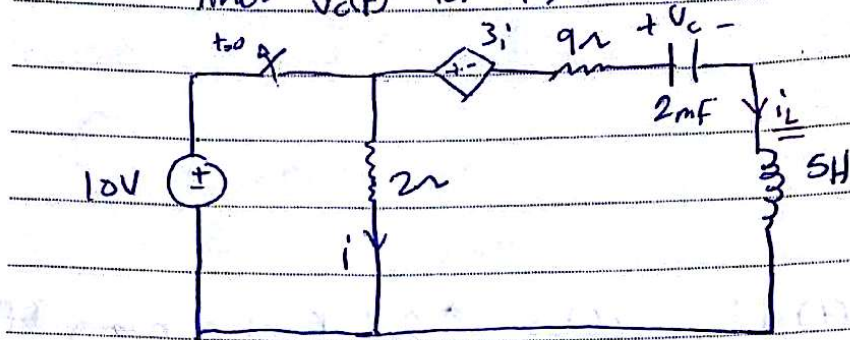

for $t < 0$

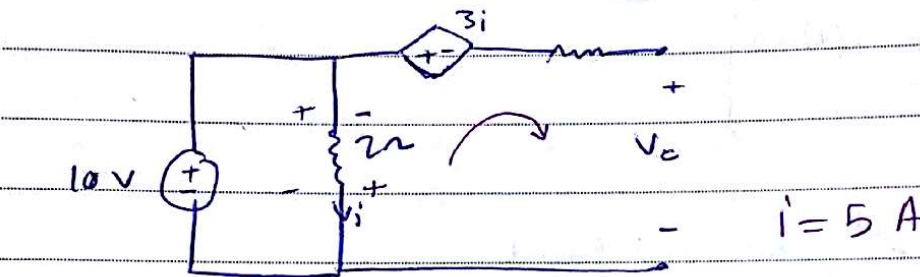switch closed, $L \rightarrow s.c$, $C \rightarrow o.c$




$$i_L(0^-) = 0 = i_L(0)$$

$$v_c(0^-) = 10 - 15$$


$$v_c(0^-) = -5 \text{ volt} = v_c(0)$$

} initial conditions

for $t > 0$

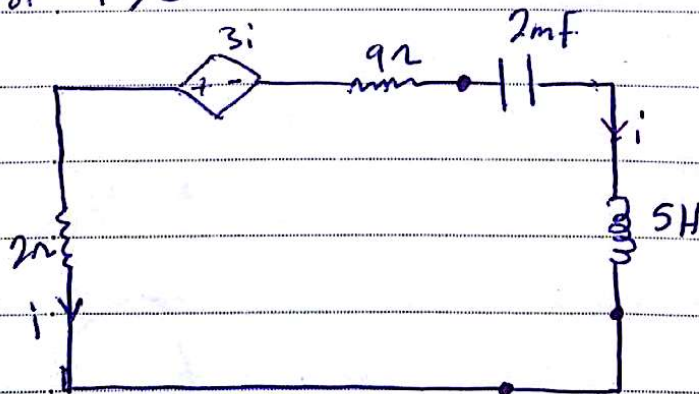


Thevenin's eqn

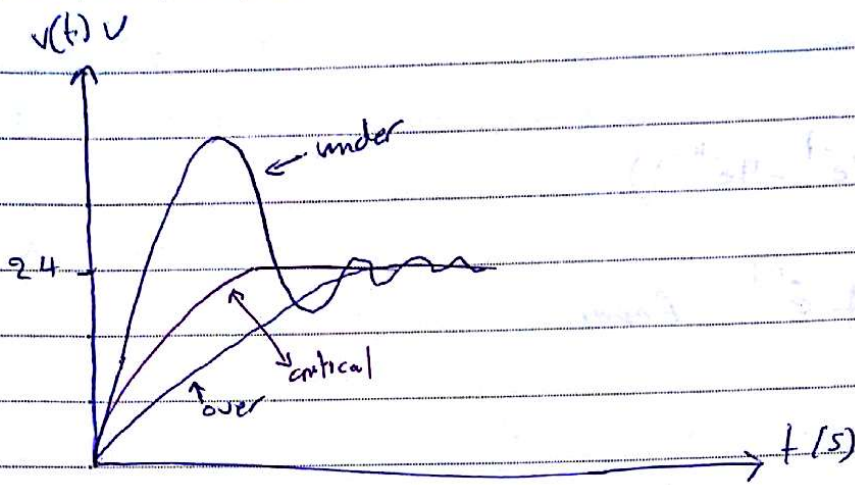

* LC circuit Lossless critical

($R=0 \rightarrow$ series RLC)

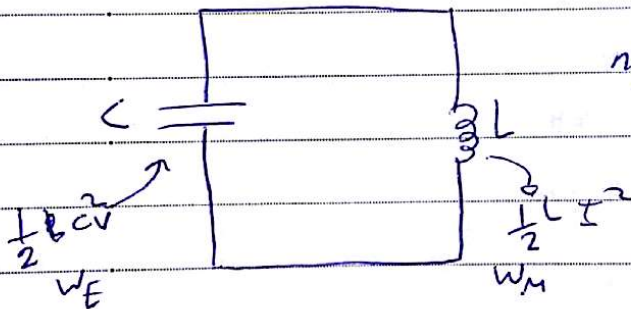($R \rightarrow \infty \rightarrow$ parallel RLC)



not practical



$$\alpha = \frac{1}{2RC} = \frac{1}{\infty} = 0$$

$$\alpha = \frac{R}{2L} = 0$$

There is no damping function we solve this by $\sin \omega t$ or $\frac{\cos \omega t}{e^{-\alpha t}} = 1$

Ch. 10

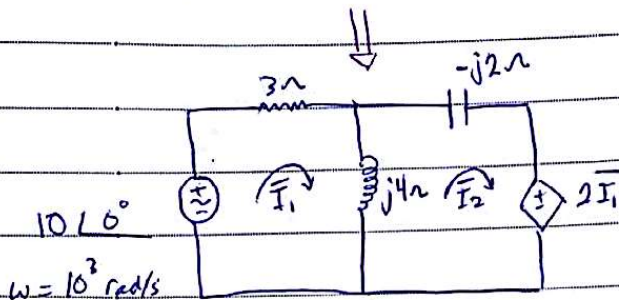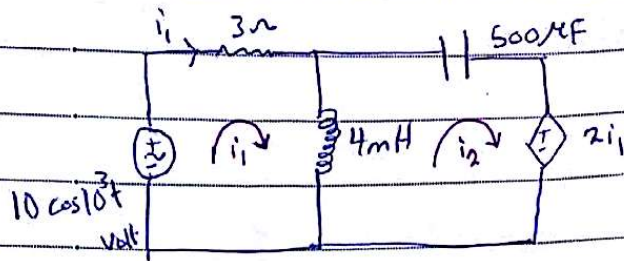* Ex 2 Find the time domain currents $i_1(t)$, and $i_2(t)$?



KVL at Mesh (1) =

$$-10 \angle 0^\circ + 3\bar{I}_1 + j4(\bar{I}_1 - \bar{I}_2) = 0$$

$$(3 + j4)\bar{I}_1 - j4\bar{I}_2 = 10 \quad \text{--- ①}$$

$$10 \angle 0^\circ = 10 \cos 0^\circ + j10 \sin 0^\circ = 10$$

KVL at mesh (2) =

$$+j4(\bar{I}_2 - \bar{I}_1) - j2\bar{I}_2 + 2\bar{I}_1 = 0$$

$$(2 - j4)\bar{I}_1 + j2\bar{I}_2 = 0 \quad \text{--- ②}$$

from ② =

$$\bar{I}_2 = \frac{-(2 - j4)\bar{I}_1}{j2}$$

$$\bar{I}_2 = \frac{j(2 - j4)\bar{I}_1}{2}$$

$$\bar{I}_2 = \frac{-(j2 + 4)\bar{I}_1}{2}$$

$$\bar{I}_2 = -(j + 2)\bar{I}_1 \text{ subm ①}$$

$$(3 + j4) \bar{I}_1 - j4(2 + j) \bar{I}_1 = 10$$

$$(3 + j4) \bar{I}_1 - j8 \bar{I}_1 + 4 \bar{I}_1 = 10$$

$$7 \bar{I}_1 - j4 \bar{I}_1 = 10$$

$$\bar{I}_1 = \frac{10}{7 - j4}$$

$$\bar{I}_1 = 10 \angle 0^\circ$$


$$\sqrt{49 + 16} \angle \tan^{-1} \frac{-4}{7}$$

$$\bar{I}_1 = 1.24 \angle 29.7^\circ \text{ A}$$

$$\bar{I}_2 = 2.77 \angle 56.3^\circ \text{ A}$$


$$i_1(t) = 1.24 \cos(10^3 t + 29.7^\circ) \text{ A}$$
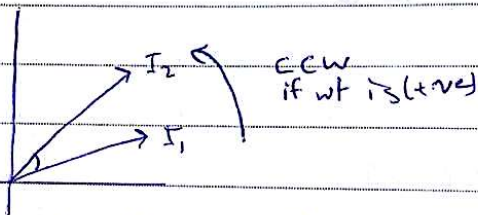
$$i_2(t) = 2.77 \cos(10^3 t + 56.3^\circ) \text{ A}$$



i_2 lags i_1 by $(56.3 - 29.7^\circ)$

* Ex =

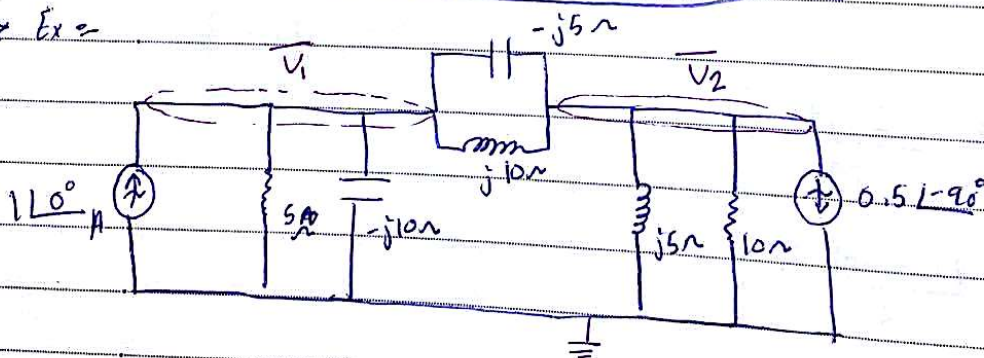

* Nodal → (find the Nodal voltages)

3 nodes

angle $0^\circ \rightarrow 1$

$$-1 + \frac{\bar{V}_1}{5} + \frac{\bar{V}_1}{-j10} + \frac{\bar{V}_1 - \bar{V}_2}{j10} + \frac{\bar{V}_1 - \bar{V}_2}{-j5} = 0$$

$$-1 + \frac{\bar{V}_1}{5} + \frac{j\bar{V}_1}{10} + \frac{-j(\bar{V}_1 - \bar{V}_2)}{10} + \frac{j(\bar{V}_1 - \bar{V}_2)}{5} = 0$$

$$(0.2 + j0.2)\bar{V}_1 + (-j0.1)\bar{V}_2 = 1 \quad \text{--- (1)}$$

KCL for node (2) =

$$0.5 \angle -90^\circ = 0.5 \angle 0^\circ + j5 \angle -90^\circ = -j0.5$$

$$-j0.5 + \frac{\bar{V}_2}{10} + \frac{\bar{V}_2}{j5} + \frac{\bar{V}_2 - \bar{V}_1}{j10} + \frac{\bar{V}_2 - \bar{V}_1}{-j5} = 0 \quad \text{--- (2)}$$


$$\bar{V}_1 = 2.24 \angle -63.4^\circ \text{ V} = \boxed{1 - j2 \text{ V}}$$

$$\bar{V}_2 = 4.47 \angle 116.6^\circ \text{ V} = -2 + j4 \text{ V}$$

$$v_1(t) = 2.24 \cos(\omega t - 63.4^\circ) \text{ V}$$

V_2 leads by $(116.6 + 63.4)$

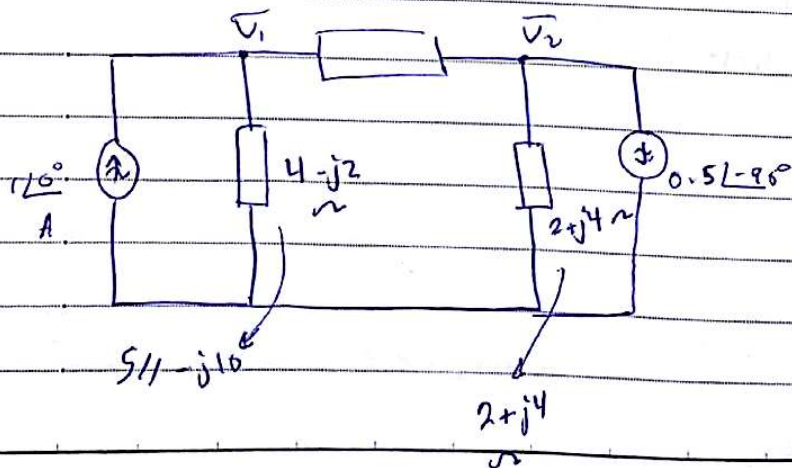- * Voltage leads I \rightarrow Inductive
- * Voltage lags I \rightarrow capacitive
- * V, I same angle \rightarrow in phase



Use source transformation

* Find \bar{V}_1 using super position
 linear circuit, Independent can't be killed

\bar{V}_1 due to $1\angle 0^\circ$ source, $0.5\angle -90^\circ \rightarrow$ open circuit

$$\bar{Z}_{eq} = (-j10 + 2 + j4) // (4 - j2)$$

$$= (2 - j6) // (4 - j2)$$

$$= 2 + j2 \Omega$$

$$\bar{V}_1' = 1(2 + j2) = 2 + j2 \text{ Volt}$$


\bar{V}_1 due to $0.5\angle -90^\circ$ source only

CDR =

$$\bar{V}_1' = (4 - j2) * \left(\frac{-j0.5 * 2 + j4}{(4 - j2 - j10) + (2 + j4)} \right)$$

$$\bar{V}_1'' = (4 - j2) * (-j0.5) \left(\frac{2 + j4}{6 - j2} \right)$$

$$\bar{V}_1'' = -1 \text{ Volt}$$

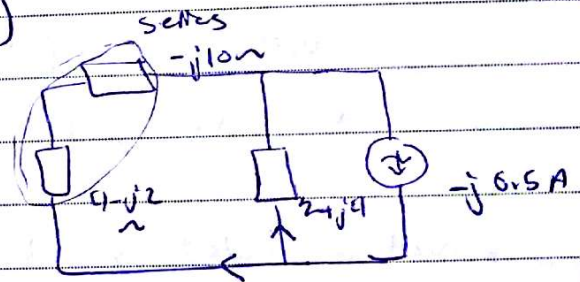

$$\bar{V}_1 = \bar{V}_1' + \bar{V}_1''$$


$$= 2 + j2 - 1$$

$$\bar{V}_1 = 1 + j2 \text{ Volt}$$

* Find Thevenin's eq as seen by $-j10\Omega$ then find \bar{V}_1

$$\bar{Z}_{th} = 4 - j2 + 2 + j4$$

$$= 6 + j2 \Omega$$

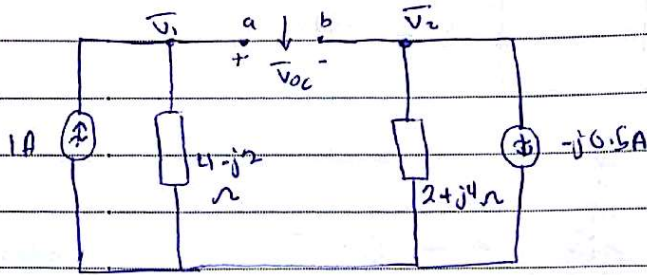


$$\bar{V}_{OC} = \bar{V}_1 - \bar{V}_2$$


$$= 1(4 - j2) - (2 + j4)(+j0.5)$$

$$= 4 - j2 - j1 + 2$$
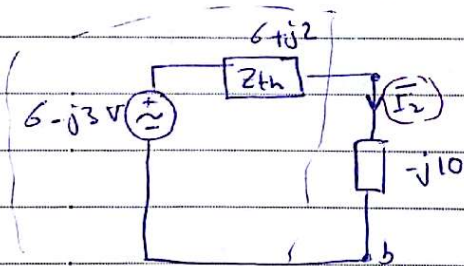
$$\bar{V}_{OC} = \bar{V}_{th} = 6 - j3 \text{ V}$$



Find \bar{V}_1 in the original circuit

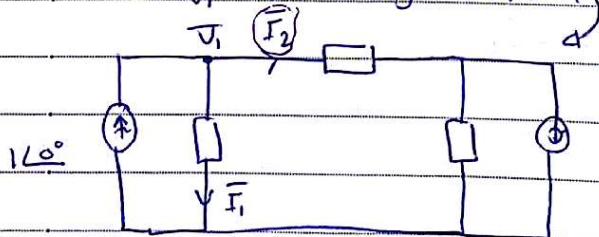

$$\bar{I}_2 = \frac{6 - j3}{6 + j2 - j10} = 0.06 + j0.3 \text{ A}$$

$$\bar{I}_1 = 1 - \bar{I}_2 = 0.4 - j0.3 \text{ A}$$



$$\bar{V}_1 = (0.4 - j0.3)(4 - j2)$$

$$\bar{V}_1 = 1.6 - j0.8 - j1.2 - 0.6$$

$$\bar{V}_1 = 1 - j2 \text{ V}$$

For two different frequencies use only superposition

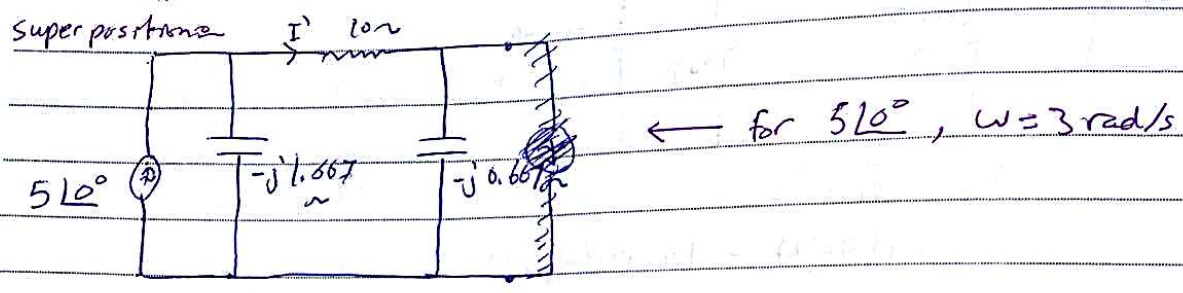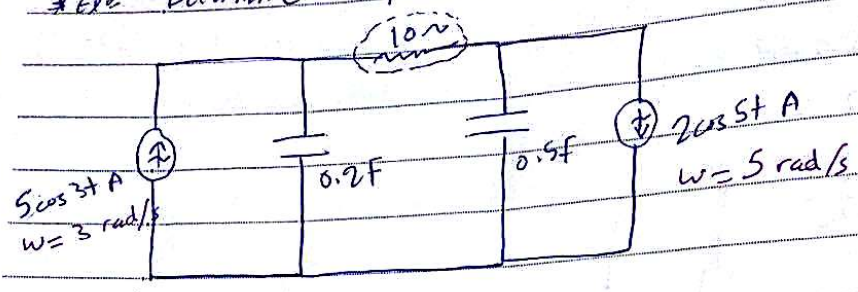* Ex. Determine the power dissipated by the 10Ω resistor




CDR =

$$I' = 5 \left(\frac{-j1.667}{10 - j1.667 - j0.667} \right)$$

$$I_1 = 811.71 \angle -76.86^\circ \text{ mA}$$

for $2L^\circ$ A only =

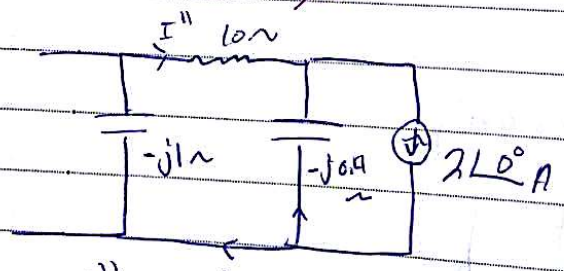

$$I'' = 2 \left(\frac{-j0.4}{10 - j0.4 - j1} \right)$$

$$= 79.23 \angle -83.03^\circ \text{ mA}$$

to find Power →

$$i'(t) = 811.7 \cos(3t - 76.86^\circ) \text{ mA}$$

$$i''(t) = 79.23 \cos(5t - 82.03^\circ) \text{ mA}$$

$$i(t) = i'(t) + i''(t)$$

$$P = 10 i^2(t)$$

* Phasor diagram

Better view for leading and lagging for all values (responses in the circuit)


$$\vec{V}_1 = 6 + j8 = 10 \angle 53.1^\circ \text{ volt}$$

$$\vec{V}_2 = 3 - j4 = 5 \angle -53.1^\circ \text{ V}$$


$$\vec{Y} = 1 + j1 \text{ S} = \sqrt{2} \angle 45^\circ \text{ } \rightarrow \text{capacitance}$$

$$\vec{I}_1 = \vec{V}_1 \vec{Y} = (6 + j8)(1 + j1) = 10\sqrt{2} \angle 98.1^\circ \text{ A}$$

$\omega t \rightarrow +ve$ CCW

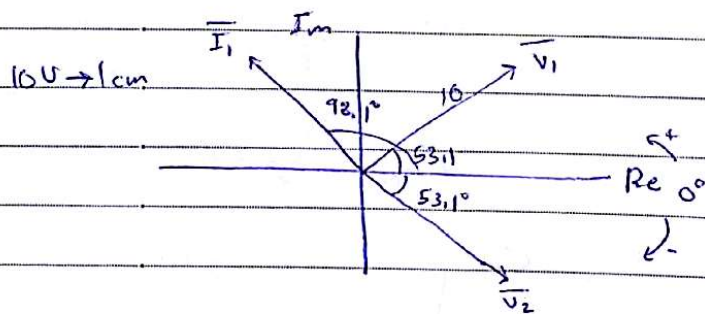

* Example for a simple RLC

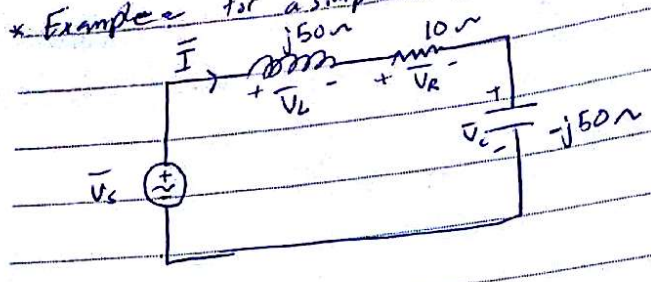

reference values:-

→ series → \bar{I} is the ref
 ↳ parallel → \bar{V} is the ref

Assume as

wt → +ve
ccw

$\bar{I} = 1 \angle 0^\circ \text{ A as ref}$

$\bar{V}_R = I R = 10 \angle 0^\circ \text{ V}$




$\bar{V}_L = j\omega L I = j50(1)$
 $= 50 \angle 90^\circ \text{ V}$


$\bar{V}_C = \frac{1}{j\omega C} I$

$= -j50 I$

$= -j50 \text{ V}$

$= 50 \angle -90^\circ \text{ V}$

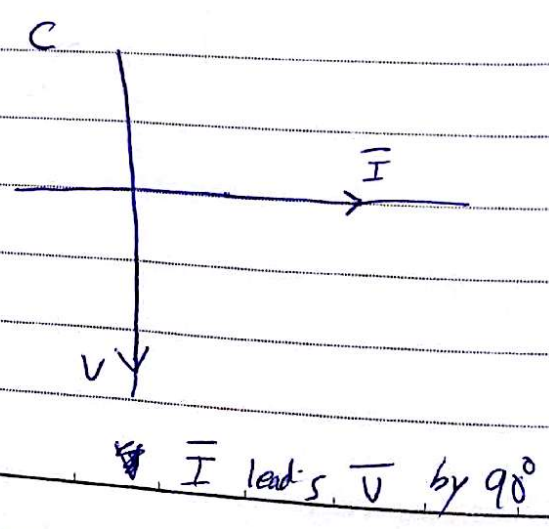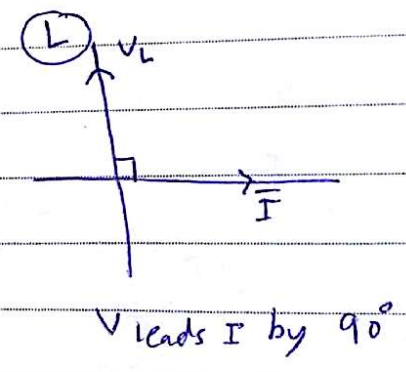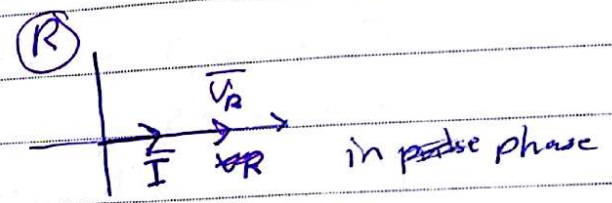

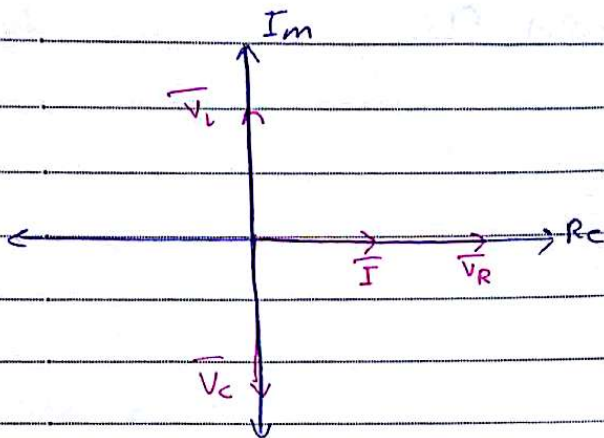

KVL e

$$\begin{aligned} \bar{V}_s &= \bar{V}_L + \bar{V}_R + \bar{V}_C \\ &= j50 + 10 - j50 \\ &= 10 \text{ volt} \end{aligned}$$

→ $j\omega L$ cancel with $\frac{1}{j\omega C}$
 circuit is at resonance (series Resonance) $\Rightarrow \bar{Z} \Big|_{\text{at resonance}} = R$

$$j\omega L = -\frac{1}{j\omega C}$$


$$\bar{Z} = \cancel{j\omega L} + R - \cancel{\frac{1}{j\omega C}}$$

$$-\omega^2 LC = -1$$


$$\boxed{\omega_0 = \frac{1}{\sqrt{LC}}}$$

* Single Node-par ckt parallel RLC

$$V \rightarrow \text{ref} = 110^\circ$$

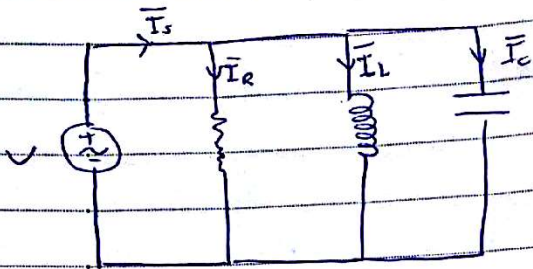

$$\bar{V} = 110^\circ$$

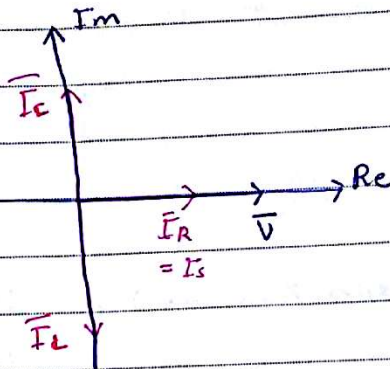

$$\text{at } \omega_0 = \frac{1}{\sqrt{LC}}$$

for parallel RLC take $I = 110^\circ$ as ref

→ Assume $V = 110^\circ$

$$\bar{I}_R$$

$$\bar{I}_C$$

$$\bar{I}_L$$


$$\bar{I} = \bar{I}_R + \bar{I}_C + \bar{I}_L$$

$$= 0.2 + j0.1 \neq 1$$

$$\bar{V} = \frac{110^\circ}{0.2 + j0.1} \leftarrow \text{Assume}$$

$$\bar{V} = \sqrt{20} \angle -26.1^\circ \text{ V}$$

Example

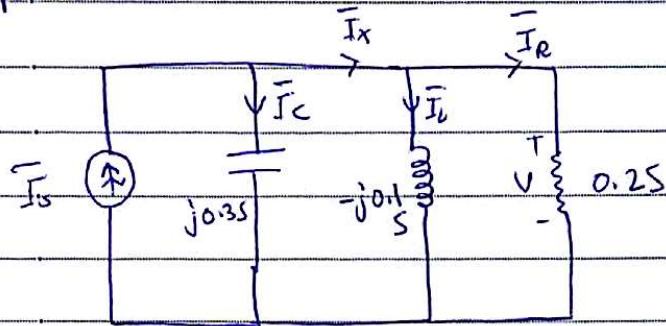

Determine how much \bar{I}_s leads \bar{I}_x , \bar{I}_R , \bar{I}_C , \bar{I}_L ?

Solution

Assume $\bar{V} = 1 \angle 0^\circ$

$$\bar{I}_R = 0.2 \angle 0^\circ$$

$$\bar{I}_L = -j0.1(1) = 0.1 \angle -90^\circ$$

$$\bar{I}_C = 0.3 \angle 90^\circ$$

$$\bar{I}_x = \bar{I}_L + \bar{I}_C = 0.224 \angle -26.6^\circ \text{ A}$$

$$\bar{I}_s = \bar{I}_x + \bar{I}_C = 0.282 \angle 45^\circ \text{ A}$$

