

8.5
زد

The University of Jordan
 Department of Electrical Engineering
 Circuit I, EE-211

Time: 60 Min.

Fall 2014
 First Exam

Date: Oct. 23, 2014

8-9:30 ج

Name (Arabic):

Student #:

Section #:

ج

Problem #1 (1 pt)


Find the absorbed power for each element of the following: $P = IV$, I^2R , $\frac{V^2}{R}$

- 1.
- $i=3 \text{ A}$
- and
- $v=8\text{V}$



$$\begin{aligned} P &= IV \\ &= 3 \times 8 \\ &= 24 \text{ W} \end{aligned}$$

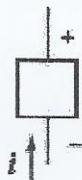- 2.
- $i=3 \text{ A}$
- and
- $v=-8\text{V}$



$$\begin{aligned} P &= IV \\ &= (-3)(-8) \\ &= 24 \text{ W} \end{aligned}$$

Problem #2 (1.5 pts)



Find R_{eq} of the following connection:

(3+6)

~~$$\frac{5}{5+7} = 2.91 \Omega$$~~

series

~~$$2.9 + 3 + 6 + 4 = 15.9 \Omega$$~~

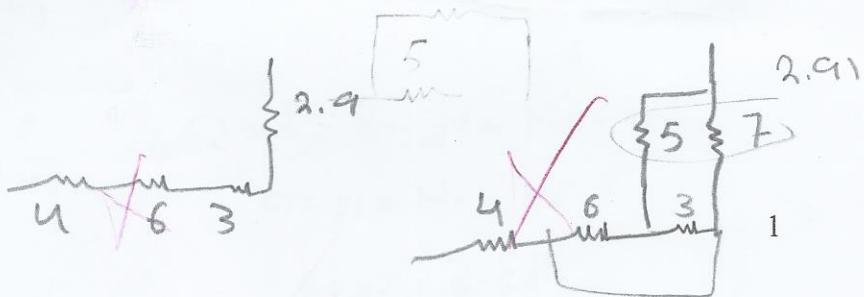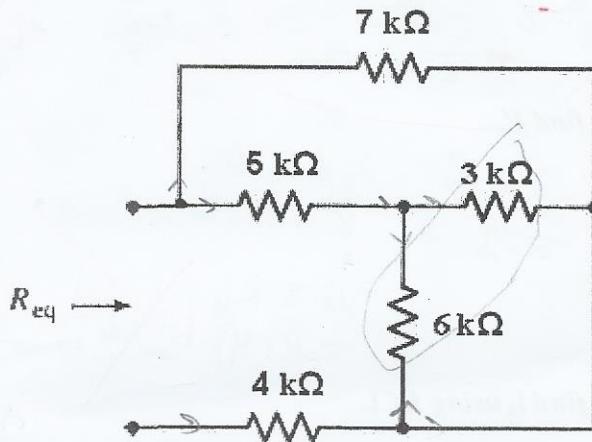

Problem #3 (4.5 pts)


Don't use MESH, NODAL or SUPERPOSITION to solve the following circuit:

$$\begin{aligned} V &= IR \\ \frac{U}{I} &= R \\ I &= 1A \end{aligned}$$

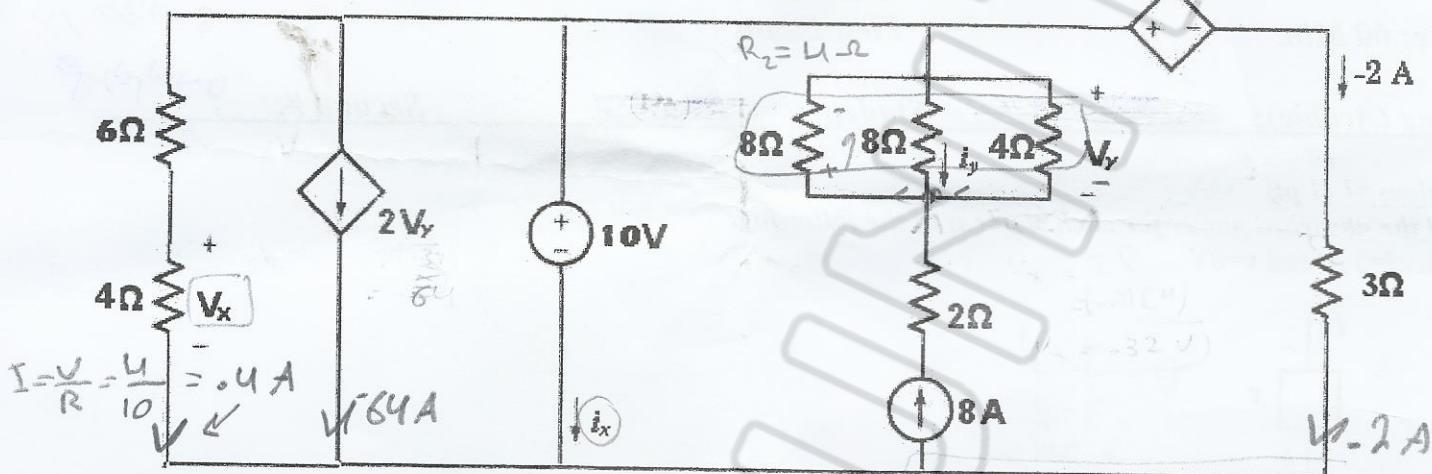1.5

$$V = IR$$

$$\begin{aligned} R &\propto T \\ R &\propto L \end{aligned}$$



1. find V_x by voltage division rule only.

$$V = V_T \frac{R}{R_1 + R_2 + \dots}$$

$$V = 10 \frac{4}{10} = 4V$$

2. find i_y by current division rule only.

$$\begin{aligned} i_y &= i_x \frac{\frac{1}{R_y}}{\frac{1}{R_x} + \frac{1}{R_y} + \frac{1}{R_z}} \\ &= -8 \frac{\frac{1}{2}}{\frac{1}{8} + \frac{1}{8} + \frac{1}{2}} = -8 \times \frac{1}{2} = -0.25A \end{aligned}$$

3. find V_y

$$\begin{aligned} V_y &= I R \\ &= -2 \\ R_y &= \frac{V_y}{I} = \frac{-2}{-0.25} = 8\Omega \\ R_y &= R_8 \parallel R_{14} \\ \frac{1}{R_y} &= \frac{1}{R_8} + \frac{1}{R_{14}} \\ \frac{1}{8} &= \frac{1}{8} + \frac{1}{14} = 4\Omega \end{aligned}$$

some Voltage

$$V = I R_y = -8(4) = -32V$$

4. find i_x using KCL.

$$-4 - 64 + i_x - 8 - 2 = 0$$

$$-74 + -4 + i_x = 0$$

$$-73.6 + i_x = 0$$

$$i_x = 73.6A$$

$$\begin{array}{c} 6 \\ 8 \\ 2 \\ \hline 14 \end{array}$$

$$V = IR$$

Problem #4 (4 pts)

The Mesh Equations of the following Circuit are given by:

$$20I_1 - 40I_2 - 5I_3 = V_1$$

$$-15I_1 + 65I_2 - 25I_3 = -V_2$$

$$-5I_1 - 25I_2 + 35I_3 = 0$$

Find R_1 , R_2 , R_3 and R_4 .


~~$$I_1 = 0.3571$$

$$I_2 = -7.14$$

$$I_3 = 0$$~~

~~$$R_F =$$~~

~~$$V = R_1(I_1 - I_3)$$~~

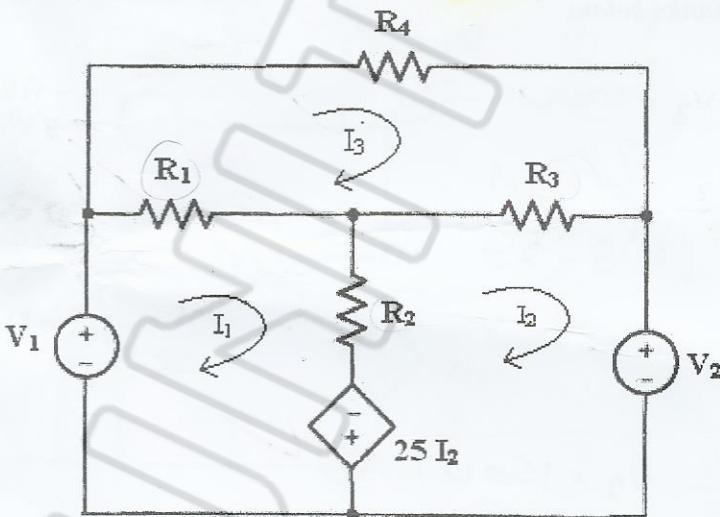

$$\textcircled{1} \rightarrow -V_1 + R_1(I_1 - I_3) + R_2(I_1 - I_2) - 25I_2 = 0$$

$$R_1(I_1 - I_3) + R_2(I_1 - I_2) - 25I_2 = V_1$$

$$R_1(0.3571) + R_2(-7.14 + 17.85) = V_1$$

$$\textcircled{3} \rightarrow R_1(I_2 - I_1) + R_3 I_3 + R_3(I_3 - I_2) = 0$$

$$\textcircled{2} \rightarrow 25I_2 + R_2(I_2 - I_1) + R_3(I_2 - I_1) + V_2 = 0$$

~~$$V_1 = 286.3142 \text{ V}$$~~

~~$$V_2 = 464.8 \text{ V}$$~~

~~$$R_F = R_1 = \frac{286.3142}{I_1 - I_3} = \frac{286.314}{0.3571} = 8017.8 \Omega$$~~

~~$$R_2 =$$~~

~~$$R_3 = \frac{V_2}{I_2 - I_3} = \frac{464.8}{-7.14} = 65.09 \Omega$$~~

~~$$R_4 =$$~~

(5)

Problem #5 (5 pts)

Write the NODAL voltage equations for the following circuit (Don't solve them; just arrange them to fill the blanks below.

$$V_1 - V_3 = 100 \text{ V} \quad \text{---} \textcircled{1} \quad \begin{matrix} V_1 \text{ & } V_3 \\ \text{same} \end{matrix}$$

$$\frac{V_1 - V_2}{12.5} - 5 + \frac{V_3}{20} + \frac{V_2 - V_4}{10} = 0 \quad \text{---} \textcircled{2}$$


V_2

$$\frac{V_2 - V_1}{12.5} \quad N_2 = 150 \text{ V} \quad \text{---} \textcircled{3}$$

V_4

$$\frac{V_4 - V_3}{10} + \frac{V_4}{25} + 10 = 0 \quad \text{---} \textcircled{4}$$

$$V_1 - V_3 = 100$$

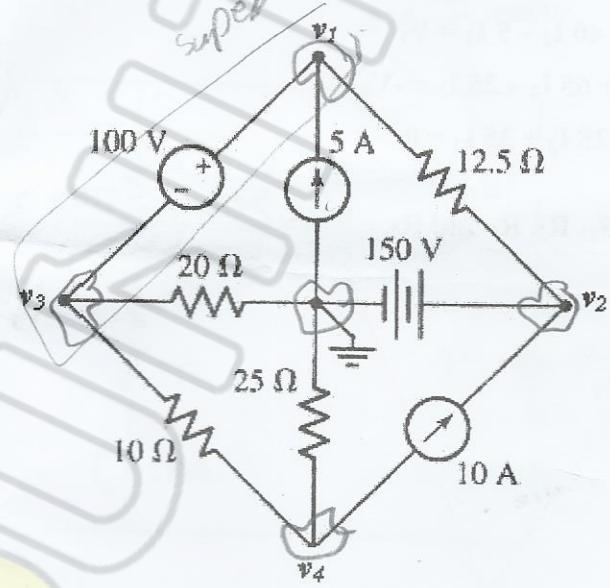

$$V_1 - V_3 = 100$$

$$\frac{V_1 - V_2}{12.5} + \frac{V_3}{20} + \frac{V_3 - V_4}{10} = 5$$

$$V_2 = 150$$

$$\frac{V_4 - V_3}{10} + \frac{V_4}{25} = -10$$

$$\frac{V_1}{12.5} - \frac{V_2}{12.5} + \frac{V_3}{20} + \frac{V_3}{10} - \frac{V_4}{10} = 5$$

$$94V_1 - 94V_2 + 915V_3 - 61V_4 = 5 \quad \text{---} \textcircled{1}$$

$$\frac{V_4}{10} - \frac{V_3}{10} + \frac{V_4}{25} = -10 \quad \text{---} \textcircled{2}$$

$$V_1 - V_2 = 100 \quad \text{---} \textcircled{3}$$

$$V_2 = 150 \quad \text{---} \textcircled{4}$$

$v_1 +$	$v_2 +$	$v_3 +$	$v_4 =$
---------	---------	---------	---------


$v_1 +$	$v_2 +$	$v_3 +$	$v_4 =$
---------	---------	---------	---------

$v_1 +$	$v_2 +$	$v_3 +$	$v_4 =$
---------	---------	---------	---------

$v_1 +$	$v_2 +$	$v_3 +$	$v_4 =$
---------	---------	---------	---------

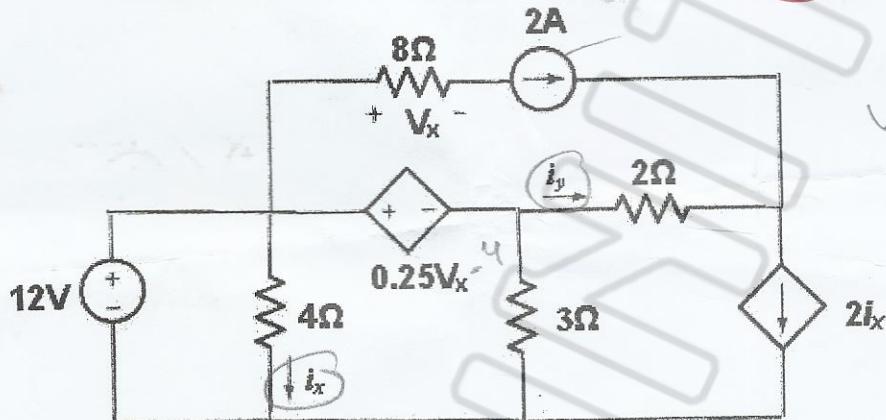
Problem #6 (4 pts)

Use Superposition Principle to find i_x and i_y in the following circuit.



$$\begin{aligned} V_x &= IR \\ &= 8(2) \\ &= 16V \end{aligned}$$

due to 2A

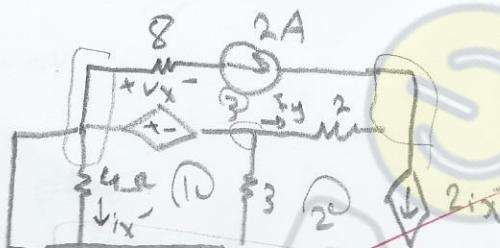


$$\begin{aligned} \text{mesh 1: } 4I_1 + 0.25(V_x) + 3(I_1 - I_2) &= 0 \\ 4I_1 + 3I_1 - 3I_2 &= -4 \\ 7I_1 - 3I_2 &= -4 \end{aligned}$$

$$\text{mesh 2: } 3(I_2 - I_1) + 2(I_2 - I_3) = 0$$

$$I_2 = 2I_1$$

due to 12V [$V_x = 0$]

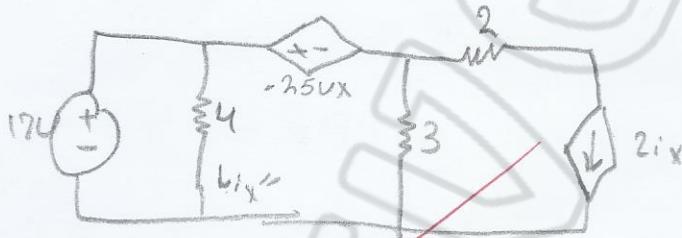

$$\begin{array}{r} \cancel{+} \\ \cancel{-} \end{array} \quad \begin{array}{r} \cancel{-} \\ \cancel{+} \end{array}$$

$$I_3 = 2A$$

V_1, V_2 sup

$$V_1 - V_2 = .2V_x$$

$$-\frac{V_1 - V_3}{8} + 2 + \frac{V_2 - V_3}{2} + \frac{V_3}{3} + \frac{V_1}{4} = 0$$

$$-\frac{V_3 - V_2}{2} - 2i_x - 2 + \frac{V_3 - V_1}{8} = 0$$

$$\begin{aligned} V_1 &= \\ V_2 &= \\ V_3 &= 0 \end{aligned}$$

$$i_x = \frac{V_1}{4}$$