

CKT II


* Average Power across a resistor :-

$$P_{avg} = \frac{1}{2} * V_m * I_m$$

Ex.

Find the average power delivered to the impedance
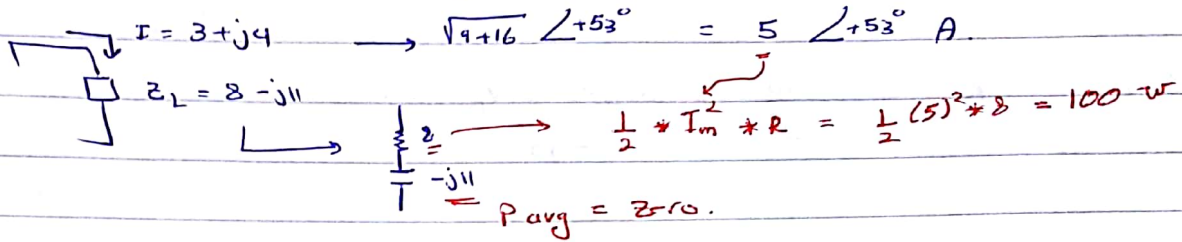
$$Z_L = 8 - j11 \quad \text{if} \quad I = 3 + j4$$



→ To Find power according to voltage.

$$\rightarrow V_R = 8 * (3 + j4) = 24 + j32 \rightarrow V_{Rm} = \sqrt{(24)^2 + (32)^2}$$

$$P_{avg} = \frac{1}{2} V_{Rm}^2 * \frac{1}{R}$$

X wrong.

$$\rightarrow V = (3 + j4)(8 - j11) = 68 - j \text{ volt}$$

$$V_m = \sqrt{(68)^2 + (-1)^2} = 68.001 \angle -84^\circ$$

$$P_{avg} = \frac{1}{2} (68.001)^2 * \frac{1}{8} \quad \checkmark \text{ right.}$$

* Instantaneous :-

$$p(t) = v(t) \cdot i(t)$$


$$i(t) = 5 \cos(\omega t + 53^\circ)$$

$$v(t) = 68.001 \cos(\omega t - 84^\circ)$$

inst. power absorbed
by Z_L .

Ex.

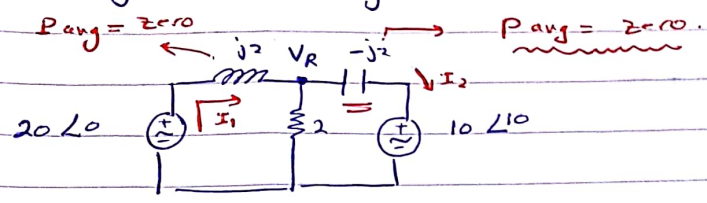Find the average power absorbed by elements and generated by sources.



* Nodal analysis. "जोड़ो, बिटो" (Join, Cut)

$$\frac{20\angle 0 - V_R}{j2} + \frac{-V_R}{2} + \frac{10\angle 10 - V_R}{-j2} = 0$$

$$V_R = -j10 = 10\angle -90^\circ$$

$$I_1 = \frac{20\angle 0 - V_R}{j2} = 11.8\angle -63.43^\circ$$

$$I_2 = \frac{10\angle -90^\circ - 10\angle 0}{-j2} = 7.071\angle -45^\circ$$


$$P_{avg} \text{ (by } R) = \frac{1}{2} V_m^2 * \frac{1}{R} = \frac{1}{2} (10)^2 * \frac{1}{2} = 25 \text{ W} \rightarrow \text{absorbed.}$$

$$P_{avg} \text{ (by } 20 \text{ volt source)} = \frac{1}{2} V_m I_m \cos(\theta - \phi) = \frac{1}{2} * 20 * 11.8 \cos(0 + 63.43) = 50 \text{ W} \rightarrow \text{generated}$$

$$P_{avg} \text{ (by } 10 \text{ volt source)} = \frac{1}{2} * V_m * I_m * \cos(\theta_V - \phi_I) = \frac{1}{2} * 10 * 7.071 \cos(0 + 45^\circ) = 25 \text{ W} \rightarrow \text{absorbed.}$$

Maximum power transference :-

$Z_{th} = R_{th} + jX_{th}$

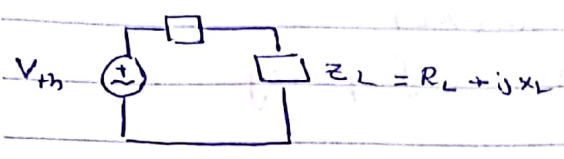

$I = \frac{V_m}{Z_L + Z_{th}}$

$V_L = \frac{V_{th} * Z_L}{Z_L + Z_{th}}$

$P_L = \frac{1}{2} V_m I_m \cos(\theta_v - \phi_I)$

$I_L = \frac{|V_{th}| \angle 0}{(R_L + R_{th}) + j(X_L + X_{th})}$

$= \frac{1}{2} |I_L| |V_L| \cos(\theta_v - \phi_I)$

$V_L = \frac{(R_L + jX_L) * |V_{th}| \angle 0}{(R_L + R_{th}) + j(X_L + X_{th})}$

~~$\Rightarrow \frac{1}{2} * \dots$~~

$= \frac{1}{2} |V_{th}| * \frac{1}{\sqrt{(R_L + R_{th})^2 + (X_L + X_{th})^2}} * \cos\left(\left[\tan^{-1}\left(\frac{X_L}{R_L}\right) - \tan^{-1}\left(\frac{X_L + X_{th}}{R_L + R_{th}}\right) + \tan^{-1}\left(\frac{X_L + X_{th}}{R_L + R_{th}}\right)\right]\right)$

" maximum power transference \equiv reduce absorbed power by Z_{th} "

$\frac{dP_L}{dR_L} = 0 ; R_L = R_{th}$


* To achieve maximum power transference (minimize losses)

$\frac{dP_L}{dX_L} = 0 ; X_L = -X_{th}$

$Z_L = Z_{th}^*$

Ex.

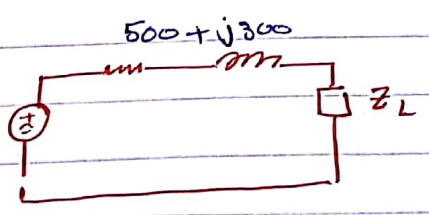
Find the load value that maximize the power transference



$Z_L = Z_{th}^* = 500 - j300$

Ex.

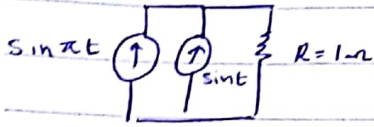Find the average power across $R = 1 \Omega$ if $i(t) = \sin t + \sin(\pi t)$
 Different frequency.



$P_{avg} = \frac{1}{2} I_m^2 R$ X

$$P_{avg} = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{T} \int_0^T i^2(t) \cdot R dt$$

$$= \frac{1}{T} \int_0^T (\sin t + \sin \pi t)^2 dt = \frac{1}{T} \int_0^T \sin^2 t + 2 \sin t \sin \pi t + (\sin \pi t)^2 dt$$

$$= \frac{1}{T} \int_0^T \sin^2 t dt + \frac{1}{T} \int_0^T 2 \sin t \sin \pi t dt + \frac{1}{T} \int_0^T \sin^2(\pi t) dt$$

$\int_0^T \sin^2 t dt = \frac{1}{2} - \frac{1}{2} \cos 2t$
 $\int_0^T 2 \sin t \sin \pi t dt = \frac{1}{2} \cos(\pi t - t) - \frac{1}{2} \cos(\pi t + t)$
 $\int_0^T \sin^2(\pi t) dt = \frac{1}{2} - \frac{1}{2} \cos 2\pi t$

$= \frac{1}{T} + 1 + 1 = 1 W$

* integral over complete periods of sinusoidal = zero

$P(\text{source 1}) = \frac{1}{2} I_m^2 R = \frac{1}{2}$

$P(\text{source 2}) = \frac{1}{2} I_m^2 R = \frac{1}{2}$

$P_{avg} = P_{s1} + P_{s2} = \frac{1}{2} + \frac{1}{2} = 1 W$

Power of each source (superposition) will average into instantaneous.

IF we have sources with multiple frequency

$P_{avg} = \frac{1}{2} R [I_{m1}^2 + I_{m2}^2 + I_{m3}^2 + \dots]$

Ex. \rightarrow Peak value (3 not -3)

$$i(t) = 2 \cos(10t) - 3 \cos(20t), R = 4 \Omega$$

Find P avg.

$$P_{avg} = \frac{1}{2} R [I_{m1}^2 + I_{m2}^2] = \frac{1}{2} * 4 * [(2)^2 + (3)^2]$$

$$= 2 * 13 = 26$$

Ex. $i(t) = 2 \cos 10t - 3 \sin(10 - 90^\circ), R = 4 \Omega$

sin ال داس لا *
Peak value

$$P_{avg} = \frac{1}{2} (2)^2 * 4 + \frac{1}{2} (3)^2 * 4$$

Ex.

$$i(t) = 2 \cos(10t) - 3 \cos(10t), R = 4 \Omega$$

same frequency

$$i(t) = 2 \cos(10t) - 3 \cos(10t) = -\cos(10t)$$

$$P_{avg} = \frac{1}{2} (1)^2 * 4 = 2 \text{ W}$$

Ex.

$$i(t) = 5 \cos(\omega t) + 3 \sin(\omega t), R = 4 \Omega$$

$$i_1(t) = 5 \cos(\omega t) = 5 \angle 0$$

$$i_2(t) = 3 \sin(\omega t) = 3 \cos(\omega t - \frac{\pi}{2}) = 3 \angle -90^\circ$$

$$i_1 + i_2 = 5 \angle 0 + 3 \angle -90 = 5 - j3$$

Peak value (Im) = $\sqrt{25 + 9} = \sqrt{34}$

$$P_{avg} = \frac{1}{2} (I_m)^2 * R = \frac{1}{2} (\sqrt{34})^2 * 4 \text{ W}$$

Ex.

$$v(t) = 5 \cos(\omega t) + 3 \cos(\omega t - \frac{\pi}{4})$$

$$V = 5 \angle 0 + 3 \angle -45^\circ$$


$$= 5 + 3 * \frac{1}{\sqrt{2}} - j 3 * \frac{1}{\sqrt{2}}$$

$$= (5 + \frac{3}{\sqrt{2}}) - j \frac{3}{\sqrt{2}}$$


$$|V| = \sqrt{(\frac{5+3}{\sqrt{2}})^2 + (\frac{3}{\sqrt{2}})^2}$$

$$P_{avg} = \frac{1}{2} V_m^2 * \frac{1}{R} = \frac{1}{2} \frac{|V|^2}{R}$$


" Effective values "

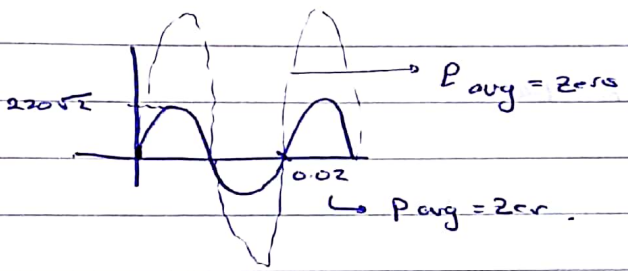


P_{avg} ??? No X

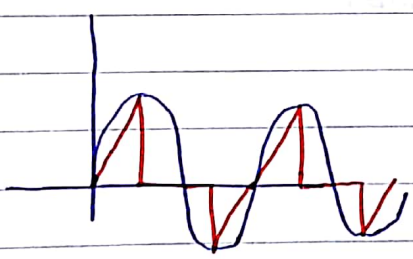

Peak value ??? No X

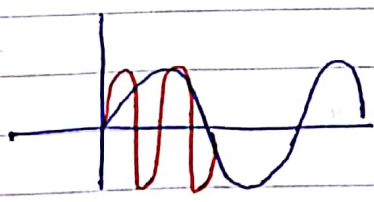

frequency ??? No X

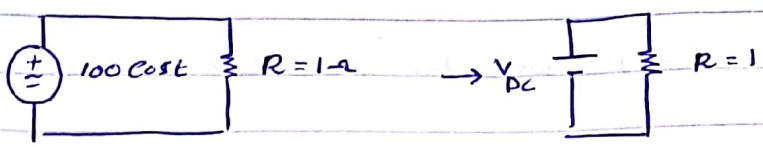

$$P_{ac} = \frac{1}{2} (100)^2 \cdot \frac{1}{1} = 5000 \text{ W}$$

$V_{DC} ??$

$$P_{DC} = \frac{V^2}{R} \rightarrow 5000 = V^2$$

$$V_{DC} = \sqrt{5000} = \frac{100}{\sqrt{2}} \text{ volt.}$$

Effective values:

The value of an AC signal that is equivalent in generated power to a DC source that gives the same power.


$$P_{DC} = P_{AC}; \text{ consider } R=1 \Omega$$

$$V_{DC}^2 = \frac{1}{T} \int_0^T P(t) \cdot dt$$

$$V_{DC}^2 = \frac{1}{T} \int_0^T v^2(t) dt$$

$$V_{DC} = V_{eff} = V_{RMS} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

Root mean square value.

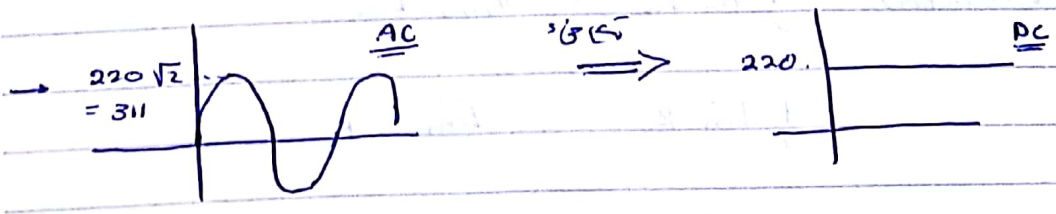

Ex.

Find the effective (RMS) value for the current waveform:

$$i(t) = I_m \cos(\omega t + \Phi) \quad ; \quad P_{avg} = \frac{1}{2} I_m^2 R$$

$$I_{eff} = I_{RMS} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} \quad ; \quad T = \frac{2\pi}{\omega}$$

$$= \sqrt{\frac{1}{T} \int_0^T I_m^2 \cos^2(\omega t + \Phi) dt} = \sqrt{\frac{I_m^2}{T} \int_0^T \left[\frac{1}{2} + \frac{1}{2} \cos(2\omega t + 2\Phi) \right] dt}$$

~~$= 2\pi$~~

$$= \sqrt{\frac{I_m^2}{2T} * T} = \frac{I_m}{\sqrt{2}}$$

For sinusoidal (V or I)

$$\rightarrow V_{RMS} = \frac{V_{peak}}{\sqrt{2}} = \frac{V_m}{\sqrt{2}}$$

$$\rightarrow P_{avg} = \frac{1}{2} V_m I_m \cos(\theta - \Phi)$$

$\swarrow \sqrt{2} V_{RMS} \quad \searrow \sqrt{2} I_{RMS}$

$$P_{avg} = V_{rms} I_{rms} \cos(\theta - \Phi)$$


$$\rightarrow P_{avg} (\text{resistor}) = \frac{1}{2} V_m I_m = V_{rms} I_{rms}$$

$$= \frac{1}{2} I_m^2 R = I_{rms}^2 \cdot R$$

$$= \frac{1}{2} \frac{V_m^2}{R} = \frac{V_{rms}^2}{R}$$

Ex.

Find the RMS value for the signal shown:

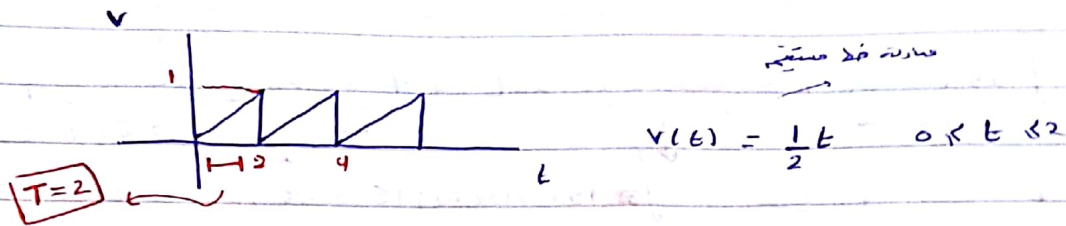

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} = \sqrt{\frac{1}{2} \int_0^2 \left(\frac{1}{2}t\right)^2 dt} = \frac{1}{\sqrt{3}} \text{ volt.}$$

$$P_{avg} = \frac{V_{rms}^2}{R} = \frac{\left(\frac{1}{\sqrt{3}}\right)^2}{4} = 1/12 \text{ W}$$

Ex.

Find the RMS value for : $v(t) = 5 \cos \omega t$

$$V_{rms} = \frac{5}{\sqrt{2}}$$

~~graph of a sine wave~~

Ex.

$$i(t) = 5 \cos(\omega t + \frac{\pi}{4})$$

$$I_{rms} = \frac{5}{\sqrt{2}}$$

Ex.

$$v(t) = 5 \sin(\omega t)$$

$$V_{rms} = \frac{5}{\sqrt{2}}$$

phase shift not effect.

Ex.

$$v(t) = 5 \cos \omega t + 3 \cos(2\omega t) \text{ [multiple frequency]}$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$$\rightarrow V_{rms} = \sqrt{\frac{1}{T} \int_0^T (5 \cos \omega t + 3 \cos(2\omega t))^2 dt}$$

$$= \sqrt{\frac{1}{T} \int_0^T 25 \cos^2 \omega t + 30 \cos \omega t \cos 2\omega t + 9 \cos^2 2\omega t dt}$$

$\xrightarrow{\text{Zero}}$ $\int_0^T 15 \cos(3\omega t) + 15 \cos \omega t dt = \text{Zero}$

$\xrightarrow{\text{Zero}}$ $\frac{25}{2} + 25 \cos 2\omega t$

$\xrightarrow{\text{Zero}}$ $\frac{9}{2} + \frac{9}{2} \cos(4\omega t)$

$$= \sqrt{\frac{1}{T} \int_0^T \frac{34}{2} dt} = \sqrt{\frac{34}{2}} = \sqrt{17} = \sqrt{(V_{rms1})^2 + (V_{rms2})^2}$$


#

NOTE :-

$$V_{rms} = \sqrt{V_{rms1}^2 + V_{rms2}^2 + V_{rms3}^2 + \dots}$$

Ex.

Find the RMS value.

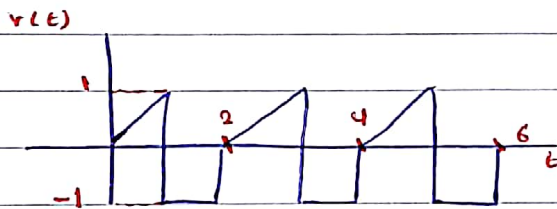

$$T=4$$

$$v(t) = \begin{cases} \frac{1}{2}t, & 0 \leq t < 2 \\ -1, & 2 \leq t < 4 \end{cases}$$

$$V_{rms} = \sqrt{\frac{1}{4} \int_0^4 v^2(t) dt}$$

Since the period is 4.

$$= \sqrt{\frac{1}{4} \left[\int_0^2 \left(\frac{t}{2}\right)^2 dt + \int_2^4 (-1)^2 dt \right]}$$

$$V_{rms} = 0.816 \text{ Volt.}$$

Ex. Find the RMS value

frequency zero

$$V(t) = 5 + 3 \cos \omega t$$

$$V_{rms} = \sqrt{(5)^2 + \left(\frac{3}{\sqrt{2}}\right)^2}$$

ans L DC 11
√2 etc

Ex. H.W

if $v(t) = 5 \cos \omega t$ & $i(t) = 3 \sin(\omega t + 60^\circ)$

for an element find its P avg.

Ex.

Find the average power across a 4-Ω resistor

when ~~$v(t) = 8 \sin 200t - 8 \cos(200t - 90^\circ)$~~

when $v(t) = 8 \sin 200t - 6 \cos(200t - 45^\circ)$
 $8 \cos(200t - 90^\circ)$


$$v(t) = 8 \angle -90^\circ - 6 \angle -45^\circ = -j8 - \left[\frac{6}{\sqrt{2}} - \frac{j6}{\sqrt{2}} \right]$$

$$= -j8 - \frac{6}{\sqrt{2}} + j \frac{6}{\sqrt{2}} = \frac{-6}{\sqrt{2}} - j \left(8 - \frac{6}{\sqrt{2}} \right)$$

$$\text{Peak value} = \sqrt{\left(\frac{-6}{\sqrt{2}}\right)^2 + \left(8 - \frac{6}{\sqrt{2}}\right)^2}$$

$$V_{rms} = \frac{\sqrt{\left(\frac{-6}{\sqrt{2}}\right)^2 + \left(8 - \frac{6}{\sqrt{2}}\right)^2}}{\sqrt{2}}$$
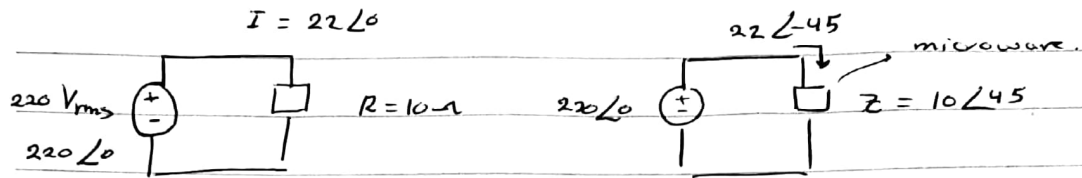
$$; P_{avg} = \frac{V_{rms}^2}{R} \quad \text{OR} \quad \frac{1}{2} \frac{V_m^2}{R}$$




$$2000 \text{ W} \xrightarrow{1 \text{ h}} 2000 \text{ Wh} = 2 \text{ kWh}$$

$$P_1 = V_{rms} I_{rms}$$

$$= 220 * 22 = 4840$$

$$P_2 = V_{rms} I_{rms} \cos(\theta - \phi)$$
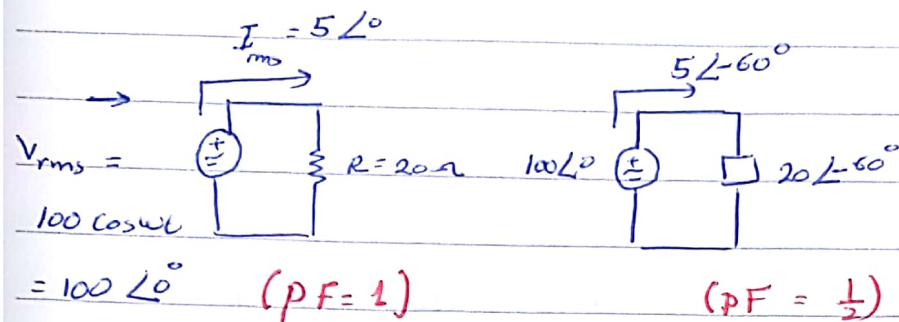
$$= 220 * 22 * \cos 45 = \frac{4840}{\sqrt{2}}$$



$$P = V_{rms} I_{rms}$$


$$= 100 * 5 = \underline{500 \text{ W}}$$

$$P = V_{rms} I_{rms}$$

$$= 100 * 5 * \cos(0 + 60)$$

$$= \underline{250 \text{ W}}$$

"Same current with different power"

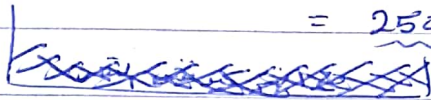

$$\# \text{ power factor (PF)} = \frac{\text{Real power}}{\text{Apparent power}} = \frac{V_{rms} I_{rms} \cos(\theta - \phi)}{V_{rms} I_{rms}}$$

$$\text{PF} = \cos(\theta - \phi)$$

* In general for sinusoidal signals
 $\text{PF} = \cos(\theta - \phi)$

→ for pure resistive load,
 $\text{PF} = \cos(\theta - \phi) = 1$

→ for pure inductive / capacitive loads


$$PF = \cos(\theta - \bar{\Phi}) = \underline{\underline{Zero}}$$

→ for other loads in general (impedance)

$$PF = \cos(\theta - \bar{\Phi})$$

$$0 \leq PF \leq 1 \quad \rightarrow \quad 0 \leq \theta - \bar{\Phi} \leq \pi/2$$

Ex.

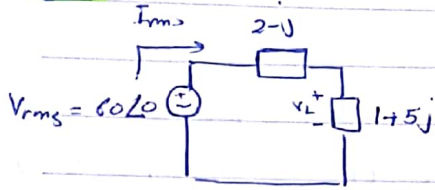


* Find source PF.

$$PF = \cos(\theta - \bar{\Phi}) \quad \rightarrow \quad PF = \cos(0 + 53.13^\circ)$$

$$I_{rms} = \frac{V_{rms}}{Z_L} = \frac{60 \angle 0}{(2-j) + (1+j5)} = \frac{60 \angle 0}{3+j4} = 12 \angle -53.13^\circ$$

"voltage leads current"

inductive. ← load الـ ١١

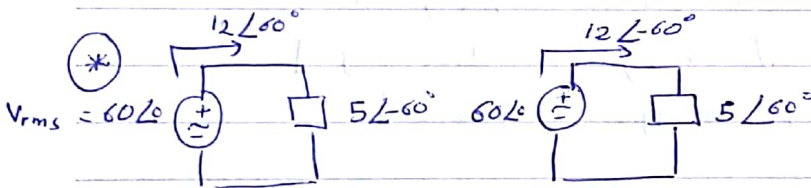

$$PF = \cos(0 + 60^\circ)$$

$$= \underline{0.5}$$



0.5 leading

↳ "current lead voltage"

$$PF = \cos(0 + 60^\circ)$$

$$= \underline{0.5}$$



0.5 lagging "voltage leads current"

→ Continue of previous example :-

$$P_{avg} = V_{rms} I_{rms} \cos(\theta - \bar{\Phi})$$

$$= 60 * 12 * \cos(0 + 53.13^\circ) = 432 \text{ W}$$

$$\text{Apparent power} = V_{rms} I_{rms} = 720 \text{ W}$$

$$PF = \frac{P_{avg}}{App.} = 0.6 \text{ lagging}$$

real power
Apparent

→ Find load power factor. [PF for source \neq PF of load]

$$V_{rms}(\text{load}) \Rightarrow \text{voltage division} = \frac{60 \angle 0^\circ * (1+j5)}{(3+j4)} = 61.18 \angle 25.5^\circ$$

$$I_{rms}(\text{load}) \Rightarrow 12 \angle -53.13^\circ$$

$$PF = \cos(\theta - \phi) = \cos(25.5^\circ + 53.13^\circ) = 0.19 \text{ lagging.}$$

Complex power: is defined to represent the power consumption in resistors & (inductors/capacitors)

Complex power \rightarrow Real power [Heat]
 \rightarrow reactive power [electromagnetic fields]

$\$$ \rightarrow P (power in resistor)
 \rightarrow Q (power in inductor/capacitor)
 [reat of charge & discharge]
 [reat of energy trasphere]

→ Suppose.

$$V = \frac{|V_{rms}| \angle \theta}{\angle |V_{rms}| e^{j\theta}} \quad \& \quad I = \frac{|I_{rms}| \angle \phi}{\angle |I_{rms}| e^{j\phi}}$$

$$P = |V_{rms}| |I_{rms}| \cos(\theta - \phi)$$

→ we know :-

$$e^{j(\theta - \phi)} = \underbrace{\cos(\theta - \phi)}_{\text{Re} \{ e^{j(\theta - \phi)} \}} + j \underbrace{\sin(\theta - \phi)}_{\text{Im} \{ e^{j(\theta - \phi)} \}}$$

$$P = |V_{rms}| |I_{rms}| * \text{Re} \{ e^{j(\theta - \phi)} \}$$


$$= \text{Re} \left\{ \underbrace{|V_{rms}| e^{j\theta}}_V * \underbrace{|I_{rms}| e^{-j\phi}}_{I^*} \right\} = \text{Re} \{ V I^* \}$$

→ conjugat.

$$P = \text{Re} \{ S \} ; S = V I^*$$

Ex.

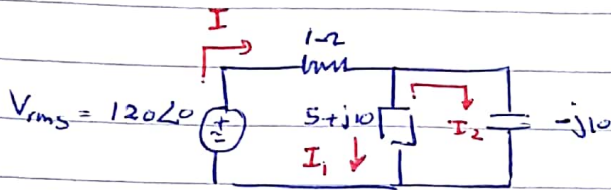Find the Complex power absorbed/produced by every element in the circuit.



$$I_{rms} = \frac{120 \angle 0}{1 + (5+j10 \parallel -j10)} = \frac{120}{1 + \frac{(5+j10)(-j10)}{5}} = 5.16 \angle 25.46^\circ \text{ A}$$

$$S(\text{source}) = V_{rms} I_{rms}^* = 120 \angle 0 \times 5.16 \angle -25.46^\circ = 552.98 - j266.14 \text{ VA}$$

$$P = 552.98 \text{ W}$$

$$Q = -266.14 \text{ VAR}$$

$$S(1\Omega) = V_{rms} I_{rms}^*$$

$$\rightarrow V_{rms}(1\Omega) = 1 + 5.16 \times \angle 25.46 \text{ volt.}$$

$$\rightarrow S = 5.16 \angle 25.46^\circ \times 5.16 \angle -25.46^\circ = 26.6 + 0j \text{ VA}$$

P (pure real power) Q (No reactive power in Resistor)

$$P(1\Omega) = \frac{V_{rms}^2}{R}$$

OR

$$I_{rms}^2 \times R$$

$$= \underline{26.6} \text{ W}$$

$$* I_2 = \frac{I \times (5+j10)}{5} = 11.53 \angle 88.89$$

$$V(-j10) = I \times X_c = -j10 \times 11.53 \angle 88.89 = 115.3 \angle -1.11^\circ$$

$$S(-j10) = V_{rms} \times I_{rms}^* = 115.3 \angle -1.11 \times 11.53 \angle -88.89$$

$$= 1331 \angle -90$$

$$= 0 - j1331 \text{ VA}$$

the capacitor work as a generator of reactive power (يولد باوان سُمِّية في العنصر)

$$\rightarrow Q = V_{rms} I_{rms} \sin(\theta - \phi)$$

$$= 115.3 * 11.53 \sin(-1.11 - 28.89)$$

$$= -1331 \text{ VAR}$$

-ve \rightarrow generated. Source
 +ve \rightarrow absorbed. load

$$\rightarrow I_1 = I - I_2$$

$$I_1 = 10.31 \angle -64.53$$

-ve \rightarrow absorbed. load
 +ve \rightarrow generated. Source

$$S(5+j10) = 115.3 \angle -1.11 * 10.31 \angle 64.53$$

$$= 531.48 + j1062$$

Real power \leftarrow

$$S(\text{source}) = V_{rms} I_{rms}^* = 120 \angle 0 * 5.16 \angle -25.46^\circ$$

$$= 558.98 - j266.14$$

* E.x.


given

$$V_L = 60 \cos(\omega t - 10) \text{ volt.}$$

$$i_L = 1.5 \cos(\omega t + 50) \text{ A.}$$

Capacitive load (current leads voltage)

peak values (because of time domain)

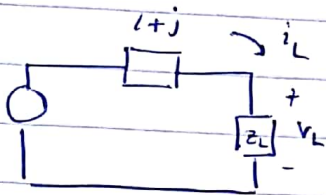

III find load complex power

$$S = V_{rms} * I_{rms}^*$$

$$\text{OR } \frac{1}{2} V_m I_m$$

$$\frac{60}{\sqrt{2}} \angle -10 * \frac{1.5}{\sqrt{2}} \angle -50$$

$$= \frac{1}{2} * 60 \angle -10 * 1.5 \angle -50$$

$$S_L = 45 \angle 60^\circ = 22.5 - j38.97$$

جناك الجناك

Capacitive load.

load Apparent power =

$$|S_L| =$$

$$= |V_{rms}| |I_{rms}| = \frac{60}{\sqrt{2}} * \frac{1.5}{\sqrt{2}} = 45 \text{ VA.}$$

→ load PF = $\cos(\theta - \phi)$

$$= \cos(-10 - 50)$$

$$= 0.5 \text{ leading.}$$

$$Z_L = \frac{60 \angle -10}{1.5 \angle 50} = 40 \angle -60$$

→ to find PF & source complex power


$$V_S = 60 \angle -10 + (1+j) * 1.5 \angle 50$$

$$V_{rms} = \frac{60}{\sqrt{2}} \angle -10 + (1+j) * \frac{1.5}{\sqrt{2}} \angle 50 = 42 \angle -8^\circ$$

$$\text{PF (source)} = \cos(\theta - \phi) = \cos(-8 - 50) = 0.53 \text{ leading.}$$


$$S(\text{Source}) = V_{rms} * I_{rms}^* = 42 \angle -8 * \frac{1.5}{\sqrt{2}} \angle -50$$

*** Power Factor Correction**

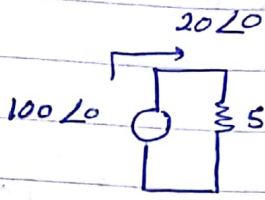

$P = 2000 \text{ W}$

$PF = \cos(\theta - \phi)$
 $= 1$

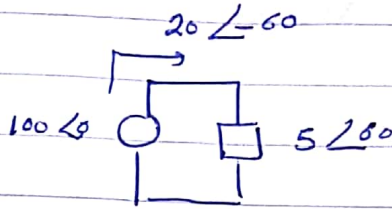


$P = 100 \times 20 + 10 \times \cos(60)$
 $= 1600 \text{ W}$

$PF = \cos(\theta - \phi) = \cos(60) = \frac{1}{2}$ lagging.

لذا نحتاج كابل قريب من ال 1

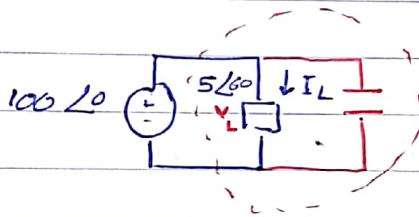PF Correction: increasing PF without altering the voltage & current of the actual load.



ال I_L و ال V_L في ال
 الحمل زي ما كان
 اضافة ال capacitor

*** Before adding the capacitor:-**




$I_S = I_L$

$\theta = \tan^{-1} \left(\frac{Q_L}{P_L} \right)$

$PF = \cos \theta$ → the angle difference between voltage & current
 ($\theta - \phi$, here)

*** After adding the capacitor:**

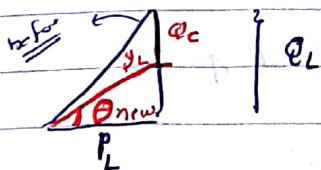

$I_S = I_L + I_C$

$\theta_{new} = \tan^{-1} \left(\frac{Q_L - Q_C}{P_L} \right)$

نقل θ
 ↓
 بزيادة $\cos \theta$
 ↓
 بزيادة PF