

11.5

Name: Salim Al-Hadi

ID# 015 63 27 Serial # 48

Questions 1 (5 points)


a) Find the RMS value for the following voltage waveforms:

1) $v_1(t) = 5\sin(\omega t) + 8\cos(\omega t)$ V

2) The signal shown in the figure $v_2(t)$.

b) Find the RMS value of a source V where $V = V_1 + V_2$.

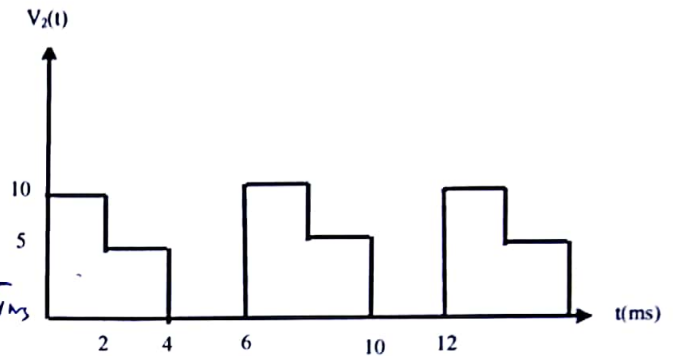c) Find the real power absorbed by a load $Z = 4 + j5 \Omega$ that is connected in parallel with a voltage source $V = V_1 + V_2$.



a) 1) $\sqrt{\frac{5^2}{2} + \frac{8^2}{2}} = 6.67 V_{rms}$

2)
$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt} = \sqrt{\frac{1}{6} \left(\int_0^2 10^2 dt + \int_2^6 5^2 dt \right)}$$

$$= \sqrt{\frac{1}{6} (100t \Big|_0^2 + 25t \Big|_2^6)} = \sqrt{\frac{1}{6} (200 + 50)} = 6.45 V_{rms}$$

b)
$$\sqrt{(6.67)^2 + (6.45)^2}$$

$$= \sqrt{6.67^2 + 6.45^2}$$

$$= 9.278$$

c) ~~Power absorbed by load Z~~

\Rightarrow

$P = V I = 21.52$

$V = I R$

$9.278 = I (4 + j5)$

$I = 2.319$


V_{1RMS}	V_{2RMS}	$V_{RMS(eff)}$	P
6.67 V	6.45 V	9.278 V	21.52 W



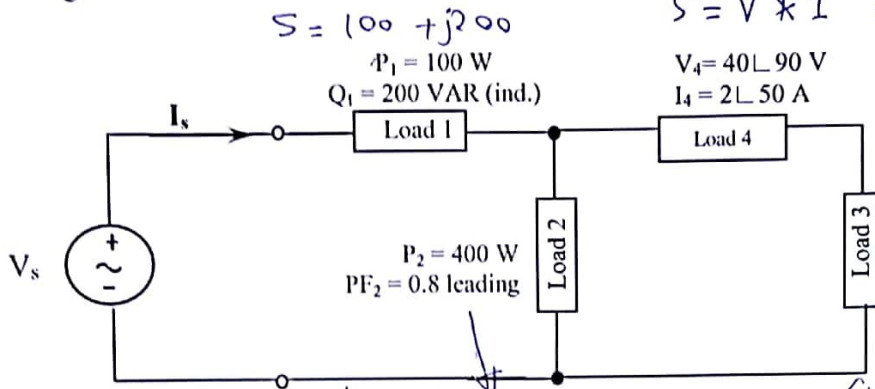Questions 2 (5 points)

The circuit shown below consists of four loads in a series-parallel connection, with each of the loads defined as indicated. Find:

- The overall complex power supplied by the source, S_s .
- The overall source power factor, PF_s .
- The source phasor current, I_s .
- The phase and magnitude of the current that flows in load 2.



a)

$$S_1 = 100 + j200$$


$$S_2 = 400 - j299.5$$

$$S_3 = 54.54 - j65$$

$$S_4 = 61.2 + j51$$

$$S_{total} = 615.74 - j113.5$$

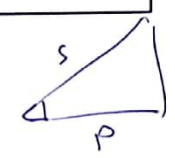
$\cos^{-1}(0.8) = 36.8^\circ$
 $\sin 36.8^\circ = \frac{3}{5}$



$|S| = \frac{P}{\cos \theta} = \frac{400}{0.8} = 500$
 $Q = |S| \sin 36.8^\circ = 299.5$

b) $PF = \frac{P}{|S|} = \frac{615.74}{626.11} = 0.983$

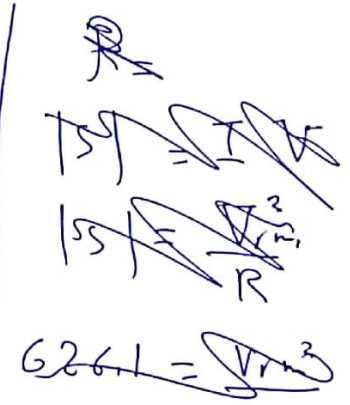c) ~~...~~ $S = \frac{I_s^2}{R} \cos \theta \Rightarrow$




S_s	PF_s	I_s	I_2
$615.74 - j113.5$	0.983		

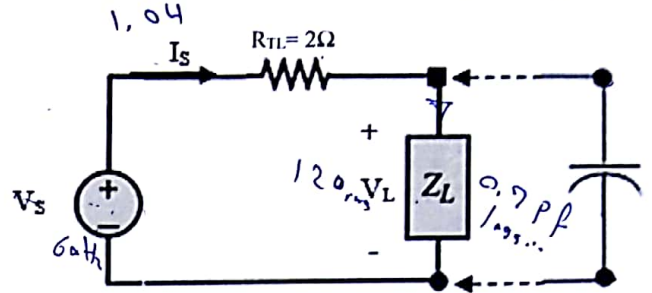Questions 3 (5 marks)

The circuit shown depicts a load with 0.8 lagging PF that absorbs 100 W, the load voltage V_L is 120 V and the source frequency is 60 Hz. It is required to correct the power factor of the load by adding a capacitor of $10\mu\text{F}$. Find:

- the PF of the source before connecting the capacitor.
- the new load PF after connecting the capacitor.
- the new source current after connecting the capacitor.
- the losses in the line before and after the connecting the capacitor.



3.5


$$V_L = Z_L I_S \quad P = I_L V_L \cos \phi$$

$$120 = Z_L I_S \quad 100 = I_L 120 \cdot 0.8$$

$$I_L = 1.04 \text{ A}$$

~~$$V_S = I_S (2 + 115.24)$$~~
~~$$1.04 \times (117.24)$$~~

$$V_S = I_S 2 + 120 = 122.08$$

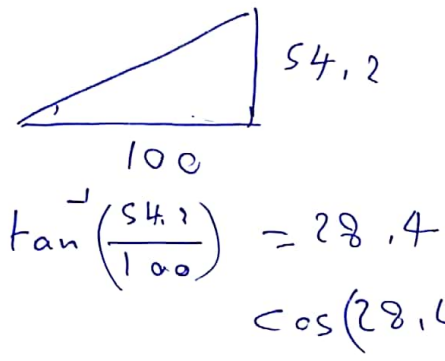

$$Q = I_S V_S \sin \phi = 9.279$$

$$54.2 = I_C 120 (0.47) = 0.94$$

$$\tan \phi = \frac{Q}{P} = \frac{54.2}{100} = 0.542$$

$$C = \frac{Q_C}{\omega V^2} = \frac{54.2}{2\pi \cdot 60 \cdot 120^2}$$


$$Q_C = 54.2$$

PF _{before(source)}	PF _{after(Load)}	I _{S(new)}	P _{losses(before)}	P _{losses(after)}
0.8	0.879	1.04 + 0.94	75 VAR	54.2 VAR

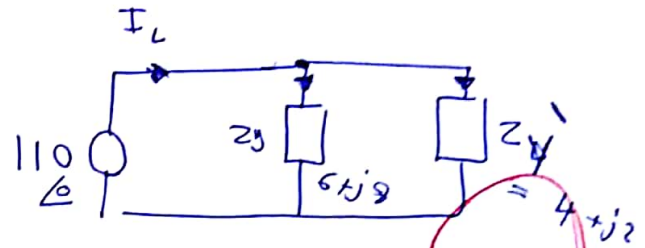Questions 4 (5 points)

The circuit drawn shows a balanced 3 phase Y source of 110 V phase to neutral voltage supplying a balanced Y connected load of $Z_Y = 6+j8$ connected in parallel with Delta load with $Z_\Delta = 12 +j6$. Find:

- the phase current in phase B of the Y load.
- the phase current in phase CA in the Delta load.
- the total current in line A supplied by the source.
- the total power supplied to the load.
- the combined load power factor.



3


$$Z_{eq} = \frac{Z_Y * Z_Y'}{Z_Y + Z_Y'}$$

$$= 2.6 + j1.8$$

$$I_a = \frac{110 \angle 0^\circ}{2.6 + j1.8}$$

$$= 34.7 \angle -34^\circ$$

$$I_b = 34.7 \angle -154^\circ$$

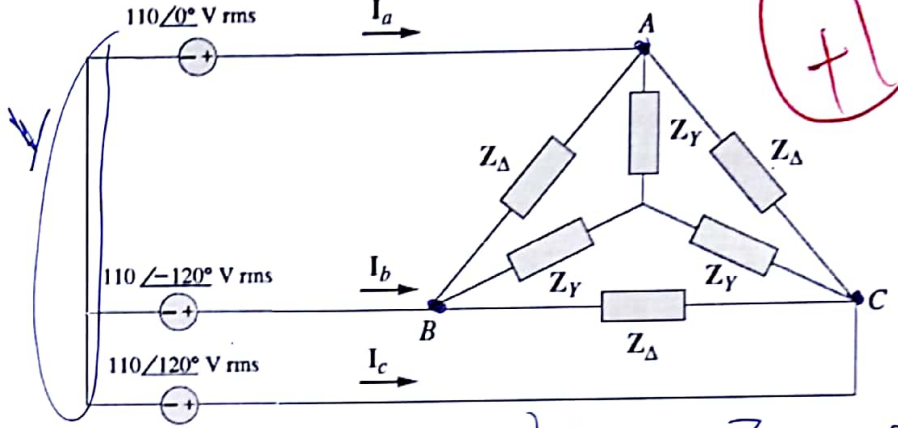

4 + j2

$$Z_Y = \frac{Z_\Delta}{3} = \frac{12 + j6}{3} = 4 + j2$$

$$\Rightarrow I_{B \text{ yload}} = \frac{34.4 \angle 154^\circ * 4 + j2}{10 + j10} = 4 + j2$$

$$I_B = 10.8 \angle -172^\circ$$

~~$I_{AC} = \frac{110 \angle 120^\circ}{12 + j6} = 9.37 \angle 120^\circ$~~

I_B	I_{CA}	$I_{Line(total)}$	$P_{(total)}$	$PF_{(load)}$
$34.7 \angle -154^\circ$	$14.12 \angle 120^\circ$			

$$10.2 \angle -172^\circ$$

