

13.5

Name: محمد علي العبد ID# 0156397 Section # Serial #

Questions 1 (4 points)

If the source line voltage in the figure below is 208 V_{rms}, determine the source currents I_a, I_b, I_c and the current in the neutral line, I_{nN}. What is the total complex power supplied by the source, and what is the total power losses in the transmission lines.




$$V_{an} = \frac{208}{\sqrt{3}} \angle -30^\circ$$

$$= 120 \angle -30^\circ$$

$$V_{bn} = 120 \angle -150^\circ$$

$$V_{cn} = 120 \angle 150^\circ$$

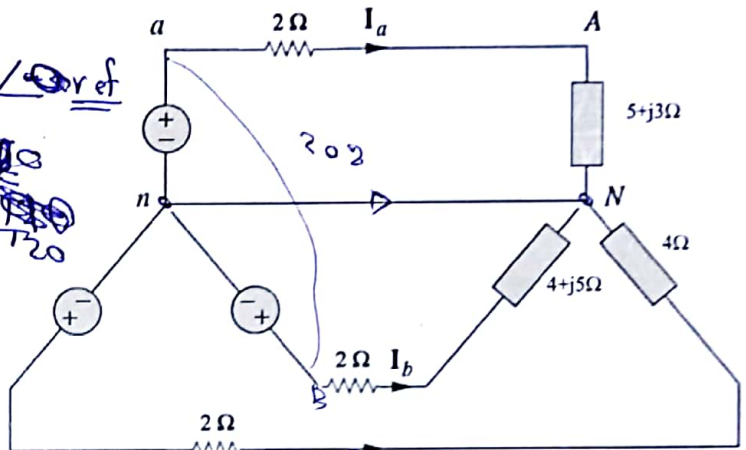

$$I_a = \frac{V_{an}}{2 + 5 + j3}$$

$$= \frac{120 \angle -30^\circ}{7 + j3} = 15 \angle -23.1^\circ$$

$$I_b = \frac{V_{bn}}{2 + 4 + j5} = 15.36 \angle -159.19^\circ$$

$$I_c = \frac{V_{cn}}{2 + 4} = 20 \angle 120^\circ$$

$$I_n = -(I_a + I_b + I_c)$$

$$I_n = -12.13 \angle -29.5^\circ$$

$$I_{nN} = I_n - I_N = 12.13 \angle -29.5^\circ$$

$$S_{source} = 3 V_l I_l^*$$

$$S_1 = 180 \angle -23.1^\circ$$

$$S_2 = 1943 \angle -159.19^\circ$$

$$S_3 = 2400 \angle 120^\circ$$

$$S = S_1 + S_2 + S_3 = 4359.3 + j2525.4$$


I _a	I _b	I _c	I _{nN}	S _{source}	P _{T.L. losses}
15 ∠ -23.1°	15.36 ∠ -159.19°	20 ∠ 120°	12.13 ∠ -29.5°	4359.3 + j2525.4	

POWERUNIT

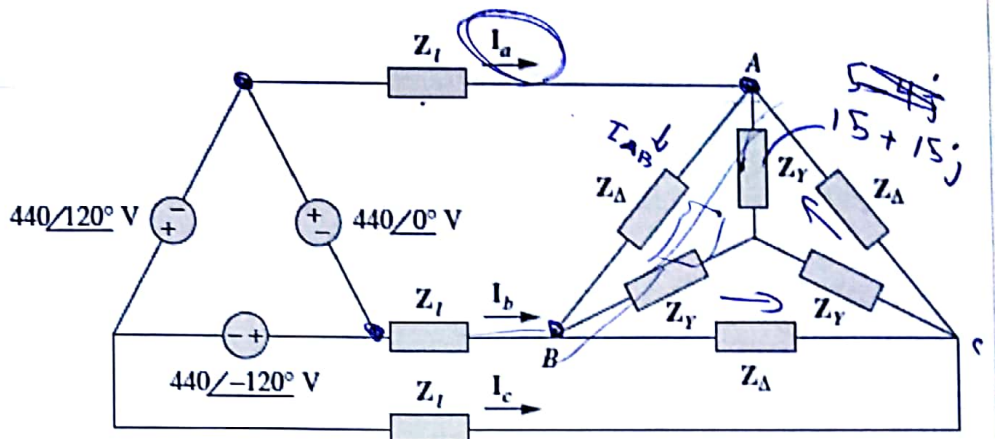Questions 2 (4 points)

For the shown figure below, if $Z_A = 15 - j12 \Omega$, $Z_Y = 5 + j5$, $Z_I = 3 \Omega$. The source voltages are given in RMS values. Find:

- The total line current I_a .
- The phase current I_{AB} in the Δ connected load.
- The line voltage at the load side V_{AB} .
- The total complex power consumed by the Y connected load.




$$I_a = I_{\Delta} + I_Y \Rightarrow I_{\Delta} = I_{AB} = \frac{V_{AB}}{Z_{\Delta}}$$

$$I_{\Delta} = I_{AB} - I_{CA} =$$

$$I_{AB} = 19.45 \left(\frac{3 + 3 + 15 + j5}{3 + 3 + 15 + j5 + 15 - j12} \right)$$

$$= 19.45 \angle 16.4^\circ$$


$$V_{AB} = 440$$

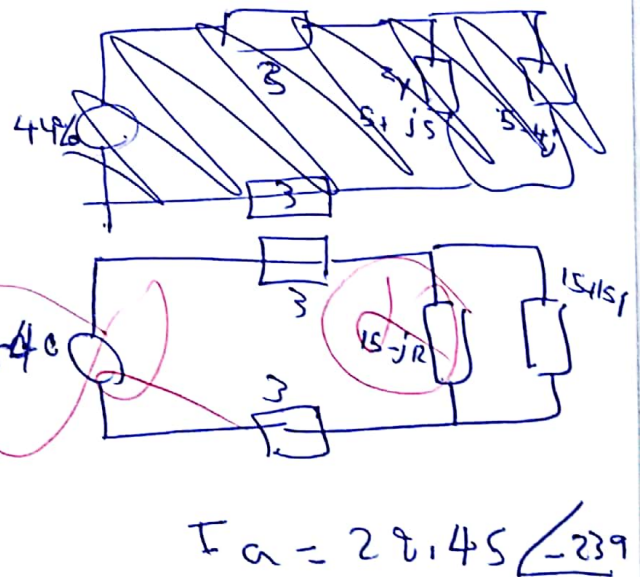

I_a	$I_{AB(\Delta)}$	$V_{AB(load)}$	S_Y
$28.45 \angle -23.9^\circ$	$20 \angle 16.4^\circ$		

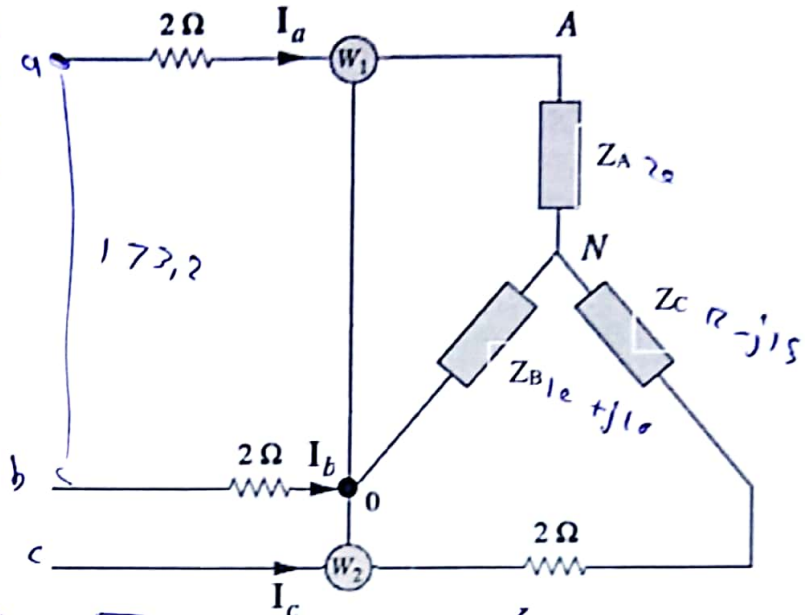Questions 3 (5 points)

For the circuit shown $Z_A = 20 \Omega$, $Z_B = 10 + j10 \Omega$, and $Z_C = 12 - j15 \Omega$, while the line voltage of the source is $173.2 V_{RMS}$. Find the readings of the two wattmeter's, the load power factor, and the apparent power supplied to the load.



3

$$W_1 \Rightarrow V_{ab} I_{aA}$$

$$W_2 \Rightarrow V_{cb} I_{cC}$$

$$V_{ab} = V_{AB} = 173.2 \angle 0^\circ$$

$$V_{bc} = 173.2 \angle -120^\circ$$

$$V_{ca} = 173.2 \angle +120^\circ$$

$$V_{an} = 99.9 \angle -30^\circ$$

~~$V_{an} = 173.2 \angle -30^\circ = 99.9 \angle -30^\circ$~~

$$I_{an} = \frac{V_{an}}{2 + 20} = 4.5 \angle -30^\circ$$

$$I_{bn} = \frac{V_{bn}}{2 + 10 + j10} = 6.3 \angle 170.1^\circ$$

$$I_{cn} = \frac{V_{cn}}{2 + 12 - j15} = 4.2 \angle 136.9^\circ$$

$$P_1 = |173.2| |4.5| \cos(0 - -30) = 674.9$$

$$P_2 = |173.2| |4.2| \cos(120 - 136.9) = 795.4$$

P_1	P_2	PF	S
674.9	795.4	0.990	1494.7

$$|S| = \sqrt{P_1^2 + P_2^2}$$


$$\tan \theta = \frac{\sqrt{3}(P_2 - P_1)}{P_1 + P_2}$$

$$\theta = 8.07^\circ$$

POWERUNIT

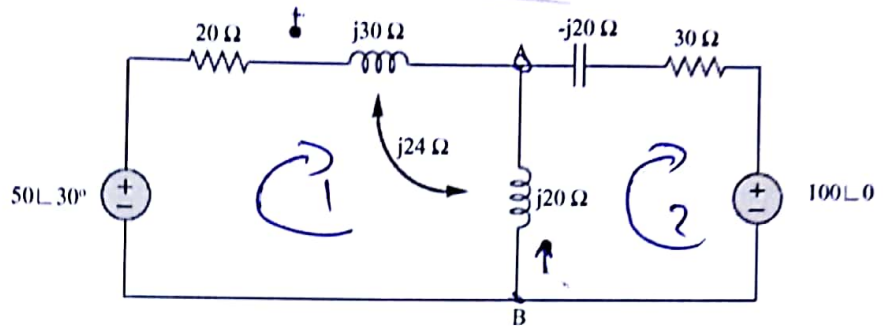Questions 4 (5 points)

In the shown network, write down the 2 mesh equations that governs the current relations in the circuit in their simplest form. Then find V_{AB} . The given voltages are in RMS.



$$-50 \angle 30^\circ + (20 + j30 + j20) I_1 + j24 I_2 = 0$$

$$(-j20j + 30 + j20j) I_2 + 100 \angle 0^\circ + j20 I_1 = 0$$

$$I_1 = \frac{-100 - 30 I_2}{20j}$$

$$(20 + 50j) \left(\frac{-100 - 30 I_2}{20j} \right) + 24j I_2 = 50 \angle 30^\circ$$

$$\frac{-2000 - 600 I_2 - 5000j - 1500j I_2}{20j} + 24j I_2 = 50 \angle 30^\circ$$

$$\frac{(-2000 - 5000j)}{20j} + \frac{(-600 - 1500j) I_2}{20j} + 24j I_2 = 50 \angle 30^\circ$$

Equations
1) $(20 + 50j) I_1 + 24j I_2 = 50 \angle 30^\circ$
2) $30 I_2 + 20j I_1 = -100$
$V_{AB} = 193.4 \angle 30^\circ$

$$(-250 + 100j) + (-75 + 30j) I_2 + (24j) I_2 = 50 \angle 30^\circ$$

$$(-75 + 54j) I_2 = 50 \angle 30^\circ$$

$$I_2 = \frac{50 \angle 30^\circ}{-75 + 54j} = \frac{-250 + 100j}{-1585}$$

$$I_2 = 3.27 \angle -79.38^\circ$$

$$I_1 = 0.4761 + 0.1925j$$


$$= 9.74 \angle -79.38^\circ$$

$$V_{AB} = V_A - V_B = I_1 R = (I_1 - I_2) j20$$



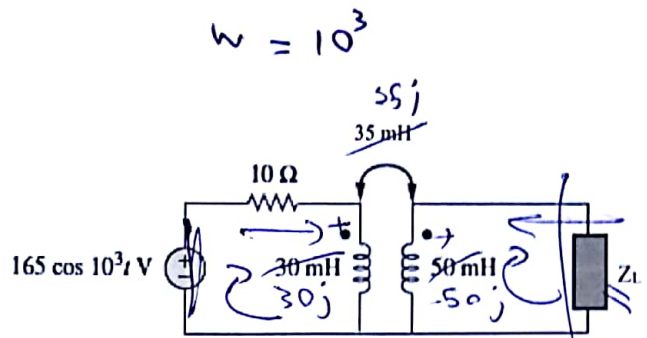Question 5 (5 points)


For the circuit shown, find the value of Z_L that maximize the power transferred to the load, and what is this maximum power. Find the energy stored in the coupled coils at $t=0^-$.



$$Z_L = Z_{th}$$

$$10 + 30$$

$$10 + 30j$$

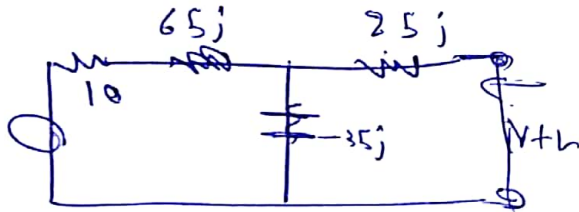

$$(10 + 65j) // -35j + 25j$$

$$Z_{th} = 12.25 + 13.25j$$

$$Z_L = 12.25 - 13.25j$$

$$P_{max} = \frac{V_{th}^2}{8R} = 340.23 \text{ W}$$

~~$$30 \text{ mH} = j\omega L$$~~

~~$$30 \text{ mH} = j$$~~

$$30 \rightarrow j 10^3 30 \cdot 10^{-3} = 30j$$

$$L_a = L_1 + M$$

$$L_b = L_2 + M$$

$$L_c = -M$$

$$L_a = 30j + 35j$$

$$= 65j$$

$$L_b = 50j + 35j$$

$$= 85j$$

$$L_c = -35j$$

$$V_{th} = 165 \left(\frac{-35j}{10 + 65j - 35j} \right) = 122.6 \angle -1.61$$


Z_L	P_{max}	W_{total}
12.25	340.23	XXXX

~~$$-13.25j$$~~

2.8

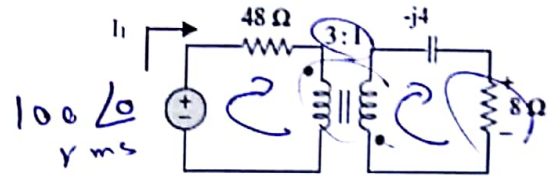Question 6 (3 points):

For the circuit shown below find the input current I_1 and the power absorbed by the 8Ω resistor.



~~$100 + 48$~~

~~$100 + 48$~~

$$Z_{in} = \frac{Z_L}{n^2}$$

$$= \frac{8 - j4}{\left(\frac{1}{3}\right)^2} = 72 - 36j$$

$M =$

$$\frac{N_2}{N_1} = \frac{1}{3}$$

$$-\frac{1}{3} = \frac{I_1}{I_2}$$

$$I_2 = -3I_1$$


$100 \angle 0 + 48 I_1 +$

I_1	P



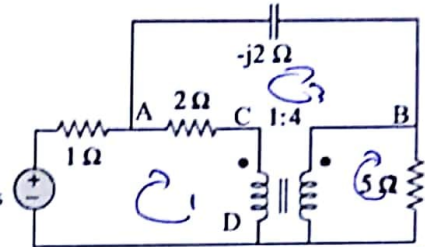Question 7 (4 points)

For the circuit shown, find the power absorbed by the 5Ω load. Find the voltages V_{AB} , V_{CD} , and the source PF.



$$-10 + I_1 + 2(I_1 - I_3) + V_1 = 0 \quad V_1 = 10 \angle 0 \text{ V}_{\text{RMS}}$$

$$5 I_2 + V_2 = 0$$

$$-2j I_3 + V_1 + V_2 + 2 I_3 = 0$$

$$5 I_2 + V_2 = 0$$

$$\frac{V_2}{V_1} = \frac{4}{1}$$

$$V_2 = 4V,$$

P	V_{AB}	V_{CD}	PF_{source}