

CIRCUITS 2
SECOND EXAM
FALL-2013



Q1	12/12
Q2	5/5
Q3	12/12
Q4	0/5
Q5	0/5
Q6	5/5
Q7	13/15
Q8	10
Q9	15
Q10	10

22
25

University of Jordan

Electrical Eng. Dept

EE 93212 circuit (2)

الرقم الجامعي: ٥٦٤٩٢١

رقم التفقد (١٣)

Second Exam.

16-12-2013

الاسم: ريم جعفر ابراهيم

Q1) Evaluate the energy stored in the circuit shown in Fig.1 at $t=2 \text{ ms}$

given that $i_1=0$, $i_2=5\cos(1000t+30^\circ)$, $k=0.5$ and $L_1=2 \text{ H}$. [10 %]

$$L = \frac{M}{\sqrt{L_1 L_2}} = \frac{2}{\sqrt{2 \times 8}} = 0.5 \text{ H}$$

$$\boxed{L = 0.5 \text{ H}}$$

$$L_{21} = \frac{16}{2} = 8 \text{ H}$$

$$\boxed{L_2 = 8 \text{ H}}$$

$$\omega = \frac{1}{2} L_2 I_2^2$$

$$L_2 = 5 \cos(1000t+30^\circ) @ t = 2 \times 10^{-3}$$

$$I_2(2 \times 10^{-3}) = 5 \cos(2 + 30^\circ) = 5 \times -0.815 = -4.075 \text{ A}$$

$$\omega = \frac{1}{2} \times (8) \times (-4.075)^2 = 66.434 \text{ rad/s}$$

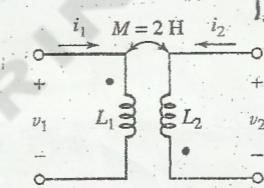


Fig. 1

Q2) Write the mesh equation in frequency domain for the mesh of I_3 in the circuit shown in Fig. 2. [5 %]

$$(11 + j6\omega) I_3 - j6\omega I_2 - 6 I_1 + j2\omega I_2 = 0$$

$$\boxed{(11 + j6\omega) I_3 - j6\omega I_2 - 6 I_1 = 0}$$

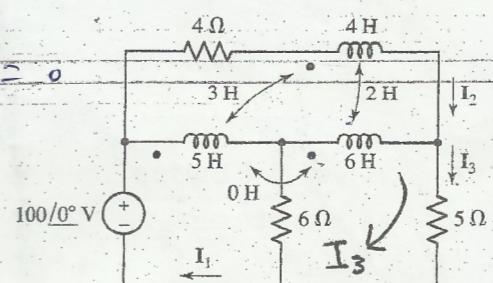


Fig. 2

Q3) Evaluate Z_{in} of the circuit shown in Fig.3, if Z_L is $100 \mu\text{F}$ having impedance of $-j31.38 \Omega$. [10 %]

$$Z_L = -j31.38 = \frac{1}{j\omega \times 100 \times 10^{-6}}$$

$$\omega = \frac{-1}{-531.38 \times j100 \times 10^{-6}} = 318.67$$

$$Z_{in} = Z_{11} + \frac{\omega^2 M^2}{Z_{22}}$$

[10 %]

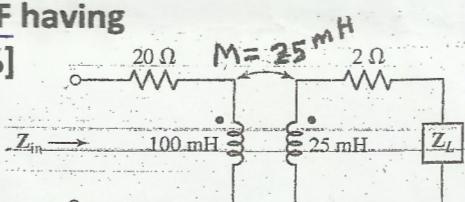


Fig. 3

$$Z_{11} = 20 + j31.867$$

$$Z_{22} = 2 - j31.38 + j8 = 2 - j23.41$$

$$Z_{in} = 20 + j31.867 + \frac{(25 \times 10^{-3})^2 \times (318.67)^2}{2 - j23.41} = 20.23 + j34.56$$

Q4) In the circuit shown in Fig.4, if $C=0$ evaluate V_2 . [5 %]


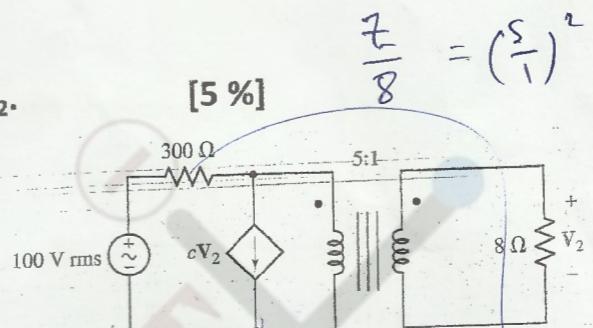
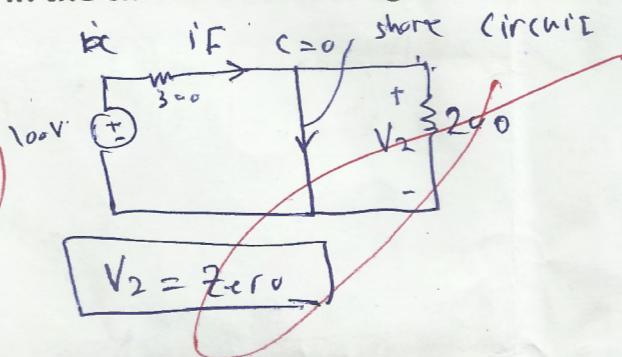


Fig. 4

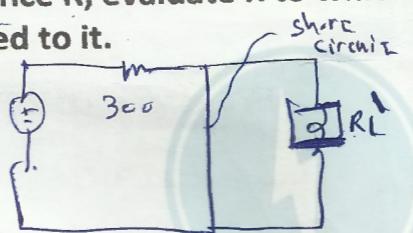Q5) In the circuit shown in Fig. 4, if $c=0$ and the 8Ω is replaced by a resistance R , evaluate R to which maximum average power is supplied to it. [5 %]




$$RL' = 5^2 R$$

$$R = \text{Zero}$$

[5 %]

No current passes through

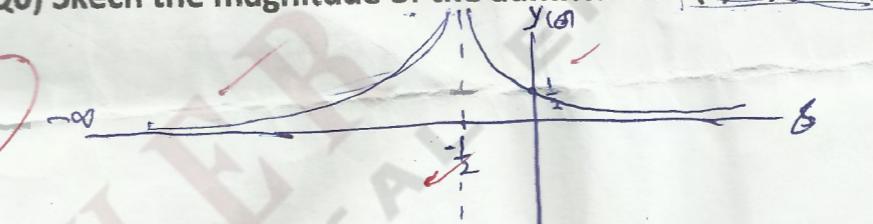Q6) Sketch the magnitude of the admittance $Y(s)=1/(2+4s)$ with s if $s=\sigma+j0$. [5 %]



[5 %]

Q7) The input admittance $Y(s)$ of a given a two terminal network is given as $Y(s)=(s^2+6s+8)/(15s^2+45s)$, evaluate the complete response of the input voltage $v(t)$ if the input current is $i(t)=150 e^{-t}$. [15 %]

$$Y(s) = \frac{s^2 + 6s + 8}{15s^2 + 45s} = \frac{I(s)}{V(s)} \quad Z(s) = \frac{V(s)}{I(s)} = \frac{15s^2 + 45s}{s^2 + 6s + 8}$$

$$s^2 + 6s + 8 = 0$$

$$s = -2 \quad s = -4 \quad \text{poles}$$

~~$$V_n(t) = A e^{-2t} + B e^{-4t}$$~~

~~$s < 0$~~

3
6
4

$$V_F(s) = 150 \angle 0^\circ + \frac{15(-1)^2 - 45}{1 - 6 + 8} = -1500 \text{ V}$$

$$V_{\text{com}} = V_n(t) + V_F(t) = A e^{-2t} + B e^{-4t} - 1500 \text{ V}$$

Q8) Evaluates the poles and zeros of Z_{in} of the circuit shown in Fig. 5 [10 %]

$$Z_{in}(s) = (12+6s) \parallel 2s \parallel 3$$

$$\text{W} \quad (12+6s) \parallel (2s) = \frac{(12+6s) * 2s}{12+8s} = \frac{2us + 12s^2}{12+8s}$$

$$12+6s \parallel 2s \parallel 3 = \frac{2us + 12s^2 * 3}{12+8s} = \frac{3(2us + 12s^2)}{36 + 48s + 12s^2}$$

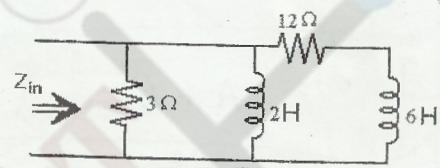


Fig. 5

Zeros $s=0$
 $s=-2$
Poles $s=-1$
 $s=-3$

Q9) For the circuit shown in Fig. 6, evaluate $i_L(t)$ if $i_s(t)=64\cos(100\pi t)$ mA. [15 %]

$$I_s = 6U < 0$$

$$(j12+3) i_L - j12 * 6U < 0 + jUx6U < 0 + jUx6U < 0$$

$$-jU i_L - jU i_L = 0$$

$$(3+jU)i_L - jUx6U < 0 = 0$$

$$\cancel{i_L = 6U < 0}$$

$$\boxed{i_L = 51.2 < 36.869 \text{ mA}}$$


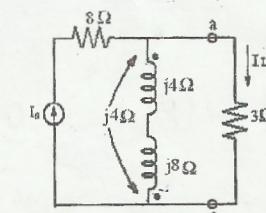
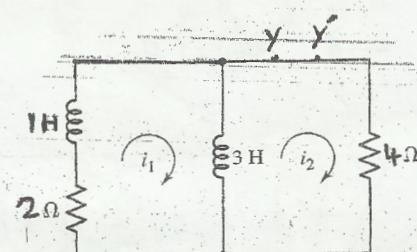


Fig. 6

$$i_L(t) = 51.2 \cos(100\pi t + 36.869) \text{ mA}$$

Q10) Evaluate $i_2(t)$ in the circuit shown in Fig. 7 by installing a suitable source across the points y and y'. Given that $i_1(0)=i_2(0)=1$ A. [20 %]

Solution:

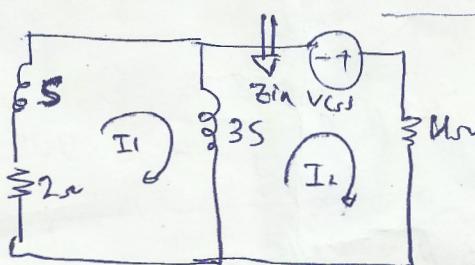

$$\frac{I_2(s)}{V(s)} = Y(s) = \frac{1}{Z(s)}$$

Fig. 7

$$Z(s) = ((s+2) \parallel 3s) + u = \frac{3s(s+2)}{us+2} + u$$

$$= \frac{3s^2 + 6s}{us+2} + u \left(\frac{us+2}{us+2} \right) = \frac{3s^2 + 6s + 18s + 8}{us+2} = \frac{3s^2 + 22s + 8}{us+2}$$

$$\frac{I_2(s)}{V(s)} = \cancel{Y(s)} = \frac{1}{Z(s)} = \frac{us+2}{3s^2 + 22s + 8}$$

Celó dsl al s
Tere, ekk!

$$Y(s) = \frac{Us + 2}{3s^2 + 22s + 8} = \frac{I_2(s)}{\sqrt{s}}$$

$$I_2(s) = A e^{-0.3837s} + B e^{-6.949s}$$

$$I_2(0) = A + B = 1 \quad \dots \textcircled{1}$$

$$L_1 \left. \frac{dI_1(T)}{dT} \right|_{T=0} + 2I_1(0) + U(I_2(0)) = 0$$

$$\left. \frac{dU_1(U)}{dU} \right|_{U=0} = -6$$

$$U(I_2(0)) + 3 \left. \frac{dI_2(U)}{dT} \right|_{T=0} - 3 \left. \frac{dI_1(U)}{dT} \right|_{T=0}$$

$$3 \left. \frac{dI_2(U)}{dT} \right|_{T=0} = -18 - U = -22$$

$$\left. \frac{dI_2(U)}{dT} \right|_{T=0} = -\frac{22}{3} = -7.33$$

$$\therefore \frac{\sqrt{I_2(0)}}{I_2} = -0.383A e^{-0.3837} - 6.949B e^{-6.949}$$

$$-7.33 = -0.383A - 6.949B \quad \dots \textcircled{2}$$

$$A = -0.058$$

$$B = 1.058$$

$$I_2(T) = -0.058 e^{-0.3837T} + 1.058 e^{-6.949T}$$

173