

CIRCUITS 2
FIRST EXAM
FALL-2013



$$\left(\frac{70}{100}\right) = \left(\frac{18}{25}\right)$$

University of Jordan

Electrical Eng. Dept

- Q1) 11/15
- Q2) 8/8
- Q3) 17/17
- Q4) 5/25
- Q5) 29/35

EE 93212 circuit (2)

First Exam.

4-11-2013

الاسم: رضا يوسف اسمعيل عيسى رقم التفتقد (٤٥) الرقم الجامعي: ٥١٥ ٤٩٢١

Q1) The phasor voltage $V=8/0^\circ$ V is applied across the impedance $Z=4/60^\circ$

Ω . If $\omega=\pi$ Rad./S, draw on the same graph the followings:

a-The instantaneous power $p(t)$ with time t .

b-The voltage $v(t)$ with time t .

[15%]

$$v(t) = 8 \cos(\pi t)$$


$$I = \frac{8 \angle 0^\circ}{4 \angle 60^\circ} = 2 \angle -60^\circ$$

$$p(t) = v(t) i(t)$$

$$i(t) = 2 \cos(\pi t - 60^\circ)$$

$$= 8 \cos(\pi t) \times 2 \cos(\pi t - 60^\circ) = 16 \left(\frac{1}{2} \cos(60^\circ) + \frac{1}{2} \cos(2\pi t - 60^\circ) \right)$$

$$p(t) = 4 + 8 \cos(2\pi t - 60^\circ)$$

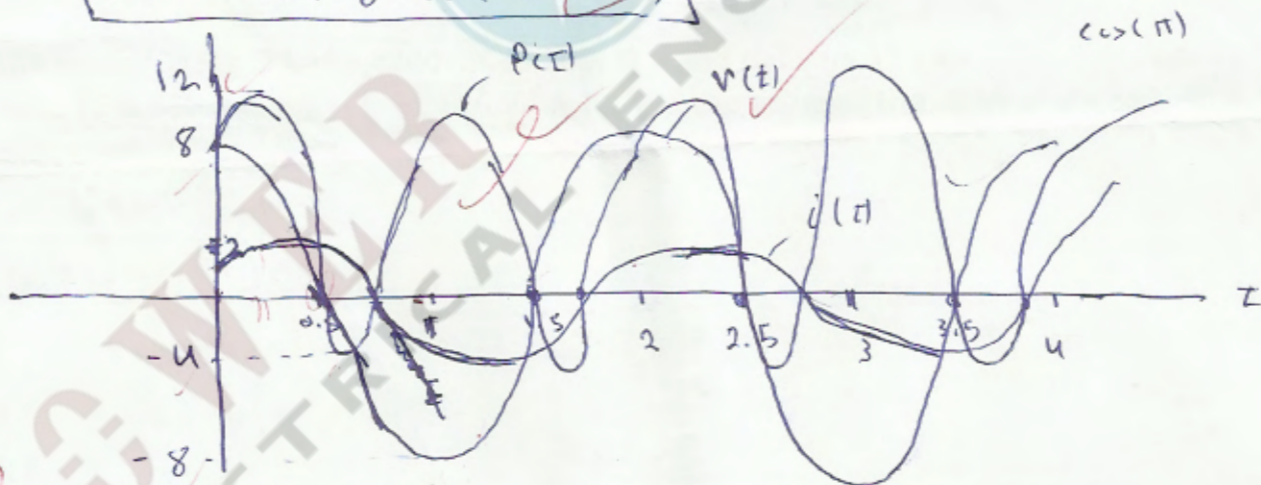

Q2) Evaluate R in Fig.1 to which maximum power is supplied. [8%]

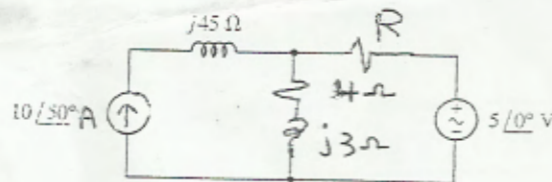
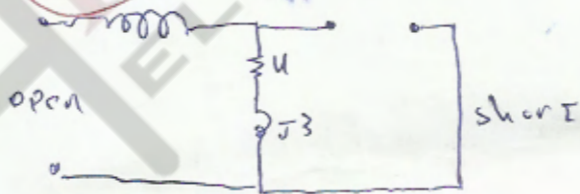


Fig. 1

$$Z_{th} = 4 + j3 = R_{th} + jX_{th}$$

$$R_L = \sqrt{(R_{th})^2 + (X_{th})^2} = \sqrt{4^2 + 3^2} = 5 \Omega$$

$$R_L = 5 \Omega$$

Q3) For the signals shown in Fig. 2, calculate the effective value of the voltage $v(t)$, if $v(t) = v_1(t) + v_2(t) + v_3(t)$ [17%]

$v_1(t) = 40 \sin\left(\frac{2\pi}{20 \times 10^{-3}} t\right) = 40 \cos\left(\frac{2\pi}{20 \times 10^{-3}} t - 90^\circ\right)$
 $v_2(t) = 50 \cos\left(\frac{2\pi}{20 \times 10^{-3}} t - 36^\circ\right)$
 $v_3(t) = -\sin\left(\frac{2\pi}{6.667 \times 10^{-3}} t + 5\mu\right)$
 $v_3(t) = \sin\left(\frac{2\pi}{6.667 \times 10^{-3}} t + 23\mu\right)$
 $v_3(t) = 30 \cos\left(\frac{2\pi}{6.667 \times 10^{-3}} t + 14\mu\right)$

$v_2(t), v_3(t)$ — same freq
 $40 \angle -90^\circ + 50 \angle -36^\circ = 80.31899 \angle -60^\circ$

$v(t) = 80.31899 \cos\left(\frac{2\pi}{20 \times 10^{-3}} t - 60^\circ\right) + 30 \cos\left(\frac{2\pi}{6.667 \times 10^{-3}} t + 14\mu\right)$

$V_{r.m.s} = \sqrt{\frac{(80.31899)^2}{2} + \frac{30^2}{2}} = 60.626 \text{ r.m.s}$

Fig. 2

Q4) The source in Fig. 3 has $v_s = 240\sqrt{2} \cos(100\pi t)$ V and delivers 12 kVA with PF 0.866 lagging. If $I_L = 50\sqrt{3} \angle -60^\circ$ A_{rms}, find the value of the capacitor. [25%]

$S = 12 \text{ kVA} \angle 30^\circ$
 $V_s = 240 \angle 0^\circ \text{ r.m.s}$

$P = 12 \text{ kVA} \times \cos(30^\circ) = 10.3923 \text{ kW}$

$V_R = 50.6 \times 50 \angle -60^\circ$

$V_R = 51.961524 \angle 30^\circ$

$V_L = 240 \angle 0^\circ - 51.9615 \angle 30^\circ = 196.723 \angle -7.589^\circ$

$Z_L = \frac{V_L}{I_L} = \frac{196.723 \angle -7.589^\circ}{50\sqrt{3} \angle -60^\circ} = 2.27156 \angle 52.411^\circ = 1.3856 + j1.8$

$Z_{eq} = (1.3856 + j1.8 + j0.6) \times \frac{1}{j\omega C}$

$Y_{eq} = \frac{1}{Z_L + j0.6} = \frac{1}{1.3856 + j1.8 + j0.6} = 0.18042 - j0.3125$

$Y_C = j\omega C$

$Y_{eq} = j\omega C + 0.18042 - j0.3125 = 0.18042 + j(\omega C - 0.3125)$

$\cos^{-1}(0.866) = 30$

$\tan(30) = 0.57735 = \frac{\omega C - 0.3125}{0.18042} \Rightarrow C = 1.325 \times 10^{-3} \text{ F}$

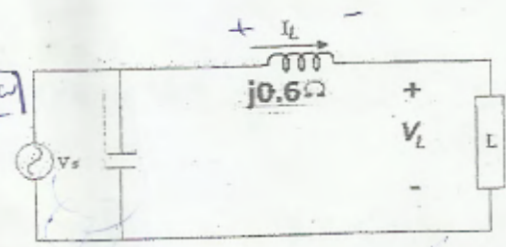



Fig. 3

Q5) A balanced Δ -load is connected in parallel with a balanced Y-load. The impedance per phase for Δ is $50 \angle -30^\circ \Omega$ and for Y is $25 \angle 60^\circ \Omega$.

If $V_{ac} = 200 \angle 0^\circ V_{RMS}$ and assuming positive phase sequence, find:

a- The current I_{bb} .

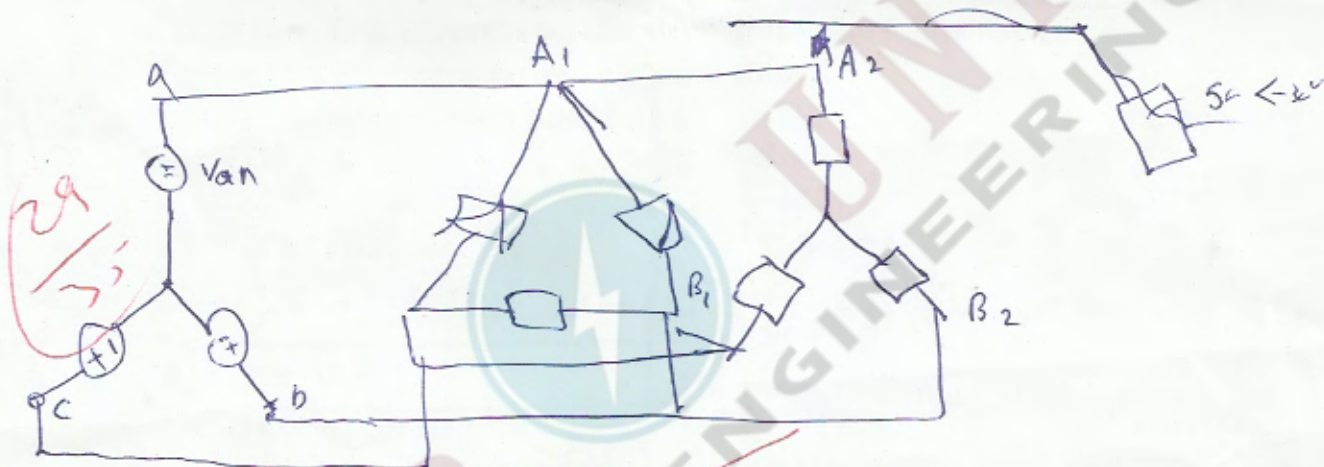b- The reading of the wattmeter connected in phase C with its potential coil connected between C and N of the Y-load. [35%]



$V_{bc} = 200 \angle 0^\circ \rightarrow V_{ca} = 200 \angle 180^\circ$

$V_{ab} = 200 \angle 30^\circ$ $200 \angle 120^\circ =$

$V_{bc} = 200 \angle 300^\circ$

$V_{ca} = 200 \angle 180^\circ$

$V_{bN} = \sqrt{3} V_{bn} \angle 30^\circ$

$V_{bn} = \frac{V_{bc}}{\sqrt{3}} \angle 300^\circ = \frac{200 \angle 300^\circ}{\sqrt{3}} \angle 30^\circ$

$= \frac{200 \angle 300^\circ}{\sqrt{3}} \angle 30^\circ$

$= 115.47 \angle 270^\circ$

$I_{B2N} = \frac{V_{bn}}{Z_Y} = \frac{115.47 \angle 270^\circ}{25 \angle 60^\circ} = 4.6188 \angle -150^\circ$

$I_{B1C1} = \frac{V_{bc}}{Z_{\Delta}} = \frac{200 \angle 300^\circ}{50 \angle -30^\circ} = 4 \angle 330^\circ$

$I_{B1} = \sqrt{3} I_{B1C1} \angle -30^\circ = 6.928 \angle 300^\circ$

$I_{Bb} = I_{B1} + I_{B2N} = 6.928 \angle 300^\circ + 4.6188 \angle -150^\circ$

$I_{Bb} = 8.3211 \angle -93.7^\circ$

$I_{Bb} = -I_{bB}$

Handwritten note: $I_{Bb} = -I_{bB}$

$P = |I_{cc}| |V_{cn}| \cos(\angle V_{cn} - \angle I_{cc})$

$I_{cc} = I_{cn} = -I_{c2N} = 4.6188 \angle -150^\circ - 120^\circ = 4.6188 \angle -270^\circ$

$V_{cn} = 115.47 \angle 270^\circ - 120^\circ = 115.47 \angle 150^\circ$

$$\begin{aligned} W &= |I_{cc}| \times |V_{cc}| \cos(\angle V_{cc} - \angle I_{cc}) \\ &= 115.47 \times 1.6188 \cos(390 - (-270)) = \boxed{266.666 \text{ W}} \end{aligned}$$

$$W = 115.47 \times 1.6188 \cos(150 + 270) = \boxed{266.666 \text{ W}}$$



POWER ELECTRICAL ENGINEERING