

Circuits I Notebook

Dr. Ra'ed Alzo3bie

By : Marah Alomarie

بأفكارنا نبدع

*** units**

International system of units (SI)

⇒ 7 basic units:

meter m

kilogram kg

second s

Ampere A


kelvin K

mole mol

candela cd


*** other units**⇒ unit of work or energy is Joule (J) = kgm^2/s^2 ⇒ unit of power is watt (W) = J/s*** SI prefixes** 10^{-3} milli (m) 10^{-6} micro (μ) 10^{-9} nano (n) 10^{-12} pico (p)*** Charge** → **negative** (electron) $-1.602 \times 10^{-19} \text{ C} \rightarrow \text{Coulomb}$ → **positive** (proton) $+1.602 \times 10^{-19} \text{ C}$

Subject:

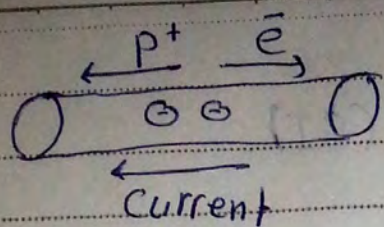

=> The direction of the current is opposite to direction of negative charges.

* Current

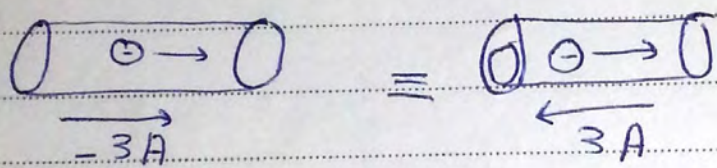

التيار الكهربائي


* Types of current

① DC (Direct current) :

A current that is constant with time

e.g => $I = 4 A$


$I = -2.3 A$

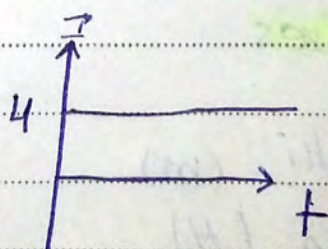

② AC (Alternating Current) :


a current that changes sinusoidally with time

e.g => $i(t) = -4.5 \sin(200\pi t) A$

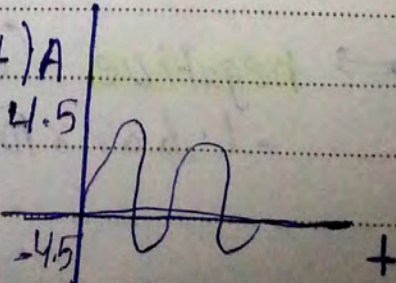

Subject:

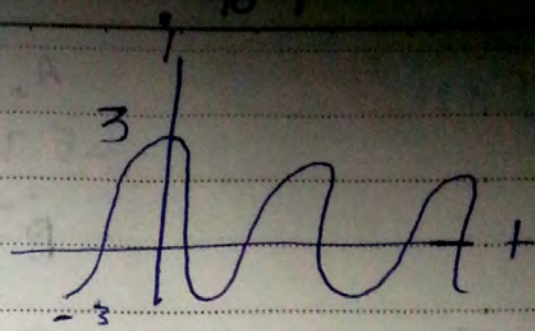
eg $\Rightarrow i(t) = 3 \cos(100\pi t) \text{ A}$




③ other types:

\Rightarrow exponential current

$i(t) = 2e^{-3t} \text{ A}$

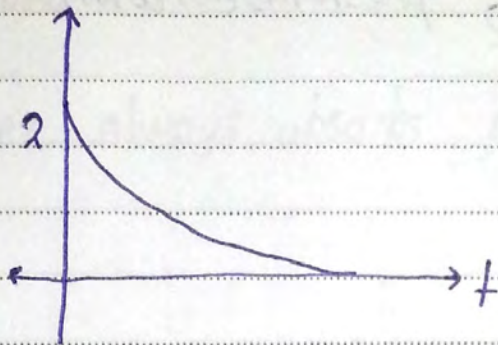

\Rightarrow damped sinusoidal current

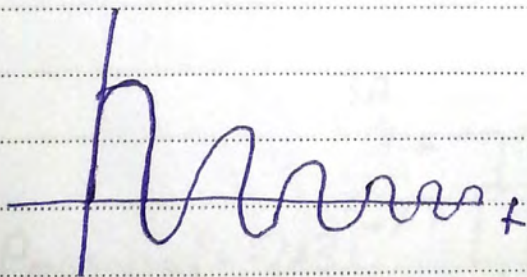


التيار المتذبذب *

* Voltage V_0

\Rightarrow unit \Rightarrow Volt (V)

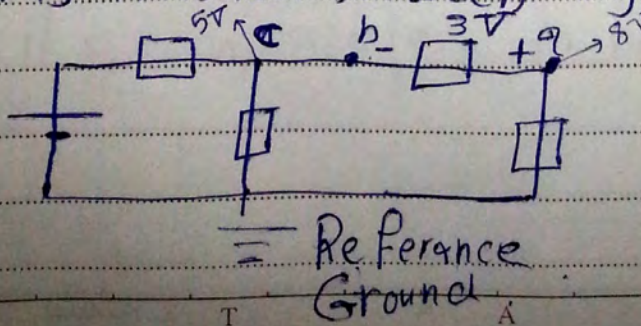\Rightarrow it is measured between any two points in the circuit




Terminal a is 3V positive with respect to terminal b

Subject:

16/9/1

Ex 20

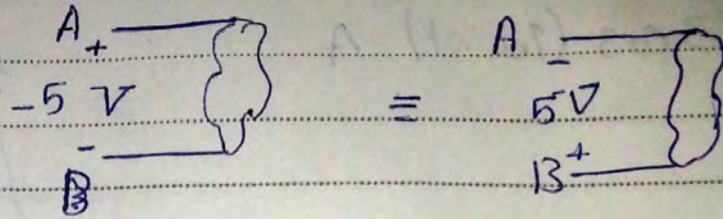

* Terminal A is $5V$ negative with respect to Terminal B

* Terminal B is $5V$ positive with respect to Terminal A

* power is
unit : watt (w)


$$p(t) = i(t)v(t)$$

$$P = I \cdot V$$

⇒ power could be Generated (supplied) or absorbed (consumed)

⇒ Resistor always absorbs power


* $P_{\text{absorbed}} = I \cdot V$

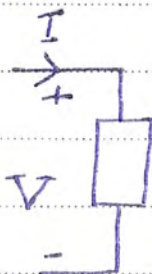

Ex:

Find $P_{\text{absorbed}} = -2 \times 3 = -6$


$$P_{\text{generated}} = +6 \text{ W}$$

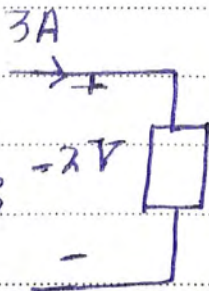

التيار في المقاومة *
Pgenerated في الدارة
هو +

⇒ it is impossible to be resistor.

Ex 2

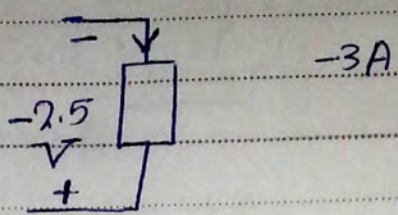


$$P_{\text{absorbed}} = -2.5 \times 3$$

$$= -7.5 \text{ W}$$

$$P_{\text{generated}} = 7.5 \text{ W}$$

Ex 3

$$P_{\text{generated}} = 25 \text{ W}$$

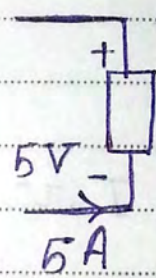


$$P_{\text{absorbed}} = 5 \times -5 = -25 \text{ W}$$

$$0 = \sum P_{\text{absorbed}} + \sum P_{\text{generated}} = 0$$


$$\sum P_{\text{absorbed}} = -\sum P_{\text{generated}}$$

* Sources


① Voltage Sources

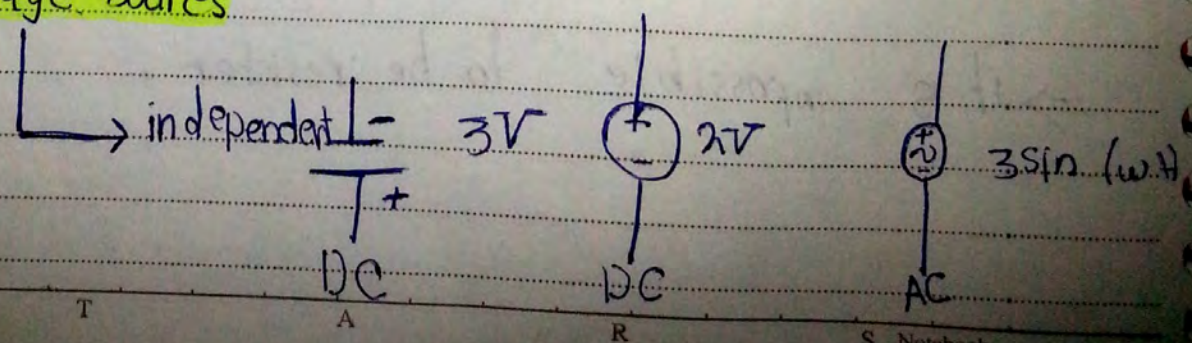





* dependent

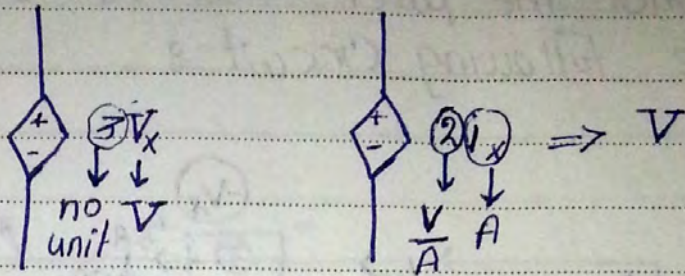


Ex 30

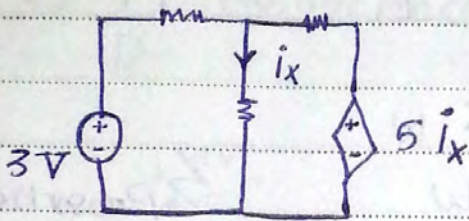

② Current Sources

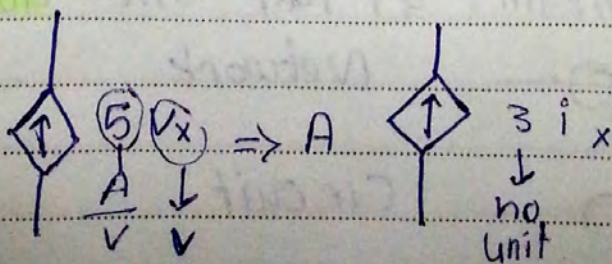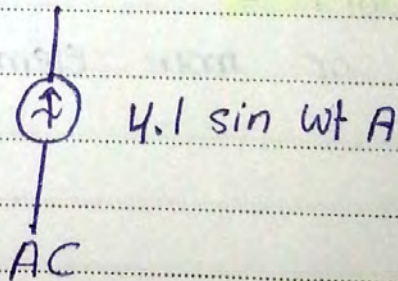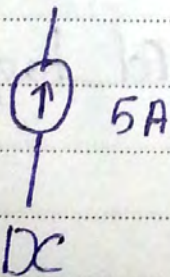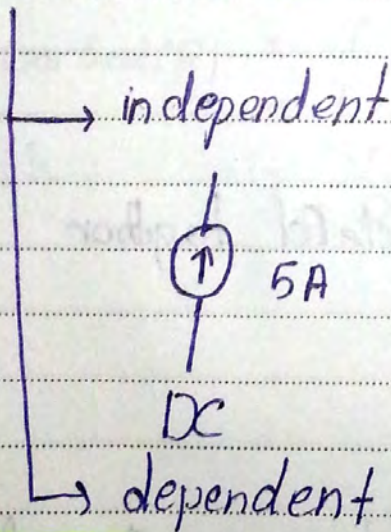

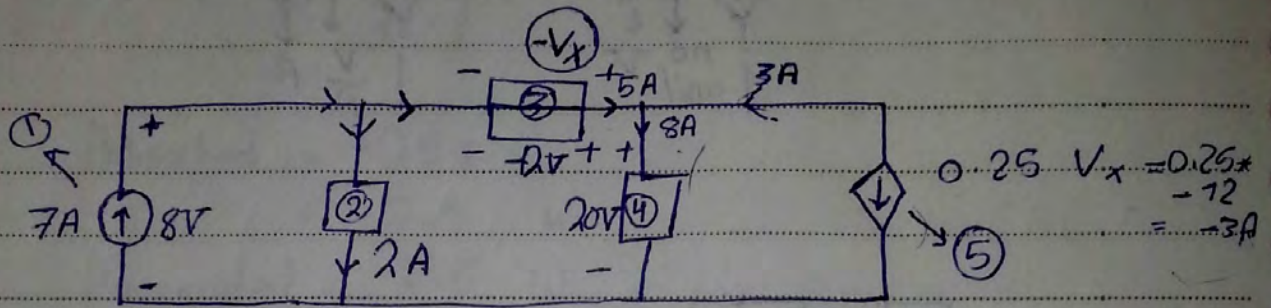Ex. 6 Find the power absorbed by each element in the following circuit:



$P_{\text{absorbed}}(1) = 8 \times -7 = -56 \text{ W}$

$P_{\text{absorbed}}(2) = 8 \times 2 = 16 \text{ W}$

$P_{\text{absorbed}}(3) = 20 \times -5 = -100 \text{ W}$


$\sum P_{\text{absorbed}} = 0$

$P_{\text{absorbed}}(4) = 20 \times 8 = 160 \text{ W}$

$P_{\text{absorbed}}(5) = 20 \times -3 = -60 \text{ W}$


* Network :-

Two or more elements connected together

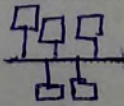


* Circuit

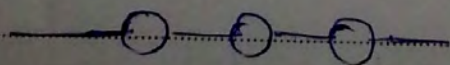
a Network contains at least one closed path



Network

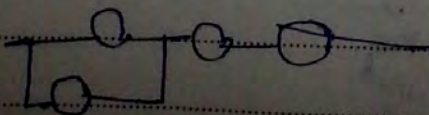

Circuit

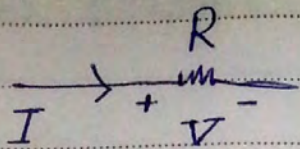
*** Ohm's law**

$$\Rightarrow I = \frac{V}{R}$$

$$\Rightarrow R: \text{resistance } (\Omega)$$

$$\Rightarrow G = \frac{1}{R} \text{ conductance (U mho)}$$

$$\text{(S siemens)}$$

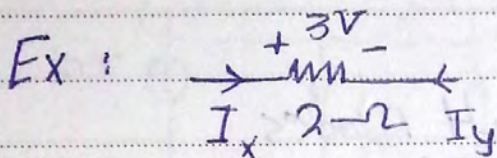find I_x .

$$I_x = \frac{3}{2} = 1.5 \text{ A}$$

$$I_y = -\frac{3}{2} = -1.5 \text{ A}$$

$$P_{\text{absorbed (R)}} = IV$$

$$= I \cdot I \cdot R$$

$$= \frac{V^2}{R}$$


$$\begin{aligned}
 P_{\text{absorbed}} &= I V \\
 &= I^2 R \\
 &= \frac{V^2}{R}
 \end{aligned}$$

↓

+ve

Ch 3 : KVL, KCL, series and parallel connection

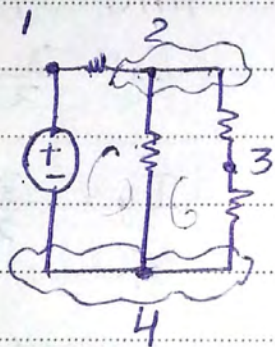⇒ Node : a point at which two or more elements are connected



⇒ 4 nodes

⇒ 3 loops

⇒ 5 branches


⇒ Path : a set of elements and nodes passed. (one element should be passed one time) from node to node

⇒ loop : a closed path.

⇒ Branch : element

* Kirchhoff current law (KCL)


=> charge conservation

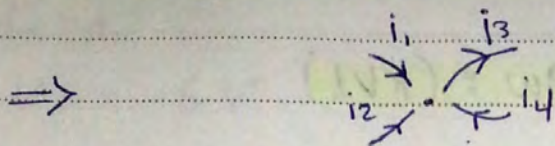

$$\sum i_{in} = \sum i_{out}$$

$$i_1 + i_2 + i_4 = i_3$$

Ex Find i_x .

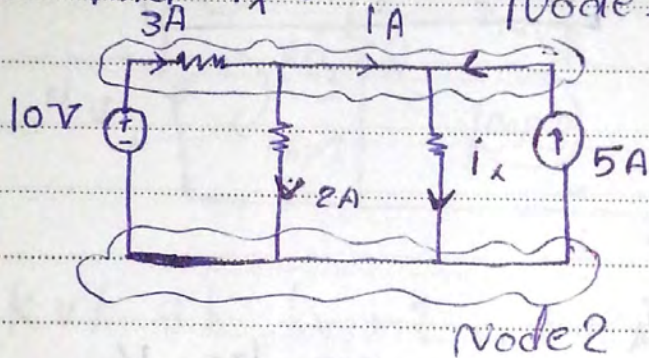

$i_x =$

KCL at Node 1:


$$3 + 5 = 2 + i_x$$

$$i_x = 6 \text{ A}$$

KCL at Node 2

$$2 + i_x = 5 + 3$$

$$i_x = 6 \text{ A}$$

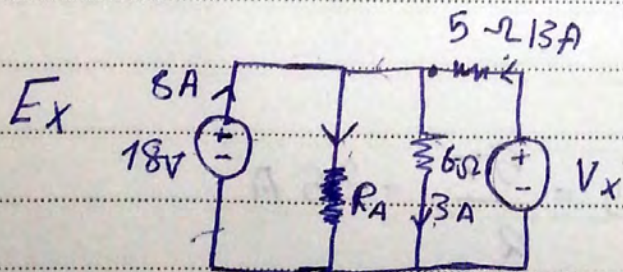

Find $R_A = 8 + 13 = 3 + jA$


$$jA = 18$$

$$R = \frac{18}{18} = 1 \Omega$$

$$U_{5\Omega} = 13 * 5 = 65 \text{ V}$$

$$65 = V_x - 18$$


$$\Rightarrow V_x = 83 \text{ V}$$

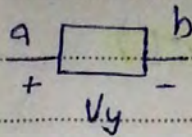*  $\Rightarrow V_y = V_a - V_b$

* Kirchhoff Voltage Law: (KVL)


\Rightarrow energy conservation

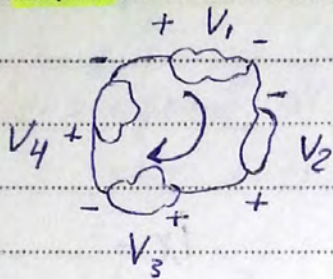\Rightarrow The sum of voltages over a closed path is zero.



$$V_1 - V_2 + V_3 + V_4 = 0$$

Ex: Find i_x and V_x

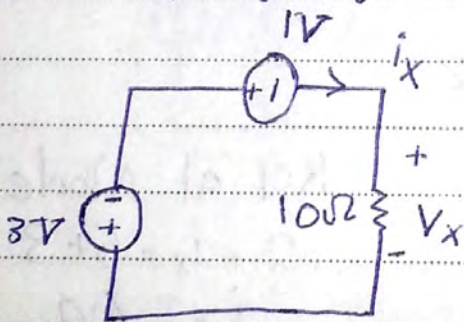


$$3V + 1V + V_x = 0$$

$$V_x = -4V$$

$$i_x = \frac{-4}{10} = -0.4A$$


Ex

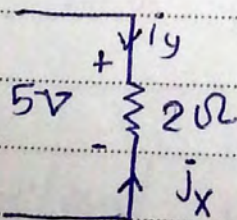

$$i_y = \frac{5V}{2} = 2.5A$$

$$i_x = -2.5A$$

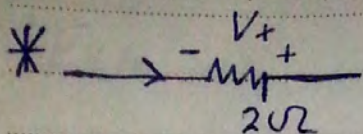
Positive direction of current is downwards \leftarrow



$$i = 3A$$

$$V_x = -6V$$

Ex Find V_{R_2} and V_x

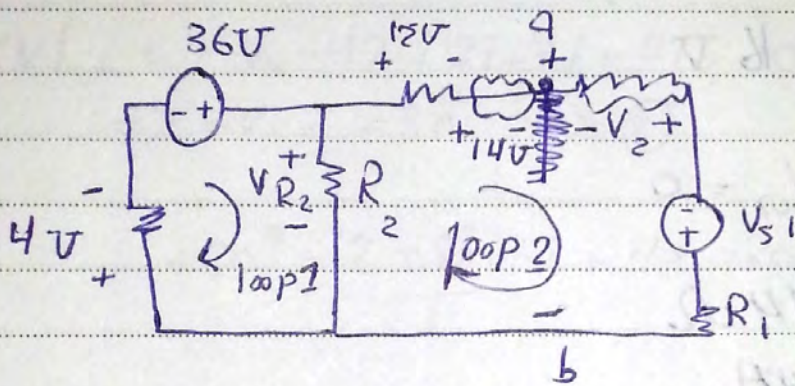

$$\text{KVL at loop 1: } 4 - 36 + V_{R_2} = 0$$


$$V_{R_2} = 32V$$

$$\text{KVL at loop 2: } -32 + 12 + 14 + V_x = 0$$

$$V_x = 6V$$

$$\text{KVL at loop 3: } 4 - 36 + 12 + 14 + V_x = 0$$

$$V_x = 8V$$

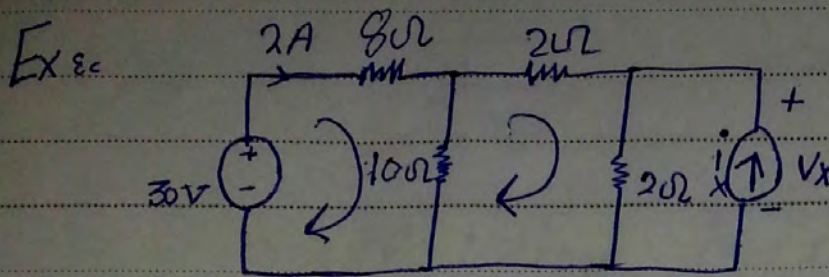

Find V_x and i_x ∞

* 4 nodes

$$\Rightarrow V_{8\Omega} = 2 \times 8 = 16 \text{ V}$$

$$\Rightarrow -30 + 16 + \frac{V}{100\Omega} = 0$$

$$V_{100\Omega} = 14 \text{ V}$$

$$\Rightarrow \frac{I}{100\Omega} = \frac{14}{10} = 1.4 \text{ A}$$

$$\Rightarrow \frac{I}{2\Omega} = 2 - 1.4 = 0.6 \text{ A}$$

$$\Rightarrow V_{2\Omega} = 0.6 \times 2 = 1.2 \text{ V}$$


$$\Rightarrow -14 + 1.2 + V_x = 0$$

$$V_x = 12.8 \text{ V}$$

$$\Rightarrow i_{2\Omega} = \frac{V_x}{2} = \frac{12.8}{2} = 6.4 \text{ A}$$

$$i_x + 0.6 = 6.4$$

$$i_x = 5.8 \text{ A}$$

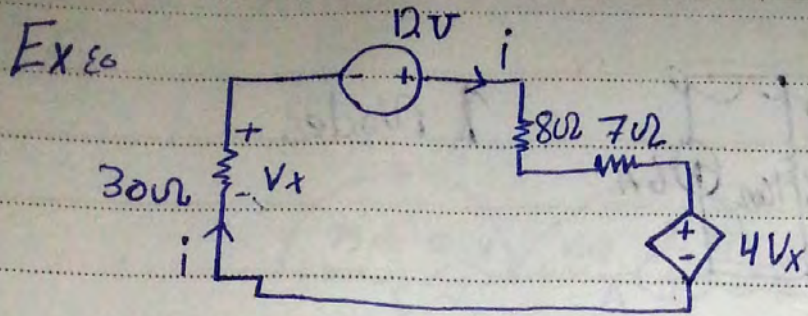

Find V_x

$$\text{KVL} = -V_x - 12 + 8i + 7i + 4V_x = 0 = \textcircled{1}$$

$$\Rightarrow +V_x = -30i = \textcircled{2}$$

$$+30i - 12 + 8i + 7i + 4(-30i) =$$

$$i = -0.16 \text{ A}$$

$$V_x = -30 \times 0.16 = 4.8 \text{ V}$$

* Calculate the absorbed power by each element

$$P_{\text{absorbed}} = I^2 R = (0.16)^2 \times 30 \Omega = 0.768 \text{ W}$$

30Ω

$$P_{\text{absorbed}} = 12 \times 0.16 = 1.92 \text{ W}$$

12V

$$P_{\text{absorbed}} = I^2 R = (0.16)^2 \times 8 = 0.2048 \text{ W}$$

8Ω

$$P_{\text{absorbed}} = I^2 R = 0.1792 \text{ W}$$

7Ω


$$P_{\text{absorbed}} = 4V_x \times i$$

$$(4V_x) = 4 \times (4.8) \times (-0.16) = -3.072 \text{ W}$$

↑ generated

$$\sum P_{\text{absorbed}} = \text{Zero}$$

Ex 60

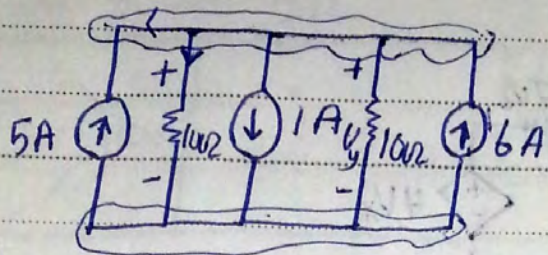Find U_y

$$\text{Kcl Node 1} \Rightarrow 5 + 6 = 1 + \frac{U_y}{10} + \frac{U_y}{10}$$

$$10 = 2 \frac{U_y}{10}$$



$$\frac{100}{2} = U_y$$

$$\sqrt{50} = U_y$$

$$P_{\text{generated}} = 250$$

$$P_{\text{absorbed}} = I \cdot V = 50 \cdot -5 = -250$$

Ex

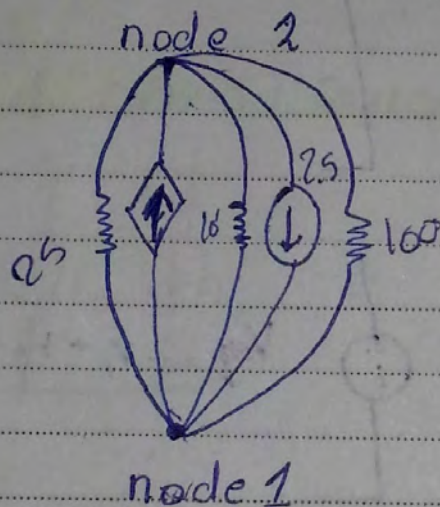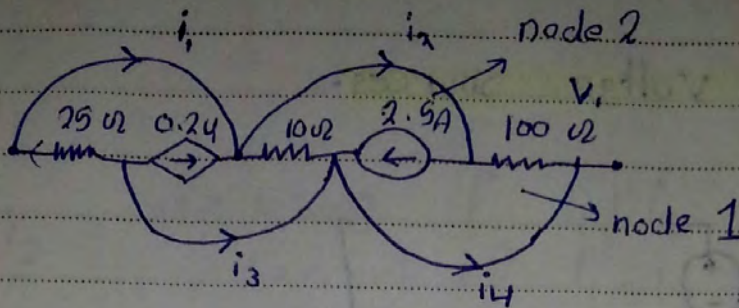

$$i_1 = -2A$$

$$i_2 = 3A$$

$$i_3 = -8A$$

$$i_4 = -0.5A$$

KCL \Rightarrow at Node 2

$$0.24 V_1 = \frac{V_1}{25} + \frac{V_1}{10} + 2.5 + \frac{V_1}{100}$$

$$\Rightarrow V_1 = 50V$$

$$i_1 = \frac{-V_1}{25} = \frac{-50}{25} = -2A$$

$$i_3 + 0.24 V_1 = i_1 = 0$$

$$i_4 = \frac{-V_1}{100} = -0.5A$$


$$i_3 = -8A$$

$$i_2 + i_4 = 2.5$$

$$i_4 = 3A$$

* series and parallel connections

=> series voltage sources.

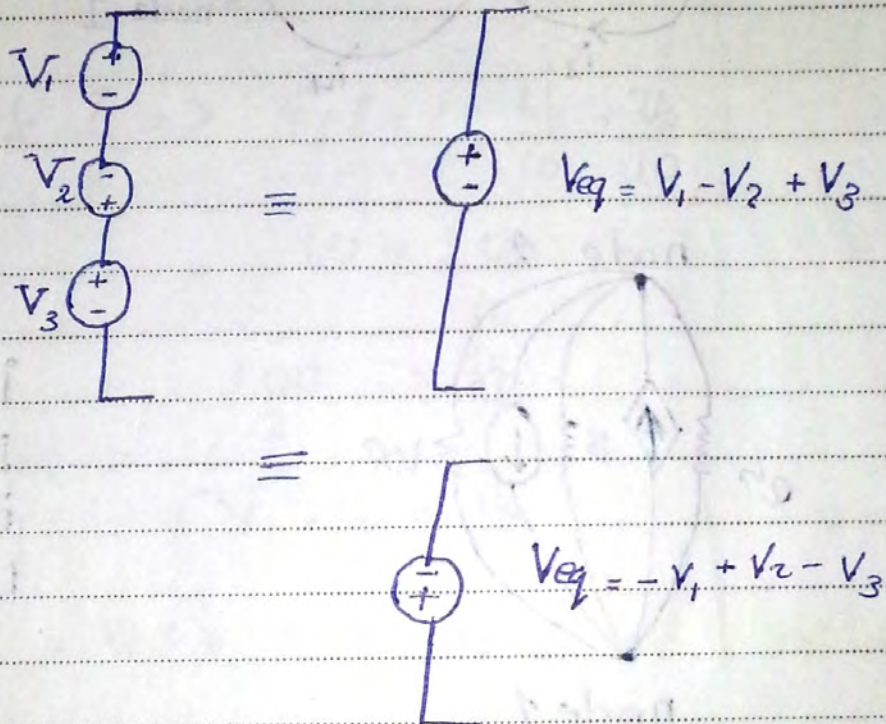


=> parallel voltage sources.

=> wrong connection if $V_1 \neq V_2$
but it is correct if $V_1 = V_2$

KVL: $-V_1 + V_2 = 0$

$V_1 = V_2$


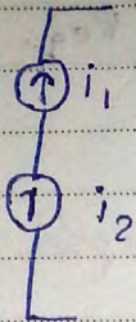
→ Series ~~current~~ ^{current} Source go



⇒ wrong if $i_1 \neq i_2$
 correct if $i_1 = i_2$

KCL ⇒ $i_2 = i_1$

⇒ parallel current sources go

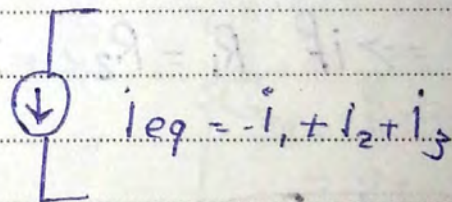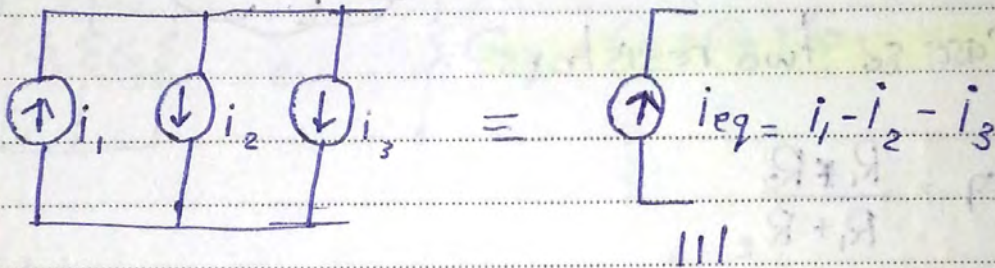

* series resistors go

$$\frac{R_1}{\text{---}} \frac{R_2}{\text{---}} \frac{R_3}{\text{---}} = \frac{R_{eq}}{\text{---}} \quad R_{eq} = R_1 + R_2 + R_3$$




$$\text{KVL: } -V_s + iR_1 + iR_2 + iR_3 = 0$$

$$i = \frac{V_s}{R_1 + R_2 + R_3}$$

$$-V_s + iR_{eq} = 0$$

$$i = \frac{V_s}{R_{eq}}$$



* parallel resistor

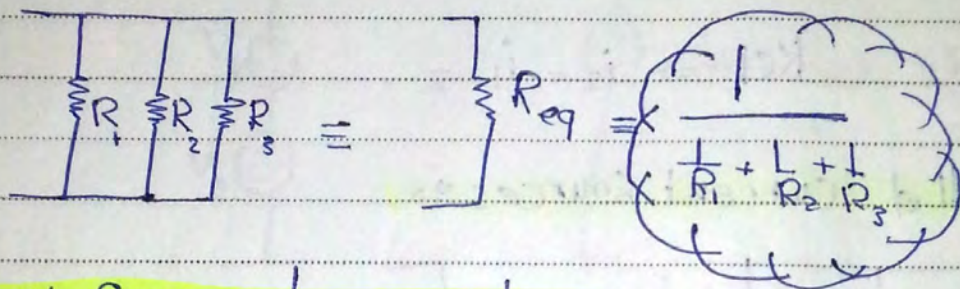

⇒ Special Case for two resistors

$$R_{eq} = \frac{R_1 * R_2}{R_1 + R_2}$$
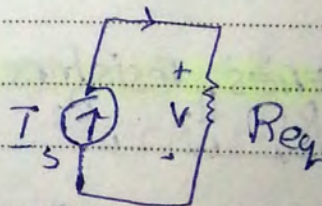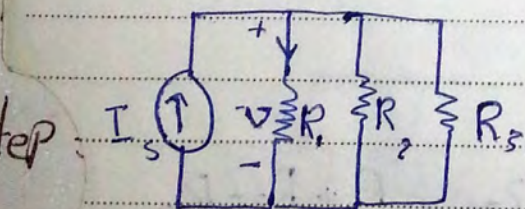
$$\Rightarrow \text{if } R_1 = R_2 \Rightarrow R_{eq} = \frac{R_1}{2}$$



$$\text{KCL: } I_s = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$I_s = \frac{V}{R_{eq}}$$

$$I_s = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

Subject:

25/9/20
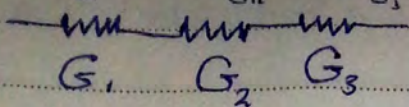
$$R_1 = \frac{1}{G_1} \quad R_2 = \frac{1}{G_2} \quad R_3 = \frac{1}{G_3}$$




(V)

(S)


$$= \frac{1}{\frac{1}{G_1} + \frac{1}{G_2} + \frac{1}{G_3}}$$

$$R_{eq} = \frac{1}{G_1} + \frac{1}{G_2} + \frac{1}{G_3}$$


$$G_{eq} = \frac{1}{\frac{1}{G_1} + \frac{1}{G_2} + \frac{1}{G_3}}$$

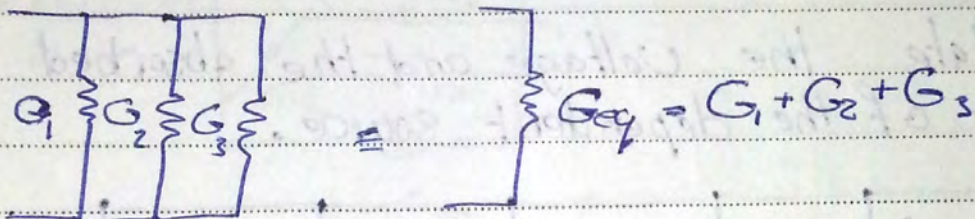


Ex 80

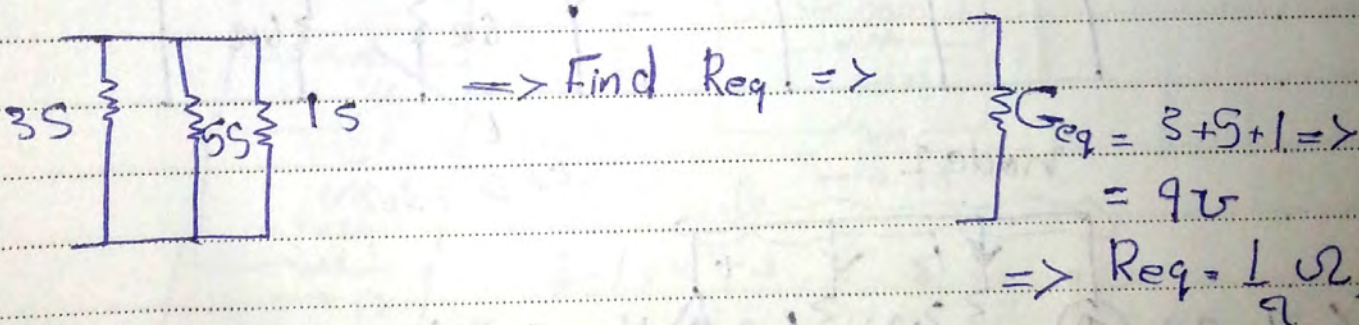

Ex 80

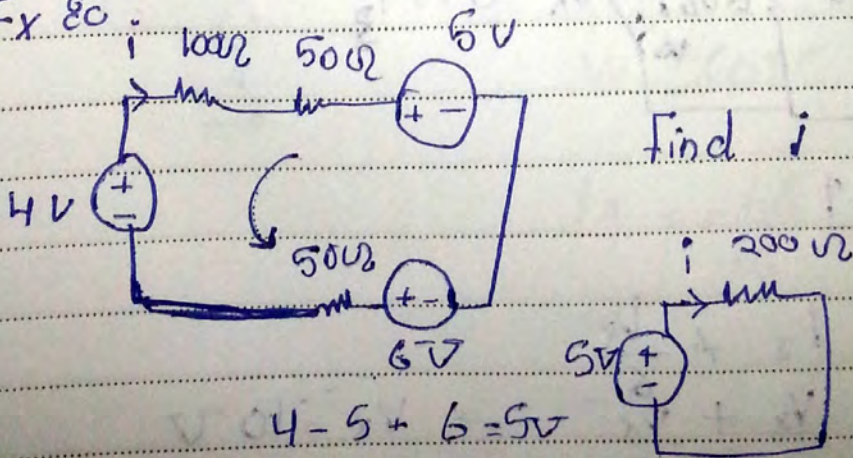


Ex-5

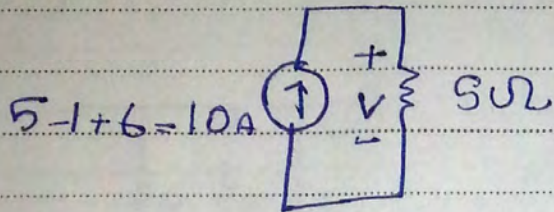

$$V = 10 \times 5 = 50V$$

Ex-6. Calculate the voltage and the absorbed power of the dependent source.

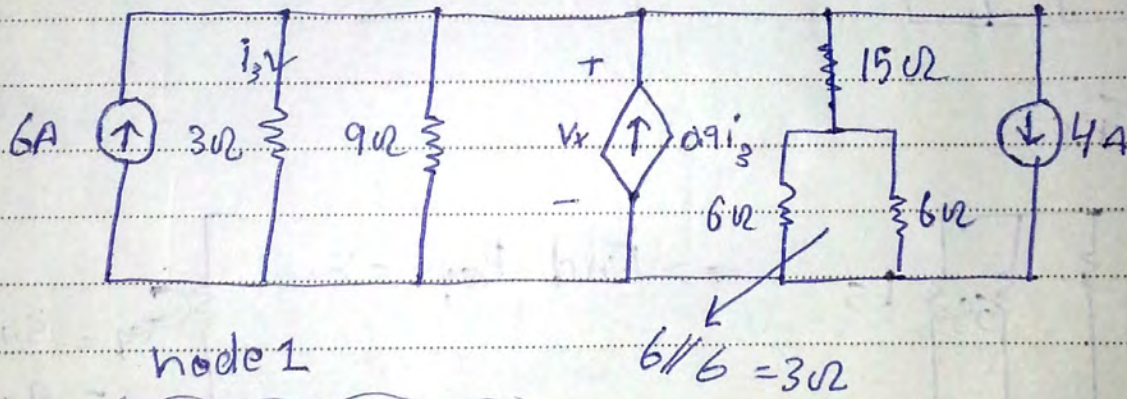

node 1



Kcl at Node 1


$$2 + 0.9 i_3 = i_3 + \frac{V_x}{3}$$

$$2 + \frac{0.9 \times V_x}{3} = \frac{V_x}{3} + \frac{V_x}{6} \Rightarrow V_x = 10V$$


$\Rightarrow P_{\text{absorbed}} = 0.9 \times i_3 \times V_x = -0.9 \times \frac{10}{3} \times 10 = -30 \text{ W}$

28/9/2014

Ex 80

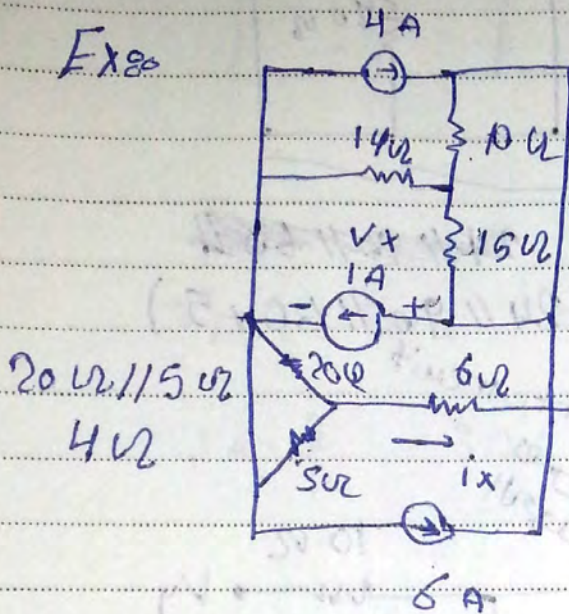

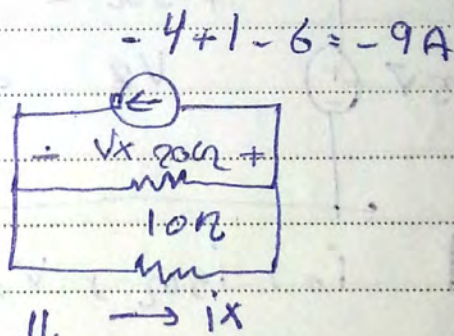$10\Omega // 15\Omega \Rightarrow 6\Omega$
 $6\Omega = 14\Omega \Rightarrow 20\Omega$



$-4 + 1 - 6 = -9 \text{ A}$

KCL: $-9 + \frac{V_x}{20} + \frac{V_x}{10} = 0$


$V_x = 60 \text{ V}$

$i_x = \frac{-60}{10} = -6 \text{ A}$

Subject:

28/9/2014

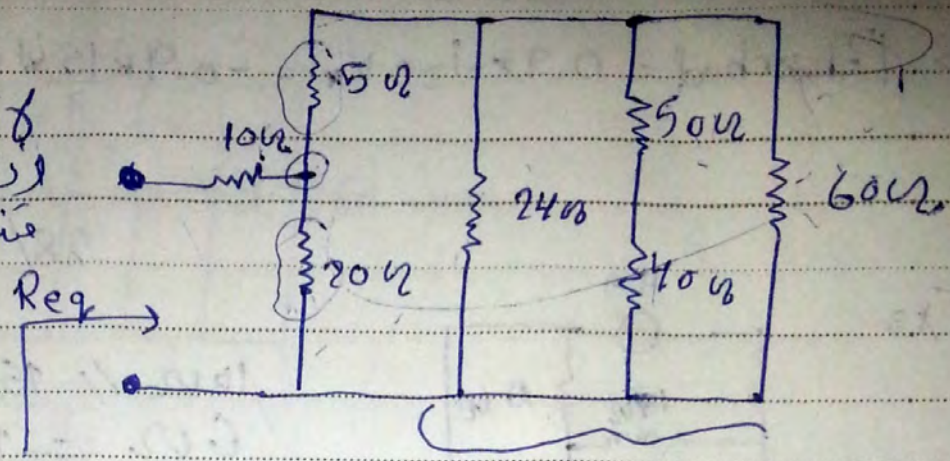
Ex 80
 إيجاد المقاومة
 المكافئة
 من اليسار



Find $R_{eq} = 10 + 20 \parallel (24 \parallel 40 \parallel 60 + 5)$


$= 9.85$ short circuit

Ex 80

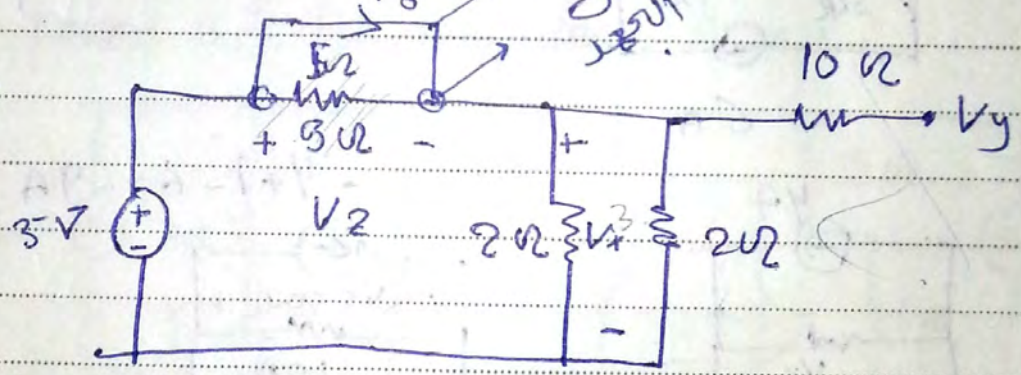

Find $i_0, i_{s2}, V_x, V_y, V_z$

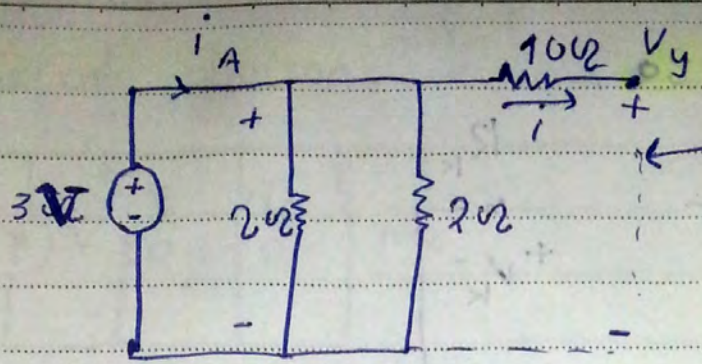
\Rightarrow short circuit $\Rightarrow i_{s2} = \text{Zero}$
 $V_z = \text{Zero}$
 $i_A = i_0$




لحل المسألة
بالتراكب
الخطي

$I_{10\Omega} = \text{Zero}$
 $V_{10\Omega} = \text{Zero} \Rightarrow V_y = V_x = 3V$

$i_A = \frac{3}{10} = 3A$

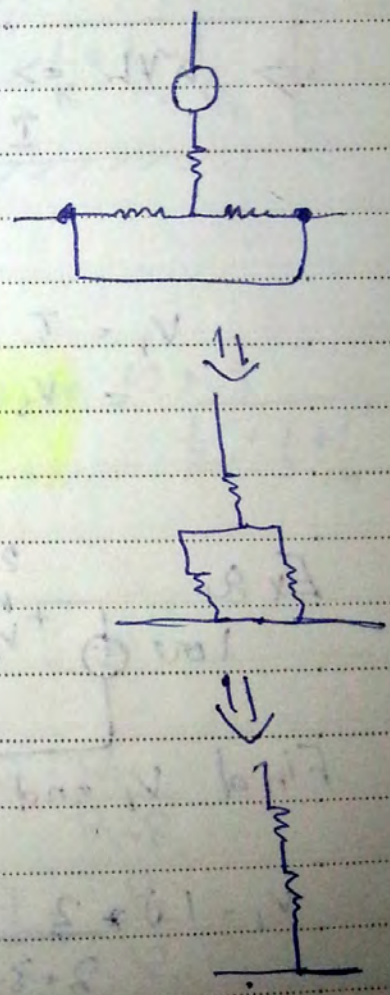

* Voltage Division eq.

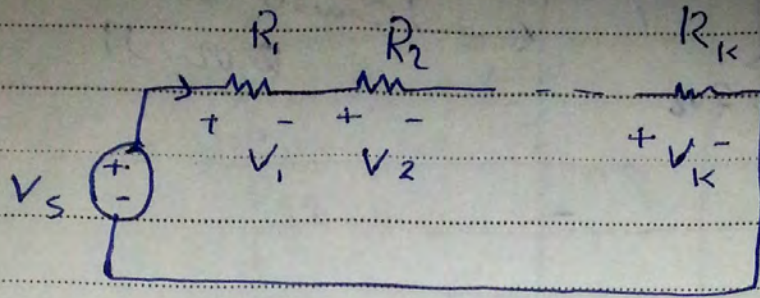


$$V_k = V_s \frac{R_k}{R_1 + R_2 + \dots + R_k}$$

$$\Rightarrow \text{KVL} \Rightarrow -V_s + IR_1 + IR_2 + \dots + IR_k = 0$$

$$I = \frac{V_s}{R_1 + R_2 + \dots + R_k}$$

$$V_1 = IR_1 = V_s \frac{R_1}{R_1 + R_2 + R_k}$$

Ex. 8.

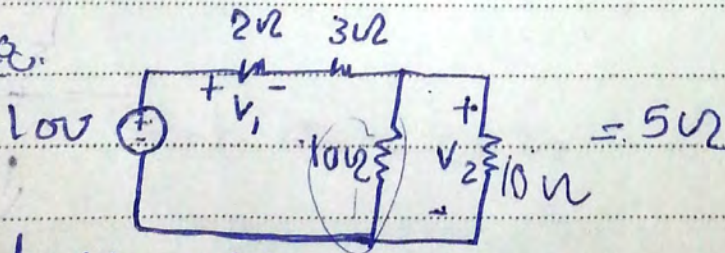


$$\frac{1}{\frac{1}{10} + \frac{2}{10}} = \frac{10}{3}$$

Find V_1 and V_2 ?

$$V_1 = 10 \times \frac{2}{2+3+5} = 2V$$

$$V_2 = 10 \times \frac{5}{2+3+5} = 9V$$

* Current division

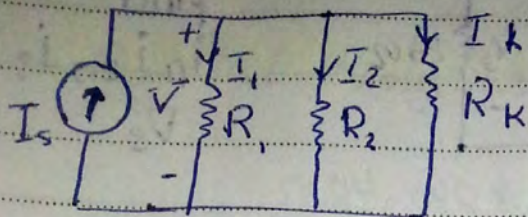


KCL \Rightarrow at node one $\Sigma i = 0$

$$I_s - \frac{V}{R_1} - \frac{V}{R_2} - \frac{V}{R_k} = 0$$


$$I_s = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_k} \right)$$

$$V = \frac{I_s}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_k} \right)}$$

$$I_k = \frac{V}{R_k}$$

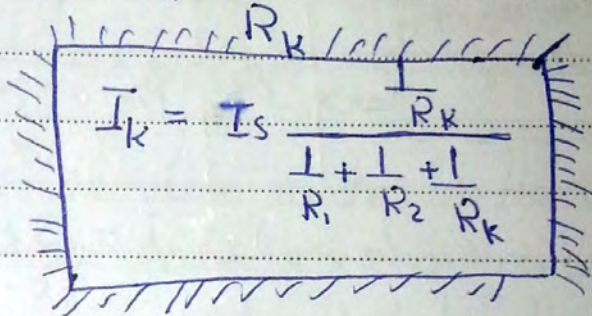


Ex

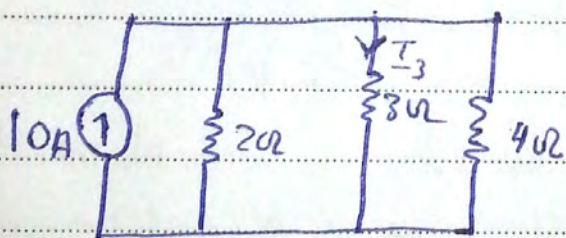

$$I_{3\Omega} = 10 \times \frac{\frac{1}{3}}{\frac{1}{2} + \frac{1}{3} + \frac{1}{4}}$$

* Special case & two resistors

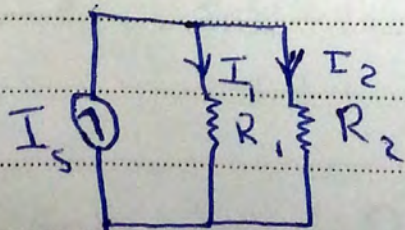

$$\Rightarrow I_1 = I_s \frac{R_2}{R_1 + R_2}$$

$$\Rightarrow I_2 = I_s \frac{R_1}{R_1 + R_2}$$


Driven RL and RC Circuit

Subject:


Series

30/9/2014

Ex

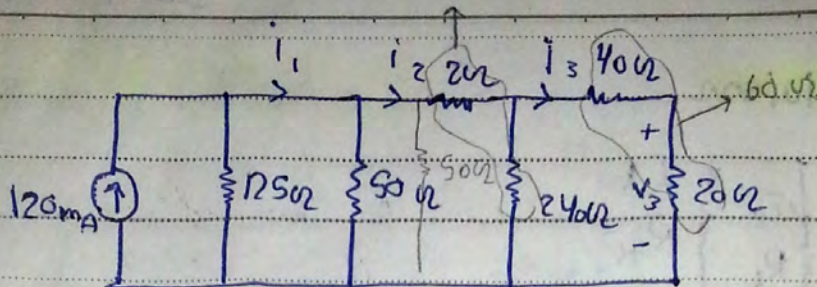

Find i_1, i_2, i_3 and V_3

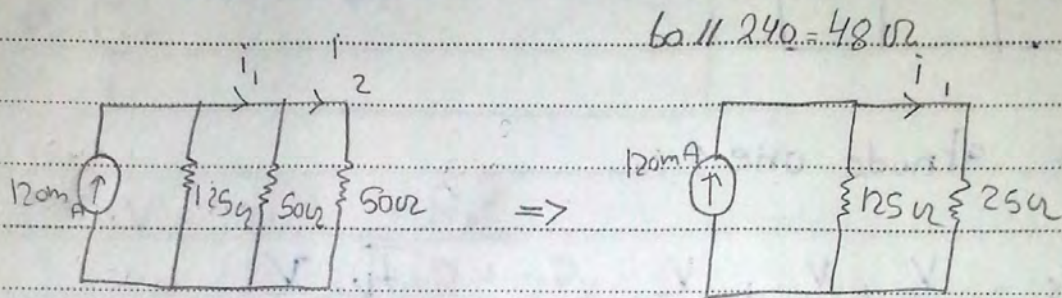

$$60 \parallel 240 = 48 \Omega$$

$$\Rightarrow i_1 = 120 \times \frac{125}{125+25} = 100 \text{ mA}$$

$$\Rightarrow i_2 = i_1 \times \frac{50}{50+50} = 50 \text{ mA}$$

$$\Rightarrow i_3 = i_2 \times \frac{240}{240+60} = 40 \text{ mA}$$


$$\Rightarrow V_3 = 20 \times i_3 = 0.8 \text{ V}$$

tep

* Chapter 4

* Nodal Analysis is to Find the voltage at each node in the circuit.

Ex 4.0

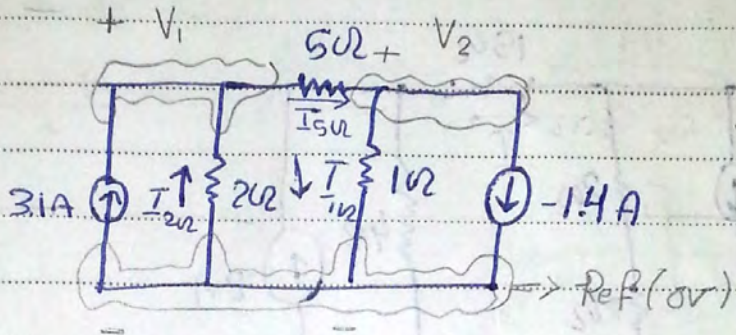


KCL at node 1
Node 2
node 1
node 2
branch

- Steps of solution
- 1- locate all the nodes in the circuit
 - 2- select one node as a reference node ($V=0$) (the node that has the highest number of connection)
 - 3- locate V_1, V_2, \dots

KCL at node 1 (Σ $i_{out} = 0$)
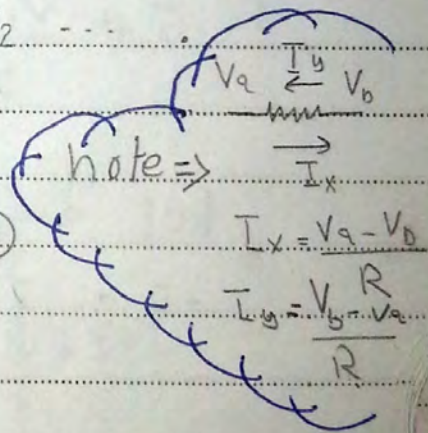
$$-3.1 + \frac{V_1 - 0}{2} + \frac{V_1 - V_2}{5} = 0 \quad \text{--- (1)}$$



$$I_x = \frac{V_a - V_b}{R}$$

$$I_y = \frac{V_b - V_a}{R}$$

KCL at node 2

$$-1.4 + \frac{V_2 - 0}{1} + \frac{V_2 - V_1}{5} = 0 \quad \text{--- (2)}$$

⇒ solve 1 and 2

$$V_1 = 5V \quad V_2 = 2V$$


$$I_{10\Omega} = \frac{V_2 - 0}{10} = 2 \text{ A}$$

$$I_{5\Omega} = \frac{V_1 - V_2}{5} = \frac{3}{5} \text{ A}$$

$$I_{2\Omega} = \frac{0 - V_1}{2} = -\frac{5}{2} \text{ A}$$

2.5 A
node 1

Ex. 4

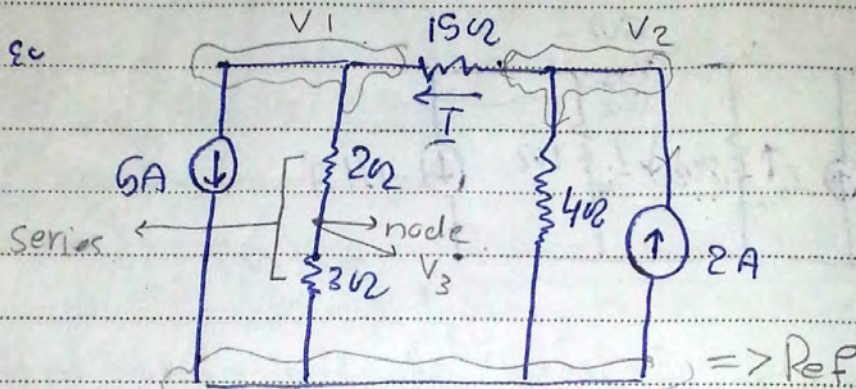

Use nodal analysis to find I & ϵ_0
KCL at node 1 & 2

$$5 \text{ A} + \frac{V_1 - 0}{5} + \frac{V_1 - V_2}{15} = 0 \quad \text{--- (1)}$$

KCL at node 2 & 3

$$-2 + \frac{V_2 - 0}{4} + \frac{V_2 - V_1}{15} = 0 \quad \text{--- (2)}$$

$$\Rightarrow V_1 = -\frac{145}{8} \text{ V}$$

$$\Rightarrow V_2 = \frac{5}{2} \text{ V}$$

$$\Rightarrow I = \frac{V_2 - V_1}{15} = 2.57 \text{ A}$$


$V \Rightarrow$ 1. voltage Division
2.

KCL at node 3:

$$\frac{V_3 - V_1}{2} + \frac{V_3 - 0}{3} = 0$$

$$V_3 = \frac{-145 \times 3}{8 + 5}$$

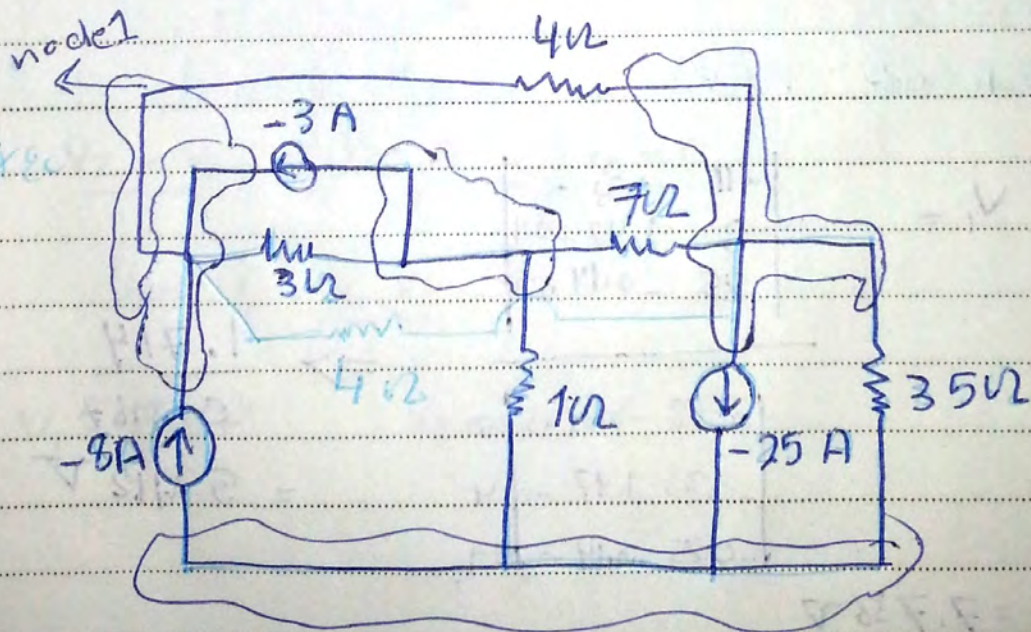CH2 Ex 20, 22, 26, 28, 30, 32, 34, 36, 38
 CH3 Ex 13, 14, 15, 17, 19, 21, 23, 25, 27, 29, 31, 33, 35, 37, 39
 42, 50, 52, 54, 56, 58, 60, 62, 64, 66, 68, 70, 72, 74, 76, 78, 80, 82, 84, 86, 88, 90, 92, 94, 96, 98, 100



Q1 apply the nodal analysis to analysis this circuit

KCL at node 1c

$$8 + 3 + \frac{V_1 - V_2}{3} + \frac{V_1 - V_3}{4} = 0 \quad \text{--- (1)}$$

KCL at node 2c

$$-3 + \frac{V_2 - V_1}{3} + \frac{V_2 - V_3}{7} + \frac{V_2 - 0}{1} = 0 \quad \text{--- (2)}$$

KCL at node 3c

$$-25 + \frac{V_3 - V_2}{7} + \frac{V_3 - V_2}{7} + \frac{V_3 - V_1}{4} + \frac{V_3 - 0}{5} = 0 \quad \text{--- (3)}$$

$$0.58 V_1 - 0.33 V_2 - 0.25 V_3 = -11 \quad \text{--- (1)}$$

$$-0.33 V_1 + 1.47 V_2 - 0.14 V_3 = 3 \quad \text{--- (2)}$$

$$-0.25 V_1 - 0.14 V_2 + 0.59 V_3 = 25 \quad \text{--- (3)}$$

By Cramer's
By ~~matrix~~ rule:

$$V_1 = \frac{\begin{vmatrix} -11 & -0.33 & -0.25 \\ 3 & 1.47 & -0.14 \\ 25 & -0.14 & 0.59 \end{vmatrix}}{\begin{vmatrix} 0.58 & -0.33 & -0.25 \\ -0.33 & 1.47 & -0.14 \\ -0.25 & -0.14 & 0.59 \end{vmatrix}}$$


$$\Rightarrow \frac{1.714}{0.3167} = 5.412 \text{ V}$$

$$V_2 = 7.736 \text{ V}$$

$$V_3 = 46.32 \text{ V}$$

$\frac{1}{\infty} \rightarrow$ Ref (0V)

Exa
5 mA
5V
 v_1

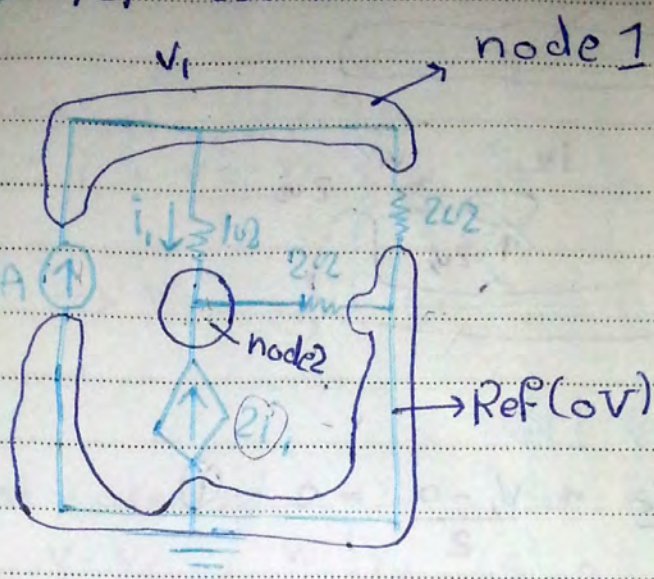

Q find i_1 using nodal analysis

* KCL at node 1

$$-5 + \frac{v_1 - v_2}{1} + \frac{v_1 - 0}{2} = 0 \quad \text{--- (1)}$$

*
پہلے سے
یہی ہے


* KCL at node 2

$$\frac{v_2 - v_1}{1} + \frac{v_2 - 0}{2} - 2i_1 = 0$$

but $i_1 = \frac{v_1 - v_2}{1}$

$$v_1 = \frac{70}{9} \text{ V} \quad , \quad v_2 = \frac{20}{3} \text{ V}$$

Ex 9

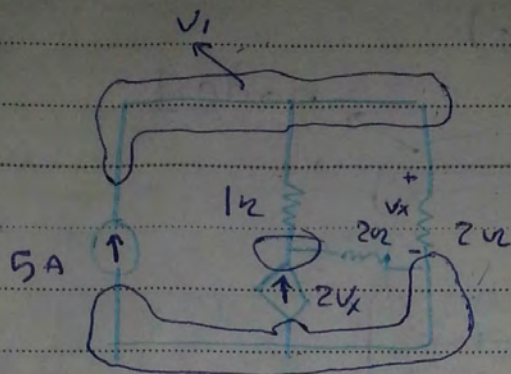

KCL at node 1 &

$$-5 + \frac{V_1 - V_2}{1} + \frac{V_1 - 0}{2} = 0 \quad \text{--- (1)}$$

KCL at node 2 &

$$-2V_x + \frac{V_2 - V_1}{1} + \frac{V_2 - 0}{2} = 0 \quad \text{--- (2)}$$

but $V_x = V_1 - 0$

$$V_1 = -10V$$

$$V_2 = -20V$$


\Rightarrow at node 1 ϵ $4 - 0 = 5$

$V_1 = 5V$

\Rightarrow at node 2 ϵ


$-2i_1 + \frac{V_2 - V_1}{1} + \frac{V_2 - 0}{2} = 0$

$\Rightarrow V_2 = 3.0/7 V$

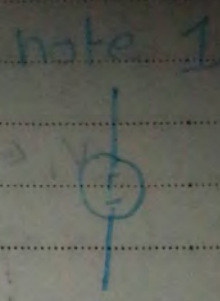


KCL at node 1 ϵ

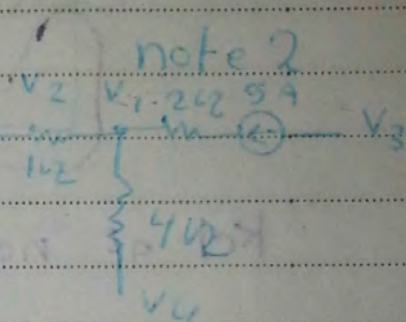
$\frac{V_1 - V_2}{1} + \frac{V_1 - V_4}{4} - 5 = 0$



KCL at node 1 ϵ

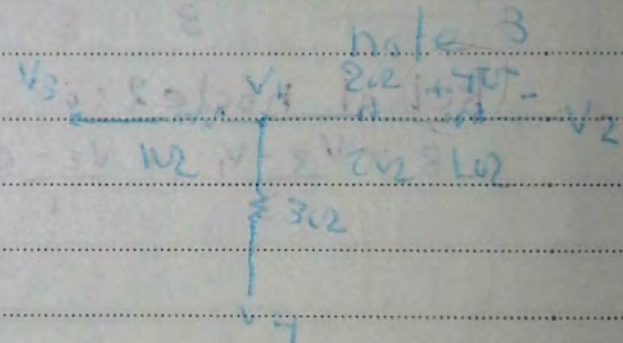$\frac{V_1 - V_3}{1} + \frac{V_1 - V_4}{3} + 4 = 0$



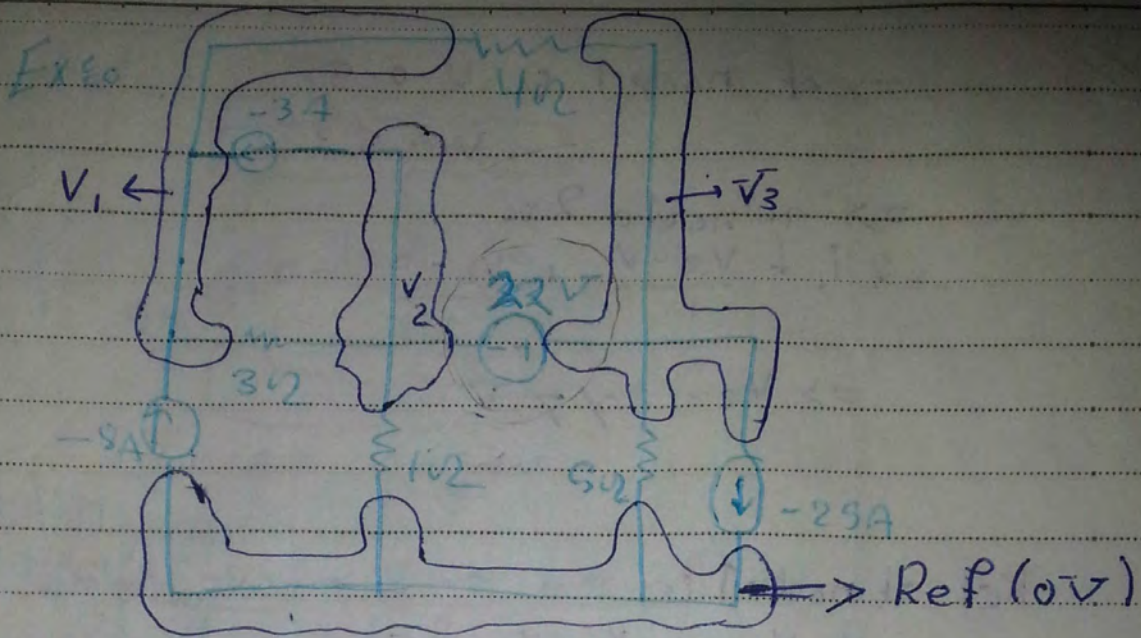

Kcl at node 1:


$$8 + \frac{V_1 - V_2}{3} + \frac{V_1 - V_3}{4} = 0 \quad \text{--- (1)}$$

Kcl at node 2:

$$-\frac{3 + V_3 - V_1}{3} + \frac{V_2 - 0}{1} + 22 \quad X$$

7th edition

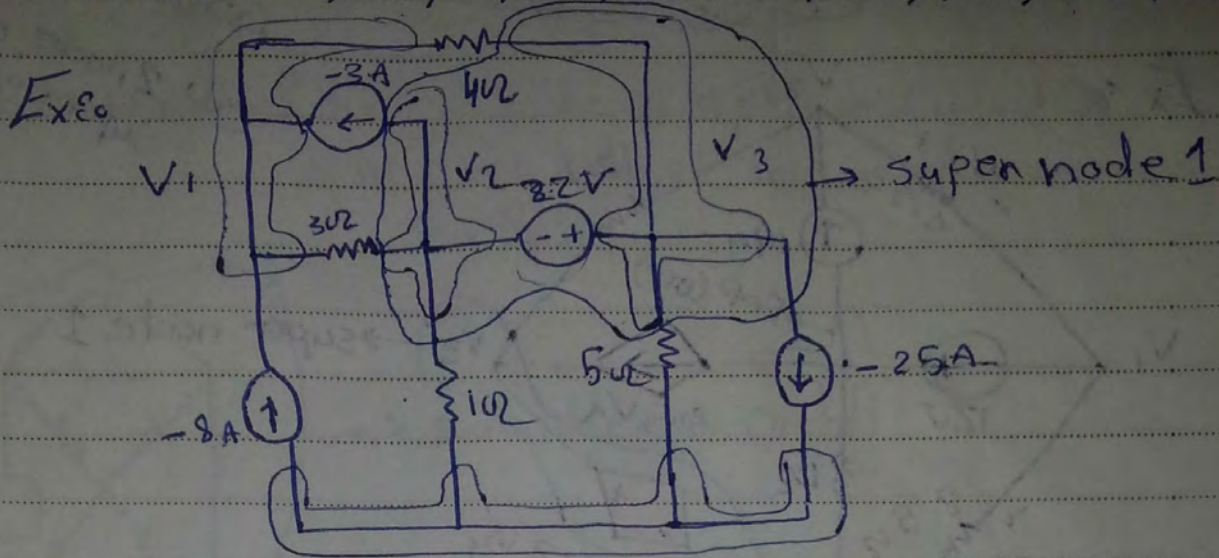Ch3: 56, 57, 59, 60, 67, 68, 69, 72, 74, 78, 80



* KCL at Supernode 1 &

$$-25 + \frac{V_3 - 0}{5} + \frac{V_2 - 0}{1} + \frac{V_2 - V_1}{3} - 3 + \frac{V_3 - V_1}{4} = 0 \quad \text{--- (2)}$$

* inside supernode 1 &

$$V_3 - V_1 = 22$$


$$V_1 = 1.071 \text{ V}$$

$$V_2 = 10.5 \text{ V}$$

$$V_3 = 32.5 \text{ V}$$

Super node

اینجا 2 nodes یک Supernode

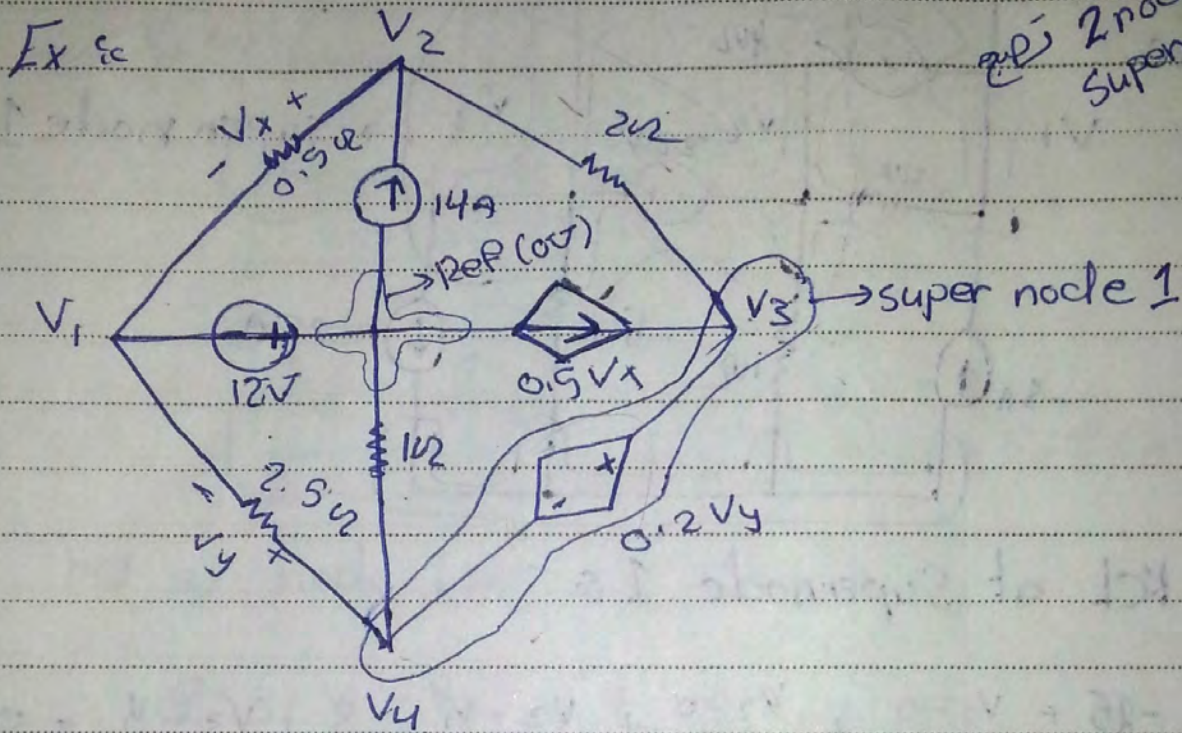

KCL at node 1

$$\Rightarrow V_1 = -12V$$

KCL at node 2

$$\Rightarrow -14 + \frac{V_2 - V_1}{2} + \frac{V_2 - V_3}{1} = 0$$

KCL at super node 1

$$\Rightarrow \frac{V_4 - V_1}{2.5} + \frac{V_4 - V_3}{1} + 0.5V_x + \frac{V_3 - V_2}{2} = 0$$

inside super node 1

$$V_3 - V_4 = 0.2V_y$$

$$V_1 = -12V$$

$$V_2 = -4V$$

$$V_3 = 10^{-14} V \approx 0$$

$$V_4 = -2V$$

but $V_x = V_2 - V_1 = V_2 + 12$

$V_y = V_4 - V_1 = V_4 + 12$

Mesh Analysis E.C.


⇒ it is used if the circuit is a planar circuit
 a) circuit that can be drawn on a plane surface)



⇒ non planar circuit

mesh

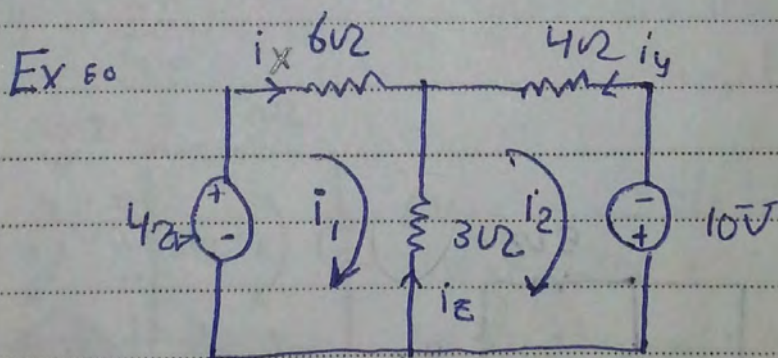∴ it is a loop that does not contain any other loop



رابطه
 مع
 الساعة

$$i_x = 6A$$

$$i_y = -4A$$

$$i_z = i_2 - i_1 = -2A$$

KVL For mesh 1 ∴


$$-42 + 6i_1 + 3(i_1 - i_2) = 0 \quad \text{--- (1)}$$

KVL For mesh 2 ∴

$$-10 + 3(i_2 - i_1) + 4i_2 = 0 \quad \text{--- (2)}$$

$$i_1 = 6A$$

$$i_2 = 4A$$

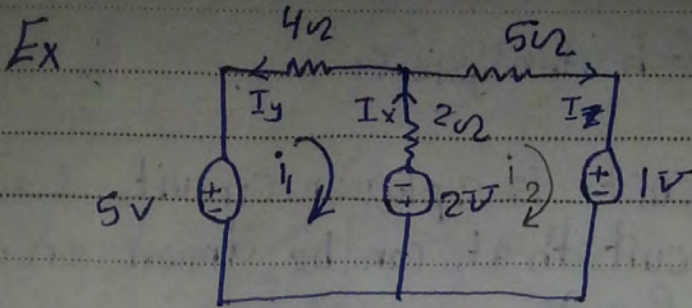

Find I_x, I_y, I_z
using mesh analysis &

\Rightarrow KVL of mesh 1:-

$$-5 + 4i_1 + 2(i_1 - i_2) - 2 = 0 \quad (1)$$

\Rightarrow KVL of mesh 2:-

$$5i_2 + 1 + 2 + 2(i_2 - i_1) = 0 \quad (2)$$


$$i_1 = \frac{43}{38} \text{ A}$$

$$i_2 = \frac{2}{19}$$

$$I_y = -i_1$$

$$I_x = i_2 - i_1$$

$$I_z = i_2$$

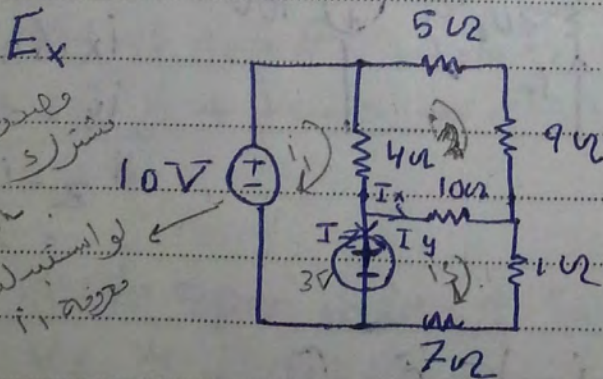

Super mesh
لو استعملنا
i1, i2, i3

\Rightarrow KVL at mesh 1 & 2

$$-10 + 4(i_1 - i_2) + 3 = 0 \quad (1)$$

\Rightarrow KVL of mesh 2 & 3

$$4(i_2 - i_1) + 5i_2 + 9i_2 + 10(i_2 - i_3) = 0 \quad (2)$$

\Rightarrow KVL of mesh 3 & 4

$$-3 + 10(i_3 - i_2) + i_3 + 7i_3 = 0 \quad (3)$$

$$i_1 = 2.22 \text{ A}$$


$$i_2 = 0.47 \text{ A}$$

$$i_3 = 0.427 \text{ A}$$

$$I_x = i_2 - i_1$$

$$I_y = i_3 - i_2$$

$$I_z = i_1 - i_3$$

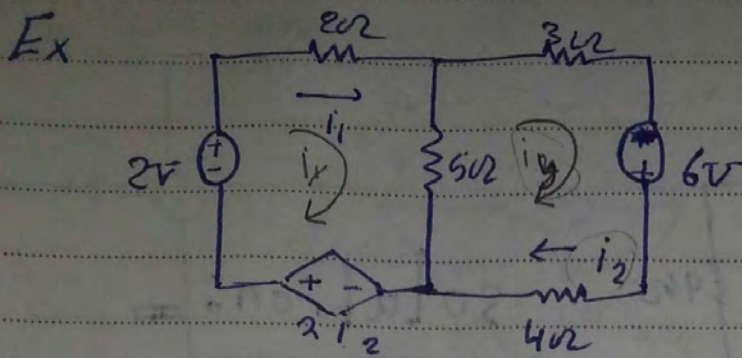

* Find i_1 & i_2 using the mesh analysis etc.

KVL at mesh 1 etc


$$-2 + 2i_1 + 5(i_1 - i_2) - 2i_2 = 0 \quad \text{--- (1)}$$

KVL at mesh 2 etc

$$3i_2 - 6 + 4i_2 + 5(i_2 - i_1) = 0 \quad \text{--- (2)}$$

$$i_1 = i_x = \frac{66}{44} \text{ A}$$

$$i_2 = i_y = \frac{52}{44} \text{ A}$$

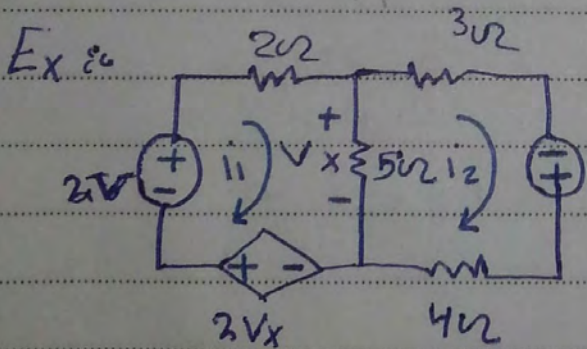


solution :-

KVL $\Rightarrow -2V + 2i_1 + 5(i_1 - i_2) - 2V_{x1} = 0$

KVL $\Rightarrow 3i_2 - 6 + 4i_2 + 5(i_2 - i_1) = 0$

but $V_x = 5(i_1 - i_2)$

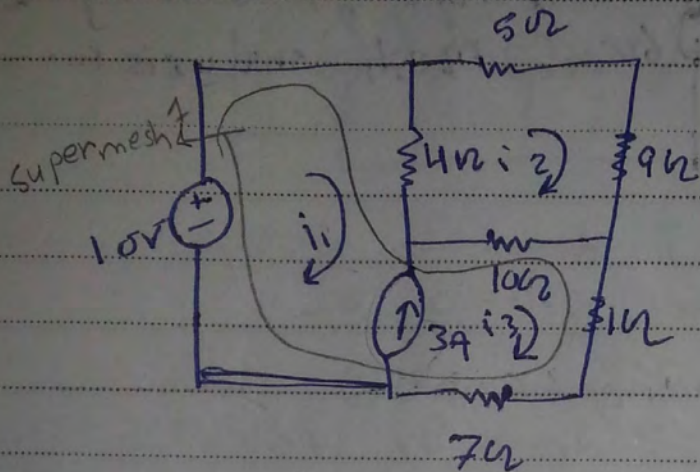Ex 6: Super mesh

solution: \Rightarrow $\begin{matrix} \curvearrowright \text{JoJo} \\ 3\text{A} \end{matrix}$

\Rightarrow mesh 2 cc

$$5i_2 + 9i_2 + 10(i_2 - i_3) + 4(i_2 - i_1) = 0 \quad \text{--- (1)}$$

\Rightarrow Super mesh 1 cc

$$-10 + 4(i_1 - i_2) + 10(i_3 - i_2) + 7i_3 + 7i_3 = 0 \quad \text{--- (2)}$$


\Rightarrow inside Supermesh cc

$$i_3 - i_1 = 3 \quad \text{--- (3)}$$

$$i_1 = -\frac{29}{15} \text{ A}$$

$$i_2 = \frac{11}{105} \text{ A}$$

$$i_3 = \frac{16}{15} \text{ A}$$

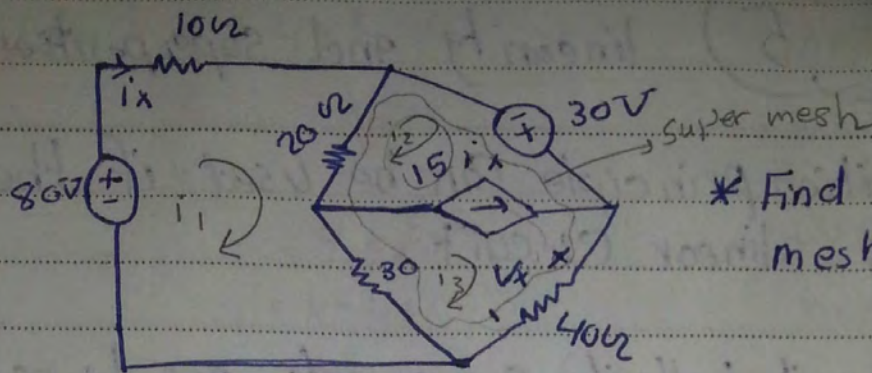

* Find i_x and V_x using mesh analysis etc.

mesh 1 eq

$$-80 + 10i_1 + 20(i_1 - i_2) + 30(i_1 - i_3) = 0 \quad \text{--- (1)}$$

KVL For Supermesh 1 eq

$$-30 + 40i_3 + 30(i_3 - i_1) + 20(i_2 - i_1) = 0 \quad \text{--- (2)}$$

inside supermesh 1,

$$i_3 + i_2 = 15i_x$$

$$i_1 = i_x = \frac{87}{149} \text{ A}$$

$$i_2 = \frac{-917}{149} \text{ A}$$

$$i_3 = \frac{388}{149} \text{ A}$$


$$V_x = 40i_3 = 104.16 \text{ V}$$

* Chapter 5 linearity and superposition.


- Superposition principle can be used if the circuit is a linear circuit.

* linear circuit: all its components are linear element.


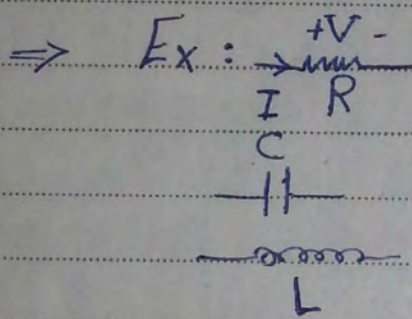
* linear element: the relationship between voltage and current is linear.



$$\Rightarrow I = \frac{V}{R}$$

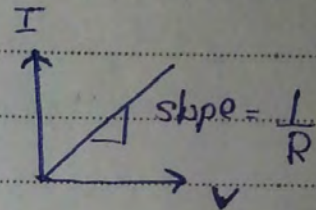

⇒ non-linear elements

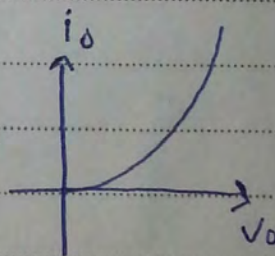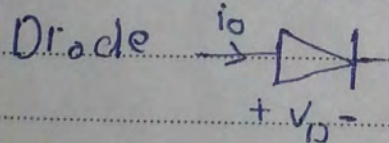

* To check any relationship

⇒ Methode 1^o

$y = 3x \Rightarrow x = kx \rightarrow \text{if } y_{\text{new}} = ky$, then it is linear relationship.

$$y_{\text{new}} = 3(kx)$$

$$y_{\text{new}} = k \cdot 3x$$

$$y_{\text{new}} = ky$$

Exéc $y = 4X^2$

$X_{new} = kX$

$y_{new} = 4X_{new}^2$
 $= 4 \times k^2 X^2$
 $= k^2 4 X^2$

$y_{new} = k^2 y$ non-linear

methode 2 :

$y = 4X^2$

$y = 4(X_1 + X_2)^2$

$y = 4(X_1^2 + 2X_1X_2 + X_2^2)$

non-linear

Methode 2 :

Exéc $y = 3X$

$X_{new} = X_1 + X_2$


$y_{new} = 3X_{new}$
 $= 3(X_1 + X_2)$

$y_{new} = 3X_1 + 3X_2 \Rightarrow y_{new} = y_1 + y_2$ linear


Exéc



$i_2 = k i_x$ (linear)

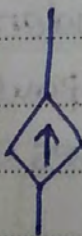


$i_2 = k i_x^2$ (non-linear)

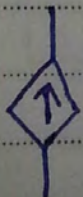


$i_2 = 2i_x V_x$ (non-linear)


Ex :

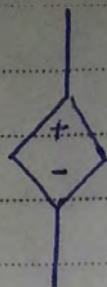

$$V_2 = 3i_x \quad (\text{linear})$$

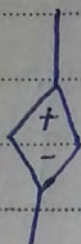
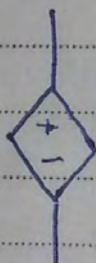
$$V_2 = 7i_x - 5V_x \quad (\text{linear})$$






$$V_2 = V_x^2 + 1 \quad (\text{non-linear})$$


* Super position \Rightarrow Can be used to Find Current or Voltage but not power.

* Super position technique \Rightarrow The response in a linear circuit having more than one independent source can be obtained by adding the responses caused by the separate independent sources acting alone.

Ex 6c

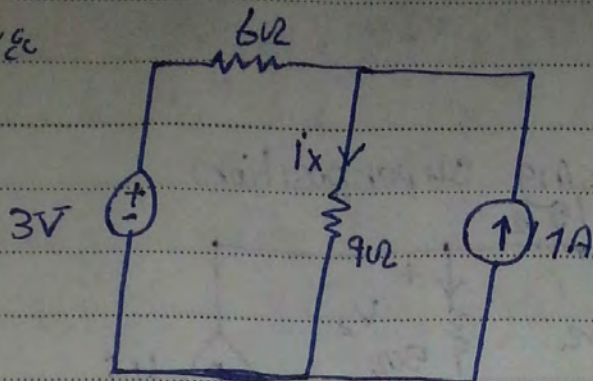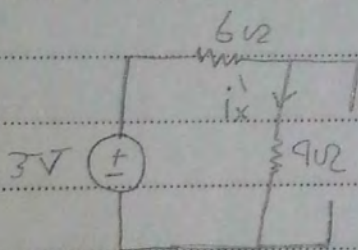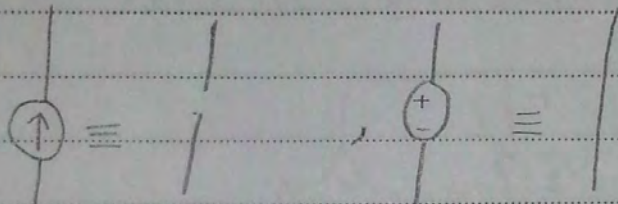a) Find i_x using superpositionb) Find the absorbed power by 9Ω $\Rightarrow i_x$ due to 3V only (i_x')Kill all other independent source \Rightarrow 

$$i_x' = \frac{3}{15} = 0.2 \text{ A}$$

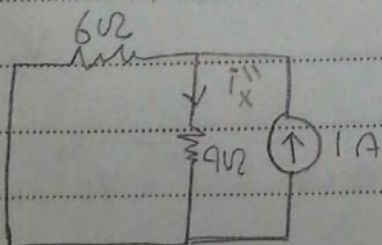 $\Rightarrow i_x$ due to 1A only (i_x'')Kill all other independent source \Rightarrow 

$$i_x'' = 1 \times \frac{6}{15} = 0.4 \text{ A}$$


$$i_x = i_x' + i_x'' = 0.2 + 0.4 = 0.6 \text{ A}$$

Subject:


14/10/2014

⑥ $P_{\text{absorbed}} = i_x^2 * 9 = (0.16)^2 * 9 = 3.24W$

Ex. find V_1 and V_2 using superposition

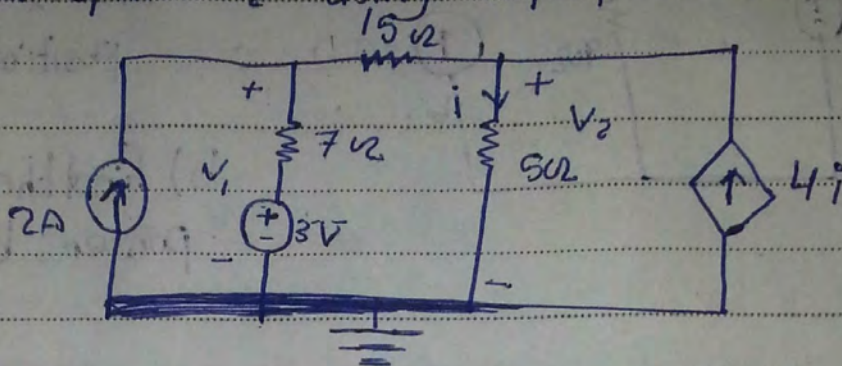

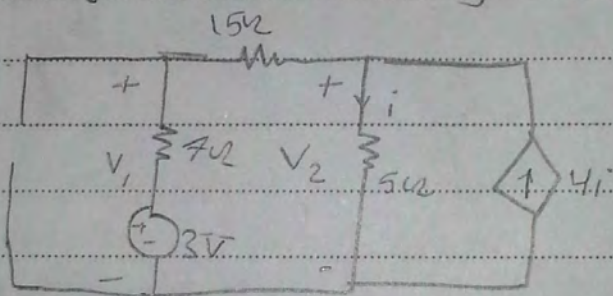$\Rightarrow V_1$ and V_2 due to 3V only (V_1', V_2')



Kcl at node 1 :-

$$\frac{V_1' - 3}{7} + \frac{V_1' - V_2'}{15} = 0 \quad \text{--- (1)}$$

Kcl at node 2


$$\frac{V_2' - 0}{5} + \frac{V_2' - V_1'}{15} - 4i = 0 \quad \text{--- (2)}$$

Solve 1 & 2

$$V_1' = 1.967V$$

$$V_2' = -0.245V$$

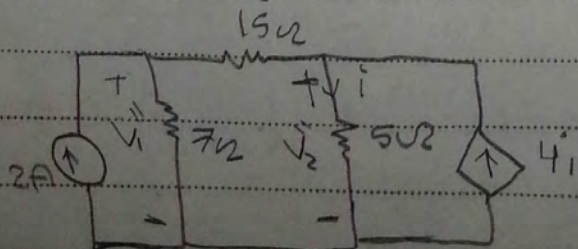$\Rightarrow V_1$ and V_2 due to 2A only (V_1'', V_2'')



Subject:

14/10/2014

=> KCL at node 1:

$$-2 + \frac{V_1'' - 0}{7} + \frac{V_1'' - V_2''}{15} = 0 \quad \text{--- (1)}$$

=> KCL at node 2:

$$\frac{V_2'' - 0}{5} + \frac{V_2'' - V_1''}{15} = 0 \quad \text{--- (2)}$$

$$V_1'' = 9.18 \text{ V}$$

$$V_2'' = -1.148$$


$$V_1 = V_1' + V_1''$$

$$= 11.197 \text{ V}$$

$$V_2 = V_2' + V_2''$$

$$= -1.394 \text{ V}$$

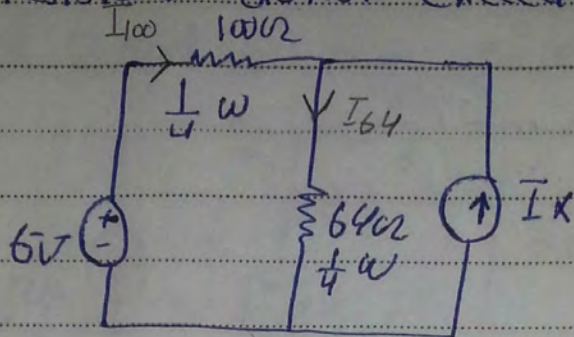Ex^o Find the maximum current I_x such that the resistors do not exceed their power rating



Sol^o

\Rightarrow Power rating : maximum absorbed power

$$P_{\max}(100\Omega) = \frac{1}{4} = W$$

$$(I_{100})_{\max}^2 R = \frac{1}{4}$$

$$\frac{I^2 * 100}{(100)_{\max}} = \frac{1}{4}$$

$$\sqrt{\frac{I^2}{(100)_{\max}}} = \sqrt{\frac{1}{400}} \Rightarrow I_{(100)_{\max}} = 50 \text{ mA}$$

$$P_{\max}(64\Omega) = \frac{1}{4} = W$$

$$\frac{I^2}{64} = \frac{1}{64 * 4} = \frac{I_{64}}{64} = 62.5 \text{ mA}$$

$$I_{(100\Omega)} \leq I_{100(\text{Max})}$$

$$I'_{100} + I'' \leq 50 \text{ mA}$$

\downarrow \downarrow

due to 6V only

$$\frac{6}{164} + (-I_x \frac{64}{64+100}) \leq 50 \text{ mA}$$


$$\Rightarrow \boxed{I_x \geq -34.36 \text{ mA}}$$

$$I_{64} < I_{64(\text{max})}$$

$$I'_{64} + I''_{64} \leq 62.5 \text{ mA}$$

$$\frac{6}{64+100} + I_x \frac{100}{100+164} \leq 62.5 \text{ mA}$$


$$I_x \leq 42.49 \text{ mA}$$

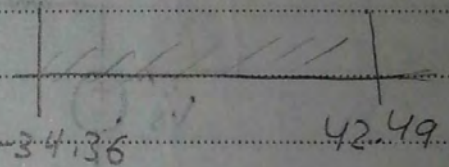


~~~~~ (First Exam)

\* practical and ideal sources 30

- Ideal voltage source

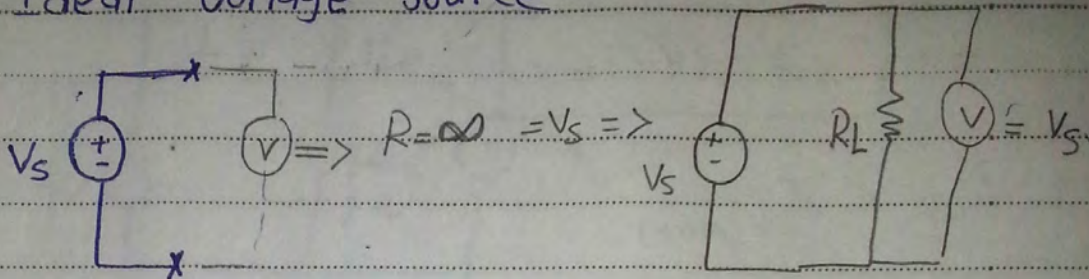


- practical voltage source

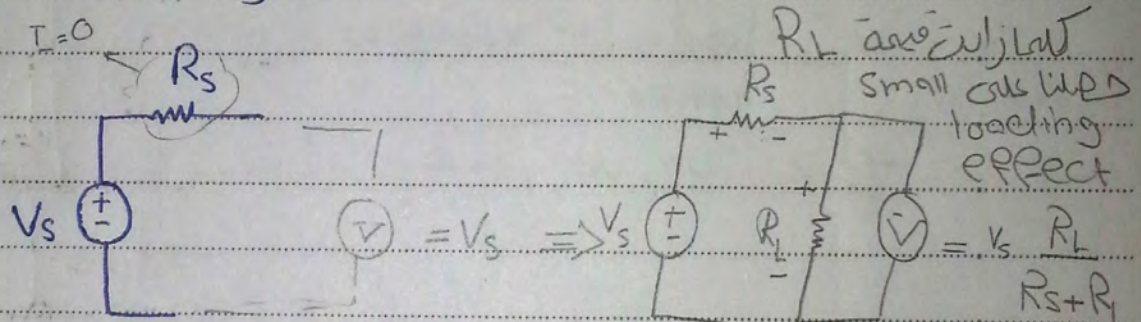


$R_L$   $\rightarrow$   $\infty$   $\rightarrow$   $V = V_s$   
 Small  $R_L$   $\rightarrow$   $V < V_s$   
 loading effect


loading effect

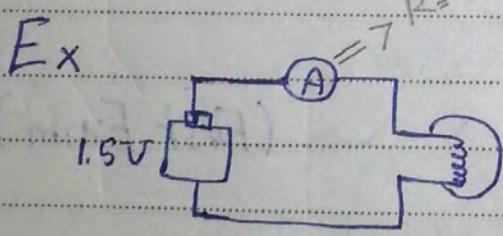

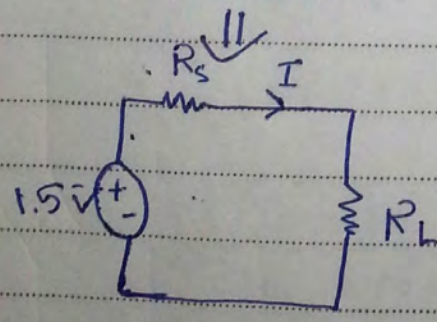
as  $R_L \uparrow =$  small loading effect







\* Ideal Current Source  $I_s$

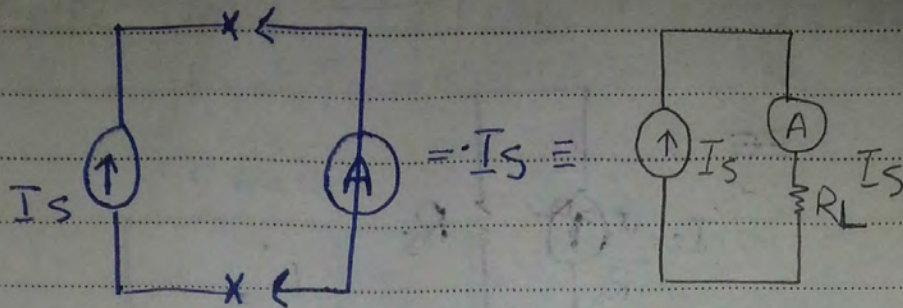




\* Practical Current Source  $I_s$ :

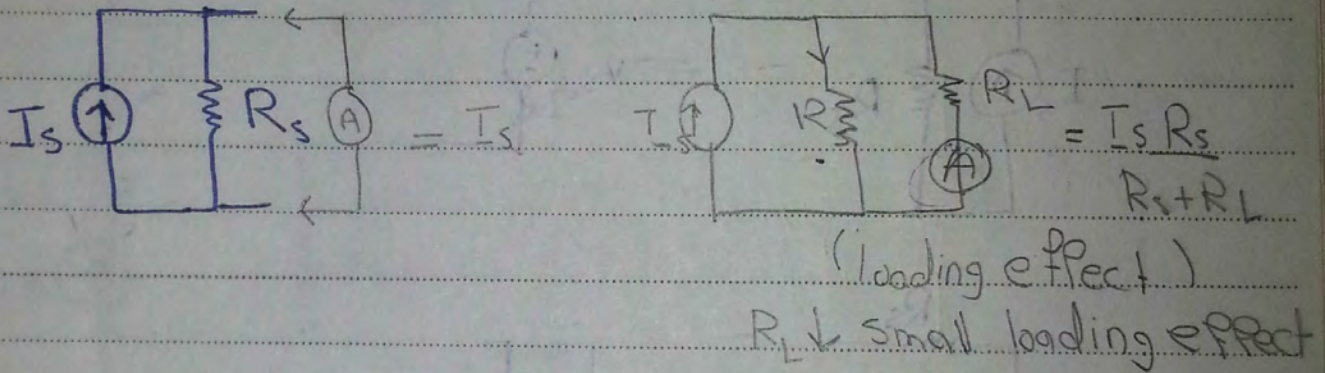

## Source Transformation 33

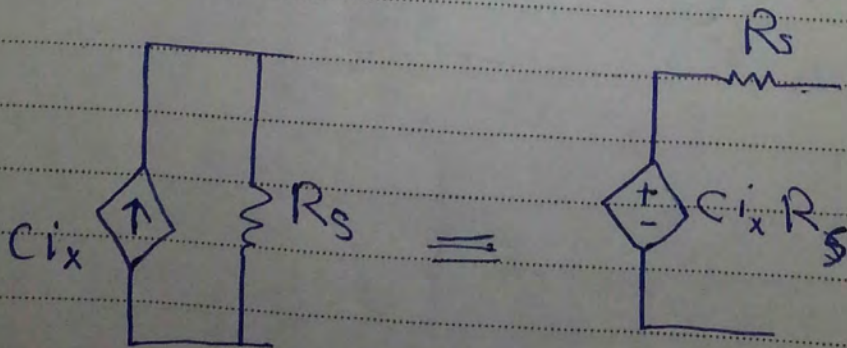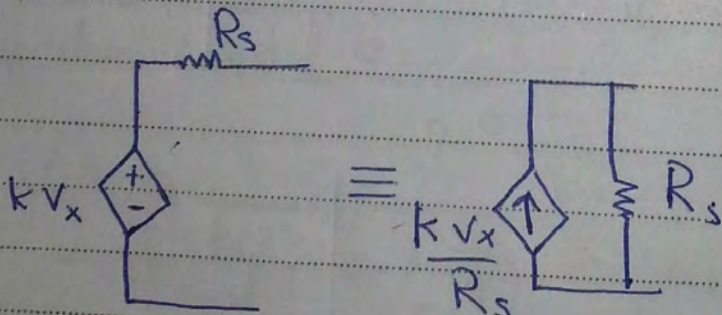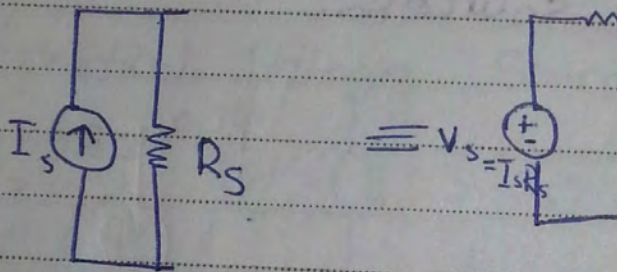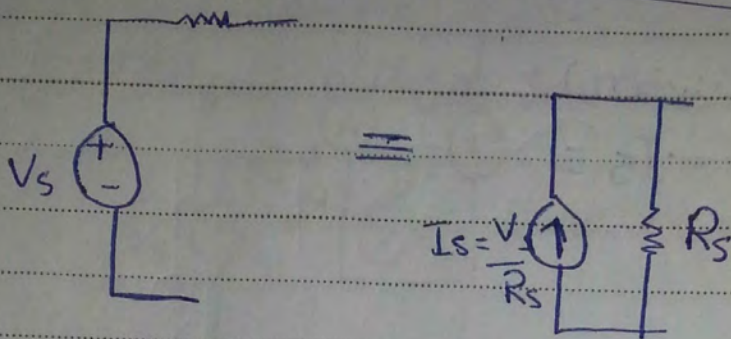

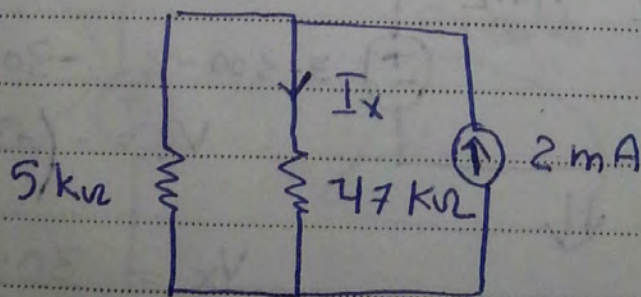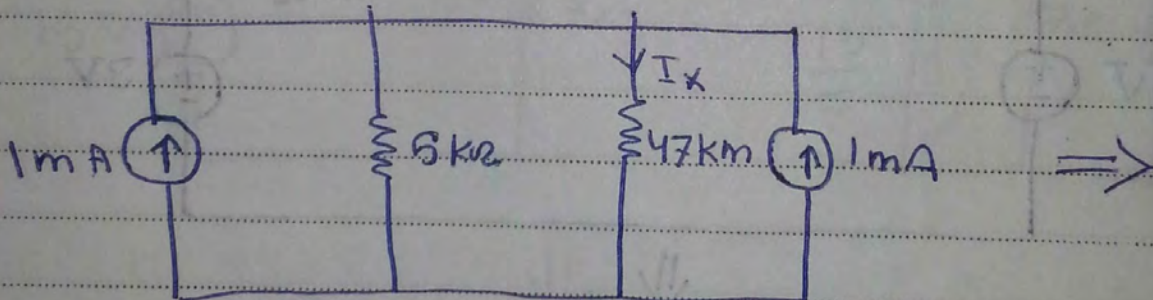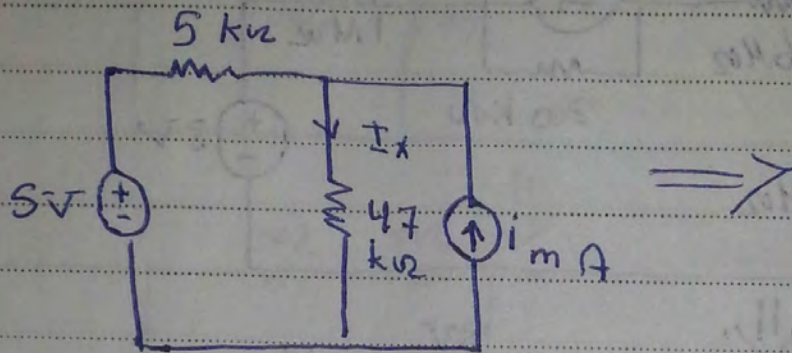Ex 8c Find  $I_x$  (use in your solution source transformation)






$$I_x = 2 \times \frac{5}{5+47}$$

$$= 192 \mu\text{A}$$



Source transformation 30

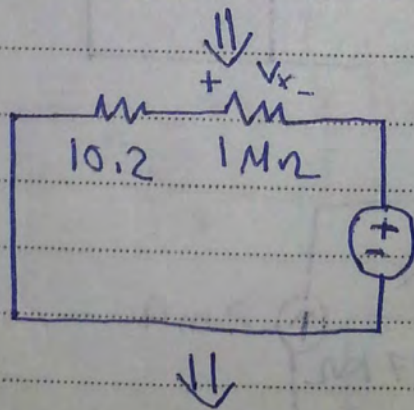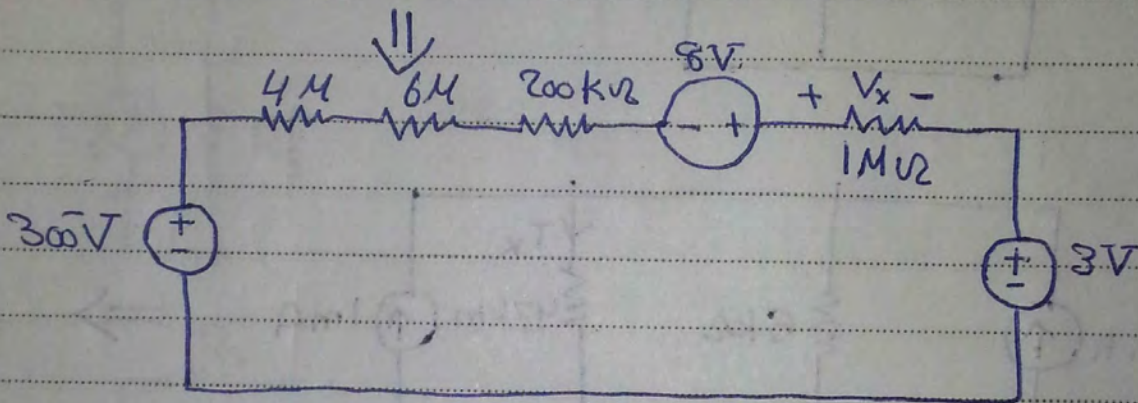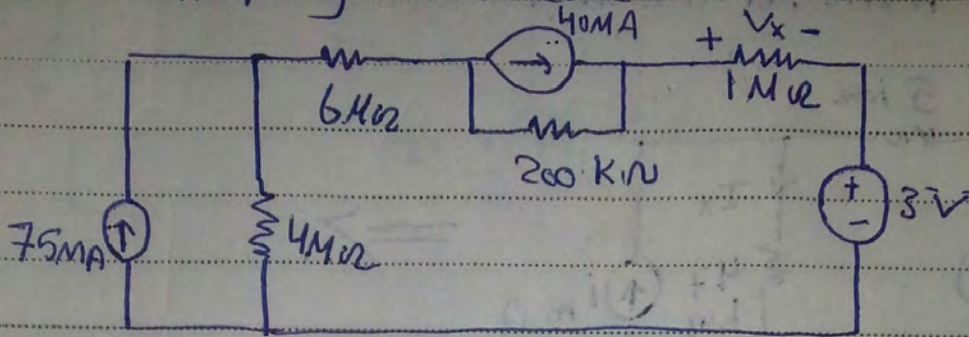
Ex: simplify this circuit and find  $V_x$



$$3 - 300 - 8 = -305 \text{ V}$$




$$V_x = - \left( -305 \times \frac{1}{1 + 10.2} \right)$$

$$V_x = \frac{305}{11.2} = 27.25 \text{ V}$$

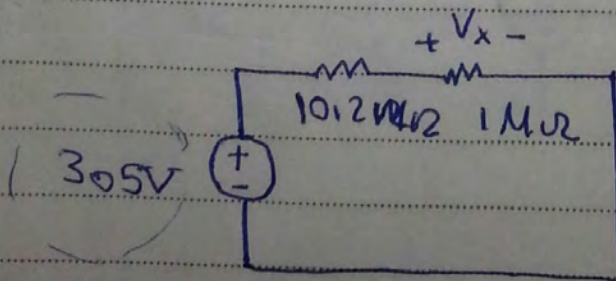

Ex. 8c

Find  $I_x$

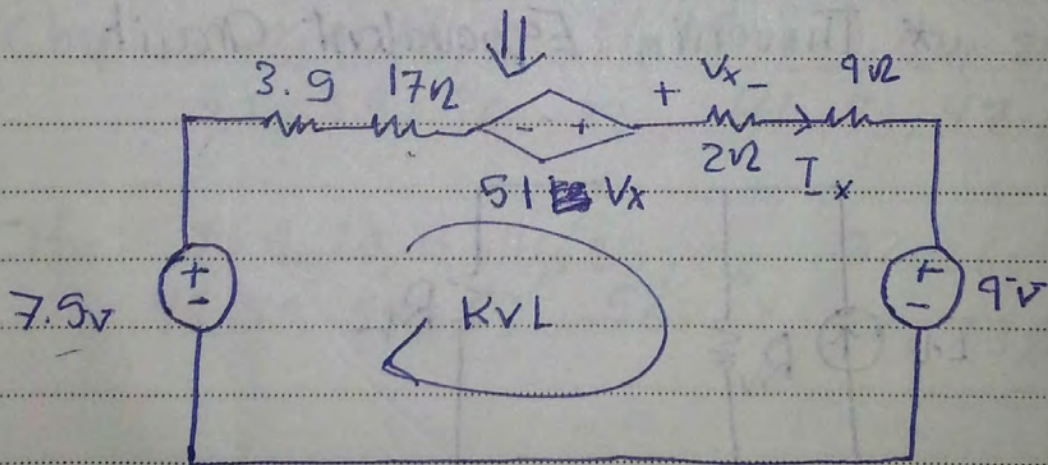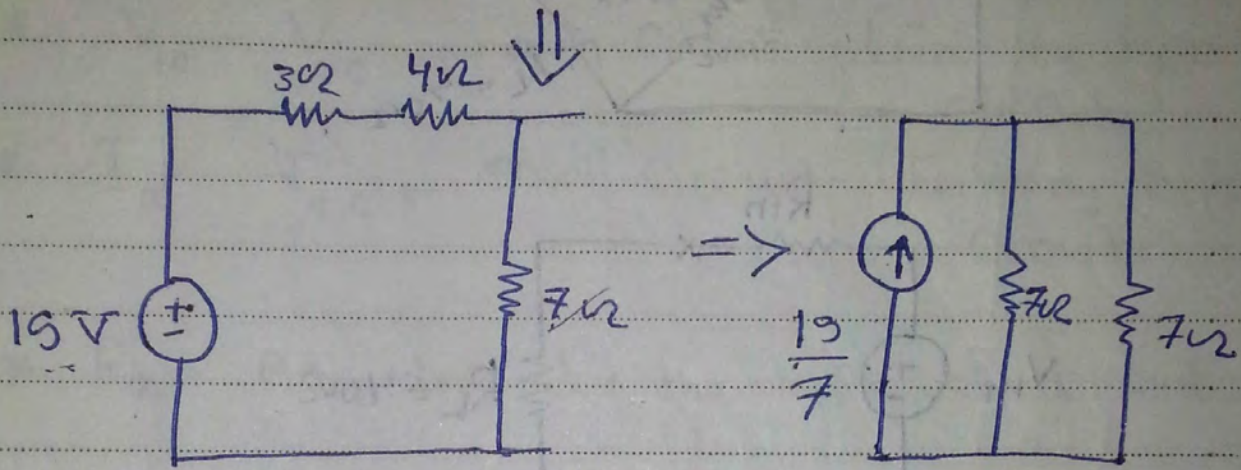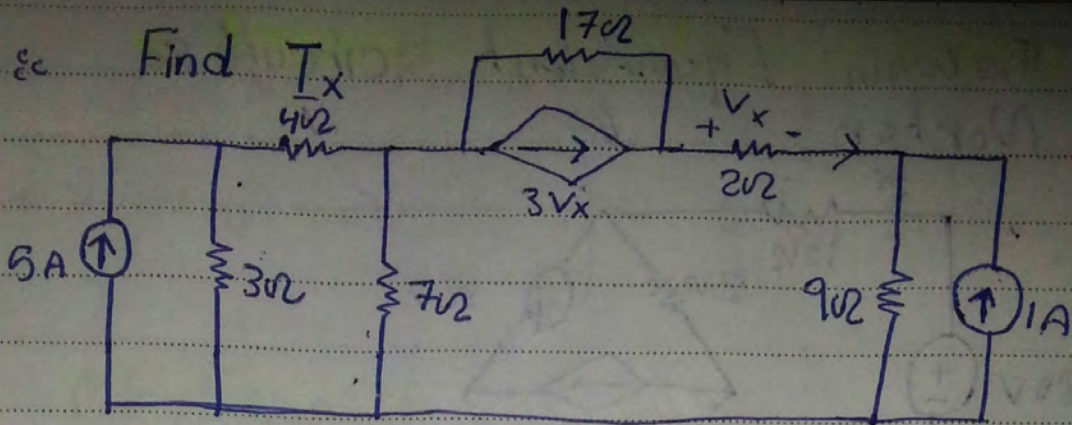



$$-7.5 + 31.5 I_x - 51 V_x + 9 = 0$$

$$\Rightarrow I_x = 21.276 \text{ mA}$$


$V = 30 \times 17$

\* Thevenin Equivalent circuit &c.

\* Norton " " "

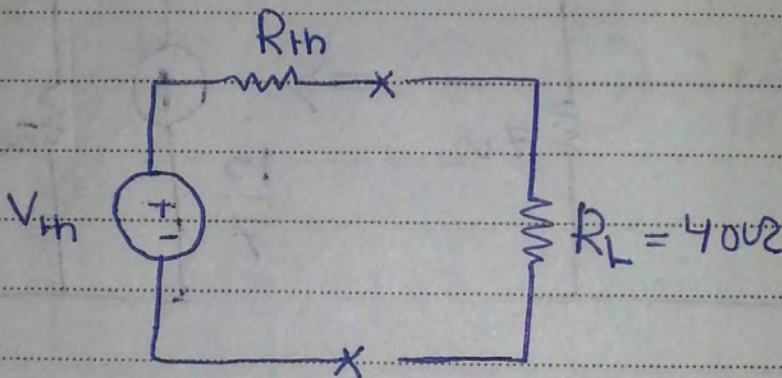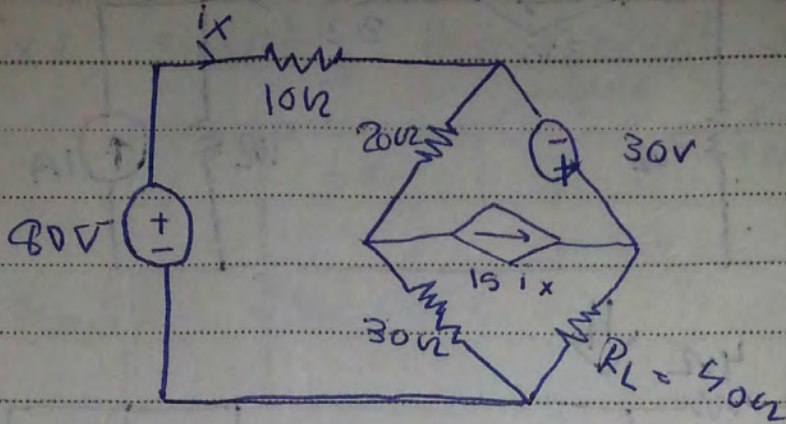

\* Thevenin Equivalent Circuit

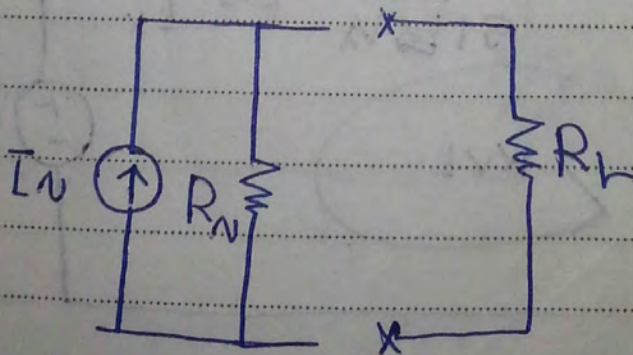


\* norton equivalent circuit




# Rev

Ex & Superposition

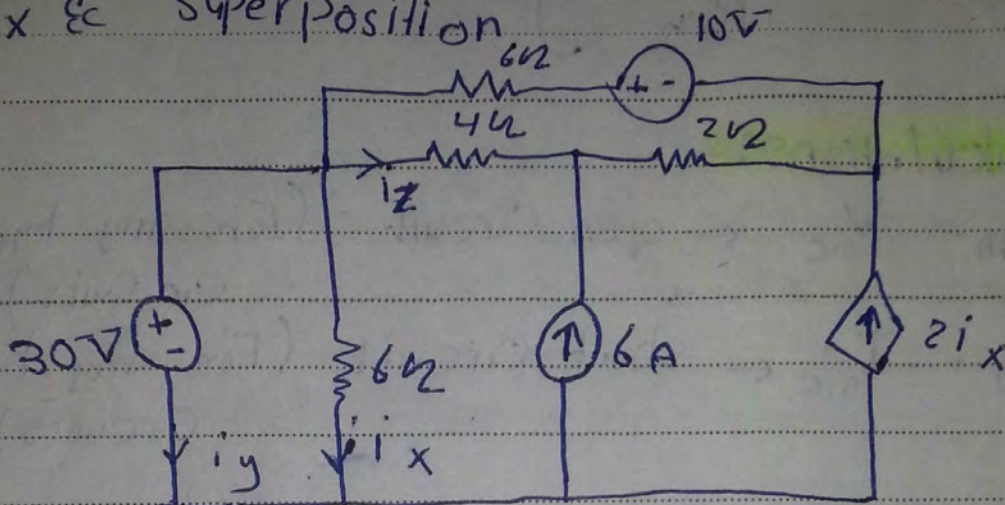

Find  $i_x$ ,  $i_y$ ,  $i_z$

due to 30V only

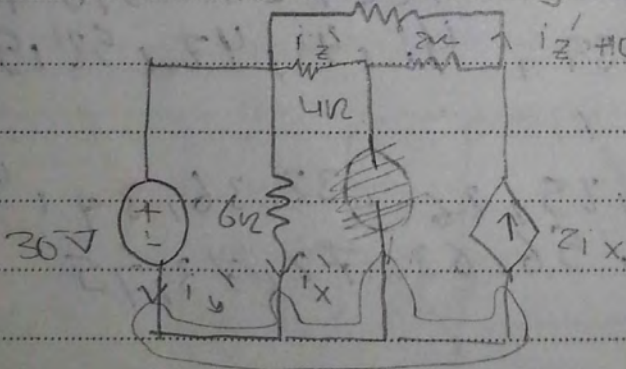

$$i_x = \frac{30}{6} = 5A$$

KCL

$$i_y + i_x = 2i_x \Rightarrow i_y = 5A$$

KVL

$$4i'_z + 2i'_z + 6(i'_z + 10) = 0$$


$$12i'_z = -60$$

$$i'_z = -5A$$

Subject: .....

21/10/2014

due to 10 V

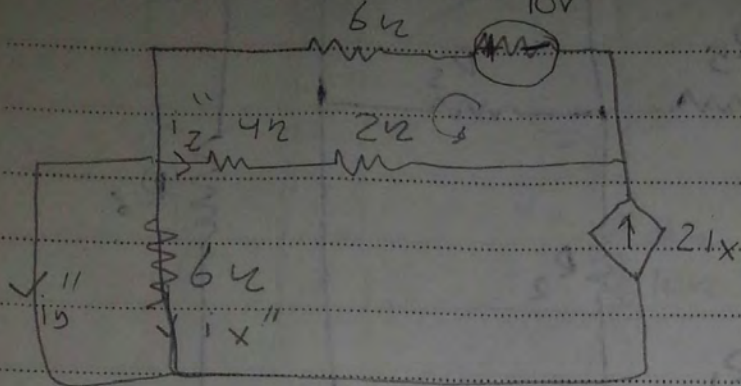

$$i_x'' = \frac{0}{6} = 0 \text{ A} \Rightarrow 2i_x'' = 0$$

$$\text{KCL } I_y'' + i_x'' = 2i_x''$$


$$I_y'' = 0 \text{ A}$$

$$4I_z'' + 2i_x'' - 10 + 6i_2'' = 0$$

$$12i_z'' = 10$$

$$i_z'' = \frac{10}{12}$$

due to 6 A

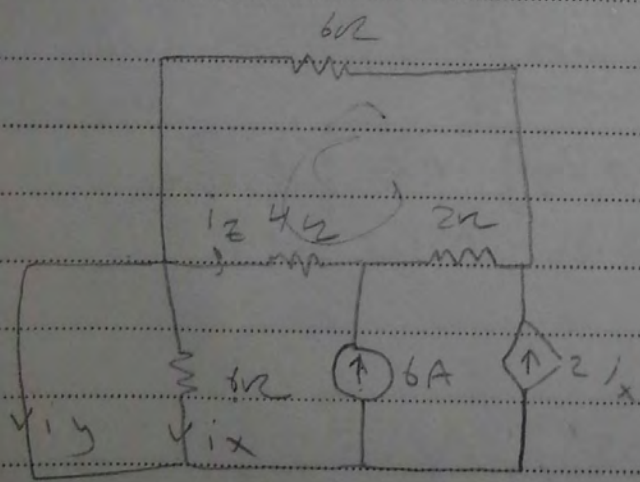

$$i_x''' = 0$$

KCL

$$i_y''' + i_x''' = 6 + 2i_x'''$$


$$i_y''' = 6 \text{ A}$$

$$\text{KV} = 4i_z''' + 2(6 + i_z''') + 6(6 + i_z''') = 0$$


$$i_z''' = \frac{-48}{12} \text{ A}$$

Excc

Req L

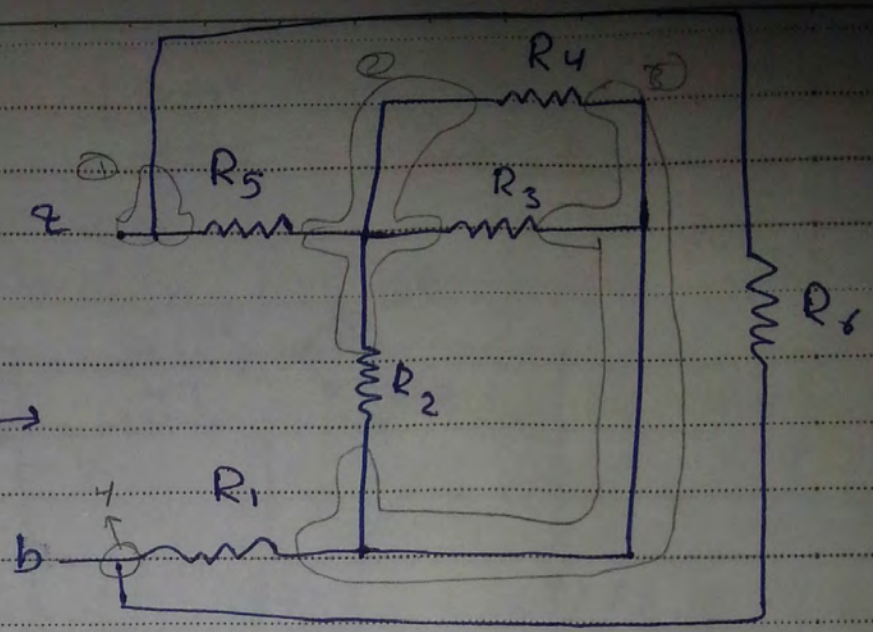

$$Req = 2$$

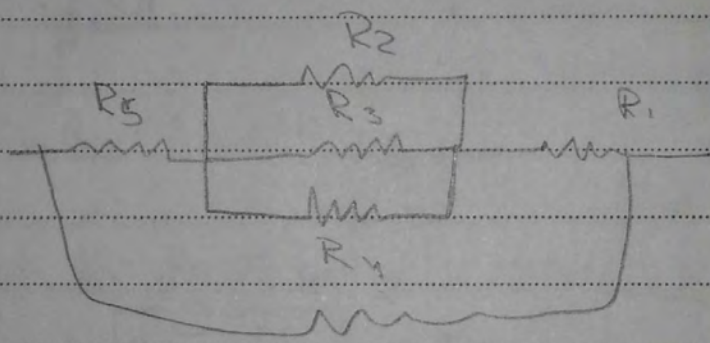


$$Req = [R_5 + [R_2 \parallel R_3 \parallel R_4] + R_1] \parallel R_6$$

ep =

Subject: .....

21 / 10 / 2014

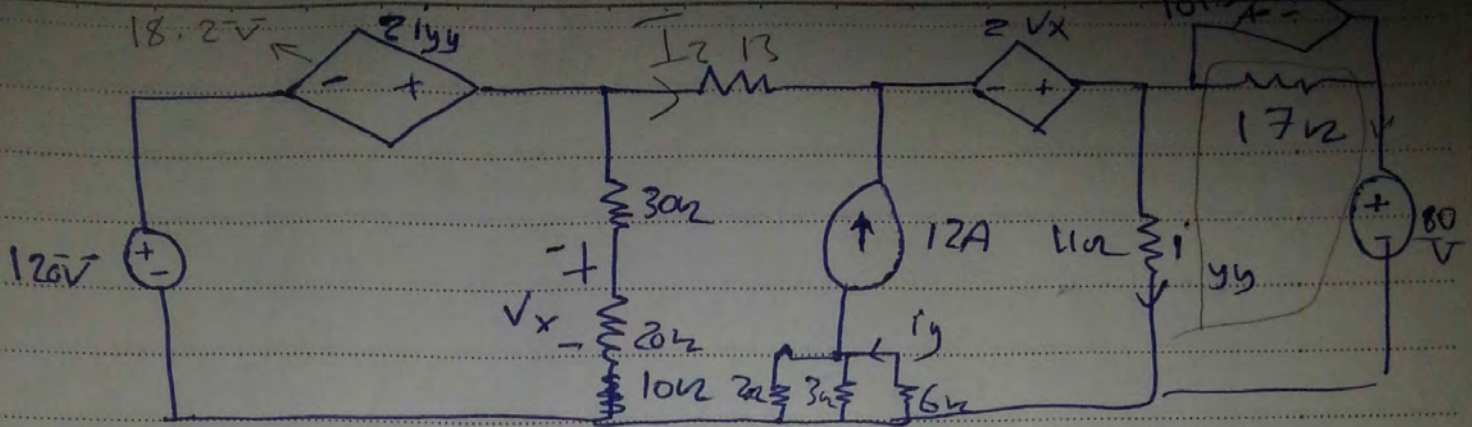

Sol<sup>n</sup>

$$i_y = 12 \times \frac{1}{\frac{1}{2} + \frac{1}{3} + \frac{1}{6}} = 2A \rightarrow 10i_y = 20V$$

KVL  $11i_y - 80 - 20 = 0$

$$i_y = \frac{100}{11} A$$

KVL  $-120 - 18.2 + V_+ = 0$   
 $V_+ = 138.2V$

$$V_x = V_+ \frac{20}{20+3+10} = 46.1V$$

KVL  $-120 - 18.2 + 13 \times i_x - 2 \times 46.1 + 20V + 80 = 0$

$$i_x = 10.02A$$

Power absorbed (80V) =  $I \times V$   
 $= 80 \times 12.92A$   
 $P = 1033.6W$

$$I = I_2 - I_y$$


$$= i_x + R - I_y$$

$$= 10.02 + 2 - \frac{100}{11}$$


$$= 12.92A$$



Thevenin and Norton Circuit etc.

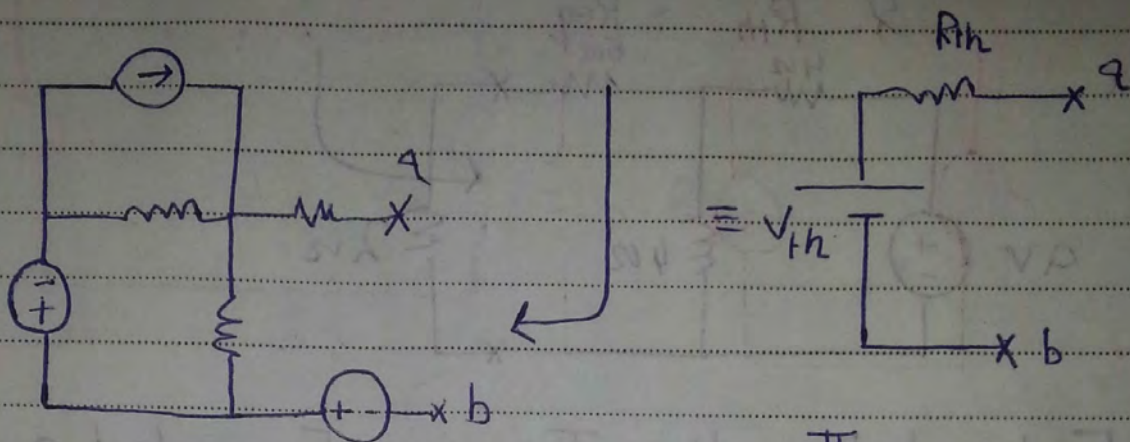

Thevenin eq. circuit

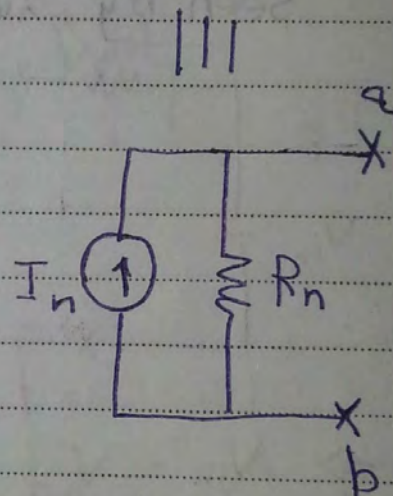


norton eq. circuit

- ① Type 1 etc. The circuit has only independent source.
- ② Type 2 etc. The circuit has dependent and independent sources.
- ③ Type 3 etc. The circuit has only dependent source.





$R_{th} ??$

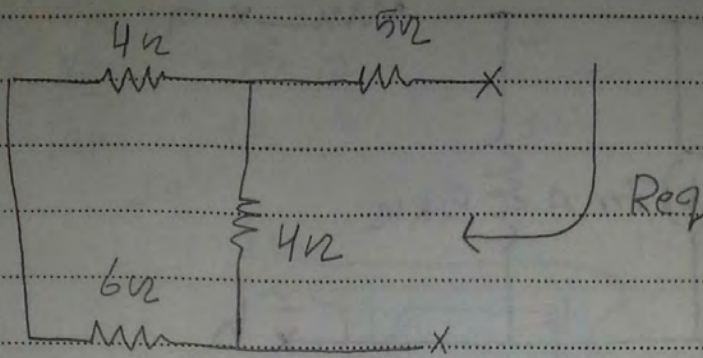

$$R_{th} = R_{eq} = (6+4) \parallel 4+5$$


$$R_{th} = \frac{55}{7} \Omega$$

$$V_{th} = \frac{18}{7} V$$

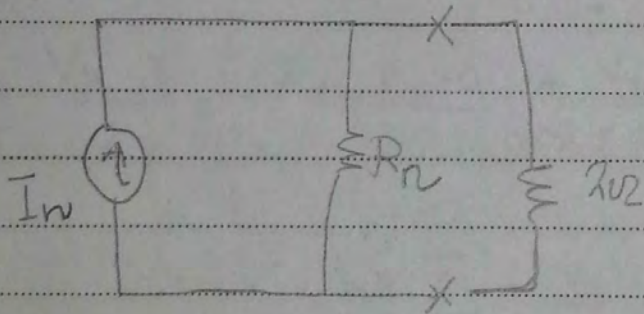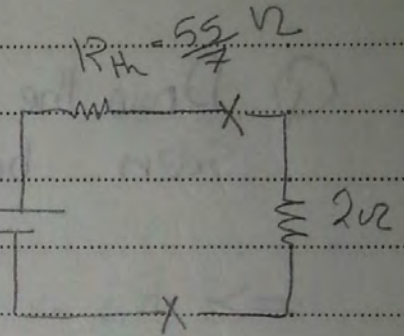

$$\Rightarrow R_n = R_{th} = \frac{55}{7} \Omega$$

$$\Rightarrow I_n = I_{s.c} \quad \text{or} \quad I_n = \frac{V_{th}}{R_{th}} \Rightarrow \frac{\frac{18}{7}}{\frac{55}{7}} = \frac{18}{55} A$$

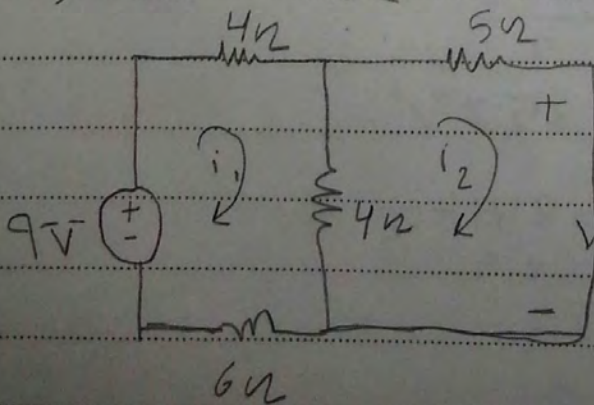

mesh 1:  $-9 + 4I_1 + 4(I_1 - I_2) + (I_1 - I_2) = 0$

mesh 2:  $5I_2 + 4(I_2 - I_1) = 0$

$$I_{s.c} = I_2 = \frac{18}{55} A$$

Ex 2c



Q Draw the Thevenin and Norton Equivalent Circuits seen between a & b.

$\Rightarrow R_{th} \rightarrow$  - kill all sources  
 $R_{eq} =$


$$* R_{eq} = 2 // 5 + 1 = 2.43 \text{ k}\Omega$$

$$\Rightarrow V_{th} = V_{o.c}$$

kd at  $V_{o.c}$ :

$$\frac{V_{o.c} - 0}{5} + 7 + \frac{V_{o.c} - 3}{2} = 0$$


$$V_{o.c} = V_{th} = -7.857 \text{ V}$$

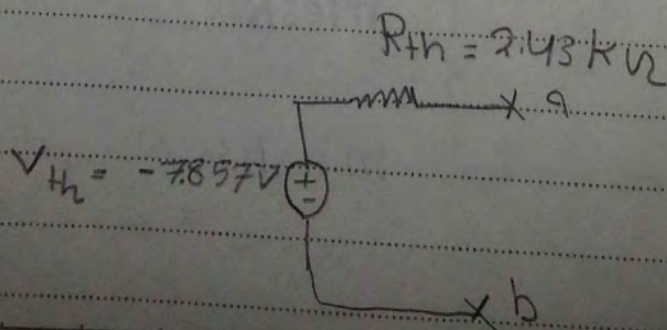

$$R_{Th} = R_{Th} = 2.45 \text{ k}\Omega$$

$$I_n = \frac{V_{Th}}{R_{Th}} = \frac{-55}{17} \text{ A}$$

$$\text{or } I_n = I_{S.C}$$

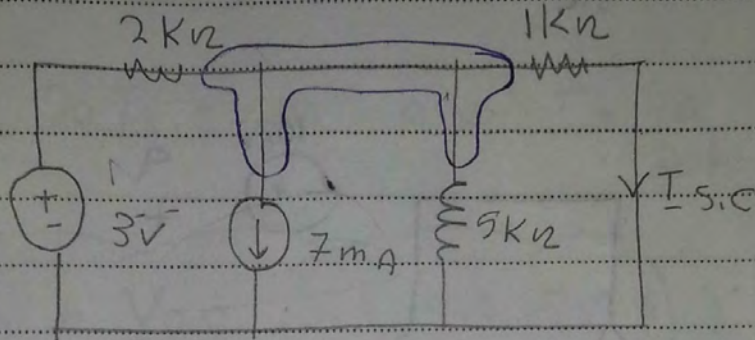

KVL at  $y$  node

$$\frac{V_y - 3}{2} + 7 + \frac{V_y - 0}{5} + \frac{V_y - 0}{1} = 0$$

$$V_y = V \Rightarrow I_y = \frac{V_y}{1} = \frac{-55}{17} \text{ mA}$$


ins

Type 2: The circuit has independent and dependent sources.

$$R_{th} = \frac{V_{o.c}}{I_{s.c}}$$

نهر انظمتها \*  
Type 2

Ex. 2

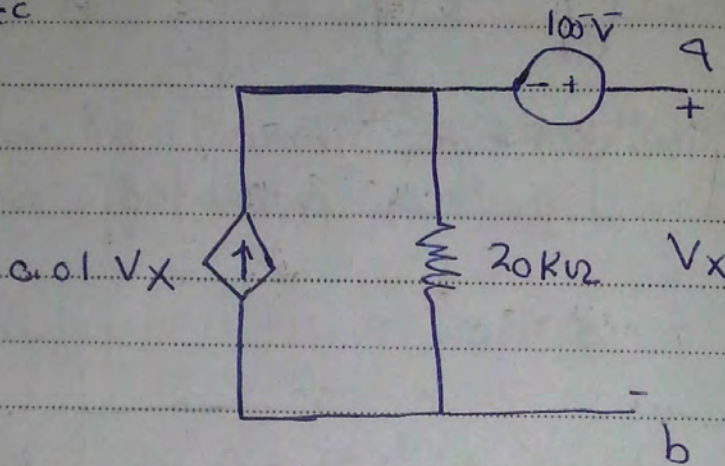

Q. 2 Draw the Thevenin and Norton equivalent circuits seen between a & b

$\Rightarrow$  Type 2


$$\Rightarrow V_{o.c} = V_x$$

$$KVL \Rightarrow -V_x + 100 + 20(0.01V_x) = 0$$

$$V_x = -0.503V$$

$$= V_{th} = V_{o.c}$$

$$\Rightarrow I_{s.c} \Rightarrow ??$$

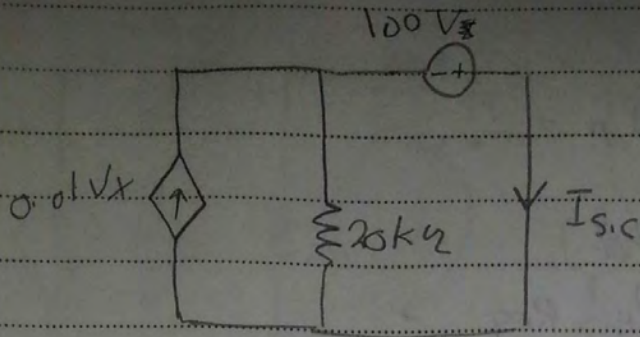


short circuit  $\Rightarrow V_x = 0 \Rightarrow$   
 o. of  $V_x = 0$  open circuit

$$\text{KVL } \Rightarrow 20 I_{s.c} - 100 = 0 \Rightarrow I = \frac{100}{20k} = 5 \text{ mA}$$

$$\Rightarrow R_{th} = \frac{V_{o.c.}}{I_{s.c.}} = -100,5 \Omega$$

$$= 100,5 \Omega$$

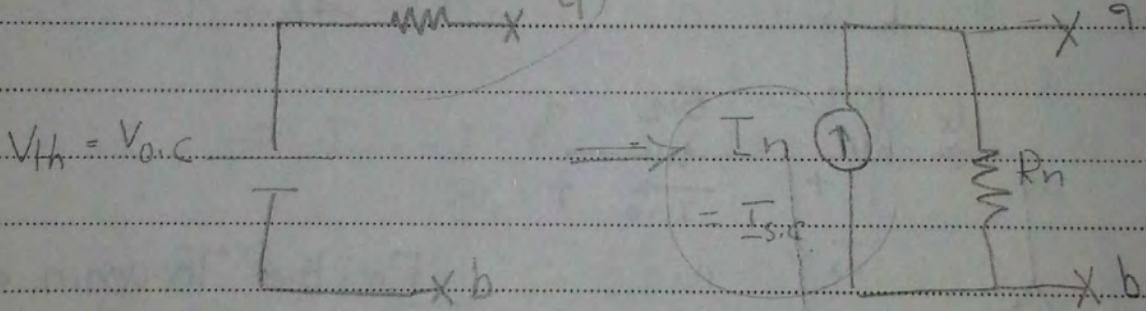

ins

$V_{th} = V_{o.c}$        $I_n = \frac{I}{s.c}$


$R_{th} =$

- ① Type 1 s.c.      (A) kill  
 (B)  $R_{th} = R_{eq}$


② Type 2 s.c.       $R_{th} = \frac{V_{o.c}}{I_{s.c}}$

③ Type 3 s.c. the circuit has only dependent source.

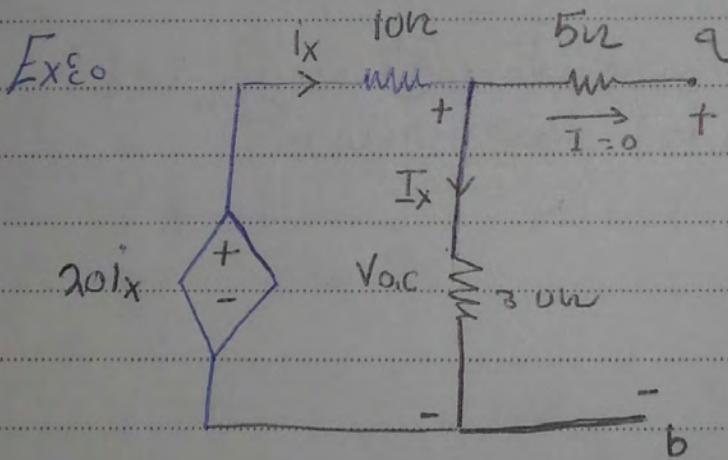$R_{th} = \frac{V_{test}}{I} = \frac{V}{I}$       or       $R_{th} = \frac{V}{I_{test} = 1A}$




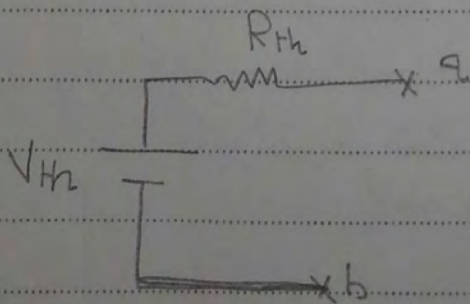Find the Thevenin eq circuit seen between a & b



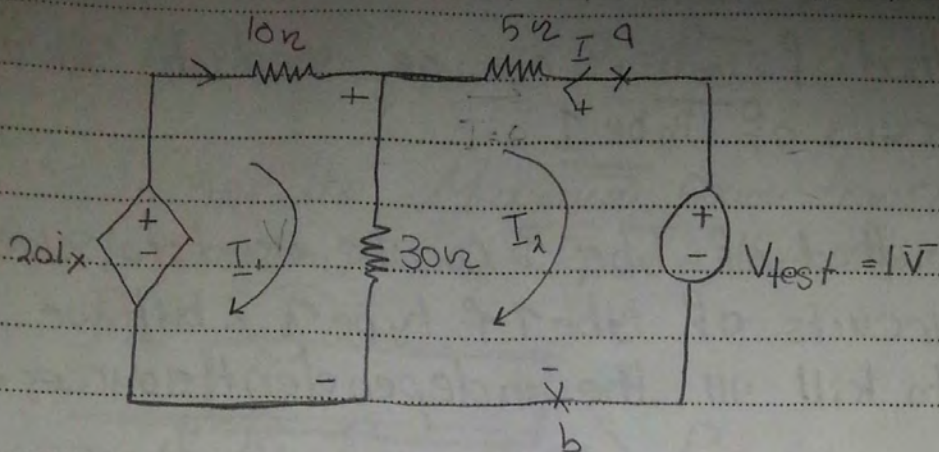$V_{th} = V_{o.c} = 30 i_x$   
 KVL:  $-20 i_x + 10 i_x + 30 i_x = 0$   
 $\Rightarrow i_x = 0 A$   
 $V_{th} = 0 V \leftarrow$





$$R_{th} = \frac{V_{test}}{I} \Rightarrow$$

$$-20i_x + 10i_1 + 30(I_1 - I_2) = 0 \quad \text{--- ①}$$

$$5i_2 + 1 + 30(I_2 - I_1) = 0 \quad \text{--- ②}$$

$$\Rightarrow I_2 = -\frac{1}{20} \text{ A} \quad I \Rightarrow -I_2 = \frac{1}{20} \text{ A}$$

$$* R_{th} = \frac{V_{test}}{\frac{1}{20}} = 20 \Omega$$


$$\frac{1}{20} \leftarrow I$$

ins

Note: ① The method of Type 2 can be used to solve the circuits of Type 1.


② The method of Type 3 can be used to solve the circuits of type 1 & type 2, but we have to kill all the independent sources.

Ex. 4c

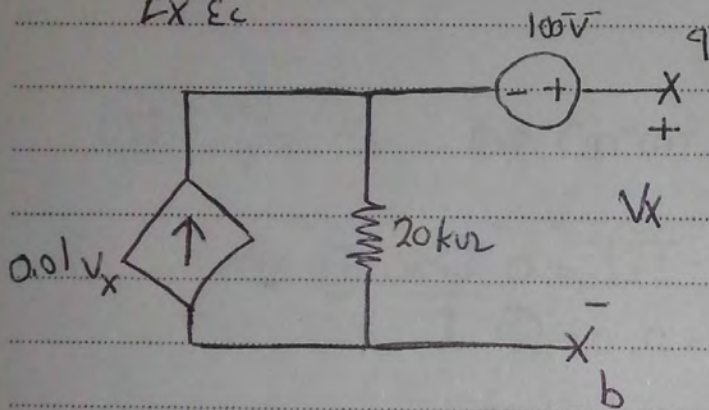

This circuit is type 2 circuit but, we can solve it using the method of type 3.

⇒ Kill all independent source

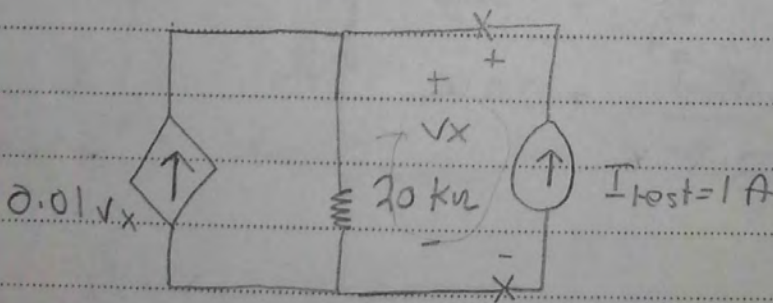

$$R_{th} = \frac{V}{I_{test}} = \frac{V}{1A}$$

$$KCL \Rightarrow \frac{V}{20} - 0.01V_x - 1 = 0$$

$$V = -100.5 V$$


$$R_{th} = \frac{V}{I_{test}} = -100.5 \Omega$$

1 A test

## \* Maximum power transfer

To get the Maximum power transfer from the circuit to a certain load ( $R_L$ ) in this circuit,  $R_L$  must equal  $R_{th}$

$\Rightarrow$  if  $R_L = R_{th}$ , then  $P_L(\max)$  why?? | sc

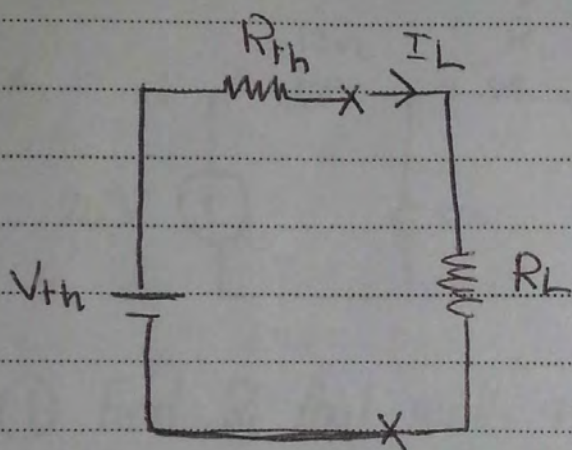

$$\begin{aligned}
 P_L &= I_L^2 R_L \\
 &= \left( \frac{V_{th}}{R_{th} + R_L} \right)^2 R_L \\
 &= \frac{V_{th}^2 R_L}{(R_{th} + R_L)^2}
 \end{aligned}$$

$$\frac{dP_L}{dR_L} = \frac{V_{th}^2 (R_{th} + R_L)^2 - 2 (R_{th} + R_L) V_{th}^2 R_L}{(R_{th} + R_L)^4}$$

$$\Rightarrow \frac{V_{th}^2 (R_{th} + R_L)^2}{(R_{th} + R_L)^4} = \frac{2 (R_{th} + R_L) V_{th}^2 R_L}{(R_{th} + R_L)^4}$$

$$R_{th} + R_L = 2 R_L$$


$$R_{th} = R_L \quad *$$

$$P_{L(\max)} = \left( \frac{V_{th}}{R_{th} + R_{th}} \right)^2 R_{th}$$

$$P_{L(\max)} = \frac{V_{th}^2}{4 R_{th}}$$

Subject: .....

28/10/2014

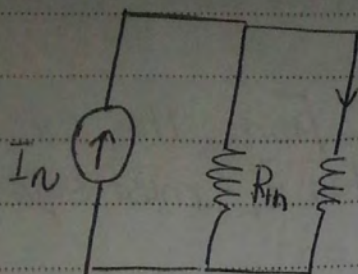

$$I_L = \frac{1}{2} I_N$$

$$R_L = R_{Th} \Rightarrow$$

$$P_{L(max)} = I_L^2 R_L$$




$$P_{L(max)} = \frac{I_N^2}{4} R_{Th}$$

$$\Rightarrow P_{max} \text{ if } R_L = R_{th}$$

$$\Rightarrow P_{max} = \frac{V_{th}^2}{4R_{th}}$$

$$= \frac{I_{sc}^2 R_{th}}{4}$$

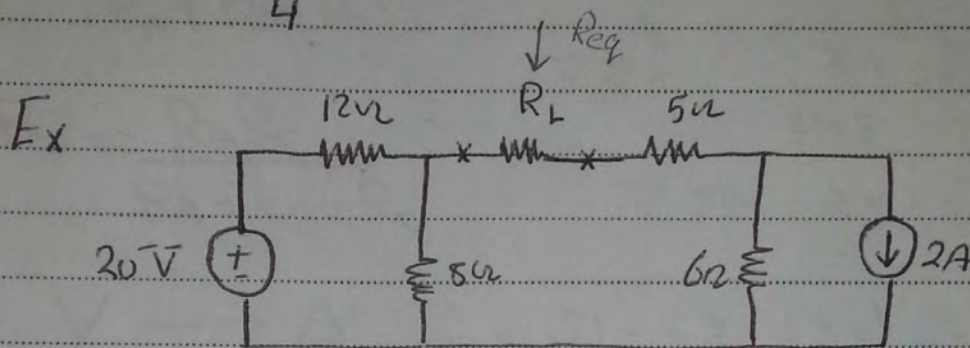


① Find  $R_L$  that will absorb the maximum power from the circuit ( $P_{max}$ )

② Find  $P_{max}$

Sol<sup>n</sup>:

$$R_L = R_{th}$$

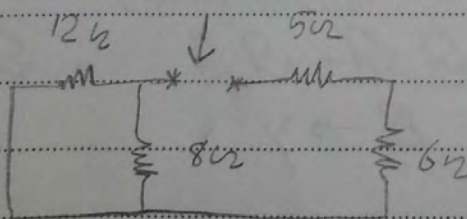


$$R_{eq} = (12 \parallel 8) + 5 + 6$$

$$= 15.8 \Omega$$

$$* P_{max} = \frac{V_{th}^2}{4R_{th}}$$

$$V_{th} = V_{oc}$$

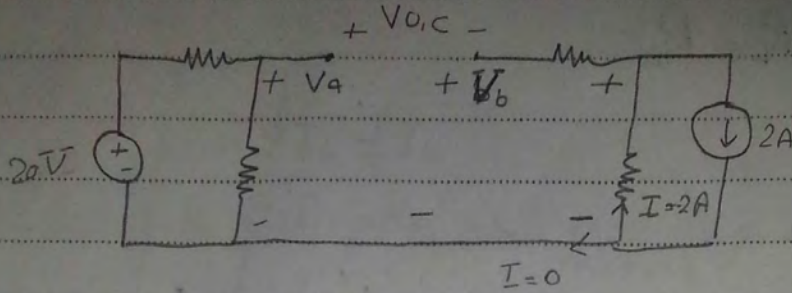

short circuit  
مع التوازي  
I=0

$$V_{oc} = V_a - V_b$$

$$V_a = \frac{20 * 8}{8+12} = 8V$$

$$V_b = -2 * 6 = -12V$$


$$V_{th} = V_{oc} = 8 - (-12) = 20V$$

$$P_{max} = \frac{20^2}{4 * 15.8} = 6.329W$$

$\Delta \rightarrow Y, Y \rightarrow \Delta$

Conversions 30

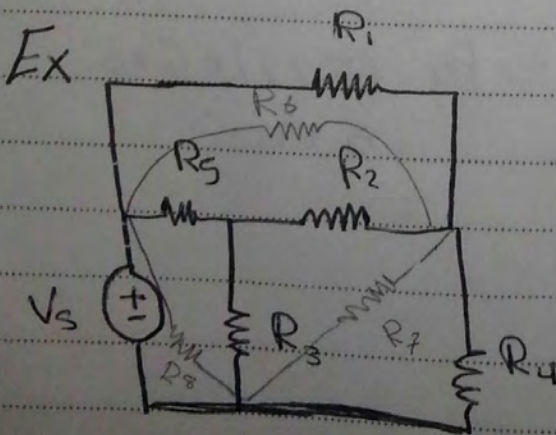$Y \Rightarrow$  ثلاثة مقاومات متشككين  
نقطة واحدة Node



$\Delta \rightarrow Y$  e

- \* No parallel
- \* No series

Subject: .....


30/10/2014

$\Delta \rightarrow Y$

$$R_1 = \frac{R_A R_B}{R_A + R_B + R_C}$$

$$R_2 = \frac{R_B R_C}{R_A + R_B + R_C}$$
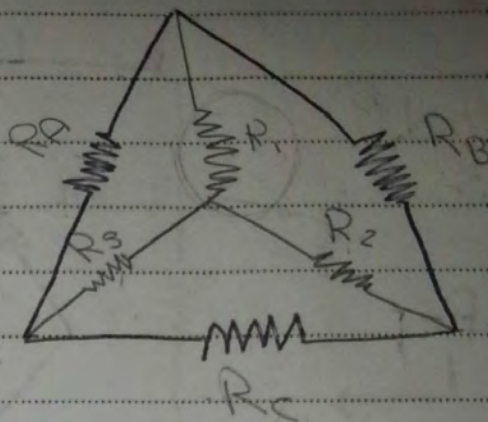
$$R_3 = \frac{R_A R_C}{R_A + R_B + R_C}$$



$Y \rightarrow \Delta$


$$R_A = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_B = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_C = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

Ex

Method (1)

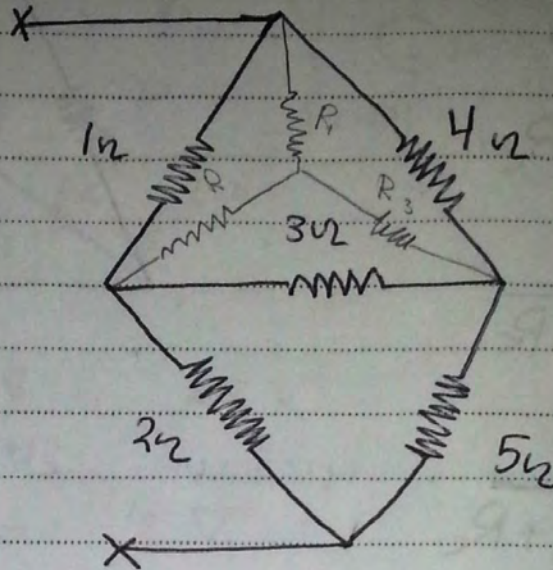Req  
→


$$R_1 = \frac{4 \times 1}{1 + 3 + 4} = \frac{4}{8} \Omega$$

$$R_2 = \frac{3 \times 1}{1 + 3 + 4} = \frac{3}{8} \Omega$$

$$R_3 = \frac{4 \times 3}{4 + 1 + 3} = \frac{12}{8} \Omega$$


$$R_{eq} = [(R_2 + 2) \parallel (R_3 + 5)] + R_1$$

Method (2)


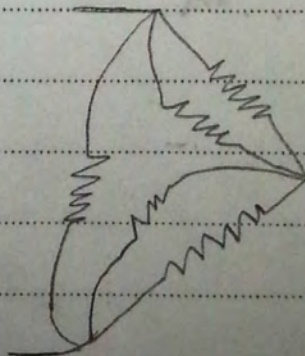




Exe

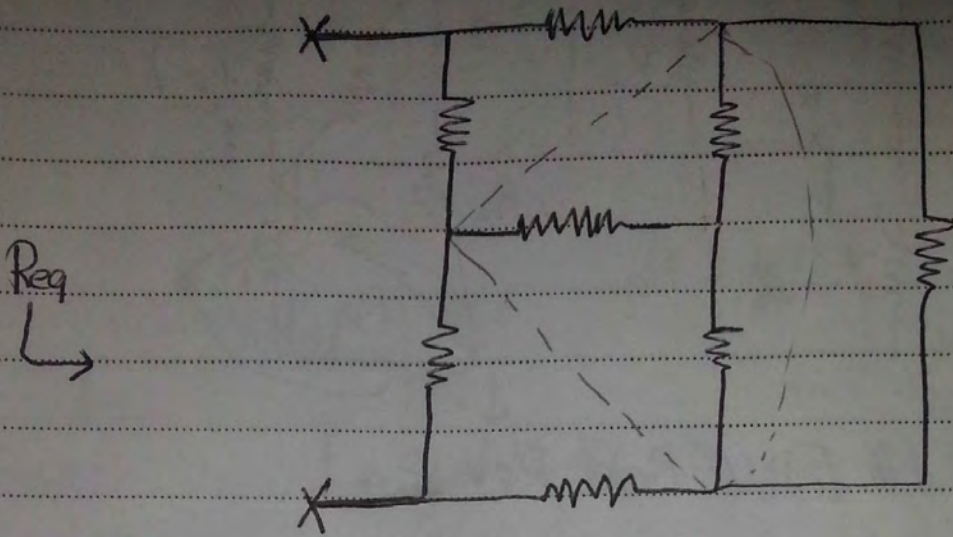


answer is  $R_{eq} = \frac{8}{7} R$

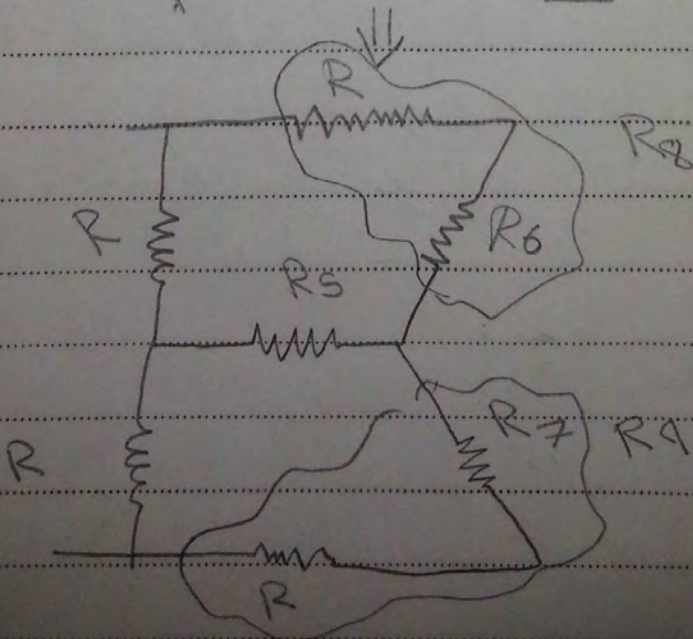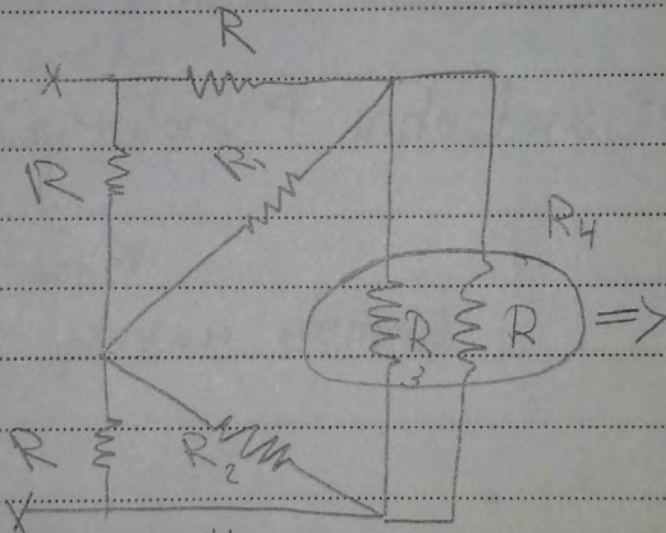

30 / 10 / 2014

Subject: .....

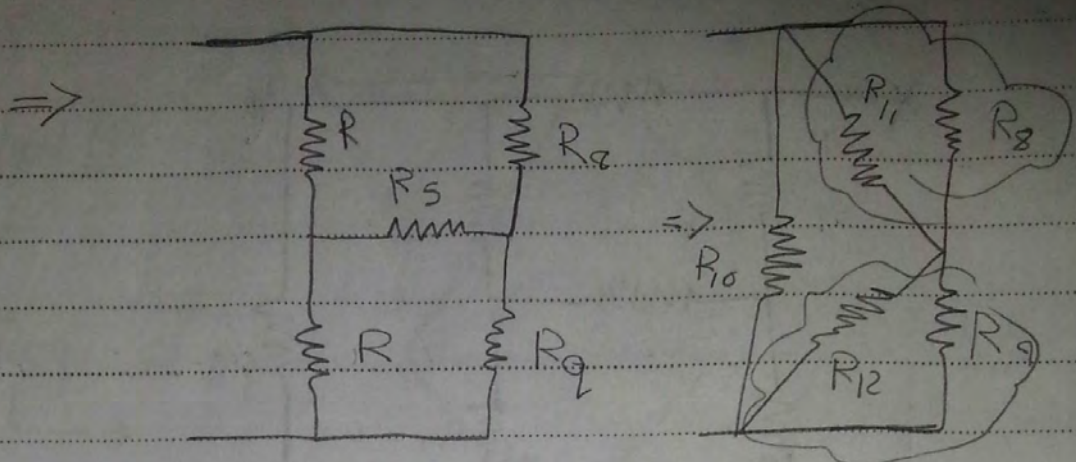

$$R_{eq} \Rightarrow R_{10} \parallel [R_{11} \parallel R_8 + R_9 \parallel R_{12}]$$

$P = \sum \text{all DC sources}$

study date

\* Circuits

\* AC mixed

\* DC (only DC sources) include DC independent sources

\* Transient

\* steady-state

① Analysis

Analysis

(there is a switch)

(no switch)

② there is an initial condition

\* AC independent sources

\*  $CH \neq \epsilon$  Capacitors & inductors <sup>30</sup>

\* Capacitor <sup>30</sup>


=> linear passive element

ins

**CH 7  $\epsilon_c$**




\* Capacitor  $\epsilon_c$  -

$\Rightarrow$  linear passive element

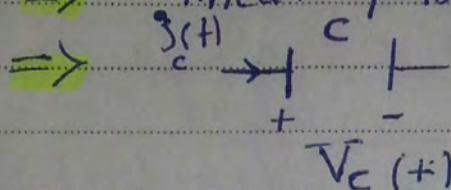

$\Rightarrow$  C: Capacitance (Farad) (F)

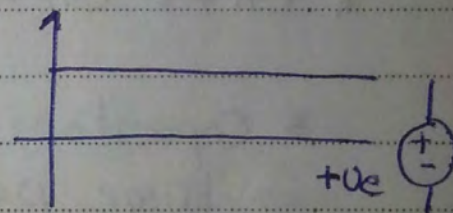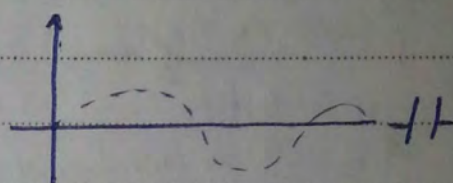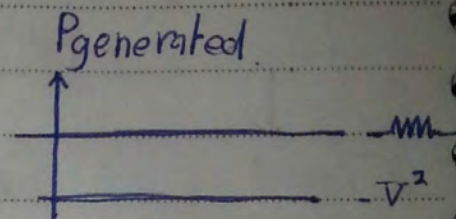- e.g.  $\Rightarrow$
- $C = 3 \text{ MF}$
  - $C = 4.1 \text{ pF}$
  - $C = 3.2 \text{ nF}$
  - $C = 1 \text{ F}$




$$\Rightarrow I_c(t) = C \frac{dV_c(t)}{dt}$$

**Notes  $\epsilon_c$**


① The capacitor in the DC circuits is considered as open circuit, why?!

Since  $V_c(t) = \text{constant} \Rightarrow I_c(t) = C \frac{dV_c(t)}{dt} = 0 \text{ A}$

**Ex  $\epsilon_c$**

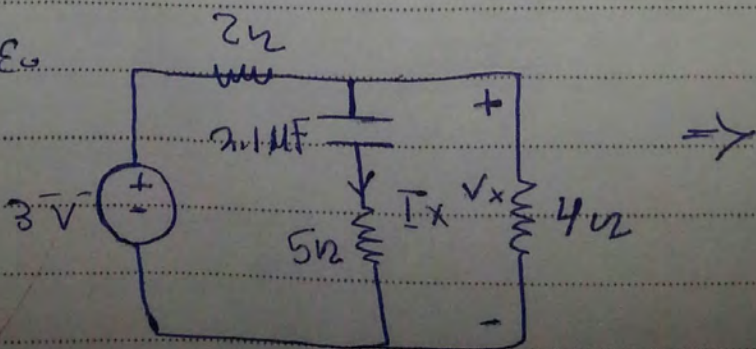


Dc circuit

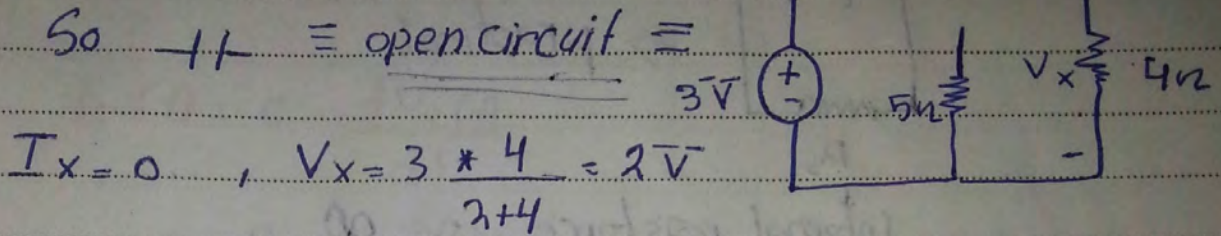

② The Voltage on the capacitor can't change in a zero time

Why?

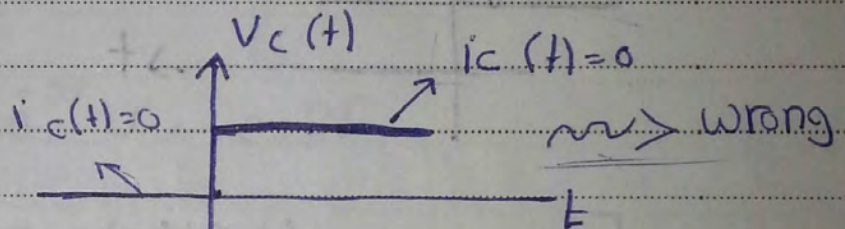

$$i_c(t) = C \frac{dv_c(t)}{dt}$$


slope  $\leftarrow \frac{dv_c(t)}{dt}$


slope =  $\frac{3}{0} = \infty$

$i_c(t) = \infty \Rightarrow$  impossible




$$V_c(0^-) = V_c(0^+) = V_c(0)$$

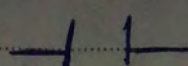\*   $\Rightarrow$  ideal  $\checkmark$

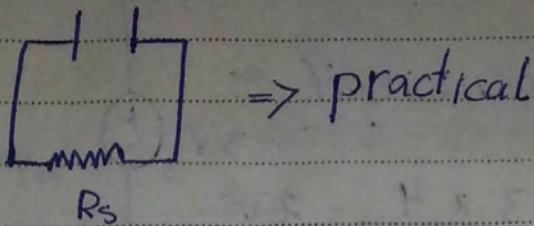

internal resistance  $\approx \infty$

Ex. find  $i_c(t)$ , if  $C = 2F$


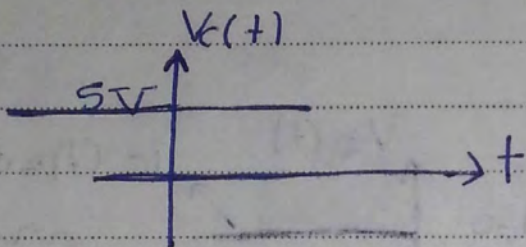


$$i_c(t) = C \frac{dv_c(t)}{dt}$$

slope  $\rightarrow$

$= 0$

Ex. find

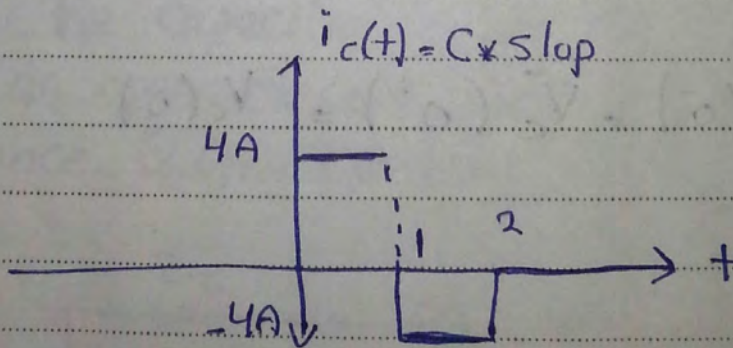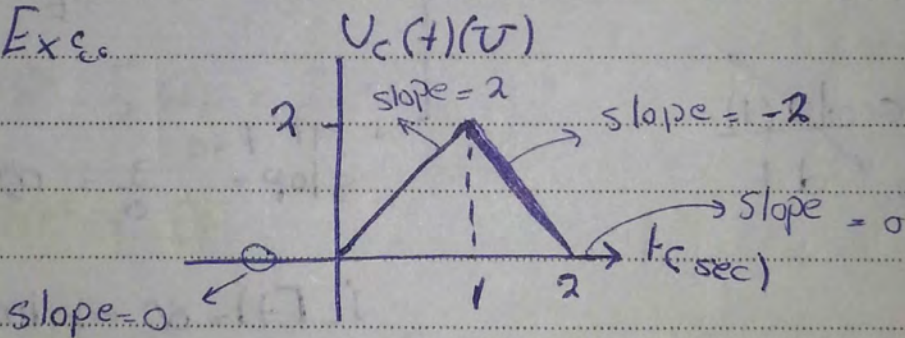

Subject: .....

2/11/2014

Exec IF  $V_c(t) = 5 \sin(\pi t)$

Sol 30  $C = 2F$ , Find  $i_c(t)$

$$i_c(t) = C \frac{dV_c(t)}{dt}$$
$$= 2 * 5 \pi \cos(\pi t)$$

$$i_c(t) = 10 \pi \cos(\pi t) \quad \leftarrow$$

↓

$$\frac{22}{7}$$

Exec  $V_c(t) = 2e^{-5t} V$ ,  $C = 2F$

$I_c(t) = ??$


Sol 30

$$I_c(t) = C * \frac{dV_c(t)}{dt}$$

$$I_c(t) = 2 * (-2 * 5 e^{-5t})$$

$$I_c(t) = -20 e^{-5t}$$

$\Rightarrow$  discharging

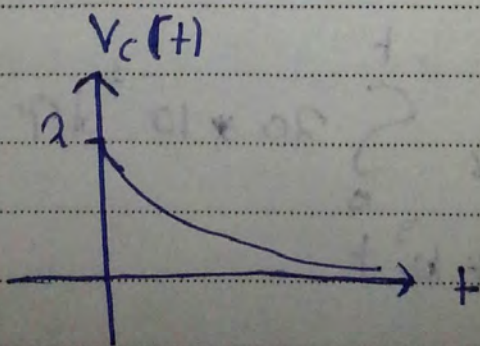


$$\Rightarrow V_c(t) = \left[ \frac{1}{C} \int_{t_0}^{+} i_c(\tau) d\tau \right] + V_c(t_0)$$

After we put  
them in the  
Circuit

initial value  
of  $V_c(t)$

zero "لك"

Ex. 20

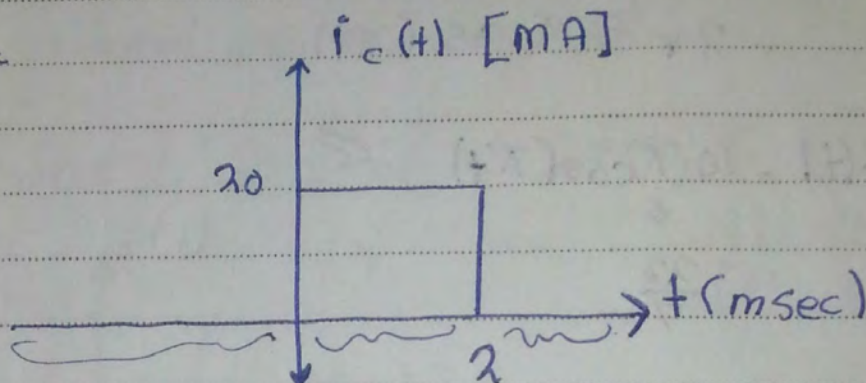

$$C = 5 \text{ MF}$$

Draw  $V_c(t)$

نقسم الرسمة إلى جزأين

For  $-\infty \leq t \leq 0$  msec.

$$V_c(t) = \frac{1}{C} \int_{-\infty}^{+} i_c(\tau) d\tau + V_c(-\infty)$$

$$V_c(t) = 0 \text{ V}$$

For  $0 \leq t \leq 2$

$$V_c(t) = \frac{1}{5 \times 10^{-6}} \int_0^t 20 \times 10^{-3} d\tau + V_c(0)$$


$$V_c(t) = 4 \times 10^3 t$$



\* For  $2 \leq t < \infty$

$$V_c(t) = \frac{1}{C} \int_2^t i_c(\tau) d\tau + V_c(2) \quad 8V$$

$$V_c(t) = 8V$$

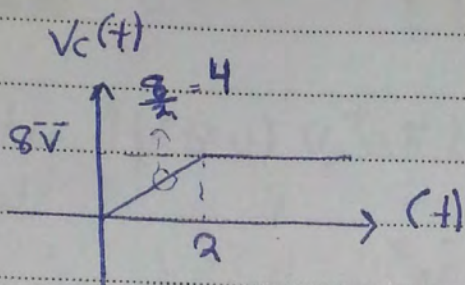

### \* Stored Energy in a capacitor

$$W_c(t) = \frac{1}{2} C [V_c^2(t) - V_c^2(t_0)] + W_c(t_0) \quad (\text{Joule})$$

↓ initial value     ↓ initial value

⇒ if  $V_c(t_0) = 0$  &  $W_c(t_0) = 0$

$$W_c(t) = \frac{1}{2} C V_c^2(t) \quad (\text{J})$$

\* energy with time

$$* P_c(t) = i_c(t) V_c(t) \quad \text{W} \quad (\text{watt})$$

\* watt (تسعة) يكون استهلاكها

$$P_c(t) = \frac{dW_c(t)}{dt} \quad \text{W}$$

اقتراحات الوقت \*


Ex: c

عالم تسعون watt 23

\* العالم الثانية

تسعون watt 75

↑ P = I V xali

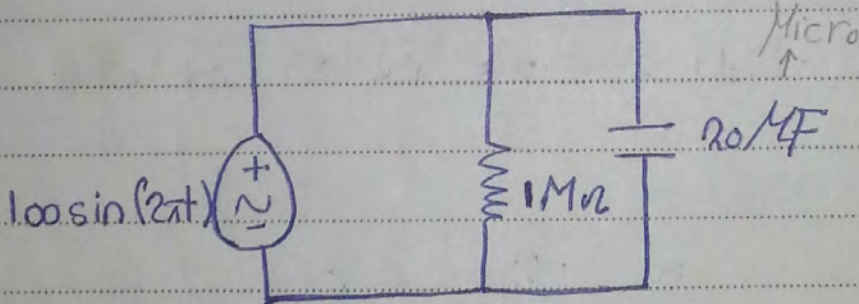




\* Find the Maximum energy stored in capacitor over the interval  $0 \leq t \leq 0.5$  sec. also Find the dissipated energy in the resistor during the same interval ?!

Sol ⇒

$$\begin{aligned}
 W_c(t) &= \frac{1}{2} C V_c^2(t) \\
 &= \frac{1}{2} * 20 * 10^{-6} * (100 \sin(2\pi t))^2 \Rightarrow \\
 &= 0.1 \sin^2(2\pi t) \quad \text{J}
 \end{aligned}$$

Subject: .....

4/11/2014

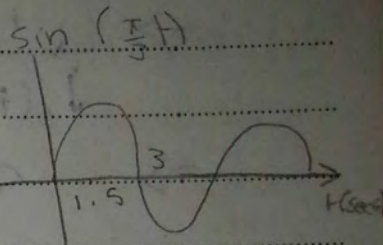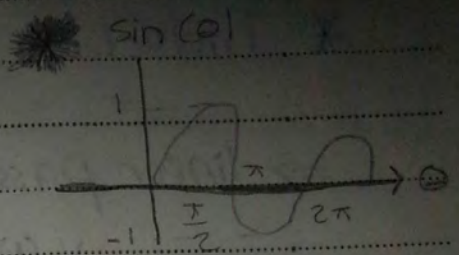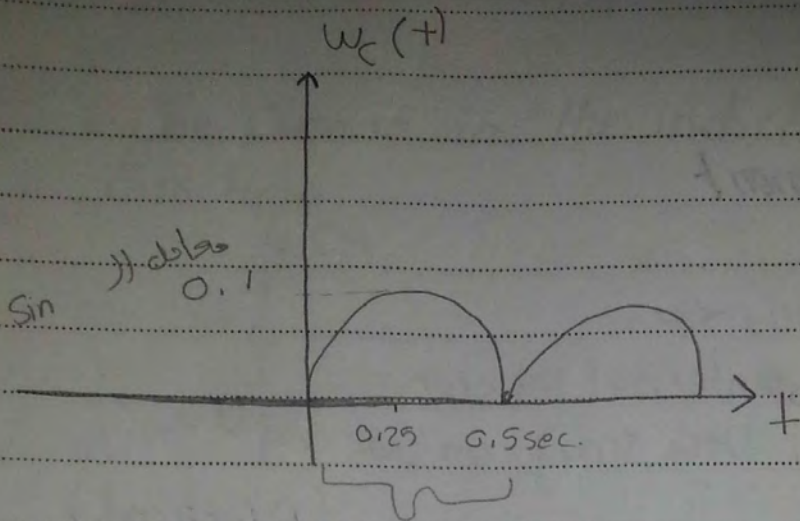

$$\Rightarrow P_R(t) = i_R(t) \cdot V_R(t)$$

$$= \frac{V_R^2(t)}{R} = \frac{(100 \sin(2\pi t))^2}{1 \cdot 10^6}$$

$$= 0.01 \sin^2(2\pi t) \text{ W}$$

$$\Rightarrow W_R = \int_0^{0.5} P_R(t) dt = \int_0^{0.5} 0.01 \sin^2(2\pi t) dt = 1 \text{ mJ}$$

$$0.01 \int_0^{0.5} \frac{1}{2} [1 - \cos(4\pi t)] dt$$



$$= 2.5 \text{ mJ}$$

$$\frac{\pi}{3} t = \pi$$

$$t = 3 \text{ sec.}$$

\* Inductance

=> linear passive element

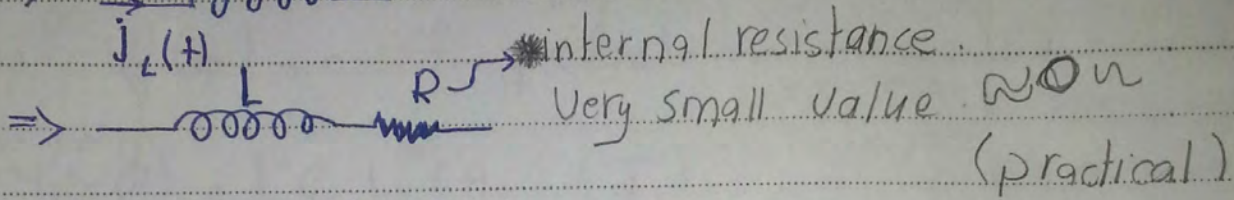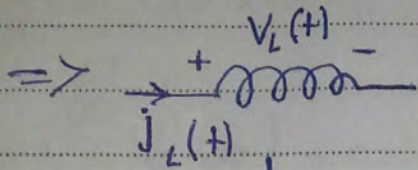


$$\Rightarrow V_L(t) = L \frac{di_L(t)}{dt}$$

$$\Rightarrow i_L(t) = \frac{1}{L} \int_{t_0}^t V_L(\tau) d\tau + i_L(t_0)$$


=>  $L_i$  inductance [Henry] => H

\* In Dc circuit, we consider the inductor as short-circuit
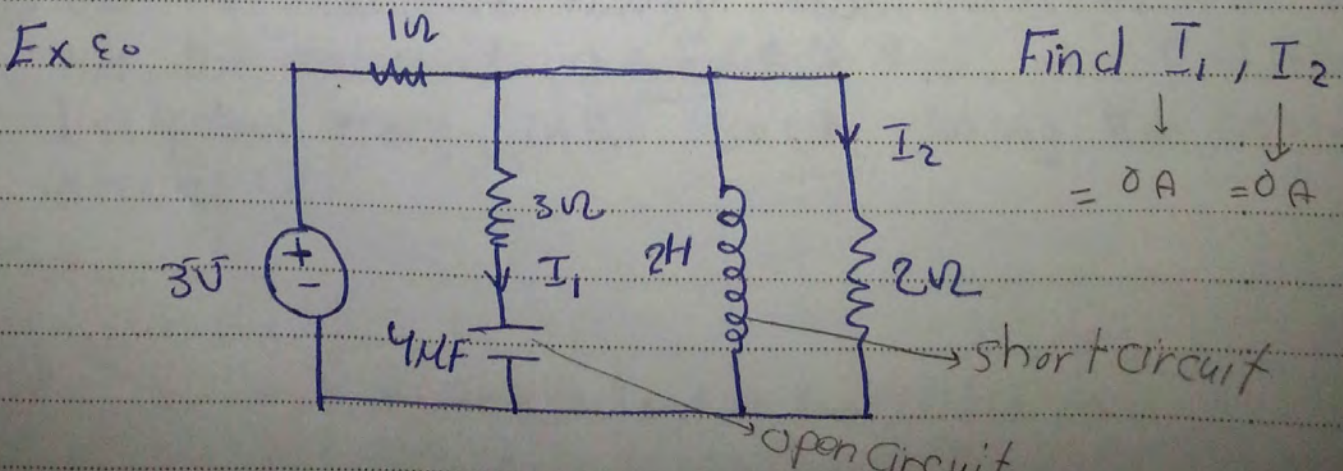
$$\Rightarrow V_L(t) = L \frac{di_L(t)}{dt} \stackrel{\text{Constant}}{=} 0 \Rightarrow \text{Shortcircuit}$$



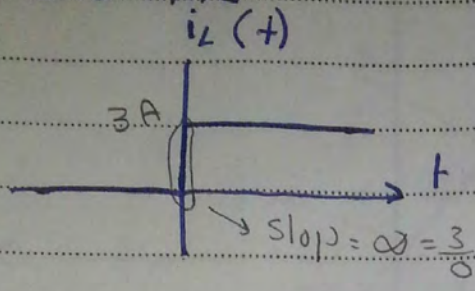\* The current in the inductor cannot change in a zero time




=> wrong, because  $V_L(t) = L \frac{di_L(t)}{dt}$

$V_L(t) =$  impossible.   
 $\downarrow$  Slope  $\downarrow$   $\infty$


6/11/2014

Ex: if  $L=3H$ , Find  $V_L(t)$


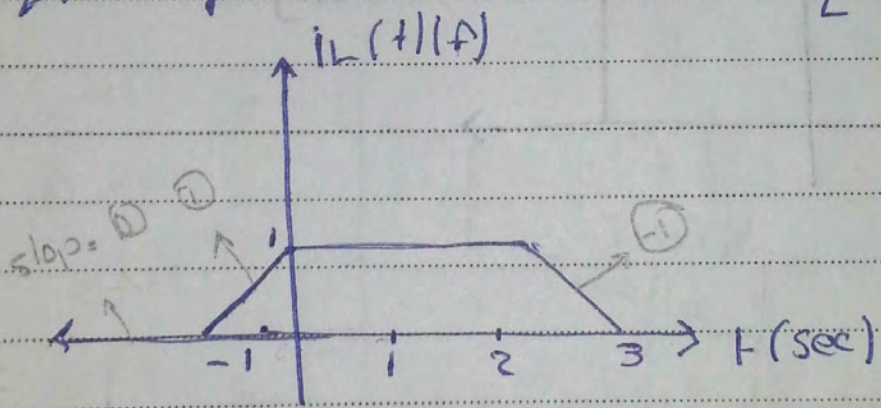


$$V_L(t) = L \frac{di_L(t)}{dt} = L * \text{Slope}$$



ins

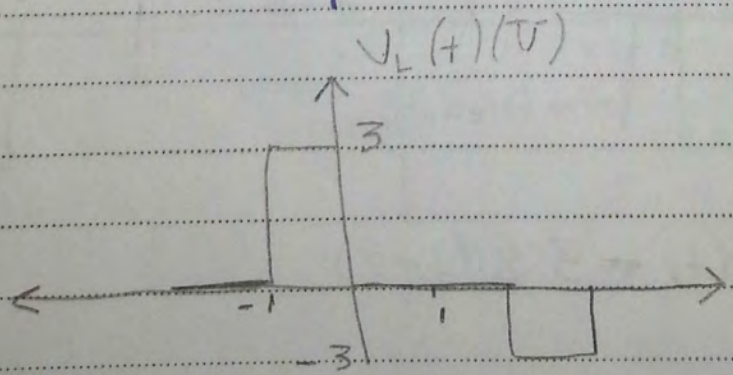

Ex 6.0

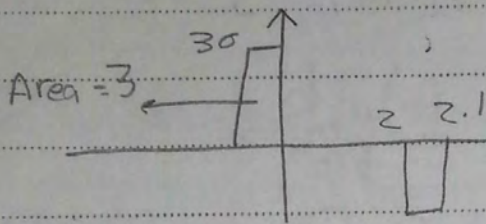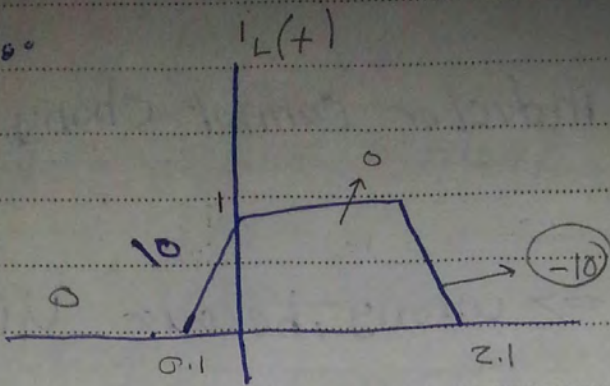

Ex 6.1

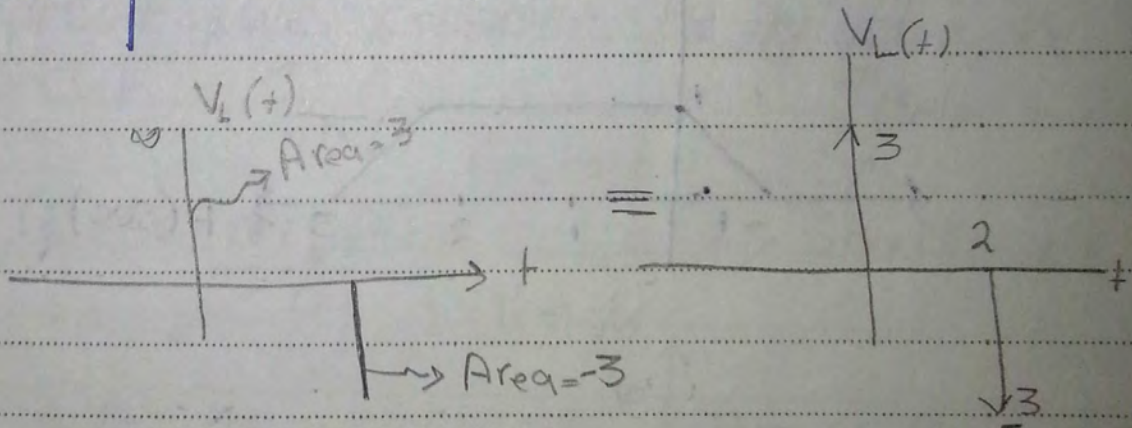
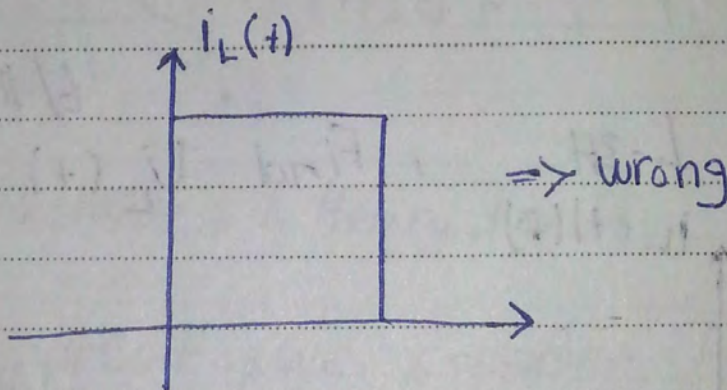


$$V_L(t) = 3 \delta(t) = 3 \delta(t-2)$$

↓

impulse function

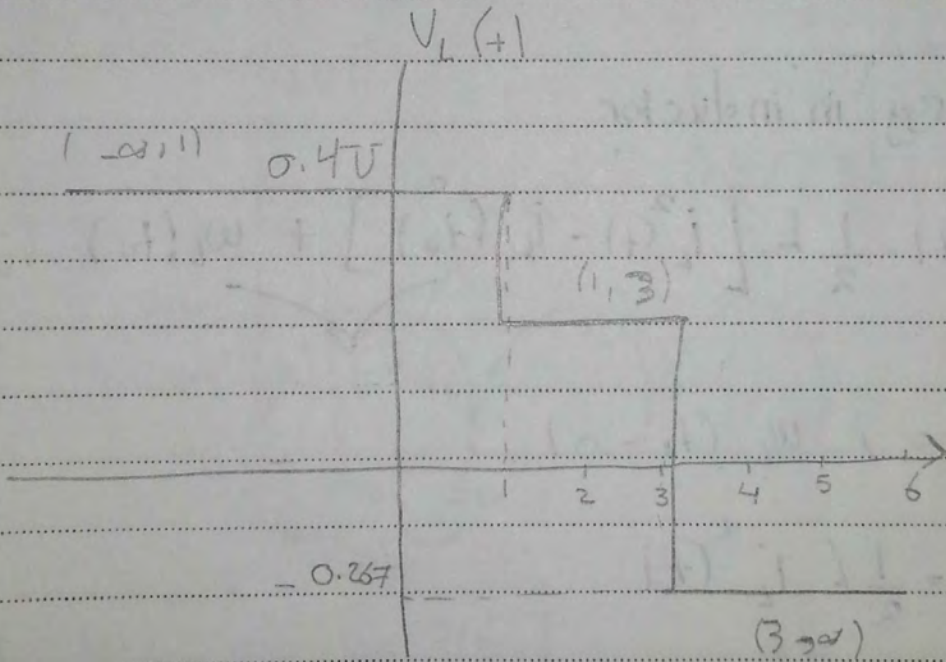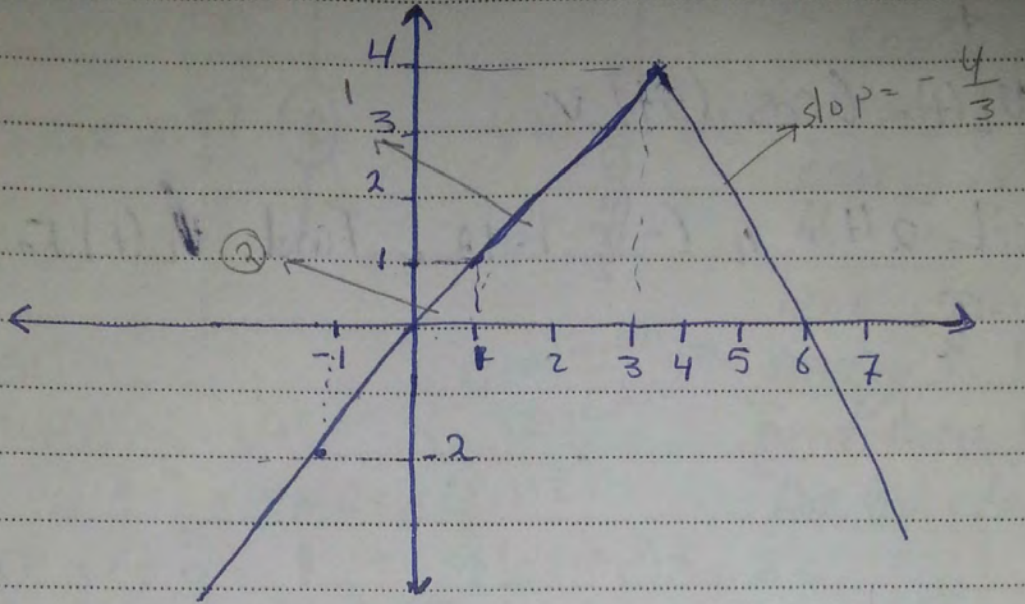Ex 1P  $L = 200 \text{ mH}$ , Find  $V_L(t)$



ins

Subject: .....

6/11/2014

$$* i_L(t) = \frac{1}{L} \int_{t_0}^t v_L(\tau) d\tau + i_L(t_0)$$

Ex: if  $v_L(t) = 6 \cos(5t) \text{ V}$

and  $L = 2 \text{ H}$ ,  $i_L(-\frac{\pi}{2}) = 1 \text{ A}$ , Find  $i_L(t)$  for  $t > -\frac{\pi}{2}$

Sol:  $t_0 = -\frac{\pi}{2}$

$$\Rightarrow i_L(t) = \frac{1}{2} \int_{-\frac{\pi}{2}}^t 6 \cos(5\tau) d\tau + 1 = 0.6 \sin 5t + 1 \text{ A}$$

\* stored energy in inductor

$$w_L(t) = \frac{1}{2} L [i_L^2(t) - i_L^2(t_0)] + w_L(t_0) \text{ (J)}$$

initial values

if  $i_L(t_0) = 0$ ,  $w_L(t_0) = 0$


then

$$w_L(t) = \frac{1}{2} L i_L^2(t)$$

$$* p_L(t) = \frac{dw_L(t)}{dt} = i_L(t) v_L(t)$$



Ex. 20

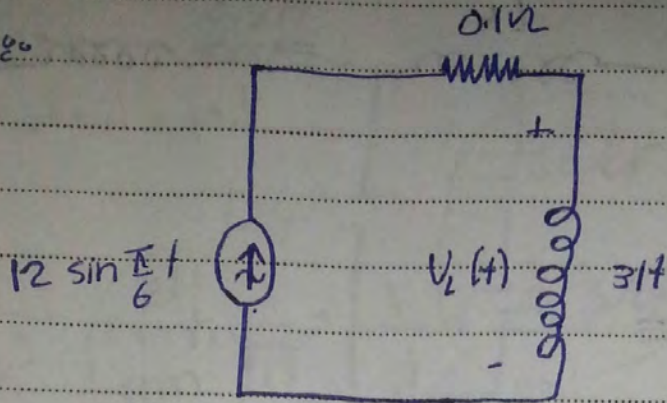

Find the maximum energy stored in the inductor and the energy dissipated in the resistor in the time during which the energy is being stored and then recovered from the inductor.



Sol. 30

$$W_L(t) = \frac{1}{2} L i^2(t)$$

$$= \frac{1}{2} * 3 * (12 \sin(\frac{\pi}{6}t))^2$$

القوة التي تسمى  
الطاقة وتبقى في
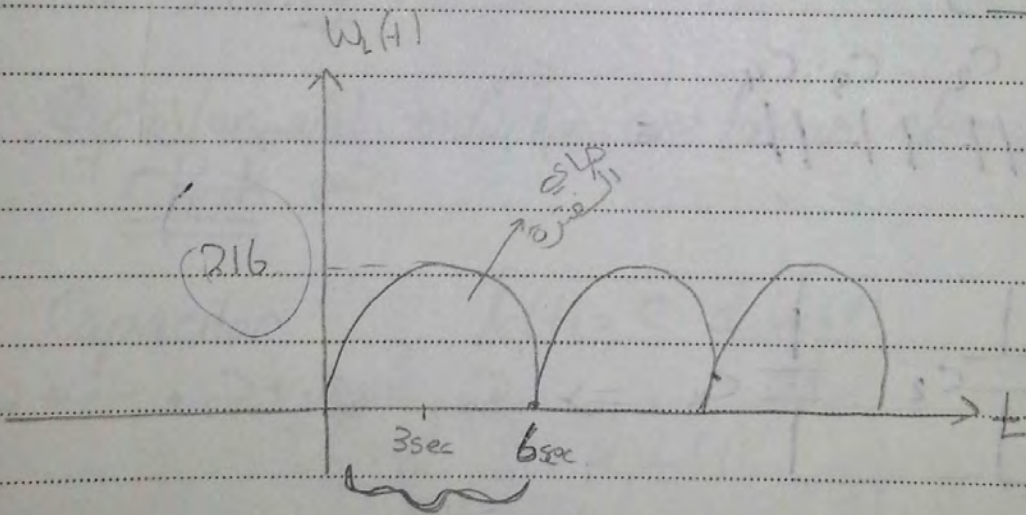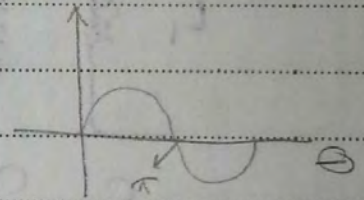
$$= 216 \sin^2(\frac{\pi}{6}t) \text{ J}$$








(a)  $W_{L(\text{maximum})} = 216 \text{ J}$


(b)  $P_R(t) = I_R^2(t) R$   
 $= (12 \sin(\frac{\pi}{6}t))^2 * 0.1$   
 $= 14.4 \sin^2(\frac{\pi}{6}t) \text{ W}$

$$W_{R(t)} = \int_0^6 14.4 \sin^2(\frac{\pi}{6}t) dt \Rightarrow 43.2 \text{ J}$$

Subject: .....

6/11/2014

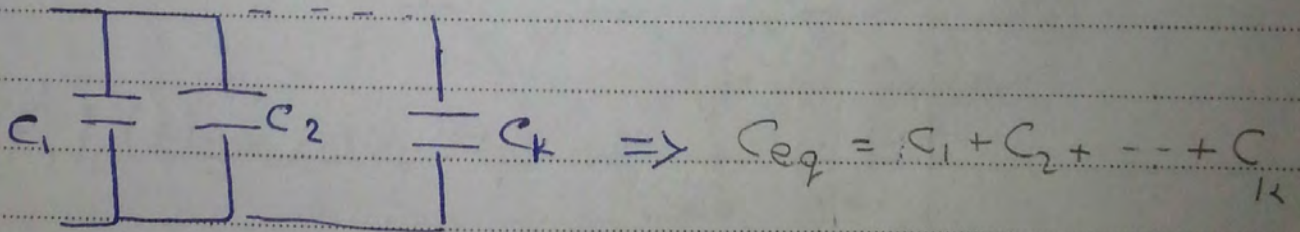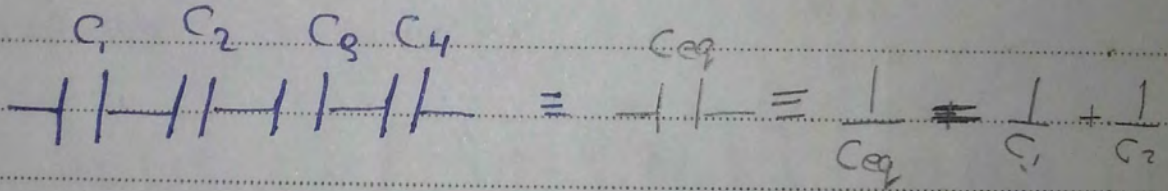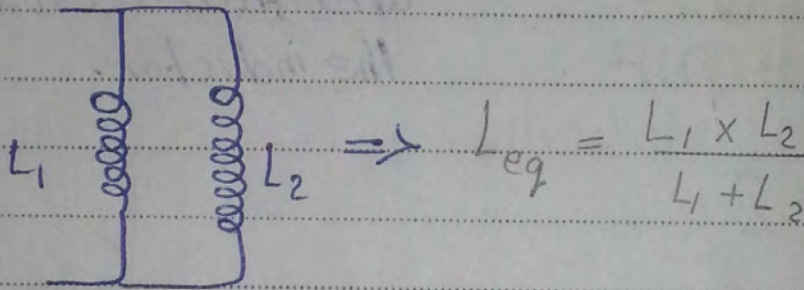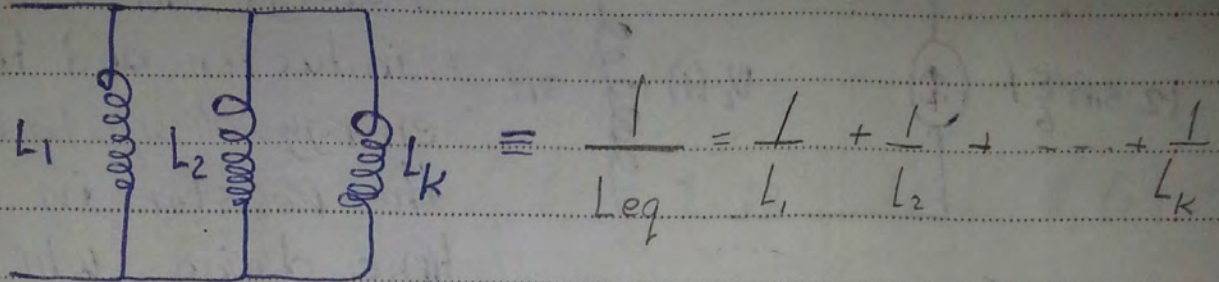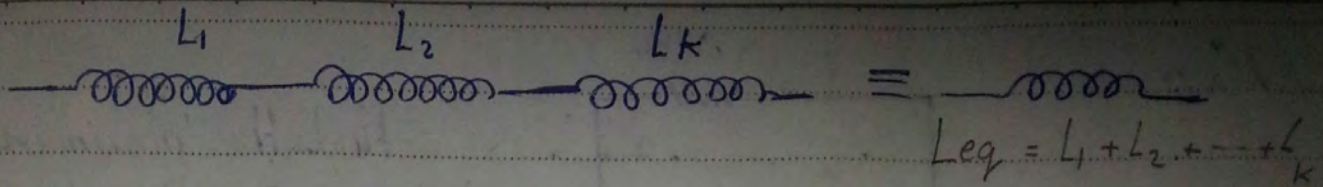

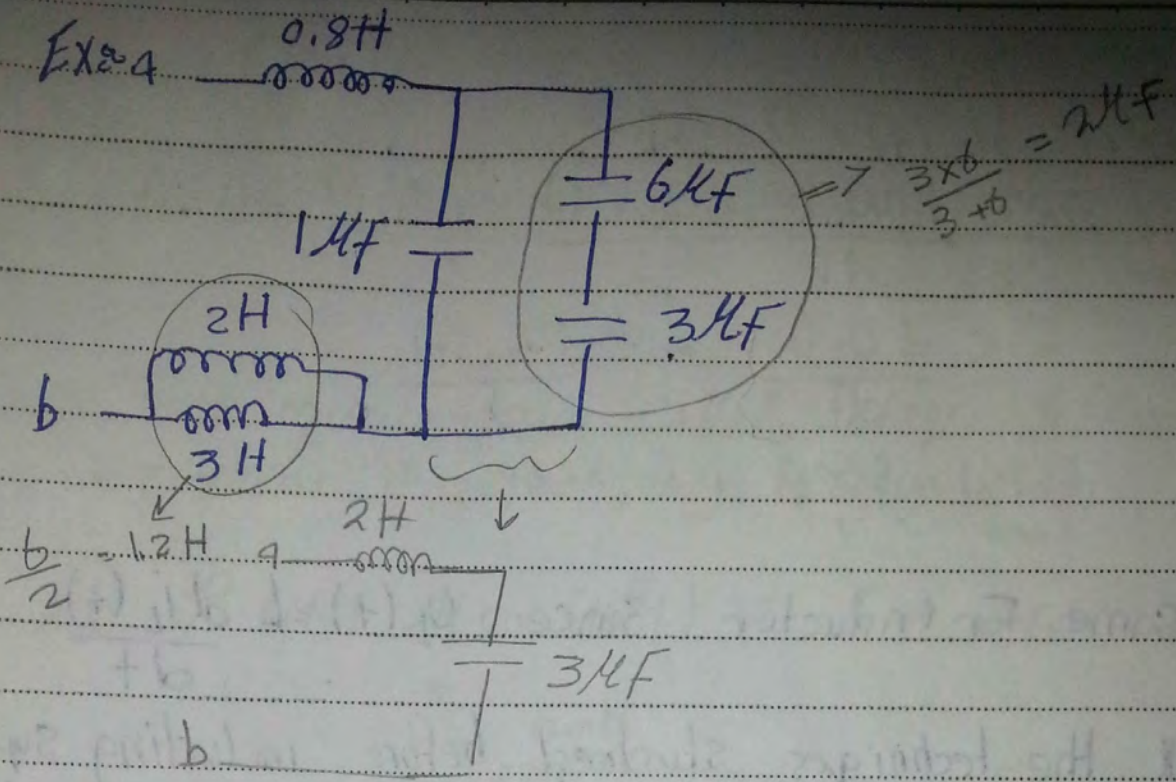

\* Linearity

Capacitor and inductor are linear elements.

Check

Capacitor

$$i_c(t) = C \frac{dV_c(t)}{dt}$$

$$V_{c, \text{new}}(t) = k V_c(t)$$

$$i_{c, \text{new}}(t) = C \frac{dV_{c, \text{new}}(t)}{dt}$$

$$= C \frac{d(k V_c(t))}{dt}$$

$$i_{c, \text{new}}(t) = k C \frac{dV_c(t)}{dt}$$

$$i_{c, \text{new}}(t) = k i_c(t)$$

∴ linear relation

OR ⇒

$$V_{c_{new}}(t) = V_{c_1}(t) + V_{c_2}(t)$$

$$i_{c_{new}}(t) = C \frac{d(V_{c_1}(t) + V_{c_2}(t))}{dt}$$


$$= C \frac{dV_{c_1}(t)}{dt} + C \frac{dV_{c_2}(t)}{dt}$$

$$i_{c_{new}}(t) = i_{c_1}(t) + i_{c_2}(t)$$

\* Same for inductor since  $V_L(t) = L \frac{di_L(t)}{dt}$

\* all the techniques studied before including superposition can be applied to analyze circuits that have capacitors and inductors.
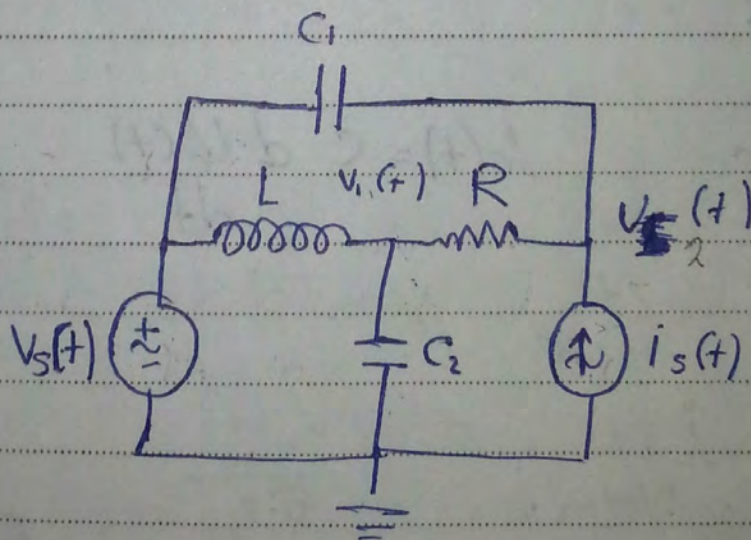
<sup>Ex 20</sup> Ex: write down the nodal equations



Sol/Ex

Node 1 (KCL) :


$$\frac{V_1(t) - V_2(t)}{R} + C_2 \frac{d(V_1(t) - 0)}{dt} + \frac{1}{L} \int_{t_0}^t (V_1(\tau) - V_2(\tau)) d\tau + i_s(t) = 0$$

node 2 (Kcl):

$$-i_s(t) + \frac{v_2(t) - v_1(t)}{R} + C_1 \frac{d(v_2(t) - v_s(t))}{dt} = 0 \quad \text{--- (2)}$$

=> These equations are called Integro-differential equations. It is not easy to solve them.

Ex: if  $v_c(t) = 4 \cos(10^5 t) \text{ V}$ , Find  $v_s(t)$ .

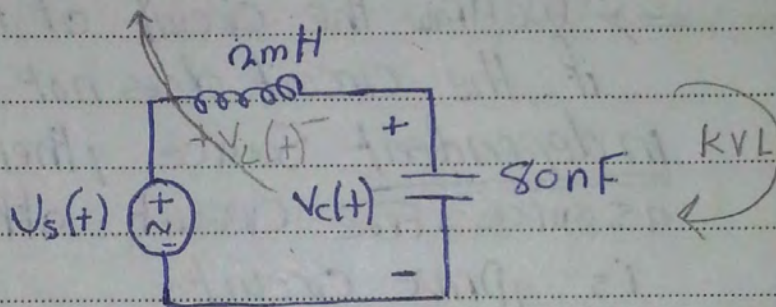
sol<sup>n</sup> =

$$i_s(t) = C \frac{dv_c(t)}{dt} = 80 \times 10^{-9} \times (-4 \times 10^5 \sin(10^5 t)) = -32 \times 10^{-3} \sin(10^5 t) \text{ A}$$

ins

$$v_L(t) = L \frac{di_s(t)}{dt} = 2 \times 10^{-3} \times (-32 \times 10^{-3} \times 10^5 \cos(10^5 t)) = -64 \times 10^{-3} \cos(10^5 t) \text{ V}$$

$$\begin{aligned} v_s(t) &= v_L(t) + v_c(t) \\ &= -64 \cos(10^5 t) + 4 \cos(10^5 t) \\ v_s(t) &= -2.4 \cos(10^5 t) \text{ V} \end{aligned}$$

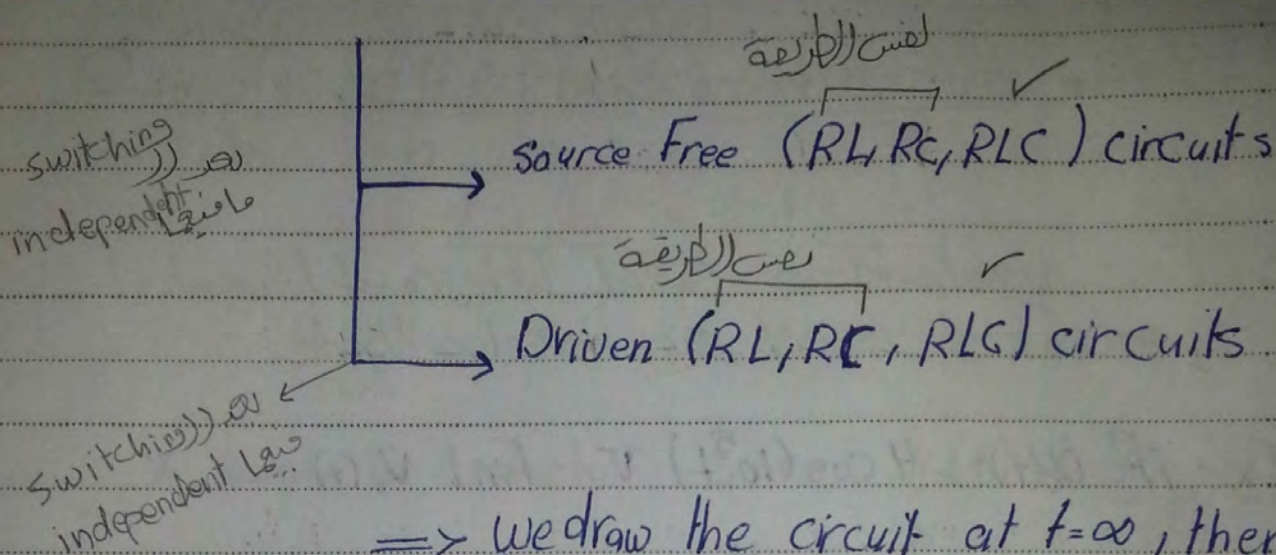\* CH<sub>3</sub>: Transient Analysis 80

⇒ we draw the circuit at  $t = \infty$ , then if the circuit does not have any independent source, then we it is a source-free circuit otherwise, it is a drive circuit.

 $t = \infty$  $t = 0^-$  $t = 0^+$ 

## \* Source Free RL or RC circuit &amp; c

Step 1° at  $t = \infty$ 

⇒ Find the Type of the circuit

⇒ Find the Time constant  $\tau$ .

$$\tau = \frac{L_{eq}}{R_{eq}} \quad (\text{for RL circuit})$$

$$\tau = R_{eq} C_{eq} \quad (\text{for RC circuit})$$

⇒ solution

$$\begin{aligned} \text{any voltage or current on the circuit} & \left[ \begin{aligned} U(t) &= U(0^+) e^{-t/\tau} \\ i(t) &= i(0^+) e^{-t/\tau} \end{aligned} \right. \end{aligned}$$

Subject: .....

9/11/2014

step 2<sub>2c</sub> at  $t=0^-$

$\Rightarrow$  Find the Voltage on the capacitor  $V_c(0^-) \Rightarrow$  For RC circuit

$\Rightarrow$  Find the current on the inductor  $i_L(0^-) \Rightarrow$  For RL circuit

$\Rightarrow$  Find the required Voltage or current.

step 3<sub>3a</sub> at  $t=0^+ = 0$

$\Rightarrow$  replace the capacitor by a voltage source that has a value of  $V_c(0^-)$


$\Rightarrow$  Replace the inductor by a current source that has a value of  $i_L(0^-)$

$\Rightarrow$  Find the required Voltage or current  $V(0^+)$  or  $i(0^+)$

$\uparrow$                        $\uparrow$   
o                              o

ins

Exo Find  $V(t)$  at  $t = 200 \text{ msec}$  :

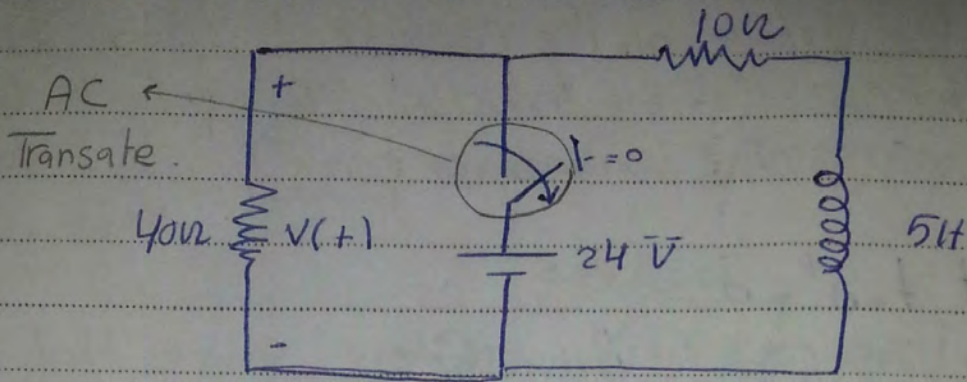


sol 30

$V(t)$  as a function of time After we substitution  $t = 200 \text{ msec}$ .

3 step solution

Step 1:  $t = \infty$

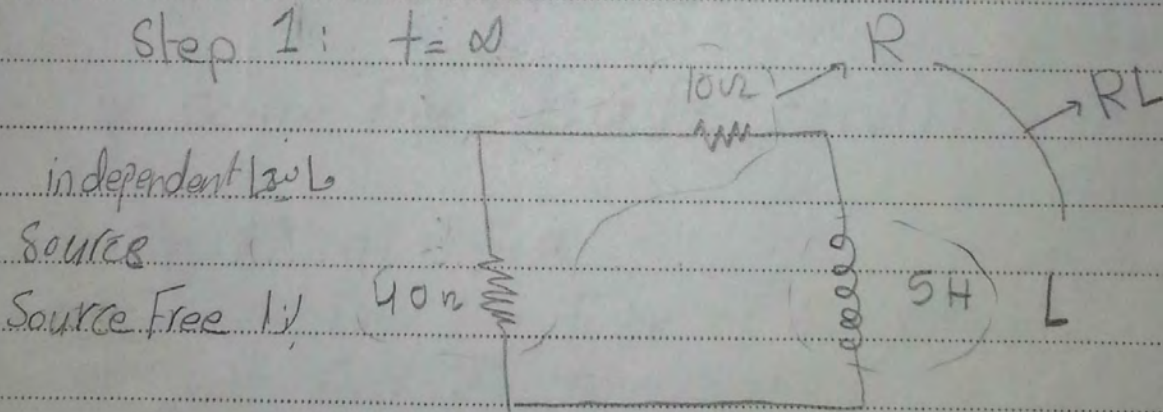


$\Rightarrow$  Typ: source Free RL circuit

$$\Rightarrow \tau = \frac{L_{eq}}{R_{eq}} = \frac{5}{50} = 0.1 \text{ sec}$$

$$\Rightarrow \text{solution: } V(t) = V(0) e^{-t/\tau} \approx (t \geq 0)$$




Step 2:  $t = 0^-$

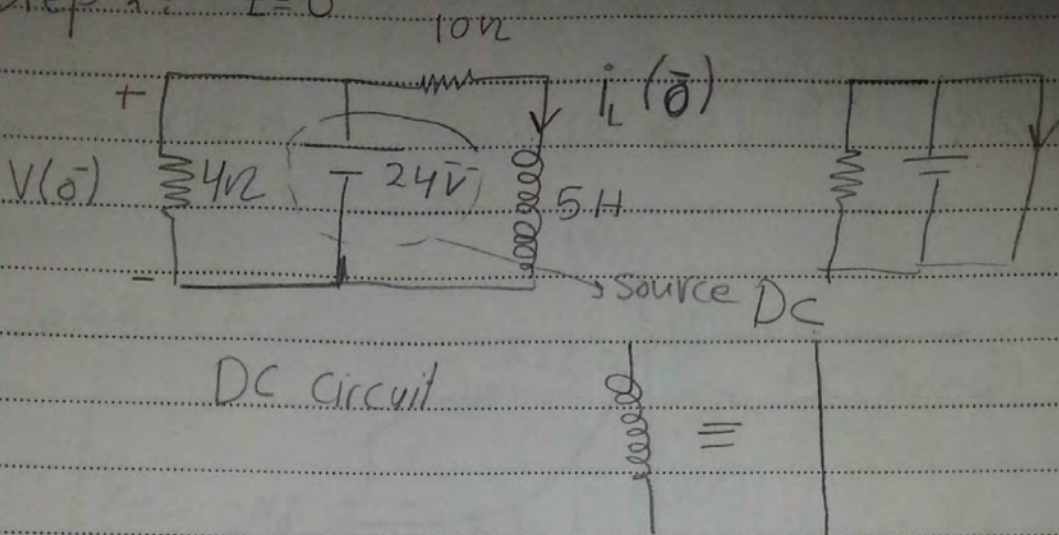

$\Rightarrow V(0^-) = 24 \text{ V}$   
 $\Rightarrow i_L(0^-) = \frac{24}{10} = 2.4 \text{ A}$

Step 3:  $t = 0^+ = 0$

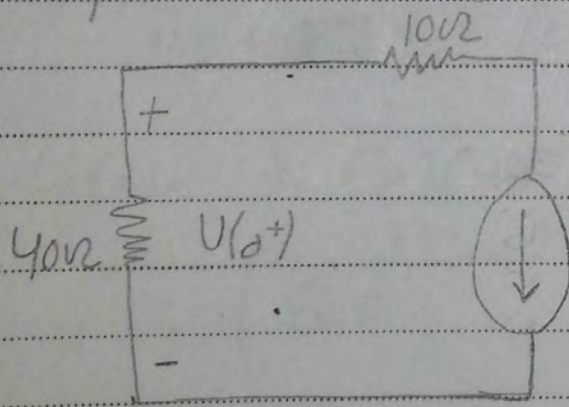


العودة للحالت  
 التي كانت عليها  
 عند التوقيت  
 السابق


$(2.4 \text{ A}) \quad i_L(0) = i_L(0^+) = i_L(0^-)$

$V(0^+) = -40 \times 2.4 = -96 \text{ V}$

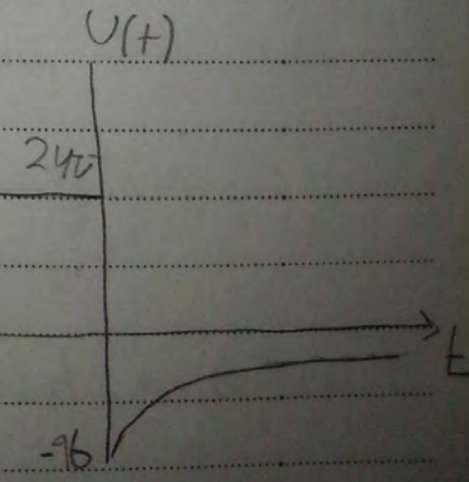
$$V(t) = \begin{cases} 24 \text{ V} & t < 0 \\ -96 e^{-t/\tau} \text{ V} & t \geq 0 \end{cases}$$



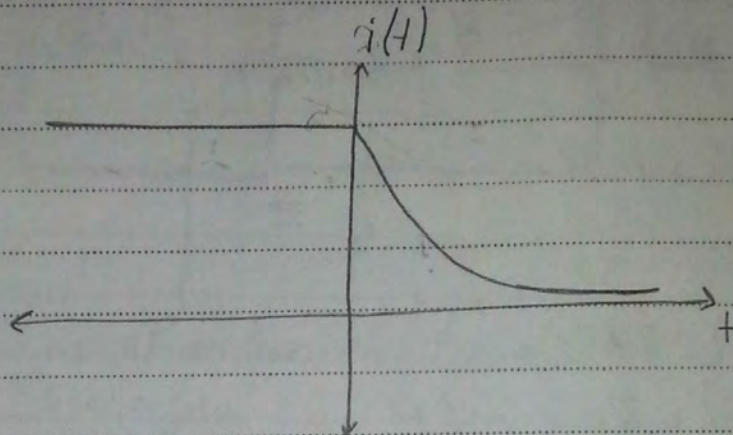
$$i(t) = \begin{cases} 2.4 & , t < 0 \\ 2.4 e^{-t/0.1} & , t \geq 0 \end{cases}$$



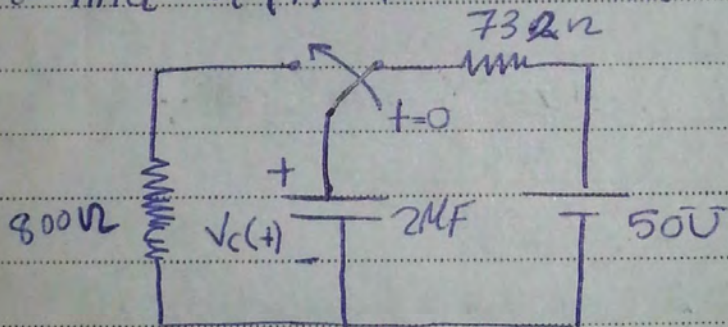Ex<sup>c</sup>: Find  $V_c(t)$  at  $t = 0$  and  $t = 2 \text{ msec}$  :-



Sol<sup>n</sup>: Step 1 :  $t = \infty$

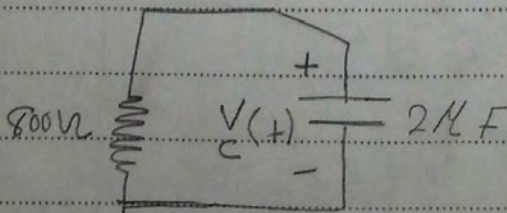

Types Source Free RC circuit


Subject: .....

11/11/2014

$$\Rightarrow \tau = R_{eq} C_{eq} = 800 * 2 \mu F = 1.6 \text{ msec}$$

$$\Rightarrow \text{solution: } V_c = V_c(0^+) e^{-t/\tau} \quad (t \geq 0)$$

step 2:  $t = 0^-$

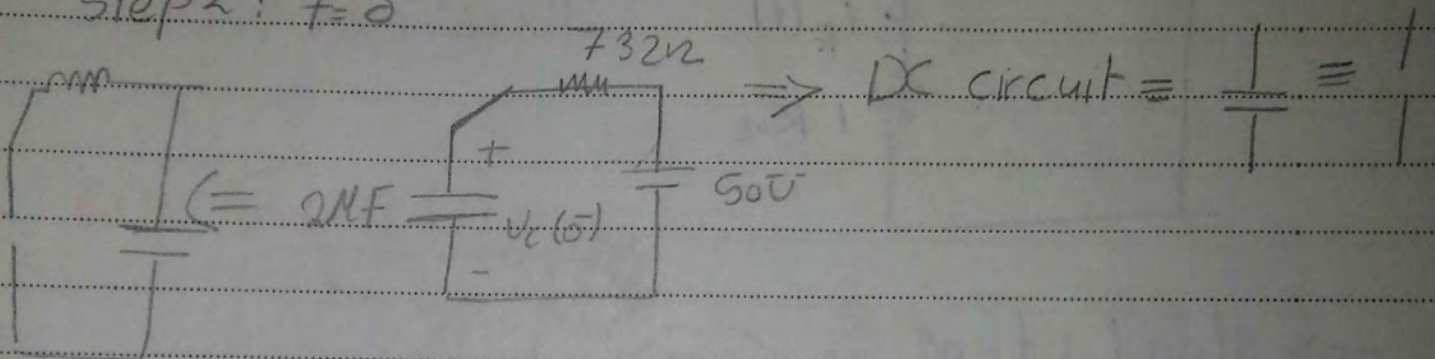


$$V_c(0^-) = 50V$$

step 3:  $t = 0^+$

we know that  $V_c(0^+) = V_c(0^-) = 50V$


$$V_c(t) = \begin{cases} 50V, & t < 0 \\ 50e^{-t/1.6 \times 10^{-3}}, & t \geq 0 \end{cases}$$

دقیق  
درجہ

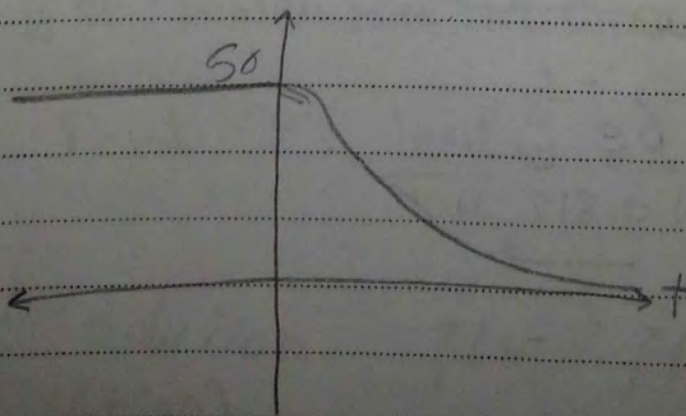

Ex: Find  $i_R(t)$  at  $t = 1 \text{ nsec}$

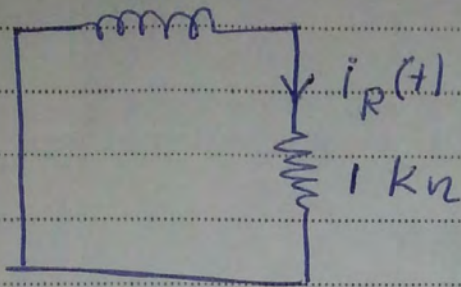step 2 or 3 if  $i_R(0) = 6 \text{ A}$   
 $500 \text{ nH}$



\* Switch or initial condition transit analysis.

$\Rightarrow$  step 1:  $t = \infty$

Type  $\Rightarrow$  Source Free RL circuit

$$\Rightarrow \tau = \frac{L_{eq}}{R_{eq}} = \frac{500 \times 10^{-9}}{1000} = 0.5 \text{ nsecond}$$

$$\Rightarrow \text{solution: } i_R(t) = i_R(0) e^{-t/\tau}$$

$$i_R(t) = 6 e^{-t/0.5 \times 10^{-9}} \quad t \geq 0$$

$$= 6 e^{-\frac{1}{0.5}}$$


$$= 0.812 \text{ A}$$

CH 7: 1, 10, 15, 24, 27, 28, 35, 36, 48, 49, 50

CH 8: 6, 9, 10, 24, 35, 37, 39, 40, 42, 43, 44, 57

\* Mid-term exam to the end of Source-Free RL & RC circuit.

Ex: Find  $i(t)$

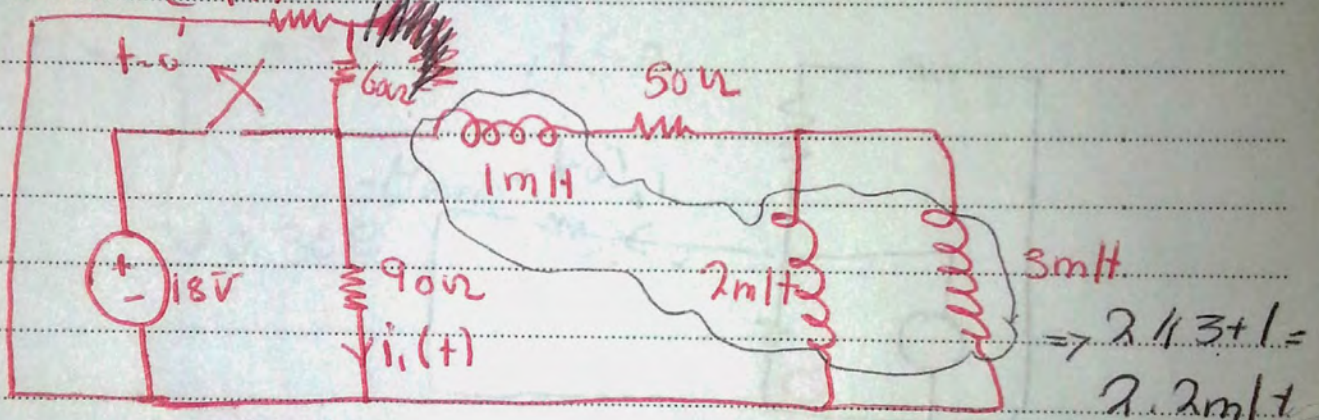

Sol:

$$R_{eq} = (60 + 120) // 90 \Omega = 110 \Omega$$

Step 1:  $t = \infty$

Type: Source Free RL Circuit


$$\text{Find } \tau = \frac{L_{eq}}{R_{eq}} = \frac{2.2}{110} = 20 \text{ msec}$$


⇒ solution  $i(t) = i(0^+) e^{-t/\tau}$  ( $t \geq 0$ )

Subject: .....


13/11/2014

Step 2:  $t = 0^-$

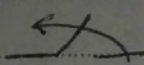 is closed

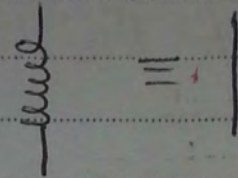$\Rightarrow$  DC circuit  $\Rightarrow$  

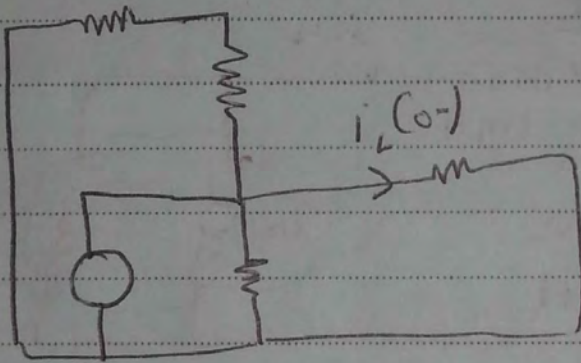
$$\Rightarrow i_L(0^-) = \frac{18}{90} = 0.2 \text{ A}$$



$$\Rightarrow i_L(0^-) = \frac{18}{50} = 0.36 \text{ A}$$

\* Step 3

$t = 0^+ = 0$

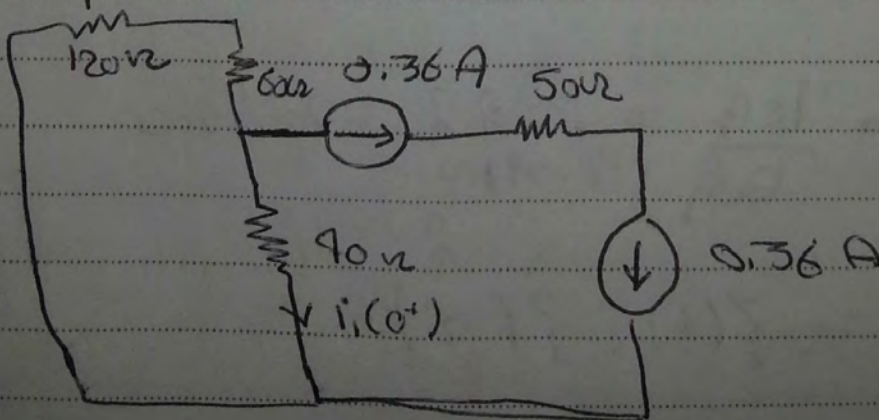

Subject:.....

13/11/2014

$$i_1(0^+) = \frac{-0.36 \times 180}{180 + 90}$$
$$= -0.24 \text{ A}$$

$$i_1(t) = \begin{cases} 0.2 & , t < 0 \\ -0.24 e^{-t/20 \times 10^{-6}} \text{ A} & , t \geq 0 \end{cases}$$

$$i_2(t) = \begin{cases} 0.36 & , t < 0 \\ 0.36 e^{-t/20 \times 10^{-6}} & , t \geq 0 \end{cases}$$




ins

# Given RL and RC circuit

Subject: .....

13/11/2018

Ex. Find  $V_o(t)$

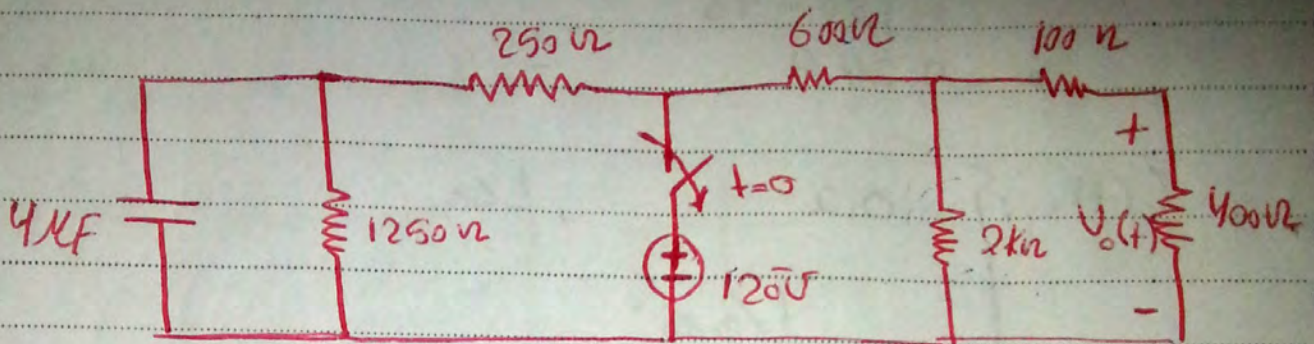

Sol<sup>n</sup>

Step 1:  $t = \infty$



$$R_{eq} = ((100 + 400) // 2 + 600 + 250) // 1250 = 625 \Omega$$

Type  $\Rightarrow$  Source-Free RC circuit

$$\Rightarrow \tau = R_{eq} C_{eq} = 625 * 4 * 10^{-6} = 2.5 \text{ msec}$$

Solution  $V_o(t) = V_o(0^+) e^{-t/\tau}$

Step 2:  $t = 0^-$

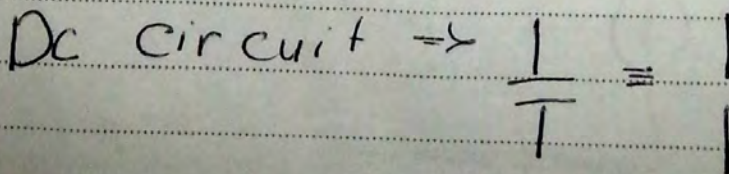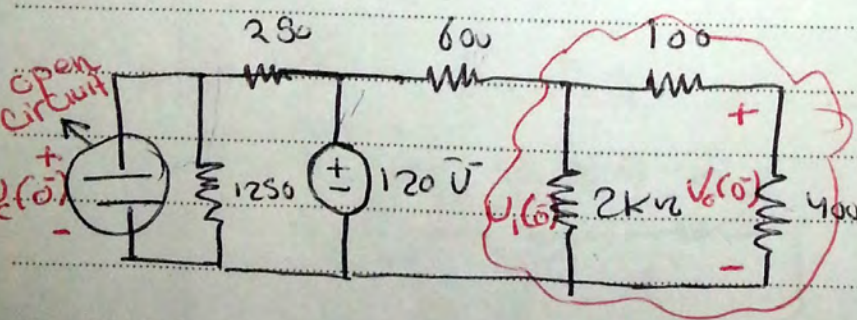






$$\Rightarrow V_c(0^-) = \frac{120 * 1250}{1250 + 250} = 100 \text{ V}$$

$$V_1(0^-) = 120 \frac{400}{400 + 600} = 48 \text{ V}$$

$$V_0(0^-) = V_1(0^-) * \frac{400}{400 + 100} = 38.4 \text{ V}$$

Step 3  $t = 0^+ = 0$

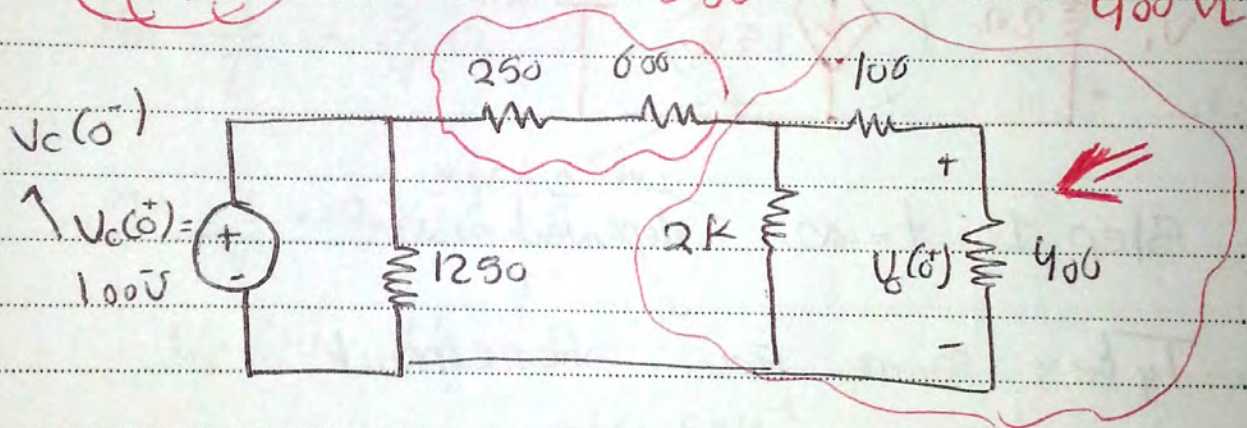

$$V_0(0^+) = V_1(0^+) * \frac{400}{400 + 100}$$


$$V_c(0^+) = 100 * \frac{400}{400 + 850}$$

$$V_0(0^+) = V_0(0^-) = 25.6 \text{ V}$$

$$V_0(t) = \begin{cases} 38.4 \text{ V} & t < 0 \\ 25.6 e^{-t/2.5 * 10^{-3}} & t > 0 \end{cases}$$



$$V_c(t) = \begin{cases} 100 & t < 0 \Rightarrow 0 \\ 100 e^{-t/2.5 \times 10^{-3}} & t \geq 0 \Rightarrow C^* \text{ (initial)} \end{cases}$$

$$i_c(t) = C \frac{dV_c(t)}{dt}$$

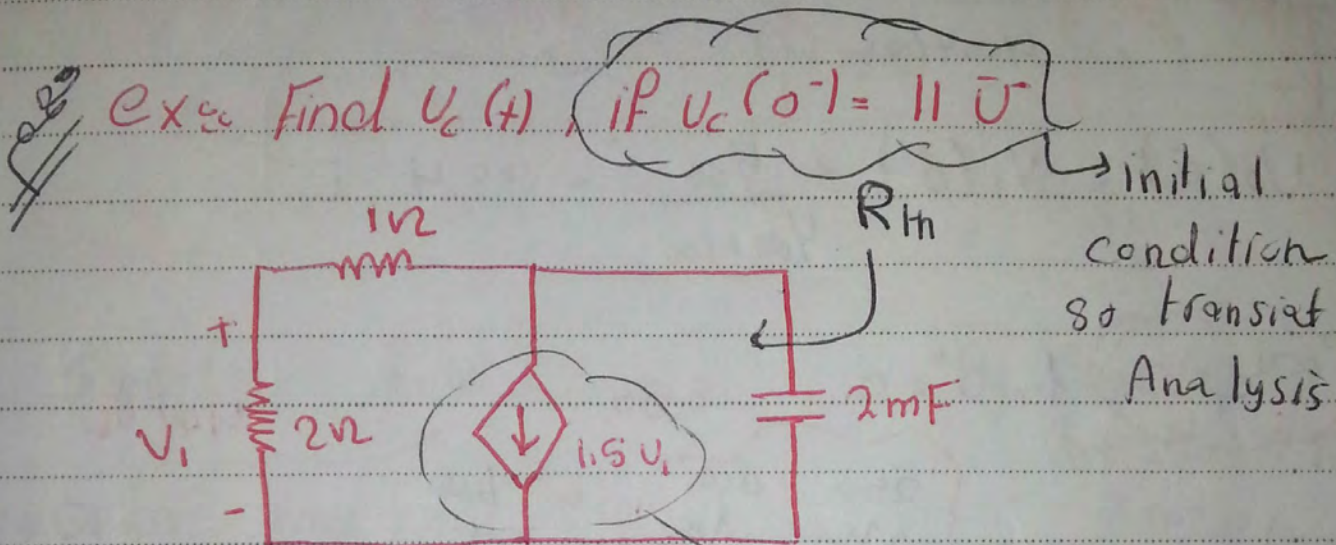

Step 1  $t = \infty$  حالت ديمومة  
 dependent circuit

Type: source free RC circuit

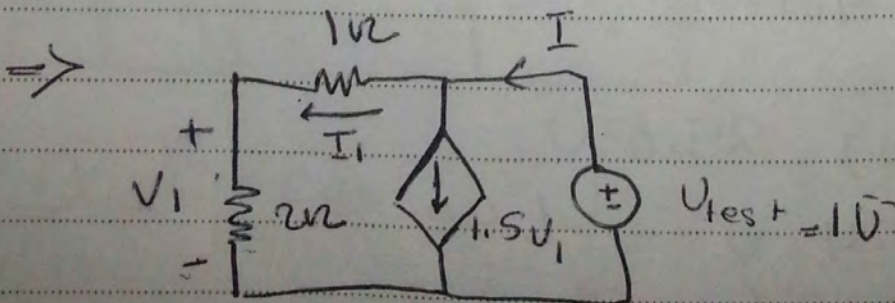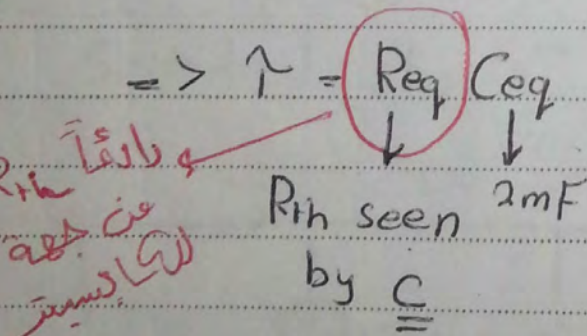

$$R_{th} = \frac{U_{test}}{I} = \frac{1}{I}$$

$$I = \frac{U}{4} + 1.5V$$

$$= \frac{U_{test} - U_1}{1\Omega} + 1.5 \left( U_{test} \times \frac{2}{2+1} \right)$$

$$= \frac{4}{3} A$$


$$R_{th} = \frac{1}{I} = \frac{3}{4} \Omega$$

$$\tau = \frac{3}{4} \times 2 \times 10^{-3} = 1.5 \text{ m sec}$$

$$U_C(t) = U_C(0) e^{-t/\tau}$$

$$U_C(t) = \begin{cases} 11 e^{-t/1.5 \times 10^{-3}}, & t \geq 0 \\ 11, & t < 0 \end{cases}$$

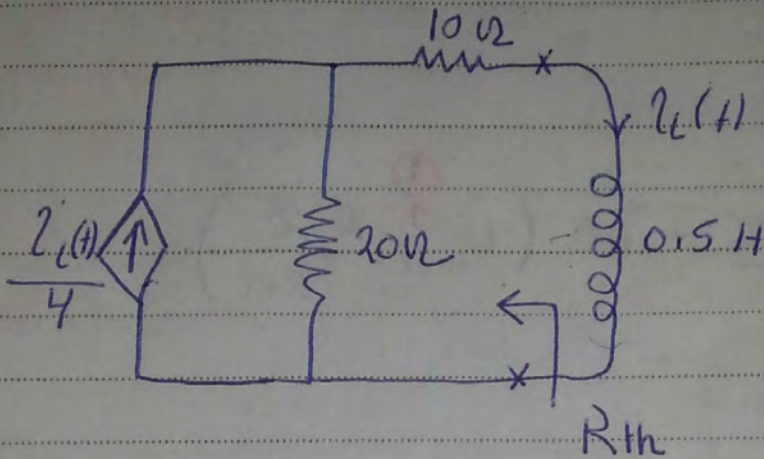Ex: Find  $i_L(t)$ ,  $P_L$   $i_L(0) = 10A$




general case  
 $R_{eq} = R_{th}$

Type 1  
 parallel series

Step 1  $t = \infty$

Type Source-Free RL Circuit
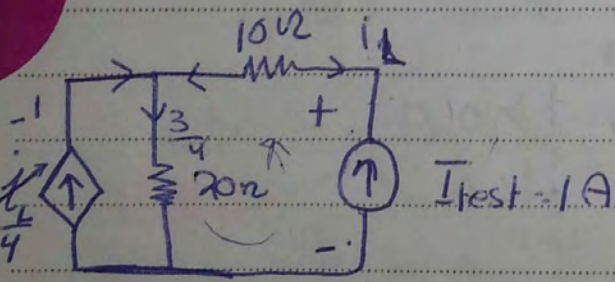
$$\Rightarrow \tau = \frac{L_{eq}}{R_{eq}} = \frac{0.5}{R_{th}}$$



$$R_{th} = \frac{V}{I_{test}} = \frac{V}{1}$$

KVL  $\frac{3}{4} * 20 - V + 1 * 10 = 0$

$V = 25V$

$$\therefore \tau = \frac{0.5}{25} = 0.02 \text{ sec}$$


$$\Rightarrow i_L(t) = \frac{i_L(0^+)}{10} e^{-t/\tau} \quad \tau = 0.02$$

$$(t \geq 0)$$


$$i_L(t) = \begin{cases} 10 & , t < 0 \\ 10 e^{-t/0.02} & , t \geq 0 \end{cases}$$

\* Time constant ( $\tau$ )

Current or Voltage

it is the time required for a response to reach zero if it  at its initial decaying rate decreases

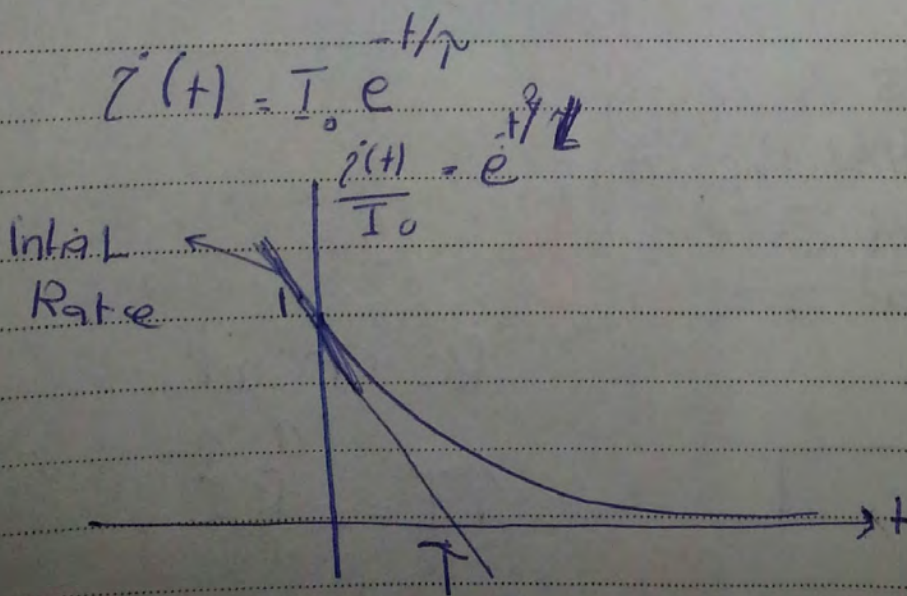$\Rightarrow$  For source free RL(circuit) :



$$\text{initial rate} = \left. \frac{d \frac{v(t)}{I_0}}{dt} \right|_{t=0} = \left. -\frac{1}{\tau} e^{-\frac{t}{\tau}} \right|_{t=0} = \boxed{\frac{-R}{L}}$$

$$-\frac{R}{L} = \text{slope} = \frac{1-0}{0-\tau}$$

initial Rate slope

$$\frac{-R}{L} = \frac{1}{-\tau} \Rightarrow \tau = \frac{L}{R}$$

$$i_L(\tau) = 36.8\% I_0$$

$$i_L(2\tau) = 13.53\% I_0$$



$$i_L(3\tau) = 4.9\% I_0$$

$$i_L(4\tau) = 0.832\% I_0$$

$$i_L(5\tau) = 0.6738\% I_0$$

we can say that the current is almost zero


استقرت  
لا يكون رائحة  
discharge

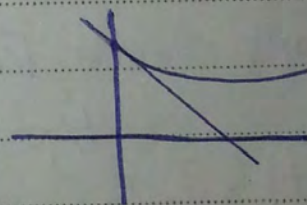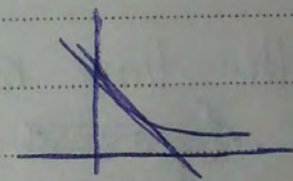

Ex مدار التوقيت

RC circuit

$$\tau = RC$$

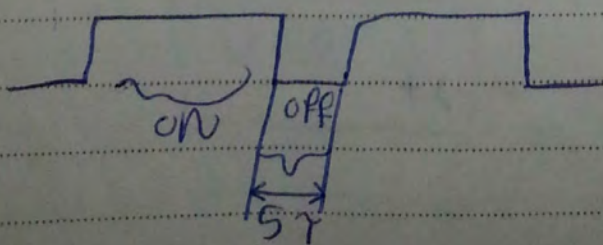

# Driven RL and RC circuit

Step 1 =  $t = \infty$

$\Rightarrow$  Type: if there is an independent source,  
then Driven circuit

$$\text{Find } \tau = \frac{L_{eq}}{R_{eq}} \quad | \quad T = R_{eq} C_{eq}$$

$$\Rightarrow \text{solution} \Rightarrow i(t) = \underbrace{i(\infty)}_{\text{forced response}} + \underbrace{(i(0) - i(\infty)) e^{-t/\tau}}_{\text{natural response}}$$

$\Rightarrow$  find  $i(\infty)$

Step 2:  $t = 0^-$

Same as For source-free circuit

Step 3:  $t = 0^+$



Same as For source-free circuit.

# \* Singularity Functions

Function that have discontinuous derivatives.

① unit step function  $u(t)$



② unit impulse function  $\delta(t)$

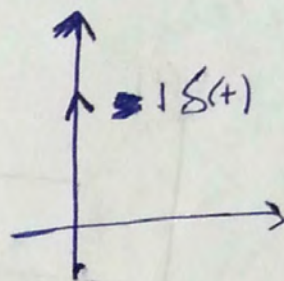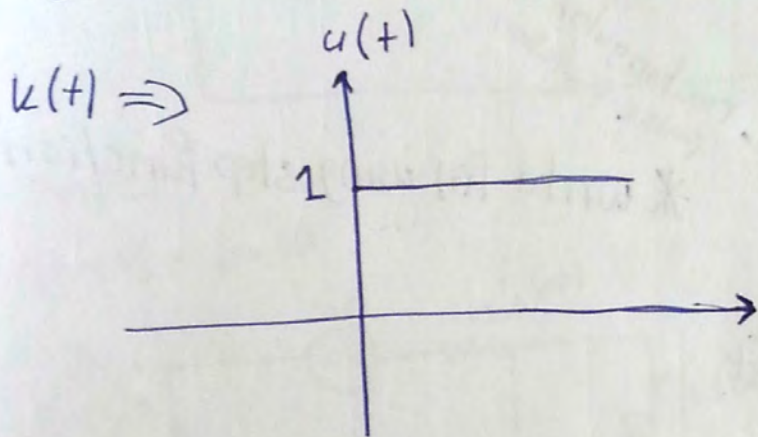



$$\Rightarrow u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \\ \text{undefined}, & t = 0 \end{cases}$$

Ex 3

3.1  $u(t)$

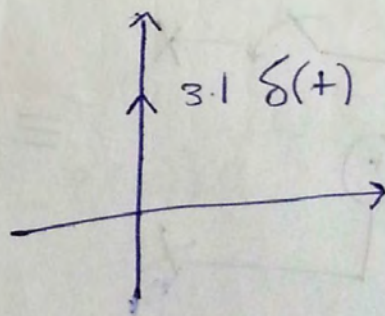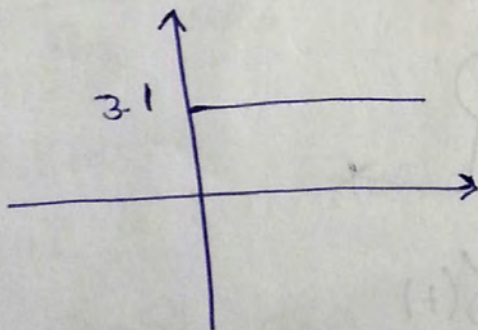


Ex 4  $4u(t-3)$

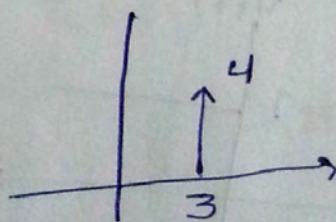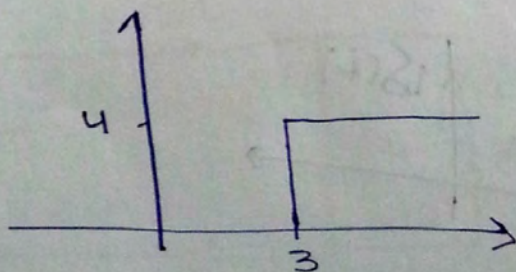




Ex 1.  $-2u(t+1)$


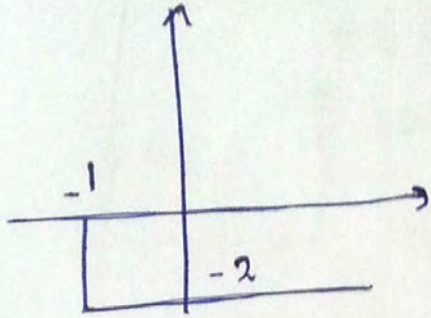


rectangular pulse function  
\* write  $f(t)$  using step function?

Ex


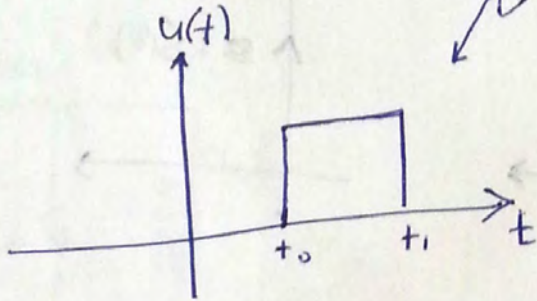


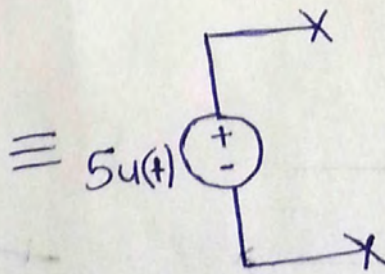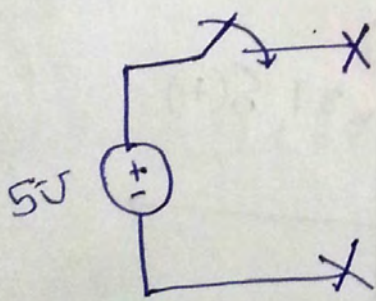Sol<sup>n</sup>:  $f(t) = U_m u(t-t_0) - U_m u(t-t_1)$




② unit impulse function  $\delta(t)$

$$\delta(t) = \frac{du(t)}{dt}$$

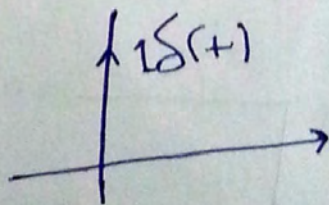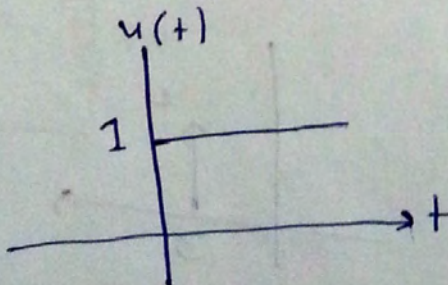


Ex: Find  $i_L(t)$

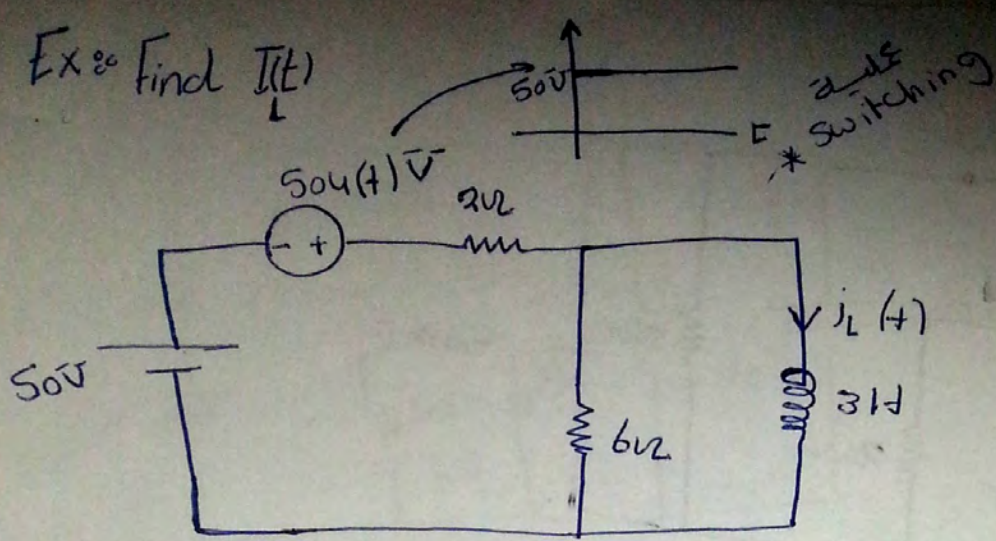

Sol: 30

Step 1:  $t = \infty$

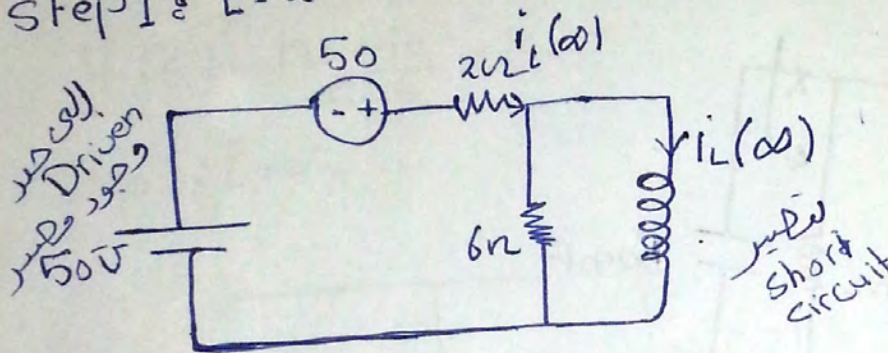

50V(t) عند التحويل Short circuit 50 Volt

Short circuit

⇒ Type: Driven RL Circuit

$$\Rightarrow \tau = \frac{L_{eq}}{R_{eq}} = \frac{3}{2 \parallel 6} = \frac{3 \times 6}{2 + 6} = 2 \text{ sec}$$


⇒ Solution:  $(t \geq 0)$

$$i_L(t) = i_L(\infty) + (i_L(0^+) - i_L(\infty)) e^{-t/\tau}$$

$$i_L(\infty) = \frac{50 + 50}{2} = 50 \text{ A}$$


$$i_L(0^-) = \frac{50}{2} = 25 \text{ A} = i_L(0^+)$$

Step 2:  $t = 0^-$

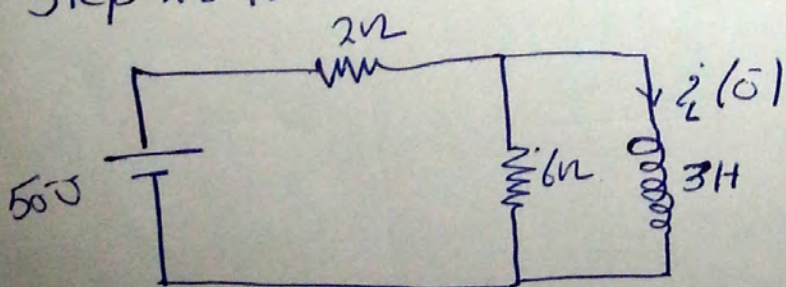


$$i_L(t) = \begin{cases} 25, & t < 0 \\ 50 + (25 - 50)e^{-t/2}, & t \geq 0 \end{cases}$$

Ex: find  $i(t)$

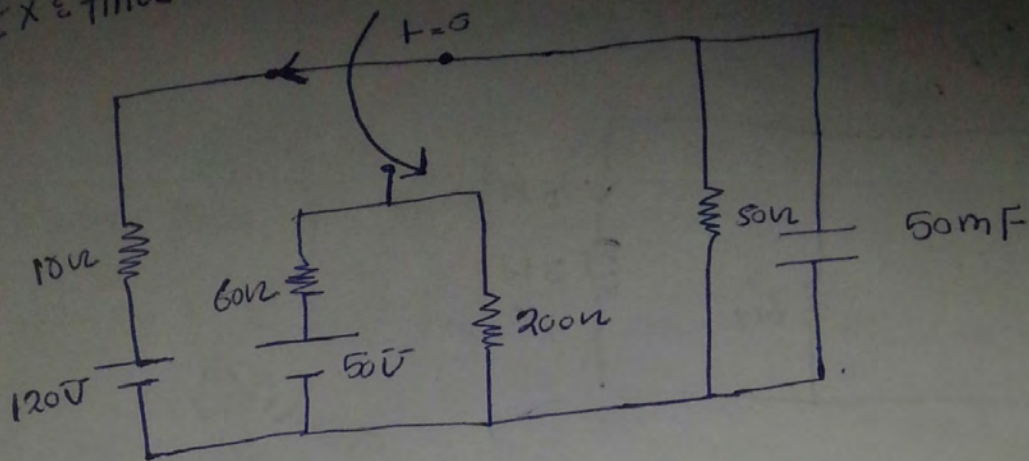

\* step 1:  $t = \infty$

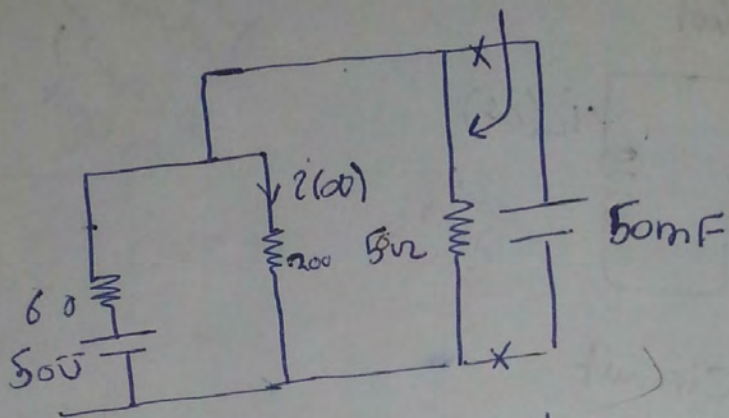

$\Rightarrow$  Type: Driven RC circuit

$$\Rightarrow \tau = R_{eq} C_{eq} = (60 \parallel 200 \parallel 50) * 50 = 1.2 \text{ sec}$$


$$\Rightarrow \text{solution: } i(t) = i(\infty) + (i(0) - i(\infty)) e^{-t/\tau}$$

$$\Rightarrow i(\infty) = 22$$

$$U_{200\Omega} = 50 * \frac{(50 \parallel 200)}{(50 \parallel 200 + 60)}$$

$$i(\infty) = \frac{U_{200\Omega}}{200} = 0.1 \text{ A}$$


Step:  $t=0^-$

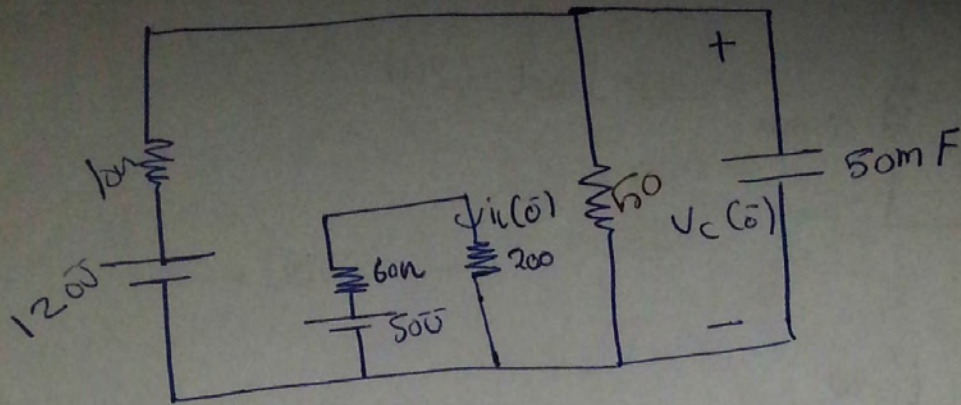

$$i(0^-) = \frac{50}{60+200} = 0.1923 \text{ A}$$

$$V_c(0^-) = \frac{120 \times 50}{50+10} = 100 \text{ V}$$


Step 3:  $t=0^+ = 0$

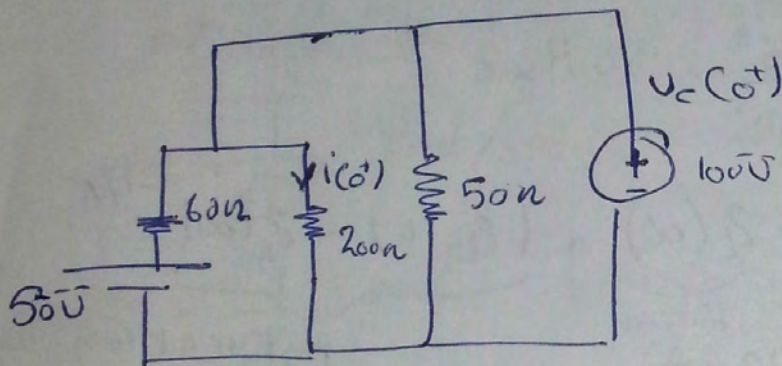

$$i(0^+) = \frac{100}{200} = \frac{1}{2} \text{ A}$$

$$i(t) = \begin{cases} 0.1923 \text{ A} & , t < 0 \\ 0.1 + (0.5 - 0.1)e^{-t/1.2} & , t \leq 0 \end{cases}$$


Ex 2

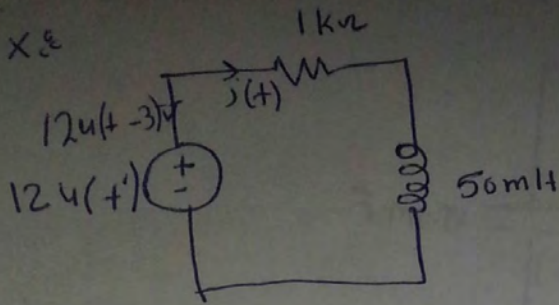

Find  $i(t)$

$$\Rightarrow t' = t - 3$$

$\Rightarrow$  step at  $t' = \infty$

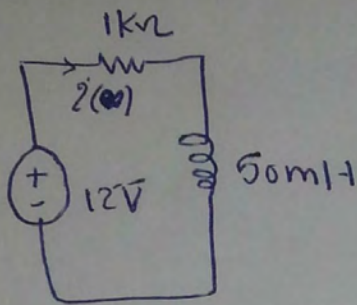


Driven  
 $\Rightarrow$  Type 2  $\uparrow$  RL circuit

$$\Rightarrow \tau = \frac{L_{eq}}{R_{eq}} = \frac{50 \times 10^{-3}}{1 \times 10^3} = 50 \text{ Msec}$$

$$\Rightarrow \text{solution } i_L(t) = \underbrace{i_L(\infty)}_{\text{Forced}} + \underbrace{(i_L(0) - i_L(\infty)) e^{-t/\tau}}_{\text{natural response}}$$

$$i_L(\infty) = \frac{12}{1 \text{ km}} = 12 \text{ nA}$$

\* step 2  $t' = 0^-$

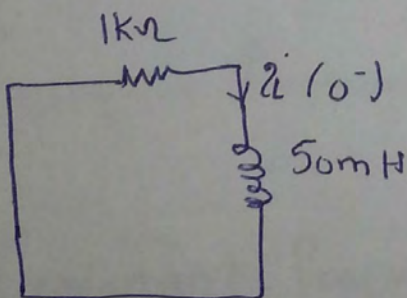


$$i_L(0^-) = 0 \text{ A}$$

$$i_L(0^-) = i_L(0^+)$$

$$i_L(t) = \begin{cases} 0, & t < 0 \\ 12 - 12e^{-t'/\tau}, & t' \geq 0 \end{cases}$$

$$i_L(t) = \begin{cases} 0, & t < 3 \\ 12 - 12e^{-\frac{t-3}{50 \times 10^{-6}}}, & t \geq 3 \end{cases}$$


\* RLC Circuit  $\epsilon_c$

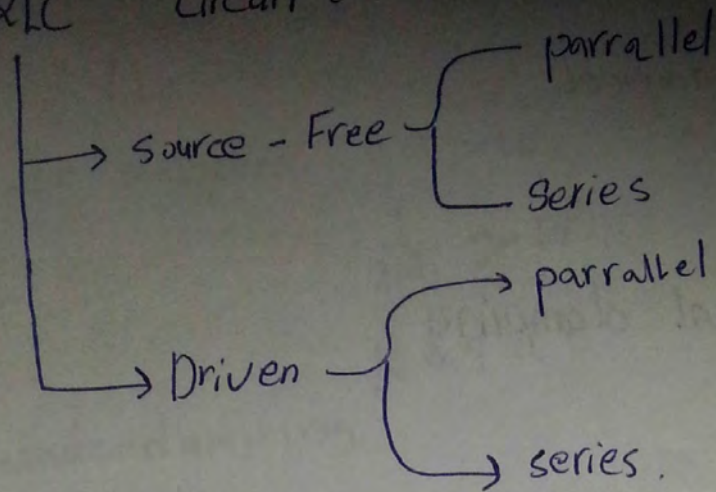

\* source-Free RLC  $\epsilon_c$

Step 1  $\Rightarrow t = \infty$

$\Rightarrow$  Type  $\epsilon_c$

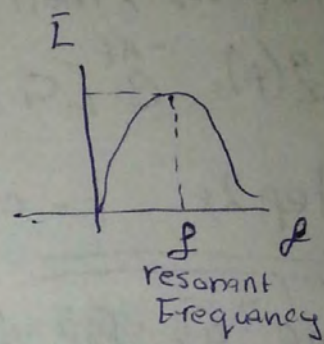

$\Rightarrow$  Find The following parameter  $\epsilon_c$

\*  $\omega_c = \frac{1}{\sqrt{LC}}$  rad/sec (resonant Frequency)  $\epsilon_c$  ظاهرة الرنين  
 \* response Max  $\epsilon_c$

\*  $\alpha = \frac{1}{2RC}$  sec $^{-1}$  (parallel)  $\Rightarrow$  (Nepor Frequency) ظاهرة الرنين  
 or (exponential damping coefficient)

\*  $\alpha = \frac{R}{2L}$  sec $^{-1}$  (series)

\*  $s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$   
 \*  $s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$  } complex frequency

\*  $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$  natural resonant Frequency

\*  $\zeta \Rightarrow \frac{\alpha}{\omega_0}$  damping factor on  
 Zeta

⇒ Solution:  $t \geq 0$

\* if  $\alpha > \omega_0$ , then overdamped

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

\* if  $\alpha = \omega_0$ , then critical damping


$$i(t) = B_1 t e^{-\alpha t} + B_2 e^{-\alpha t}$$

\* if  $\alpha < \omega_0$ , then underdamped

$$i(t) = e^{-\alpha t} [C_1 \cos(\omega_d t) + C_2 \sin(\omega_d t)]$$

\* step 2:  $t = 0^-$

same as for RL circuit  
or RC

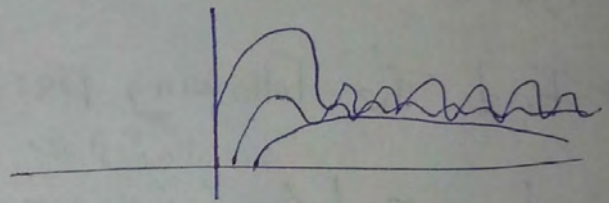

\* step 3:  $t = 0^+$

same as for RL circuit  
or RC

Ex: a parallel RLC circuit

Given  $L = 10 \text{ mH}$ ,  $C = 100 \text{ } \mu\text{F}$ , Find  $R$  such that:

① overdamping response

② underdamping

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} = 10^3 \text{ rad/sec}$$

$\Rightarrow$  over damped  $\alpha > \omega_0$

$$\frac{1}{2RC} > 10^3$$

$$R < 5 \Omega$$

$\Rightarrow$  underdamping

$$\Rightarrow \alpha < \omega_0$$

$$\frac{1}{2RC} < 10^3 \Rightarrow R > 500$$

$\Rightarrow$  critical damp

$$R = 0$$

Ex: if  $R = 100 \Omega$ ,  $\alpha = 1000 \text{ sec}^{-1}$  (parallel RLC)

$\omega_0 = 800 \text{ rad/sec}$ , find  $L, C, s_1, s_2$

$$\Rightarrow \alpha = \frac{1}{2RC} \Rightarrow C = 5 \mu\text{F}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow L = 312.5 \text{ mH}$$

$$\Rightarrow s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -400 \text{ sec}^{-1}$$


$$\Rightarrow s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -1600 \text{ sec}^{-1}$$

$\Rightarrow$  overdamping  $\Rightarrow s_1$  and  $s_2$  are negative real number

$\Rightarrow$  critical damping  $\Rightarrow s_1 = s_2 = -\alpha$




Ex 9. Find  $v_c(t)$  and  $i_R(t)$ .

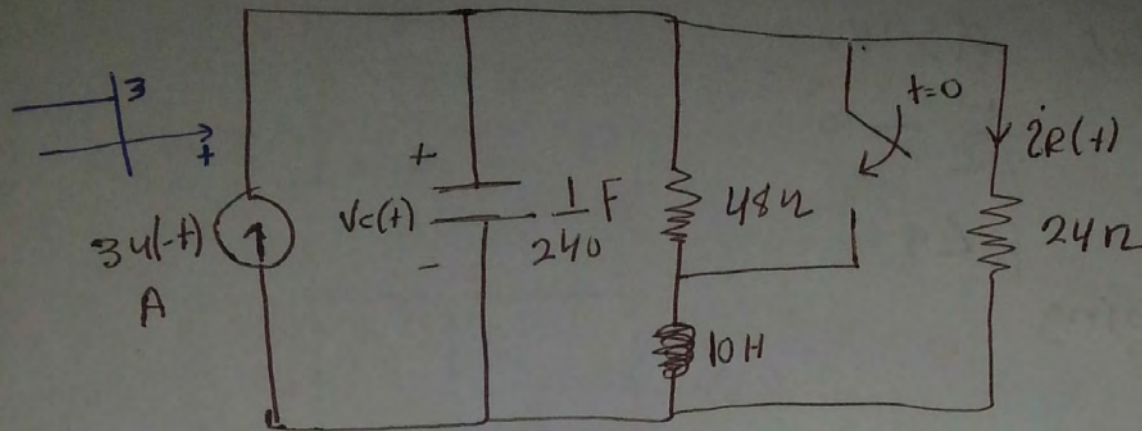

Sol<sup>9</sup> Transient analysis  $\Rightarrow$  3 steps solution

Step 1  $t = \infty$

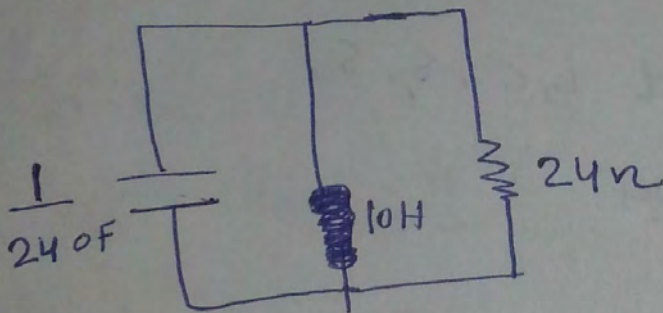

$\Rightarrow$  Type  $\Rightarrow$  Source-Free parallel RLC circuit

$\Rightarrow$  parameters

$$\omega_0 = \frac{1}{\sqrt{LC}} = \sqrt{24} \text{ rad/sec}$$

$$\alpha = \frac{1}{2RC} = 5 \text{ sec}^{-1}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -4 \text{ sec}^{-1}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -6 \text{ sec}^{-1}$$


→ solution  $\varepsilon_0$   $\alpha > \omega_0 \Rightarrow$  overdamping

$t \geq 0$

$$v_c(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$i_R(t) = B_1 e^{s_1 t} + B_2 e^{s_2 t}$$

step 2  $t = 0^-$

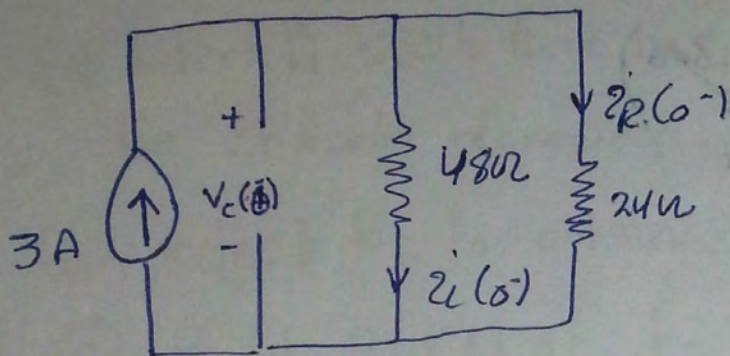


$$\Rightarrow i_L(0^-) = \frac{3 * 24}{24 + 48} = 1A$$

$$\Rightarrow i_R(0^-) = 2A$$

$$\Rightarrow v_c(0^-) = 48 * 1 = \underline{\underline{48V}}$$

step 3  $t = 0^+ = 0$

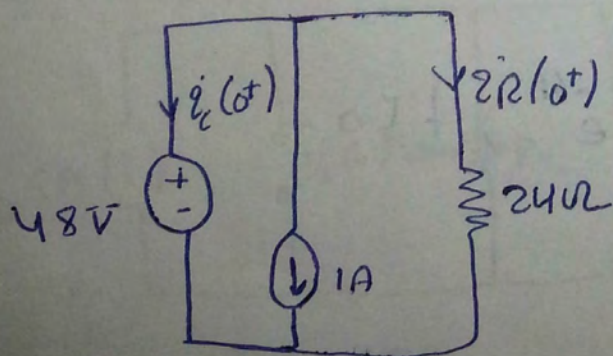

$$i_R(0^+) = \frac{48}{24} = 2A$$

$$\boxed{i_c(0^+) = -3A}$$

$$V_c(t) = A_1 e^{-4t} + A_2 e^{-6t}$$

$$V_c(0^+) = A_1 + A_2$$

$$\boxed{48 = A_1 + A_2} \quad \text{--- (1)}$$

$$\Rightarrow i_c(0^+) = C \frac{dV_c(t)}{dt} \Big|_{t=0}$$

$$-3 = \frac{1}{240} (-4A_1 e^{-4 \cdot 0} - 6A_2 e^{-6 \cdot 0})$$

$$\boxed{-3 = \frac{1}{240} (-4A_1 - 6A_2)} \quad \text{--- (2)}$$



$$\star A_1 = -216$$

$$\star A_2 = 264$$

$$V_c(t) = \begin{cases} 48 \text{ V} & t < 0 \\ -216e^{-4t} + 264e^{-6t} & t > 0 \end{cases}$$

$$i_p(t) = \frac{V_c(t)}{24} \Rightarrow \begin{cases} 2 \text{ A} & , t < 0 \\ -9e^{-4t} + 11e^{-6t} & , t > 0 \end{cases}$$

Ex 20

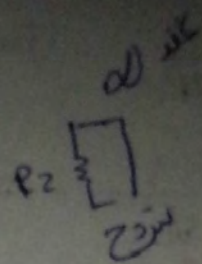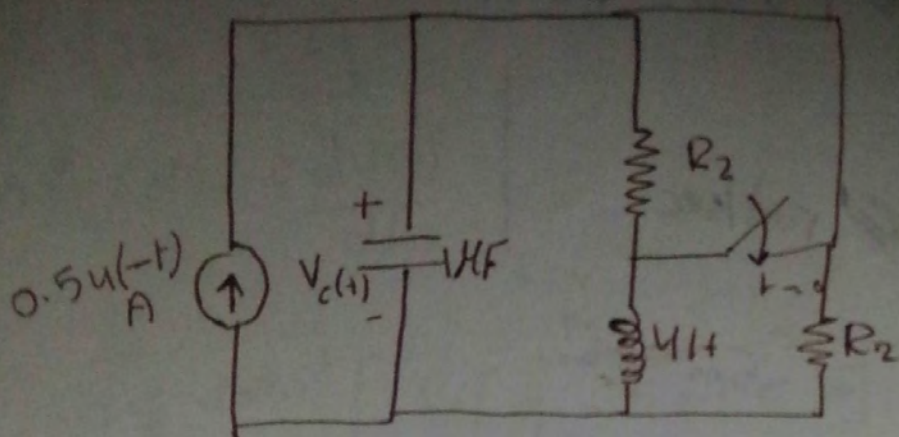

(a) select  $R_1$  such that the response after  $t=0$  will be critically damped


(b) select  $R_2$  to obtain  $V_c(0) = 100 \text{ V}$

(c) Find  $V_c(t)$  at  $t = 1 \text{ msec}$ .

Sol: ...

(a)  $\alpha = \omega_0$   
 $\frac{1}{2R_1C} = \frac{1}{\sqrt{LC}} \Rightarrow R_1 = 1 \text{ k}\Omega$

(b)  $V_c(0) = 100 \text{ V}$

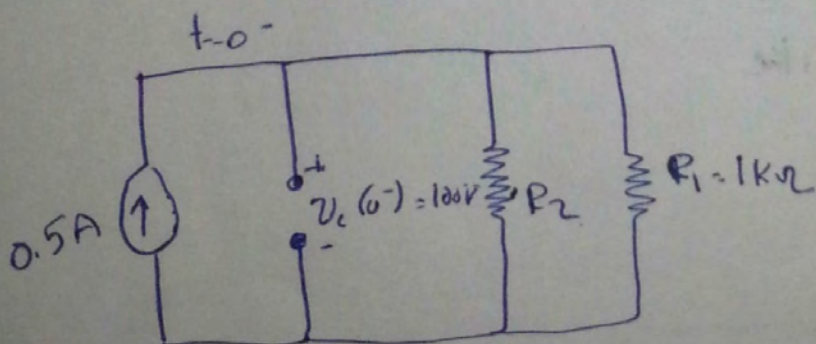

$I_{R_1} = \frac{100}{1k} = 0.1 \text{ A}$

$I_{R_2} = 0.4 \text{ A} = \frac{100}{R_2} \Rightarrow R_2 = 250$

ⓐ step 1 :  $t = \infty$

⇒ Type : source-free Parallel RLC.

$$\alpha = \frac{1}{2RC} = 500 \text{ sec}^{-1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 500 \text{ rad/sec}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -500 \text{ sec}^{-1}$$


$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -500 \text{ sec}^{-1}$$

Solution :  $\alpha = \omega_0 \Rightarrow$  critical damping

$$v_c(t) = B_1 e^{-\alpha t} + B_2 t e^{-\alpha t}$$


step 2 :  $t = 0^-$

We know that  $v_c(0^-) = 100 \text{ V}$

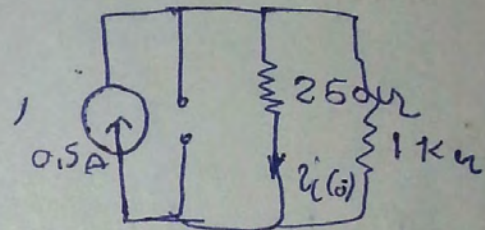

$$i_c(0^-) = \frac{0.5 \times 1 \text{ k}\Omega}{250 + 1 \text{ k}\Omega} = 0.4 \text{ A}$$

step 3 :  $t = 0^+$

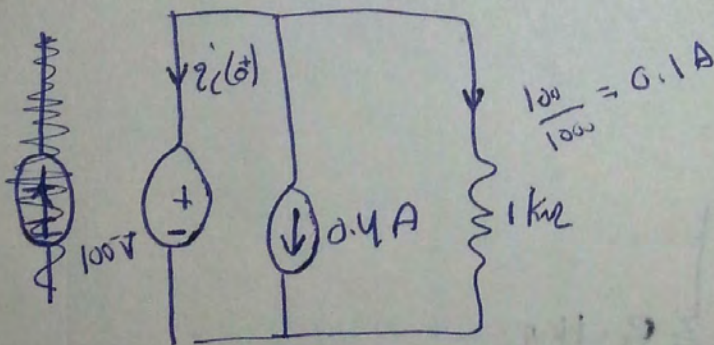

$$i_c(0^+) = -0.5 \text{ A}$$

$$\Rightarrow v_c(t) = B_1 e^{-500t} + B_2 e^{-500t}$$

$$\Rightarrow \boxed{100 = B_2}$$


$$\Rightarrow i_c(t) = \left. \frac{dv_c(t)}{dt} \right|_{t=0}$$

$$-0.5 = 1 \times 10^{-6} \left[ B_1 \left[ e^{-500t} - 500t e^{-500t} \right] - 500 B_2 e^{-500t} \right]_{t=0}$$


$$\Rightarrow B_1 = -4.5 \times 10^6$$

$$\Rightarrow v_c(t) = \begin{cases} 100 & t < 0 \\ -4.5 \times 10^6 e^{-500t} + 100 e^{-500t} & t \geq 0 \end{cases}$$


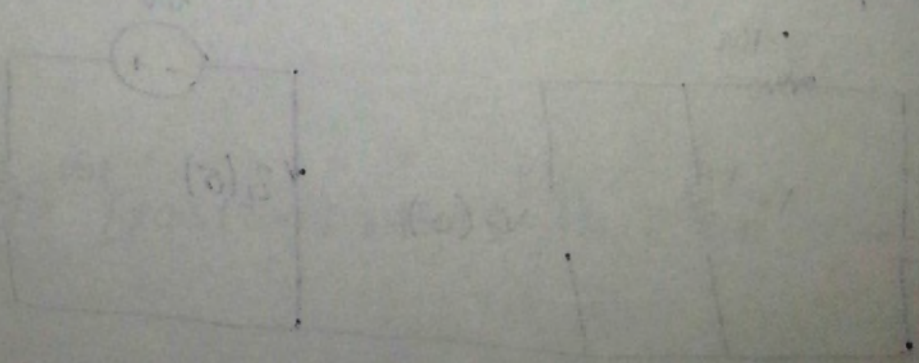
$$v_c(t=1 \text{ msec}) = -212 \text{ V}$$



Ex: Find  $V_C(t)$  &  $i_L(t)$

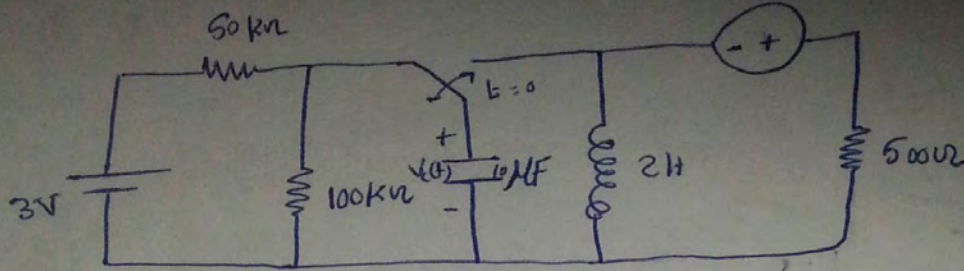

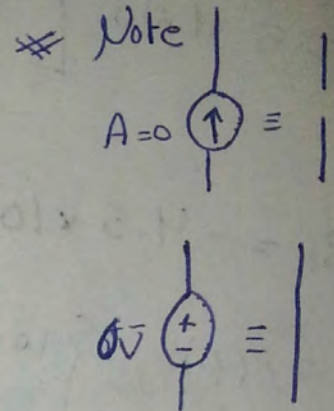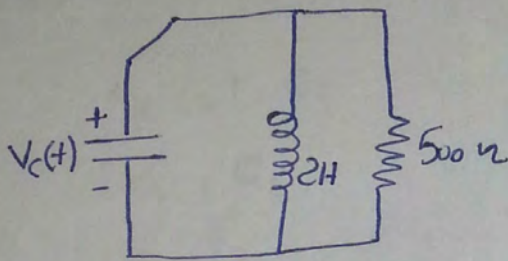⇒ Step 1 at  $t = \infty$  ⇒ Switch ⇒ Transient analysis ⇒ 3 step sol



⇒ Type 1 & Source Free parallel RLC-Circuit


⇒ parameter &  $\omega_0 = \frac{1}{\sqrt{LC}} = 223.6 \text{ rad/sec}$

$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 500 \times 10 \text{ kF}} = 100 \text{ sec}^{-1}$

under damping  
س مازوفا

$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 200 \text{ rad/sec}$


⇒ Step 2 & at  $t = 0^-$

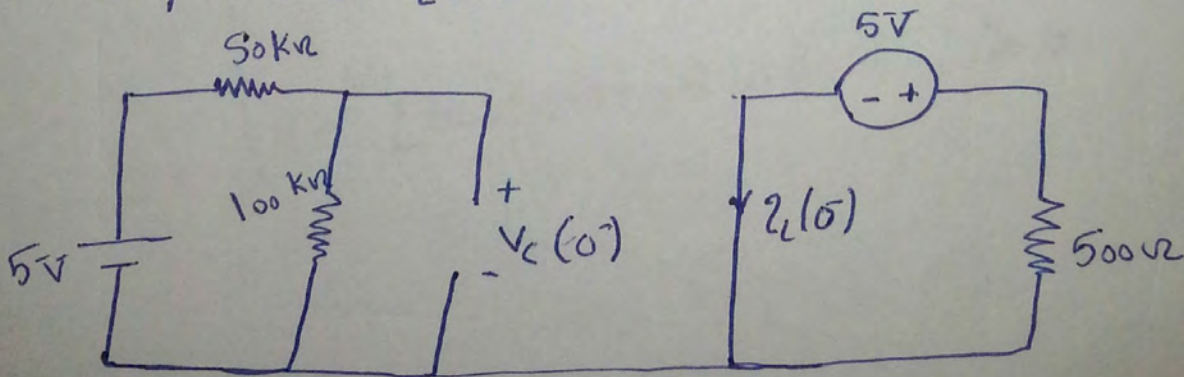

$$V_c(0^-) = 3 + \frac{100}{150} = 2V$$

$$i_c(0^-) = \frac{-5}{500} = -0.01A$$

⇒ step 3 at  $t = 0^+ = 0$

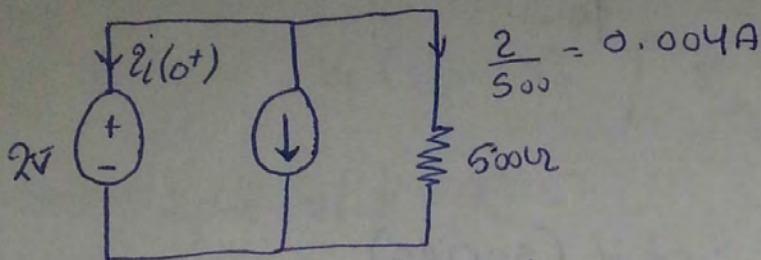

$\alpha > \omega_0$  under damping

⇒ solution:  $V_c(t) = e^{-\alpha t} [C_1 \cos(\omega_d t) + C_2 \sin(\omega_d t)]$

$$V_c(0) = C_1$$

$$2 = C_1$$

$$i_c(0^+) = C \frac{dV_c(t)}{dt}$$


$$0.006 = 10 \times 10^{-6} [-\alpha e^{-\alpha t} [C_1 \cos(\omega_d t) + C_2 \sin(\omega_d t)] + e^{-\alpha t} [-C_1 \omega_d \sin(\omega_d t) + C_2 \omega_d \cos(\omega_d t)]]$$

$$C_2 = 4$$

$$V_c(t) = \begin{cases} 2V & , t < 0 \\ e^{-100t} [2\cos(200t) + 4\sin(200t)], & t \geq 0 \end{cases}$$




Ex 80 Find  $v_c(t)$  & 0

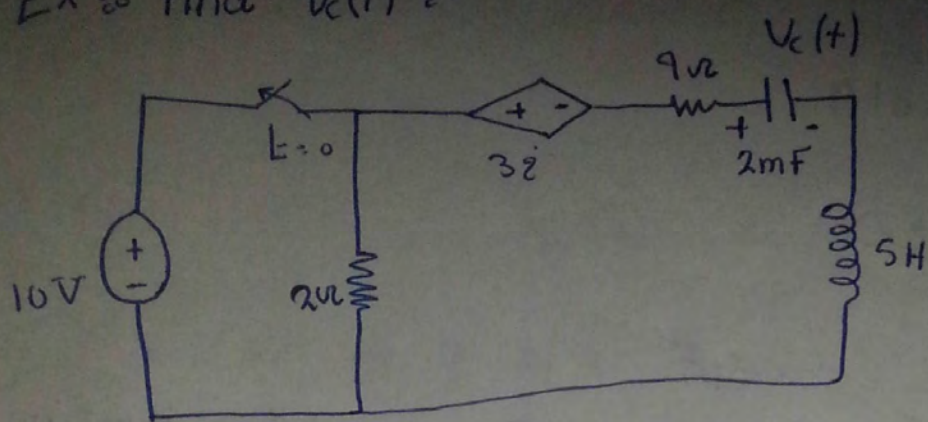

Step 1 at  $t = \infty$


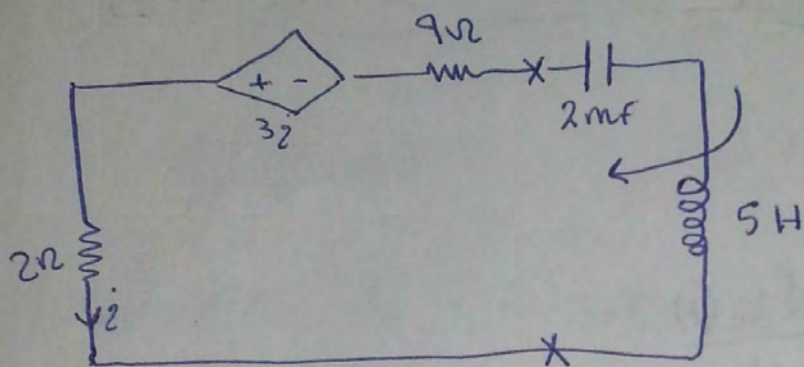
$\Rightarrow$  Type & source-free-RLC-circuit (series)



$\Rightarrow$  parameters:  $\omega_0 = \frac{1}{\sqrt{LC}} = 10 \text{ rad/sec}$

$$\alpha = \frac{R_{th}}{2L} = 0.8 \text{ sec}^{-1}$$

$R_{th} \Rightarrow$  Type 3

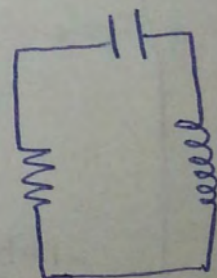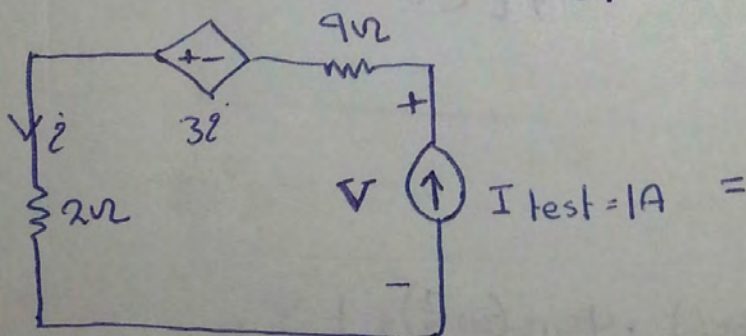

$$\text{KVL: } -V - 3 \times 1 + 2 \times 1 + 9 \times 1 = 0$$

$$V = 8V \Rightarrow R_{th} = \frac{8}{1} = 8\Omega$$


$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 9.96 \text{ rad/sec}$$

Solution is underdamping  $\alpha > \omega_0$

$$t \geq 0$$

$$V_c(t) = e^{-\alpha t} [C_1 \cos(\omega_d t) + C_2 \sin(\omega_d t)]$$

$\Rightarrow$  step 2 at  $t = 0^-$

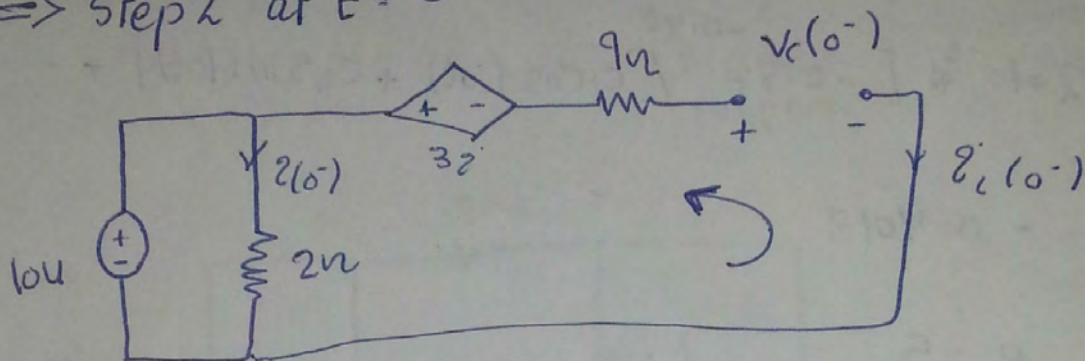


$$i_c(0^-) = 0 \text{ A} \quad i(0^-) = \frac{10}{2} = 5 \text{ A}$$

$$\text{KVL } \varepsilon: -V_c(0^-) - 3 \cdot 5 + 10 = 0$$

$$V_c(0^-) = -5 \text{ V}$$

$\Rightarrow$  step 3 at  $t = 0^+ = 0$

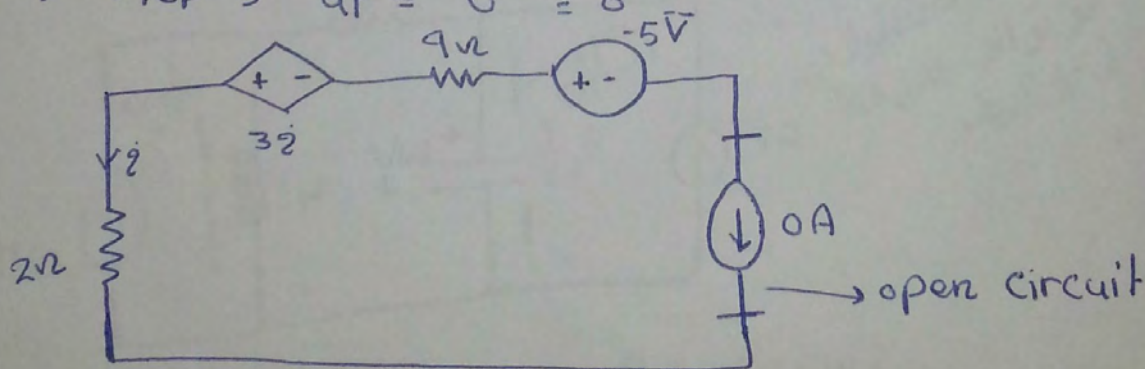

$$i_c(0^+) = 0 \text{ A}$$

Solution  $\varepsilon_0$

$$v_c(t) = e^{-0.8t} [C_1 \cos(10t) + C_2 \sin(10t)]$$

$$v_c(0) = C_1$$


$$-5 = C_1$$

$$i_c(t) = C \frac{dv_c(t)}{dt}$$

$$0 = 2 \times 10^{-3} [-0.8 e^{-0.8t} [C_1 \cos(10t) + C_2 \sin(10t)] + -$$

$$C_2 = -0.4013$$
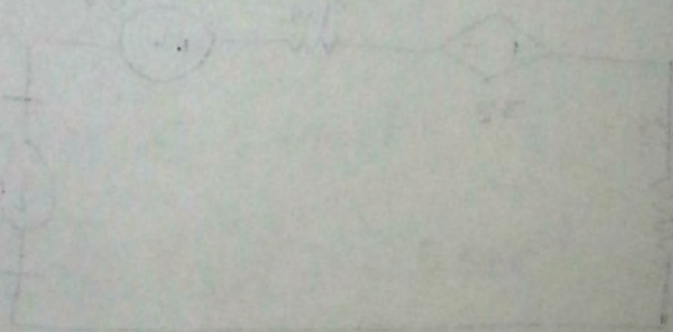
$$v_c(t) = \begin{cases} -5 & , t < 0 \\ e^{-0.8t} [-5 \cos(10t) - 0.4013 \sin(10t)] & , t \geq 0 \end{cases}$$



# Driven RLC circuit


steps of solution all the same of source free RLC circuit

but  $\omega$

over damping  $\omega < \alpha$   $v(t) = v(\infty) + A_1 e^{s_1 t} + A_2 e^{s_2 t}$


Critical damping  $\omega = \alpha$   $v(t) = v(\infty) + A_1 t e^{-\alpha t} + A_2 e^{-\alpha t}$

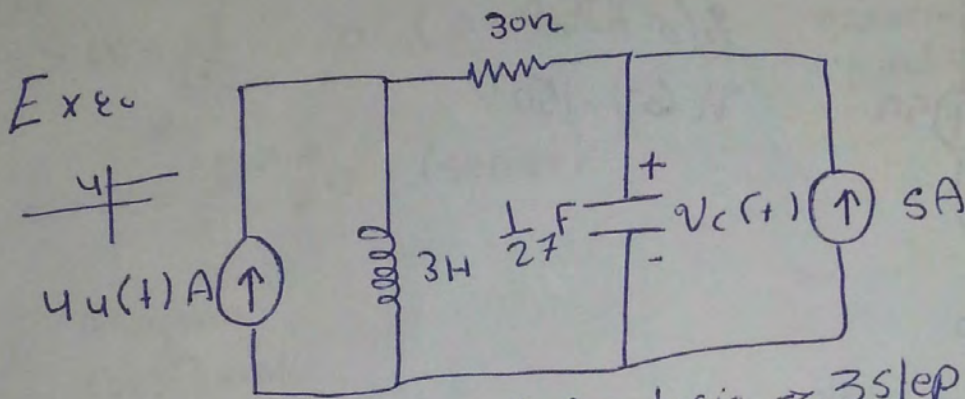under damping  $\omega > \alpha$   $v(t) = v(\infty) + e^{-\alpha t} [A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)]$   
 Forced response                      natural response



$\Rightarrow v(t) \Rightarrow$  Transient Analysis  $\Rightarrow$  3 step solution

Step 1 =  $t = \infty$

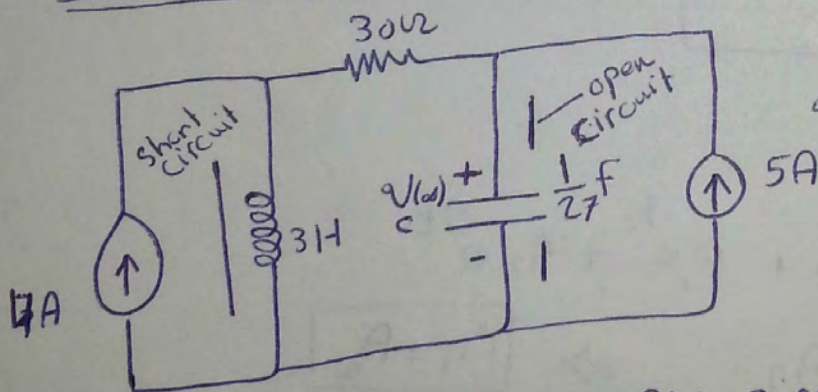

از ابتدا ظرف تواری  
 تو توالتی سلف کلا  
 یک الی

$\Rightarrow$  Type : Driven series RLC circuit

$\Rightarrow$  parameters:  $\alpha = \frac{R}{2L} = \frac{30}{2 \times 3} = 5 \text{ sec}^{-1}$

$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{3 \times \frac{1}{27}}} = 3 \text{ rad/sec}$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -5 + \sqrt{25 - 9} = -1 \text{ sec}^{-1}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -5 - \sqrt{25 - 9} = -9 \text{ sec}^{-1}$$


$\Rightarrow$  Solution:  $\alpha > \omega_0 \Rightarrow$  over damped.

$$v_c(t) = v_c(\infty) + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$-v_c(\infty) + 5 \times 30 = 0$$

$$v_c(\infty) = 150 \text{ V}$$


Step 2  $\Rightarrow t = 0^-$

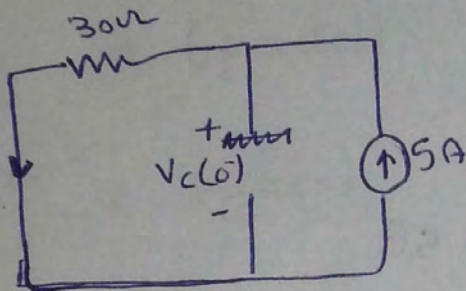

$$i_c(0^-) = 5 \text{ A}$$

$$v_c(0^-) = 150 \text{ V}$$

Step 3  $\Rightarrow t = 0^+ = 0$

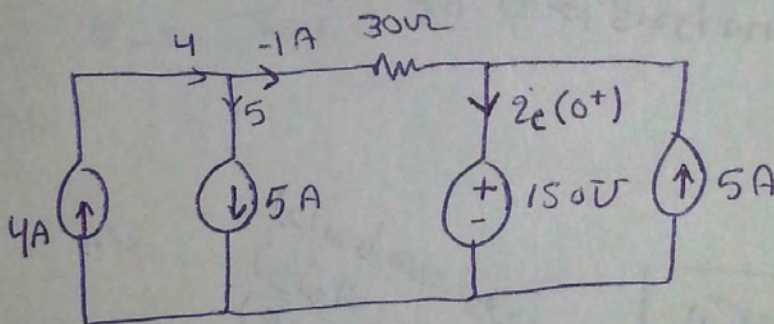

$$i_c(0^+) = 4 \text{ A}$$

Solution:  $v_c(t) = 150 + A_1 e^{-t} + A_2 e^{-9t}$

$$v_c(0) = 150 + A_1 + A_2$$

$$\Rightarrow A_1 \neq A_2$$

$$i_c(t) = 0 + (-A_1 e^{-t} - 9A_2 e^{-9t})$$

$$i_c(t) = C \frac{dv_c(t)}{dt}$$

$$4 = \frac{1}{27} [-A_1 e^{-t} - 9A_2 e^{-9t}]$$

From (1) and (2)

$$A_1 = 13.5$$

$$A_2 = -13.5$$

$$v_c(t) = \begin{cases} 150, & t < 0 \\ 150 + 13.5e^{-t} - 13.5e^{-9t}, & t \geq 0 \end{cases}$$

$$150 + 13.5e^{-t} - 13.5e^{-9t}, t \geq 0$$

\* Lossless LC circuit :

if  $R = \infty$  in the parallel RLC circuit

if  $R = 0$  in the series RLC circuit


$$\Rightarrow \alpha = \frac{1}{2RC} = 0 \text{ (parallel)}$$

$$\Rightarrow \alpha = \frac{R}{2L} = 0 \text{ (series)}$$

↓  
damping  
coefficient

$\Rightarrow$  Since  $\alpha = 0$  There is no damping

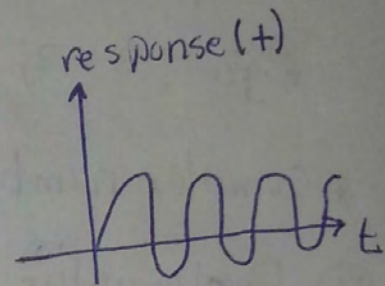Theorem <sup>موجودة</sup>  
practically <sup>مستحالة</sup> \*



Review complex numbers

$\Rightarrow X^2 = -1 \Rightarrow X = \sqrt{-1}$   
 $X = j \Rightarrow$  imaginary operator

$\Rightarrow j^2 = -1, j^3 = -\sqrt{-1} = -j, j^4 = 1, \frac{1}{j} = -j$

$\Rightarrow$  Imaginary number = real number  $\times j$


e.g.  $3j, -3 \cdot 1j, 4j$

$\Rightarrow$  Complex number = real number + Imaginary number

e.g.  $3 + 3j, -2.1 + j2.4, 3j, -5 + 1.5j$

\* Complex number can be represented using two forms

① Rectangular Form:  $\vec{X} = a + jb$

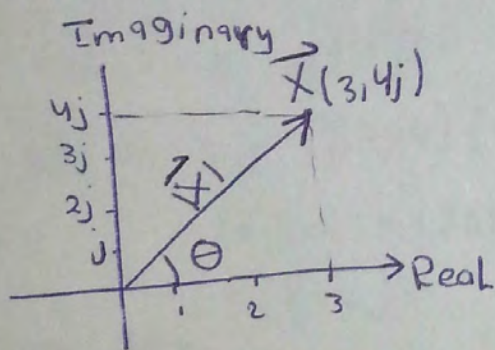

$e^{j\theta} = \cos\theta + j\sin\theta$

Ex:  $\vec{X} = 3 + j4$

② polar Form:  $\vec{X} = |\vec{X}| e^{j\angle \vec{X}}$

Ex:  $\vec{X} = 3 + j4$  (rectangular form)

$|\vec{X}| = \sqrt{3^2 + 4^2}$  (polar Form)

$\vec{X} = 5 e^{j \tan^{-1} \frac{4}{3}}$

$\angle \vec{X} = \tan^{-1} 4$

Ex:  $\vec{X} = 3.1 e^{j30^\circ}$

find  $\vec{X}$  in rectangular form?

$$\vec{X} = 3.1 \cos(30^\circ) + j 3.1 \sin(30^\circ)$$

Ex:  $\vec{X} = 4 e^{j50}$

$$\Rightarrow \vec{X} = 4 \cos(50^\circ) + j 4 \sin(50^\circ)$$

Notes:  $\vec{X} = -5.39 e^{-j21.8^\circ}$

means  $\pm 180^\circ$   
 $\vec{X} = 5.39 e^{+j(-21.8^\circ - 180^\circ)} = 5.39 e^{-j201.8^\circ}$

$$\vec{X} = +5.39 e^{j(-21.8^\circ + 180^\circ)} = 5.39 e^{j158.2^\circ}$$

\* Mathematic operations:

if  $\vec{X} = 3 + j4$  ,  $\vec{Y} = 2 - j5$

①  $\vec{X} + \vec{Y} = 5 - j$

②  $\vec{X} - \vec{Y} = 1 + j9$

③  $\vec{X} \times \vec{Y} = (3 + j4)(2 - j5)$   
 $= 3 \times 2 - j 3 \times 5 + j 4 \times 2 + 20$   
 $= 26 - j7$

④  $\vec{X}^* \equiv$  Conjugate of  $\vec{X}$

$$\vec{X}^* = 3 - j4$$

Note:

①  $\vec{X} + \vec{X}^* = 2 \times 3 = 6$

②  $\vec{X} - \vec{X}^* = j 2 \times 4 = j8$

③  $\vec{X} * \vec{X}^* = (3 + j4)(3 - j4)$   
 $= 3^2 + 4^2$

$\vec{X} * \vec{X}^* =$  real number



$$\textcircled{5} \frac{\vec{X}}{y} = \frac{3+j4}{2-j5}$$

$$\begin{aligned} &= \frac{(3+j4)(2+j5)}{(2-j5)(2+j5)} = \frac{6+j15+j8-20}{2^2+5^2} \\ &= \frac{-14+j23}{29} = \frac{-14}{29} + j\frac{23}{29} \end{aligned}$$

part ③ can be solved using polar form

$$\vec{X} = 3+j4 = 5 e^{j \tan^{-1} \frac{4}{3}}$$

$$\vec{y} = 2-j5 = \sqrt{29} e^{j \tan^{-1} \frac{-5}{2}}$$

$$\Rightarrow \vec{X} * \vec{y} = 5\sqrt{29} e^{j(\tan^{-1} \frac{4}{3} + \tan^{-1} \frac{-5}{2})}$$

$$\Rightarrow \frac{\vec{X}}{y} = \frac{5 e^{j \tan^{-1} \frac{4}{3}}}{\sqrt{29} e^{j \tan^{-1} \frac{-5}{2}}} = \frac{5}{\sqrt{29}} e^{j(\tan^{-1} \frac{4}{3} - \tan^{-1} \frac{-5}{2})}$$

Exe. if  $\vec{X} = 3 e^{j60^\circ}$        $\vec{y} = 4 e^{j45^\circ}$

Find  $\vec{X} + \vec{y} \Rightarrow$

$$\vec{X} = 3 \cos(60^\circ) + j 3 \sin(60^\circ)$$

$$\vec{y} = 4 \cos(45^\circ) + j 4 \sin(45^\circ)$$


$$\vec{X} + \vec{y} = (3 \cos 60^\circ + 4 \cos 45^\circ) + j(3 \sin 60^\circ + 4 \sin 45^\circ)$$


Exe<sup>o</sup>  $e^{j90^\circ} = j$        $e^{j360^\circ} = 1$



$$e^{j180^\circ} = -1$$

$$e^{j270^\circ} = -j$$


$$e^{j360 \times 2} = 1$$

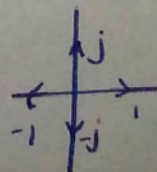

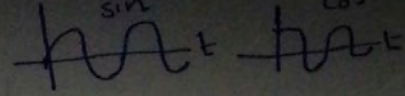\* Sinusoidal signal  $\epsilon_0$  

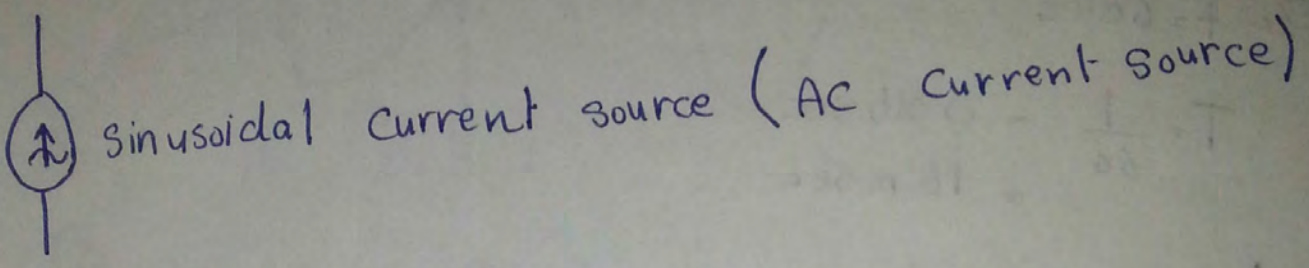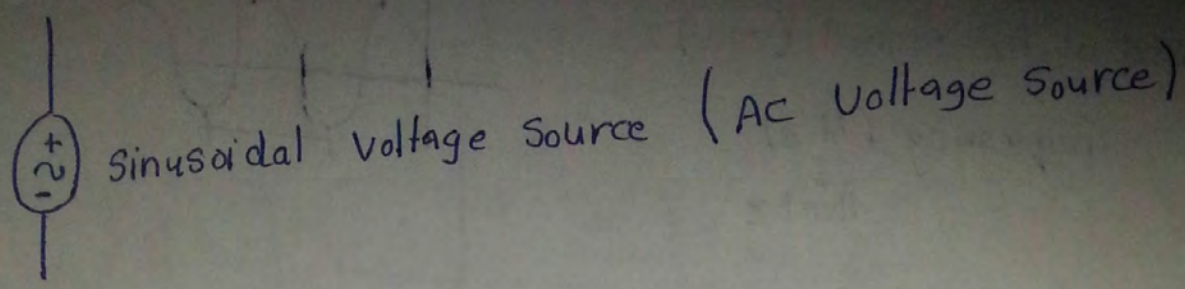

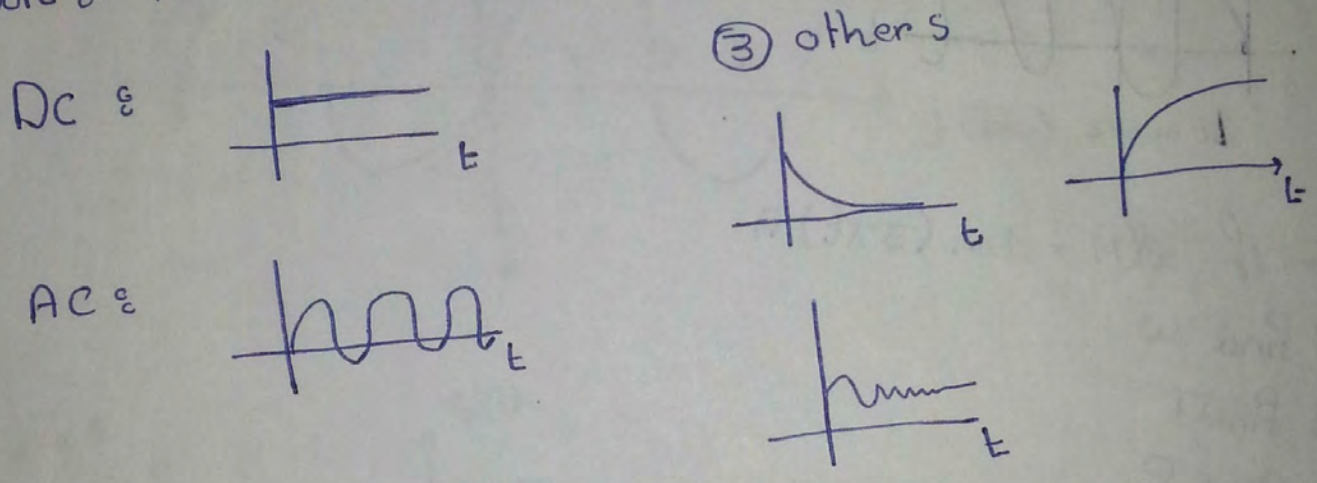Note  $\epsilon_0$  Voltage or Current could be  $\epsilon_0$



\* Characteristic of sinusoidal signal

$$V(t) = V_m \sin(\omega t) \quad \text{or} \quad \text{V/A}$$

$\downarrow$  Peak value or magnitude       $\underbrace{\hspace{2cm}}_{\text{angle}} \rightarrow$  degree / radian

deg.  $360^\circ \rightarrow 2\pi$  rad

$40^\circ \rightarrow X$

$X = \frac{2\pi \times 40}{360}$

$\omega$  radian frequency (or angular frequency)


[rad/sec]

$$\omega = \frac{2\pi}{T}$$

$$\omega = \frac{2\pi}{T}$$


T: period of the signal (sec.)

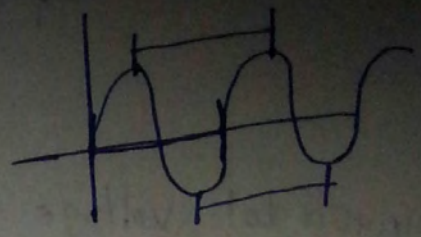$F = \frac{1}{T}$  frequency (Hz)  
↓  
Hertz



Ex:  $f = 60 \text{ Hz}$
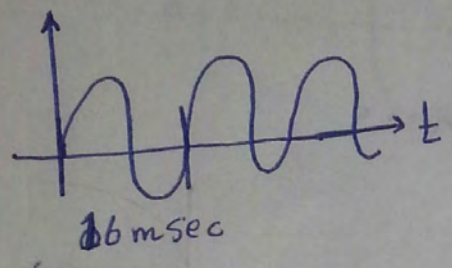
$$T = \frac{1}{60} = 0.016 \text{ sec} \\ = 16 \text{ msec}$$




Ex: if  $i(t) = 3\sin(3\pi t) \text{ A}$

- a) find  $\omega$
- b) find T
- c) find f


- d) Draw  $i(t)$  as a function of  $\omega t$
- e) Draw  $i(t)$  as a function of  $t$

Solution: a)  $\omega = 3\pi$   
b)  $T = \frac{2\pi}{3\pi} = \frac{2}{3} \text{ sec}$   
c)  $f = \frac{1}{T} = \frac{3}{2} \text{ Hz}$


(d)

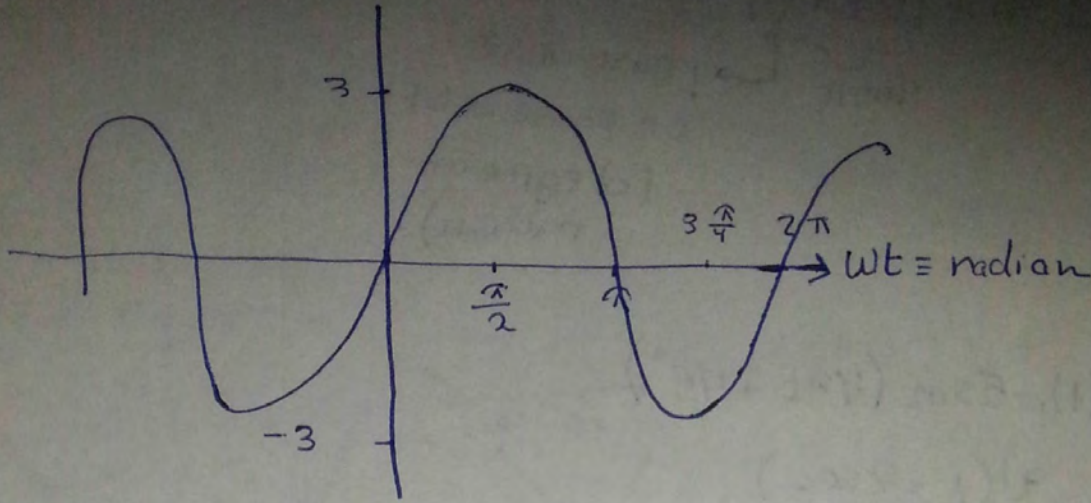

(c)

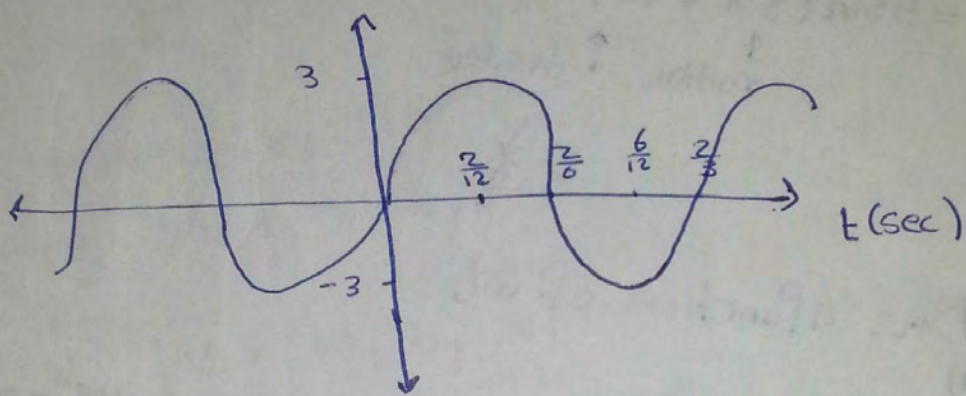

Ex 3

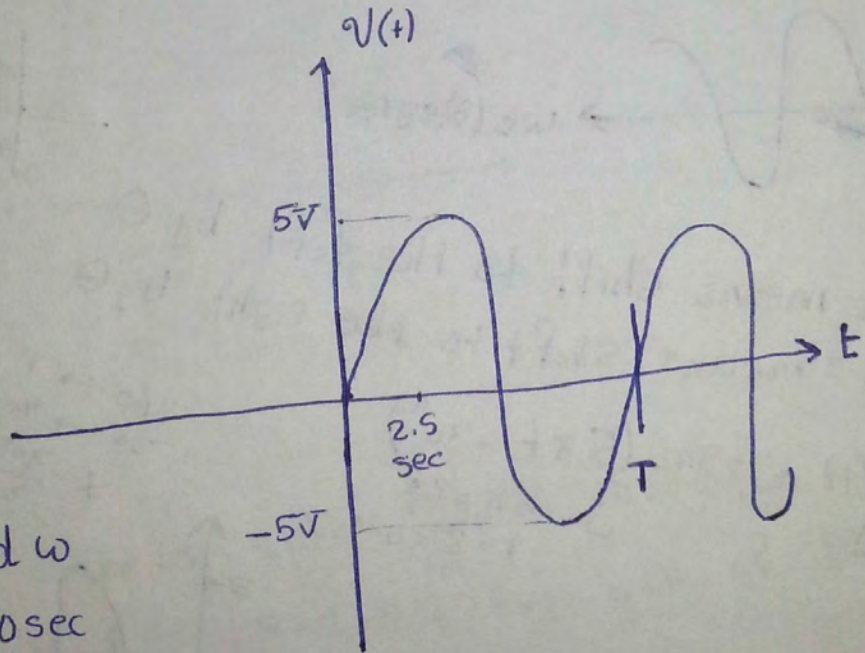

(a) Find  $\omega$ .

$T = 10 \text{ sec}$

$\omega = \frac{2\pi}{T} = \frac{\pi}{5} \text{ rad/sec}$

(b)  $f = \frac{1}{T} = 0.1 \text{ Hz}$

(c)  $v(t) = 5 \sin\left(\frac{\pi}{5} t\right) \text{ V}$

\* More general form of the sine wave is:

$$v(t) = V_m \sin(\omega t + \theta)$$

$\underbrace{\hspace{10em}}$  angle  
 $\uparrow$  phase angle or phase-shift  
 (degree or radian)

Ex: if  $v(t) = 5 \sin(4\pi t + 45^\circ)$

① Find  $v(t = 2 \text{ sec})$


$$v(t = 2 \text{ sec}) = 5 \sin(8\pi + 45^\circ)$$

$\uparrow$  radian     $\uparrow$  degree


$2\pi \rightarrow 360^\circ$   
 $8\pi \rightarrow ?$

$$\frac{8\pi}{4}$$

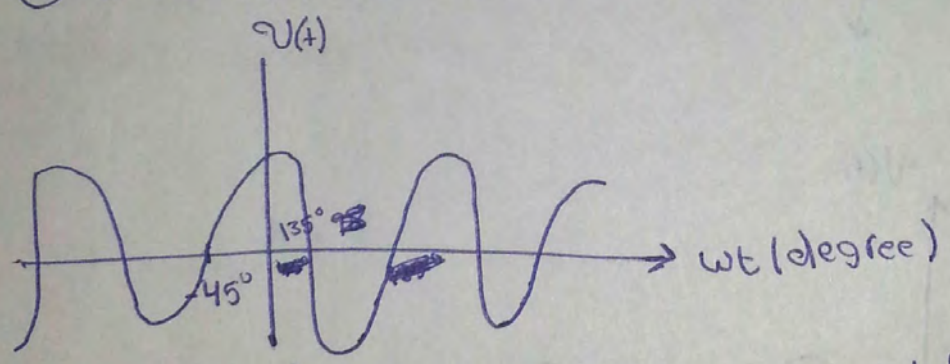② Draw  $v(t)$  as a function of  $\omega t$



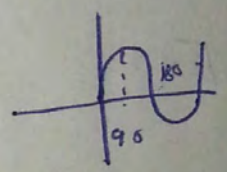$\omega t + 45^\circ = 0$   
 $\omega t = -45^\circ$





$\Rightarrow V_m \sin(\omega t + \theta) \equiv$  means shift to the left by  $\theta$   
 $\Rightarrow V_m \sin(\omega t - \theta) \equiv$  means shift to the right by  $\theta$


Ex: Draw  $v(t) = 3 \sin(5\pi t - 30^\circ)$

$\omega = 5\pi = \frac{2\pi}{T}$   
 $T = \frac{2}{5} = 0.4$

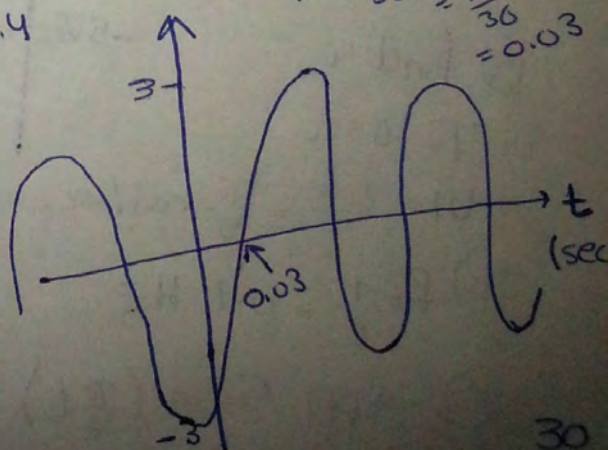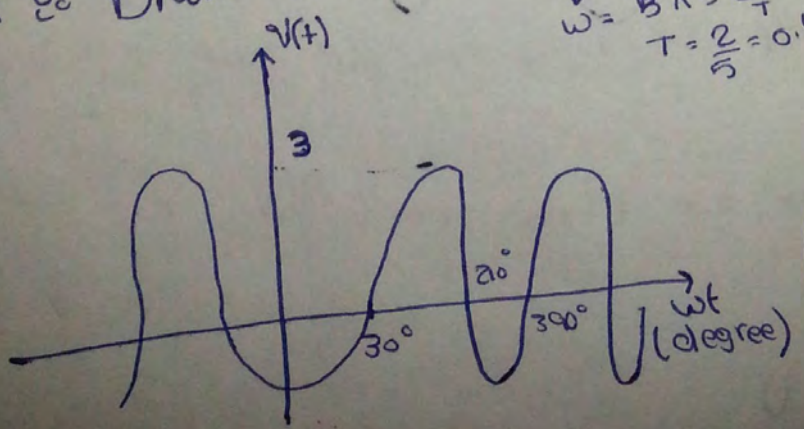
$360 \rightarrow T$   
 $30 \rightarrow x$   
 $x = \frac{30T}{360} = \frac{30 \times 0.4}{360}$   
 $= \frac{1.2 \text{ sec}}{36}$   
 $= 0.03$



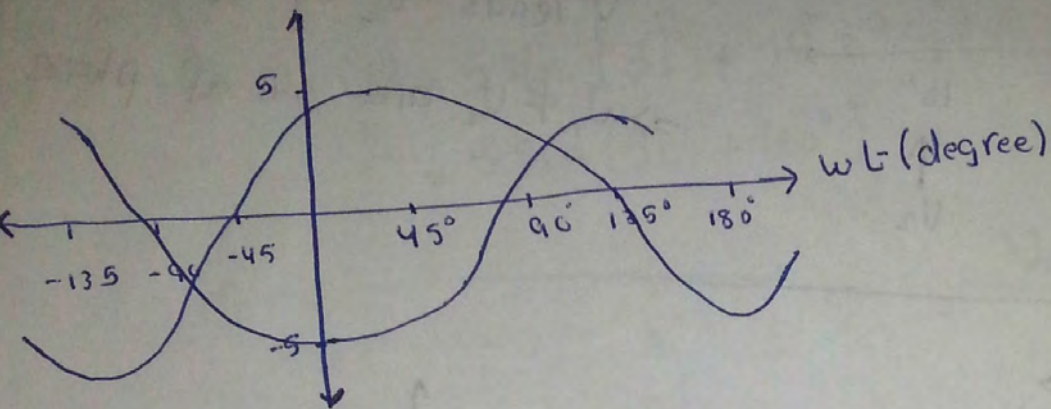Ex: if  $v_1(t) = 5\sin(2\pi t + 135^\circ)$   
 $v_2(t) = 5\sin(2\pi t - 90^\circ)$



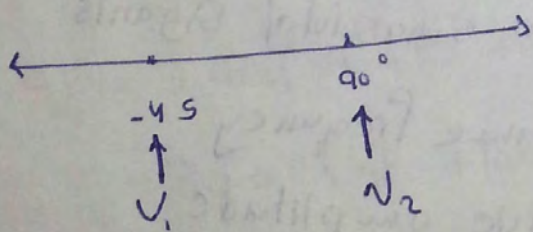
$v_1$  leads  $v_2$  by  $135^\circ$   
 or  $v_2$  lags  $v_1$  by  $135^\circ$   
 or  $v_1$  lags  $v_2$  by  $-135^\circ$   
 or  $v_2$  leads  $v_1$  by  $-135^\circ$



\* Note  
 if there is a phase shift between  $v_1$  &  $v_2$  we say that  $v_1$  and  $v_2$  are out-of-phase.

\* if there is no phase shift we say that  $v_1$  &  $v_2$  are in-phase.

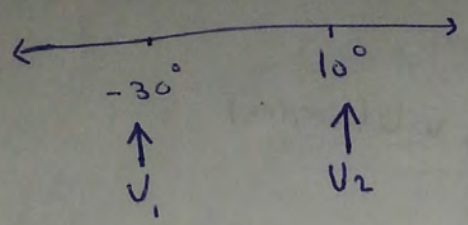
Ex:  $v_1(t) = 3 \cos(2\pi t + 30^\circ)$   
 $v_2(t) = 4 \cos(2\pi t - 10^\circ)$



$v_1$  leads  $v_2$  by  $40^\circ$   
 $\Rightarrow v_1 \neq v_2$  are out-of-phase

Ex:

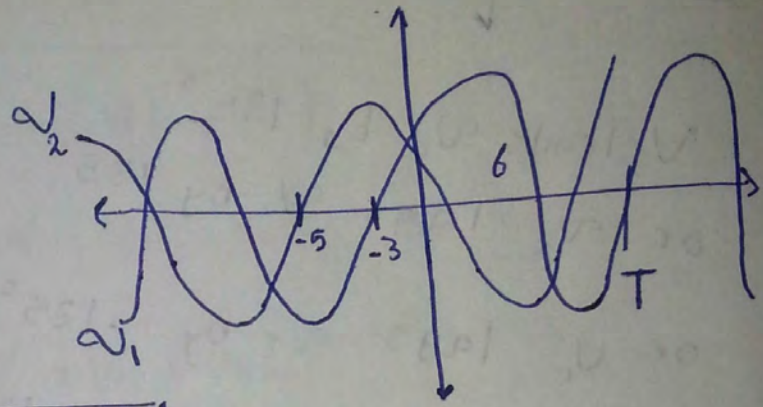$\Delta t = 2 \text{ msec}$   
 $18 \text{ msec} \rightarrow T$   
 $2 \text{ msec} \rightarrow \Delta \theta$   
 $360^\circ$   
 (نسبة زمنية) (نسبة) (سقطوا انهم degree) (لازم بال degree) (بنظير))



$$\Delta \theta = \frac{360 \times 2}{18} = \boxed{\Delta \theta \Rightarrow 40^\circ}$$

\* Note : to compare any two sinusoidal signals

- ① They must have the same frequency
- ② They must have positive amplitude
- ③ They must be sine or cosine.

$-\sin(\omega t) = +\sin(\omega t \pm 180^\circ)$

$-\cos(\omega t) = +\cos(\omega t \pm 180^\circ)$

$\sin(\omega t) = \cos(\omega t - 90^\circ)$

$\cos(\omega t) = \sin(\omega t + 90^\circ)$


Ex:  $v_1(t) = 5 \cos(5t + 10^\circ)$

$v_2(t) = 3 \sin(5t - 30^\circ)$

\* لازم ربطوا  
الشروط

$v_1(t) = 5 \sin(5t + 10^\circ + 90^\circ)$   
 $= 5 \sin(5t + 100^\circ)$

$v_1$  leads  $v_2$  by  $130^\circ$

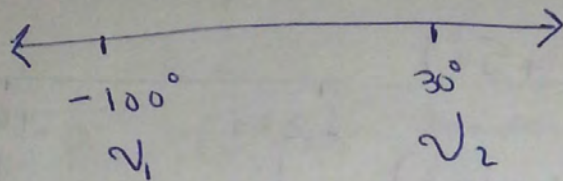

Ex:  $v_1(t) = -3 \sin(4t + 10^\circ)$


$v_2(t) = -4 \cos(4t - 50^\circ)$

$\Rightarrow v_1(t) = 3 \sin(4t + 10^\circ + 180^\circ)$

$\Rightarrow v_2(t) = 4 \cos(4t - 50^\circ + 180^\circ) \Rightarrow 4 \cos(4t + 130^\circ)$

$v_1(t) = 3 \cos(4t + 10^\circ + 180^\circ - 90^\circ)$   
 $= 3 \cos(4t + 100^\circ)$

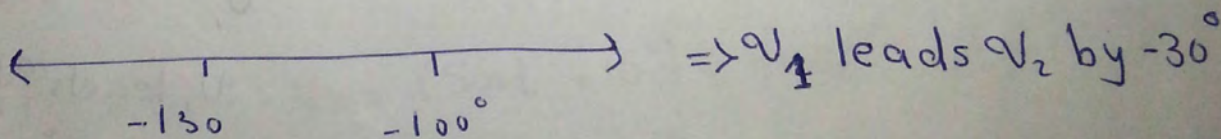$\Rightarrow v_1$  lags  $v_2$  by  $30^\circ$





$$\text{Ex: } z_1(t) = 10 \sin(\underline{3t} + 45^\circ)$$

$$z_2(t) = -5 \cos(\underline{4t} + 30^\circ)$$

We cannot compare them since different frequency.

$$\text{Ex: } v_1(t) = -3 \sin(4t + 10^\circ)$$


$$v_2(t) = -5 \sin(4t + 50^\circ)$$

$$+180 \rightarrow v_1(t) = 3 \sin(4t + 190^\circ)$$


$$v_2(t) = 5 \sin(4t + 230^\circ)$$

$$-180 \rightarrow v_1(t) = 3 \sin(4t - 170^\circ)$$

$$v_2(t) = 5 \sin(4t - 130^\circ)$$

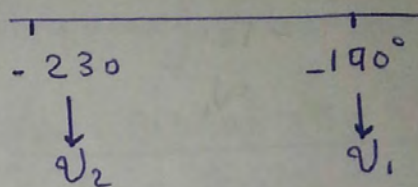


$v_2$  leads  $v_1$  by  $40^\circ$

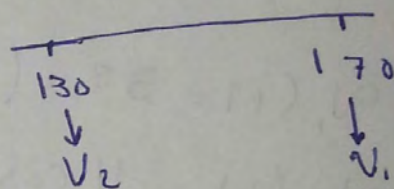


$v_1$  leads  $v_2$  by  $40^\circ$

$$\pm 180 \rightarrow v_1(t) = 3 \sin(4t + 190^\circ)$$

$$v_2(t) = 5 \sin(4t - 130^\circ)$$

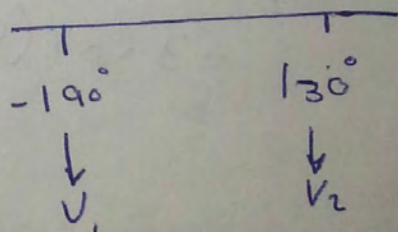

$v_1$  leads  $v_2$  by  $320^\circ$

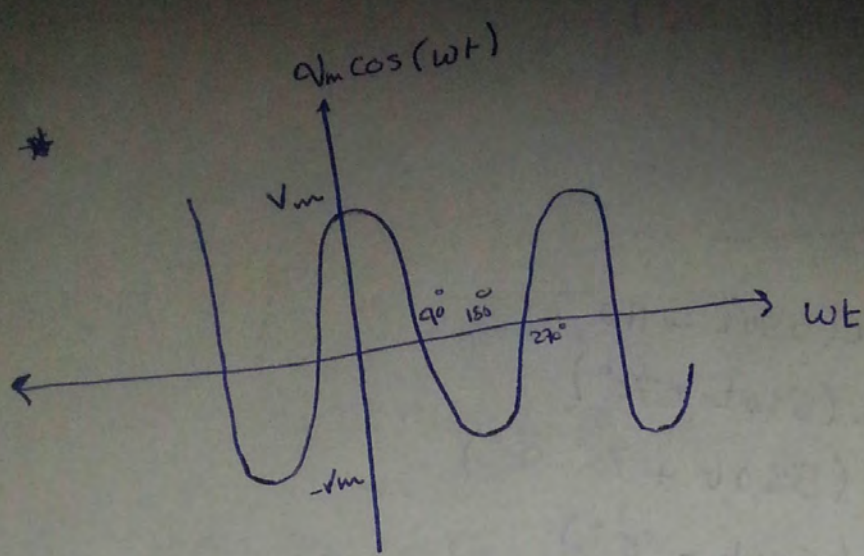

Phasor form (phasor-domain or frequency domain)  $\leftrightarrow$

$E_{x \text{ } \infty} \quad v(t) = \underline{3} \cos(200\pi t + 30^\circ) \leftarrow \text{(this signal is in the time domain)}$

Convert this signal from time-domain into frequency domain (phasor-domain)

\* Solution  $\infty$

$\vec{v} = 3 \angle 30^\circ \leftarrow \text{phasor domain}$

Note  $\infty$  to write the phasor form of sinusoidal signals, it should be a positive cosine function.

Ex: if  $i(t) = -4 \cos(500t + 10^\circ) = 4 \cos(500t + 190^\circ)$

Find  $i(t)$  in the phasor form

$\vec{I} = 4 \angle 190^\circ$

$$\text{Exe. if } v(t) = 100 \cos(400t - 30^\circ)$$

$$\vec{v} = 100 \angle -30^\circ$$

---

$$\begin{aligned} \text{Exe. if } i(t) &= -5 \sin(580t - 110^\circ) \\ &= 5 \sin(580t + 70^\circ) \\ &= 5 \cos(580t + 70^\circ - 90^\circ) \\ &= 5 \cos(580t - 20^\circ) \end{aligned}$$

$$\vec{I} = 5 \angle -20^\circ$$

---

$$\text{Exe. } i(t) = 8 \cos(4t - 30^\circ) + 4 \sin(4t - 100^\circ)$$

Write  $i(t)$  in phasor form (Frequency - domain)  
(or Phasor - domain)

$$i(t) = 8 \cos(4t - 30^\circ) + 4 \cos(4t - 100^\circ - 90^\circ)$$

$$\vec{I} = 8 \angle -30^\circ + 4 \angle -190^\circ$$

$$= 8 e^{-j30^\circ} + 4 e^{-j190^\circ}$$

$$= 8 [\cos(-30^\circ) + j \sin(-30^\circ)] + 4 [\cos(-190^\circ) + j \sin(-190^\circ)]$$

$$= 6.92 - j4 - 3.93 + j0.69$$

$$= 2.99 - j3.3$$

$$\vec{I} = 4.45 \angle -47.8^\circ$$

Ex. if  $\vec{I} = 20 \angle 10^\circ$  A,  $\omega = 2000$

Find  $i(t)$

$$\vec{I} = \sqrt{20^2 + 10^2} \angle \tan^{-1} \frac{10}{20}$$

$$= 22.36 \angle 26.57^\circ$$

$$i(t) = 22.36 \cos(2000t + 26.57^\circ) \text{ A}$$

## Steady state Analysis


Step 1: Convert the circuit from the time-domain into frequency-domain (phasor-domain)

time domain

Frequency domain

Sources  $\begin{array}{c} \oplus \\ \ominus \end{array} v_s(t) = V_m \cos(\omega t + \theta) \rightarrow \begin{array}{c} \oplus \\ \ominus \end{array} \vec{V}_s = V_m \angle \theta$

$\begin{array}{c} \uparrow \\ \downarrow \end{array} i_s(t) = I_m \cos(\omega t + \phi) \rightarrow \begin{array}{c} \uparrow \\ \downarrow \end{array} \vec{I}_s = I_m \angle \phi$

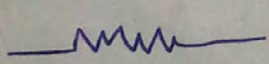  $R (\Omega)$

$\rightarrow$

$R (\Omega)$

$C (F)$


$\rightarrow$

$Z_c = \frac{1}{j\omega C} (\Omega)$  impedance of  $C$   
 complex


$$L(H) \longrightarrow Z_L = j\omega L (\Omega)$$

↓  
impedance of L

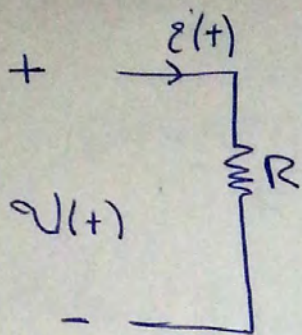\* The Resistor in frequency domain is  $R(\Omega)$ . why?!



time domain

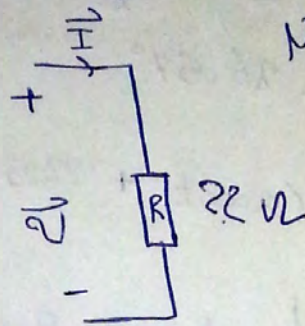

Frequency - domain

Note: \* The general form of a sinusoidal signal is:

$$v(t) = v_m \cos(\omega t + \theta) + j v_m \sin(\omega t + \theta)$$

Complex      Real      Imaginary

$$v_m e^{j(\omega t + \theta)}$$

$$v(t) = R i(t)$$

$$v_m e^{j(\omega t + \theta)} = R i_m e^{j(\omega t + \phi)}$$

$$v_m e^{j\theta} = R i_m e^{j\phi}$$


$$v_m \angle \theta = R i_m \angle \phi$$

$$\vec{V} = R \vec{I}$$


↓  
 $\Omega$

$$\theta = \phi$$

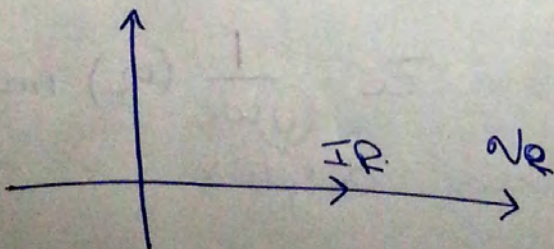The current and voltage in R are in phase ✓




Ex: if  $v(t) = 8\cos(100t - 50^\circ)$  and  $R = 4\Omega$ , find  $i(t)$ ?

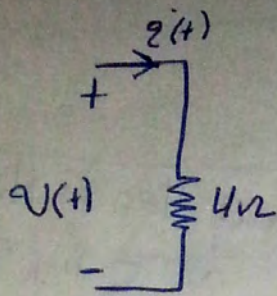

Method 1: Time-domain

$$i(t) = \frac{v(t)}{R} = 2\cos(100t - 50^\circ)$$


Method 2: Frequency-domain

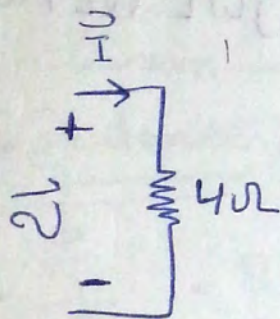

$$\Rightarrow \vec{I} = \frac{\vec{V}}{R} = \frac{8\angle -50^\circ}{4} = 2\angle -50^\circ$$

$$i(t) = 2\cos(100t - 50^\circ)$$

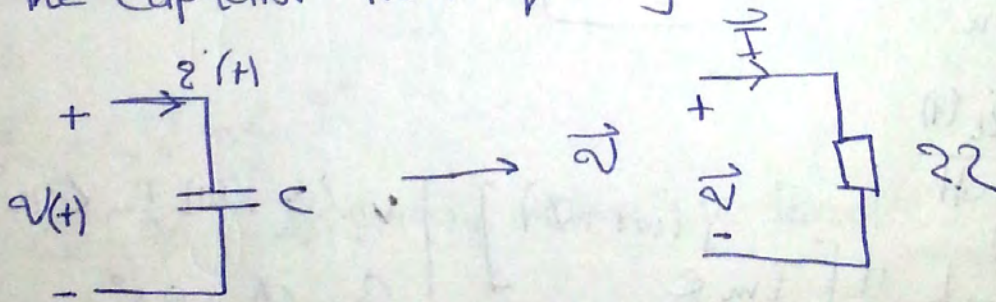\* The capacitor in frequency-domain is  $\frac{1}{j\omega C}$  why?



$$i(t) = C \frac{dv(t)}{dt}$$

$$I_m e^{j(\omega t + \theta)} = C \frac{d}{dt} V_m e^{j(\omega t + \theta)}$$

$$I_m e^{j(\omega t + \theta)} = C V_m j \omega e^{j(\omega t + \theta)}$$

$$I_m e^{j\theta} \cdot e^{j\omega t} = j\omega C V_m e^{j\theta} \cdot e^{j\omega t}$$

$$I_m \angle \theta = j\omega C V_m \angle \theta$$

$$\vec{I} = j\omega C \vec{V}$$

$$\vec{V} = \frac{1}{j\omega C} \vec{I}$$

$$I_m \angle \phi = \omega C \angle 90^\circ * V_m \angle \theta$$

$$I_m \angle \phi = \omega C V_m \angle \theta + 90^\circ$$

$$\phi = \theta + 90^\circ$$


$$\angle I \quad \angle V$$




$$\cos(\omega t + 90^\circ)$$

$$\cos(\omega t + \theta)$$

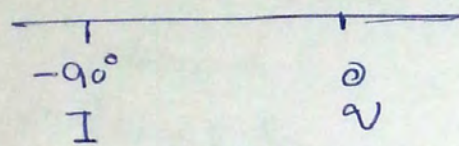
The current leads the voltage on C by  $90^\circ$



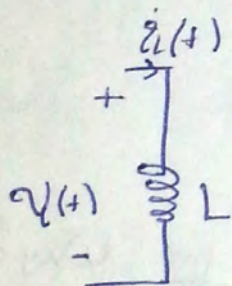\* The inductor in frequency domain is  $j\omega L (\Omega)$  why?



time domain

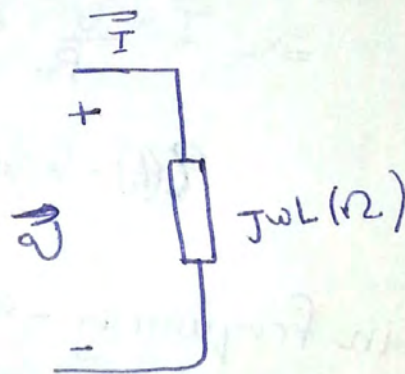

$$v_L(t) = L \frac{d i_L(t)}{dt}$$

$$V_m e^{j(\omega t + \theta)} = L \frac{d [I_m e^{j(\omega t + \phi)}]}{dt}$$

$$V_m e^{j(\omega t + \theta)} = L I_m j\omega e^{j(\omega t + \phi)}$$

$$V_m e^{j\theta} \cdot e^{j\omega t} = j\omega L I_m e^{j\phi} \cdot e^{j\omega t}$$

$$V_m \angle \theta = j\omega L I_m \angle \phi$$

$$\vec{V} = j\omega L \vec{I}$$


$$V_m \angle \theta = \omega L \angle 90^\circ + I_m \angle \phi$$

$$V_m \angle \theta = \omega L I_m \angle 90^\circ + \phi$$




$$\theta = \phi + 90^\circ$$

$$\angle V_L = \angle I_L$$
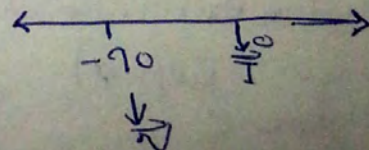
$$\cos(\omega t + 90^\circ) \quad \cos(\omega t + \phi)$$



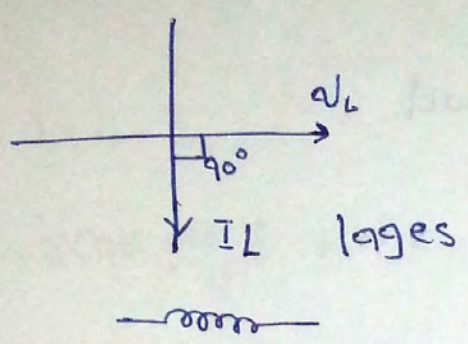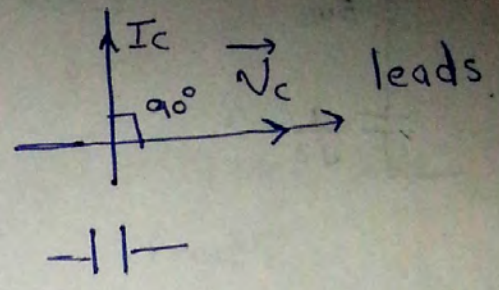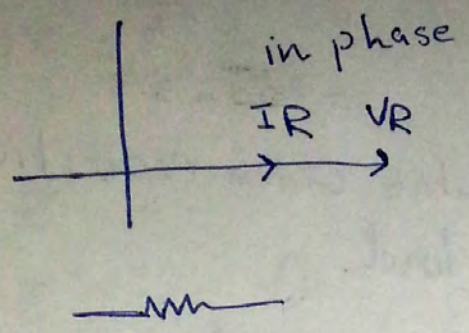The Current Lags Voltage by  $90^\circ$  on L



\* Impedance  $Z$

$$\vec{Z} = \frac{\vec{V}}{\vec{I}} = R + jX \rightarrow \text{reactance } (\Omega)$$

$\downarrow$   
 Resistance ( $\Omega$ )

$\downarrow$   
 impedance.  
 $\Omega$

$$\angle \vec{Z} = \angle \vec{V} - \angle \vec{I}$$

if  $\angle \vec{Z} = 90^\circ \Rightarrow$  purely inductive load

if  $\angle \vec{Z} = -90^\circ \Rightarrow$  purely capacitive load.


if  $\angle \vec{Z} = 0 \Rightarrow$  purely resistive load

if  $\angle \vec{Z} =$  is positive The load is an inductive load  
(but not pure inductive)

if  $\angle \vec{Z} =$  is negative The load is an capacitive load  
(but not pure capacitive)



Ex 20

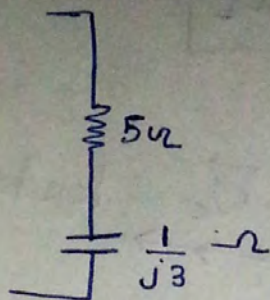

$$\vec{Z} = 5 - j\frac{1}{3} \Omega \Rightarrow \angle \vec{Z} = \tan^{-1} \frac{-\frac{1}{3}}{5}$$

$$= -3.8^\circ$$


Negative value capacitive load.

Ex 20 if  $\vec{Z} = 3 \oplus j5.5$  inductive load

this load is inductive load

if  $\vec{Z} = 4 \ominus j2$  capacitive load.

Ex 21

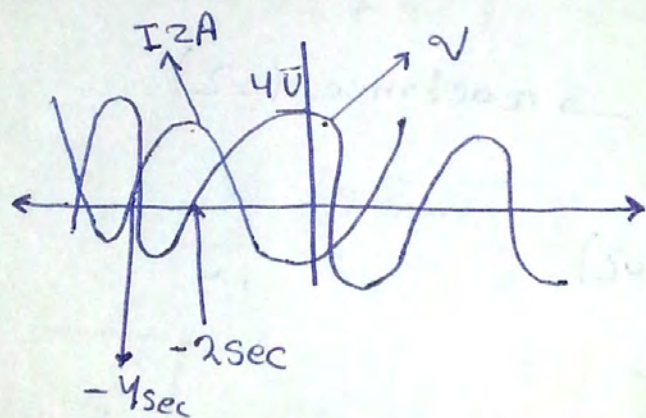

(a) the type of the load ??

Capacitive load because  $\vec{I}$  leads  $\vec{V}$

(b) the angle of the load ??

$T = 8 \text{ sec}$

$\Delta t = 2 \text{ sec}$

$T \rightarrow 360^\circ$

$\Delta t \rightarrow \Delta \theta$

$\Delta \theta = \frac{360^\circ \times 2}{8} = 90^\circ$

$\angle \vec{Z} = -90^\circ$

$$|\vec{Z}| = \frac{|\vec{V}|}{|\vec{I}|}, \quad \angle \vec{Z} = \angle \vec{V} - \angle \vec{I}$$

$$\angle \vec{Z} = -90^\circ$$

$$|\vec{Z}| = \frac{4\text{V}}{2\text{A}} = 2 \Omega$$

$$\vec{Z} = 2 \angle -90^\circ$$

$$\vec{Z} = 0 - j2 \Omega$$

$\uparrow$        $\uparrow$   
 R      X

© reactance part of the load?


ⓐ resistance part of the load?

$$\Rightarrow v(t) = ??$$




$$\omega = \frac{2\pi}{T} = \frac{2\pi}{8} = \frac{\pi}{4} \text{ rad/s}$$

$$4 \cos\left(\frac{\pi}{4}t + 0\right)$$
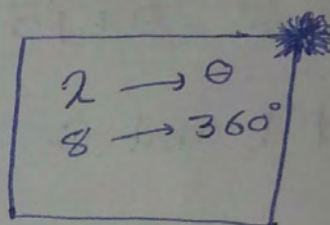
$$\text{or } v(t) = 4 \sin\left(\frac{\pi}{4}t + 90^\circ\right)$$



Shift Jinnal  
⊕ via

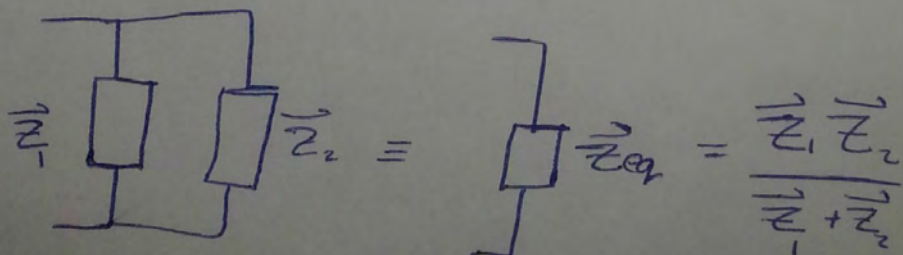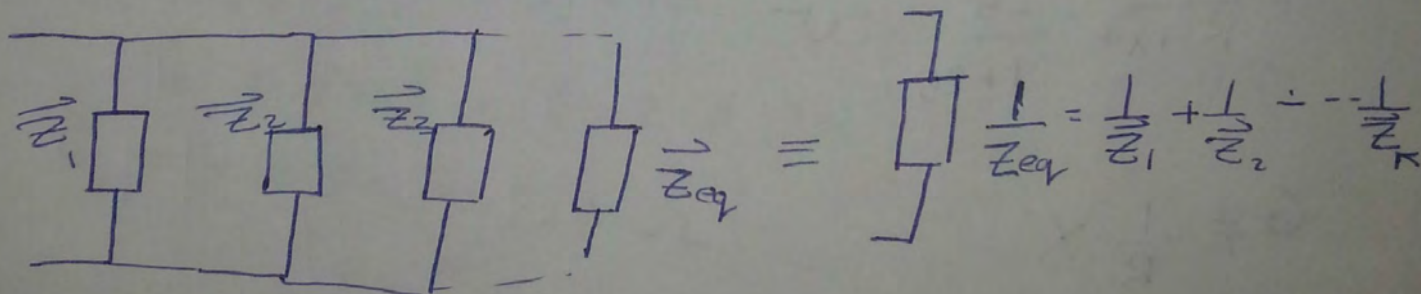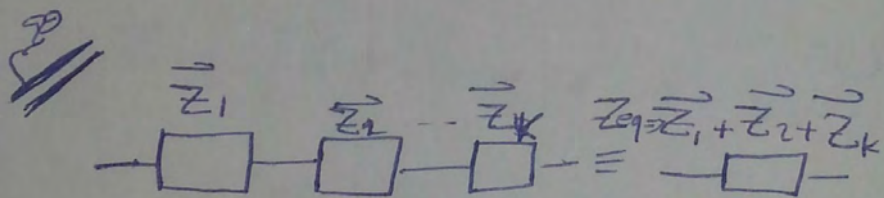



Ex 10.10  $\vec{Z} = 4 + j2 \Omega$



a) Find the type of load.

b) phase shift between the voltage and current on  $\vec{Z}$

a) inductive load (But not purely)

b)  $\vec{I}$  lags  $\vec{v}$  by  $\tan^{-1} \frac{2}{4}$

ب) بهیجانی /  
purely

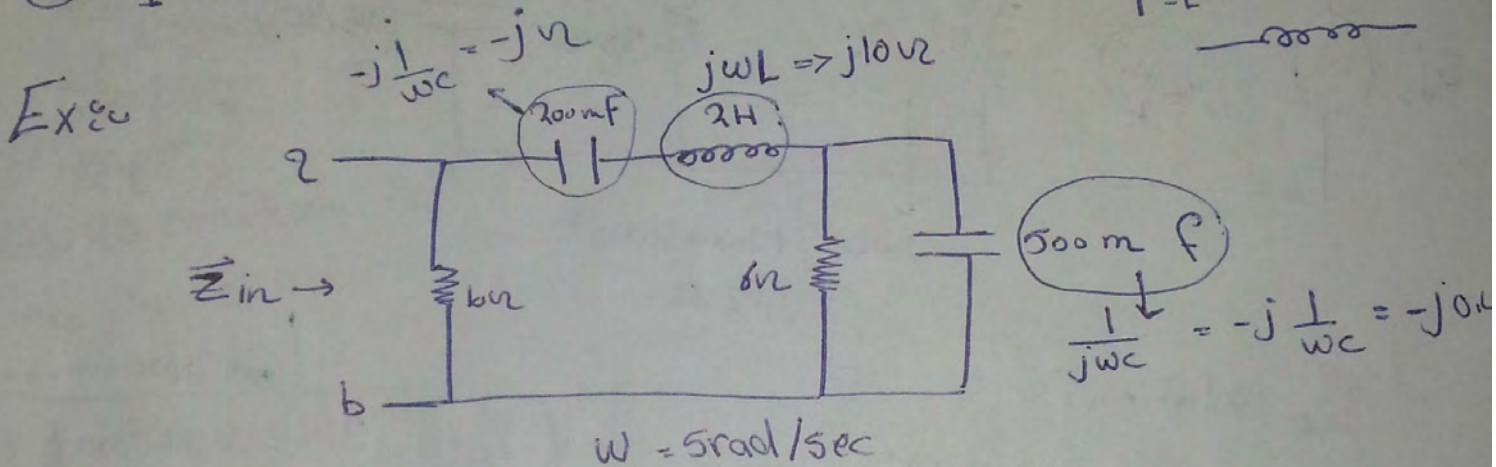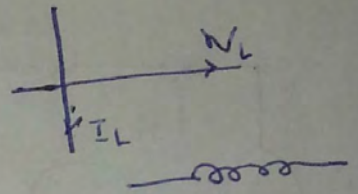

Find  $\vec{Z}_{in}$

$$\vec{Z}_{eq} = [6 \parallel -j0.4 + j10 + (-j)] \parallel 10 \Omega$$

$$= \left[ \frac{-j2.4}{6 - j0.4} + 9j \right] \parallel 10$$

$$= 0.0265 + j8.602 \parallel 10$$


$$\vec{Z}_{eq} = 4.255 + j4.929 \Omega$$

Exc<sub>cc</sub> if  $\omega = 1200 \text{ rad/sec}$

$$\vec{I}_c = 1.2 \angle 28^\circ$$

$$\vec{I}_L = 3 \angle 53^\circ$$

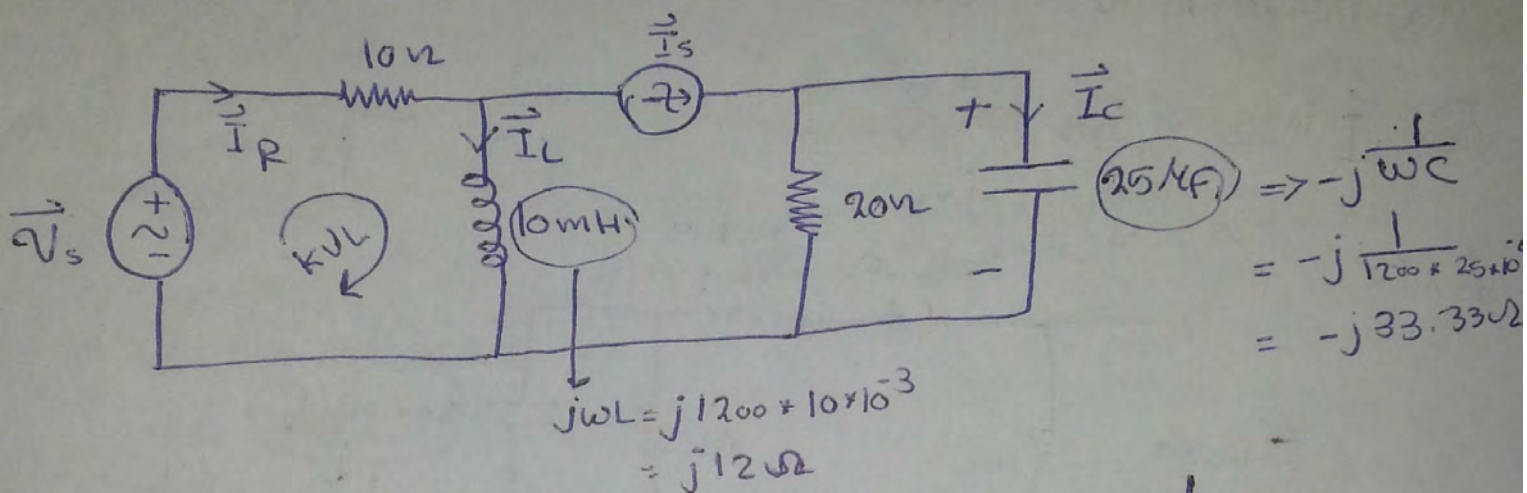\* Find  $\vec{I}_s$ ,  $\vec{V}_s$ ,  $i_R(t)$  ??



Solution<sub>cc</sub>

$$v_s = I_c * (-j33.33)$$

$$= 1.2 \angle 28^\circ * (-j33.33)$$

$$= 40 \angle -62^\circ \text{ V}$$

time domain.

$$i_R(t) = 3.99 \cos(1200t + 17.42^\circ) \text{ A}$$

$$I_{20\Omega} = \frac{v_c}{20} = \frac{40 \angle -62^\circ}{20} = 2 \angle -62^\circ \text{ A}$$

$$\vec{I}_s = \vec{I}_c + \vec{I}_{20} = 1.2 \angle 28^\circ + 2 \angle -62^\circ$$

$$= 2.33 \angle -31^\circ \text{ A}$$


$$\vec{I}_R = \vec{I}_s + \vec{I}_L$$

$$= 2.33 \angle -31^\circ + 3 \angle 53^\circ = 3.99 \angle 17.42^\circ \text{ A}$$

$$-v_s + 10 * \vec{I}_R + j12 * (3 \angle 53^\circ) = 0$$

$$v_s = 34.9 \angle 74.5^\circ$$

Ex 8 Find  $i(t)$

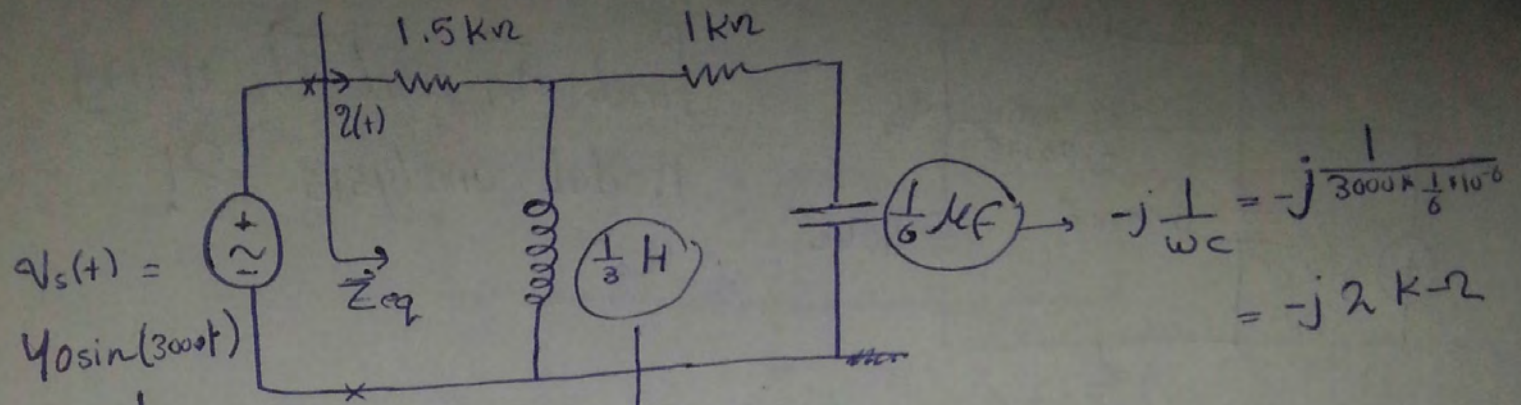

↓  
 لا نعرف  
 position  
 cos  
 لا نعرف  
 phasor.)

$v_s(t) = 40 \cos(3000t - 90^\circ)$   
 $\vec{v}_s = 40 \angle -90^\circ$

$j\omega L = j * 3000 * \frac{1}{3} = j1000 \Omega = j1 \text{ k}\Omega$

$-j \frac{1}{\omega C} = -j \frac{1}{3000 * \frac{1}{6} * 10^{-6}} = -j2 \text{ k}\Omega$

$\vec{Z}_{eq} = (1 - j2) // j + 1.5$   
 $= 2 - j1.5 \text{ k}\Omega$

$\vec{I} = \frac{\vec{v}_s}{\vec{Z}_{eq}} = \frac{40 \angle -90^\circ}{2 - j1.5} = 16 \angle -126.9^\circ \text{ mA}$

$i(t) = 16 \cos(3000t - 126.9^\circ) \text{ mA}$

Time domain


$-v_s(t) + i_1(t)1.5 + 3 \int_0^t (i_1(t) - i_2(t)) dt = 0$

$i_2 + \frac{1}{6} \frac{d i_2(t)}{dt} + 3 \int_0^t (i_1(t) - i_2(t)) dt = 0$

Ex:

$50 \angle -90^\circ \text{ mA}$

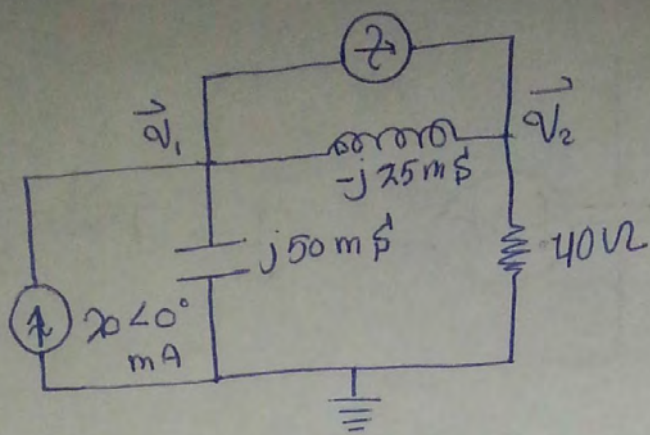find  $\vec{v}_1$  and  $\vec{v}_2$  using nodal analysis ?!



\* At Node 1 (KCL):

$$-20 \angle 0^\circ + (\vec{v}_1 - 0)j50 + (\vec{v}_1 - \vec{v}_2)(-j25) + 50 \angle -90^\circ = 0$$

$$20 + j50 = j25\vec{v}_1 + j25\vec{v}_2 \quad \text{--- (1)}$$

\* At Node 2 (KCL):

$$-50 \angle -90^\circ + (\vec{v}_2 - \vec{v}_1)(-j25) + (\vec{v}_2 - 0)40 = 0$$

$$-j50 = j25\vec{v}_1 + (40 - j25)\vec{v}_2 \quad \text{--- (2)}$$


(1) AND (2)

$$20 + j100 = (-40 + j50)\vec{v}_2$$

$$\vec{v}_2 = \frac{20 + j100}{-40 + j50} = \frac{42}{41} - j\frac{50}{41} = 1.59 \angle -50^\circ$$

$$\vec{v}_1 = \frac{20 + j50 - j25(1.59 \angle -50^\circ)}{j25} = 1.06 \angle 23.3^\circ$$

Ex 8.0

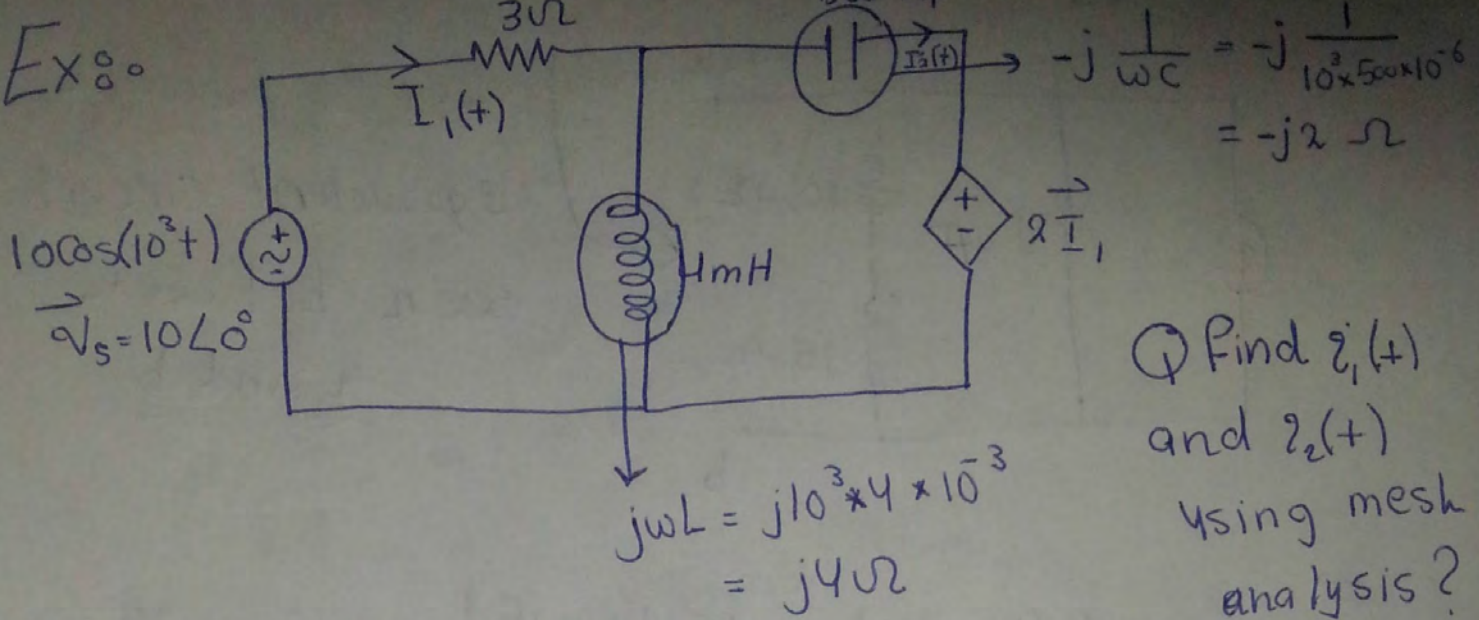

Find  $\vec{i}_1(t)$  and  $\vec{i}_2(t)$  using mesh analysis?

$\Rightarrow$  mesh 1

$$-10 + 3\vec{I}_1 + j4(\vec{I}_1 - \vec{I}_2) = 0$$

$$-10 + (3 + j4)\vec{I}_1 - j4\vec{I}_2 = 0 \quad \dots (1)$$

$$\vec{I}_2 = \frac{-10 + (3 + j4)\vec{I}_1}{j4}$$

$\Rightarrow$  mesh 2

$$j4(\vec{I}_2 - \vec{I}_1) - j2(\vec{I}_2) + 2\vec{I}_1 = 0$$

$$(2 - j4)\vec{I}_1 + j2\vec{I}_2 = 0 \quad \dots (2)$$

From (1)

$$(2 - j4)\vec{I}_1 + j2 \left[ \frac{10 + (3 + j4)\vec{I}_1}{j4} \right] = 0$$


$$(2 - j4)\vec{I}_1 - 5 + (1.5 + j2)\vec{I}_1 = 0$$

$$0.5 - j6\vec{I}_1 = 5 \Rightarrow \vec{I}_1 = \frac{5}{0.5 - j6} = \underline{1.24 \angle 29.7^\circ \text{ A}}$$

$$\vec{I}_2 = \underline{2.77 \angle 56.3^\circ \text{ A}}$$




Ex 80

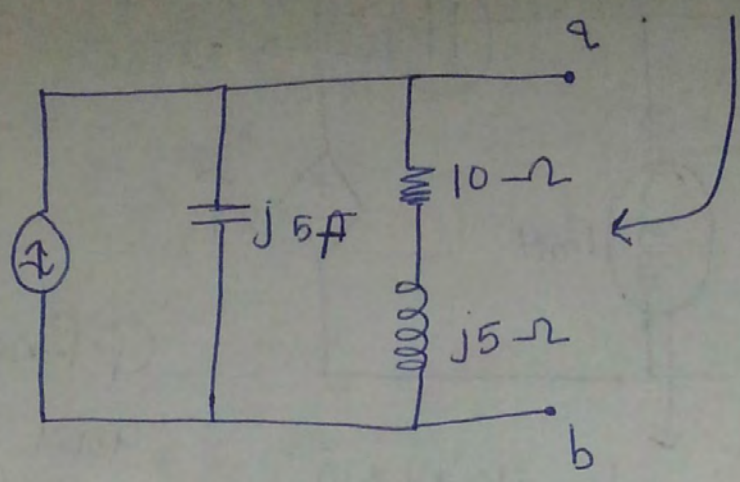


Find the thevenin equivalent circuit seen between a and b

$$\vec{Z}_{eq} = -j5 \parallel (10 + j5) = \frac{-j5(10 + j5)}{10} = \frac{-j50 + 25}{10} \Rightarrow 2.5 - j5 \Omega$$
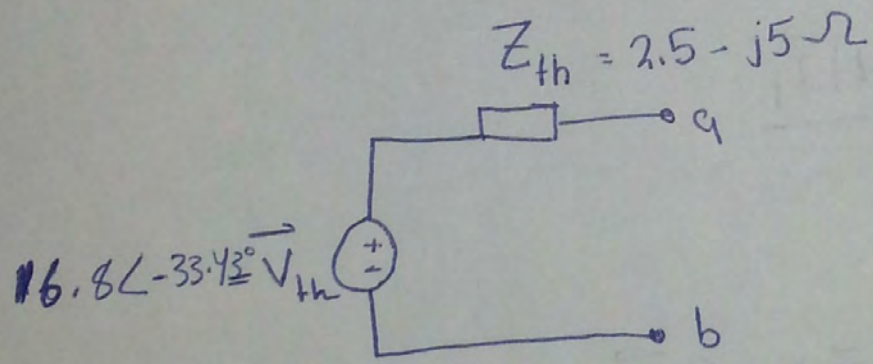
$$\vec{V}_{th} = 3 \angle 30^\circ * \vec{Z}_{th} = 16.8 \angle -33.43^\circ$$



⇓ or

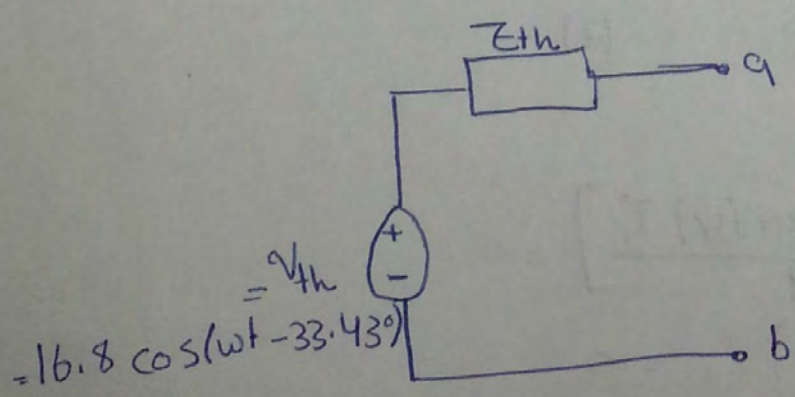


$$I_Z = 2.77 \angle 56.3^\circ A$$

Note: To get the maximum power transfer from

a give circuit to a certain load ( $\vec{Z}_L$ ) in the


Circuit  $\boxed{Z_L = Z_{th}}$

Ex 8.

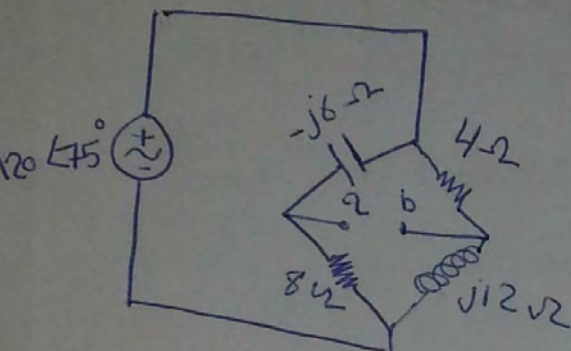

Find the thevenin equivalent seen between a and b ??

Sol: Kill the source.

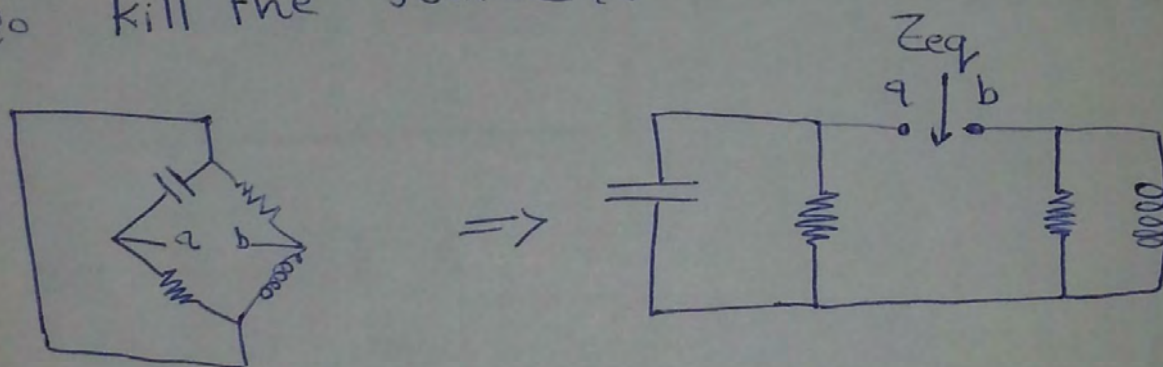

$$\begin{aligned} \vec{Z}_{eq} &= (8 \parallel -j6) + (4 \parallel j12) \\ &= \frac{8 * (-j6)}{8 - j6} + \frac{4 * (j12)}{4 + j12} \\ &= 2.88 - j3.84 + 3.6 + j1.2 \\ &= 6.48 - j2.64 \Omega \end{aligned}$$

$V_{th} = V_{o.c} = V_a - V_b$  \* using nodal analysis

$$\frac{\vec{V}_a - 0}{8 \Omega} + \frac{\vec{V}_a - \frac{120 \angle 75^\circ}{-j6}}{-j6} \dots (1)$$

$$\vec{V}_a \left( \frac{1}{8} - \frac{1}{j6} \right) = \frac{-120 \angle 75^\circ}{j6} \Rightarrow \frac{[-120 \angle 75^\circ / j6]}{\frac{1}{8} - \frac{1}{j6}}$$

$$\frac{\vec{V}_b - 0}{j12} + \vec{V}_b = \frac{120 \angle 75^\circ}{4} = \dots (2)$$


$$\vec{V}_{th} = \vec{V}_{oc} = \vec{V}_a - \vec{V}_b \Rightarrow 37.95 \angle 220.31^\circ \text{ V}$$

# Notes:


If the circuit has different sources with different Frequencies ( $\omega$ ) then we use

## Super position

Find the current on  $10 \Omega$  ??

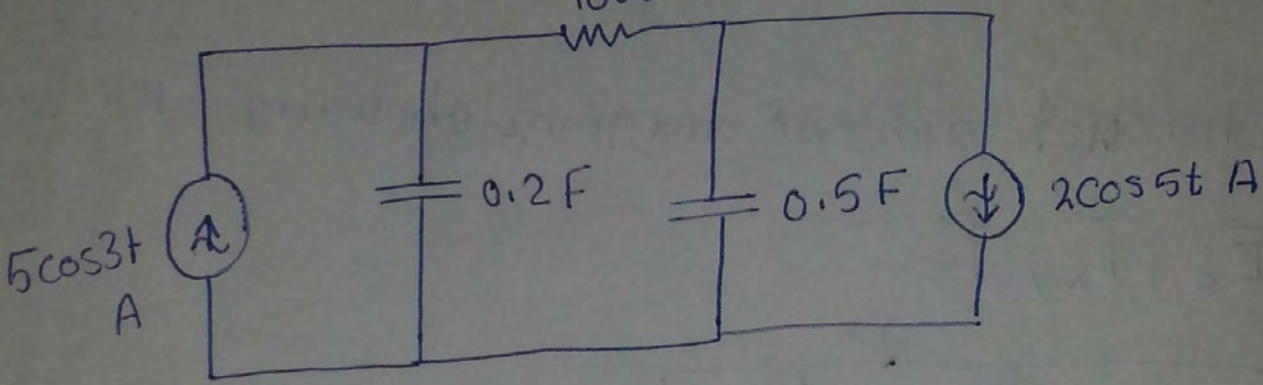


due  $2\cos 5t$  A

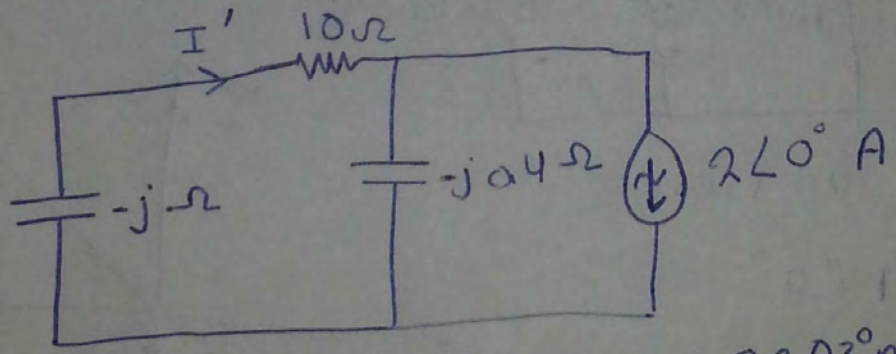

$$I' = 2\angle 0^\circ \left[ \frac{-j0.4}{10 - j - j0.4} \right] = 79.23 \angle -82.03^\circ \text{ mA} \Rightarrow 79.23 \cos(5t - 82.03^\circ) \text{ mA}$$

due  $5\cos 3t$  A

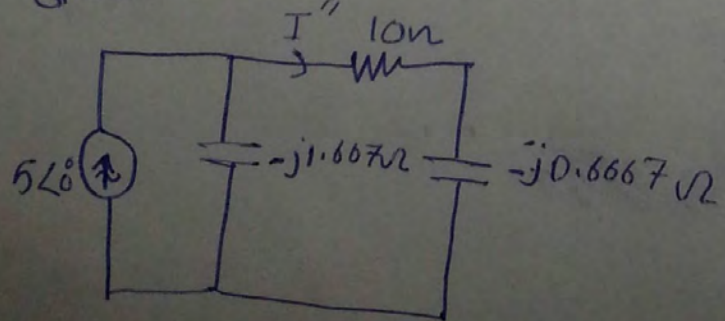

$$I'' = 5\angle 0^\circ \left[ \frac{-j1.667}{10 - j0.6667 - j1.667} \right] = 811.7 \angle -76.86^\circ \text{ mA}$$

$$I'' = 811.7 \cos(3t - 76.86^\circ) \text{ mA}$$

$$I = I' + I''$$


\* phasor diagram :-

it provides a graphical method for solving certain problems which may be used to check more exact analytical methods.

=> it shows the relationships between the current and voltages in a circuit

Ex :- construct a phasor diagram showing  $\vec{I}_R, \vec{I}_L,$

$\vec{I}_C, \vec{I}_X, \vec{I}_S$

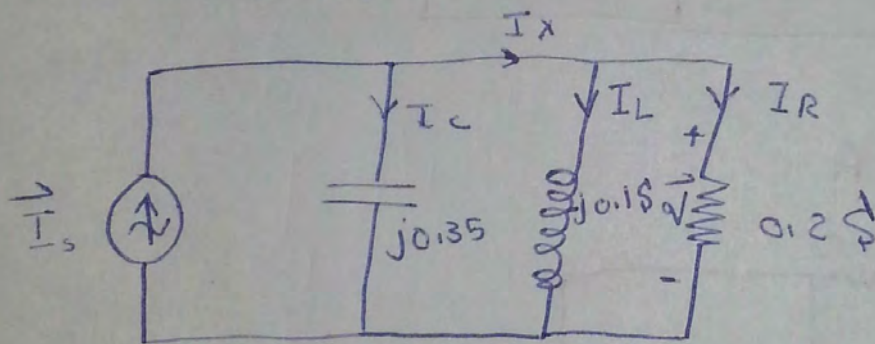



select  $\vec{V}$  as a reference

$$\vec{V} = 1 \angle 0^\circ$$

$$\vec{I}_R = 0.2 \times 1 \angle 0^\circ = 0.2 \angle 0^\circ$$


$$\vec{I}_L = -j0.1 \times 1 \angle 0^\circ = 0.1 \angle -90^\circ$$
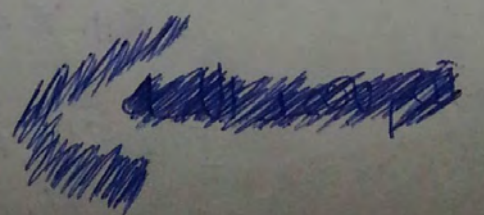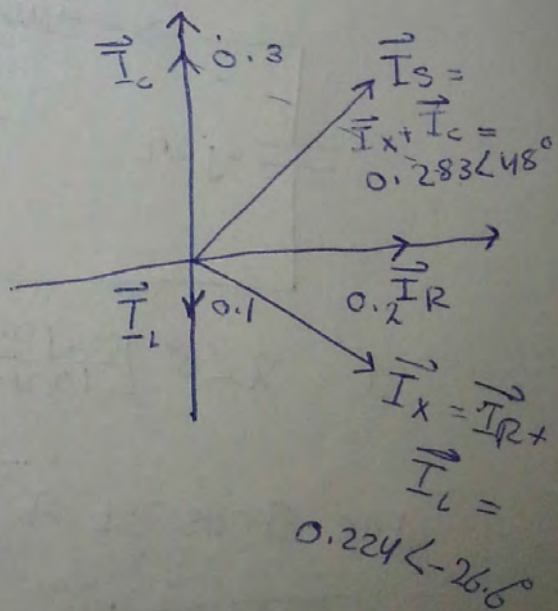
$$\vec{I}_C = j0.3 \times 1 \angle 0^\circ = 0.3 \angle 90^\circ$$



Ex:  $\vec{V}(t) = 4 \cos(\omega t + 45^\circ)$  phasor diagram??  
 $\vec{I}(t) = 3 \cos(\omega t - 60^\circ)$

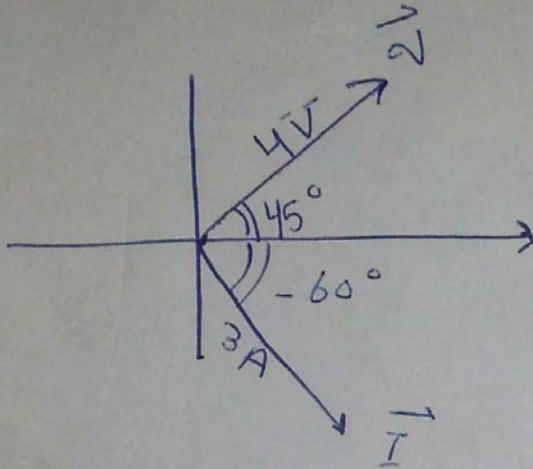$4 \angle 45^\circ$   
 $3 \angle -60^\circ$



تم بجز اللہ