

14/30

Jordan University
 Faculty of Engineering and Technology
 Electrical Engineering Department
 Summer 2012/2013



EE211 Lina Alghanem

Second Exam

Time: 90 mints

Q1) For the circuit shown in Fig. 1

- 1) The value of I_x in A is
 a. 2 **b. 1.33** c. -2 d. -1.33 **d. none**
- 2) R_{Th} in $m\Omega$ between a and b is
a. 250 b. 444.4 c. 500 d. none
- 3) The maximum power transfer in Joules to the load is
 a. 1.7776 b. 14.2 **c. 28.4** **d. none**

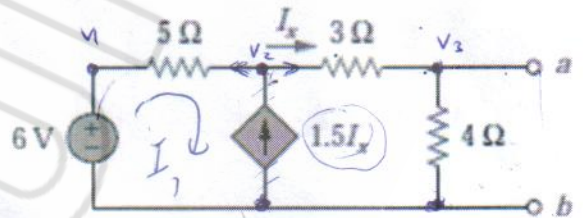


Fig. 1

The current $i(t)$ through the network in Fig. 2.1 is shown in Fig. 2.2

- 4) the equivalent inductor seen by a and b is
 a. 0.588 b. 0.645 **c. 8** **d. none**
- 5) the voltage $V(t)$ in Volts for the period of $[0, 3ms]$
 a. -10.66 b. -3.33 c. 3.33 **d. 10.66** e. none
- 6) the voltage $V_x(t)$ in Volts for the period of $[3ms, 6ms]$
 a. -2.22 **b. 6.66** c. 2.22 **d. -6.66** e. none
- 7) the energy stored in μJ in the equivalent inductor at $t=3ms$
 a. -32 b. 32 c. -64 **d. 64** e. none

4

$L_1 R = 1.5 I_x = I_x$

$0.5 I_x = 1.2$

$I_x = \frac{1.2}{0.5}$

2.4

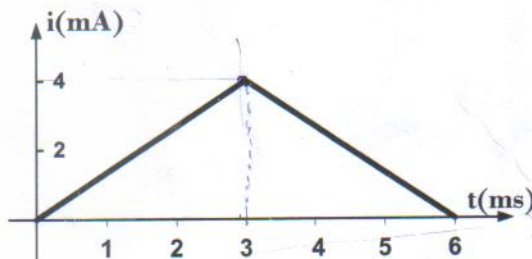
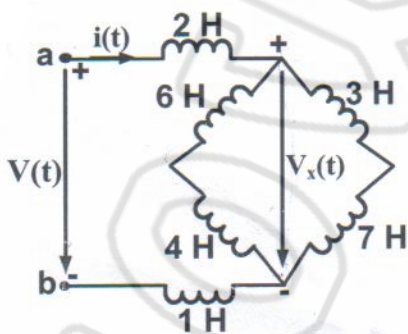


Fig. 2.1

For the circuit shown in Fig. 3 under dc conditions
 (All resistors are in Ω , $C_1=C_2=2\mu\text{F}$ and $L_1=L_2=2\text{mH}$)

8) The voltage V_{C_1} across the capacitor C_1 is
 a. 10 V b. 12 V **c. 18 V** d. 30 V e) none

9) The energy stored in the capacitor C_2 is
 a. none b. 0 J c. 0.144 mJ **d. 0.324 mJ**

10) The energy stored in the inductor L_2 is
 a. 56 mJ b. 0 J c. 25 mJ **d. 9 mJ** e) none

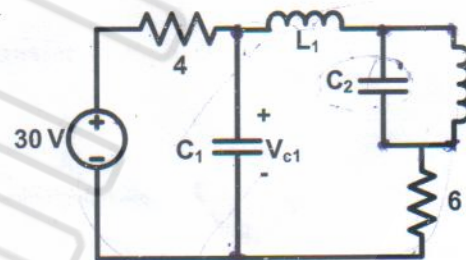


Fig. 3

For the circuit shown in Fig. 4 under dc conditions

11) the value of R in Ω that will make the energy stored in the capacitor the same as that stored in the inductor
 a. -5 **b. 5** **c. both a and b** d. 3 e. -3 f. None

12) The voltage through the capacitor is
 a. 3.235 **b. 7.142** **c. 17.857** d. None

13) The energy stored in the inductor is
 a. 56 mJ b. 0 J c. 25 mJ **d. 4 mJ** e) none

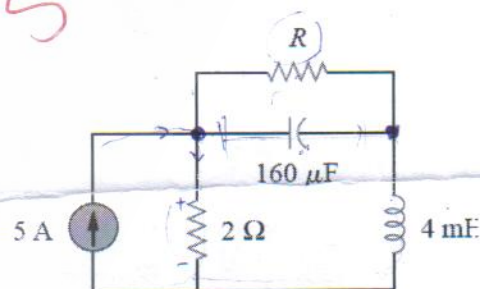





Fig.4

Q2) Consider the circuit shown below

(9 marks)

a. Draw the equivalent Thevenin's circuit

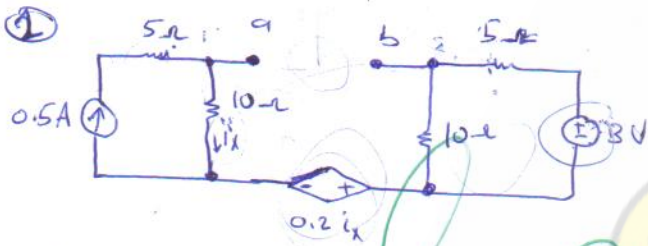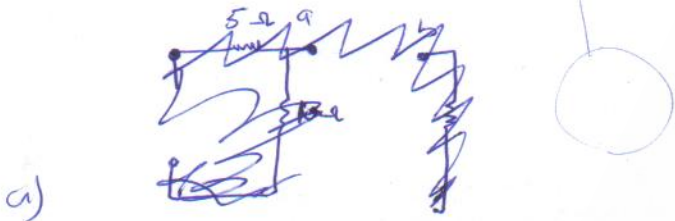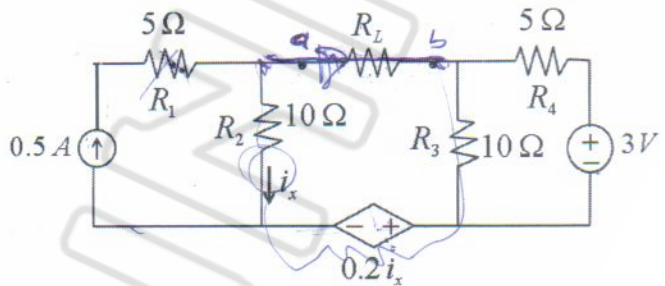b. Find the value of the load resistance R_L such that power transfer to R_L is $P=20\text{mW}$.



$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{V_{th}}{I_{th}} =$$



$$V_{ab} = V_a - V_b$$

$$V_{ab} = 5 - 2 = 3V$$

$$V_{ab} = 3V = V_{th}$$




$$V_a = IR = (0.5)(10) = 5V$$

$$V_b = \frac{(3)(10)}{15} = 2V$$

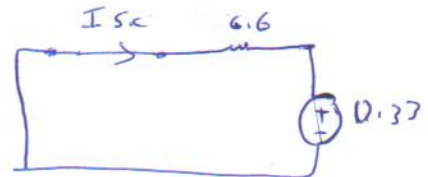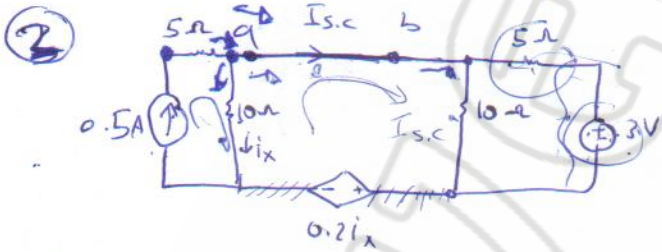

$$I_{sc} = \frac{0.37}{6.6} = 0.05 A$$
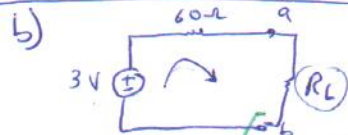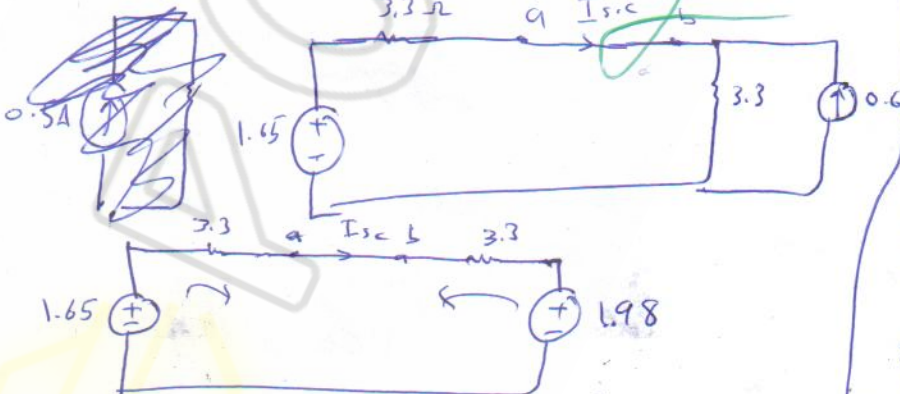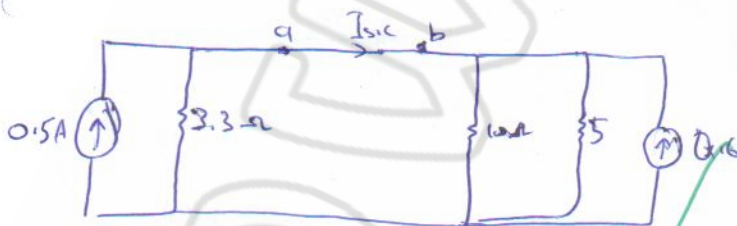
$$\text{So } R_{th} = \frac{V_{th}}{I_{sc}} = \frac{3}{0.05} = 60\Omega$$



$$P = I^2 R_L$$

$$20 = \left(\frac{3}{R_L + 60}\right)^2 R_L$$

$$20 = \frac{9}{R_L}$$

$$20R_L = 9$$

$$R_L = \frac{9}{20} = 0.45\Omega$$

Q3-

The switch in the circuit shown in Fig. P7.51 has been closed a long time before opening at $t = 0$. For $t \geq 0^+$, find




(9 Marks).

- $v_o(t)$.
- $i_o(t)$.
- $i_1(t)$.
- $i_2(t)$.
- $i_1(0^+)$.

c) $i_1(t) = i_o(t) = 1 \text{ mA}$

d) $i_2(t) = \frac{(5)(60)}{75} = 4 \text{ mA}$

Figure P7.51

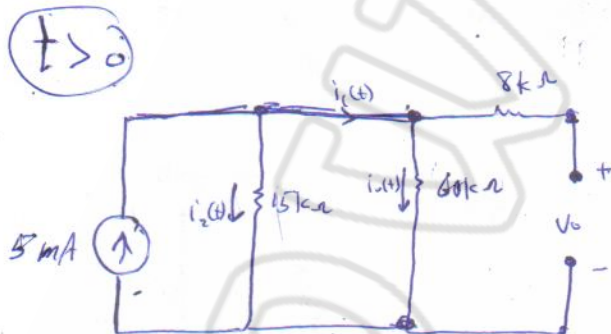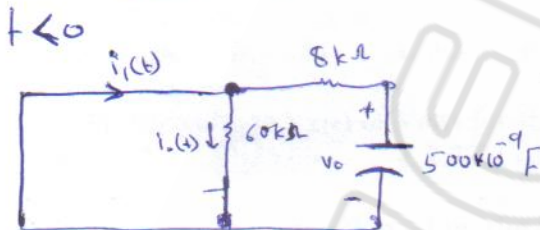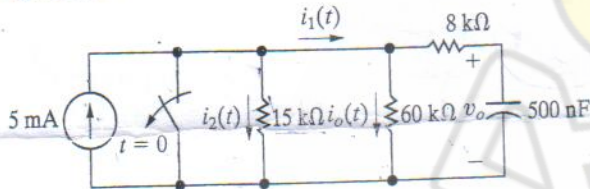

b) $i_o(t) = \frac{(5)(15)}{75} = 1 \text{ mA}$ $v_o(t) = v_{60k\Omega}$

So $v_o(t) = i_o(t) \times 60$
 $= 1 \times 60$

a) $v_o(t) = 60 \text{ V}$

3

e) $i_1(0^+) = 1$

$i_1(t) = i_o + e^{-t/\tau}$

$\tau = R_{eq} C_{eq}$

$\tau = (7.05)(500 \times 10^{-9})$

$\tau = 3529.4 \times 10^{-9}$

$i_2(t) = 1 \cdot e^{-t/3529.4 \times 10^{-9}}$

$i_1(0^+) = 1$