

Time : 75 Min.

Fall 2012



Date: Dec. 18, 2012

Name (in Arabic): محمد عبد الجبار Student #: 0119203



Section #: Pr. Iyad Jabr

Show the details of your solution

Problem 1: Determine the equivalent capacitance seen through terminals A and B. (2 points)

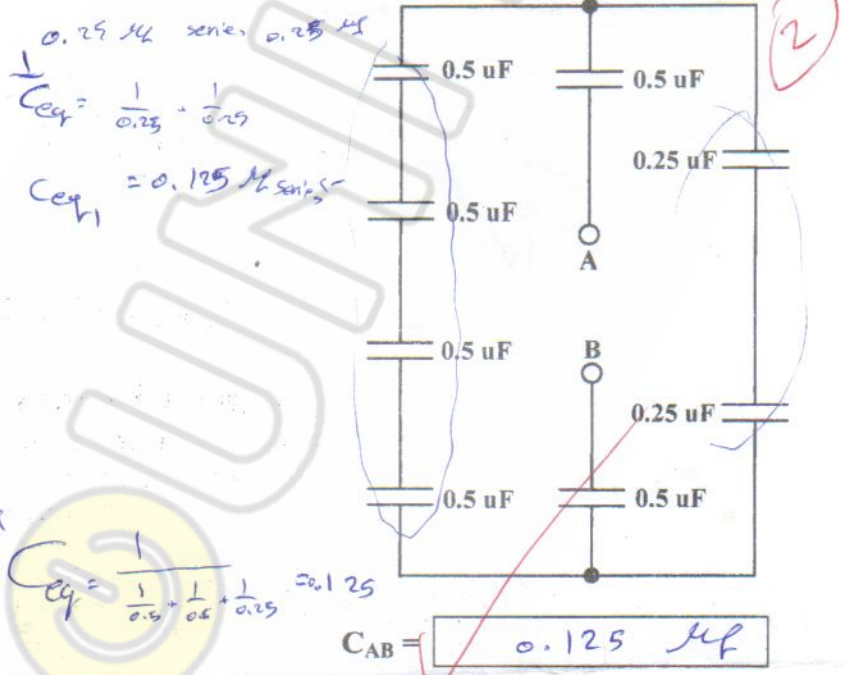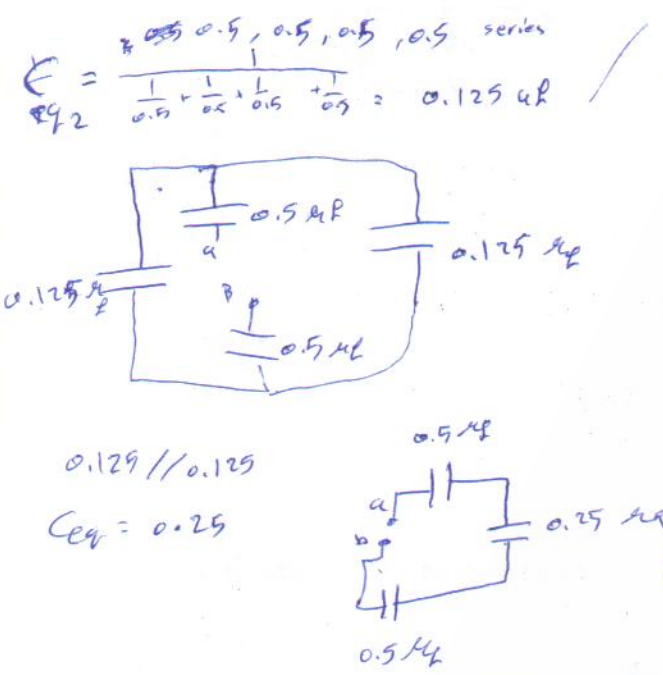

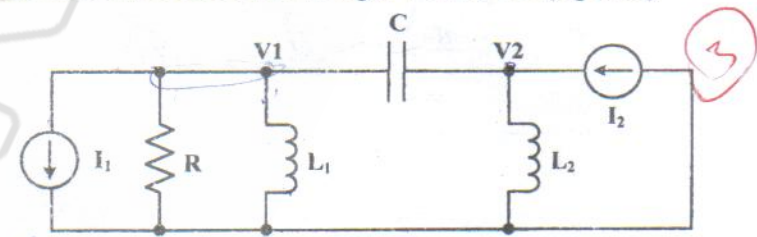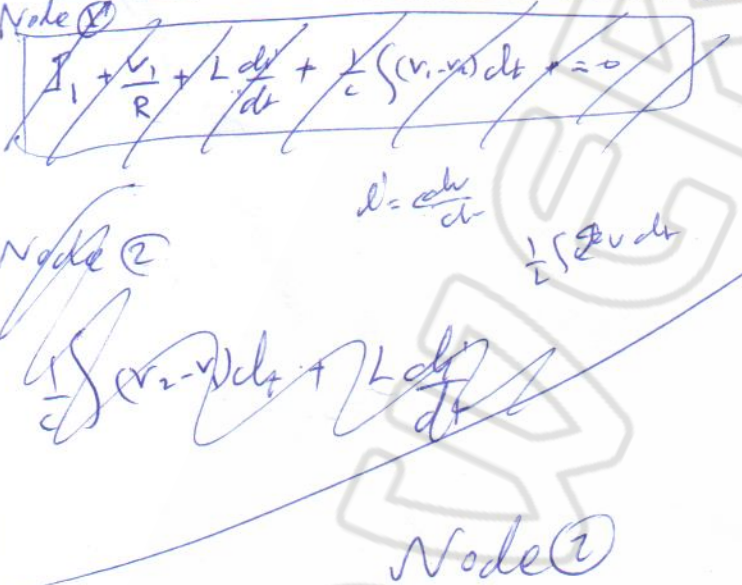Problem 2: Write the nodal equations for the following circuit in terms of the nodal voltages V_1 and V_2 . (4 points)



Node ①

$$I_1 + \frac{V_1}{R} + C \frac{d(V_1 - V_2)}{dt} + \frac{1}{L} \int V_1 dt = 0$$

I_0





Node ②

$$C \frac{d(V_2 - V_1)}{dt} + \frac{1}{L} \int V_2 dt = I_2$$

40

Problem 3: For the following circuit, determine the value of R_L that absorbs the maximum power. Also, compute the value of this maximum power. (7 points)

$$R_L (\text{max power}) = R_{th}$$

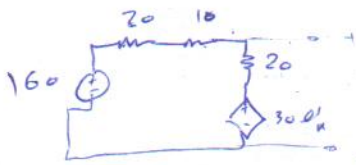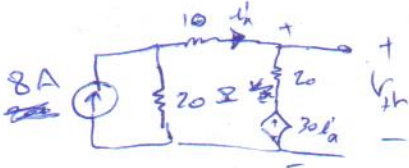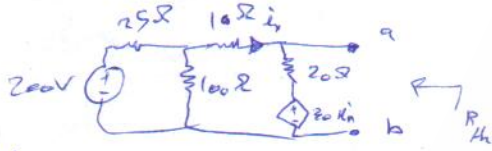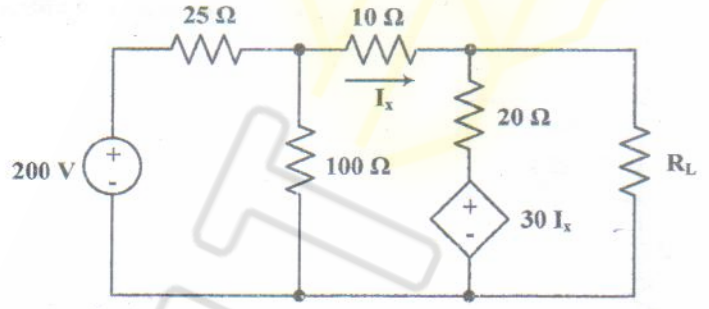

$$-160 + 20I_x + 10I_x + 20I_x + 30I_x = 0$$

$$160 = 80I_x$$

$$I_x = 2A$$

$$V_{th} = 100V$$

$$R_L = R_{th} = \frac{V_{th}}{I_N} = 18.75 \Omega$$

$$P_{max} = \frac{V^2}{R} = 533.33 J$$




$$R_L = 18.75 \Omega$$

$$P_{max} = 533.33 J$$

Problem 4: In the following circuit, use superposition to find I_1 . (7 points)

7

$$I_1 = I_{1(30V)} + I_{1(3A)}$$

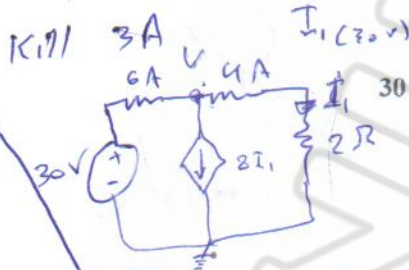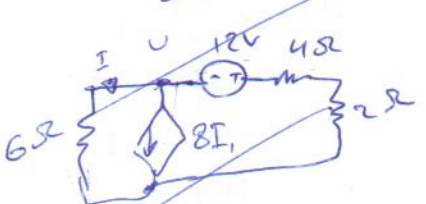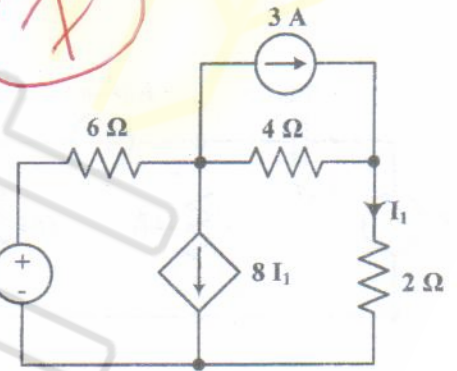

$$\frac{V-30}{6} + \frac{V}{6} + 8I_1 = 0$$

$$\frac{V-30}{6} + \frac{V}{6} + 8\frac{V}{6} = 0$$

$$I_1 = \frac{V}{6}$$

$$10V = 30$$

$$V = 3$$

$$I_1 = \frac{V}{6} = \frac{3}{6} = 0.5$$

$$\frac{V}{6} + \frac{V+12}{6} + 8I_1 = 0$$

$$8I_1 + I_1 = I_1$$

$$9I_1 = I_1$$



$$I_1 = \frac{V}{6}$$

$$9I_1 = \frac{V}{6}$$

$$54I_1 + \frac{44I_1}{6} + \frac{12}{6} + \frac{48I_1}{6} = 0$$



$$156I_1 = -12$$

Kill 3A 30V

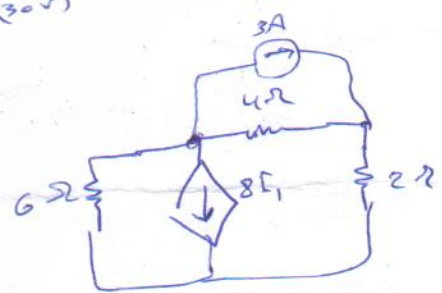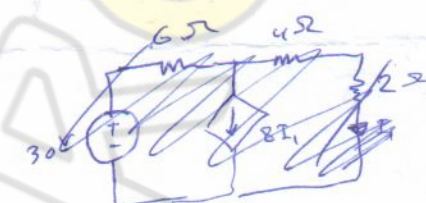

$$I_1 = I_{1(30V)} + I_{1(3A)}$$

$$= 0.7 \text{ A}$$

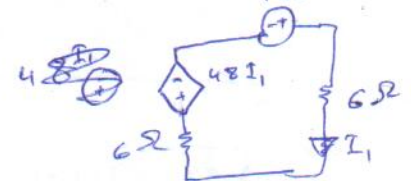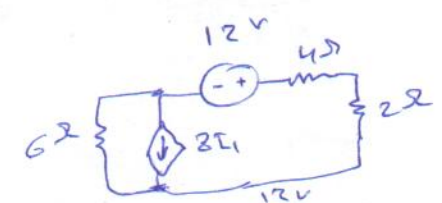

$$4.8I_1 - 12 + 6I_1 + 6I_1 = 0$$

$$60I_1 = 12$$

$$I_1 = \frac{12}{60}$$

$$I_{1(3A)} = 0.2 \text{ A}$$

$$I_1 = 0.7 \text{ A}$$


Problem 5: Study the following circuit then determine the following, (10 points)

(a) $I_L(0^-)$

(b) $V_C(0^-)$

(c) $I_L(t), t > 0$

(d) $V_C(t), t > 0$

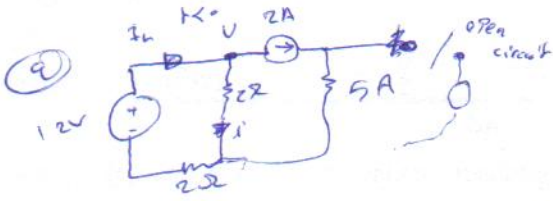

$$-12V + 2A + 2I_L = 0$$


$$I_L - 2 = 0 \Rightarrow I_L = 2A$$

$$-12 + 2I_L - 4 + 2I_L = 0$$

$$-12 + 4I_L - 4 = 0$$

$$4I_L = 16$$

$$I_L = 4A$$

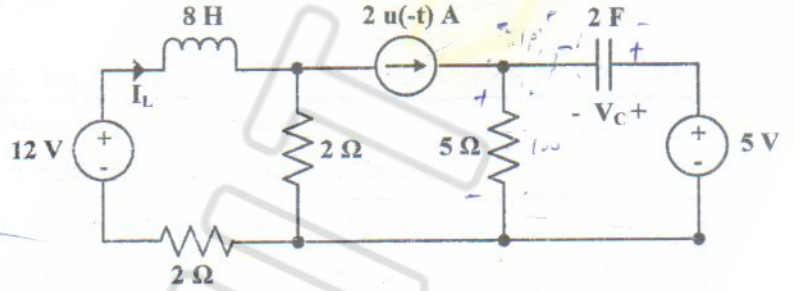

$$V_C(0^-) = -V_{5\Omega} = -(2A \times 5\Omega)$$

$$= -(2 \times 5) = -10V$$

$$I_L(t) = I_{ss} + A e^{-t/\tau}$$


$$I_L(t) = 3.5 + A e^{-t/2.33}$$

$$I_L(0) = I_L(0) = 4A$$

$$4 = 3.5 + A$$

$$A = 0.5A$$

$$I_L(t) = 3.5 + 0.5 e^{-t/2.33}$$

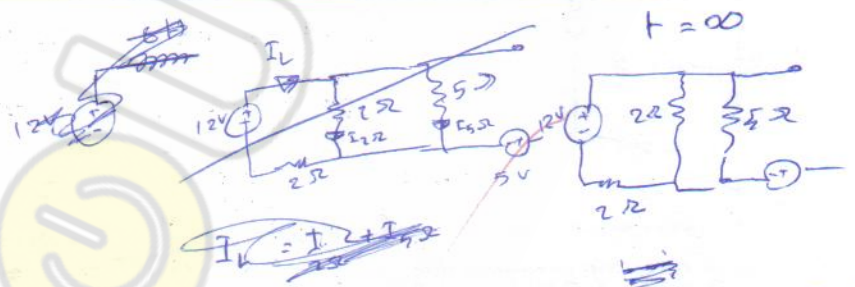


$$\tau = \frac{L}{R}$$

$$= \frac{8}{3.42}$$

$$= 2.33$$

$$I_L = \frac{12}{(2/1/5) + 2} = 3.5A$$

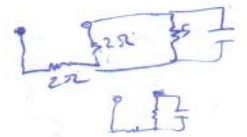

$$V_C(t) = V_{ss} + A e^{-t/\tau}$$

$$= 3.57 + A e^{-t/0.233}$$

$$V_C(0) = -10 = 3.57 + A$$


$$A = -13.57V$$

$$V_C(t) = 3.57 - 13.57 e^{-t/0.233}$$

$$\tau = RC$$

$$= 2 \times (2/1/5)$$

$$= 0.233$$

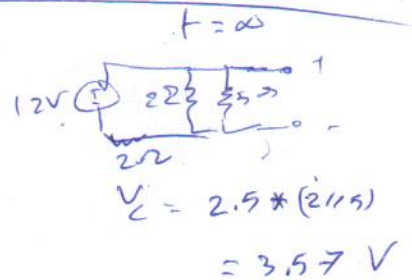

$I_L(0^-) =$	4 A	$V_C(0^-) =$	-10 V
$I_L(t) =$	$3.5 + 0.5 e^{-t/2.33} A$	$V_C(t) =$	$3.57 - 13.57 e^{-t/0.233} V$