



**UNIVERSITY OF JORDAN
FACULTY of ENGINEERING & TECH.
ELECTRICAL ENGINEERING DEPT.**

EE 211

2nd Exam

4-12-2013

8:75 min

20
30

الاسم: الرقم الجامعي: ٠١٢٠٣٨٧




Instructor:

Dr. Othman Alsmadi

Dr. Raed Alzubi

Eng. Reem Aldebs

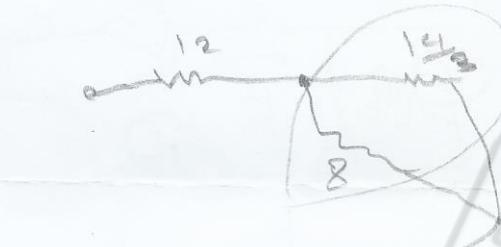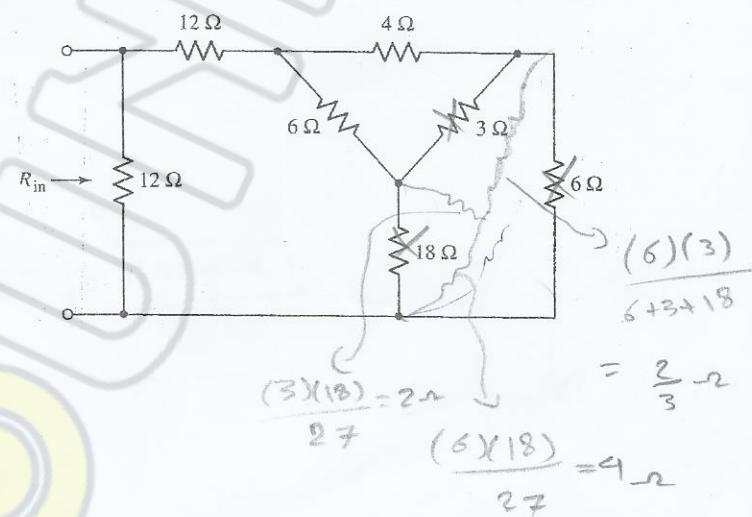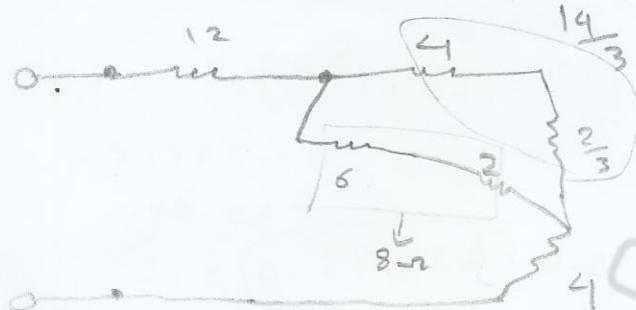
Q1) (4 marks) Determine R_{in} in the following circuit.



$$P_{in} = \frac{36.0}{19} = 18.917 \text{ N}$$

2(3)

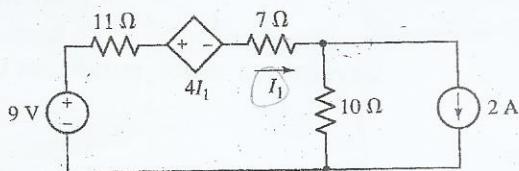(6 marks) Use superposition principle to find I_1 in the following circuit. Show all your work's details.



$$-9 + 11\bar{I}_1 + 4\bar{I}_1 + 7\bar{I}_1 + 10\bar{I}_1 = 0$$


$$-9 + 32\bar{I}_1 = 0$$

$$32\bar{I}_1 = 9$$

$$\bar{I}_1 = 0.28125 \text{ A} \text{ due to } 9\text{V-source}$$

9V-source

6

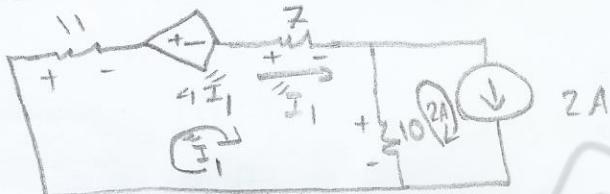

$$11\bar{I}_1 + 4\bar{I}_1 + 7\bar{I}_1 + 10(\bar{I}_1 - 2) = 0$$

$$32\bar{I}_1 - 20 = 0$$


$$\bar{I}_1 = \frac{20}{32} = \frac{5}{8} = 0.625 \text{ A} \text{ due to } 2\text{A-source}$$

2A-source

$$\therefore I_1 = \bar{I}_1 + \bar{I}_1 = 0.28125 + 0.625 = \frac{29}{32} = 0.90625 \text{ A}$$

(7 marks) For the following circuit:

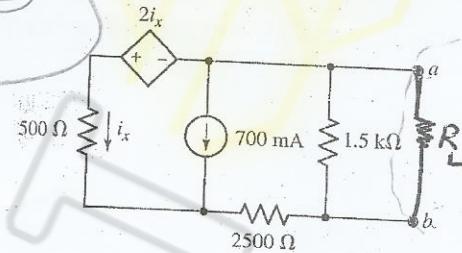- Find V_{TH} seen by the load R_L .
- Find I_N seen by the load R_L Norton
- Determine R_L to get maximum power transferred.
- Calculate P_{Lmax}



a) $V_{TH} = V_{oc} = -116.25 \text{ V}$



b) $I_N = \frac{V_{TH}}{R_{TH}}$



$$= -0.116278 \text{ A}$$

c) $R_L = R_{TH} = \frac{V_{TH}}{I_{sc}} = 999.759 \Omega$

$$500(-ix) + 2ix + (1.5)10^3 i_2 = 0$$

$$2500 i_2 = 0$$

$$(-ix - i_2) = 700 \cdot 10^{-3}$$

$$ix + i_2 = -0.7$$

d) $P_{Lmax} = \frac{(V_{TH})^2}{4R_{TH}} = 3.37933 \text{ Watt}$


$$ix = \frac{-1400}{22499} = -0.6225 \text{ A}$$

$$i_2 = \frac{-1743}{22499} = -0.0775 \text{ A}$$

$$V_{oc} = (1.5)(10^3) / -0.0775$$

$$V_{oc} = \frac{-965}{4} = -116.25 \text{ V}$$

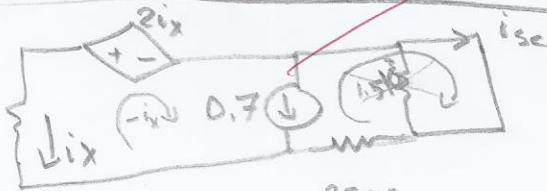Same symbols
does not necessarily
represent the
same thing
in this box
(not exactly)




$$500(-ix) + 2ix + 2500i_{sc} = 0$$

$$-ix - i_{sc} = 0.7$$

$$ix = \frac{-875}{1499} = -0.5837 \text{ A}$$

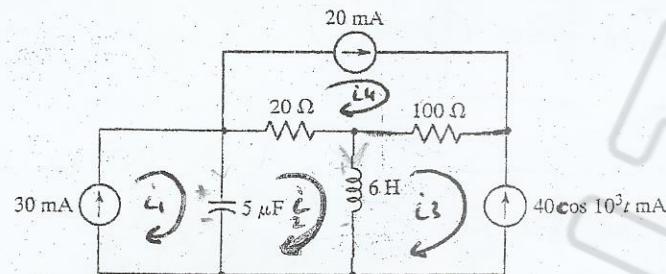• (4 marks) Write mesh equations for the following circuit. (Don't solve the integro-differential equation)



$$i_1 = 30 \cdot 10^{-3} \text{ A}$$

$$6 \frac{d(i_2 - i_3)}{dt}$$

$$v = \frac{1}{c} \int_{t_0}^t i_1 dt + V_0$$

$$\left\{ \begin{array}{l} t_0 \\ i_1 = i_2 \end{array} \right.$$

$$5 \cdot 10^6$$

$$-\frac{1}{c} \int_{t_0}^t (i_1 - i_2) dt - V_0 + 20(i_2 - i_4) + 6 \frac{d(i_2 - i_3)}{dt} = 0$$

$$-\left(\frac{10^6}{5}\right) \int_{t_0}^t (30 \cdot 10^{-3} - i_2) dt + V_0 + 20(i_2 - i_4) + 6 \frac{d(i_2 - i_3)}{dt} = 0 \quad \dots \textcircled{1}$$


$$i_3 = -40 (\cos 10^3 t) \cdot 10^{-3} \text{ A}$$

$$i_4 = 20 \cdot 10^{-3} \text{ A}$$

$$-\left(\frac{10^6}{5}\right) \int_{t_0}^t (30 \cdot 10^{-3} - i_2) dt + V_0 + 20(i_2 - 20 \cdot 10^{-3}) + 6 \frac{d(i_2 + 40 \cos 10^3 t)}{dt} = 0$$


= 0

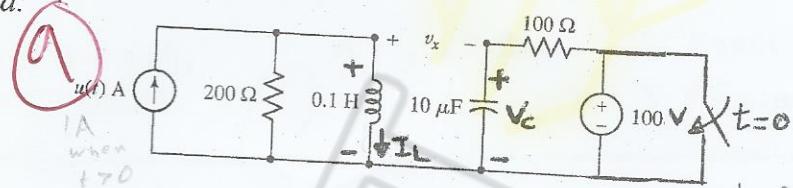a) (9 marks) For the following circuit, find:



a) $V_C(0^-) = 100 \text{ V}$

✓ ①

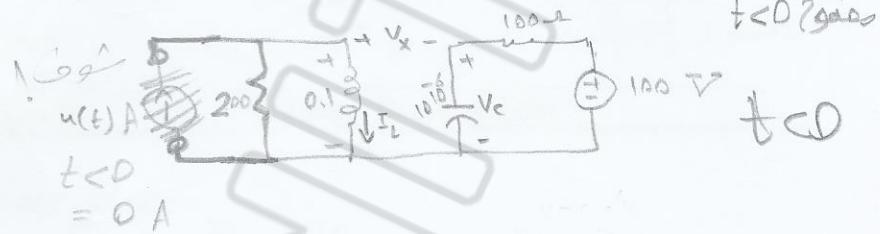

b) $I_L(0^-)$ and $I_L(0^+)$

$I_L(0^-) = I_L(0^+) = 0$

✓ ②



c) $I_L(\infty) = 1 \text{ A}$

✓ ③



d) τ of the RL circuit and τ for the RC circuit

$$\tau = \frac{L}{R_{\text{eq}}} = \frac{0.1}{200} = 5 \cdot 10^{-4} \text{ s}$$

②

$$\tau = R C_{\text{eq}} = (100)(10 \cdot 10^{-6}) = 10^{-3} \text{ s}$$

e) $V_L(t)$ for $t > 0$

$$V_L(0^+) = 0$$

$$= V_{200}(0^+) = (1)(200) \cdot 1 \text{ A} = 200 \text{ V}$$

$$V_L(\infty) = 0$$

$$1 \text{ A} \quad \frac{1}{200} \text{ s} \quad 0.1$$

$$V_L(t) = 0 + A e^{-t/5 \cdot 10^{-4}}$$

$$V_L(t) = A e^{-t/5 \cdot 10^{-4}}$$

$$\Rightarrow 200 = A e^{0}$$

$$\therefore A = 200$$

$$\therefore V_L(t) = 200 e^{-t/5 \cdot 10^{-4}}$$

①

f) $V_C(t)$ for $t > 0$

$$V_C(t) = 100 e^{-t/10^3}$$

$$-t/5 \cdot 10^{-4} \quad -t/10^3$$

$$V_C(t) = V_C(0) - V_C(\infty) = 200 e^{-t/5 \cdot 10^{-4}} - 100 e^{-t/10^3}$$

✓ ①

Good luck