

Power Unit

Circuits 1

Pastpaper

first exam


summer semester

2014-2015

Dr. ghazi alsukkar

25 Q1 (25 marks): For the network shown in Fig. 1, find the equivalent resistance between terminal a and b (R_{ab}).

power unit

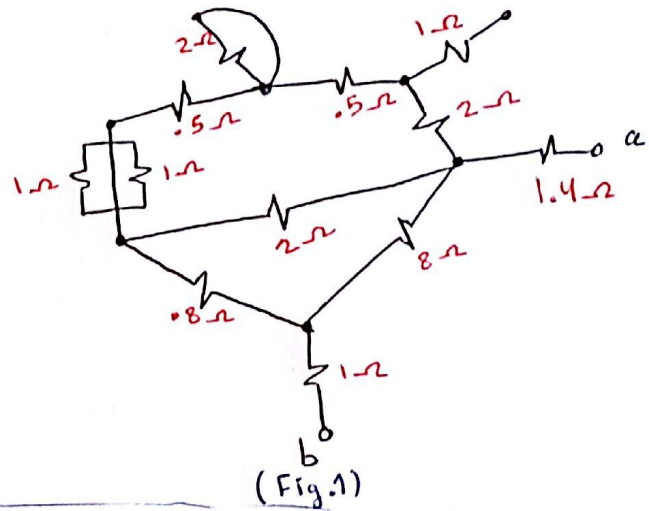

Q2 (25 marks): The network shown in Fig. 2 is the visible part of a circuit, given that the power delivered by the 6V source is 12 watt, and $V_{bc} = 26V$, find i_1 , i_2 , i_3 and V_{ab} .

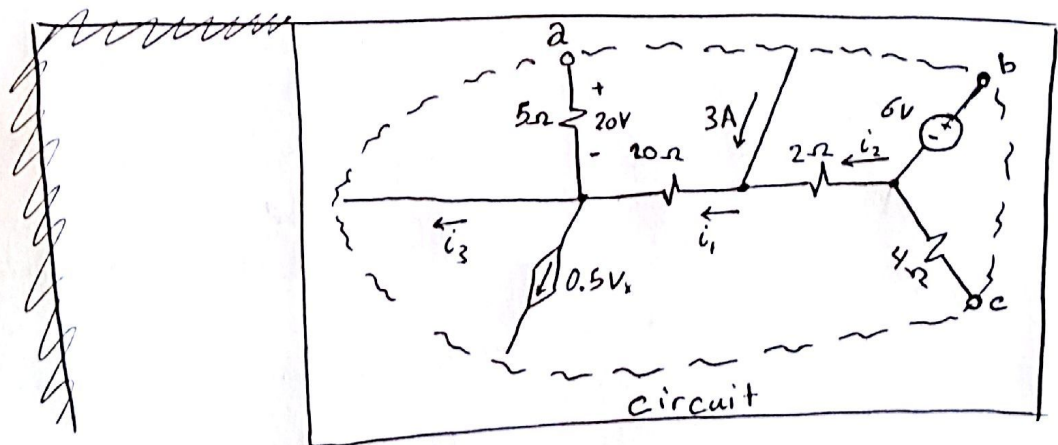


Fig. 2

Circuits 1

First exam

Dr. Ghazi Al sukkar

Summer semester

2014-2015

Power unit


* كل سؤال كان من 25 علامة
* ٤ أسئلة *

power unit

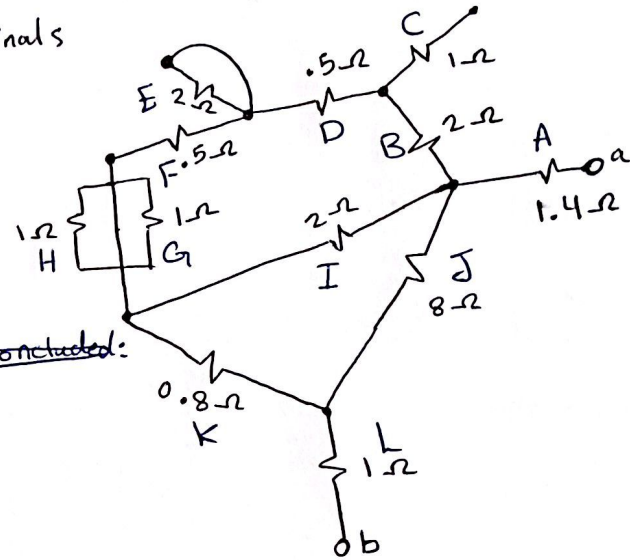Q1 Find equivalent resistance in the Figure between the two terminals a and b (R_{ab})

لستعمل على حل سؤال سوف أحسب كل Resistances بزرف .

by looking at the ~~circle~~ i concluded:
~~A and L are parallel with the rest of the circle~~



By looking at the ^{circuit} ~~circle~~ i concluded:

* ~~Resistances~~ Resistances A and L are in series with the rest of the ^{circuit} ~~circle~~

* C, E, H, G are not included in the calculations why?

- C ~~are~~ because it has a ~~dead~~ dead end

- E because it's ~~not~~ neither in parallel nor in series with the rest of the CKT.

- H & G because of the wire between them \Rightarrow short CKT

الباقي، يعني، الطريقة الأقل المقامه

بزرف

اذا قلنا ان CKT أسهل:

- B & D & F in series $\Rightarrow 2 + 0.5 + 0.5 = 3\Omega$


- I & (B, D, F) in parallel $\Rightarrow \left(\frac{1}{2} + \frac{1}{3}\right)^{-1} = \frac{6}{5} = 1.2\Omega$

*

- Z & K in series $\Rightarrow 1.2 + 0.8 = 2\Omega$

- J & (Z, K) in parallel $\Rightarrow \left(\frac{1}{8} + \frac{1}{2}\right)^{-1} = 1.6\Omega$

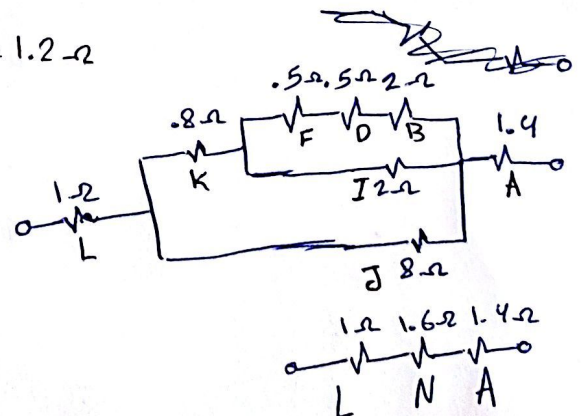$R_{ab} = L + N + A = 1.4 + 1.6 + 1 = 4\Omega$




power unit

Q2 * Power delivered by the 6V source is 12 watt

* $V_{bc} = 26 \text{ Volt}$

* find i_1, i_2, i_3 & $V_{ab}??$

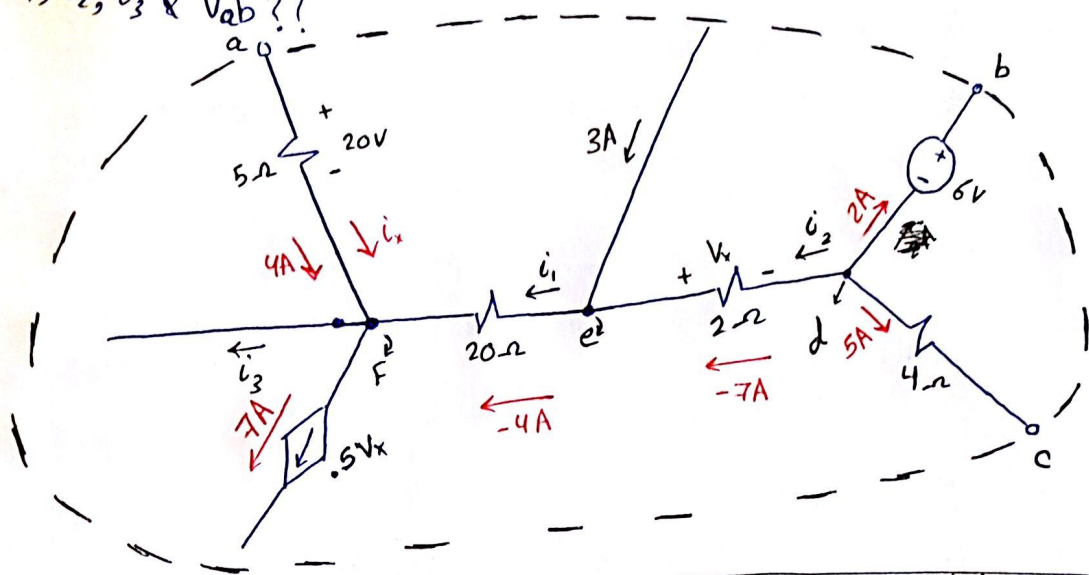

Step 1: * اقرب بالابواب

* $P = IV$
 $P_{6V} = IV$
 $12 = 6I_{6V}$
 $I_{6V} = 2A$

$V_{bc} = 26V$
 $V_{bc} = 6 + 4I_{4\Omega}$
 $26 = 6 + 4I_{4\Omega}$
 $20 = 4I_{4\Omega}$
 $5A = I_{4\Omega}$

$V = IR$

Step 2 use the methods \rightarrow KCL \rightarrow KVL to find the unknowns.

KCL at node d:

$I_{out} = I_{in}$
 $2 + 5 + i_2 = 0$
 $i_2 = -7A$

KCL at node e:

$I_{out} = I_{in}$
 $i_1 = 3 + -7$
 $i_1 = -4A$

$V_x = IR$
 $= 7 \times 2$
 $V_x = 14V$

$i_x = \frac{V}{R}$
 $= \frac{20}{5}$
 $i_x = 4A$

دروود اقلوا عنان نطلع i_3

KCL at node f

$I_{in} = I_{out}$
 $-4 + 4 = i_3 + 7$
 $i_3 = -7A$

V_{ab}


~~from a to f~~
 $a \rightarrow f = 20V$
 $f \rightarrow e = 4 \times 20 = 80V$ (Ohm's law)
 $e \rightarrow d = V_x = 14V$
 $d \rightarrow b = -6V$

$V_{ab} = 20 + 80 + 14 - 6$
 $V_{ab} = 108 \text{ Volt}$

Q3: Find V_1, V_2, V_3, V_4
 Find V_1, V_2, V_3, V_4 by Nodal Analysis:

فكرة هاد السؤال كالتالي افصل الدارة لدارتين وعلما Nodal


CKTB

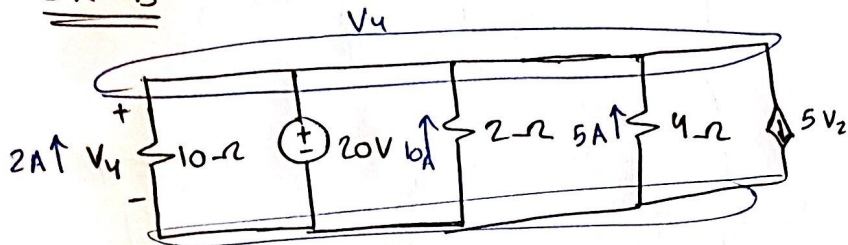

$V_4 = 20V$

~~Handwritten scribbles and equations, including $I_{in} = I_{out}$ and $V_2 = \frac{10}{10} + \frac{20}{12} + \frac{20}{4}$.~~

CKTA

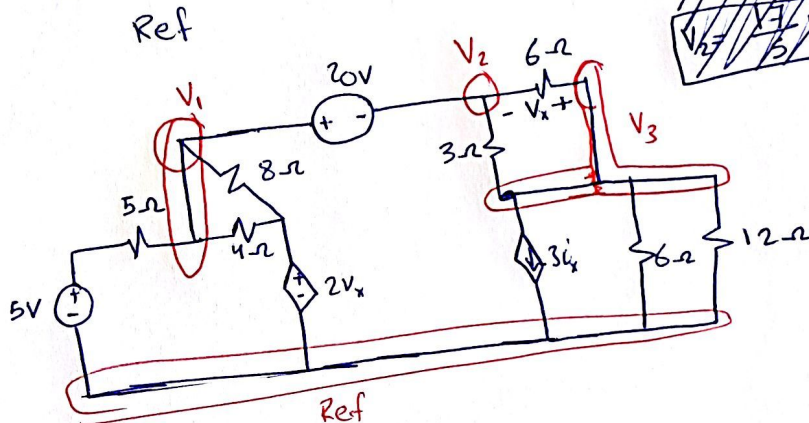

~~super node~~

~~Handwritten scribbles and equations.~~

at super node (1-2):

$$\frac{V_1 - 2V_x}{8} + \frac{V_1 - 2V_x}{4} + \frac{V_1 - 5}{5} + \frac{V_2 - V_3}{3} + \frac{V_2 - V_3}{6} = 0$$

$V_1 - V_2 = 20$

$V_x = V_3 - V_2$

at node 3

$$\frac{V_3 - V_2}{6} + \frac{V_3}{12} + \frac{V_3}{6} = 0$$


power unit

① $\frac{V_1 - 2V_3 + 2V_2}{8} + \frac{V_1 - 2V_3 + 2V_2}{4} + \frac{V_1 - 5}{5} + \frac{V_2 - V_3}{3} + \frac{V_2 - V_3}{6} = 0$

② $V_1 - V_2 = 20$


④ $V_4 = 20V$

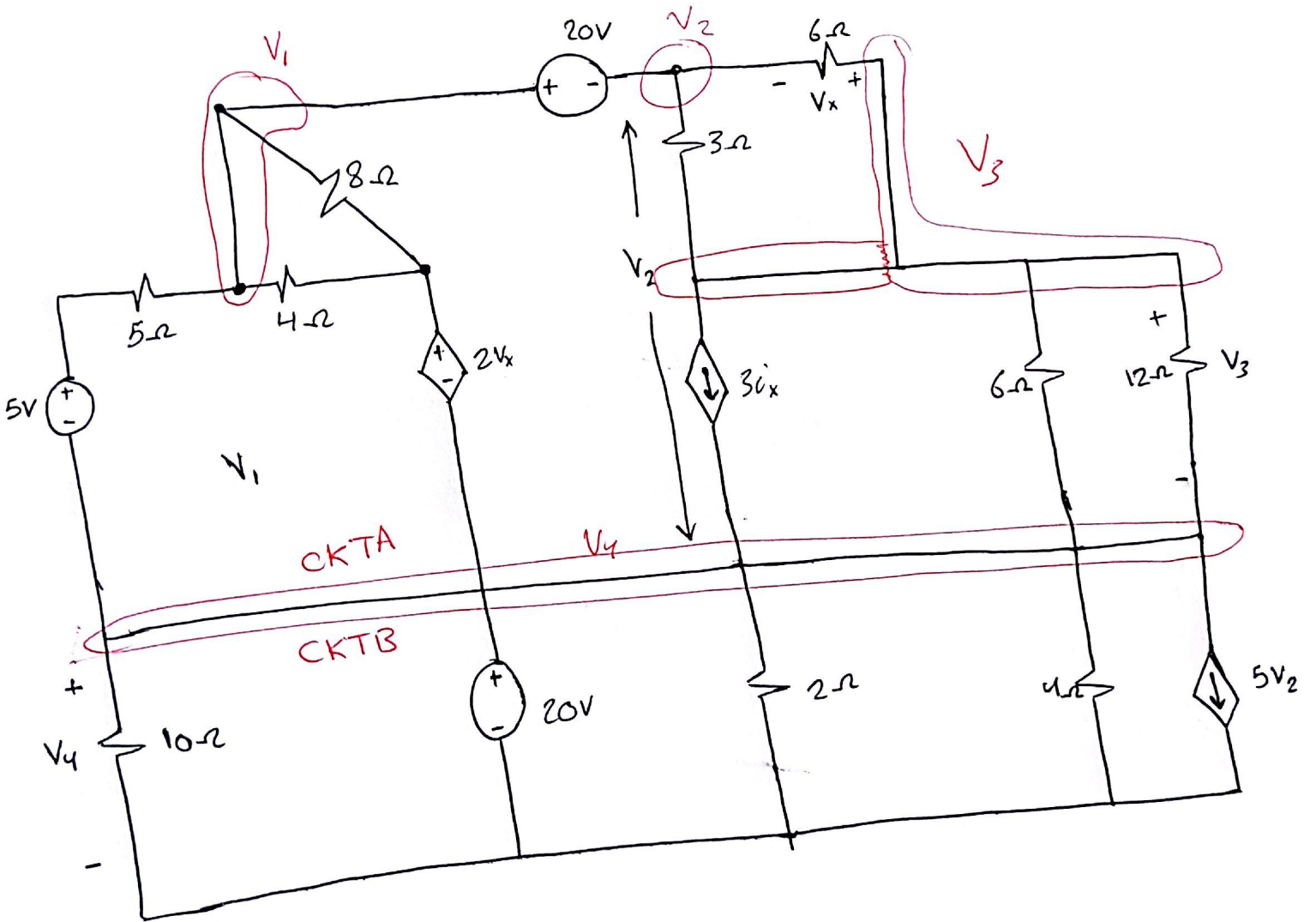③ $\frac{V_3 - V_2}{6} + \frac{V_3}{12} + \frac{V_3}{6} = 0$



power unit

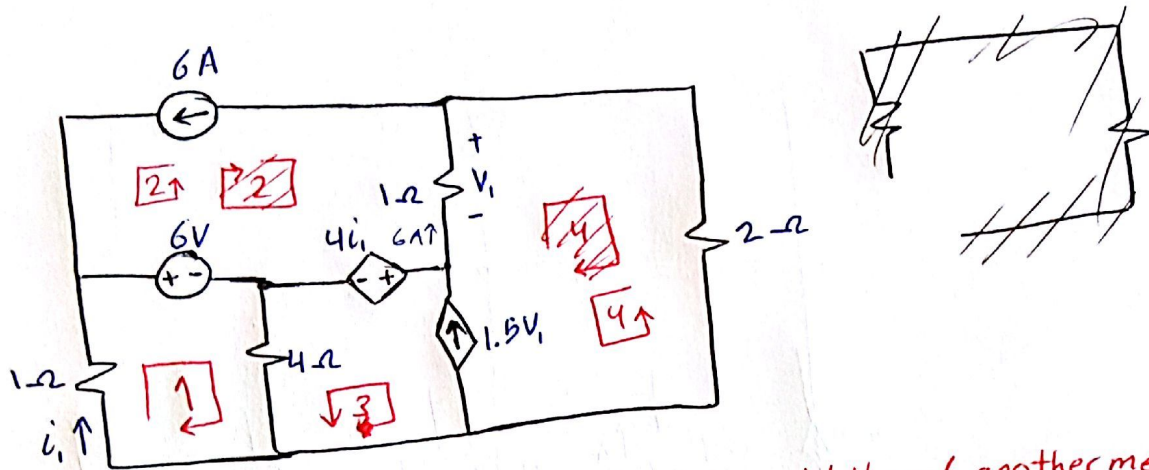Q4: Use mesh analysis to find i_1 & V_1 .



i have concluded that $i_2 = 6A$ so that *i* wouldn't need another mesh (equation).

@ Mesh 1

$$i_1 + 6 + 4i_1 - 4i_3 = 0$$

$$\textcircled{1} \quad 5i_1 + 4i_3 = -6$$

@ Super mesh (3-4)

$$i_4 + 2i_4 - 6 + 4i_1 + 4i_3 + 4i_1 = 0$$

~~$$3i_4 + 4i_1 + 4i_3 = 6$$~~

$$3i_4 + 4i_1 + 4i_3 = 6 \quad \textcircled{2}$$

$$i_3 - i_4 = 1.5V_1$$

$$= \frac{3}{2}i_4 - 9$$

$$i_3 - \frac{5}{2}i_4 = -9 \quad \textcircled{3}$$

~~$i_2 + i_3 = \dots$~~
~~mesh 2~~
 ~~$i_2 = 6A$~~

$$V_1 = i_4 - 6$$

$$\textcircled{1} \quad 5i_1 + 4i_3 = -6$$

$$\textcircled{2} \quad 4i_1 + 4i_3 + 3i_4 = 6$$

$$\textcircled{3} \quad i_3 - \frac{5}{2}i_4 = -9$$

$$i_1 = -1.2A$$

$$i_3 = 0A$$

$$i_4 = 3.6A$$

$$V_1 = i_4 - 6$$

$$V_1 = -2.4V$$

power unit