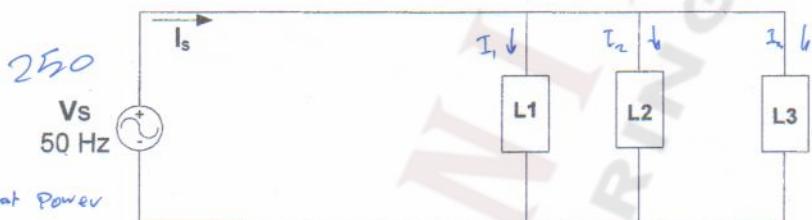


(Marks) Q(1): Three loads are connected in parallel across 250V (rms) as shown in Fig.1. Load 1 absorbs 16kW and 28 kVA. Load 2 absorbs 10kVA at 0.6 leading PF. Load 3 absorbs 8KW at unity PF.

- 1- Find the Impedance that is equivalent to the three parallel loads.
- 2- Find the power factor of the total load.
- 3- If the source operates at 50 Hz, find the value of the capacitor to be connected in order to improve the power factor to 0.96.



(i) $V I_1 = \text{apparent Power}$

$$\frac{28 \text{ kVA}}{250 \text{ V}} = I_1 = 112 \text{ Arms}$$

$$\text{P.F. } 1 = \frac{P}{\text{apparent Power}} = \frac{16 \text{ kW}}{28 \text{ kVA}} = 0.57 = \cos(\theta_1 - \phi_1) = \cos(-\phi_1)$$

Fig. 1

$$\phi_1 = \cos^{-1}(0.57)$$

$$\phi = -55.15^\circ$$

Lagging

$$I_1 = 112 \angle -55.15^\circ \text{ Arms}$$

$$L_1 = \frac{V}{I_1} = \frac{250 \angle 0^\circ}{112 \angle -55.15^\circ} \Rightarrow L_1 = 1.275 + j1.83 \text{ } \Omega$$

(ii) $V I_2 = 10 \text{ kVA} \rightarrow I_2 = \frac{10 \text{ kVA}}{250 \text{ V}} = 40 \text{ Arms}$

$$\text{P.F. } 2 = \cos(\theta - \phi) = 0.6$$

~~$$\cos \phi = \cos^{-1}(0.6)$$~~

$$\phi = 53.13^\circ$$

~~$$L_2 = 40 \angle 53.13^\circ \text{ Arms}$$~~

$$L_2 = \frac{V}{I_2} = \frac{250 \angle 0^\circ}{40 \angle 53.13^\circ} \Rightarrow L_2 = \cancel{2.75 - j3.75} \text{ } \Omega$$

$$L_2 = 3.75 \angle -55^\circ \text{ } \Omega$$

(iii)

$$I_3 \sqrt{\cos(\phi)} = 8 \text{ kW}$$

$$I_3 = 32 \text{ Arms}$$

$$L_3 = \frac{250 \angle 0^\circ}{32 \text{ Arms}} = 7.8125 \text{ } \Omega$$

$$Z_{eq} = \left(\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \right)^{-1} = \left(\frac{1}{1.275 + j1.83} + \frac{1}{3.75 - j5} + \frac{1}{7.8125} \right)^{-1}$$


$$Z_{eq} = 1.666 + j0.832 \text{ } \Omega$$

$$Z_{eq} = 1.666 + j0.832 \text{ } \Omega$$

~~$\text{P.F.} = \cos\theta$~~

$$Z_{eq} = 1.86 \angle 26.538^\circ$$

$$\text{P.F.} = \cos(26.538) = 0.8946 \text{ lagging}$$

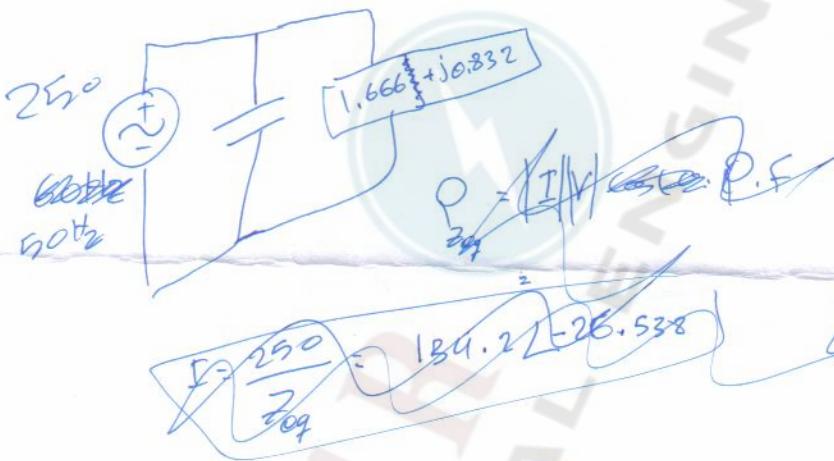~~+ $\angle 13^\circ$~~ 

$$\text{P.F.} = 0.8946 \text{ lagging}$$

$$P = P_L + P_{L2} + P_{L3}$$

~~$= 16 \text{ kW} + 10 \text{ kVA} * \cos\theta + 31 \text{ kW}$~~

~~$= 30 \text{ kW}$~~


$$C = \frac{P}{\omega V_{rms}^2} = \frac{P_2}{\tan\theta_2} = 1.2 \text{ mF}$$

~~J~~

$$C = 1.2 \text{ mF}$$

Q(2): Fig.2 shows the instantaneous power $p(t)$ consumed by the load terminals, where terminal voltage is given by $v(t) = V_m \cos(\omega t)$, then find the followings:

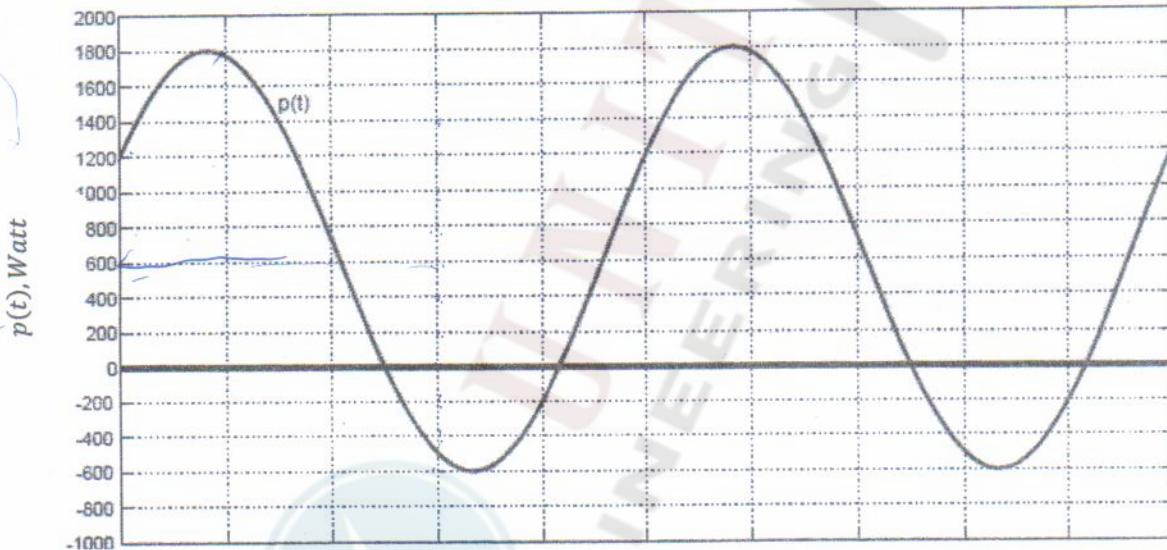- 1- PF.
- 2- The reactive power Q .
- 3- The Complex power S .



$P = 600 \text{ watt}$

Fig. 2

Apparent Power = $\frac{1800 - (-600)}{2} = 1.2 \text{ kVA}$

$P.F = \frac{P}{A.P} = \frac{600}{1.2 \text{ k}} = 0.5$

~~Efficiency~~

~~$\cos(\theta - \phi) = 0.5$~~
 ~~$\theta - \phi = \cos^{-1}(0.5)$~~
 ~~$\theta - \phi = 60^\circ$~~
 ~~$\phi = -60^\circ$~~

~~$P.F = 0.5 \text{ Lagging}$~~

$Q = \text{Apparent power } \sin(\theta - \phi)$
 $= 1.2 \text{ kVA } \sin(0 - (-60))$
 $= 1.039 \text{ kVAR}$

~~$Q = 1.039 \text{ kVAR}$~~

~~$S = 600 + j1039$~~
 ~~$S = P + jQ$~~
 ~~$= 600 + j1039$~~

~~$S = 600 + j1039$~~

(marks) Q(3): In the system shown in Fig.3, given $Z_Y = 20 + j8 \Omega$, and (+) phase sequence is assumed. If $I_{aA} = 20\angle-46^\circ A$ rms, and the source is operating with $PF = 0.94$ lagging, find the following:

- 1- R_w
- 2- The total complex power supplied by the source
- 3- V_{an} .
- 4- V_{AB} .


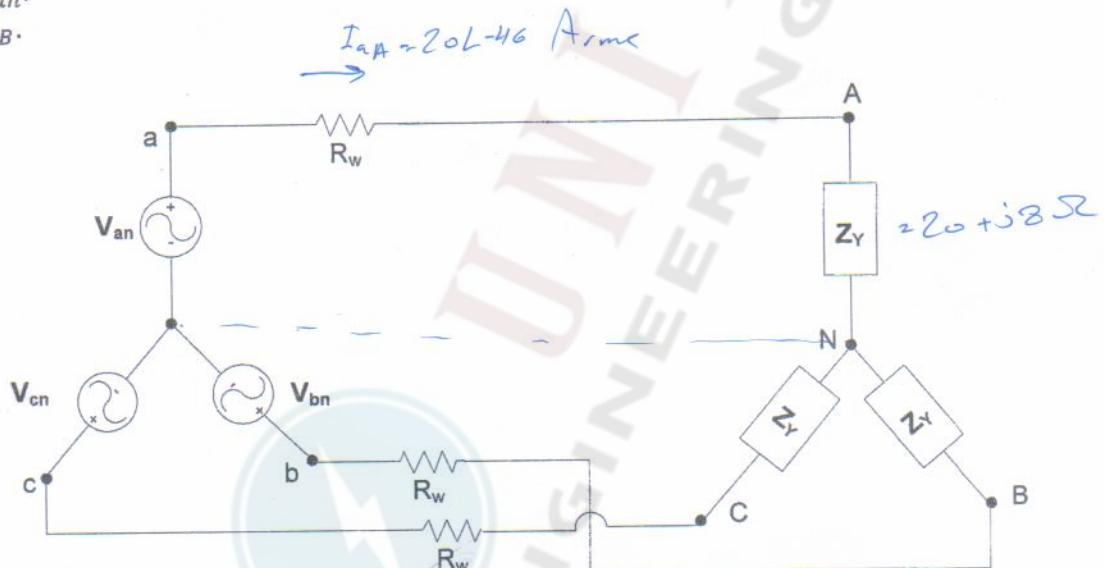


Fig. 3

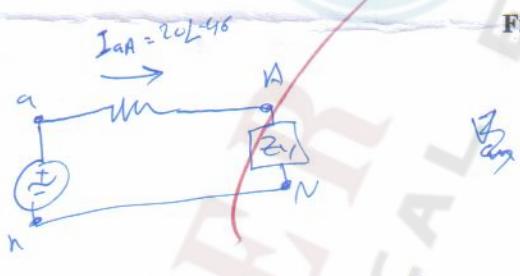

$$\cos^{-1}(0.94) = \theta + 46^\circ$$

$$\theta = -26.05^\circ$$

$$\theta - \phi = 19.95^\circ$$



~~$\cos(\theta - \phi) = L Z_Y + R$~~
 ~~$\theta - \phi = L Z_Y + R$~~

$$19.95 = L Z_Y + R$$

~~$\tan(\theta - \phi) = \frac{R}{L Z_Y}$~~

$$\tan 19.95 = \frac{8}{20 + R}$$

$$\tan 19.95 = \frac{8}{20 + R}$$

$$0.363 = \frac{8}{20 + R}$$

$$0.363(20 + R) = 8$$

$$7.26 + 0.363R = 8$$

$$R_w = 2.038 \Omega$$

$$R_w = 2.038 \Omega$$

Section: 1:00 - 2:00

Dr. Ghazi
Soltan

9:00 AM

$$I R = V$$

$$V = 20 L - 46 * 22.032 + j8$$

$$V_{an} = 468.9 L - 26.05$$

$$\boxed{S = P + jQ}$$

$$Q = |I| V \cos(\theta - \phi)$$

$$= (20 * 468.9) 0.94$$

$$Q = 8815.3 \text{ W}$$

 ζ

$$Q = (20 * 468.9) \sin(\theta - \phi)$$

$$= 3199.7 \text{ VAR}$$

$$\boxed{S = (8.815 + j3.199) \text{ kW}}$$

$$V_{an} = 468.9 L - 26.05$$



$$\boxed{V_{an} = 468.9 L - 26.05} \quad V$$

$$V_{AN} = I Z_Y$$

$$= 430.8 L - 24.2$$

$$V_{AB} = \sqrt{3} V_{AN} L^{+30^\circ}$$

$$= 746.2 L^{+5.8}$$

$$\boxed{V_{AB} = 746.2 L^{+5.8}} \quad V$$

Good Luck
Thank You ^{6/6} ☺