

Encircle the answer.

ke a mistake, mark a cross through your wrong choice and circle your next al

1. a b c d e

2. a b c d e

✓ 3. a b c d e

✗ 4. a ~~b~~ c d e

5. a b c d e

6. a b c d e

7. a b c d e

8. a b c d e

9. a b c d e

✗ 10. a b c d e

11. a b c d e

12. a b c d e

NAME: _____
 Please write your name in arabic

Question 1: A three-phase balanced voltage source feeds the load shown in the Fig.Q1 $V_{AB} = 400 \angle -30^\circ$
 V_{rms} .

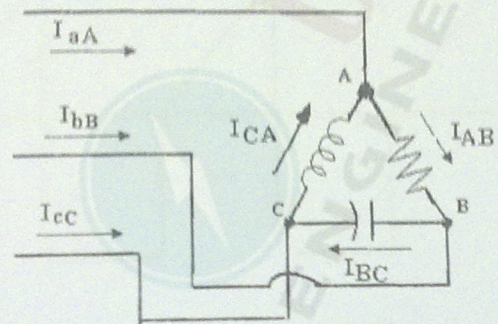


Figure: Q1

$\odot I_{CA}$

- The phase current angle of I_{CA} :
- (a) 60° .
 - (b) -60° .
 - (c) None of these.
 - (d) -30° .
 - (e) 30° .

Question 2: Fig.Q2, shows voltage $v(t)$ and current $i(t)$ when terminals ab in Fig.Q2(b) are opened and shorted respectively

NAME: _____
 Please write your name in arabic

Question 1: A three-phase balanced voltage source feeds the load shown in the Fig.Q1 $V_{AB} = 400\angle -30^\circ$
 V_{rms} .

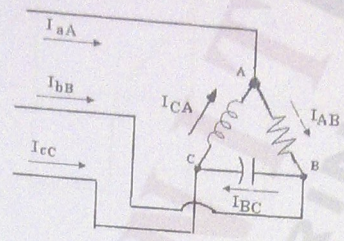



Figure: Q1

$\angle I_{CA}$

The phase current angle of I_{CA} :

- a) 60° .
- b) -60° .
- c) None of these.
- d) -30° .
- e) 0° .

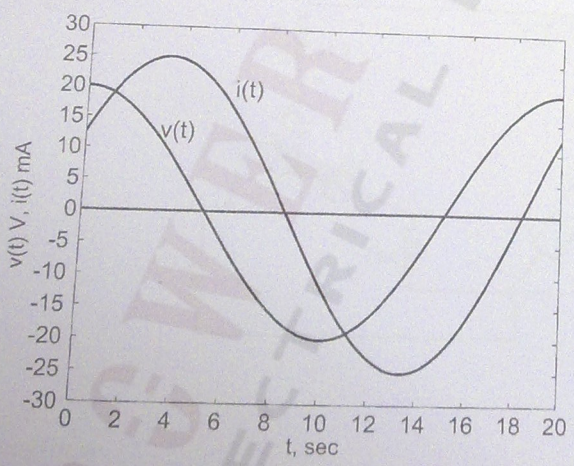Question 2: Fig.Q2, shows voltage $v(t)$ and current $i(t)$ when terminals ab in Fig.Q2(b) are opened and shorted respectively.



P_{max}


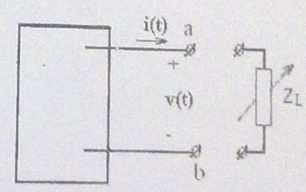
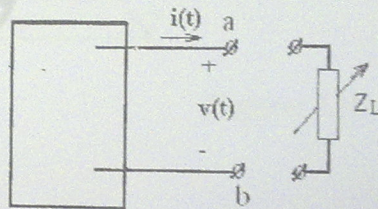


Figure: Q2

If the adjustable load resistance R_L is connected between terminals a & b to transfer the maximum average power to the load. The P_{max} is:

- a) 83.33 mW .
- b) 50 mW .
- c) 80.38 mW .
- d) None of these.
- e) 53.6 mW .

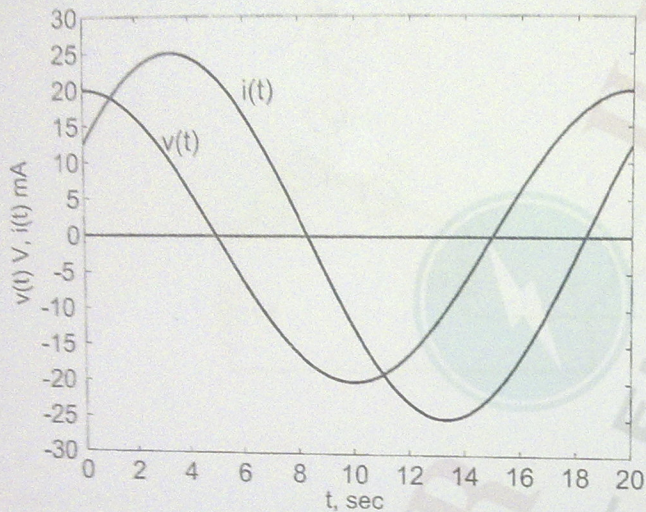Question 2: Fig.Q2, shows voltage $v(t)$ and current $i(t)$ when terminals ab in Fig.Q2(b) are opened and shorted respectively.



P_{max}

Figure: Q2

If the adjustable load resistance R_L is connected between terminals a & b to transfer the maximum average power to the load. The P_{max} is:

- a) 83.33 mW.
- b) 50 mW.
- c) 80.38 mW.
- d) None of these.
- e) 53.6 mW.

Question 4: A three-phase balanced voltage source feeds the load shown in the Fig. Q4. The $400\angle 60^\circ V_{rms}$. The $|Z_Y| = 5\angle 30^\circ \Omega$.

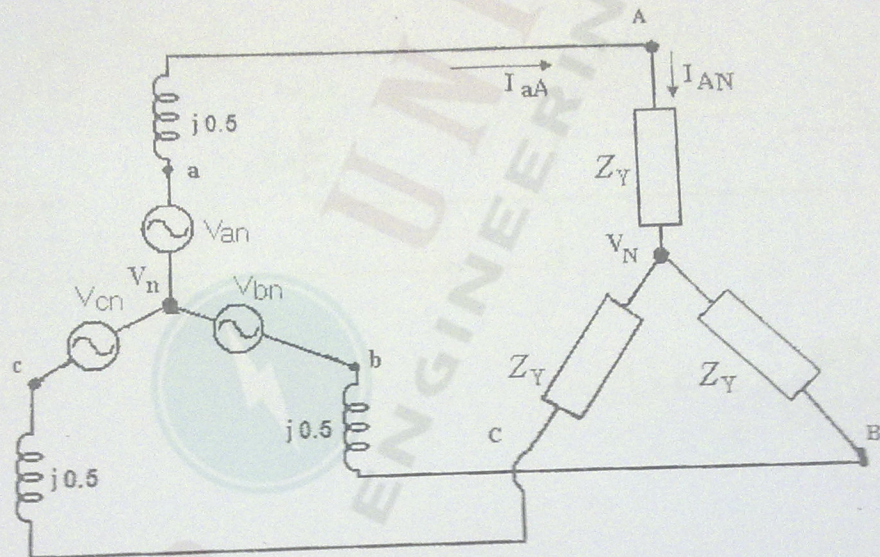


Figure: Q4

The $V_{bn} \simeq$:

- a) None of these.
- b) $252.0\angle -90^\circ A$.
- c) $250.32\angle -30^\circ A$.
- d) $2675.0\angle -132^\circ A$.
- e) $243.73\angle -186^\circ A$.



balanced voltage source feeds the load shown in the Fig.

Question 6: A three-phase voltage source feeds the balanced load shown in the Fig.Q6. The $V_{AB} = 400 \angle 30^\circ$ V_{rms}. The complex power of the load $S_{3\phi} = 9 \text{ kVA} \angle 30^\circ$.

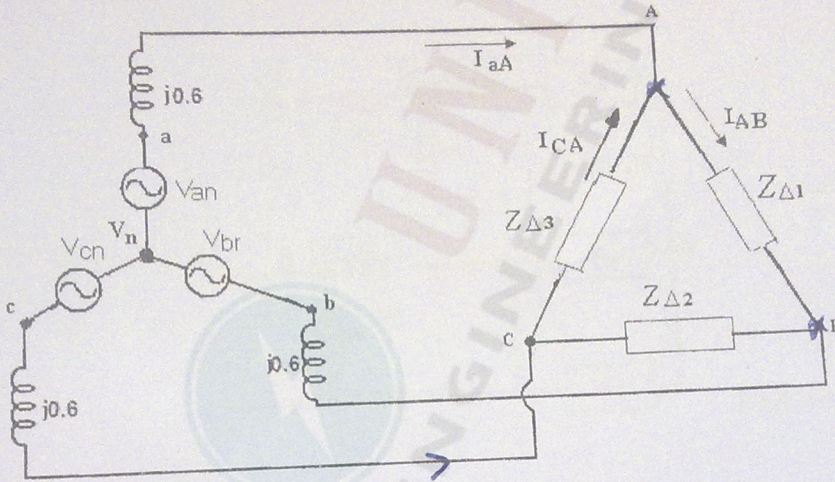


Figure: Q6

The line current \bar{I}_{cC} is:

- a) $12.99 \angle 90^\circ$ A.
- b) $7.5 \angle 90^\circ$ A.
- c) $7.5\sqrt{3} \angle -90^\circ$ A.
- d) $12.99 \angle -120^\circ$ A.
- e) None of these.

$$I_{cC} = I_{CA} - I_{BC}$$

$$= \frac{V_{CA}}{X} - \frac{V_{BC}}{X}$$

$$= 0.133$$

\bar{I}_{cC}
 $S = V$
 $S = 3 \times 1000$

$S = A \times j$
 $P = \frac{S}{\sqrt{3}}$
 2500
 $X = 0.133$

Question 7: Fig.Q7, shows the instantaneous power $p(t)$ absorbed by the load and the voltage $v(t)$ to it. The load composed of two elements in series.

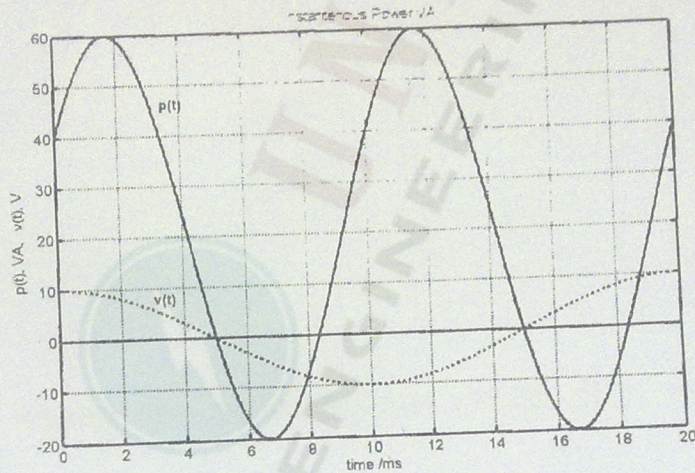


Figure: Q7


The current $i(t)$ is:

- a) $15 \cos(100\pi t + 30^\circ)$.
- b) None of these.
- c) $12 \cos(100\pi t + 60^\circ)$.
- d) $8 \cos(100\pi t - 60^\circ)$.
- e) $10 \cos(100\pi t - 30^\circ)$.

Question 8: The line voltage is $AB = 416 V_{RMS}$ and positive sequence. The load impedance

Handwritten notes:
 $10 \text{ cm} = 360$
 $2 \text{ cm} = \emptyset$
 $5 \times 10 \emptyset = 360^\circ + 2'$
 $\emptyset = \frac{360}{5} = 72$
 $P = 400 \cos(\dots)$

Handwritten equation: $P(t) = i(t) v(t)$

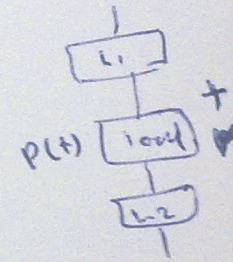

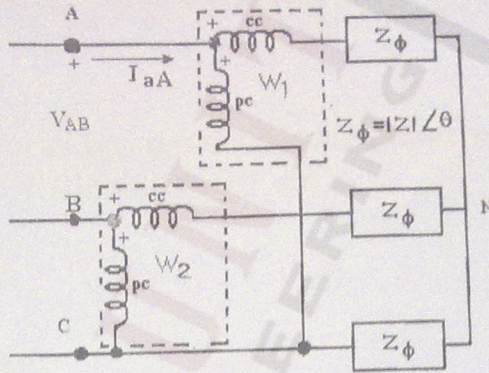


Figure: Q8


The two watt-meters read as:

- a) $W_1 = 2781.6 \text{ W}$, and $W_2 = 11172.5 \text{ W}$.
- b) $W_1 = 2981.6 \text{ W}$, and $W_2 = 16519.17 \text{ W}$.
- c) $W_1 = 11127.5 \text{ W}$, and $W_2 = 2981.6 \text{ W}$.
- d) None of these.
- e) $W_1 = 2981.6 \text{ W}$, and $W_2 = 11127.5 \text{ W}$.

Question 9: In Fig.Q9, the source delivers 7500 VA at $V_s = 250 \angle 30^\circ \text{ V}_{rms}$ with power factor lagging.

$|S| = 7500 \text{ VA}$

$V_s = 250 \angle 30^\circ$

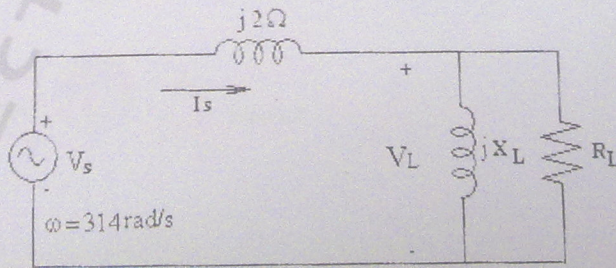

$X_L =$

Signal shown in Fig. Q3 is:

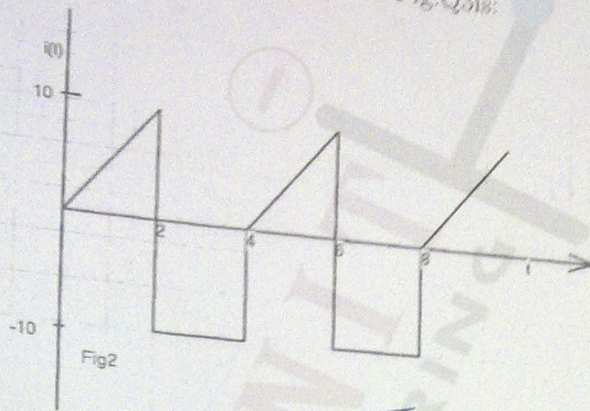


Figure: Q3

- a) 86.7 V.
- b) 6.867 V.
- c) 8.615 V.
- d) None of these.
- e) 8.166 V.

$$\sqrt{\frac{1}{4} [(66.66) + 200]}$$

$$\sqrt{\frac{1}{4} \left[\frac{25t^2}{3} \Big|_0^2 + 100t \Big|_2^4 \right]}$$

$$I_{rms} = \sqrt{\frac{1}{T} \int i(t)^2 dt}$$

$$= \sqrt{\frac{1}{4} \left[\int_0^2 (5t)^2 + \int_2^4 (-10)^2 dt \right]}$$

$$= \sqrt{\frac{1}{4} \left[\int_0^2 25t^2 + \int_2^4 100 dt \right]}$$

Question 4: A three-phase balanced voltage source feeds the load shown in the Fig. Q4. The $400 \angle 60^\circ V_{rms}$. The $|Z_Y| = 5 \angle 30^\circ \Omega$.

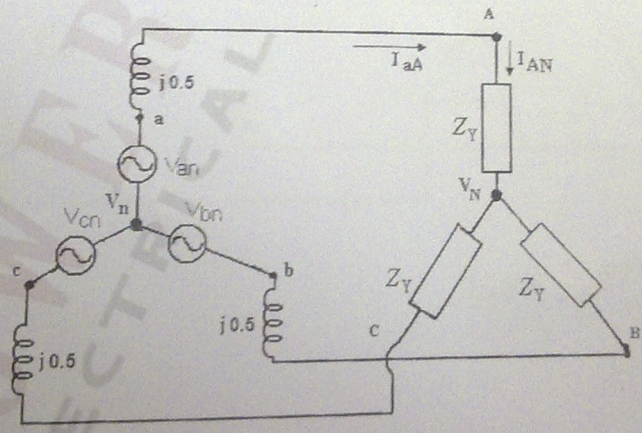


Figure: Q4

- The $V_{bn} \approx$:
- a) None of these.
 - b) $252.0 \angle -90^\circ A$.
 - c) $250.32 \angle -30^\circ A$.
 - d) $2675.0 \angle -132^\circ A$.
 - e) $243.73 \angle -186^\circ A$.

Handwritten notes on the right side of the page:

- V_{an}
- $V_{bn} = V_{cn}$
- $V_{AB} = \sqrt{3} V_{an}$
- $V_{bc} = \sqrt{3} V_{bn}$
- $V_{ca} = \sqrt{3} V_{cn}$

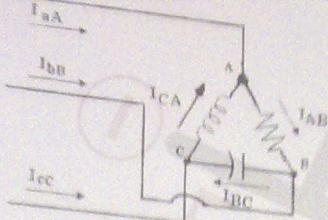


Figure: Q5

I_{aA}

The line current \bar{I}_{aA} is:

- a) None of these.
- b) $19.32 \angle -45^\circ A$.
- c) $10.0 \angle -30^\circ A$.
- d) $19.32 \angle 45^\circ A$.
- e) $10.0 \angle -45.0^\circ A$.

Question 6: A three-phase balanced voltage source feeds the balanced load shown in the Fig Q6. The $V_{AB} = 400 \angle 30^\circ V_{rms}$. The complex power of the load $S_{3\phi} = 9kVA \angle 30^\circ$.

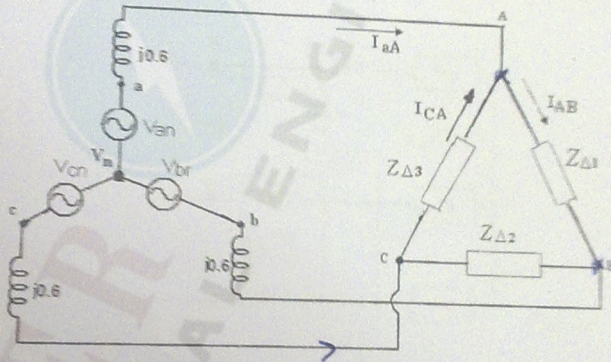


Figure: Q6

I_{cc}

$S = V$

$S = 3000 \text{ VA}$

The line current \bar{I}_{cc} is:

- a) $12.99 \angle 90^\circ A$.
- b) $7.5 \angle 90^\circ A$.
- c) $7.5\sqrt{3} \angle -90^\circ A$.
- d) $12.99 \angle -120^\circ A$.
- e) None of these.

$$I_{cc} = I_{CA} - I_{CB}$$

$$= \frac{V_{CA}}{Z} - \frac{V_{CB}}{Z}$$

$$= 0.133$$


$$S = P + jQ$$

$$P = \frac{S}{\cos \phi}$$

$$2500 \text{ W} = P$$

$$x = 0.133$$

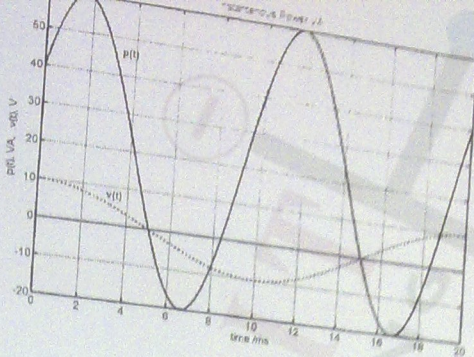Question 7: Fig. Q7, shows the instantaneous power $p(t)$ absorbed by the load and the voltage $v(t)$ applied to it. The load composed of two elements in series.




$2 \cos \theta = 0$
 $5 \cos \theta = 360^\circ \times 2$
 $\theta = \frac{360}{5} = 72$
 $P = 460 \text{ W}$ (Note: $\theta = 72^\circ$)

(4)

Figure: Q7

- The current $i(t)$ is:
- a) $15 \cos(100\pi t + 30^\circ)$.
 - b) None of these.
 - c) $12 \cos(100\pi t + 60^\circ)$.
 - d) $8 \cos(100\pi t - 60^\circ)$.
 - e) $10 \cos(100\pi t - 30^\circ)$.

$P(t) = i(t) v(t)$

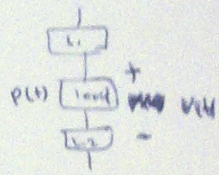

Question 8: The line voltage is $V_{AB} = 416 \text{ V}_{RMS}$ and positive sequence. The load impedance $Z_\phi = 5 \angle 45^\circ \Omega$.


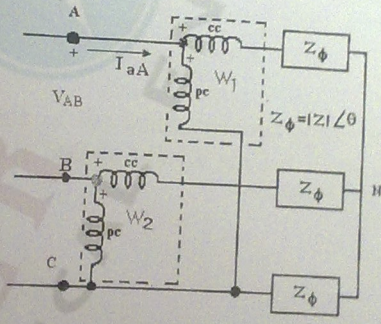


Figure: Q8

- The two watt-meters read as:
- a) $W_1 = 2781.6 \text{ W}$, and $W_2 = 11172.5 \text{ W}$.
 - b) $W_1 = 2981.6 \text{ W}$, and $W_2 = 16519.17 \text{ W}$.
 - c) $W_1 = 11127.5 \text{ W}$, and $W_2 = 2981.6 \text{ W}$.
 - d) None of these.
 - e) $W_1 = 2981.6 \text{ W}$, and $W_2 = 11127.5 \text{ W}$.

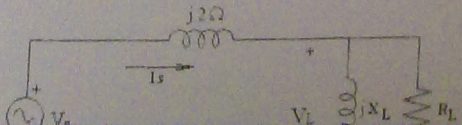Question 9: In Fig.Q9, the source delivers 7500 VA at $V_s = 250 \angle 30^\circ \text{ V}_{rms}$ with power factor of 0.866020 lagging.



7500 VA

$X_L =$

$S = V I^*$
 $P = \text{Re}(S)$

- Value of X_L is:
- 32.38Ω .
 - 18.70Ω .
 - None of these.
 - 11.0Ω .
 - 12.47Ω .

Question 10: Fig.Q10, shows the instantaneous power $p(t)$, where the voltage is given in the form $v(t) = 100 \cos(\omega t + 0^\circ) \text{ V}$

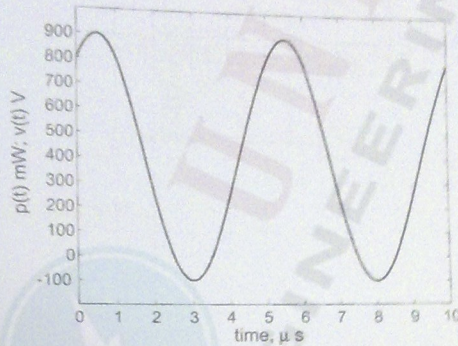


Figure: Q10

One of the numerical expression of the instantaneous power $p(t)$ is wrong:

- $400 - 500 \cos 143.13^\circ \cos 2\omega t + 500 \sin 143.13^\circ \sin 2\omega t$.
- None of these.
- $400 - 500 \cos(2\omega t + 143.13^\circ)$.
- $400 + 500 \cos(2\omega t - 36.87^\circ)$.
- $400 + 400 \cos 2\omega t + 300 \sin 2\omega t$.

Question 11: In fig.Q11, the reactive power delivered by the source to the network is:


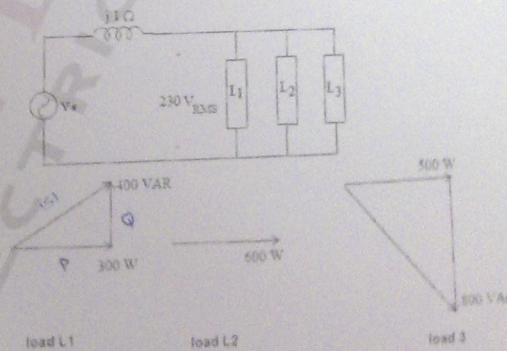


Figure: Q11

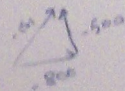- $j440 \text{ VAR}$.
- $j359.9 \text{ VAR}$.



$S = P + jQ$
 $S = VI^*$

- b) $j35.59 \text{ VAR}$.
- c) $-j359.9 \text{ VAR}$.

Question 12: The two watt-meters in Fig.Q12, read as: $W_1 = 16519.17 \text{ W}$, and $W_2 = 2119.170 \text{ W}$. The magnitude of the line voltage is 415 V_{RMS} . The phase sequence is positive.

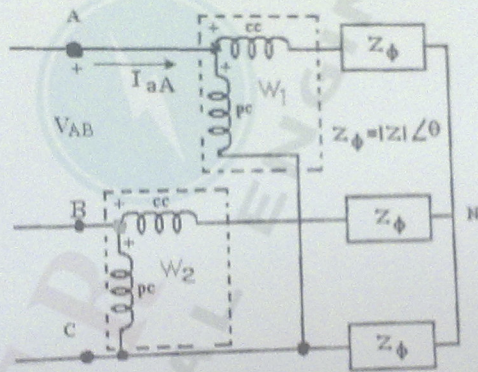


Figure: Q12

The power factor of the load PF is:

- a) None of these.
- b) 0.9823 Lag.
- c) 0.866 Lag.
- d) 0.8923 Lag.
- e) 0.5986 Lag.

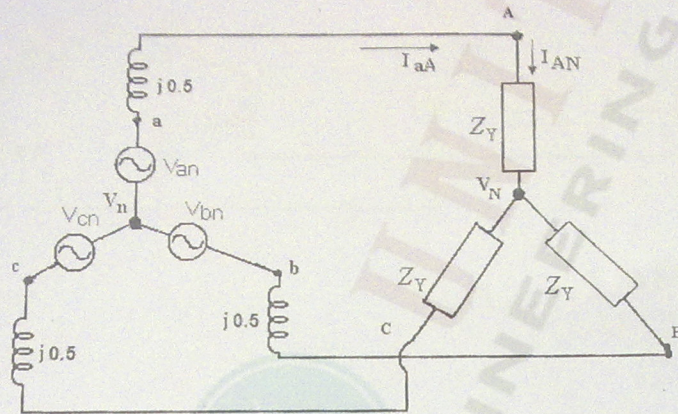


Figure: Q4

Van

$$V_{bn} = V_{cn} = V_{an}$$

$$V_{AB} = \sqrt{3} \frac{V_{an}}{\sin 30^\circ}$$

$$V_{an} = 252 \angle -120^\circ$$

$$V_{bn} = 252 \angle -120^\circ$$

$$V_{AB} = \sqrt{3} V_{an} \angle 30^\circ$$

$$X = 70 = 120$$

The $V_{bn} \simeq$:

- a) None of these.
- b) $252.0 \angle -90^\circ A$.
- c) $250.32 \angle -30^\circ A$.
- d) $2675.0 \angle -132^\circ A$.
- e) $243.73 \angle -186^\circ A$.

Question 5: A three-phase balanced voltage source feeds the load shown in the Fig.Q5. The $V_{AB} = 400 \angle 30^\circ V_{rms}$. The $|Z_{AB}| = |Z_{BC}| = |Z_{CA}|$ and the three phase load absorbs 4000W.

I_{aA}


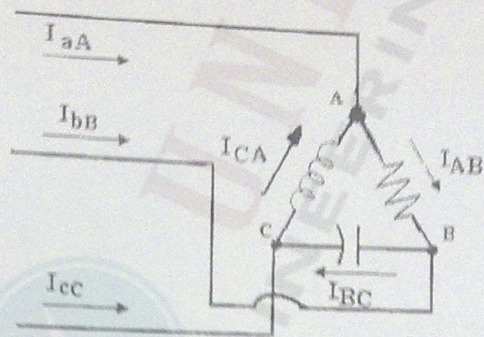



Figure: Q5

The line current \vec{I}_{aA} is:

- a) None of these.
- b) $19.32 \angle -45^\circ A$.
- c) $10.0 \angle -30^\circ A$.
- d) $19.32 \angle 45^\circ A$.
- e) $10.0 \angle -45.0^\circ A$.

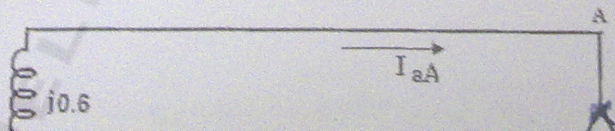Question 6: A three-phase balanced voltage source feeds the balanced load shown in the Fig. $V_{AB} = 400 \angle 30^\circ V_{rms}$. The complex power of the load $S_{3\phi} = 9kVA \angle 30^\circ$.



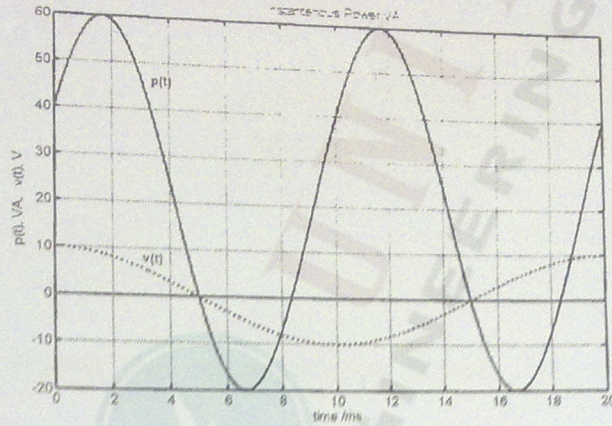


$2 \cos = \theta$
 $5 \cos \theta = 360^\circ + 2$
 $\theta = \frac{360}{5} = 72$
 $P = 460 \cos(100\pi t - 72)$

(4)

Figure: Q7

- The current $i(t)$ is:
- a) $15 \cos(100\pi t + 30^\circ)$.
 - b) None of these.
 - c) $12 \cos(100\pi t + 60^\circ)$.
 - d) $8 \cos(100\pi t - 60^\circ)$.
 - e) $10 \cos(100\pi t - 30^\circ)$.

$P(t) = i(t) v(t)$

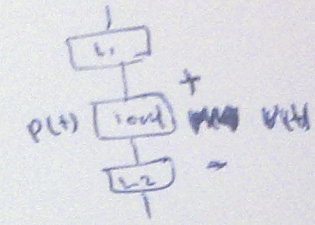

Question 8: The line voltage is $AB = 416 V_{RMS}$ and positive sequence. The load impedance $Z_\phi = 5 \angle 45^\circ$

