

- 1 For the circuit shown in Fig. (2) Answer the following questions:

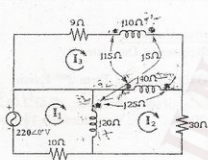


Fig. (2)

1. The 1st mesh equation: $30 \cdot 30$
- $j20(I_2 - I_1) - j25(I_2 - I_3) - j5I_3 + 10I_1 = 220\angle 0^\circ$
 - $j20(I_1 - I_2) - j25(I_2 + I_3) - j5I_3 + 10I_1 = 220\angle 0^\circ$
 - $(10 + j20)I_1 + j45I_2 + j20I_3 = 220\angle 0^\circ$
 - $(10 + j20)I_1 - j45I_2 + j20I_3 = 220\angle 0^\circ$
2. The 2nd mesh equation:
- $30I_2 + j20(I_1 - I_2) + j25(I_2 - I_3) + j5I_3 + j40(I_2 - I_3) - j25(I_1 - I_2) + j15I_3 = 0$
 - $30I_2 + j20(I_2 - I_1) + j25(I_2 - I_3) + j5I_3 + j40(I_2 - I_3) - j25(I_1 - I_2) + j15I_3 = 0$
 - $j45I_1 + (30 + j110)I_2 - j45I_3 = 0$
 - $j45I_1 + (30 + j110)I_2 - j45I_3 = 0$
3. Assume that the currents $I_1 = 16.4447\angle -5.1^\circ$ A, $I_2 = 4.1813\angle 1.6807^\circ$ A and $I_3 = 6.4526\angle -165.42^\circ$ A, the voltage across $[V_{j40\Omega}]$ is:
- 4825 V
 - 248.5 V
 - 2486 V
 - 2856 V

$$-220 + j20(I_1 - I_2) + 10I_1 + j25(I_2 - I_3) + j5I_3 = 0$$

$$j20I_1 - j20I_2 + 10I_1 + j25I_2 - j25I_3 + j5I_3 = 220$$

$$(10 + j20)I_1 + j5I_2 - j20I_3 = 220$$

2 For the circuit shown in Fig.(3) all resistances and reactances are given in Ω . Answer the following questions:

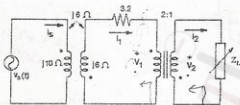


Fig.4

$$3.2 + \frac{36}{}$$

4. The load impedance Z_L is adjusted to absorb the average maximum power, so \bar{Z}_L is equal to:
- a) $1\angle -36.87^\circ\Omega$ b) $4\angle -36.87^\circ\Omega$ c) $2\angle 36.87^\circ\Omega$ d) $0.8 + j0.6\Omega$
5. The impedance looking by source terminals, when the load impedance Z_L is adjusted to absorb the average maximum power is:
- a) $8.52\angle -60^\circ\Omega$ b) $7.82\angle 60^\circ\Omega$ c) $5.82\angle -60.4^\circ\Omega$ d) $8.72\angle 60^\circ\Omega$

3 For Fig.(4) $V_s = 102\angle -36.87^\circ\text{V}_{rms}$.

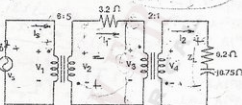


Fig.4

6. The current source I_1 is
- a) 14.167A b) $-17\angle 36.87^\circ\text{A}$ c) $-17\angle 0^\circ\text{A}$ d) -14.67A
7. The load current $|I_2|$ is
- a) 34 A b) 13.33 A c) 17 A d) -3.4A
8. The voltage $|V_3|$ is \approx
- a) $122\angle -36.87^\circ\text{V}$ b) $-26\angle 36.87^\circ\text{V}$ c) $53\angle 105^\circ\text{V}$ d) no answer
9. The reactive power delivered by the source Q_s is \approx
- a) 0 VAR b) 870 VAR c) -433.5VAR d) -867Var ;

17. If the pole zeros plot of $Z_{in}(\sigma)$ is shown in Fig.5 , then transfer function of $Z_{in}(\sigma)$ is.


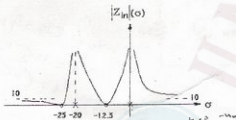


Fig. 5


- a) $10 \frac{\sigma^2 + 37.5\sigma + 312.5}{\sigma^2 + 20\sigma}$ b) $100 \frac{\sigma^2 + 37.5\sigma + 312.5}{\sigma^2 + 20\sigma + 200}$ c) $10 \frac{\sigma^2 - 37.5\sigma + 312.5}{\sigma^2 + 20\sigma + 200}$
 d) none of them

18. The poles and zeros configuration of $|Z_{in}(\sigma)|$ shown in Fig.6(a) represents the input impedance of the circuit shown in Fig. 6(b). The poles p_1, p_2 are:

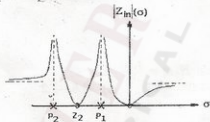

(a)

Fig. 6

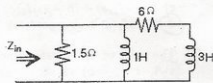

(b)

- a) 0, -2Np/s b) -1, -3Np/s c) -0.5, -1.5 Np/s d) 0.5, 1.5 N/s

19. The zeros of $|Z_{in}(j\omega)|$ shown in Fig.7 are:

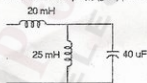


Fig. (7)

- a) -750, 750 rad/s b) -500, 500 rad/s c) -1000, 1000 rad/s d) 1500, -1500 rd/s

20. The poles of $|Z_{in}(j\omega)|$ shown in Fig.7 are:

- a) -750, 750 b) -1500, 0, 1500 rad/s c) -500, 500 rad/s d) 1000, -1000 rad/s

$$\begin{aligned}
 &6 + 3s + 11s \\
 &\frac{6s + 3s^2}{6 + 4s} \cdot \frac{1.5}{s + 4} \\
 &9 + 4.5s^2 \\
 &\frac{6s + 3s^2 + 1.5}{(6 + 4s) \cdot 6}
 \end{aligned}$$

$$\begin{aligned}
 &6s + 3 \\
 &3s^2 + 6s + 1.5 = 0 \\
 &s^2 + 2s + 0.5 = 0
 \end{aligned}$$

4 For the circuit shown in Fig.1, if the voltage source $v_s(t) = 24 \cos 377t$ V. Answer the following questions:

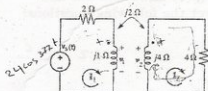


Fig.1

$$j1 I_1 - j2 I_2 = 0$$

$$-24 + 2I_1 + j1 I_1 - j2 I_2 = 0$$

$$(2 + j1) I_1 - j2 I_2 = 24$$

10. One of the following equations that describe the 1st loop is wrong, that is:

- a) $V_1 = j1 I_1 - j2 I_2$ ✓
- b) $24 \angle 0^\circ = (2 + j1) I_1 - j2 I_2$ ✓
- c) $24 \angle 0^\circ = 2 I_1 + V_1$
- d) $24 \angle 0^\circ = (2 + j1) I_1 + j2 I_2$

$$j4 I_2 - j2 I_1$$

11. One of the following equations that describe the 2nd loop is wrong, that is:

- a) $V_2 = -j4 I_2 + 4 I_2 - j2 I_1$
- b) $0 = (-4 - j4) I_2 + j2 I_1 - V_2$
- c) $0 = 4 I_2 - V_2$
- d) $V_2 = j2(I_1 - 2 I_2)$

$$-24 \angle 0 + 2 I_1 + j1 I_1 - j2 I_2 = 0$$

$$(2 + j1) I_1 - j2 I_2 = 24 \quad \text{--- (1)}$$

12. The current $i_1(t) =$

- a) $i_1(t) = 2.17 \sin(377t - 21.2^\circ) \text{ A}$ 0.71
- b) $i_1(t) = 4.91 \cos(377t + 22.5^\circ) \text{ A}$ 4.97
- c) $i_1(t) = 9.41 \cos(377t - 11.31^\circ) \text{ A}$ 9.28
- d) $i_1(t) = 6.47 \cos(377t + 51.2^\circ) \text{ A}$ 3.28

$$-j4 I_2 + 4 I_2 - j2 I_1 = 0$$

$$(4 - j4) I_2 - j2 I_1 = 0 \quad \text{--- (2)}$$

13. The current $i_2(t) =$

- a) $i_2(t) = 3.33 \cos(377t + 33.69^\circ) \text{ A}$ 2.7
- b) $i_2(t) = 2.19 \cos(377t - 30.13^\circ) \text{ A}$ 1.43
- c) $i_2(t) = 9.13 \cos(377t - 13.69^\circ) \text{ A}$ 8.4
- d) $i_2(t) = 1.31 \cos(377t + 63.19^\circ) \text{ A}$ 0.45

$$j2 I_1 = (4 - j4) I_2$$

$$I_1 = \frac{(4 - j4)}{j2} I_2$$

$$I_1 = (-j2 - 2) I_2$$

$$(2 + j1)(-j2 - 2) I_2 - j2 I_2 = 0$$

$$(-j4 - 4 + 2 - j2) I_2 - j2 I_2 = 24$$

$$(-2 - j6) I_2 - j2 I_2 = 24$$

$$(-2 - j8) I_2 = 24$$

$$I_2 = \frac{24}{-2 - j8}$$

14. The current $i_1(t = 5ms) =$

- a) 1.2A
- b) 2.1A
- c) -1.1A
- d) -2.2A

$$\frac{24}{-2 - j8} = \frac{24(-2 + j8)}{(-2)^2 + 8^2}$$

$$= \frac{-48 + j192}{68}$$

$$= -0.706 + j2.824$$

$$8.23 \angle 76^\circ$$

15. The current $i_2(t = 5ms) =$

- a) -3.2A
- b) 2.61A
- c) 3.2A
- d) 32A

16. The energy stored in the perfectly coupled circuit at $w(t = 5ms) =$

- a) 100 mj
- b) 10 mj
- c) 22.5 mj
- d) -10 mj

$$(2 + j1) I_1 - j2 I_2 = 24$$

$$I_1 = \frac{24 + j2 I_2}{2 + j1}$$

$$I_1 = \frac{48 - j24 + j12 + 6}{5}$$

$$= \frac{54 - j12}{5} = 10.8 - j2.4$$

$$= 11.06 \angle -12.53^\circ$$

$$I_2 = -2.19 \angle 30.13^\circ$$

$$I_2 = 1.9 + j1.1$$

$$(2 + j1) I_1 - j2(1.9 + j1.1) = 24$$

$$23.1 + j11.1 - j2(1.9) - j2(j1.1) = 24$$

$$23.1 + j11.1 - j3.8 - j2.2 = 24$$

~~$$I_2 = 2.91 \angle 76^\circ$$~~
~~$$26.245$$~~

5

For the circuit shown in Fig. 8., the forced source is $V_s(t) = 10e^{-2t}V$ and $i_1(0) = i_2(0) = 10A$. Answer the following questions:

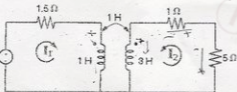


Fig. (8)

$$A + B = 10 \quad \text{--- (1)}$$

$$-V_s + 1.5I_1 + sI_1 + 3sI_2 = 0$$

$$V_s = 1.5I_1 + 3sI_2$$

$$V_s = (1.5 + s)I_1 + 3sI_2$$

21. The 1st mesh equation in s-domain may be expressed as

- a) $V_s = (1.5 + s)I_1(s) - sI_2(s)$
 b) $V_s = (1.5 + s)I_1(s) + sI_2(s)$
 c) $V_s = (1.5 + s)I_1(s) + 3sI_2(s)$
 d) none of them

22. The 2nd mesh equation in s-domain may expressed as

- a) $0 = -sI_1(s) + (6 + 3s)I_2(s)$
 b) $0 = sI_1(s) - (6 + 3s)I_2(s)$
 c) $0 = sI_1(s) + (6 - 3s)I_2(s)$
 d) $0 = sI_1(s) + (6 + 3s)I_2(s)$

$$3sI_2 + 5I_2 + I_2 + 3sI_2 = 0$$

$$3sI_2 + 6I_2 + 5I_1 = 0$$

$$(6 + 3s)I_2 + 5I_1 = 0$$

23. The poles of the transfer function $H(s) = \frac{I_2(s)}{V_s}$ are:

- a) 4, -1 b) -2, -5 c) -1.08, -4.17 d) -0.5, -1.2

24. The expression $\frac{di_2(t)}{dt}$ at $t = 0^+$ is:

- a) 22.5 b) 32 c) -12 d) $-\frac{33}{2}$

25. Assume that $i_2(t) = Ae^{-5t} + Be^{-6t} + 80e^{-2t}$ and $\frac{di_2(0)}{dt} = 32$, then constants A and B are:

- a) 0, 40 b) -228, 158 c) 96, -128 d) -158, 0

$$i_2(0) = A + B + 80 = 10$$

$$\frac{di_2(0)}{dt} = -5Ae^{-5t} + 6B e^{-6t} - 2(80)e^{-2t} = 32$$

$$A + B = -70 \quad \text{--- (1)}$$

$$-5A - 6B = 192 \quad \text{--- (2)}$$