



Electrical Engineering Department
Faculty of Engineering & Technology
University of Jordan

Electrical Circuits (2) (EE212)
Second Exam
2nd Term, 2012-2013
April 22nd, 2013. ⌚ 16:00 – 17:30

الاسم: فواز العتيق
Reg. No.: 0119203... Sec.: 1:00-2:00 / 7 غاوي

Instructor:	Dr. Othman Al Smadi	Dr. Ghazi Al Sukkar <input checked="" type="checkbox"/>	Eng. Hasan Farahneh <input type="checkbox"/>
-------------	---------------------	---	--

Lecture Time:	Sun, Tues, Thur <input checked="" type="checkbox"/> 1:00 - 2:00	Mon, Wed <input type="checkbox"/>
---------------	--	--

Notes:


- Write your name and section on all pages
- Do not write on the back of this page.

Otherwise you will lose 5 marks out of 30.

Problem No.	Marks Awarded
Q1 (10)	1.5
Q2 (10)	7
Q3 (10)	8
TOTAL (30)	16.5

Q(1): In Fig.1 below, the three phase source is balanced, P_1 reads upscale 4411 Watt, while P_2 reads downscale 1000 Watt, and $V_{AB} = 440 \angle 0^\circ$ V rms. Determine:

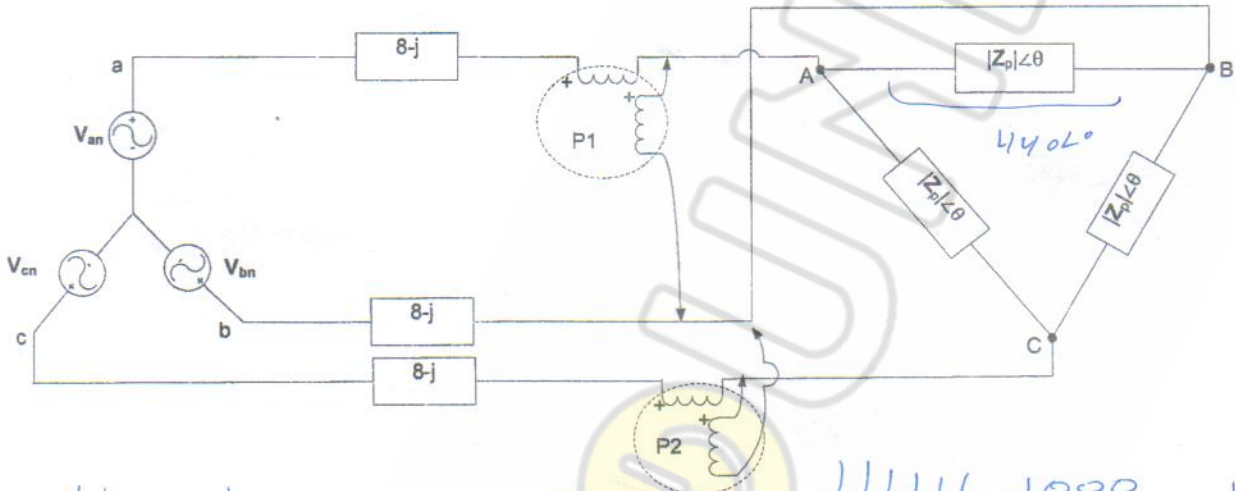- 1) (2 marks) The value of P.F. for the load (is it lagging or leading?)
- 2) (4 marks) I_{aA} and Z_p
- 3) (2 marks) V_{an}
- 4) (2 marks) The P.F. at the Source (is it lagging or leading?) and the total complex power of the source.



$$|V_{AB}| |I_{AB}| \cos(\text{ang } V_{AB} - \text{ang } I_{AB}) = \frac{4411 - 1000}{\sqrt{3}} = 1137$$

$$|440| |I_{AB}| \text{ P.F.} = 1137$$

$$|V_{AB}| |I_{aA}| = 4411$$

$$\cos(\text{ang } V_{AB} - \text{ang } I_{aA})$$

$$|V_{AB}| |I_{AB}| \sqrt{3} \cos(+90^\circ + \theta) = 4411$$

$$440 I_{AB} \sqrt{3} \cos(90^\circ + \theta) = 4411$$

$$440 I_{AB} \cos(90^\circ + \theta) = 1137$$

$$\sqrt{3} \frac{\cos(90^\circ + \theta)}{\cos(+\theta)} = 3.86$$

$$\frac{\cos(90^\circ + \theta)}{\cos(+\theta)} = 2.23$$

$$\frac{\sin \theta}{\cos \theta} = 2.23$$

$$\theta = 65.847^\circ$$

$$\theta = -65.847^\circ$$

Q(2): (a) (6 marks) For the circuit shown in Fig.2 find: V_2 and I_x .

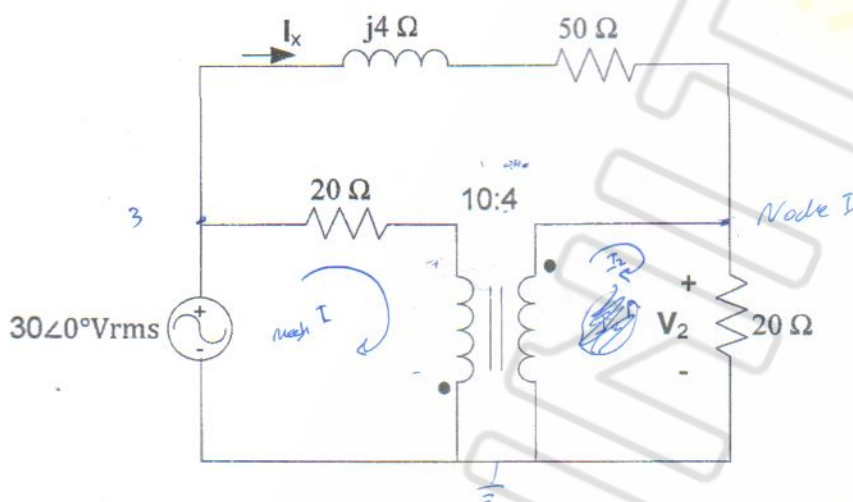


Fig. 2

$V = \sqrt{2} V_{rms}$
 $V_{rms} = \frac{V}{\sqrt{2}}$
 $V = V_{rms} \sqrt{2}$

$a = -0.4$

$\frac{V_2}{V_1} = -0.4$
 $V_1 = \frac{V_2}{-0.4}$
 $\frac{I_1}{I_2} = -0.4$
 $I_1 = -0.4 I_2$

@ Node I

@ mesh I

$-30 \angle 0 + 20 I_1 - \frac{V_2}{0.4} = 0$

$\frac{30 - V_2}{j4 + 50} = I_x$

$30 \angle 0 = 20 I_1 - \frac{V_2}{0.4}$

$30 \angle 0 = 20 I_1 - \frac{V_2}{0.4}$ (1)

@ Node I

$\frac{V_2}{20} = I_2 + I_x$

$\frac{V_2}{20} = -\frac{I_1}{0.4} + \frac{30 - V_2}{j4 + 50}$

$\frac{V_2}{20} - \frac{30 + V_2}{j4 + 50} = -\frac{I_1}{0.4}$

$(j4 + 50)V_2 - 60 - 20V_2 = -\frac{I_1}{0.4} \cdot 20(j4 + 50)$

$V_2 \left(\frac{j4 + 50}{20} - 1 \right) - 3 = -\frac{I_1}{0.4}$ (2)

$V_2 = 0.93 \angle -94.7$ V

$I_1 = 2.3 \angle -1.8$ A
 $I_2 = 5.75 \angle 178.2$

$I_2 = -\frac{I_1}{0.4}$

$I_x = \frac{V_2}{20} - I_2$

$I_x = 5.265 \angle -1.8$ A

(b) (4 marks) For the circuit shown in Fig.3 given $v_s(t) = 20 \cos 10t$ V, find $v(t)$.

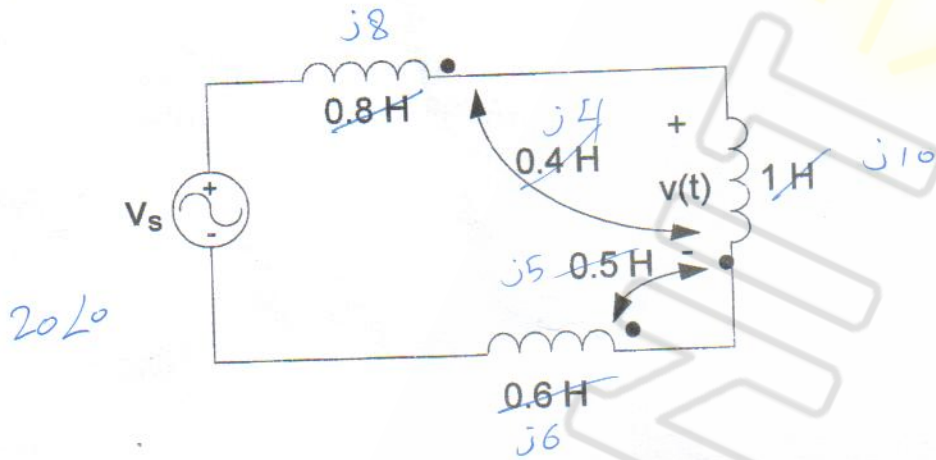


Fig. 3

~~I_1~~

~~$V_s + j8I_1 + j10I_1 + j10I_1 - j6I_1$~~

~~$-V_s + j8I_1 + j4I_1 + j10I_1 + j4I_1 - j5I_1 + j6I_1 - j5I_1 = 0$~~

~~$-20\angle 0^\circ + (j8 + j4 + j10 + j4 - j5 - j5 + j6) I_1 = 0$~~

$I_1 = \frac{20\angle 0^\circ}{j22} = 0.909 \angle -90^\circ \text{ A}$

~~V~~ $= j10I_1 + j4I_1 - j5I_1$
 $= (j10 + j4 - j5) 0.909 \angle -90^\circ$
 $= 8.1818 \angle 0^\circ$

$v(t) = 8.1818 \cos 10t \text{ Volt}$

4

Q(3): In the circuit shown in Fig.4, given $v_s(t) = 10e^{-2t} \cos(10t + 30^\circ) \bar{V}$, determine:

- 1- (6 marks) $i_1(t)$
- 2- (2 marks) The natural response for $I_2(s)$ in the s-domain.
- 3- (2 marks) Constellate all poles/zeros for I_2 .

$s = -2 + j10$

$10 \angle 30^\circ$

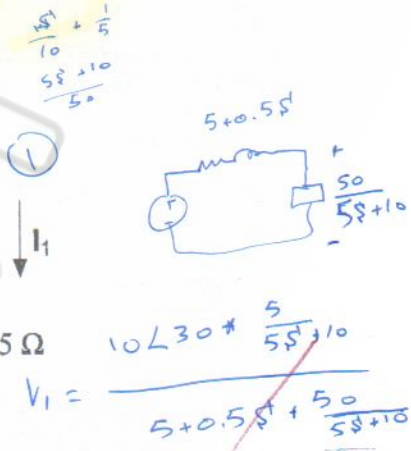
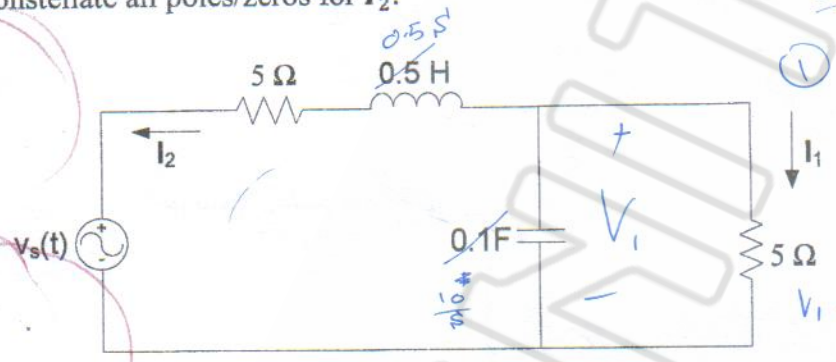


Fig. 4

$10 \angle 30^\circ = (5 + 0.5s + \frac{10}{s}) I_2 + \frac{10 I_1}{s}$

$V_1 = 1.768 \angle -105^\circ$

$I_1 = \frac{V_1}{5} = 0.35 \angle -105^\circ$

$i_1(t) = 0.35 e^{-2t} \cos(10t - 105^\circ) \text{ A}$

$Z_{in} = 5 + 0.5s + \frac{50}{5s+10}$

$I_2 = \frac{V_s}{Z_{in}} \Rightarrow H(s) = \frac{1}{Z_{in}} = \frac{1}{5 + 0.5s + \frac{50}{5s+10}}$

$H(s) = \frac{5s+10}{(5s+10)(5+0.5s) + 50}$

$I_2 = 10 \angle 30^\circ \frac{5s+10}{25s + 0.5 \times 5s^2 + 50 + 5s + 50}$


Poles: $s_1 = -6 + 2j$
 $s_2 = -6 - 2j$

$I_2 = A e^{(-6+2j)t} + B e^{(-6-2j)t}$

(3)

Zeros: $s = -2$

Poles: $s_1 = -6 + j2$
 $s_2 = -6 - j2$

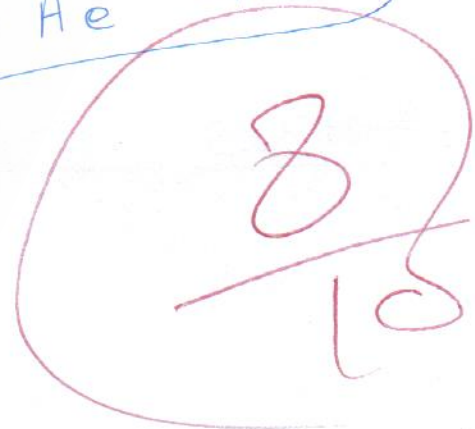

Good Luck