

Circuits II □ Notebook

Dr. Iyad Abulfailat


By . Isra' Jamil

بِأَفْكَارِنَا نَبْدَعُ


15-9-2014
- Monday

No. Lecture 1

DC cct analysis (Review)

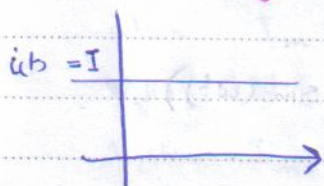

DC - current

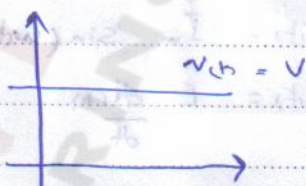

DC - voltage

$$p(t) \equiv \text{instantaneous power} = V \cdot I = v(t) \cdot i(t)$$



AC cct analysis

$v(t)$ & $i(t)$ are time varying function


$$v(t) = V_m \sin(\omega t)$$

$$i(t) = I_m \sin(\omega t + \theta)$$

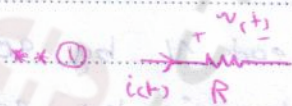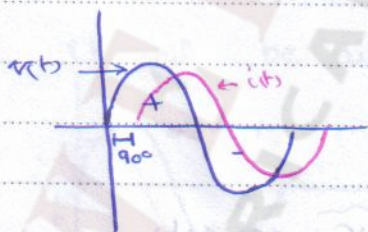
where $\omega \equiv$ Angular freq. (rad/s) = $2\pi f$


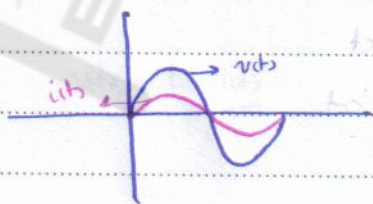
$$i(t) = \frac{v(t)}{R} = \frac{V_m}{R} \sin(\omega t) = I_m \sin(\omega t)$$




v & i \rightarrow in phase

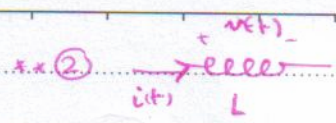

$$i(t) = I_m \sin(\omega t)$$


$$V(t) = L \frac{di(t)}{dt} = L \frac{d}{dt} (I_m \sin(\omega t))$$

$$= I_m \omega L \cos \omega t$$

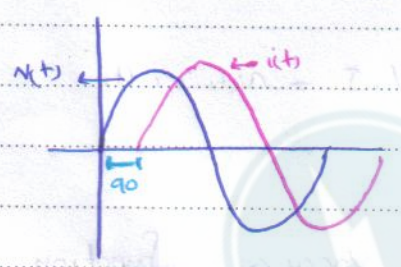

\Rightarrow i lags V by 90°
OR V leads i

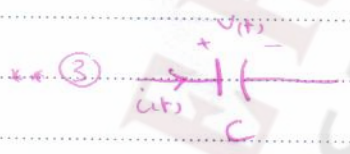- @ low freq $\xrightarrow{\text{acts as}}$ short ckt
- @ high freq $\xrightarrow{\text{acts as}}$ open ckt




$$V(t) = V_m \sin(\omega t)$$

$$i(t) = C \frac{dV_c}{dt} = V_m \omega C \cos(\omega t)$$



\Rightarrow i leads V by 90°
OR V lags i by 90°

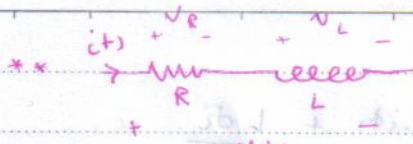- @ low freq $\xrightarrow{\text{acts as}}$ open ckt
- @ high freq $\xrightarrow{\text{acts as}}$ short ckt




$$i(t) = I_m \sin \omega t$$

$$V_R(t) = V_m \sin(\omega t)$$

$$V_L(t) = I_m \omega L \cos(\omega t)$$

$$V_{\text{tot}} = V_{Rm} \sin(\omega t) + V_{Lm} \cos(\omega t)$$


$$= V \sin(\omega t + \theta)$$

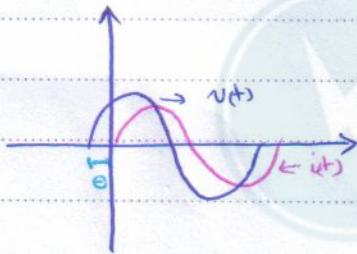

\Rightarrow i lags v by θ


xx if we have R & C

it will be like:

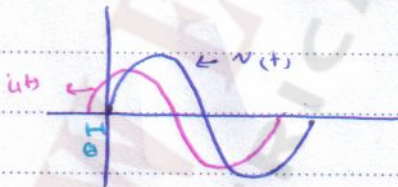


\Rightarrow i leads v by θ

*** Remember

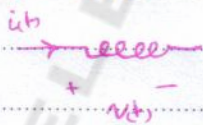

$$V_L = L \frac{di(t)}{dt}$$

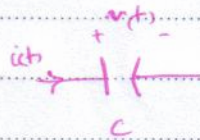

$$i(t) = C \frac{dV_C}{dt}$$




$$v(t) = R \cdot i(t) + L \frac{di}{dt}$$


$$V_m \sin(\omega t) = R \cdot i(t) + L \frac{di}{dt} \leftarrow \text{diff. equ.}$$

so \rightarrow convert from time domain \rightarrow phasor domain (freq.)

* Phasor representation:

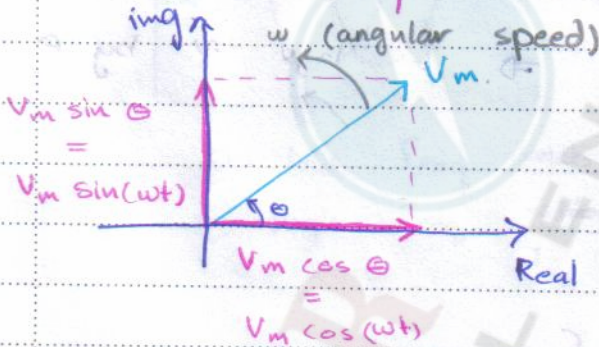

* example 10.15

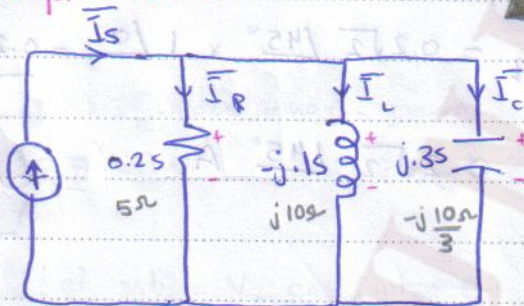

Capacitive

$\frac{10}{3} < 10$ #

Parallel → الأصغر هو الذي يتحكم
series → الأكبر قيمة هو الذي يتحكم

$V = 1 \angle 0^\circ$ V

↓ same as

$v(t) = 1 \cos(\omega t + 0)$ V

sol. by KCL $I_s = I_R + I_C$

$Z_R = R$ (ohm)

$Y_R = \frac{1}{R} = G$ (S)

$Z_L = j\omega L = jX_L$ (ohm)

$Y_L = \frac{1}{Z_L} = \frac{1}{jX_L} = -jB_L$ (S)

من الأشاران والوصية بقدر أحسن
إنها inductive Reactance

$Z_C = \frac{1}{j\omega C} = -jX_C$ (ohm)


$Y_C = \frac{1}{Z_C} = +jB_C$ (S)

capacitive Reactance

$\frac{1}{Z_{eq}} = \frac{1}{Z_R} + \frac{1}{Z_L} + \frac{1}{Z_C}$

$Y_{eq} = Y_R + Y_L + Y_C$

$= 0.2 - j0.1 + j0.3 = 0.2 + j0.2$ S

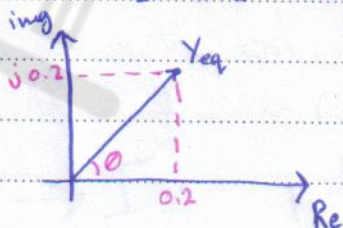


$Y_{eq} = 0.2\sqrt{2} \angle 45^\circ$ S

$$\leftarrow Z_{eq} = \frac{1}{Y_{eq}} = \frac{1}{0.2\sqrt{2} \angle 45^\circ} = \frac{5\sqrt{2}}{2} \angle -45^\circ \Omega$$

$$\bar{I}_s = \frac{\bar{V}}{Z_{eq}} = \bar{V} Y_{eq} = 0.2\sqrt{2} \angle 45^\circ \times 1 \angle 0^\circ = 0.2\sqrt{2} \angle 45^\circ \text{ A}$$
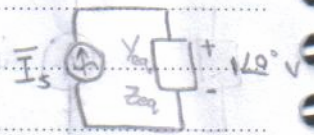
$$= \frac{1 \angle 0^\circ}{2.5\sqrt{2} \angle -45^\circ} = 0.2\sqrt{2} \angle 45^\circ \text{ A}$$




note that if $0^\circ < \theta < 90^\circ \rightarrow$ capacitive
& if $\theta = 90^\circ \rightarrow$ pure capacitive.) According to I_s

$$\bar{I}_R = \frac{\bar{V}}{Z_R} = \frac{\bar{V}}{R} = \frac{1 \angle 0^\circ}{5 \angle 0^\circ} = 0.2 \angle 0^\circ \text{ A} \quad (\text{in phase})$$

$$\bar{I}_L = \frac{\bar{V}}{Z_L} = \frac{1 \angle 0^\circ}{10 \angle 90^\circ} = 0.1 \angle -90^\circ \text{ A} = -j0.1 \text{ A}$$

$$\bar{I}_C = \frac{\bar{V}}{Z_C} = \frac{1 \angle 0^\circ}{\frac{10}{3} \angle -90^\circ} = 0.3 \angle 90^\circ \text{ A} = j0.3 \text{ A}$$

Review \rightarrow Lead & lag

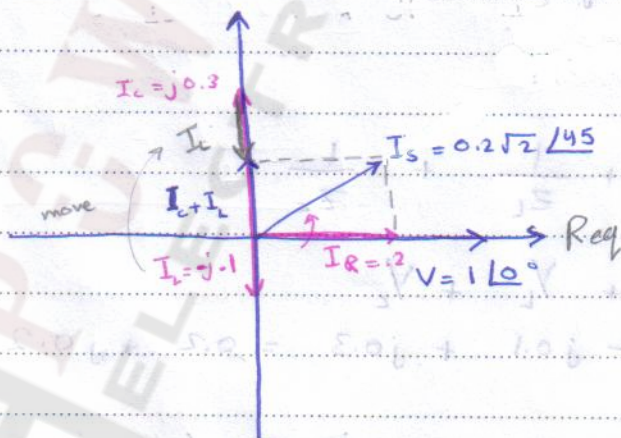


\leftarrow using sliding vectors
in order to draw

\bar{I}_s

** CH.11 "AC circuit Analysis" / Power.

$p(t) \equiv$ instantaneous power

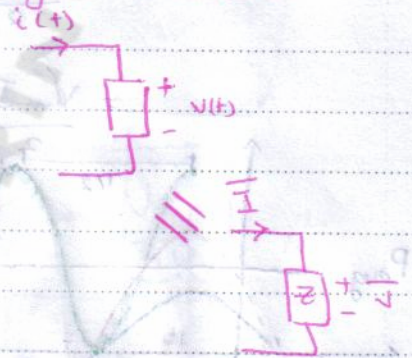AC/DC $\leftarrow p(t) = v(t) \times i(t)$



Let $v(t) = V_m \cos(\omega t + \theta)$ V

Let $i(t) = I_m \cos(\omega t + \phi)$ A

so $p(t) = v(t) \cdot i(t)$


$$= V_m \cos(\omega t + \theta) \cdot I_m \cos(\omega t + \phi)$$

$$= \frac{V_m I_m}{2} [\cos(\theta - \phi) + \cos(2\omega t + \theta + \phi)]$$

$$= \underbrace{\frac{V_m I_m}{2} \cos(\theta - \phi)}_{\text{DC quantity, shift up or down (constant)}} + \underbrace{\frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi)}_{\text{Peak value}}$$

note that 1 cycle voltage $\xrightarrow[\text{me}]{\text{gives}}$ 2 cycles of power

**ex. Let $Z = R$

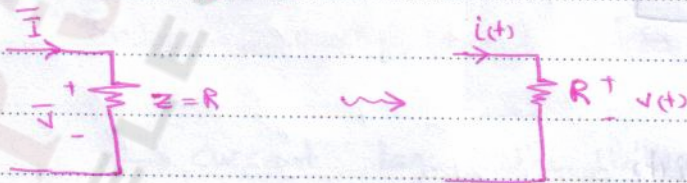


Pure Resistive

$v(t) = V_m \cos(\omega t + \theta)$

$i(t) = I_m \cos(\omega t + \theta)$] because they are in phase

\rightarrow In phase \leftarrow

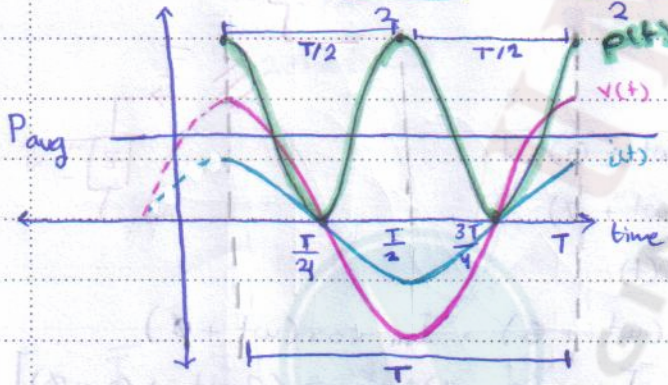
$$\begin{aligned}
 p(t) &= v(t) \cdot i(t) \\
 &= \frac{V_m I_m}{2} [\cos(\theta) + \cos(2\omega t + 2\theta)] \\
 &= \frac{V_m I_m}{2} + \frac{V_m I_m}{2} \cos(2\omega t + 2\theta)
 \end{aligned}$$



peak to peak (جهد)
power (طاقة)

note: resistor → passive element (consume power)

$P \equiv$ average power

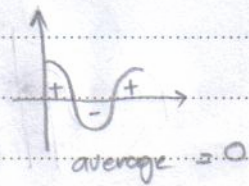

$$\begin{aligned}
 P &= \frac{1}{T} \int_0^T v(t) \cdot i(t) dt \\
 &= \frac{1}{T} \int_0^T \frac{V_m I_m}{2} dt + \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \cos(2\omega t + 2\theta) dt
 \end{aligned}$$

$$\Rightarrow \boxed{P = \frac{I_m V_m}{2}}$$

if they are constant ?!

By ohm's law

$$v(t) = R \cdot i(t)$$

$$\Rightarrow i(t) = \frac{v(t)}{R}$$

→

$$\leftarrow P = \frac{V_m I_m}{2} \Rightarrow P = \frac{V_m^2}{2R}$$


OR

$$P = \frac{I_m^2 R}{2}$$

$$\boxed{\Rightarrow P = \frac{I_m^2 R}{2} = \frac{I_m V_m}{2} = \frac{V_m^2}{2R}} \quad \#$$

also P (average power) we called it:

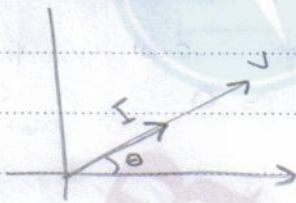- Real power / active power / usefull power



in phase \rightarrow consuming power

xxx Let $Z = Z_L = jX_L$



$$v(t) = V_m \cos(\omega t + \theta)$$


$$i(t) = I_m \cos(\omega t + \phi) = I_m \cos(\omega t + \theta + 90^\circ)$$

\rightarrow current lags the voltage \leftarrow

$$P(t) = \frac{V_m I_m}{2} [\cos(\theta - \theta - 90^\circ) + \cos(2\omega t + \theta + \phi)] \quad \text{ms}$$

$$P(t) = \frac{V_m I_m}{2} [\cos(90^\circ) + \cos(2\omega t + \theta + \phi)]$$
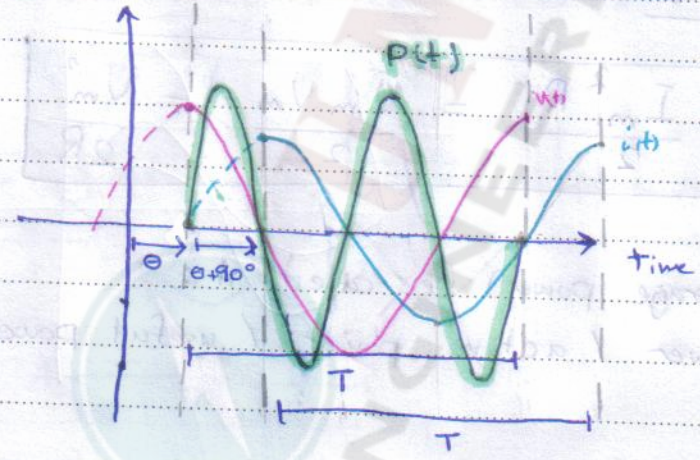
$$P(t) = \frac{V_m I_m}{2} \cos(2\omega t + \beta)$$




1 cycle of $v(t)$
OR
1 cycle of $i(t)$
= 2 cycles of $p(t)$

$$P_{avg} = 0 \Rightarrow \frac{1}{T} \int v(t) \cdot i(t) dt = 0$$

$$P_{Peak} = \frac{V_m I_m}{2} \sin 90^\circ \rightarrow \text{this is the phase shift}$$

We called it: Reactive power ($P_{avg} = 0$)

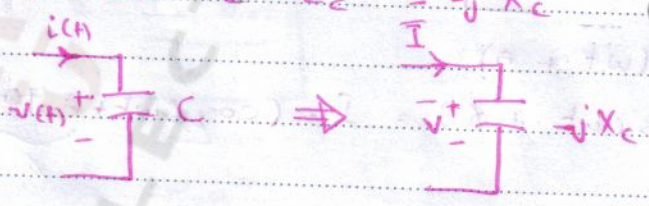ex. Let $z = z_c = -jX_c$ (inductor $1/\omega C$)




$\rightarrow I$ leads $V \leftarrow$

$$p(t) = V_m I_m \cos(\omega t) \cdot \cos(\omega t + 90)$$



$$P(t) = \frac{V_m I_m}{2} [\cos 90^\circ + \cos (2\omega t + 180^\circ)]$$
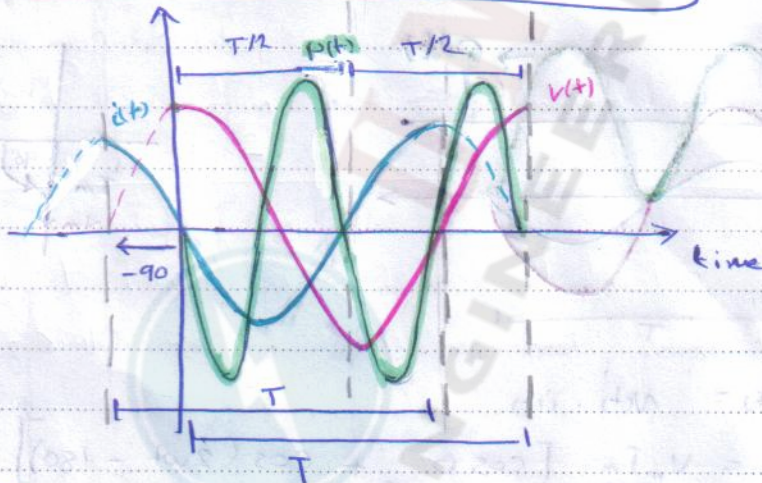
$$P(t) = -\frac{V_m I_m}{2} (\cos 2\omega t)$$




$$P_{avg} = 0$$

$$P_{peak} = \frac{V_m I_m}{2}$$



open cct

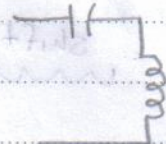


short cct

$$X_L = X_C$$

$$\omega L = \frac{1}{\omega C}$$


Resonance cct.

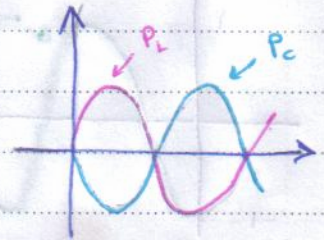

24-9-2014
Wednesday

No. Lecture 4

Pure Resistive.

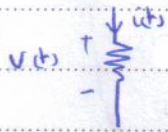


$$v(t) = V_m \sin(\omega t)$$

$$i(t) = I_m \sin(\omega t)$$

$$V_m \cos(\omega t - 90^\circ)$$

$$\bar{V} = V_m \angle -90^\circ \text{ V}$$


$$I = I_m \angle -90^\circ \text{ A}$$

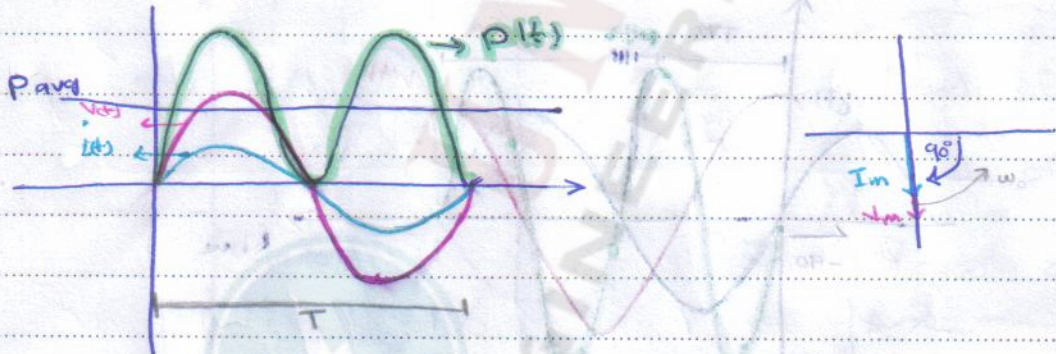

$$\text{so } p(t) = v(t) \cdot i(t)$$

$$= \frac{V_m I_m}{2} [\cos \theta + \cos(2\omega t - 180^\circ)]$$

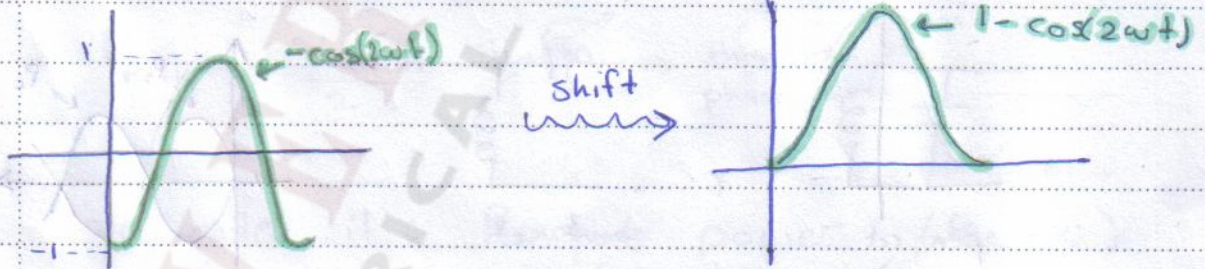
$$= \frac{V_m I_m}{2} [1 - \cos(2\omega t)]$$



$$P = \frac{1}{T} \int_0^T p(t) dt = \frac{V_m I_m}{2}$$

$$P_{avg} = \frac{V_m I_m}{2} = \frac{I_m^2 R}{2} = \frac{V_m^2}{2R}$$

→ Pure inductive -

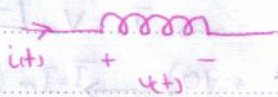

$$v(t) = V_m \sin(\omega t)$$

$$\bar{V} = V_m \angle -90$$

$$i(t) = I_m \sin(\omega t - 90)$$

$$\bar{I} = I_m \angle -180$$

$$-I_m \cos(\omega t)$$



$$p(t) = v(t) \cdot i(t)$$

$$= \frac{V_m I_m}{2} [\cos(\omega t - 90)]$$


$$= -\frac{V_m I_m}{2} [\sin(2\omega t)]$$

$$P_{avg} = 0$$


← does not consume power

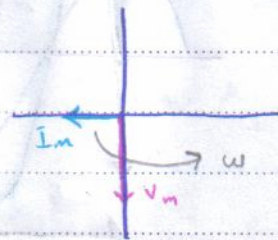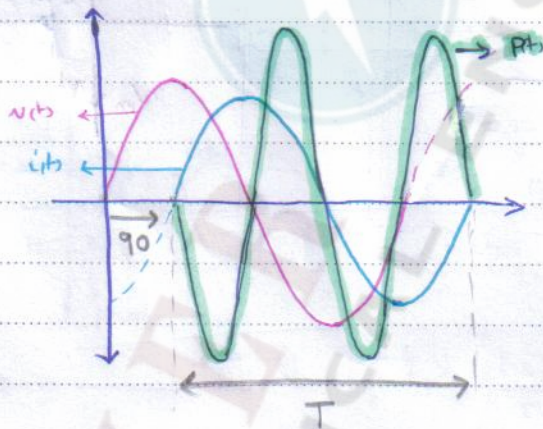


$$P_{max} = \frac{V_m I_m}{2}$$

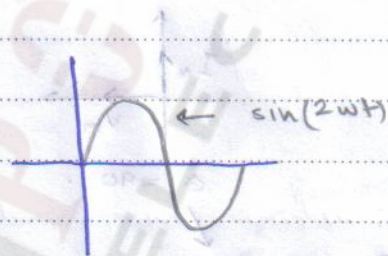

x - 1

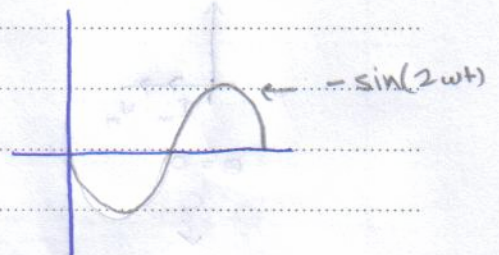

→ Pure capacitive

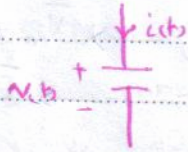



$$v(t) = V_m \sin(\omega t) \rightarrow \bar{V} = V_m / \sqrt{2}$$

$$i(t) = I_m \sin(\omega t + 90) \rightarrow \bar{I} = I_m / \sqrt{2}$$

$$I_m \cos(\omega t)$$




$$P(t) = \frac{V_m I_m}{2} [\cos(90) + \cos(2\omega t - 90)]$$
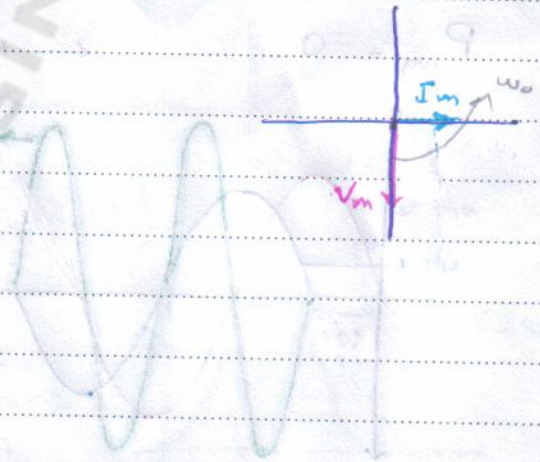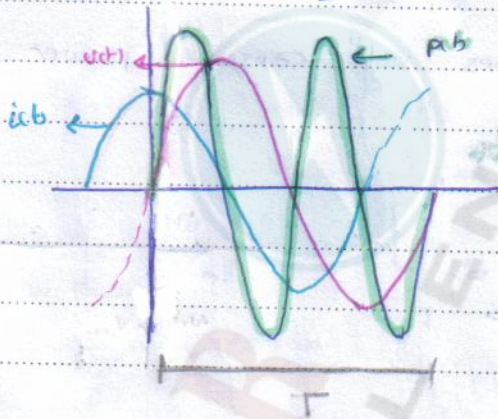
$$= \frac{V_m I_m}{2} [\sin(2\omega t)]$$




$$P_{avg} = 0$$

* Remember

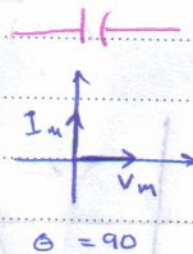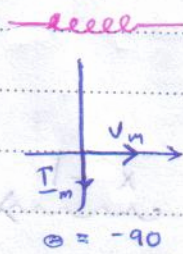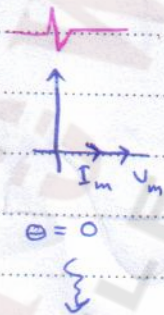


Reactive power
(Reduces the flux)

$$\frac{V_m I_m}{2} \sin \theta$$

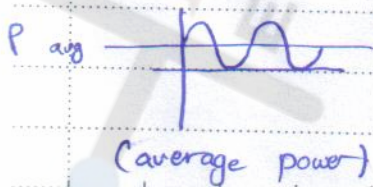

** Consider conductive load.

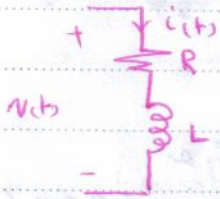

$$v(t) = V_m \sin(\omega t) \Rightarrow V_m \cos(\omega t - 90)$$

$$i(t) = I_m \sin(\omega t - \theta) \Rightarrow I_m \cos(\omega t - 90 - \theta)$$



Phase shift $\Rightarrow \theta = \theta_v - \theta_i$
 $= 90 - (-90 - \theta) = \theta \neq$

$$p(t) = v(t) \cdot i(t)$$


$$= \frac{V_m I_m}{2} [\cos(\theta) - \cos(2\omega t + \theta)]$$

← shift < 1 up/down
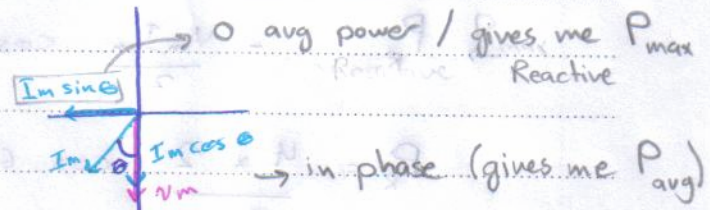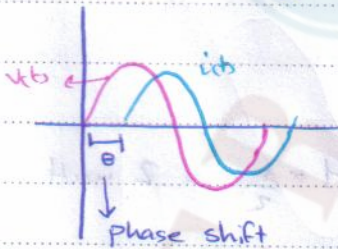
$$P = \frac{V_m I_m}{2} \cos \theta = V_m I_m \cos(\theta_v - \theta_i)$$



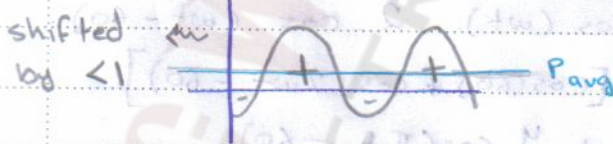
$$\Rightarrow \cos \theta = \cos(\theta_v - \theta_i) \equiv \text{we called it}$$



Power Factor

** For capacitive

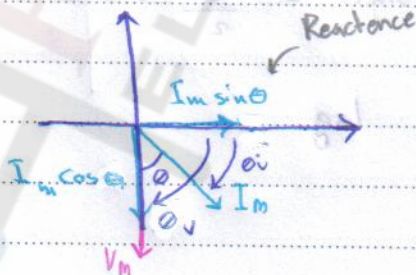

$$P_R = \frac{I_m V_m}{2} \cos \theta$$

$$P_L = \frac{V_m I_m}{2} \sin \theta$$

*ex. (11.2.)


$$v = 4 \cos(\pi t) \text{ V}$$

$$z = 2 \angle 60^\circ$$

Find P , $P(t)$

$$\omega = \frac{\pi}{6} \rightarrow f = \frac{\pi/6}{2\pi} = \frac{1}{2} \text{ Hz}$$

Sol.

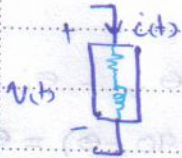

$$\rightarrow 2 \angle 60^\circ \Omega$$


$$= 2 \cos 60 + j 2 \sin 60$$

$$= 1 + j\sqrt{3} \Omega$$

$$= R + jX_L \Rightarrow \text{Inductor \& Resistor}$$

$$\bar{I} = \frac{\bar{V}}{Z} = \frac{4 \angle 0}{2 \angle 60} = 2 \angle -60 \text{ A}$$
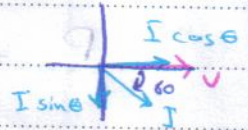
$$\Theta = \Theta_v - \Theta_i = 0 - (-60) = 60$$



$$\rightarrow P_{\text{Resistor}} = \frac{V_m I_m \cos \Theta}{2}$$


$$P_R = \frac{4 \times 2 \cos 60}{2} = 4 \times \frac{1}{2} = 2 \text{ watt}$$

$$\text{OR } P_R = \frac{I_m^2 R}{2} = \frac{(2)^2}{2} \times 1 = 2 \text{ watt}$$

$$\begin{aligned} \rightarrow P(t) &= v(t) \cdot i(t) = 4 \cos(\omega t) \cdot 2 \cos(\omega t - 60) \\ &= \frac{8}{2} [\cos(60) + \cos(2\omega t - 60)] \\ &= 2 + 4 \cos\left(\frac{\pi t}{3} - 60\right) \end{aligned}$$

$$\rightarrow \Phi_L = V_m I_m \sin \Theta = \frac{4 \times 2 \sin \Theta}{2} = \frac{4\sqrt{3}}{2} = 2\sqrt{3} \text{ VAR}$$
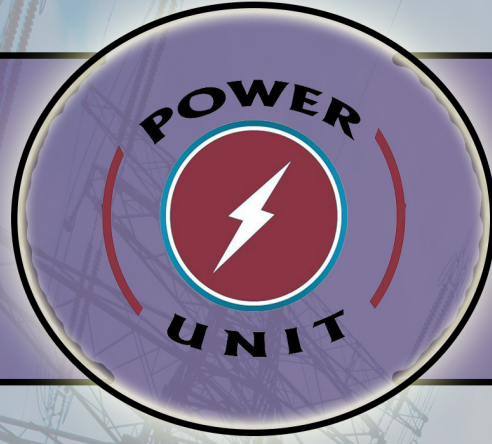
$$\rightarrow \text{PF} = \cos \Theta = \cos 60 = \frac{1}{2} \text{ lag}$$



Circuits II Notebook

Dr. Iyad Abulfailat


By . Isra' Jamil

بأفكارنا نبدع

3 & 4 Weeks

$$p(t) = V_m \cos(\omega t + \theta) \cdot I_m \cos(\omega t)$$
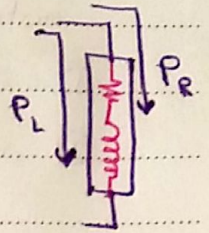
$$= \frac{V_m I_m}{2} [\cos(\theta) + \cos(2\omega t + \theta)]$$



$$= \frac{V_m I_m}{2} \cos(\theta) + \frac{V_m I_m}{2} \cos(2\omega t + \theta)$$


average power

$$P = \frac{1}{T} \int_0^T p(t) dt = \frac{V_m I_m}{2} \cos \theta$$

$$p(t) = \frac{V_m I_m}{2} \cos \theta + \frac{V_m I_m}{2} \cos(2\omega t) - \frac{V_m I_m}{2} \sin \theta \sin 2\omega t$$


$\underbrace{\hspace{10em}}$
 $\underbrace{\hspace{10em}}$

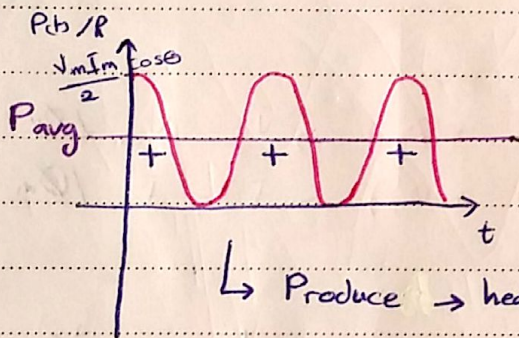$P(t) \text{ from } R$
 $P(t) \text{ from } L$



$$P = \frac{V_m I_m}{2} \cos \theta$$

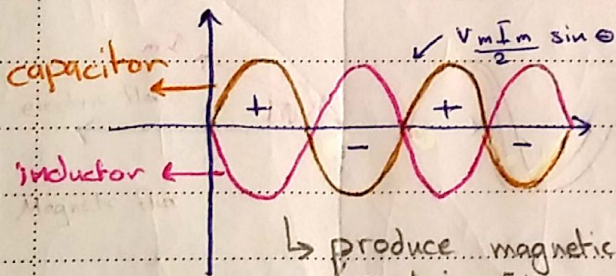↳ Produce → heat, light, mechanical motion




$$Q = \frac{V_m I_m}{2} \sin \theta$$

$> 0 \rightarrow$ inductor
 $< 0 \rightarrow$ capacitor

$$P = 0$$

↳ produce magnetic & Electric Flux

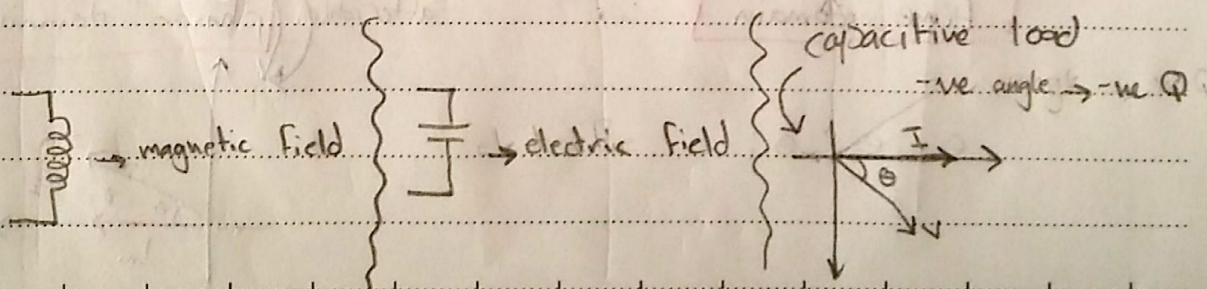

$$P = \frac{V_m I_m}{2} \cos \theta \quad (\text{watt}) \rightarrow \text{Active / Real / Average / usefull}$$

$$Q = \frac{V_m I_m}{2} \sin \theta \quad (\text{VAR}) \rightarrow \text{Reactive}$$

(Volt Ampier reactive)

$$\star V_{\text{eff}} = V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

For pure sinusoidal,

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}}$$

so,

$$P = V_{\text{rms}} I_{\text{rms}} \cos \theta \quad (\text{watt})$$

$$Q = V_{\text{rms}} I_{\text{rms}} \sin \theta \quad (\text{VAR})$$


* $\cos \theta \equiv$ Power factor

$$\text{PF} = \cos \theta = \frac{P}{V_{\text{rms}} I_{\text{rms}}}$$

$$-90 \leq \theta \leq 90$$

$$\text{so } 0 \leq \cos \theta \leq 1$$

The default is not the rms values !!

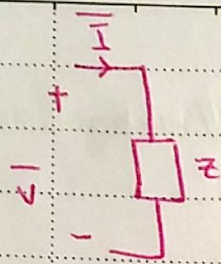

$$Z = \frac{\bar{V}}{I} = \frac{V \angle \theta}{I \angle \phi} \quad (\text{according to the previous example})$$

$$\Rightarrow Z = \frac{|V|}{|I|} \angle \theta = |Z| \angle \theta$$

** in polar form it will be:

$$Z = Z \cos \theta + j Z \sin \theta$$

Real
Imag

$$\downarrow \qquad \downarrow \qquad \downarrow$$

$$Z = R + jX$$

- For inductive load:

$$\theta = \theta_v - \theta_i > 0$$



$$\Rightarrow X > 0$$

- For capacitive load:

$$\theta = \theta_v - \theta_i < 0$$

$$\Rightarrow X < 0$$
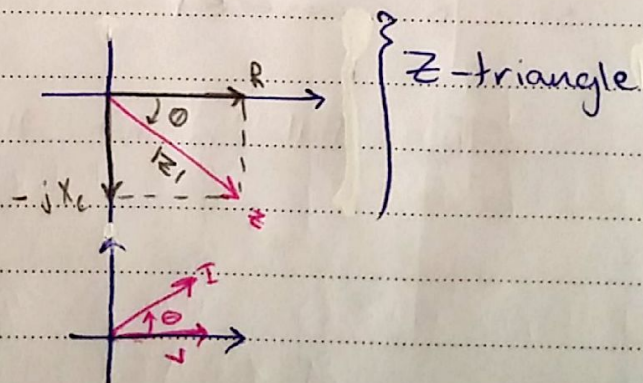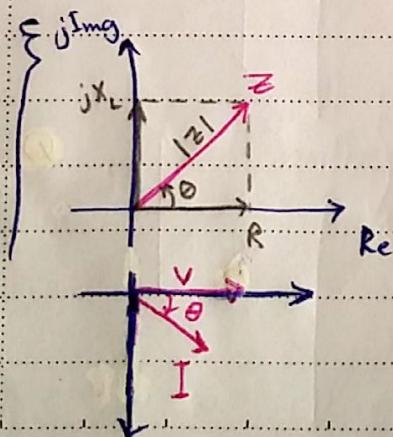
$$Z \begin{cases} \rightarrow R + jX_L & (X_L = \omega L) \\ \rightarrow R - jX_C & (X_C = \frac{1}{\omega C}) \end{cases}$$



* note that.

$$P = \text{Re} \{ S \} = V_{\text{rms}} I_{\text{rms}} \cos \theta$$

$$Q = \text{Im} \{ S \} = V_{\text{rms}} I_{\text{rms}} \sin \theta$$

also $P = \text{Re} \{ V e^{j\theta_v} \cdot I e^{-j\theta_i} \} = \text{Re} \{ \bar{V} \cdot \bar{I}^* \}$


$$Q = \text{Im} \{ \bar{V} \cdot \bar{I}^* \}$$

$$\bar{I} = I \angle \theta$$

$$\bar{I}^* = I \angle -\theta$$

→ example 11.9

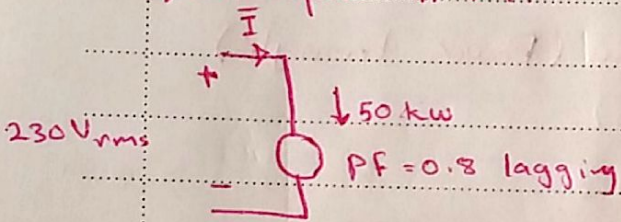- Power Factor correction -
- Power factor improvement -




; calculate the current drawn by the motor.

sol. $\text{pf} = 0.8 = \cos \theta$


$$\Rightarrow \theta = \cos^{-1}(0.8) = 36.9^\circ$$

رابطه با خازن
reference

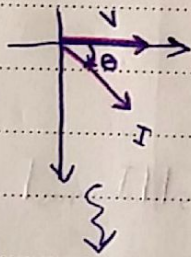

$$\bar{V} = 230 \angle 0$$

$$\bar{I} = |I| \angle -\theta$$

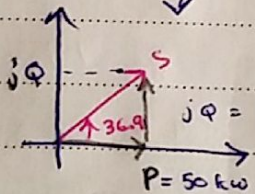

$$jQ = 37.5 \text{ kVAR}$$

$$|S| = \frac{P}{\cos \theta} = \frac{50 \text{ k}}{0.8} = 62.5 \text{ kVA}$$

$$Q = S \sin \theta = 62.5 \text{ k} \times \sin(36.9^\circ)$$

$$= \boxed{37.5 \text{ kVAR}}$$

→

$$\leftarrow S = P + jQ = \bar{V}_{rms} \cdot \bar{I}_{rms}^*$$

$$62.5 \angle 36.9 = 230 \angle 0 \cdot I \angle \theta$$





$$\bar{I} = \frac{S^*}{\bar{V}} = \frac{62.5 \angle -36.9}{230} = 271.7 \angle -36.9^\circ \text{ A}$$

$$\text{OR } |\bar{I}| = \frac{|S|}{|V|} = \frac{62.5}{230} = 271.7 \text{ A (as a magnitude)}$$

→ inductive so directly $\theta_i = -36.9^\circ$

$$\Rightarrow \boxed{\bar{I} = 271.7 \angle -36.9} \quad \#$$

* Be familiar with these triangles.

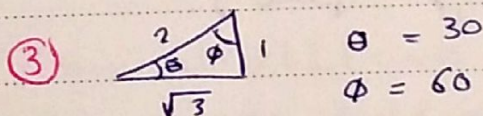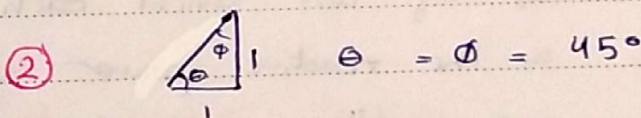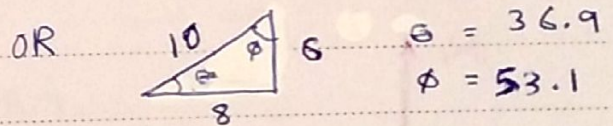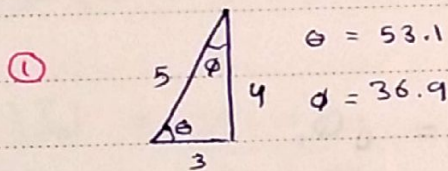

OR to find Q & $|S|$ " for the previous example

$$* Q = P_{avg} \times \tan \theta = 50 \text{ k} \times \tan(36.9)$$

$$= 37.5 \text{ kVAR}$$


$$* |S| = \frac{P_{motor}}{PF_{motor}} = \sqrt{(P_{motor})^2 + Q_{motor}^2}$$

$$= \frac{50 \text{ k}}{0.8} = 62.5 \text{ kVA}$$

* Note \rightarrow if we increase the PF, the angle θ will decrease, so (jQ) Reactive power will decrease too.

** note : we can improve P.F by:

- we can add capacitor.

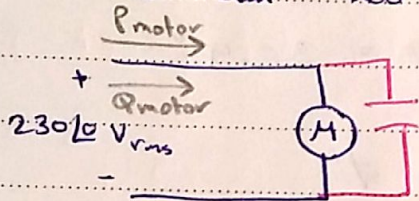


$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

where $\omega = 2\pi f$

& $f = 50 \text{ Hz}$

& $\omega = 314 \text{ rad}$

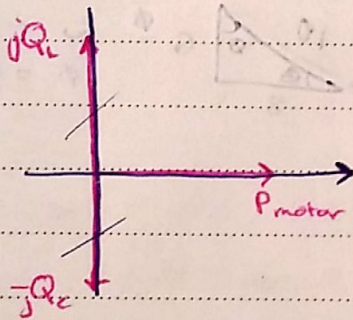


$$jQ_L = jQ_C$$

\rightarrow they will cancel each other so the reactive power will be zero. (there will be just average power).

\rightarrow back to the example, we need to improve the pf to 0.95

PF_{new} = 0.95 lagging.
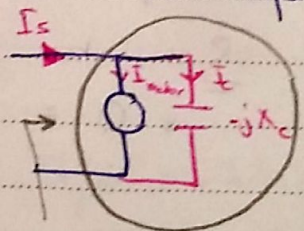
$$\theta_{\text{new}} = \cos^{-1}(0.95) = 18.2^\circ$$



PF = 0.95 lagging \rightarrow

$$|I_c| = \frac{|V_c|}{|X_c|}$$

$$Q_c = \frac{V_c^2}{X_c} = V_c^2 \text{ rms} \times \omega C$$

No.


$$\bar{I}_c = \frac{\bar{V}_s}{-jX_c} = \frac{+j\bar{V}_s}{X_c} = \frac{\bar{V}_s}{X_c} \angle 90^\circ$$

$$P_{\text{motor}} = |V_s| |I_{\text{motor}}| \cos \theta = 50 \text{ kW}$$

$$Q_{\text{motor}} = |V_s| |I_{\text{motor}}| \sin \theta =$$

$$I_{\text{motor}} = \frac{P_{\text{motor}}}{V_s \cos \theta} = \frac{50 \times 10^3}{230 \times 0.8} = 271.7 \text{ A}$$
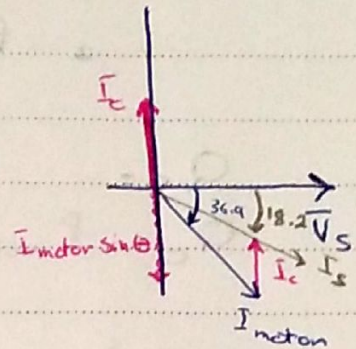
$$\hookrightarrow \bar{I}_{\text{motor}} = 271.7 \angle -36.9^\circ \text{ A}$$



$$P_{\text{source}} = |V_s| |I_s| \cos \theta$$

$$50 \text{ kW} = 230 |I_s| 0.95$$

adding the capacitor will not effect the P

$$|I_s| = \frac{50 \times 10^3}{230 \times 0.95} = 228.8 \text{ A}$$


using power triangle.

$$Q_{\text{source}} = |V_s| |I_s| \sin \theta$$

$$= 230 \times 228.8 \times \sin(18.2)$$

$$= 16.4 \text{ kVAR}$$

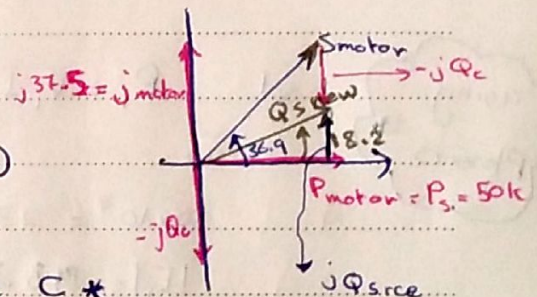* S_{motor} is S_{source} before adding the C *




$$\tan \theta = \frac{Q}{P}$$

$$\rightarrow Q = P \tan \theta$$

$$S_{\text{source}} = S_c + S_{\text{motor}}$$
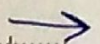
$$= -jQ_c + (P_{\text{motor}} + jQ_{\text{motor}})$$



$$\begin{aligned} \leftarrow &= P_{\text{motor}} + j [Q_{\text{motor}} - Q_c] \\ &= P_{\text{motor}} + j Q_{\text{source}} \end{aligned}$$

$$Q_c = P_{\text{motor}} [\tan \theta_{\text{old}} - \tan \theta_{\text{new}}]$$

$$\begin{aligned} \omega C V_{\text{rms}}^2 &= 50 \times 10^3 [\tan(36.9^\circ) - \tan(18.2^\circ)] \\ (314) \times C (230)^2 &= 21.1 \times 10^3 \end{aligned}$$


$$\Rightarrow C = \frac{21.2 \times 10^3}{314 (230)^2}$$

$$\Rightarrow C = 1.3 \mu\text{F}$$

where $\omega = 314$

$$Q_c = \frac{V_{\text{rms}}^2}{X_c}$$
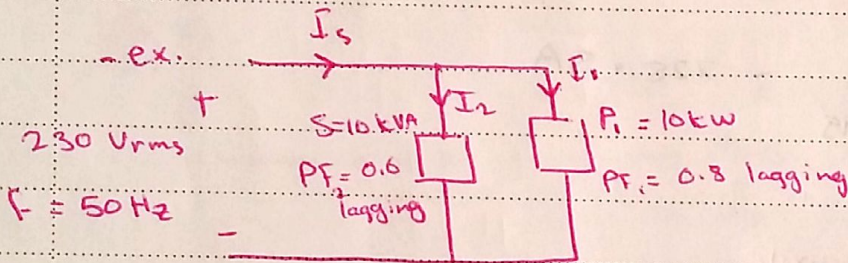
$$\Rightarrow Q_c = V_{\text{rms}}^2 \times \omega C$$




using phasors

sol. $P_i = V_i I_i \cos \theta_i$

$$10 \times 10^3 = 230 \times |I_1| \times 0.8$$

$$|I_1| = 54.3 \text{ A}$$
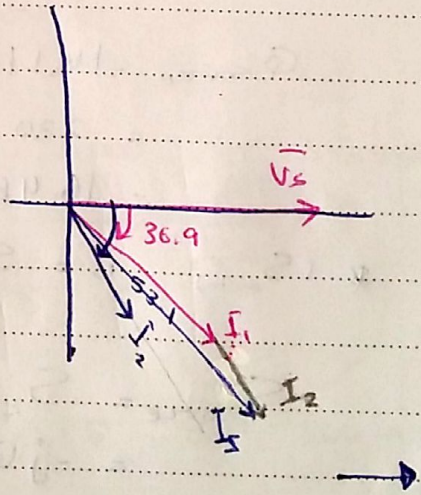
$$\rightarrow \vec{I}_1 = 54.3 \angle -36.9^\circ$$



$$S_2 = |V_s| |\bar{I}_2|$$

$$10 \times 10^3 = 230 |\bar{I}_2|$$

$$\Rightarrow |\bar{I}_2| = 43.4 \text{ A}$$

$$\rightarrow \bar{I}_2 = 43.4 \angle -53.1^\circ \text{ A}$$


$$\bar{I}_s = \bar{I}_1 + \bar{I}_2$$

$$= 54.3 \angle -36.9^\circ + 43.4 \angle -53.1^\circ$$

$$= 96.7 \angle -44.1^\circ$$

$$\begin{aligned} \bar{S}_2 &= \bar{V}_s \times \bar{I}_2^* \\ &= P_2 + jQ_2 \\ &= |S|_2 \angle \theta_2 \end{aligned}$$

Ⓘ using power triangle :

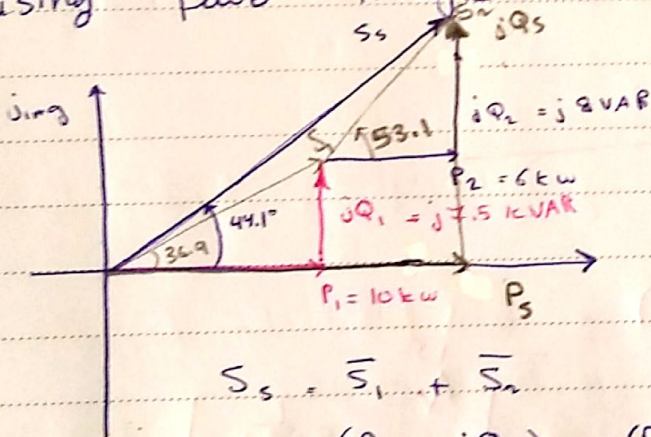

$$S_s = \bar{S}_1 + \bar{S}_2$$

$$= (P_1 + jQ_1) + (P_2 + jQ_2)$$

$$= (10 + j7.5) + (6 + j8)$$

$$= 16 + j15.5 \text{ kVA}$$

$$= 22.3 \angle 44.1^\circ \text{ kVA}$$


$$\Rightarrow P_s = 16 \text{ kW}$$

$$\& Q_s = 15.5 \text{ kVAR}$$

$$PF_{\text{new}} = \cos(44.1)$$

$$= 0.72 \text{ lagging}$$

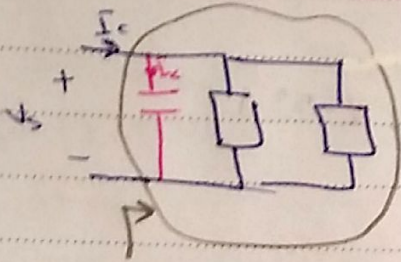→ to improve PF to a unity power factor we will add the capacitor.



$$Q_c = P_{rd} [\tan \theta_{\text{old}} - \tan \theta_{\text{new}}]$$

$$= 16 \text{ k} [\tan 44.1 - \tan 0^\circ]$$

$$= 15.5 \text{ kVAR}$$

$$\omega C V_{\text{rms}}^2 = Q_c$$

$$(314)(C)(230)^2 = 15.5 \times 10^3$$

$$C = 9.3 \times 10^{-4}$$

$$= 0.93 \text{ mF}$$

$$= 930 \text{ MF}$$

example: (Practice 11.9)


Find:

a) \vec{S} $R = 1 \Omega$

b) \vec{S} $Z = j10 \Omega$

c) \vec{S} $5 + j10 \Omega$


d) \vec{S} source

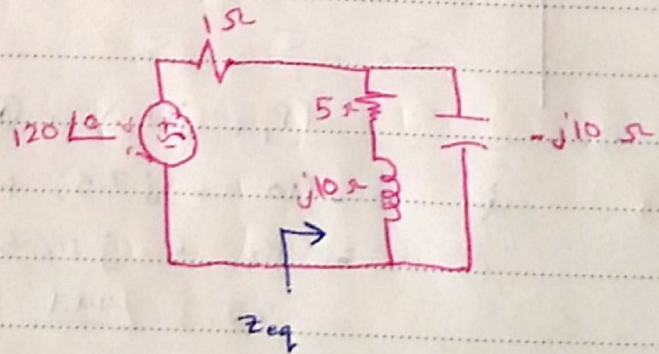

→


sol.

NOTE :-

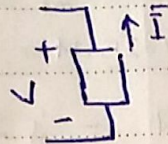

$$\bar{S} = V \cdot \bar{I}^*$$

$P > 0$
 $Q > 0$ } generated power

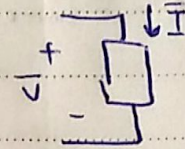


$$\bar{S} = \bar{V} \cdot \bar{I}^*$$

$$= P + jQ$$

absorbed ← $\left\{ \begin{array}{ll} P > 0 & P > 0 \rightarrow \text{absorbed} \\ Q > 0 & Q < 0 \rightarrow \text{generated} \end{array} \right.$

** we will find the current.

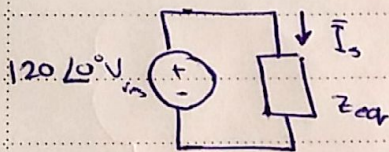

$$Z_{eq} = -j10 \parallel (5 + j10) + 1 \ \Omega$$

$$= \frac{10 \angle -90^\circ \times 11 \angle 63^\circ}{5 + j10 - j10} + 1 \ \Omega$$

$$= \frac{111 \angle -26.6^\circ}{5} + 1 \ \Omega$$


$$= 22.2 \angle -26.6^\circ + 1 \ \Omega$$

$$= 20.8 - j9.9 \ \Omega$$

$$= 23.09 \angle -25.4^\circ \ \Omega$$

$$\Rightarrow \bar{I}_s = \frac{V_s}{Z_{eq}} = \frac{120 \angle 0^\circ}{23.09 \angle -25.4^\circ} = \boxed{5.2 \angle +25.4^\circ \text{ A}_{rms}}$$

$$|I_s| = 5.2 \text{ A}$$

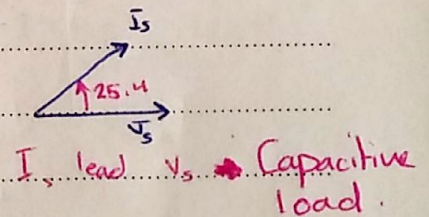

$$\bar{S}_{source} = \bar{V}_s \cdot \bar{I}_s^*$$

→

$$\begin{aligned} \text{or } \vec{S}_{\text{source}} &= 120 \angle 0^\circ \times 5.2 \angle -25.4^\circ \\ &= 624 \angle -25.4^\circ \text{ VA} \\ &= 563.7 - j267.7 \text{ VA} \end{aligned}$$

$$\Rightarrow P = 563.7 \text{ watt (generated power)}$$

$$\Rightarrow Q = -267.7 \text{ VAR (capacitive)}$$

$$\& P_{\text{absorbed}} = -563.7 \text{ watt}$$

$$Q_{\text{absorbed}} = 267.7 \text{ VAR} \quad \left. \begin{array}{l} \\ \end{array} \right\} \text{according to the convention!}$$

Note: angle of the power is $-$ (the angle of the current)

$$\begin{aligned} \vec{S} &= \vec{V} \times \vec{I}^* \\ &= \frac{\vec{V} \times \vec{V}^*}{\vec{Z}^*} = \frac{|V|^2}{\vec{Z}^*} \end{aligned}$$

$$P_{1\Omega} = |I_{\text{rms}}|^2 R$$

$$= (5.2)^2 (1) = 27.04 \text{ W}$$

$$\begin{aligned} \text{** By current divider } \rightarrow \vec{I}_L &= \frac{\vec{I}_s \times (-j10)}{5 + j10 - j10} \\ &= \frac{5.2 \angle -25.4^\circ \times 10 \angle -90^\circ}{5} \end{aligned}$$

$$\Rightarrow \vec{I}_L = 10.4 \angle -64.6^\circ \text{ A}_{\text{rms}}$$

$$\begin{aligned} \Rightarrow \vec{I}_C &= \vec{I}_s - \vec{I}_L \\ &= (4.7 + j2.2) - (4.5 - j9.3) \\ &= 0.2 + j11.5 \text{ A}_{\text{rms}} \\ &= 11.5 \angle 89^\circ \text{ A}_{\text{rms}} \end{aligned}$$



$$\bar{I} \cdot I^* = |I|^2$$

No.

$$\begin{aligned} \leftarrow S_L &= \bar{V}_L \cdot \bar{I}_L^* \\ &= I_L \cdot Z_L \cdot I_L^* = |I|^2 \cdot Z_L = (10.4)^2 (5 + j10) \end{aligned}$$

$$S_L = 1209.3 \angle +63.4 \text{ VA} \quad (\text{polar form})$$

$$\text{absorbed} \leftarrow S_L = 540.8 + 1081.6j \text{ VA} \quad (\text{rectangular form})$$

$$P_L = 540.8 \text{ W}$$

$$Q_L = 1081.6 \text{ VAR}$$

$$\begin{aligned} S_C &= \bar{V}_C \cdot \bar{I}_C^* \\ &= \bar{V}_C \cdot Z_C \cdot I_C^* \\ &= |I|^2 \cdot Z_C = (11.5)^2 (10 \angle -90) \end{aligned}$$

$$= -j 1322.5 \text{ VAR} \rightarrow \text{absorbed}$$

C generates 1322.5 VAR

$$\sum S_{\text{generate}} = \sum S_{\text{absorbed}}$$

$$\left\{ \begin{aligned} P_{\text{generated}} &= 563.7 \text{ W} \end{aligned} \right.$$



$$\left\{ \begin{aligned} P_{\text{absorbed}} &= 27.04 + 540.8 = 567.8 \text{ W} \end{aligned} \right.$$

$$\left\{ \begin{aligned} Q_{\text{generated}} &= 1322.5 \text{ VAR} \end{aligned} \right.$$




$$\left\{ \begin{aligned} Q_{\text{absorbed}} &= 267.7 + 1081.6 = 1349.3 \text{ VAR} \end{aligned} \right.$$

$$\text{OR } \sum S = 0$$
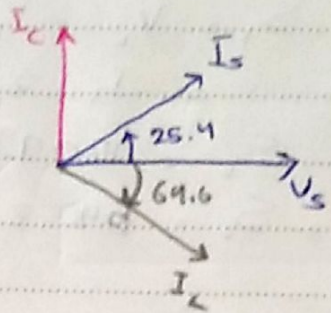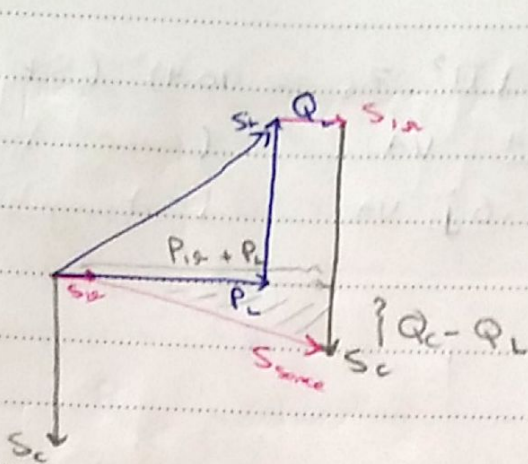
$$\bar{S}_{\text{source}} + \bar{S}_L + \bar{S}_C + \bar{S}_{\text{rest}} = 0$$




**** Maximum Power transfer**

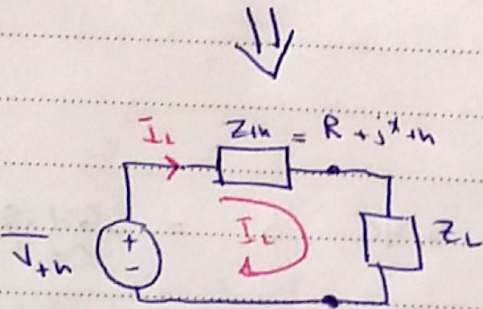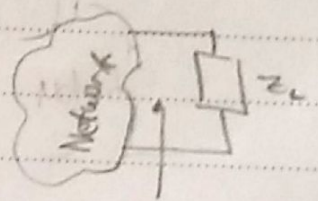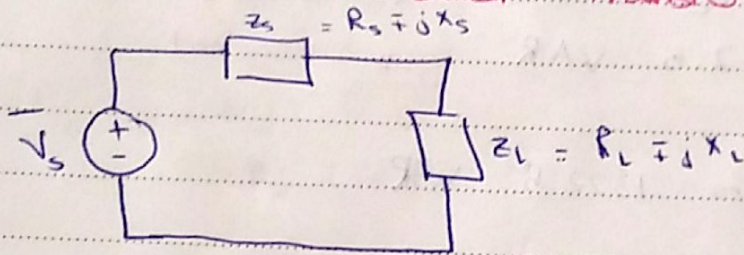

$$** \bar{I}_L = \frac{\bar{V}_{th}}{Z_{int}} = \frac{\bar{V}_{th}}{(R_{th} + jX_{th}) + R_L + jX_L}$$


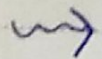
$$\bar{I}_L = \frac{\bar{V}_{th}}{(R_{th} + R_L) + j(X_{th} + X_L)}$$



$$|I_L| = \frac{|V_{th}|}{\sqrt{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}}$$

$$P_L = |I_L|^2 \times R_L$$

$$= \frac{|V_{th}|^2 \times R_L}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}$$

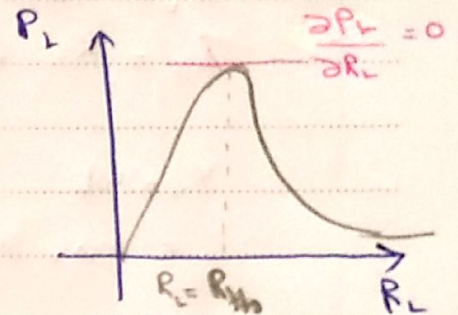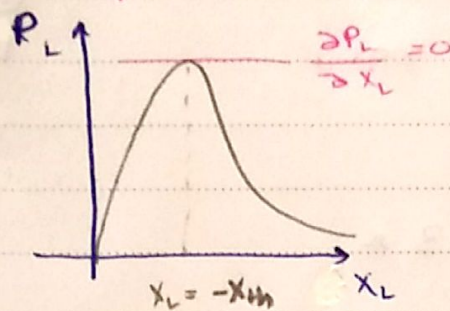

→ P_{max} occurs when :-

$$\bar{Z}_L = \bar{Z}_{th}^*$$

@ maximum power


$$\bar{I}_L = \frac{\bar{V}_{th}}{R_{th} + R_L} = \frac{\bar{V}_{th}}{2 R_{th}}$$

$$P_{max} = |I_L|^2 \times R_L$$


$$= \frac{|V_{th}|^2 \times R_{th}}{4 R_{th}^2}$$

$$\Rightarrow \boxed{P_{max} = \frac{V_{th}^2 \text{ rms}}{4 R_{th}}}$$

→ example.

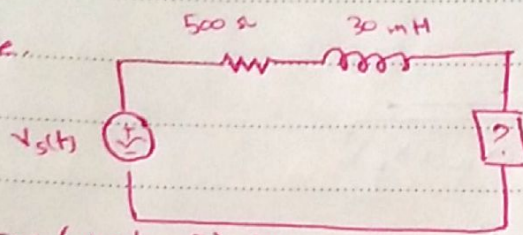


$$v_s(t) = 3 \cos(100t - 3) \text{ V}$$

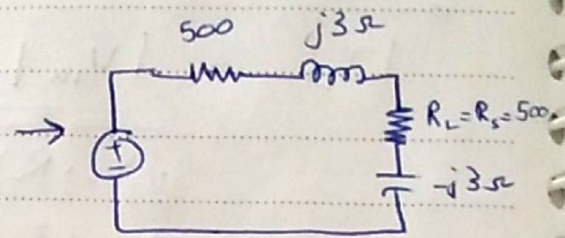

sol. For P_{\max} delivering

$$Z_L = Z_s^*$$

$$Z_s = R_s + jX_s = 500 + j3$$

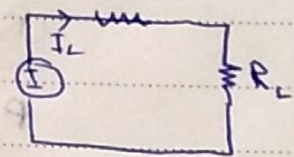

$$X_s = \omega L$$

$$= 100 \times 30 \text{ H} = 3 \Omega$$

$$P_{\max} = \frac{|V_s|_{\text{rms}}^2}{4R_s} = \frac{9/2}{4 \times 500} = \frac{9}{4 \times 1000} = 2.25 \text{ mW}$$

$$X_c = \frac{1}{\omega C}$$

$$C = \frac{1}{\omega X_c} = \frac{1}{(100)(3)}$$

$$C = 3.33 \text{ mF}$$