

8/20


اسم الطالب : محمد حسن العتيبي  
 الرقم الجامعي : .....  
 رقم التسلسل : ٤٤  
 الشعبة : ٣ : 11:00 - 12:30

ملاحظات :

- (1) الفترة الإمتحانية ساعة واحدة
- (2) لا يسمح بإدخال الهواتف الجواله
- (3) لا يسمح باستخدام الحاسبات المبرمجة
- (4) لا يسمح باستخدام القلم الرصاص بالإجابة باستثناء الرسومات
- (5) لا يسمح باستخدام قصاصات ورقية للمسودات بل يتم ذلك في الدفتر الإمتحاني


- Q1) A piece of Silicon has  $n_0 = 5 \times 10^{15} \text{ cm}^{-3}$  at 300K.  
 (a) Determine the hole concentration.  
 (b) Is the material n-type or p-type? And why?  
 (c) Calculate the impurity doping concentration.

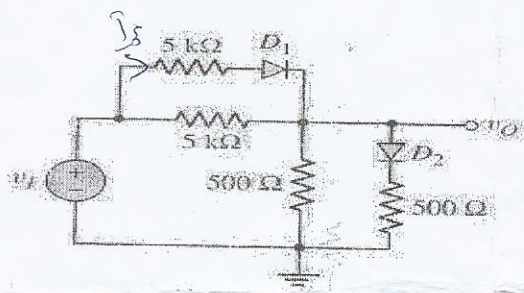- Q2) For the circuit shown, perform the following:  
 (take  $V_\gamma = 0.6 \text{ V}$ )




- (a) For  $v_i$  small, both diodes are ?  
 Therefore  $v_o = ? - - - - v_i$   
 (b) When  $D_1$  just turns on and  $D_2$  is off find  $v_o$ .

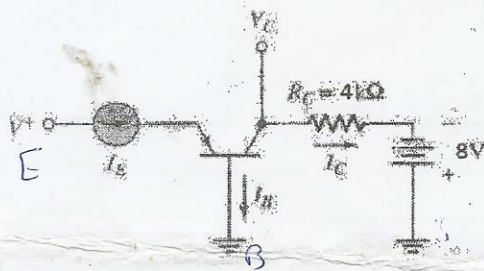Q3) For the BJT circuit shown  $\beta = 50$  and  $I_E = 0.8 \text{ mA}$



Determine  $I_B$ ,  $I_C$  and  $V_C$ .

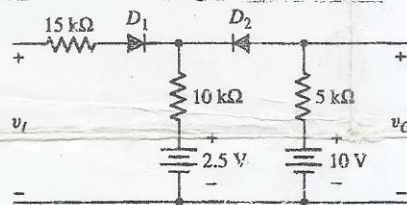Q4) For the circuit shown below  $V_\gamma = 0$  and  $r_f = 0$ . Plot  $v_o$  versus  $v_i$  for  $0 \leq v_i \leq 30 \text{ V}$



Q5) The transistor in the circuit shown below has  $\beta = 120$ . Determine  $I_C$  and  $V_{EC}$ . Plot the load line and the Q point.

