

Question 1

Consider the circuit shown in Fig. 1, with a current source of value I_I and V_I is voltage drop across it.

a) Indicate the directions of I_I and the other transistors currents.

b) Add additional components and signal(s) to the circuit for it to act as a high current amplifier.

$$A_i \approx \beta_1 \beta_2$$

c) Perform the following dc analysis.

i) Express I_R in terms of β and I_{B1} .

$$\begin{aligned} I_{RC} &= I_{C2} + I_C \\ I_{C2} &= \beta_n I_{B2} = \beta_2 I_{E1} = \beta_2 (1 + \beta_1) I_{B1} \\ I_C &= \beta_1 I_{B1} \end{aligned}$$

ii) Write two equations involving V_I .

$$eq\ 1: 0 + 520 I_{B1} + 0.7 + 0.7 + V_I - 9 = 0$$

$$eq\ 2: -9 + 100 I_R + V_{CE2} + V_I - 9 = 0$$

iii) Solve for I_{B1} given that $V_{CE2}=8V$.

$$V_{CE2} = 8V \quad , \quad I_R = (1 + \beta_1) \beta_2 I_{B1} + \beta_1 I_{B1} \quad --- (*)$$

$$\text{From the 2 eqs in (ii)}: \quad V_I = 9 - 1.4 - 520 I_{B1} = 7.6 - 520 I_{B1}$$

$$\text{Sub } ① \text{ in } ②: \quad -9 + 100 I_R + 8 + (7.6 - 520 I_{B1}) - 9 = 0$$

$$\therefore I_R \text{ eq: } -9 + 100 (101 * 100 I_{B1} + 100 I_{B1}) + 8 + 7.6 - 520 I_{B1} - 9 = 0$$

$$\therefore \cancel{10000} I_{B1} - 2.4 = 0$$

$$I_{B1} = \frac{2.4}{\cancel{10000}} = 2.4 \times 10^{-4} \text{ Ampere}$$

$$iv) \text{ Calculate } V_{CE1}: \quad V_{C2} = 9 - 100 I_R = 8.975$$

$$-8.975 + V_{CE1} +$$

d) Calculate r_x and g_m for the Q_2 transistor.

$$r_{x1} = \frac{V_T}{I_{B2}} = \frac{26 mV}{2.348 \times 10^{-3}} = 10.67 \times 10^3$$

$$I_{B2} = I_{E1} = I_B (1 + \beta_1)$$


$$\frac{26 mV}{(101) * 2.47 \times 10^{-4}} = 1042.2 \Omega$$

$$g_{m2} = \frac{I_{C2}}{V_T} = \frac{2.49 \times 10^{-3}}{26 mV} = 9.595 \times 10^{-2} \text{ Volts}$$

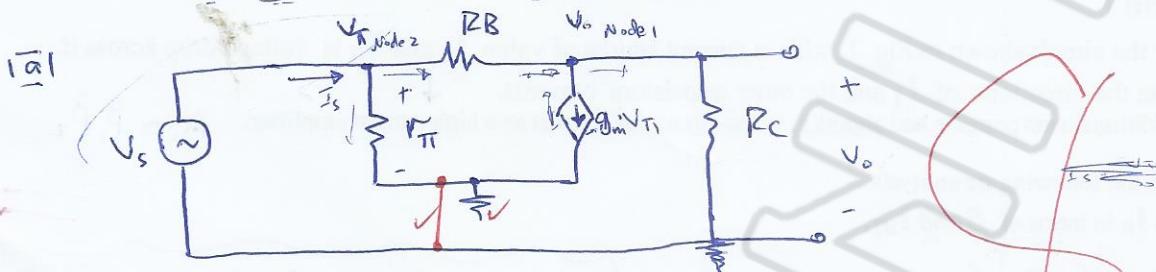Question 2

Consider the circuit shown in Fig. 2

- Draw the small signal low frequency equivalent circuit when $r_o = \infty \Omega$.
- Use the equivalent circuit together with KCL (or otherwise) to determine the voltage gain A_v in terms of R_C , R_B and g_m . What is A_v when R_B approaches $\infty \Omega$.



$$\boxed{1a} \quad \text{Node 1 : } \frac{V_o - V_{\pi}}{R_B} + \frac{V_o}{R_C} + g_m V_{\pi} = 0$$

$$\boxed{1b} \quad \text{Node 2 : } \left(\frac{V_{\pi} - V_o}{R_B} \right) + \frac{V_{\pi}}{R_{\pi}} = 0$$

$$Vs = V_{\pi} \quad (*) \quad \boxed{5}$$

$$\therefore \frac{V_o - V_{\pi}}{R_B} + \frac{V_o}{R_C} + g_m V_{\pi} = 0$$

$$Vs \left(-\frac{1}{R_B} + g_m \right) + \frac{V_o}{R_B} + \frac{V_o}{R_C} = 0$$

$$\therefore \frac{V_o}{V_i} = - \left(\frac{\frac{R_C + R_B}{R_C R_B}}{(g_m - \frac{1}{R_B})} \right) = A_v$$

- Suppose r_o is now finite, can you easily write A_v in this case based on A_v already obtained in part b?

If NO, why not? If YES, what is A_v now, (Warning: Don not calculate from first principles). *

Yes, because we put it Parallel with R_C

$$A_v = - \frac{\left(\frac{(R_C \parallel r_o) + R_B}{(R_C \parallel r_o) \times R_B} \right)}{\left(g_m - \frac{1}{R_B} \right)}$$

Question 3

Consider the circuit shown in Fig. 3

- Write down the most simple expression for A_v .
- Write down the input resistance R_i .
- Write down the configuration of the amplifier, and the output resistance R_o .
- Add a passive component to increase A_v without affecting the dc biasing. Capacitor with R_E

