

جامعة الأردن

د. مازن العبدالله

٢٠١٣/٣/٢٢

The University of Jordan  
Faculty of Engineering and Technology  
Electrical Engineering Department  
Electronics 1 First Examination  
Thurs. 7<sup>th</sup> March 2013 3-4 pm

Total

20 marks

or 20 %

إسم الطالب : .....  
الرقم الجامعي : .....  
رقم التسلسل : .....  
الشعبة : .....  
ملاحظات : .....

- (1) الفترة الامتحانية ساعة واحدة  
(2) لا يسمح بدخول الهواتف الجوالة  
(3) لا يسمح باستخدام الحاسوبات المبرمجة  
(4) لا يسمح باستخدام القلم الرصاص بالإجابة باستثناء الرسومات  
(5) لا يسمح باستخدام قصاصات ورقية للمسودات بل يتم ذلك في الدفتر الامتحاني

٤٤

Q1) A piece of Silicon has  $n_o = 5 \times 10^{15} \text{ cm}^{-3}$  at 300K.

(a) Determine the hole concentration.

$$n_o = 5 \times 10^{15} \text{ cm}^{-3}$$

$$2 \quad p_o = \frac{n_i^2}{n_o} = \frac{(1.5 \times 10^{10})^2}{5 \times 10^{15}} \Rightarrow p_o = 4.5 \times 10^4 \text{ cm}^{-3}$$

(b) Is the material n-type or p-type? And why?


$$n_o \gg p_o \Rightarrow \text{n-type}$$

(c) Calculate the impurity doping concentration.

$$n_o \equiv N_d = 5 \times 10^{15} \text{ cm}^{-3}$$

(W)

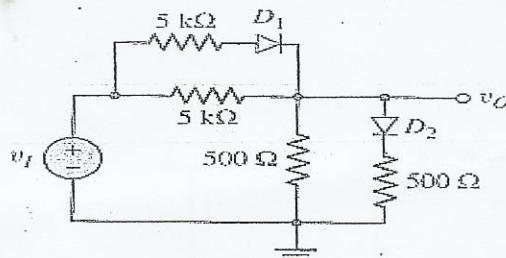Q2) For the circuit shown, perform the following: (take  $V_T = 0.6$  V)



(a) For  $v_i$  small, both diodes are OFF

Therefore  $v_o = - - - v_i \quad v_o = (0.5/5.5) v_i = 0.0909 v_i$


(b) When  $D_1$  just turns on and  $D_2$  is off find  $v_o$ .

In this case  $v_i - v_o = 0.6$  V,  $v_i - 0.0909 v_i = 0.6$ ,  $v_i = 0.66$ ,  $v_o = 0.06$  V

2

③

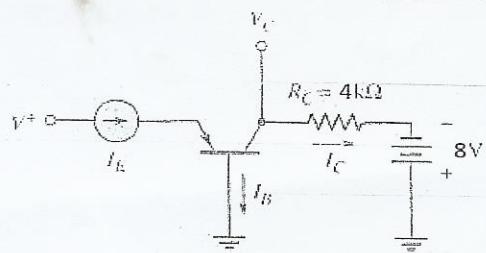Q3) For the BJT circuit shown  $\beta = 50$  and  $I_E = 0.8 \text{ mA}$



Determine  $I_B$ ,  $I_C$  and  $V_C$ .

$$I_B = I_E / (\beta + 1) = 0.8 / 51 \times 1000 = 15.686 \mu\text{A}$$

$$I_C = I_E (\beta / (\beta + 1)) = 0.8 \times 50 / 51 = 0.784 \text{ mA}$$

$$V_C = 8 - 0.784 \times 4 = 4.864 \text{ V}$$

6

- Q4) For the circuit shown below  $V_T = 0$  and  $r_f = 0$ . Plot  $v_o$  versus  $v_i$  for  $0 \leq v_i \leq 30 \text{ V}$

$$v_I = 0, D_1 \text{ off}, D_2 \text{ on}$$

$$I = \frac{10 - 2.5}{15} = 0.5 \text{ mA}$$

$$v_0 = 10 - (0.5)(5) \Rightarrow v_0 = 7.5 \text{ V for } 0 \leq v_I \leq 7.5$$


For  $v_I = 30 \text{ V}$ ,  $D_2$  off,  $v_0 = 10 \text{ V}$

Determine  $v_I$  when  $V_x = 10$

$$I = \frac{v_I - 2.5}{25}$$

$$V_x = 10 = I(10) + 2.5 \Rightarrow I = 0.75 \text{ mA}$$

$$v_I = (0.75)(25) + 2.5 = 21.25$$

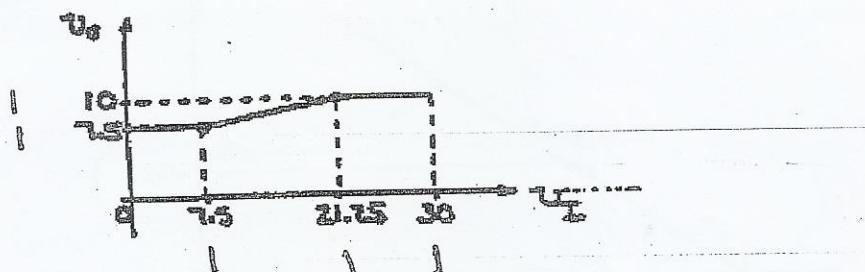

(4)

Q5) The transistor in the circuit shown below has  $\beta = 120$ . Determine  $I_c$  and  $V_{EC}$ . Plot the load line and the Q-point.

5.21

$$I_B = \frac{5 - 0.7}{250} \Rightarrow 17.2 \mu\text{A}$$

$$I_C = (120)(0.0172) = 2.064 \text{ mA}$$

$$V_C = (2.064)(1.5) - 5 = -1.90 \text{ V}$$

$$V_{EC} = 5 - (-1.90) \Rightarrow V_{EC} = 6.90 \text{ V}$$

