


Your answers should be written in ink.

0127430

14

سليم حسن العتيبي  
9:00 - 10:00

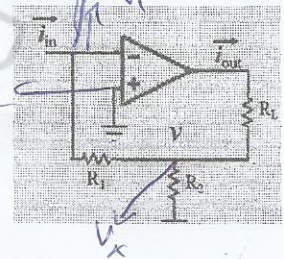Q1 a) Calculate the current gain for the op-amp circuit shown.



$$I_{in} + I_{out} = \frac{V_x}{R_2}$$

$$V_2 = V_1 = 0$$

$$V_x = V_1 - I_{in} R_1 \rightarrow$$

$$I_{in} + I_{out} = \frac{0 - I_{in} R_1}{R_2} \rightarrow (I_{in} + I_{out}) R_2 = -I_{in} R_1$$

$$I_{in} R_2 + I_{out} R_1 = -I_{out} R_2 \rightarrow$$

$$\frac{I_{out}}{I_{in}} = \frac{-(R_1 + R_2)}{R_2}$$

2

Q1 b) Draw the op-amp circuit implementing a difference amplifier and use the ideal characteristic to derive the output voltage.


by Superposition

$$V_{I2} = 0 \rightarrow V_{O1} = -\frac{R_2}{R_1} V_{I1} \rightarrow \text{inverting}$$

$$V_{I1} = 0 \rightarrow \frac{R_2}{R_1} \left( \frac{R_4}{R_3} \right) V_{I2}$$

$$V_O = V_{O1} + V_{O2}$$
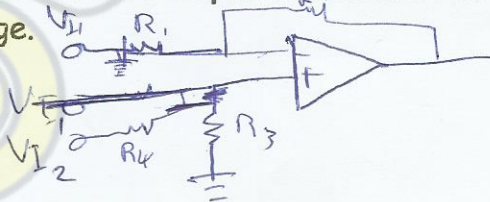
$$\frac{V_O}{V} = \frac{R_2}{R_1} \left( \frac{R_4}{R_3} \right) V_{I2} - \frac{R_2}{R_1} V_{I1}$$



3

Q1 c) Use the ideal op-amp equivalent circuit to derive the input resistance of a non-inverting amplifier when  $R_1 = \infty \Omega$  and  $R_2 = 0 \Omega$


$$R_1 = \infty$$

$$R_i = \frac{V_I}{I_{in}}$$

$$R_{in} = \frac{V_I - 0}{I_{in}} = \frac{V_I}{0} = \infty$$

because  $R_1 = \infty$

~~$$R_{in} = 2R_1$$~~

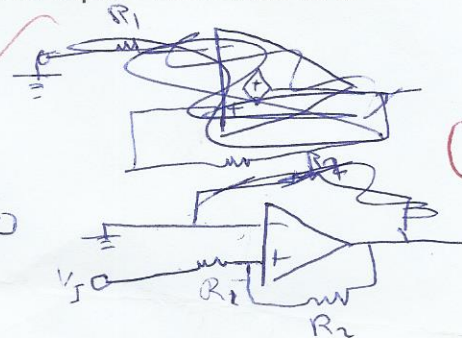

0

Q1 d) what are the advantages of field effect transistor over bipolar transistors?



Field effect transistors can Amplify more than bipolar transistors

0



$$\frac{x}{x+1}$$

Q2 Use the method of approximate time constants to determine the two corner frequencies for the circuit above and to sketch the amplitude Bode diagram, based on  $f_L$ ,  $f_H$  and the midband gain.

DO NOT DETERMINE THE TRANSFER FUNCTION.

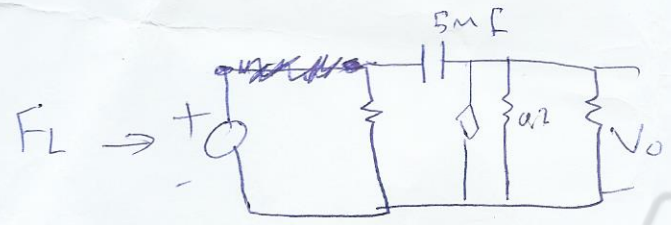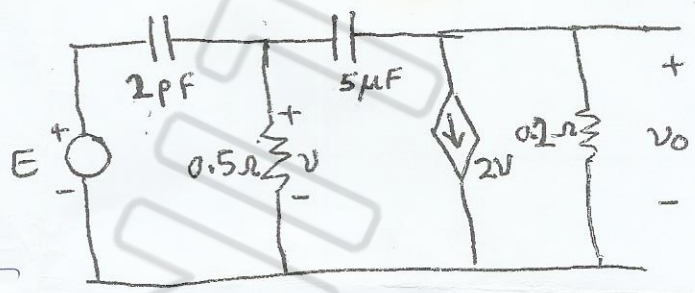

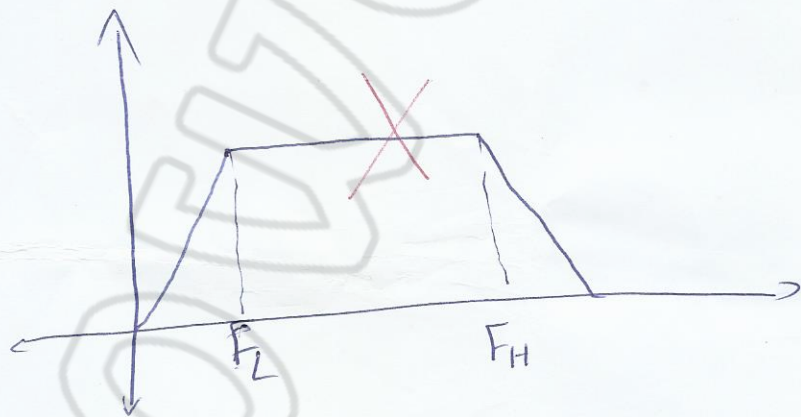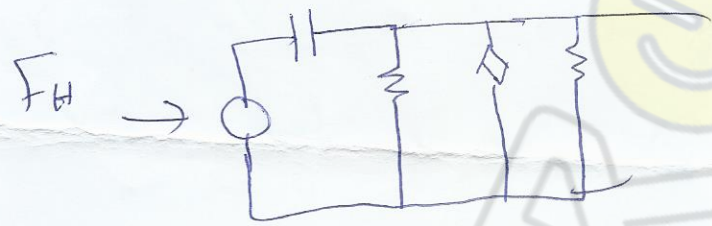
$$f_L = (0.5 + 0.2) \times 5 \mu F = 3.5 M$$



2

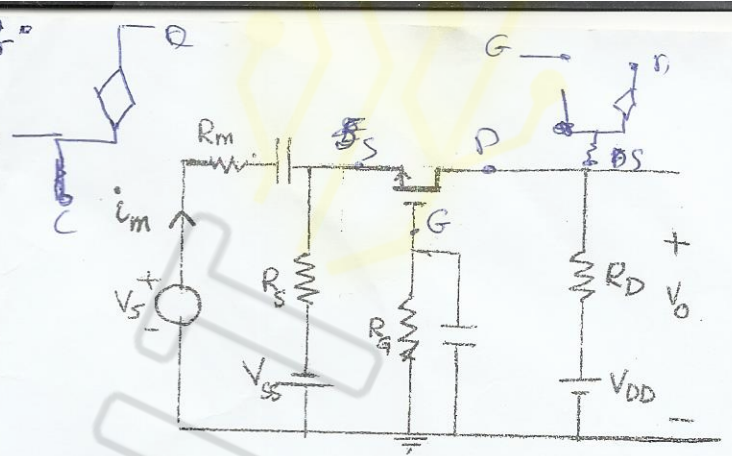Q3 Consider the circuit shown in Fig. 1  
 Draw the small signal equivalent circuit  
 And use it to calculate the current  
 Gain defined as  $\frac{i_c}{i_m}$  (BANDWIDTH)



$$i_c = -g_m v_{gs}$$

$$\frac{V_s - V_x}{R_m} + g_m v_{gs} = \frac{V_x}{R_s}$$

$$V_x = -V_{gs}$$


$$\frac{V_s + V_{gs}}{R_m} + g_m v_{gs} = -\frac{V_{gs}}{R_s}$$

$$\frac{V_s - V_x}{R_m} = i_m$$

$$i_m = \frac{-V_{gs} - g_m v_{gs}}{R_s}$$

$$i_m = \left( \frac{1}{R_s} + g_m \right) \times -V_{gs} \rightarrow V_{gs} = \frac{-i_m}{\frac{1}{R_s} + g_m}$$
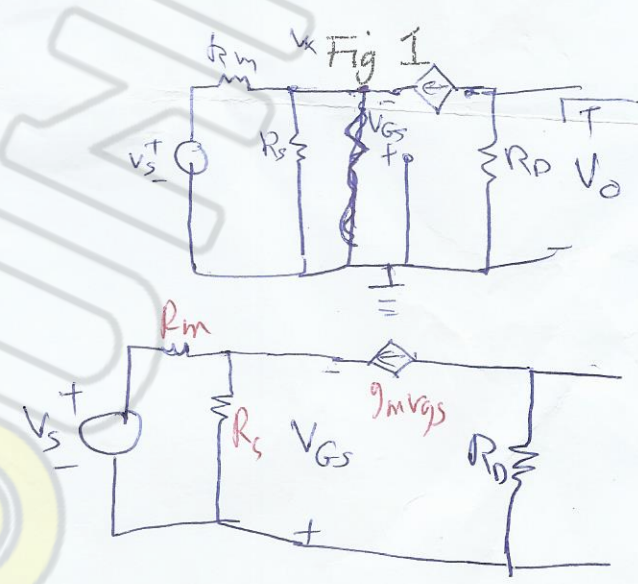
$$i_c = -g_m \times \frac{-i_m}{\frac{1}{R_s} + g_m} \rightarrow \frac{i_c}{i_m} = \frac{g_m}{\frac{1}{R_s} + g_m} = \frac{R_s g_m}{1 + g_m R_s}$$



7