



Machines1


Summer017



Dr. **M**hmd **A**lhajj





By: **H**elda **K**hader

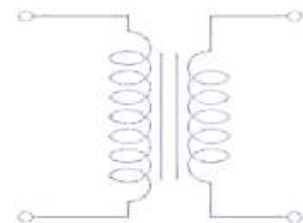

Powerunit-ju.com

Magnetic field :-
"force"

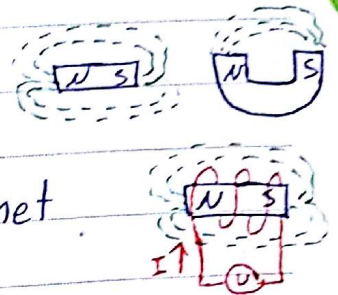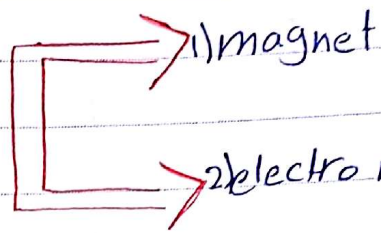


Types of materials based on it's magnetic properties :-


⇒ nonmagnetic material :- (No ability to "collect" magnetic field) $\mu_0 = \mu$ (per meability)
 $4\pi \times 10^{-7}$

⇒ Ferri - magnetic material :- It can gain ferromagnetic material properties when we apply a magnetic field on it. "AlNiCo, SmCo"

→ we have to apply a magnetic field to have another magnetic field !!! Yes, because the magnetic field that will be generated is much stronger than the ^{applied} magnetic field.

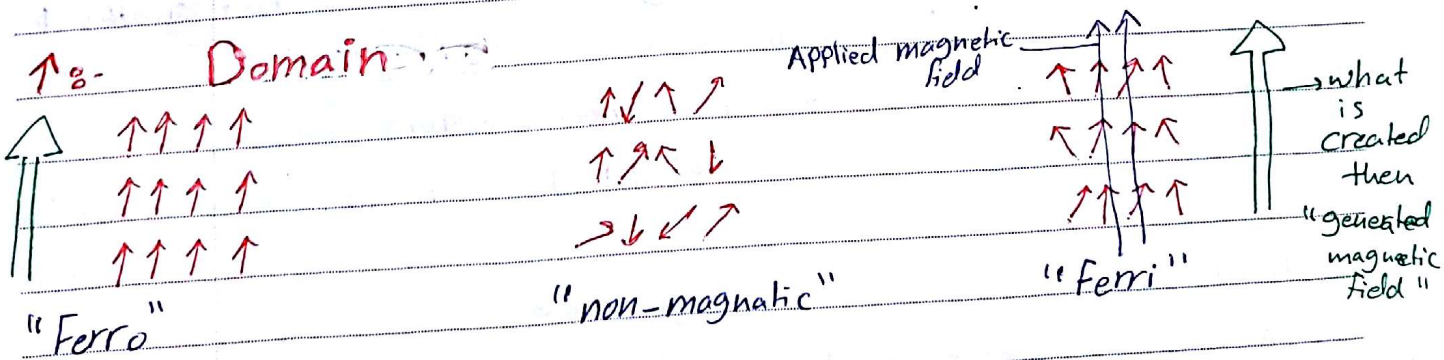
⇒ Ferromagnetic material :- has superior capability to collect magnetic field. (Iron/steel, Ni, Co)



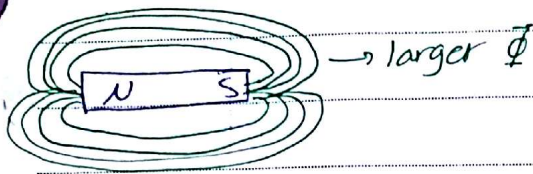

$\Phi \Rightarrow$ عدد خطوط المجال المغناطيسي

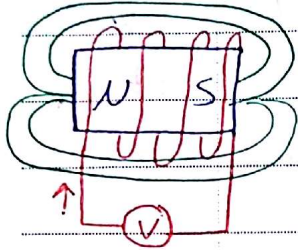$B \Rightarrow$ عدد خطوط المجال المغناطيسي على وحدة المساحة



$H \Rightarrow$ عندما يزداد التيار تزداد "H"
linear relationship

$$\oint H \cdot dl = I_{net}$$

Magnetic field is the basic force in electric machines :-


Generators :- electric machine that converts mechanical energy (in the presence of magnetic field) to electric energy

Motors :- electric machine that converts electrical energy to mechanical energy

Transformer :- converts electric AC energy with certain V & f (frequency) to electric AC energy with the same f but another V .
"by means of magnetic field"



principles of magnetic field :- a current carrying conductor establishes a magnetic field around it-self.

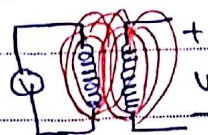\Rightarrow Transformer principle :- a time varying magnetic flux (Φ) induces a voltage in a conductor in the vicinity of the field




5/6/2017

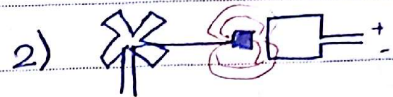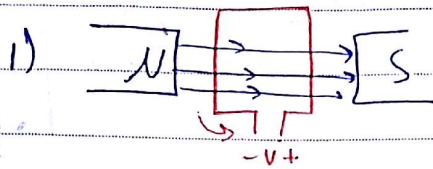
⇒ generator principle :- a moving coil in the presence of a magnetic field will have voltage induced on it.



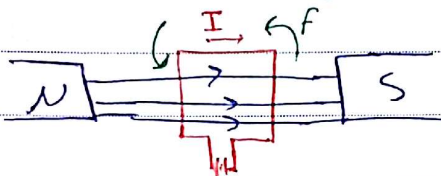
⇒ Motor principle :- a current carrying coil in the presence of a magnetic field will have force induced in it.




* Magnetic field :-

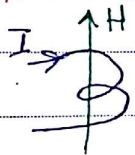

(H is weak)

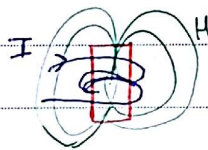

(H is stronger)

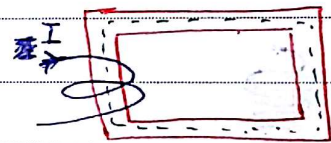

$$H \cdot L = I_{\text{enclosed}}$$

(H is much stronger)

⇒ Ampere's law

$$\oint H \cdot dl = I_{\text{enclosed}}$$

$$\oint H \cdot dl = NI = I_{\text{net}}$$

$$H \cdot L = NI$$



↳ unit $\left(\frac{\text{A} \cdot \text{turns}}{\text{m}} \right)$

H ≡ magnetic field intensity

$$\Rightarrow B = \mu H$$

↳ unit (Tesla)

B ≡ magnetic flux density

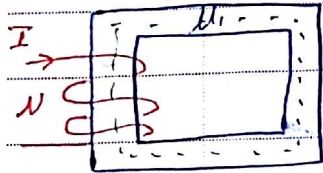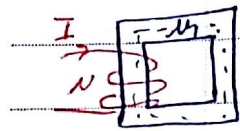



Same H
Same B → different Φ

$$\Phi = \int B \cdot dA$$

$$\Phi = B \cdot A$$


Flux → Area
Flux density
only if B is perpendicular on A.
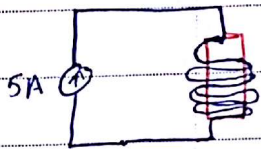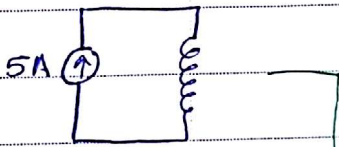
$$\Phi \Rightarrow \text{unit (Tesla} \cdot \text{m}^2) \text{ wb}$$



Same H
different B → بسبب تغير الوسط

مقطع رأسي من لوح

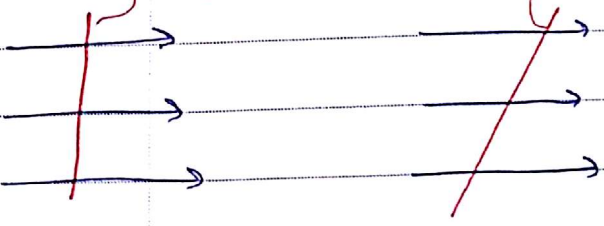



Same Φ
Same B

No. _____

$$\mu = \mu_r \mu_0 \rightarrow \text{free space permeability}$$

↳ relative permeability
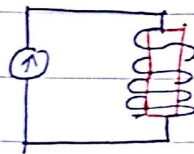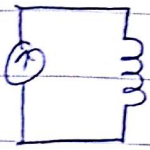
$$\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$$



$\mu_r = 2000$ (for iron)

$$H = 100 \frac{\text{A}\cdot\text{turn}}{\text{m}} \Rightarrow H \text{ is the same}$$

$$B = \mu_0 H$$

$$B = 2000 \mu_0 H$$


For Ferro $\mu_r = (2000 - 6000)$

For non-magnetic $\mu_r = 1$


* Faradys law :-

IF a flux passes through a turn of a coil of in a wire, voltage will be induced in that coil directly propotional to the rate of change of the flux.


$$e_{\text{ind}} = - \frac{d\phi}{dt}$$

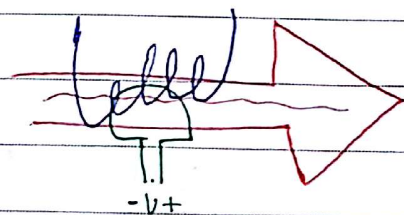

$$V = - \frac{d\phi}{dt}$$

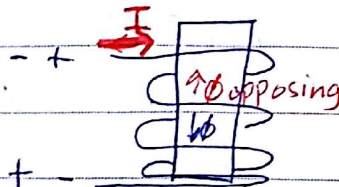

$$e_{\text{ind}} = -N \frac{d\phi}{dt}$$

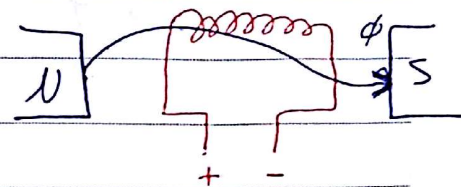

— since the polarity is figured out using right hand rule, the minus sign is sometimes omitted

6/6/2017

Faraday's Law

Transformer

$$V = -N \frac{d\phi}{dt}$$

$$\bar{\phi} = \bar{\phi}_s \cos \omega t$$


$$V = +N \bar{\phi}_s \omega \sin \omega t \quad \phi_s = B_p A$$

$$V = 2\pi N B_p A f \sin \omega t$$

$$V_{rms} = \frac{2.828}{\sqrt{2}} N f A B_p$$


$$V_{rms} = 4.44 N f A B_p \text{ peak}$$

flux linkage equation

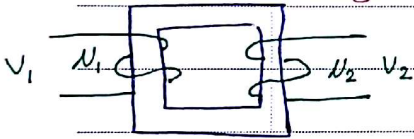

generator

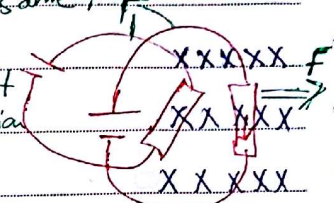they both have the same F but different direction



Flux density $F \times B$

Flux density $F \times I$

$$F = (I \times B) l$$


length \downarrow current \downarrow

$$= I B \sin \theta \quad (W/m)$$


generator

$$F = I B L \sin \theta \quad (N)$$


\downarrow
length of the wire

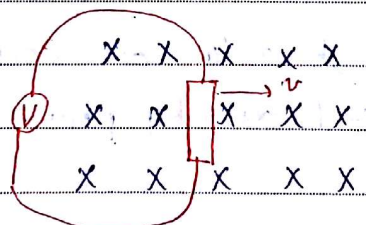

$$e_{ind} = (v \times B) \cdot l$$

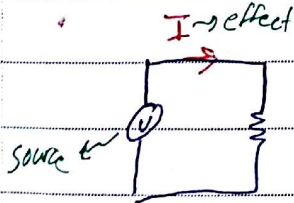

m.m.f \equiv magneto motive force

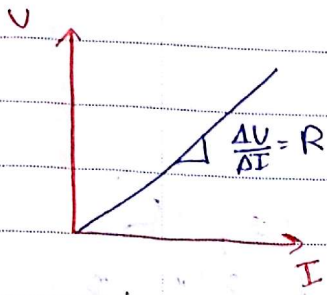

$$\frac{\Delta \Phi}{\Delta I} = R \Rightarrow R \equiv \text{reluctance}$$

$$F = \text{mmf} = NI \quad [\text{A} \cdot \text{turns}]$$

$$H = \frac{NI}{L} = \frac{F}{L}$$


$$B = \mu H = \frac{\mu F}{L}$$

$$\Phi = BA = \mu HA = \mu \frac{NI}{L} A = \frac{\mu F A}{L} = \frac{F}{(L/\mu A)} = \frac{F}{R}$$

$$R = \frac{l}{\mu A}$$

Reluctance \equiv measure of the opposition the magnetic circuit offer to flux

(\pm)

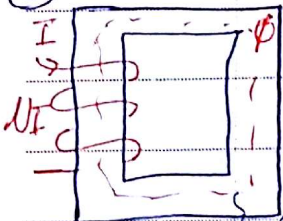


$\mu_{r1} = 2000 \rightarrow R \uparrow$ (bigger)

$\mu_{r2} = 6000 \rightarrow R \downarrow$ (smaller)

$$\downarrow \Phi = \frac{F}{R \uparrow}$$

Magnetic circuit

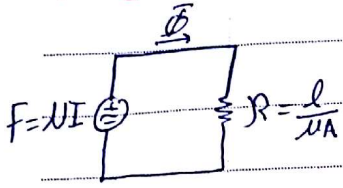


$H_1 \neq H_2$

$\Phi_1 = \Phi_2 \Rightarrow$

$B_1 = B_2$

$A_1 = A_2$

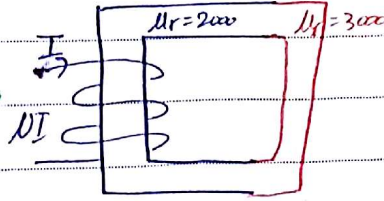



$F = \Phi [R]$

$F = \Phi [R_1 + R_2]$

$\frac{l_1}{\mu_r \mu_0 A} \quad \frac{l_2}{\mu_r \mu_0 A}$



Reluctances in series $\Rightarrow R_{eq} = R_1 + R_2$

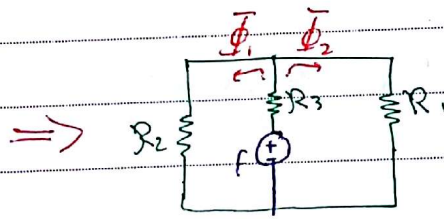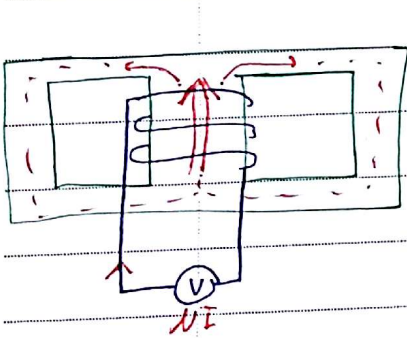Reluctances in parallel $\Rightarrow \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$



$\Phi = \Phi_1 + \Phi_2$

* Core with the Air gap

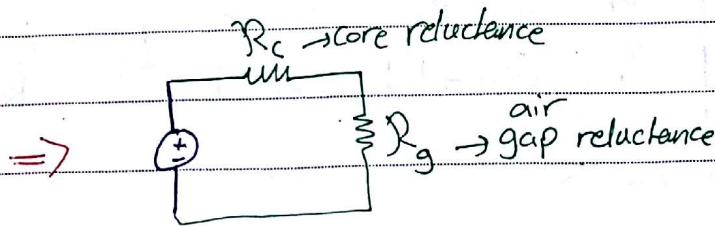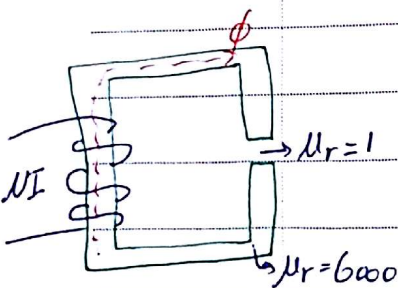


$R_c = \frac{l_c}{\mu_r \mu_0 A_c}$

$R_g = \frac{l_g}{\mu_0 A_g}$

$\Phi_c = \Phi_g \quad B_c = B_g \quad H_c \neq H_g$

7/6/2017 ☺

Example 1.2 in the book :-

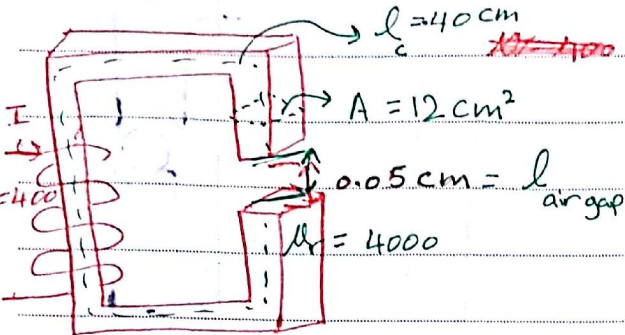

Fringing: عند ما يتم ك Φ في core

ويستقل δ air gap

انتماء في خطوط المجال عند الأركان



في مسارات اللروب غير ذات

في (A) air gap


→ fringing

التي تمر فيها خطوط المجال

Assume fringing in air gap increases it's cross sectional area by 5%.

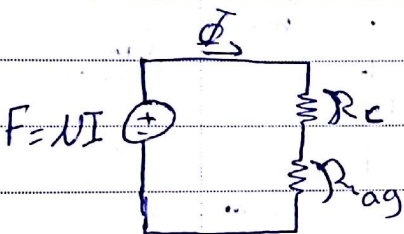(1) Find the total reluctance of the system

- Convert it to it's equivalent electric circuit.



$$R_c = \frac{l_c}{\mu A_c} = \frac{40 \times 10^{-2}}{4000 \times 4\pi \times 10^{-7} \times 12 \times 10^{-4}}$$

$$R_c = 66300 \text{ A.turns/wb} \rightarrow R = \frac{F}{\Phi} = \frac{NI}{\Phi} \text{ A.turns/wb}$$

$$R_{ag} = \frac{l_{ag}}{\mu_0 A_{ag}} = \frac{0.05 \times 10^{-2}}{4\pi \times 10^{-7} \times 12 \times 10^{-4} \times 1.05} = 31600 \text{ A.turns/wb}$$

$$R_{eq} = R_c + R_{ag} = 382300 \text{ A.turns/wb}$$

(2) The current required to produce a flux density of 0.5 Tesla in the gap.

$$F = NI = \Phi R$$

$$I = \frac{\Phi R}{N} = \frac{B A R}{N} = \frac{0.5 (12 \times 10^{-4} \times 1.05) \times 382300}{400} = 0.602 \text{ A}$$


Example 1.3 :-

$$l_{\text{f}} = 50 \text{ cm} \quad A_{\text{f}} = 12 \text{ cm}^2 \quad \mu_{\text{r}\text{f}} = 2000$$

$$I = 1 \text{ A} \quad A_{\text{R}} = 12 \text{ cm}^2 \quad \mu_{\text{r}\text{R}} = 2000$$

$$l_{\text{ag}} = 0.05 \text{ cm} \quad A_{\text{ag}} = 14 \text{ cm}^2$$

* note that there is two air gaps

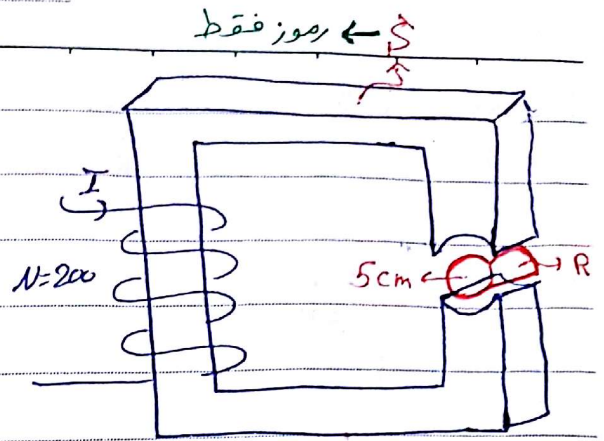

Find flux density ^B in the air gap!

Solution :-

$$F = \Phi R_{\text{eq}} \quad \text{Find } R_{\text{eq}}$$

$$R_{\text{f}} = \frac{l_{\text{f}}}{\mu A_{\text{f}}} = \frac{50 \times 10^{-2}}{2000 \times 4\pi \times 10^{-7} \times 12 \times 10^{-4} \times \pi} = 166000 \text{ A.turns/wb}$$


$$R_{\text{R}} = \frac{5 \times 10^{-2}}{2000 \times 4\pi \times 10^{-7} \times 12 \times 10^{-4}} = 16600 \text{ A.turns/wb}$$





$$R_{\text{ag}_1} = \frac{0.05 \times 10^{-2}}{4\pi \times 10^{-7} \times 14 \times 10^{-4}} = 284000 \text{ A.turns/wb} = R_{\text{ag}_2}$$

$$R_{\text{eq}} = R_{\text{f}} + R_{\text{R}} + 2R_{\text{ag}_1} = 751000 \text{ A.turns/wb}$$

$$\Phi = \frac{F}{R_{\text{eq}}} = \frac{NI}{R_{\text{eq}}} = \frac{200 \times 1}{751000} = 2.66 \times 10^{-4} \text{ wb}$$
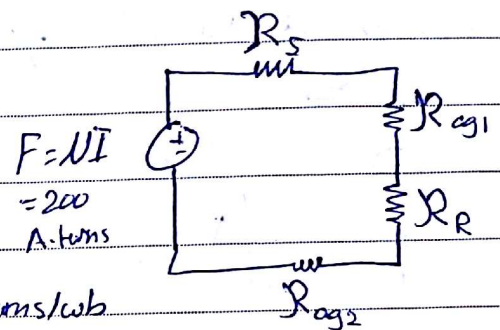
$$B_{\text{ag}} = \frac{\Phi}{A_{\text{ag}}} = \frac{2.66 \times 10^{-4}}{14 \times 10^{-4}} = 0.19 \text{ T}$$




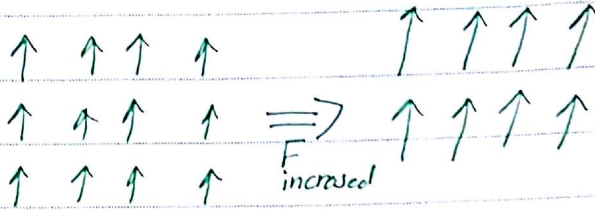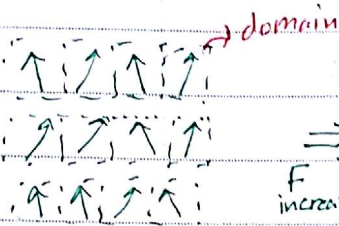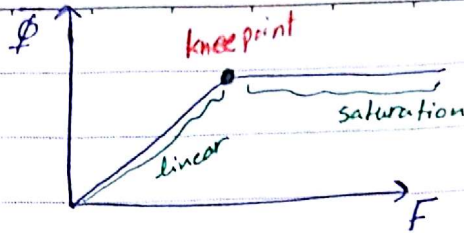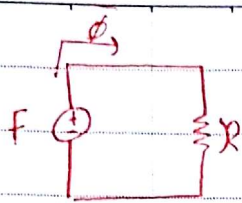





عند كبر ما لنا نوتر
زيادة F في ال domain
كأننا نستطيع تمارز
الحدود الطبقاتية للفزل
الإلكتروني

$\Phi = BA$
 $F = NI = Hl$

$\Phi \propto B$
 $F \propto H$

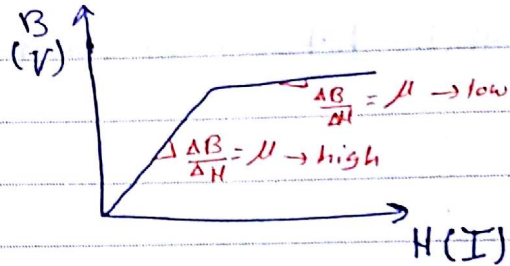


slope μ , μ is not constant

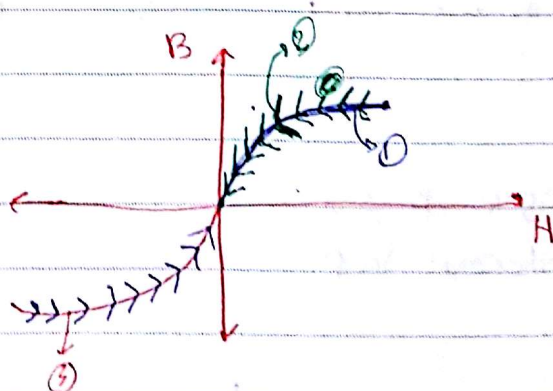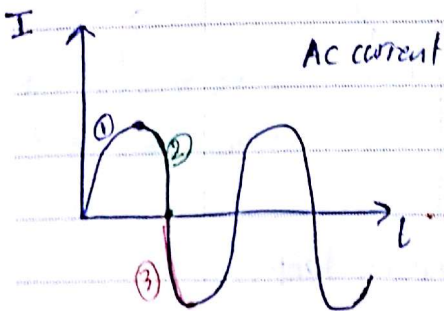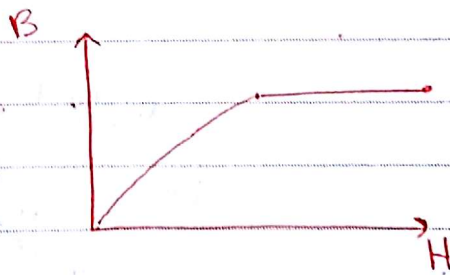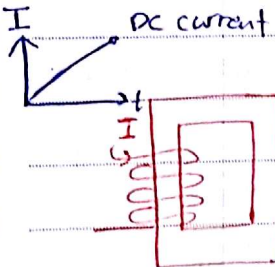


but actually this is not
the case, the real case
will be shown in next pages.

8/6/2017

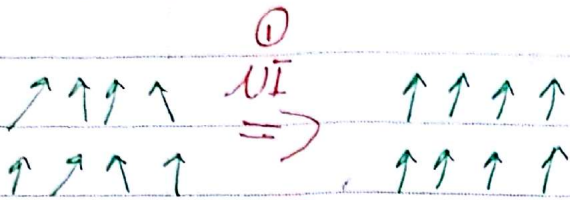

①

NI




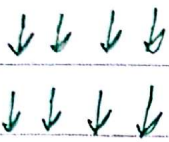


②

NI

$NI(2) > NI(1)$

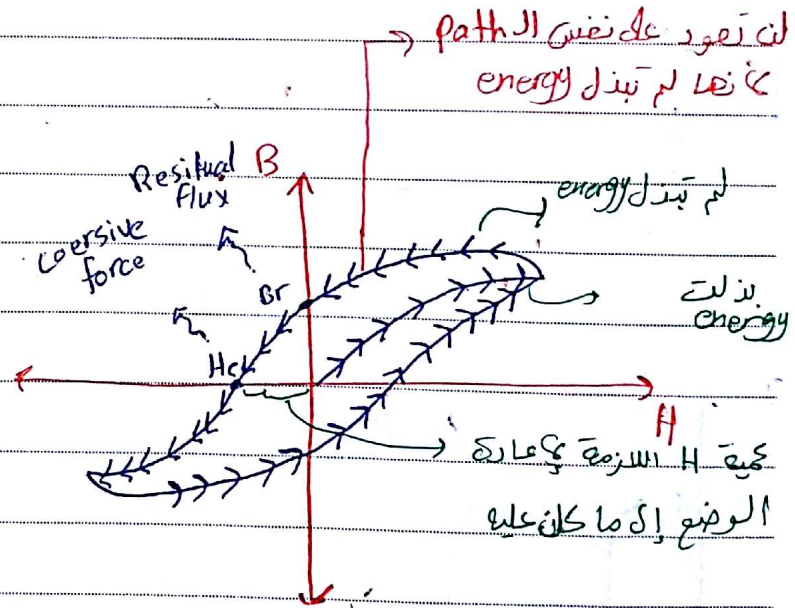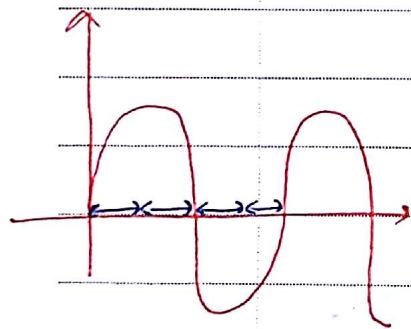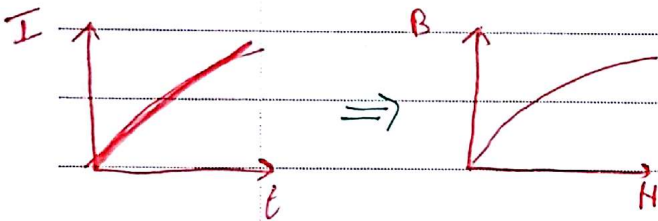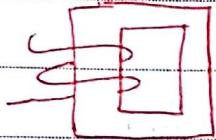
* Magnetic behavior of ferromagnetic materials :-




* في كل cycle يستهلك Hysteresis loop

"Hysteresis loop"


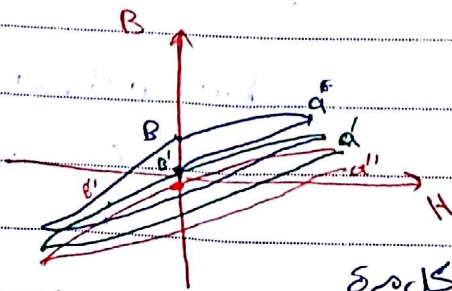
this is the real case but they are hysteresis loops and we only consider one of them.




لكن "B" تقل في كل مرة نفس مقدار التيار

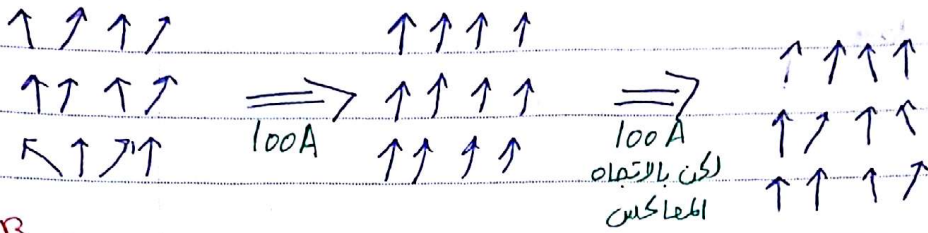

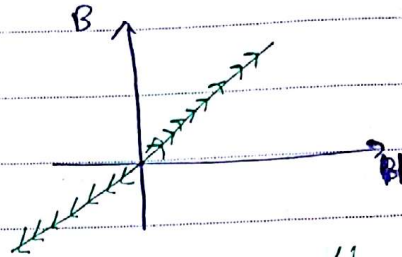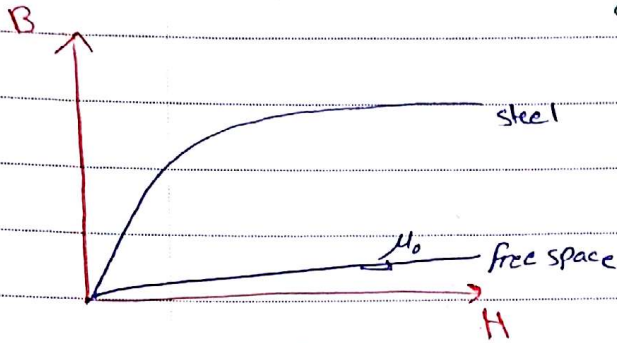it didn't return exactly to its original.



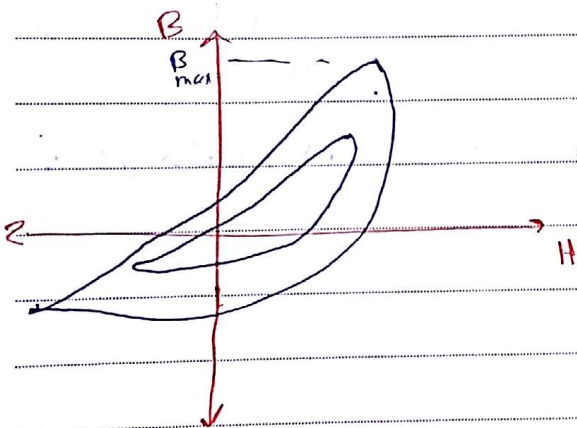"there is No Hysteresis loop in free space"



تأثير الذاكرة
 * Area of the loop of Hysteresis losses
 * $\uparrow B_{max} \rightarrow \uparrow Area \rightarrow \uparrow losses$

* The amount of flux in any core depends on :-

- 1) The current applied
- 2) The previous history of the flux. "Core الذاكرة Flux الذاكرة"

* The dependence on the preceeding Flux and failure to retrace same flux path is called (Hysteresis)

Hysteresis loss is the energy required to accomplish the reorientation of domains during each cycle of AC current applied to the core.

loss of Area of $B \times H$
 الطاقة المفقودة

losses الذاكرة
 heat.

Power loss in the loop



$$P_n = k_n f \times B_{max}^n$$

$$1.5 \leq n \leq 2.5$$

$n \equiv$ Steinmetz exponent

k_n : depends on the material

f : frequency

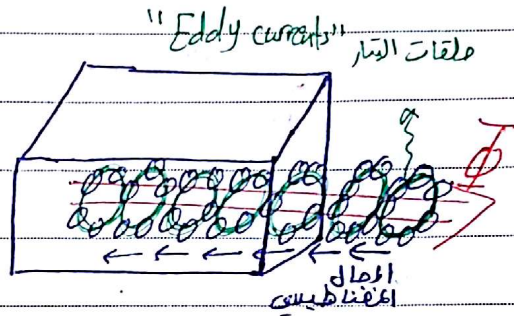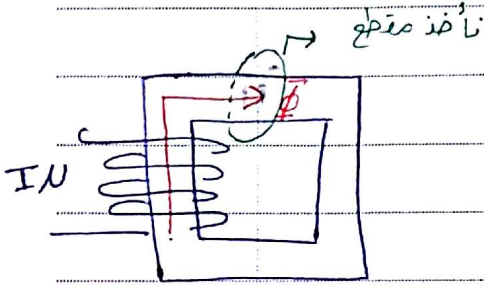

$$e = -N \frac{d\Phi}{dt}$$

* ستكون e في ال core حسب مبادئها الكهربية لها يؤدي ان ظهور تيار عاكس في دوائها **"Eddy current"** .

* كل حلقة من التيار تتولد مجال مغناطيسي بالاتجاه العكس في ال سرعة .

Solutions (for Eddy currents) :-

① Reduce the core electric resistance

→ add silicon
 $\downarrow R \Rightarrow \downarrow I^2 R$



② lamination



$$P_e = k_e (f t B_{max})^2$$

\downarrow material constant \downarrow freq \downarrow thickness


Eddy current losses is lower here.

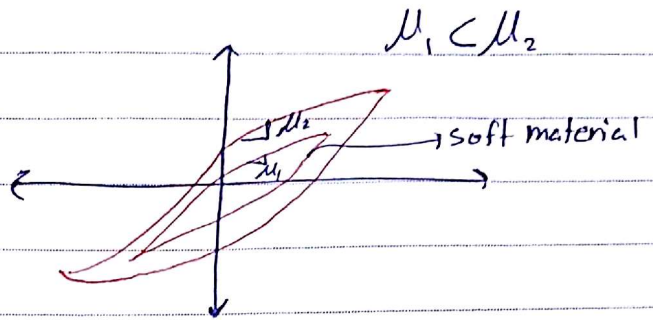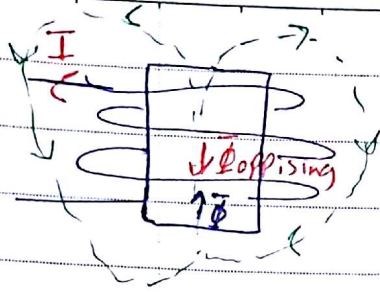

* Self Inductance :-

$$V = e_{ind} = -N \frac{d\Phi}{dt}$$


$$V = L \frac{di}{dt}$$

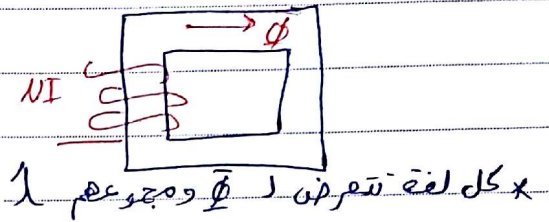

$$\lambda = N\Phi$$

↳ linkage flux

$$\lambda \propto I$$

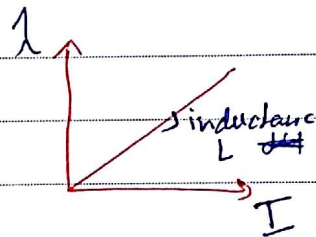


$$\lambda = LI$$

$$L = \frac{\lambda}{I} = \frac{N\Phi}{I} = \frac{NBA}{I} = \frac{NM\mu HA}{I} = \frac{NM\mu N^2 I^2 A}{LI} = \frac{N^2}{L\mu A} = \frac{N^2}{R}$$



⇒

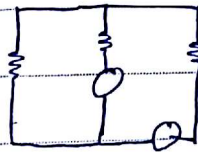

eqn. electric circuit

Suggested problems :-

- 1.1, 1.5, 1.6, 1.7, 1.8, 1.9, 1.12, 1.13, 1.14, 1.15


Chapman 5th edition

Chapter 2

* No. Transformers *

11/6/2017

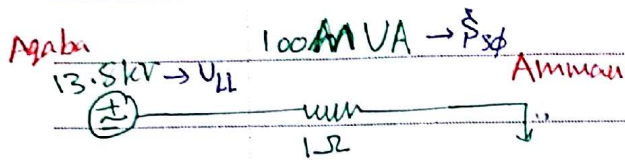
Transformer is a device that converts electric AC power from one voltage to another voltage at the same frequency.



$$I = \frac{100 \text{ MVA}}{\sqrt{3} \times 13.8 \text{ kV}} = 4.18 \text{ kA}$$


$$V_{\text{load}} = \frac{13.8}{\sqrt{3}} - 4.18 = 3.86 \text{ kV}$$
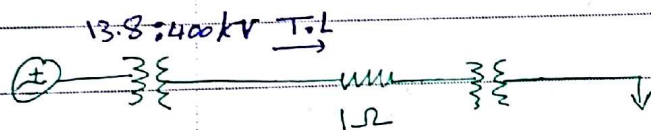
$$P_{\text{losses}} = (4.18)^2 \times 10^6 \times 1 \text{ W}$$




$$I = \frac{100 \text{ MVA}}{\sqrt{3} \times 400 \text{ kV}} = 144.3 \text{ A}$$
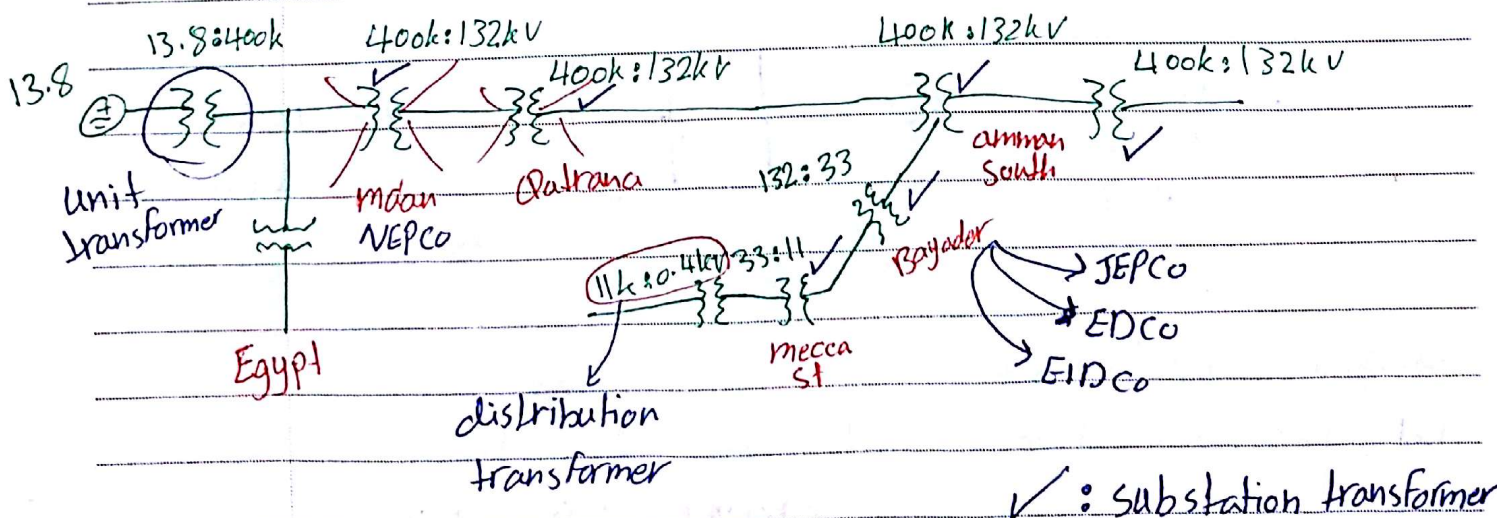
$$P_{\text{losses}} = (144.3)^2 \times 1 \text{ W}, \quad V_{\text{load}} = \frac{13.8}{\sqrt{3}} - 144.3$$



0.4 kV \rightarrow line to line Voltage = 220 Phase Voltage


Primary winding

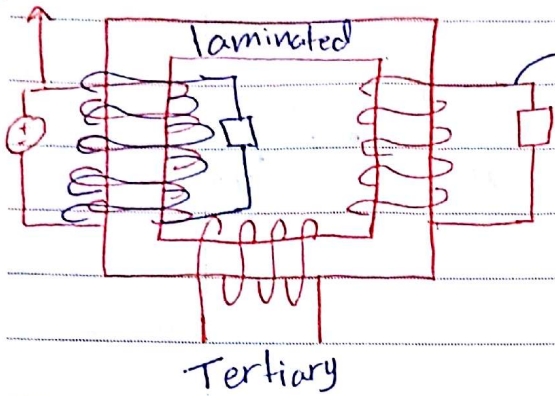


(We can put the secondary above the primary).

As long they are Isolated.

Transformer construction 8-

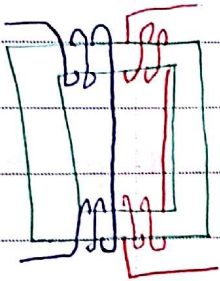

"Core type"

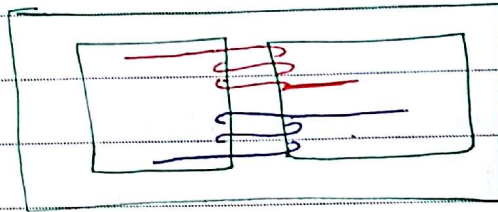

"Shell type"

physics of the design 3-

- voltage levels
- losses
- material


pri & sec

→ They are wrapped on top of each other
 → low-voltage side is wrapped on the core and the high-voltage side is wrapped on top of it. why;

(1) less leakage current.

(2) isolate the high voltage from the core (because spark can happen).

- Ideal Transformer :-

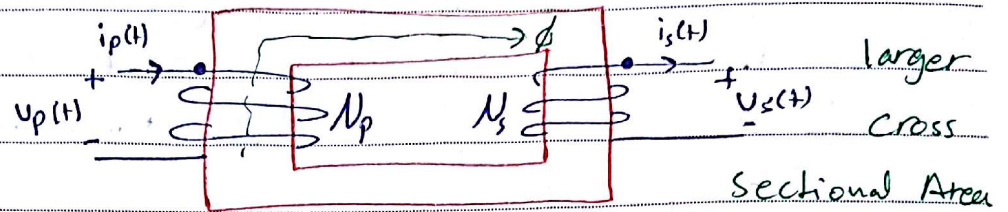

$$\frac{V_p(t)}{V_s(t)} = \frac{N_p}{N_s} = a$$

larger cross sectional Area
because it needs to hold large current

$$\frac{i_s(t)}{i_p(t)} = \frac{N_p}{N_s} = a$$

$$\frac{V_p}{V_s} = a, \quad \frac{I_s}{I_p} = a$$

⇒ There is No phase shift between the primary voltage and Secondary voltage, same for current.

⇒ The power supplied by the primary : $P_{in} = V_p I_p \cos \theta_p$

⇒ The output power on the secondary : $P_{out} = V_s I_s \cos \theta_s$

$$\theta_p = \theta_s = \theta$$

* load determines θ , always.

12/16/2017

$$P_p = V_p I_p \cos \theta_p$$

$$P_s = V_s I_s \cos \theta_s$$

$$\theta_s = \theta_p = \theta \text{ (PF angle)}$$


$$P_s = P_p$$

$$Q_s = Q_p = VI \sin \theta$$

$$= V_s I_s \sin \theta_s$$

$$= V_p I_p \sin \theta_p$$


$$S_s = S_p = V_p I_p^* = V_s I_s^*$$

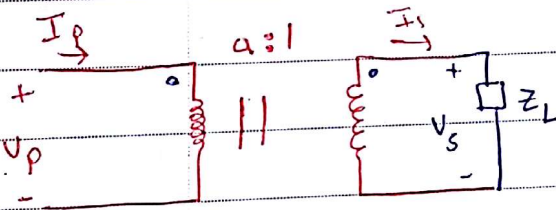


$$Z_L = \frac{V_s}{I_s} \rightarrow \text{load}$$

$$Z'_L = \frac{V_p}{I_p} = \frac{a V_s}{I_s / a} = a^2 \frac{V_s}{I_s} = \boxed{a^2 Z_L}$$

as seen by the source

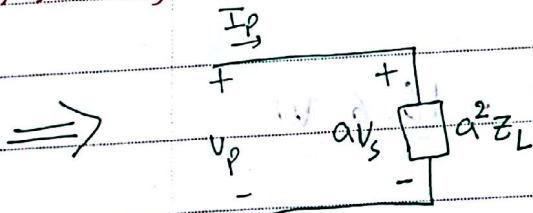


Transformer Application in ckt's (2) :-

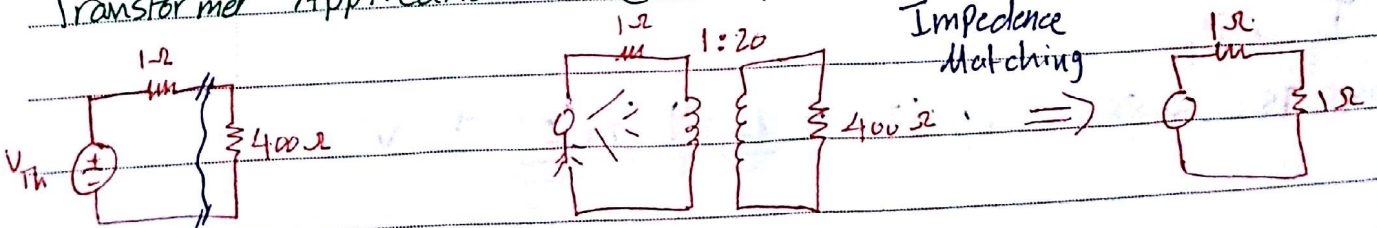

Example 2.1 9-


⇒ Find V_L & P_{TL} losses

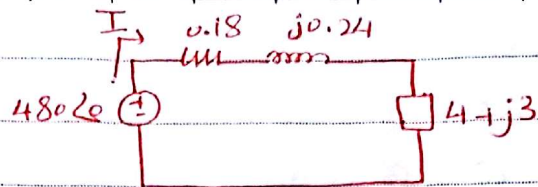


$$I = \frac{480 \angle 0^\circ}{4.18 + j3.24} = 90.8 \angle -37.8^\circ \text{ A}$$

$$V_L = I(4 + j3) = 454 \angle -0.9^\circ$$
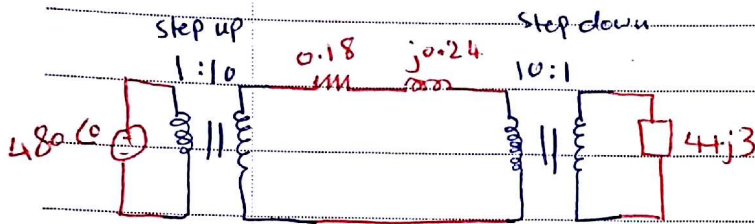
$$P_{TL \text{ losses}} = (90.8)^2 \times 0.18 = 14.84 \text{ W}$$



→ Reflection

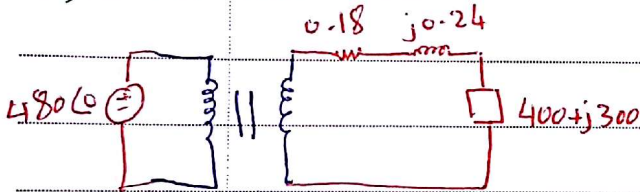

$$480 \angle 0^\circ \text{ V} \text{ is connected to a series combination of } 400.18 \times \frac{1}{100} \text{ and } j300.24 \times \frac{1}{100} \text{ } \Rightarrow 5.003 \angle 36.88^\circ$$

$$I_G = \frac{480}{5.003 \angle 36.88^\circ} = 95.95 \angle -36.88^\circ$$


$$P_{TL \text{ losses}} = (0.18) \left(\frac{I_G}{a} \right)^2 = 0.18 (9.595)^2 = 16.6 \text{ W}$$

$$\Rightarrow I_{T.L} = I_G \times \frac{1}{10} = 9.595 \angle -36.88^\circ \text{ A}$$

$$V_L = I_L \times Z_L$$

$$= (9.595 \angle -36.88^\circ) \times (4 + j3) = 479.7 \angle -0.01^\circ \text{ V}$$

Real Transformer 8-

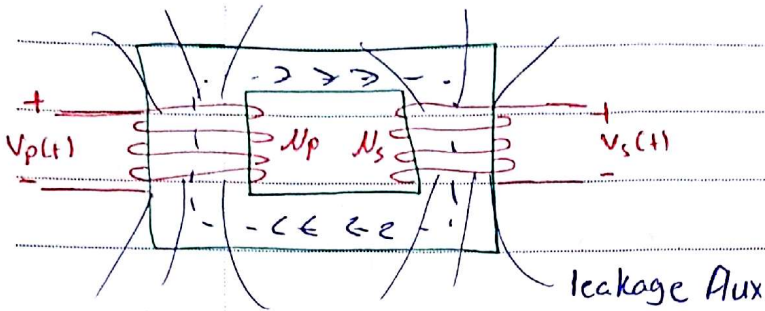

$$\lambda = \sum_{l=1}^N \bar{\Phi}_l, \quad e_{\text{ind}} = \frac{d\lambda}{dt}$$

$$\bar{\Phi} = \frac{\lambda}{N}, \quad e_{\text{ind}} = N \frac{d\bar{\Phi}}{dt}$$

$$\bar{\Phi} = \frac{1}{N} \int v(t) dt$$

$$= \frac{1}{N_p} \int v_p(t) dt = \frac{1}{N_s} \int v_s(t) dt$$

$$\bar{\Phi}_p = \bar{\Phi}_m + \bar{\Phi}_{Lp}, \quad \bar{\Phi}_s = \bar{\Phi}_m + \bar{\Phi}_{Ls}$$

$$\Rightarrow v_p(t) = N_p \times \frac{d\bar{\Phi}_p}{dt} \\ = N_p \left[\frac{d\bar{\Phi}_m}{dt} + \frac{d\bar{\Phi}_{Lp}}{dt} \right]$$

$$= N_p \frac{d\bar{\Phi}_m}{dt} + N_p \frac{d\bar{\Phi}_{Lp}}{dt}$$

$$= e_p(t) + e_{Lp}(t)$$

$$\Rightarrow v_s(t) = N_s \times \frac{d\bar{\Phi}_s}{dt} \\ = N_s \frac{d\bar{\Phi}_m}{dt} + N_s \frac{d\bar{\Phi}_{Ls}}{dt}$$

$$= e_s(t) + e_{Ls}(t)$$

$$e_s(t) = N_s \frac{d\Phi_m}{dt}$$

$$e_p(t) = N_p \frac{d\Phi_m}{dt}$$

$$\boxed{\frac{e_p(t)}{e_s(t)} = \frac{N_p}{N_s} \neq \frac{V_p}{V_s} \text{ (because of } e_{sL} \text{ and } e_{pL}\text{)}}$$


⇒ As $\mu \uparrow \uparrow$ and for well-designed transformers

$$\Phi_m \gg \Phi_{LP} \quad , \quad \Phi_m \gg \Phi_{LS}$$

$$\boxed{\frac{e_p(t)}{e_s(t)} \cong \frac{V_p(t)}{V_s(t)} \cong a \text{ turns ratio}}$$

* leakage secondary depend on i_s and $V_s(t)$

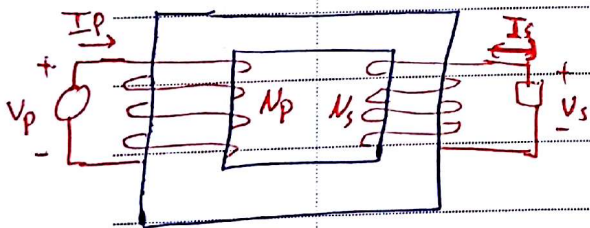The excitation current in a real transformers :-



$$\frac{V_p}{V_s} = a \quad \frac{I_s}{I_p} = a$$

⇒ At No load, $I_p \neq 0$

→ magnetizing flux I_m

→ to back up Hysteresis and eddy currents



$$I_p = I_s + I_{n.l}$$

$$\widetilde{I_e} \text{ (excitation current)} = I_m + I_{n.l}$$


$$I_e \rightarrow I_m$$


$I_e \rightarrow I_{n.l}$ hysteresis and eddy current losses backup

13/6/2017

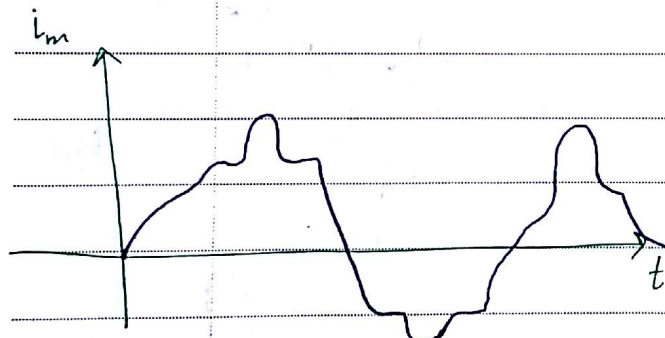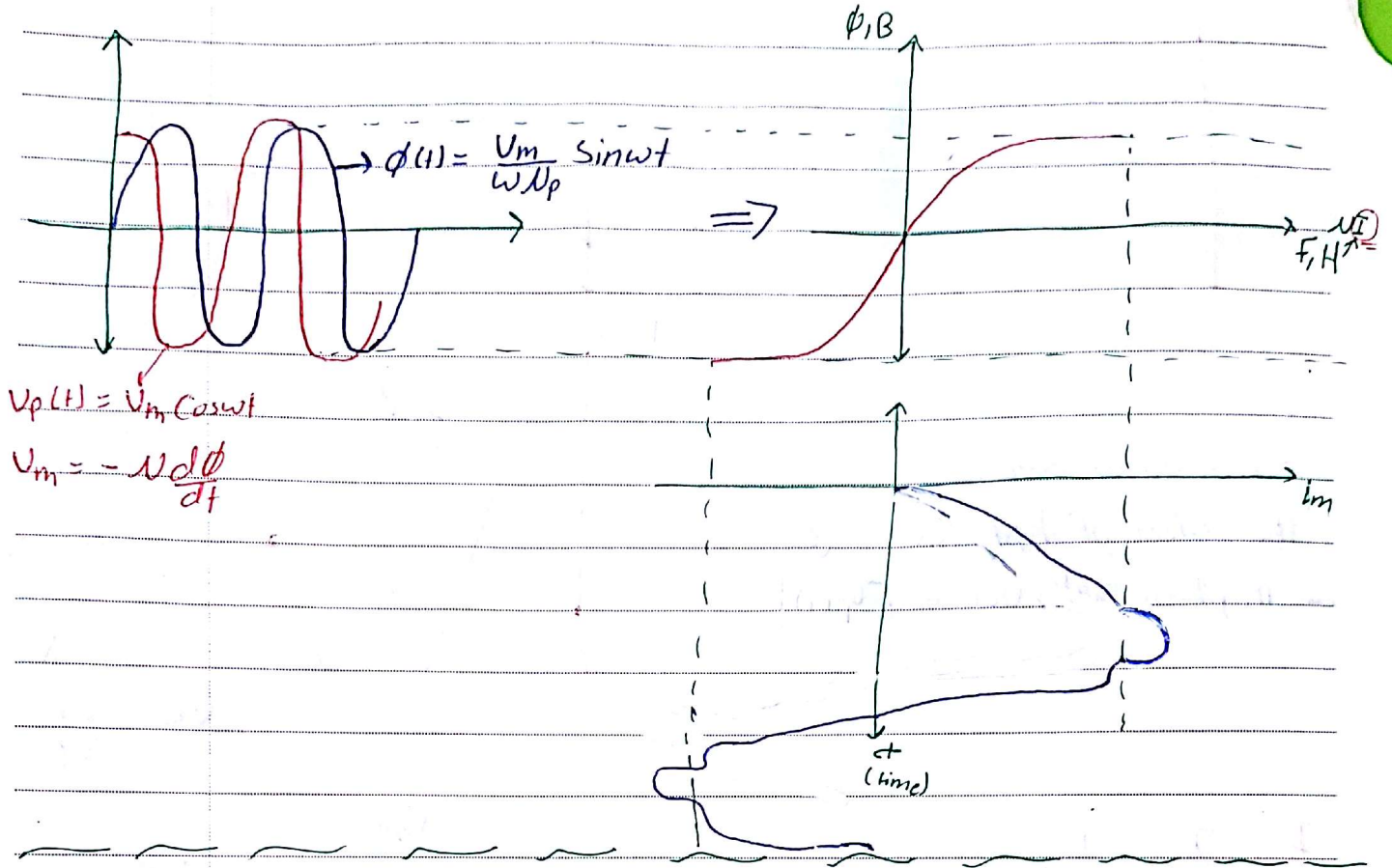

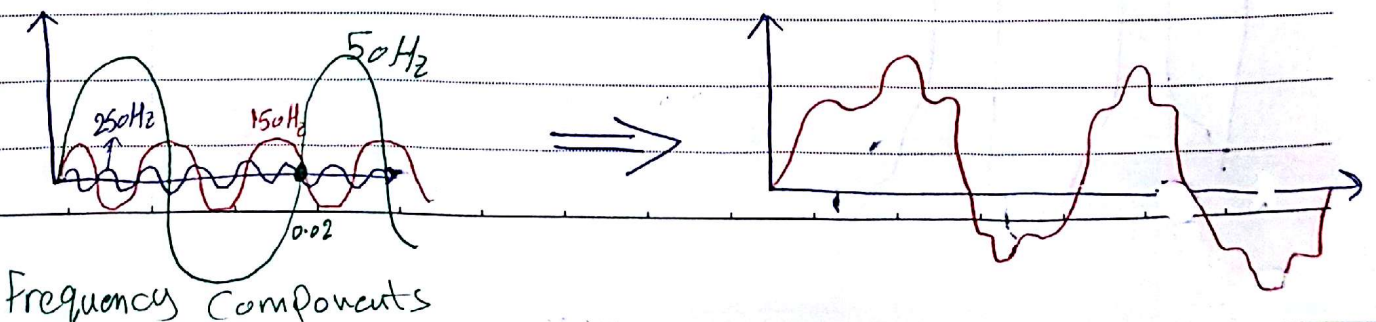- not sinusoidal, there are high frequency components because of saturation.
- when saturation is reached, small increase in flux requires large increasing in current
- I_m [it's fundamental component] lags the voltage by 90° .
- high frequency components of I_m may be large in saturation.








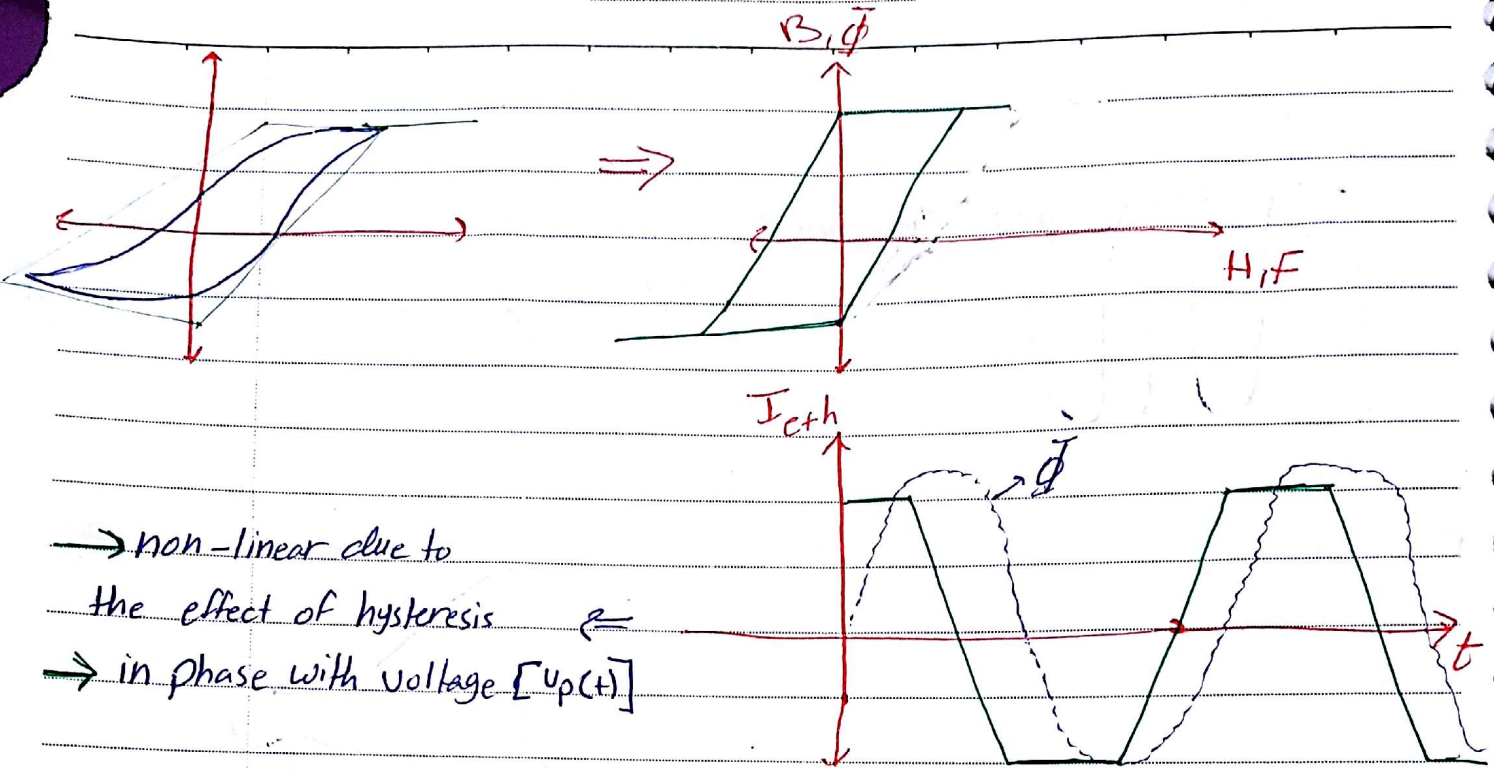

→ non-linear due to the effect of hysteresis
 → in phase with voltage $[u_p(t)]$


$$\nabla \times E = -\frac{\partial B}{\partial t}$$

$$I_c = I_m + I_{n+h}$$

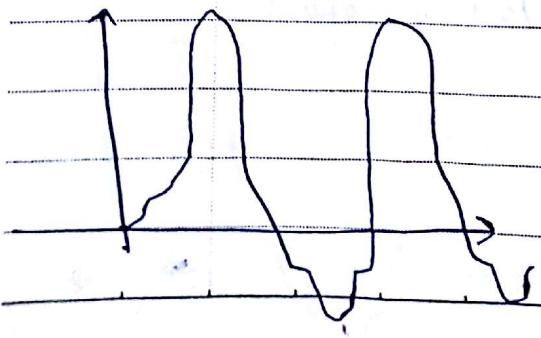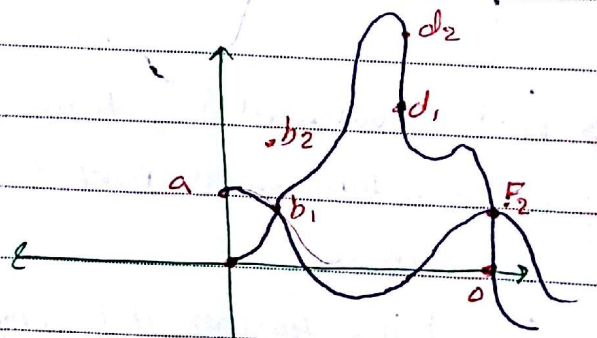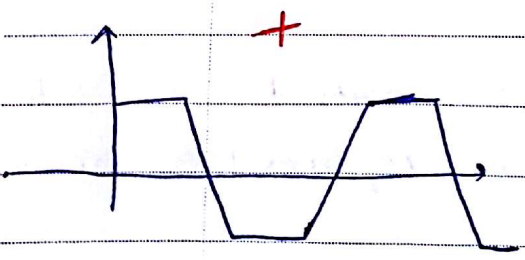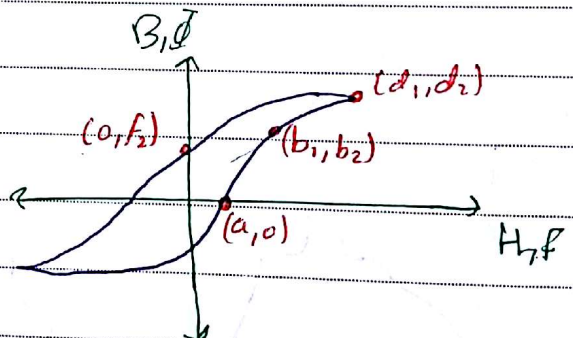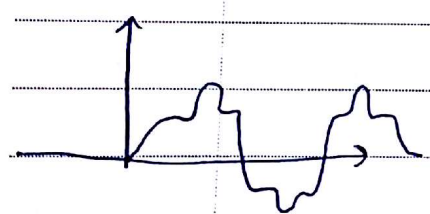

Real transformer :-
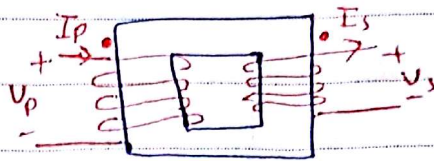
$$\frac{e_p(t)}{e_s(t)} \approx \frac{V_p(t)}{V_s(t)} \approx a$$



$$F_p = N_p I_p \quad F_s = N_s I_s$$


net flux in the core :-

$$F_{net} = N_p I_p - N_s I_s = R \phi$$

→ for a well-designed transformer that works in the linear region


$$R \approx 0 \Rightarrow F_{net} = N_p I_p - N_s I_s = 0$$
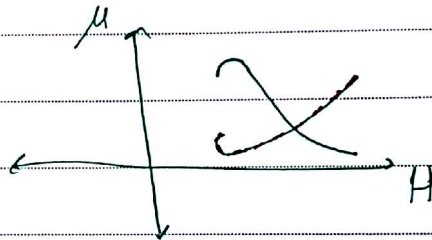
$$\frac{N_p}{N_s} \approx \frac{I_s}{I_p} \approx a$$




Ideal transformer :-

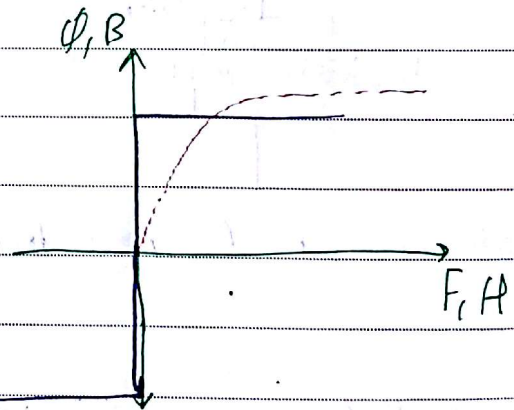- no core losses [no I_{mfe}].
- leakage flux is zero.
- the wires resistance is zero.
- the B-H curve is \Rightarrow



"Ideal"

"Real"

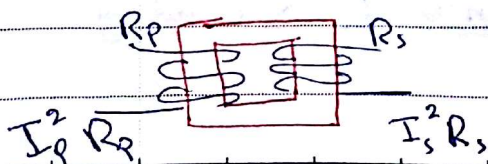


* We need a small value of (I) to get a high flux.
(constant flux)

→ full real transformer in the next page.

14/6/2017 ☺

*** Real transformer :-**

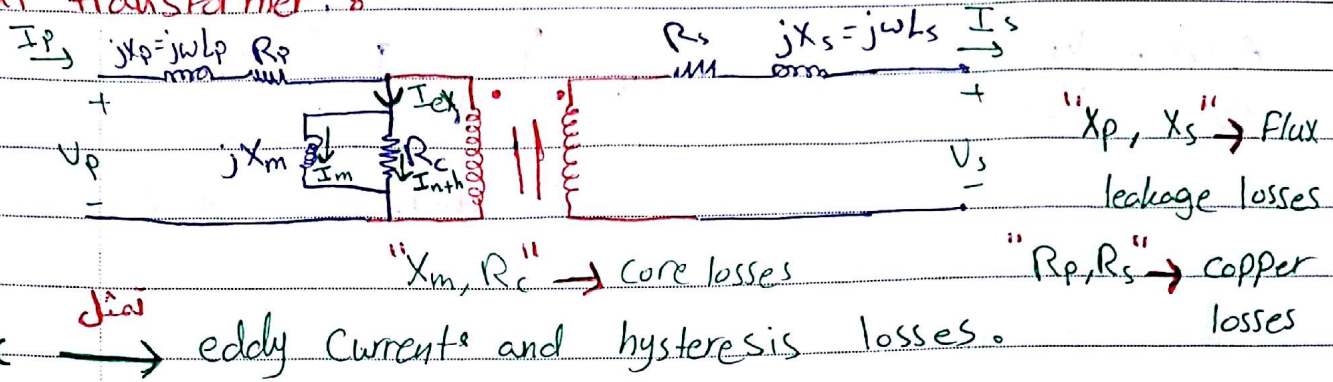


$$\Phi_p = \Phi_m + \Phi_{Lp}$$


$$e_{Lp}(t) = -N_p \frac{d\Phi_{Lp}}{dt} = -N_p \frac{d}{dt} \left(\frac{N_p I_p}{R} \right) = \left(\frac{N_p^2}{R} \right) \frac{di_p}{dt} = \boxed{L_p \frac{di_p}{dt}}$$

$$\Phi_p = \frac{N_p I_p}{R_p}$$


Same for Secondary

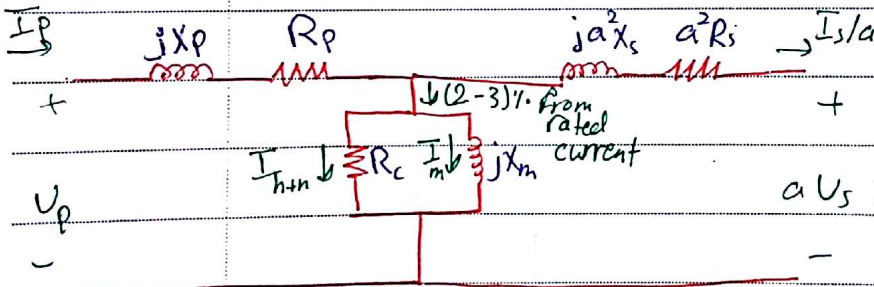

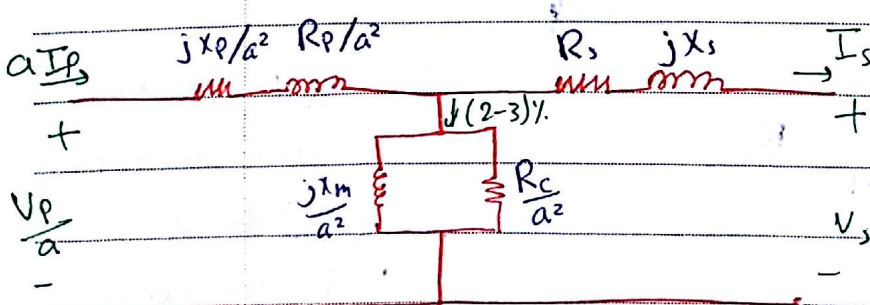equivalent circuit of a real transformer referred to primary.



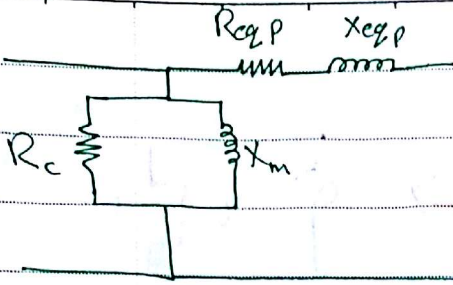
equivalent circuit of real transformer referred to secondary.



$$R_{eqP} = R_p + a^2 R_s$$

$$X_{eqP} = X_p + a^2 X_s$$



"referred to primary"

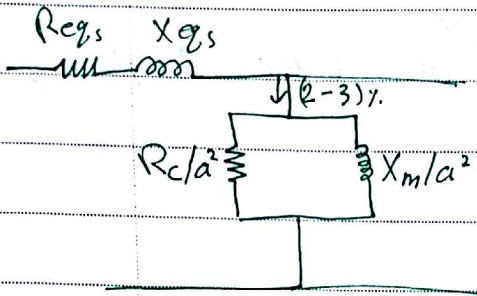

$$R_{eqS} = R_s + R_p/a^2$$

$$X_{eqS} = X_s + X_p/a^2$$

"referred to secondary"

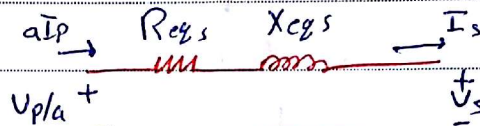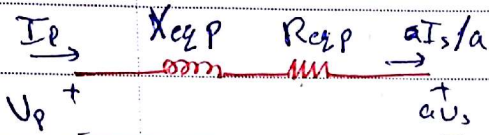

primary



* In the lab, you have a real transformer and you're required to find its equivalent circuit.

1] O.C test :- apply rated voltage at one side and keep the other side open.


2] Short.ckt test :- apply very small amount of voltage on one side and short ckt the other side.

O.C Ametre Voltmetre

S.C

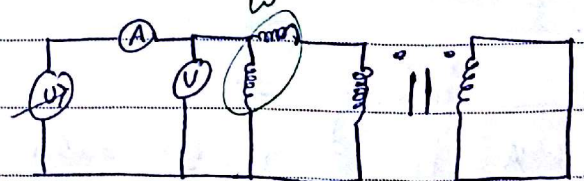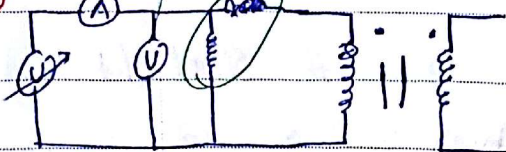

1] O.C test

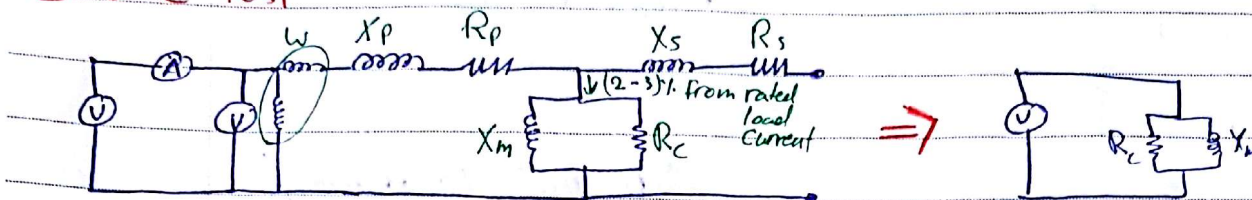

* X_p, R_p were neglected because they are ^{very} small values comparing with R_c, X_m

$$|Y_E| = \frac{I_{o.c}}{V_{o.c}} = |G_c - jB_m|$$


excitation admittance

Conductance = $\frac{1}{R_c}$

susceptance = $\frac{1}{X_m}$


$$\cos\theta = p.f = \frac{P_{o.c}}{V_{o.c} I_{o.c}} \implies \frac{V}{E} = \frac{I_{o.c}}{V_{o.c}} \angle -\theta$$

2] Short circuit test

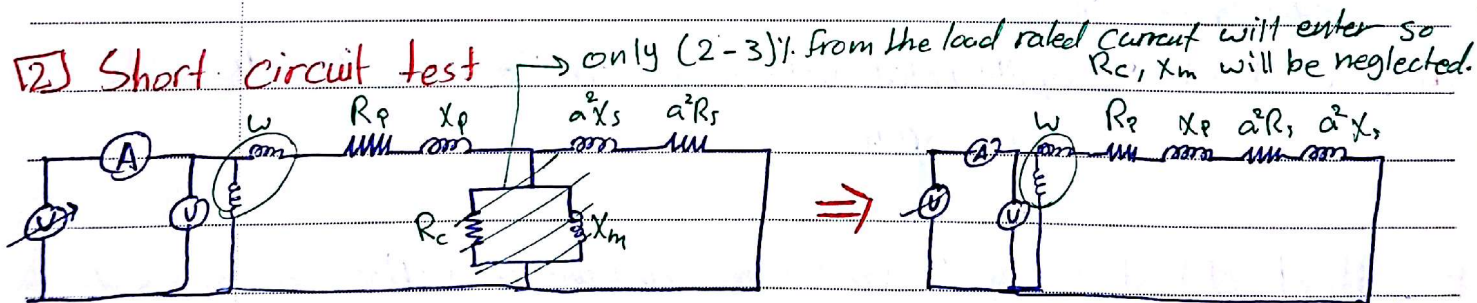

$$|Z_{SE}| = \frac{V_{s.c}}{I_{s.c}}, \quad p.f = \cos\theta = \frac{P_{s.c}}{V_{s.c} I_{s.c}}, \quad Z_{SE} = \frac{V_{s.c}}{I_{s.c}} \angle \theta$$

series elements

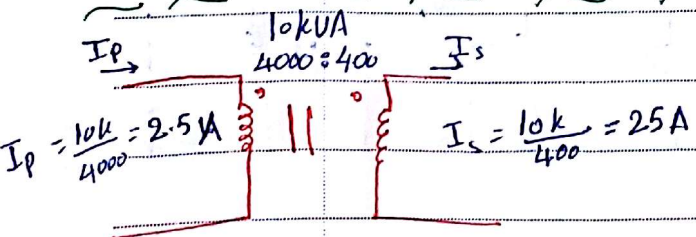

* preferred side for the short ckt test is the high voltage side.

* preferred side for the open ckt test is the low voltage side.

15/6/2017

ex 8- determine the eq ckt impedances referred to primary of a 20 kVA 8000/240 V, 60 Hz, the o.c and s.c test results &

Solution:-

1) o.c test \Rightarrow

$$Y = \frac{I_{o.c}}{V_{o.c}} \angle -\cos^{-1}\left(\frac{P_{o.c}}{I_{o.c} V_{o.c}}\right)$$

$$= \frac{7.133}{240} \angle -\cos^{-1}(0.234)$$

$$= \frac{0.00693}{G_c} - j \frac{0.02888}{B_m}$$


o.c [secondary]	s.c [primary]
$V_{oc} = 240 \text{ V}$	$V_{sc} = 489 \text{ V}$
$I_{oc} = 7.133 \text{ A}$	$I_{sc} = 2.5 \text{ A}$
$P_{oc} = 400 \text{ W}$	$P_{sc} = 240 \text{ W}$

$$R_c = \frac{1}{G_c} = \frac{1}{0.00693} = 144 \Omega, R_{c(pri)} = 144 \times a^2 = 159 \text{ k}\Omega$$

\Rightarrow referred to Secondary

$$X_m = \frac{1}{B_m} = \frac{1}{0.02888} = 34.63 \Omega$$

$$X_{m(pri)} = 38.3 \text{ k}\Omega$$

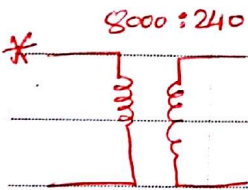



$$a = \frac{8000}{240}$$

2) s.c test \Rightarrow

$$Z_{SE} = \frac{V_{sc}}{I_{sc}} \angle \cos^{-1}\left(\frac{P_{sc}}{V_{sc} I_{sc}}\right)$$


$$= \frac{489}{2.5} \angle \cos^{-1}\left(\frac{240}{489 \times 2.5}\right)$$
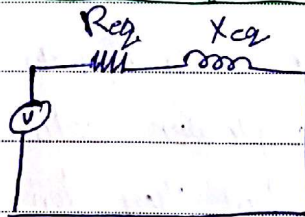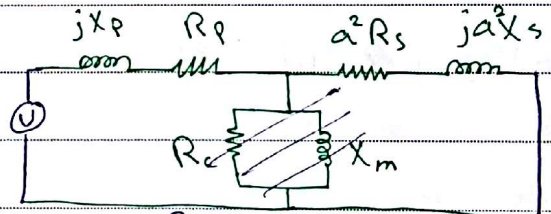
$$= \frac{38.4}{R_{eq}} + j \frac{192}{X_{eq}} \Omega$$




$$R_{eq} = 38.4 = R_p + a^2 R_s$$

$$X_{eq} = 192 = X_p + a^2 X_s$$

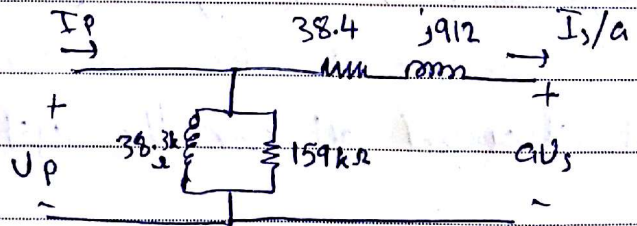

* End of first material *

Power base values :-

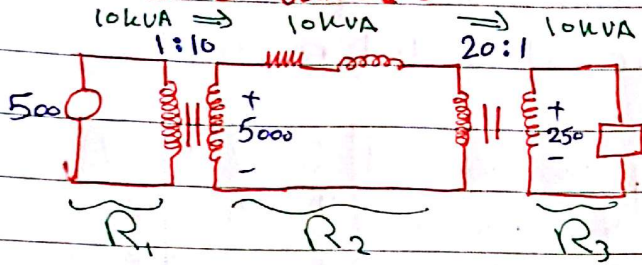

base Value \Rightarrow 600 5000 200 $\rightarrow V_{p.u} = \frac{250}{200} = 1.25 \text{ p.u}$

$V_{p.u} = \frac{V_{real}}{V_{base}} = \frac{500}{600} = 0.83 \text{ p.u}$ $\rightarrow V_{p.u} = 1 \text{ p.u}$

perunit

Quantity in p.u = $\frac{\text{actual quantity}}{\text{base value quantity}}$

base value power $\rightarrow 10 \text{ kVA}$


* In the perunit system the voltages, powers, currents are measured as decimal fractions of some base level instead of convention values :-

usually for each region in a system we choose a base voltage value and a base power value. Since the transformers change the voltage ~~value~~ level but they don't change the power level. The base voltage value of the system changes from region to another

[based on transformer's turn ratio] but, the base power isn't changed all over the system.

18/6/2017


ex 2.3 a-

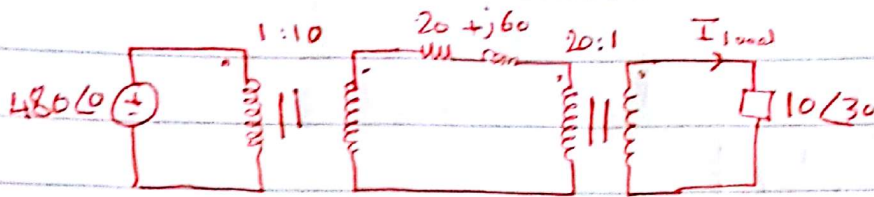

choose base voltage of generator side = 480 & base power 10 kVA

R_1	R_2	R_3
$V_{base} = 480 \text{ V}$	$V_{base} = \frac{1}{a} \times 480 = 4800 \text{ V}$	$V_{base} = 240 \text{ V}$
$S_{base} = 10 \text{ kVA}$	$S_{base} = 10 \text{ kVA}$	$S_{base} = 10 \text{ kVA}$
$I_{base} = \frac{S_{base}}{V_{base}} = 20.83 \text{ A}$	$I_b = 2.083 \text{ A}$	$I_{base} = 41.67 \text{ A}$
$Z_{base} = I_{base} \times V_{base} = 23.04 \Omega$	$Z_b = 2304 \Omega$	$Z_{base} = 5.76 \Omega$

eg ckt a- (perunit ckt)

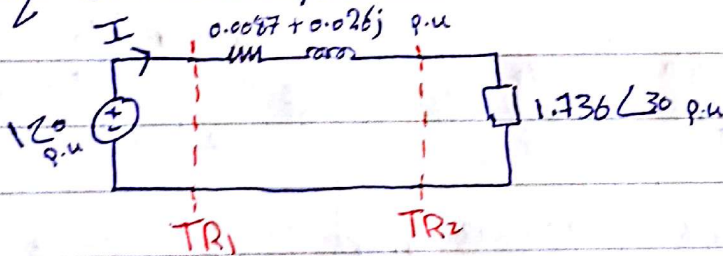

$$I = \frac{1 \angle 0}{1.736 \angle 30 + (0.0087 + j0.026j)} = 0.569 \angle -30.6$$

$$P_{load} (p.u) = I_{pu}^2 \times R_{pu} = 0.4867 \text{ pu}$$

$$P_{losses} (p.u) = I_{pu}^2 \times R_{T.L} = 0.00282 \text{ pu}$$

$$V_L (p.u) = Z_{pu} \times I_{pu} = 0.988 \angle -0.6 \text{ pu}$$

In watt a-

$$P_{load} = P_{pu} \times P_{base} = 4867 \text{ kW}$$

$$P_{loss} = 0.00282 \times 10 \text{ k} = 28.2 \text{ W}$$

$$V_L = 0.988 \times 240 = 237.12 \angle -0.6$$

Voltage Regulation :-

$$VR\% = \frac{|V_{s,ml}| - |V_{s,fl}|}{|V_{s,fl}|} \times 100\%$$

measure for
voltage drop

ex 8- $V_{s,ml} = 220$ $V_{s,fl} = 203$


$$VR = \frac{220 - 203}{203} \times 100\% = 8.37\%$$

* VR for different P.F \Rightarrow


lagging p.f

unity p.f


leading p.f

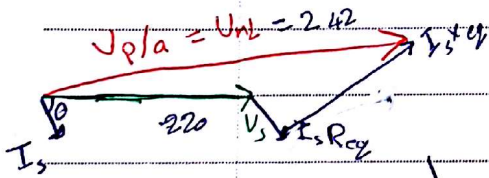


$$\frac{242 - 220}{220} = 10\%$$

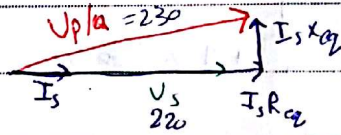

$$\frac{230 - 220}{220} = 4.54\%$$

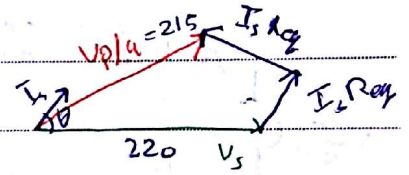

$$\frac{215 - 220}{220} = -2.27\%$$

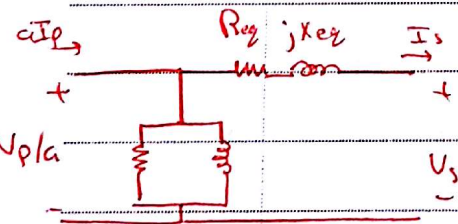

$$V_{p/a} = V_s + R_{eq} I_s + jX_{eq} I_s$$

$$V_s = V_{p/a} - R_{eq} I_s - jX_{eq} I_s$$

19/6/2017

No.

efficiency $\eta = \frac{P_{out}}{P_{in}} \times 100\%$

$$\eta = \frac{P_{out}}{P_{out} + P_{losses}} \times 100\%$$

$$\eta = \frac{P_{out}}{P_{out} + P_{Cu} + P_{core}} \times 100\%$$

\downarrow \downarrow
 $P_{s.c}$ $P_{o.c}$

$$\eta = \frac{V_s I_s \cos\theta_s}{V_s I_s \cos\theta_s + P_{Cu} + P_{core}} \times 100\%$$

ex 9- 15kVA, 2300/230V transformer was tested by o.c & s.c tests and the transformer data is obtained :-

(a) Find the equivalent ckt referred to primary and to secondary.

o.c (high volt side)	s.c (high volt side)
$V_{o.c} = 2300V$	$V_{s.c} = 47V$
$I_{o.c} = 0.21A$	$I_{s.c} = 6A$
$P_{o.c} = 50W$	$P_{s.c} = 160W$

$$Y_E = \frac{I_{o.c}}{V_{o.c}} \angle -\cos^{-1} \frac{P_{o.c}}{I_{o.c} V_{o.c}} = \frac{0.21}{2300} \angle -\cos^{-1} \left(\frac{50}{0.21 \times 2300} \right)$$

$$= 0.0000095 - j0.0000908$$

$R_c = 103k\Omega$ $X_m = 11k\Omega$


$$Z_{SE} = \frac{V_{s.c}}{I_{s.c}} \angle \cos^{-1} \left(\frac{P_{s.c}}{I_{s.c} V_{s.c}} \right)$$

$$= \frac{47}{6} \angle \cos^{-1} \frac{60}{47 \times 6} = 4.45 + j6.45 \Omega$$


$R_{eq} = 4.45\Omega$ $X_{eq} = j6.45\Omega$

the eq ckt referred to primary :-

$$\frac{2300}{230} = a = 10$$

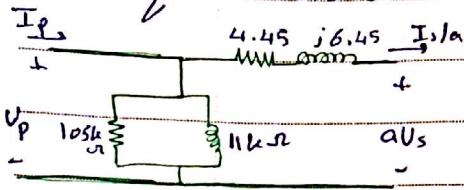

the eq ckt referred to secondary :-

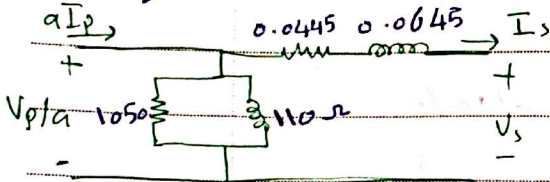

Find voltage regulation at rated load with pf = 0.8 lagging, pf = 1, pf = 0.8 leading

0.8 lagging

pf = 1

0.8 leading

$$I_{\text{rated}} = \frac{S_{\text{rated}}}{V_s} = \frac{15000}{230} = 65.2 \text{ A}$$

$$I_{\text{rated}} = 65.2$$

$$I_{\text{rated}} = 65.2$$

$$I_s = 65.2 \angle 0^\circ$$

$$I_s = 65.2 \angle 36.87^\circ$$

$$V_{p/a} = 230 + 65.2 \angle 0^\circ (0.0445 + j0.0645) = 232.94 \angle 1.04^\circ$$

$$V_{p/a} = 230 \angle 0^\circ + 65.2 \angle 36.87^\circ (0.0445 + j0.0645) = 229.85 \angle 1.27^\circ$$

$$I_s = 65.2 \angle -36.87^\circ$$




$$\frac{V_p}{a} = 230 + (0.0445 + j0.0645) \times 65.2 \angle -36.9^\circ = 234.85 \angle 0.4^\circ$$

$$VR = \frac{232.94 - 230}{230} = 1.28\%$$

$$VR = \frac{229.85 - 230}{230} = -0.062\%$$

$$VR = \frac{|V_{p/a}| - |V_s|}{|V_s|} \times 100\%$$


$$= \frac{234.85 - 230}{230} = 2.1\%$$

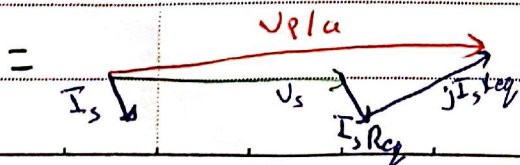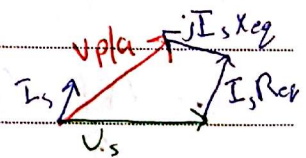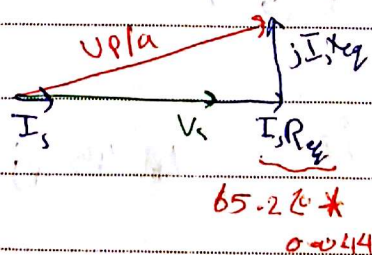

(C) Find the transformer efficiency when $\text{pf} = 0.8$ lagging

$$\eta = \frac{V_s I_s \cos \theta_s}{V_s I_s \cos \theta_s + P_{\text{core}} + P_{\text{cu}}}$$

$$I_s = 65.2 \angle -36.87^\circ$$

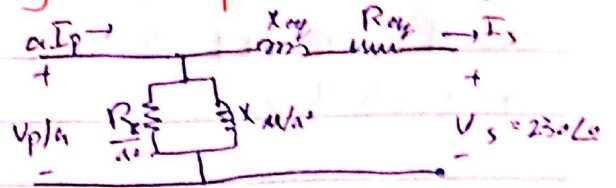


$$\rightarrow P_{\text{out}} = V_s I_s \cos \theta_s = 230 \times 65.2 \times \cos(36.87^\circ) = 12 \text{ kW}$$

$$\rightarrow P_{\text{cu}} = |I_s|^2 R_{\text{eq}} = (65.2)^2 \times 0.0445 = 189 \text{ W}$$

$$\rightarrow P_{\text{core}} = \frac{(V_p/a)^2}{R_{\text{cl/a}}} = \frac{(234.85)^2}{1050} = 52.5$$
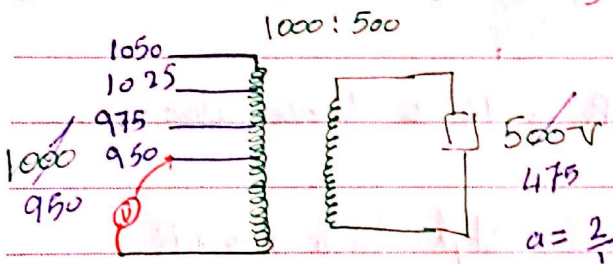
$$\eta = \frac{12000}{12000 + 189 + 52.5} = 98.03\%$$



$$a = 2, \quad \frac{950}{2} = 475$$

$$a' = \frac{950}{500} = 1.9 \rightarrow \frac{950}{1.9} = 500$$

20/6/2017

ex: 500kVA, 13200/480 V transformer has four 2.5% taps on it's primary winding, what are the transformer voltage ratios at each tap:-

5% tap 13860 : 480

2.5% tap 13530 : 480



→ 13200 : 480

-2.5% tap 12870 : 480

-5% tap 12540 : 480


ULTC: under load tap changer (Automatic change of tap while the transformer is in service)

The auto transformer :-

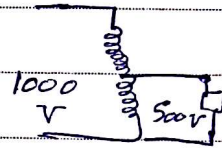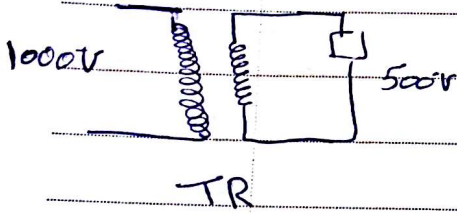


auto TR ≡ TR with one winding

step-up auto TR

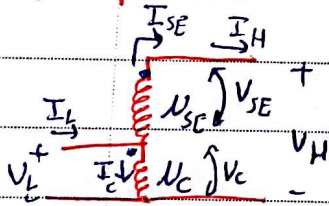

step-down auto TR

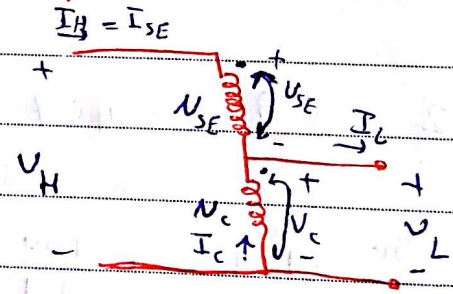

$N_c \equiv$ common winding

$N_{se} \equiv$ series winding

$V_L = V_c$

$V_H = V_c + V_{se}$

$I_L = I_{se} + I_c$ / $I_H = I_{se}$


$V_H = V_c + V_{se}$

$V_L = V_c$

$I_H = I_{se}$

$I_L = I_{se} + I_c$

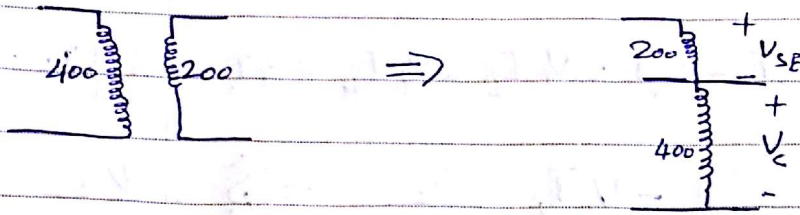Connect the two regular transformer winding in Series, then you will get an auto TR



$$\rightarrow \frac{V_C}{V_{SE}} = \frac{N_C}{N_{SE}}$$

$$N_C I_C = N_{SE} I_{SE}$$

$$\begin{aligned} V_H &= V_C + V_{SE} \\ &= V_C + V_C * \frac{N_{SE}}{N_C} \end{aligned}$$

$$= V_L + V_L * \frac{N_{SE}}{N_C} = V_L \left(1 + \frac{N_{SE}}{N_C} \right) \Rightarrow \boxed{\frac{V_H}{V_L} = \frac{N_C + N_{SE}}{N_C}} \rightarrow \boxed{\frac{V_L}{V_H} = \frac{N_C}{N_C + N_{SE}}}$$

low and high voltage relationship

$$\rightarrow I_L = I_C + I_{SE} = I_{SE} \frac{N_{SE}}{N_C} + I_{SE} = I_H \frac{N_{SE}}{N_C} + I_H$$

$$\boxed{\frac{I_L}{I_H} = \frac{N_C + N_{SE}}{N_C}} \text{ current relation}$$

* Apparent input and output power (Consider Step-up TR)

$$\dot{S}_{in} = V_L I_L$$

$$\dot{S}_{out} = V_H I_H = V_L * \frac{N_C + N_{SE}}{N_C} * I_L * \frac{N_C}{N_C + N_{SE}} = V_L I_L$$

$$\dot{S}_{in} = \dot{S}_{out} = \dot{S}_{I_0}$$

* Apparent power of each winding


$$\dot{S}_w = V_c I_c = V_{SE} I_{SE}$$

$$\dot{S}_w = V_L (I_L - I_{SE}) = V_L (I_L - I_H) = V_L I_L - V_L I_H = V_L I_L - V_L \left[\frac{I_L N_c}{N_c + N_{SE}} \right]$$

$$= V_L I_L \left[1 - \frac{N_c}{N_c + N_{SE}} \right] = V_L I_L \frac{N_{SE}}{N_c + N_{SE}} = \left[\dot{S}_{I_0} \cdot \frac{N_{SE}}{N_c + N_{SE}} \right]$$

$$\Rightarrow \boxed{\dot{S}_{I_0} = \dot{S}_w \frac{N_c + N_{SE}}{N_{SE}}} \Rightarrow \text{Apparent power advantage}$$

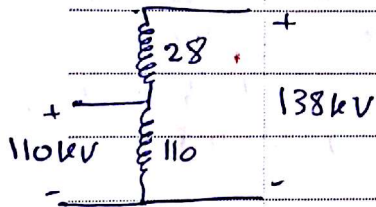ex 8: 5 MVA auto TR that connects 110kV system to 138kV system. turns ratio $N_c : N_{SE}$
110 : 28




This auto TR would actually have winding ratings:

$$\dot{S}_w = \dot{S}_{I_0} * \frac{N_{SE}}{N_c + N_{SE}} = 5 \text{ MVA} * \left[\frac{28}{28 + 110} \right]$$

$$= 1.015 \text{ MVA}$$

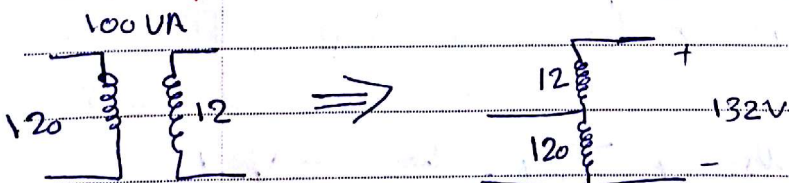ex 9: A 100 VA, 120/12V TR will be connected to form a step-up auto TR with the primary voltage of 120 V



* what will be the secondary voltage?

$$V_H = V_L * \frac{N_{SE} + N_c}{N_c} = 120 \left[\frac{120 + 12}{12} \right] = 132 \text{ V}$$

No. _____

* what will be the max power rating?! \Rightarrow " \dot{S}_{Io} "

$$\dot{S}_{Pw} = 100 \Rightarrow \dot{S}_{Io} = \dot{S}_{Pw} \frac{N_{SE} + N_c}{N_{SE}} = 100 \times \frac{120 + 12}{12} = 1100 \text{ VA}$$

$$\text{power advantage} = \frac{1100}{100} = 11$$



* I_H ?!

$$\dot{S}_{out} = I_H V_H$$

$$1100 = I_H \times 132$$

$$I_H = 8.33 \text{ A}$$

21/6/2017

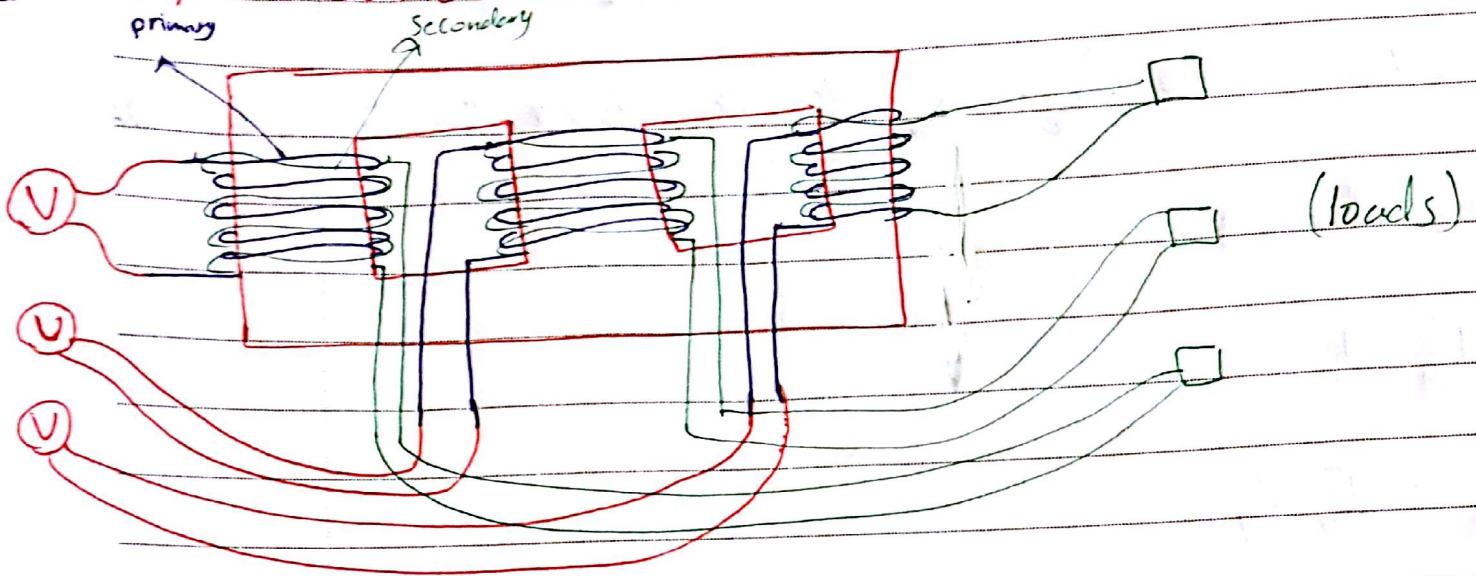
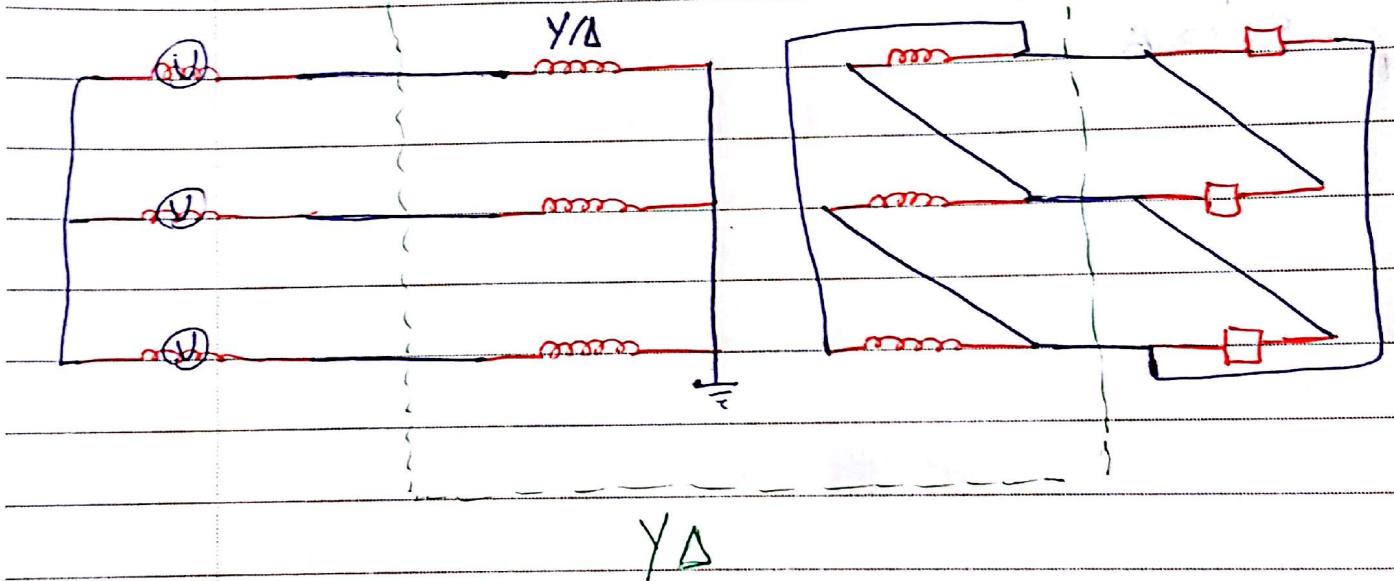
3 ϕ Transformers :-primary 3 ϕ TR Secondary

→ 4 possible Connection for 3 phase TRS :-

1) Y-Y


2) Y- Δ 3) Δ -Y4) Δ - Δ

① Y-Y

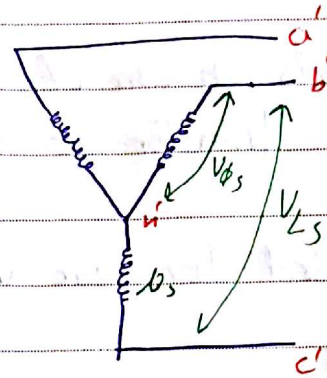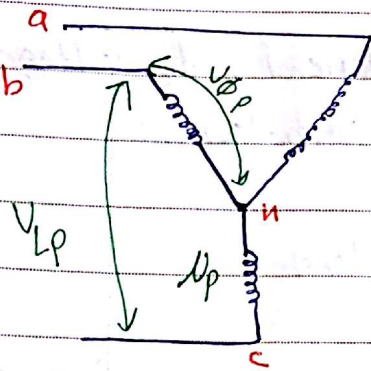


Y-Y 3φ
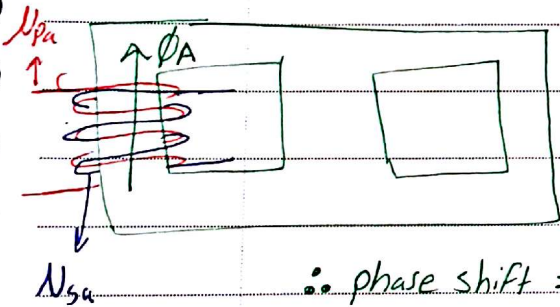
$$\rightarrow \frac{N_p}{N_s} = a = \frac{V_{\phi p}}{V_{\phi s}} = \frac{V_{Lp}/\sqrt{3}}{V_{Ls}/\sqrt{3}} = \frac{V_{Lp}}{V_{Ls}}$$




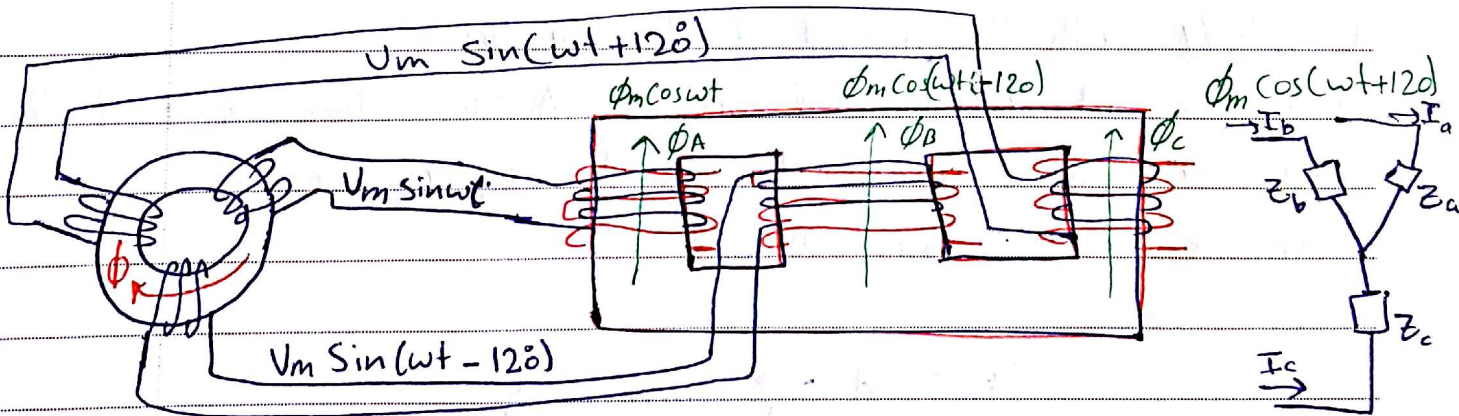∴ phase shift = 0 (same ϕ_A on the primary and secondary)



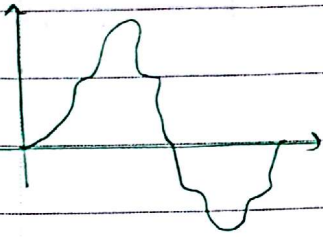problems of Y-Y TR:-

- ① if loads on one of the phase are unbalanced, the voltages on the transformer can become severely unbalanced.
- ② The 3rd harmonic voltages can be very large.



$$i(t) = I_m \cos \omega t + I_m' \cos(3\omega t) + I_m'' \cos(5\omega t) + I_m''' \cos(7\omega t)$$

$$i_a = I_m \cos \omega t + I_m' \cos 3\omega t$$


$$i_b = I_m \cos(\omega t - 120^\circ) + I_m' \cos(3\omega t - 360^\circ) \quad (+)$$

$$i_c = I_m \cos(\omega t + 120^\circ) + I_m' \cos(3\omega t + 360^\circ)$$

$$= 0 + 3I_m' \cos 3\omega t$$

Solution :-

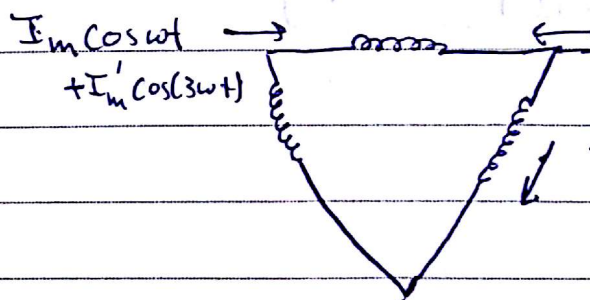- ① Solidly earth the neutral of the transformer
- ② add a 3rd Δ connected winding. A circulating current at the 3rd harmonic will flow through it suppressing the 3rd harmonic in the other winding.



$$I_a + I_{ab} = I_{bc}$$


$$I_a = I_{bc} - I_{ab}$$

$$= \sqrt{3} I_m \cos(\omega t - 30^\circ)$$

22/6/2017

No.



② Y-Δ Connection :-

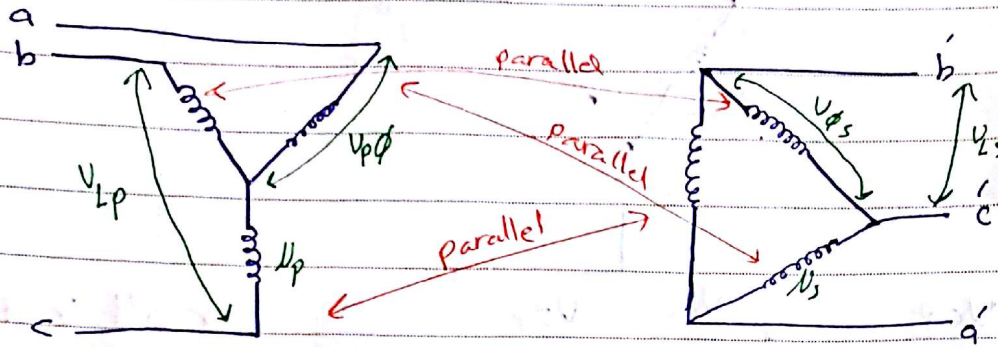

$$\frac{N_p}{N_s} = a = \frac{V_{\phi p}}{V_{\phi s}}, \quad \frac{V_{Lp}}{V_{Ls}} = \frac{\sqrt{3} V_{\phi p}}{V_{\phi s}} = \sqrt{3} a \quad \text{over all voltage ratio}$$



- * No 3rd harmonic issue, because of the Δ winding.
- * less unbalance when the load is unbalance, because the Δ partially redistribute any imbalance.

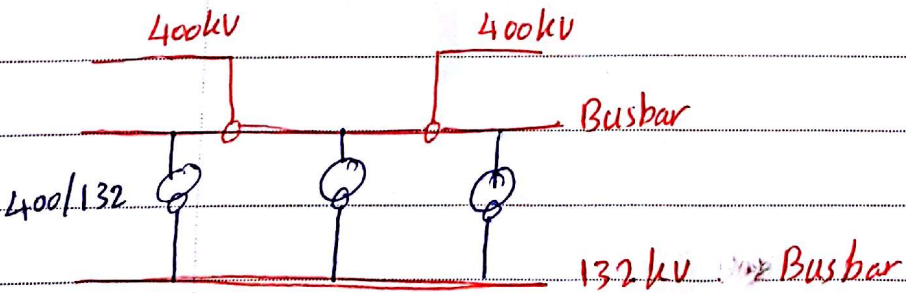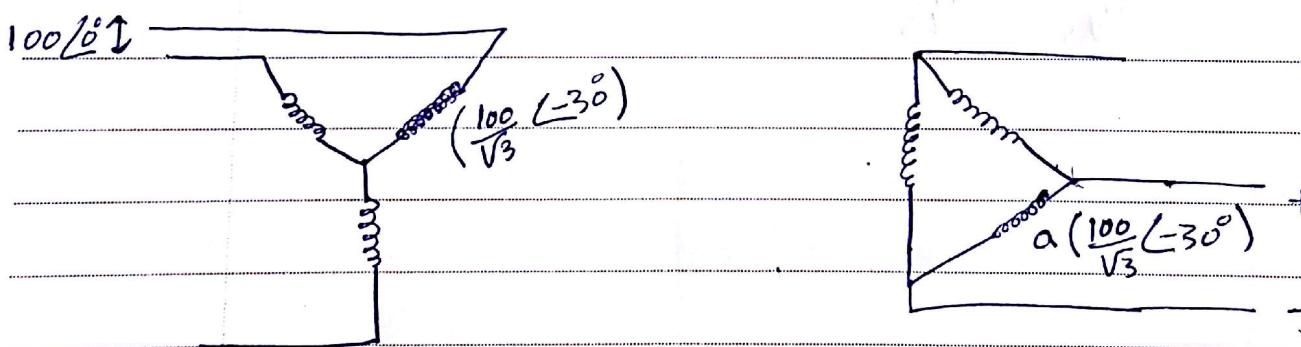Problems :- The secondary is phase-shifted by $\pm 30^\circ$ with respect to the primary voltage.



paralleling of transformers (will be discussed in vector group)



3] Δ -Y Connection :-

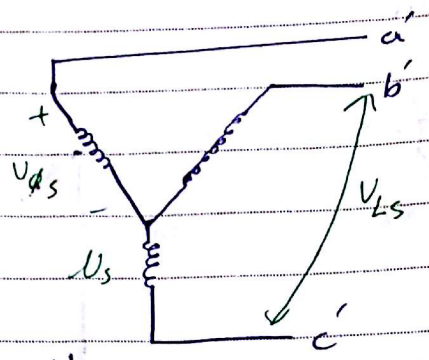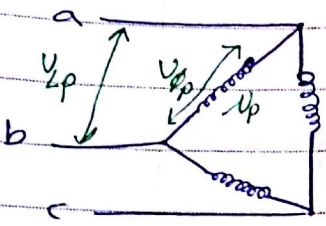

$$\frac{N_p}{N_s} = a = \frac{V_{\phi p}}{V_{\phi s}} \quad , \quad \frac{V_{Lp}}{V_{Ls}} = \frac{V_{\phi p}}{\sqrt{3} V_{\phi s}} = \underline{\underline{\frac{a}{\sqrt{3}}}}$$

overall voltage ratio



4] Δ - Δ Connection :-

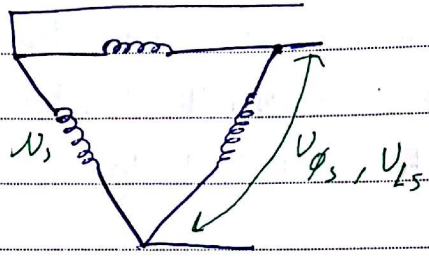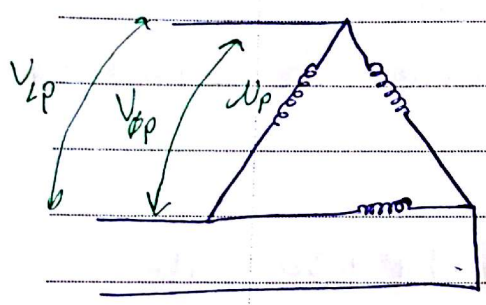

$$\frac{N_p}{N_s} = a = \frac{V_{\phi p}}{V_{\phi s}} = \frac{V_{Lp}}{V_{Ls}}$$



Vector groups 8-

①

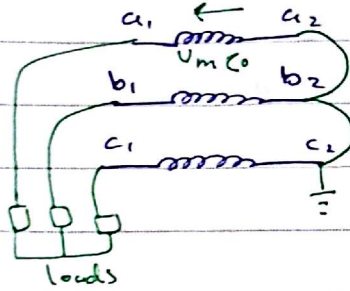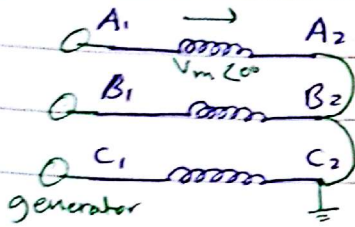

$\boxed{Y} \boxed{y} \boxed{0}$

②

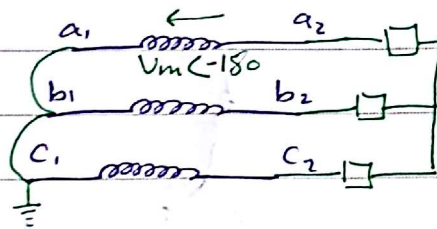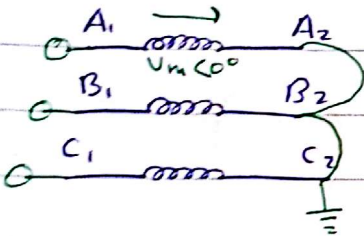

$\boxed{Y} \boxed{y} \boxed{6}$

\boxed{Y}


primary connection
"capital letter"

\boxed{y}

secondary
"small"

$\boxed{0}$

phase shift

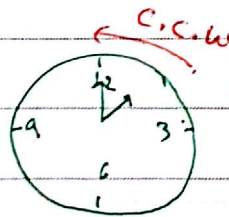

1 \rightarrow 30°

6 \rightarrow 180°

2 \rightarrow 60°


11 \rightarrow $330^\circ / -30^\circ$

① Δ / y \rightarrow L.V side lags H.V side by 30°



② y / Δ \rightarrow L.V side leads H.V side by 30°

$-30^\circ / 330^\circ$


3) $\Delta d o$

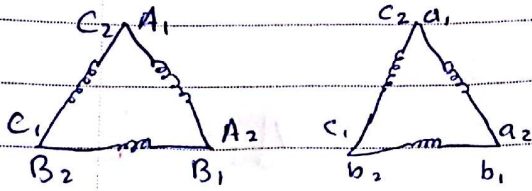

4) $y y o$

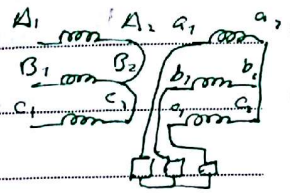
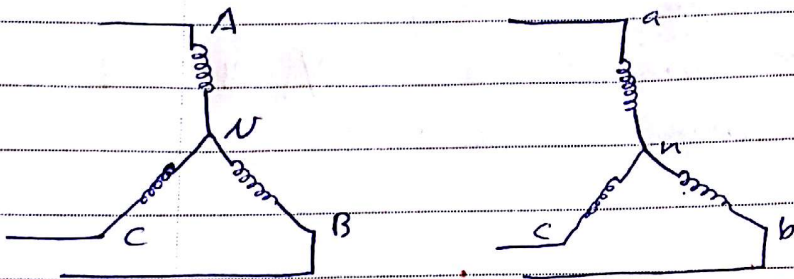


5) $y y \phi$

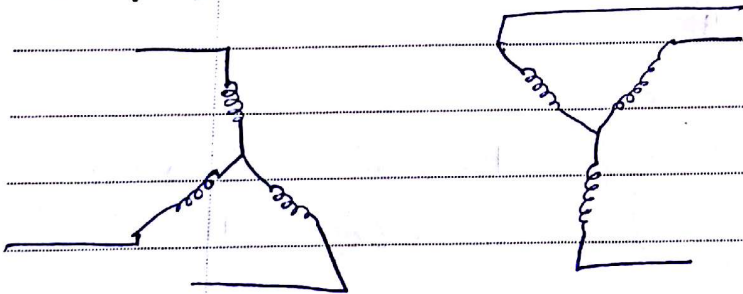






we can say leads or lags

6) $\Delta d \phi$

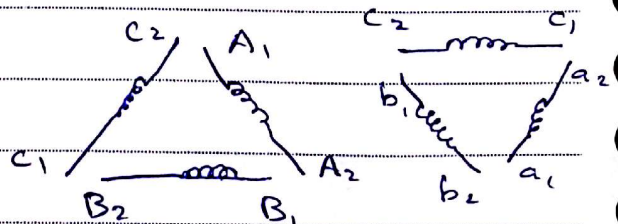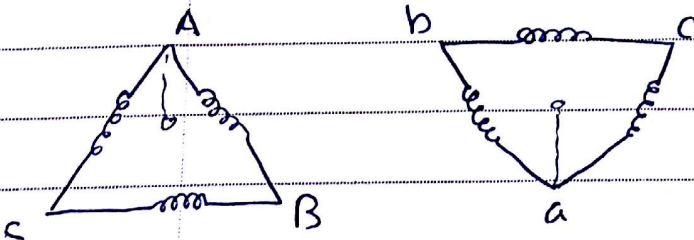







29/6/2017

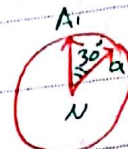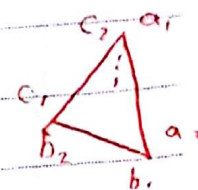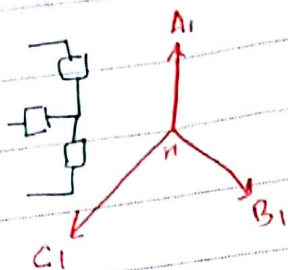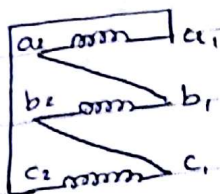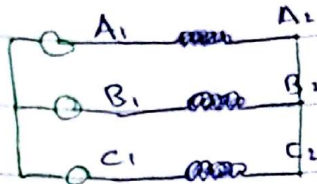$\Delta d 1 \rightarrow$ L.V lags H.V by 30°






$\Delta d II$

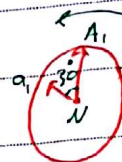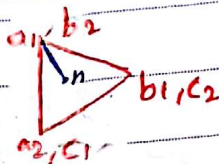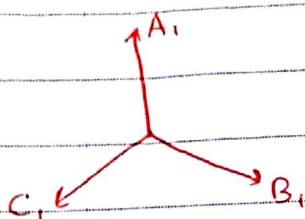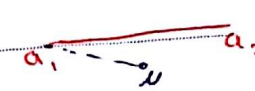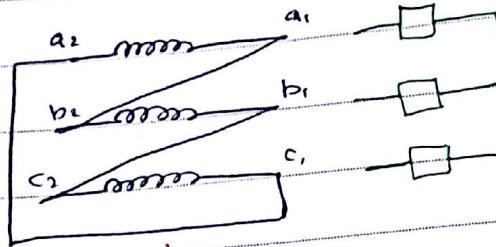
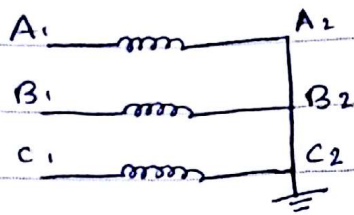
$\Delta d II \rightarrow$ L.V leads H.V by 30°







$\Delta y I$

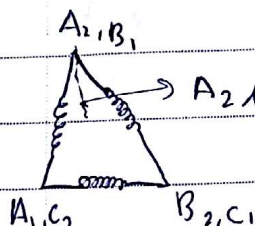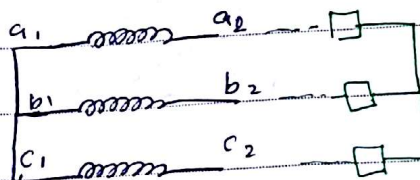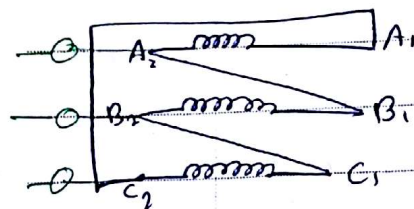

(because it's connected to the source)

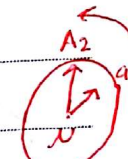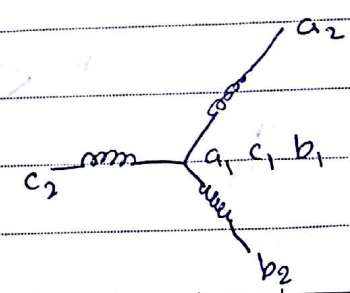




No.

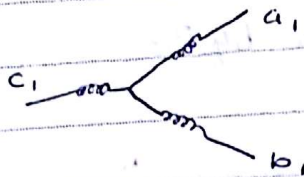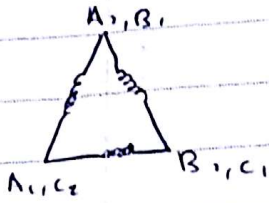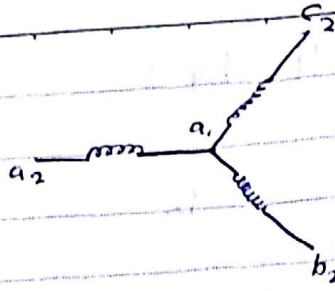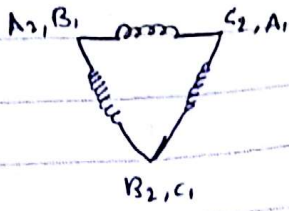

Dy 7



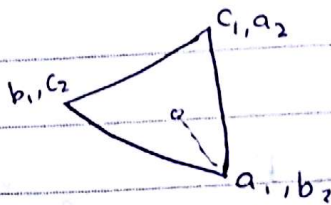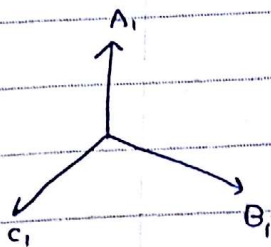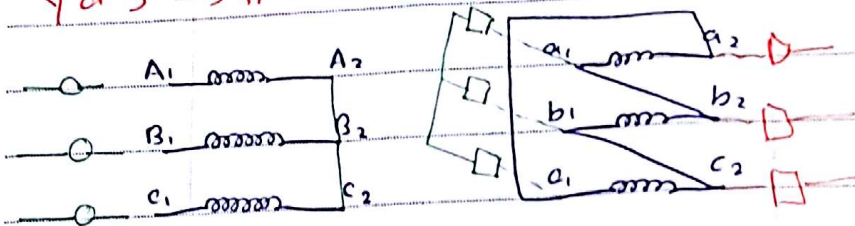
$\Delta d II \rightarrow L.V. \text{ leads } H.V. \text{ by } 30^\circ$
 $\Delta d 5 \rightarrow H.V. \text{ leads } L.V. \text{ by } 150^\circ$



Standard vector group :-






- Group I (0°) 0 o'clock $\Delta\Delta, Y Y$
- Group II (180°) 6 o'clock $\Delta\Delta, Y Y$
- Group III (-30°) 11 o'clock $Y\Delta$ or ΔY
- Group IV (30°) 1 o'clock $Y\Delta$ or ΔY

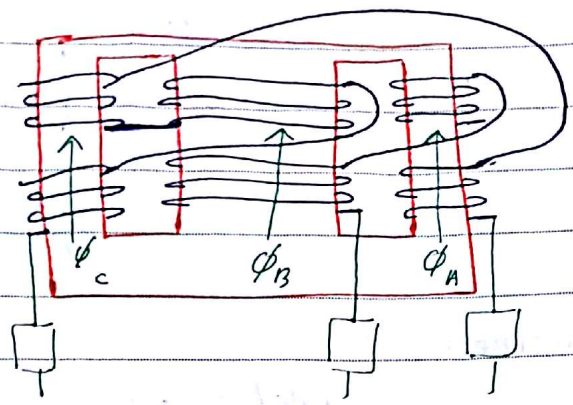Zigzag Connection [uniformly distributes the unbalanced loads] better than Δ



Inrush current :- [transient problem]
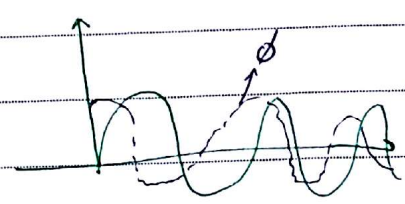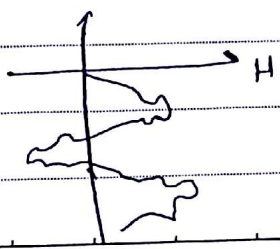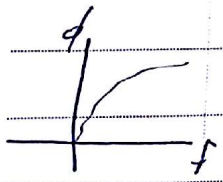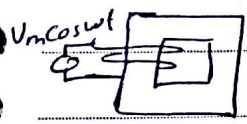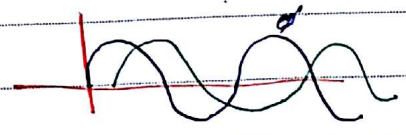
$$e_{ind} \text{ v.c.H} = -N \frac{d\phi}{dt}$$



TR acts as a short ckt $R \downarrow V. \text{low}$
 $\mu \uparrow U. \text{high}$

if $v(t) = V_m \cos \omega t$
 lets integrate for $\frac{1}{2}$ cycle

$$\phi = \frac{1}{N} \left[\int v(t) dt \right]$$

$$\phi = \frac{1}{N} \int_0^{\pi/\omega} V_m \cos \omega t dt$$

$$= 0$$

if $v(t) = V_m \sin \omega t$

→ lets integrate for $\frac{1}{2}$ cycle


$$\phi = \frac{1}{N} \int_0^{\pi/\omega} V_m \sin \omega t dt$$

$$= \frac{2 V_m}{\omega N}$$

x in general Steady State

$$\phi = \frac{1}{N} \int_0^t v(t) dt$$

$$= \frac{V_m}{\omega N}$$

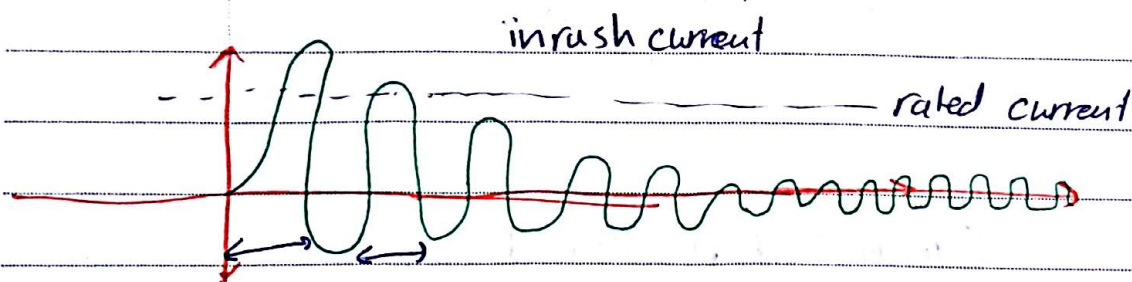

1/7/2017

No.

Per unit system in 3 ϕ transformers :-

$$a \quad \frac{100 \text{ MVA}}{3\phi, S} \quad \frac{0.480/33 \text{ kV}}{V_{LL, \text{pri}} \quad V_{LL, \text{sec}}} \quad \text{TR}$$

$$S_{1\phi, \text{base}} = \frac{S_{3\phi, \text{base}}}{3}$$

$$I_{\phi, \text{base}} = \frac{S_{1\phi, \text{base}}}{V_{\phi, \text{base}}} = \frac{S_{3\phi, \text{base}}}{3 \times V_{\phi, \text{base}}}$$

$$Z_{\text{base}} = \frac{(V_{\phi, \text{base}})^2}{S_{1\phi, \text{base}}} = \frac{3(V_{\phi, \text{base}})^2}{S_{3\phi, \text{base}}}$$

in Δ Connections :-

$$V_{L, \text{base}} = V_{\phi, \text{base}}$$

in γ Connections :-

$$V_{L, \text{base}} = \sqrt{3} V_{\phi, \text{base}}$$

The base line current :-

$$I_{L, \text{base}} = \frac{S_{\text{base}}}{\sqrt{3} V_{L, \text{base}}}$$

Example 8. (2.9)


50 kVA, 13800/208 V ΔY TR has a resistance of 1 p.u. and reactance 7 p.u.

1) What is the transformer's phase impedance referred to H.V side?!

$$Z_e = Z_{base} * Z_{p.u.}$$

$$H.V \leftarrow Z_{base} = \frac{3 * (13800)^2}{50 * 10^3} = 11426 \Omega$$
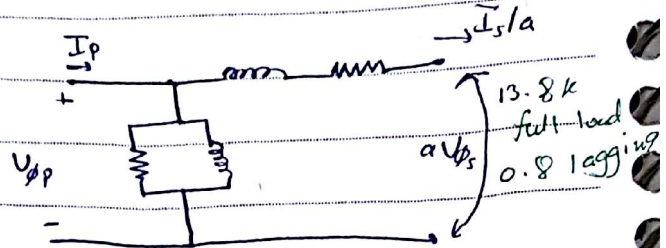
$$L.V \leftarrow Z_{base} = \frac{3 * \left(\frac{208}{\sqrt{3}}\right)^2}{50 * 10^3} = \dots$$



$$Z_s = 11426 * (0.01 + j0.07) \\ = 114 + j800 \Omega$$

100% of the current is passing

2) the voltage regulation at full load and 0.8 p.f lagging!

$$VR = \frac{V_p/a - V_s}{V_s} * 100\% \rightarrow L.V \text{ side}$$

$$VR = \frac{V_p - aV_s}{aV_s} * 100\% \rightarrow H.V \text{ side}$$

$$\rightarrow aV_s = 13800 \angle 0^\circ$$

$$I = ? \quad \rightarrow \dot{S}_{3\phi} = 3 V_\phi I_\phi$$


$$I_\phi = \frac{\dot{S}_{3\phi}}{3 V_\phi} = \frac{50 * 10^3}{3 * 13800} = 1.208 \text{ A}$$

$$V_{\phi p} = 13800 + (114 + j800) * 1.208 \angle -36.9^\circ = 14506 \angle 2.73^\circ$$

$$VR = \frac{14506 - 13800}{13800} * 100\% = 5.1\%$$

No. _____
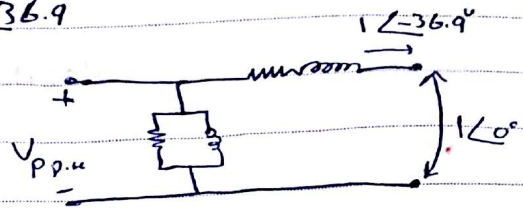
$$V_{p.u} = 1 \angle 0^\circ + (0.01 + j0.07) \times 1 \angle -36.9^\circ$$
$$= 1.051 \angle 2.73^\circ$$





$$VR = \frac{1.051 - 1}{1} = 5.1\%$$

No. "Electric Machines"

electric Machines

Generators

Motors

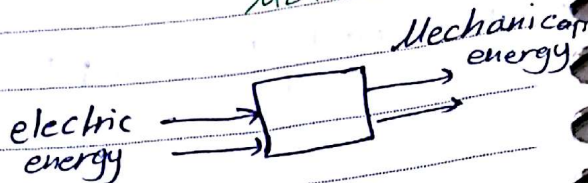
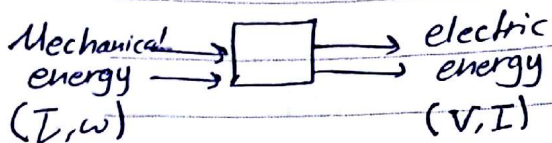


→ for Ideal machines $VI = T\omega$, $P = T\omega$

Generators

Ac generator



Dc generator

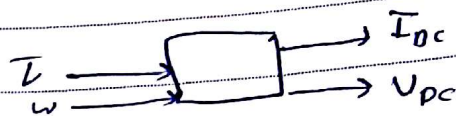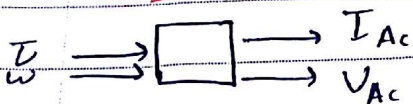

Motors

Dc motors

Ac motors

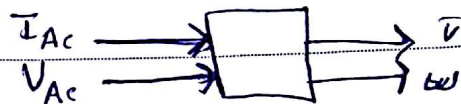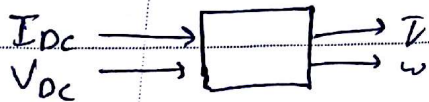


- * most of electric machines are **AC**
- * **DC** motors are - Sometimes - preferred where
 - easier to control
 - they develop rated torque at all speeds [from stand still to rated speed].
 - develop torque at stand still is several times greater than an AC machine of an equal power and speed rating.

Applications of DC motors &


- printing presses
- fans
- pumps
- cranes
- mills
- traction
- electronics
- speed control of other larger machines
- auto mobile
- air crafts

* DC generators are almost obsolete because of the use of power electronics.


parts of DC machine

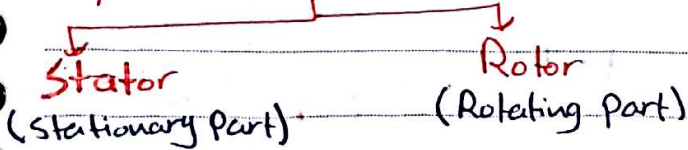

Winding

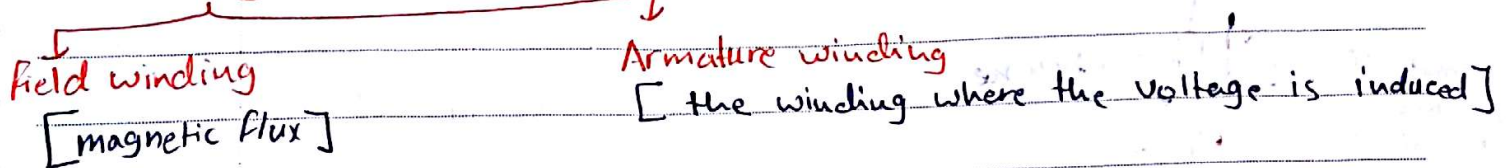


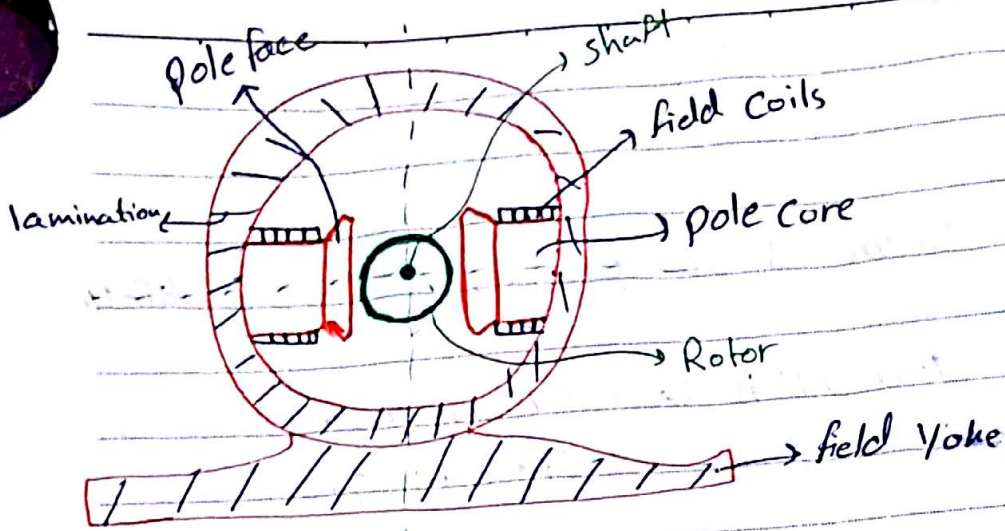→ In DC machines & - field winding → Stator
armature winding → Rotor






Stator

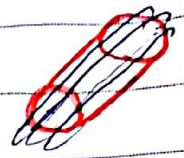- * field yoke gives physical support
- * field coils gives magnetic field



- * Armature winding on the rotor

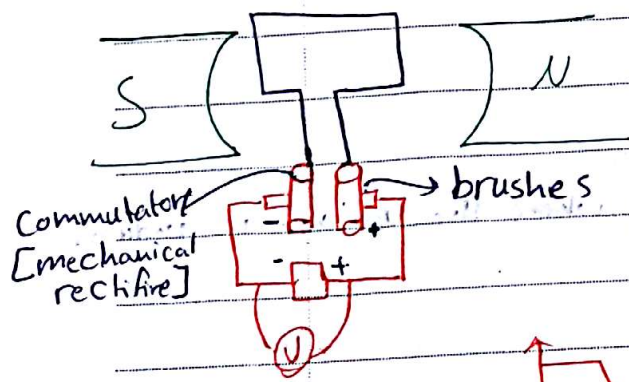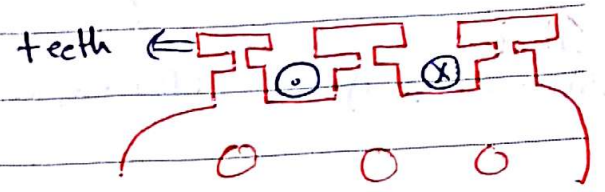
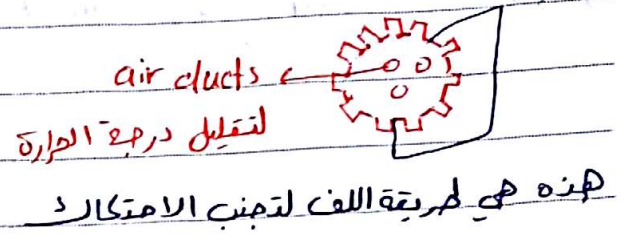


Brushes → highly conductive
and friction coefficient very low





Commutating machines

No.

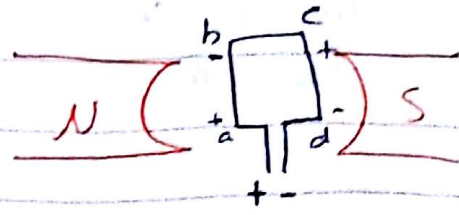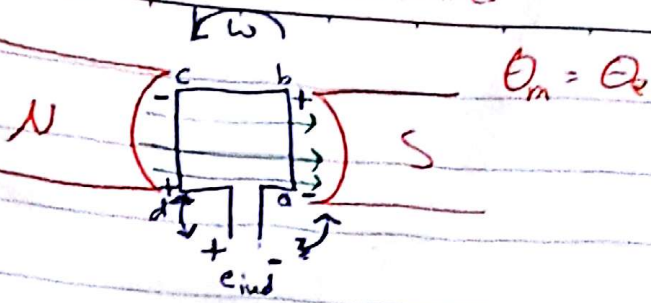
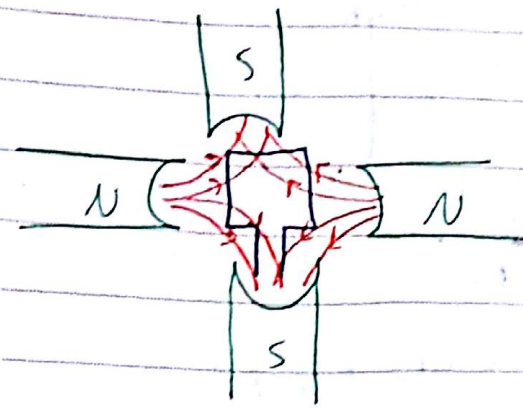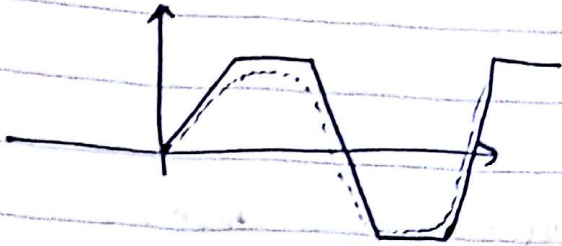
$$e_{ind} = V_{ba} + V_{cb} + V_{dc} + V_{ad}$$







$$n_{mec} = \frac{60 \times f}{P}$$

n_{mec} → mech speed
 f → frequency
 P → # of pole pairs



$$f = \frac{n_{mec} \times P}{60}$$

$$\theta_e = P \theta_m$$

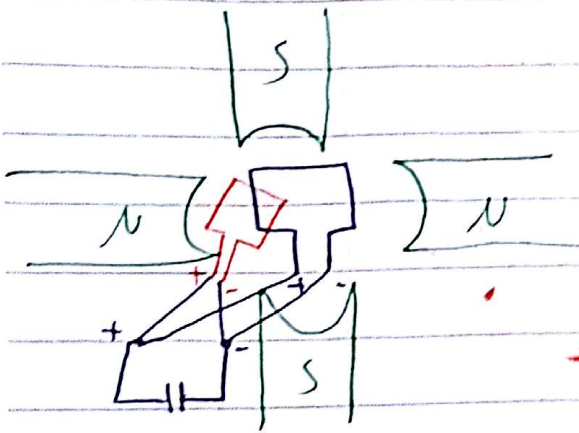


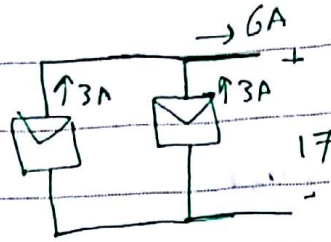
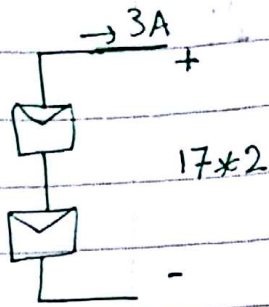
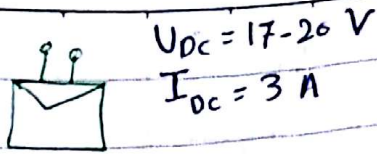


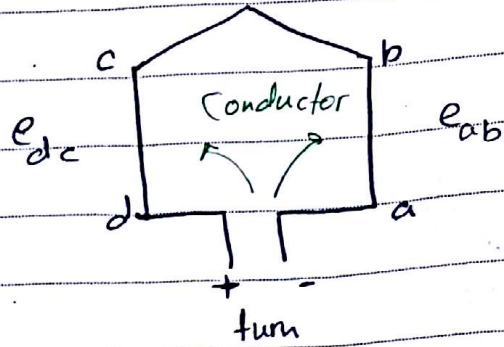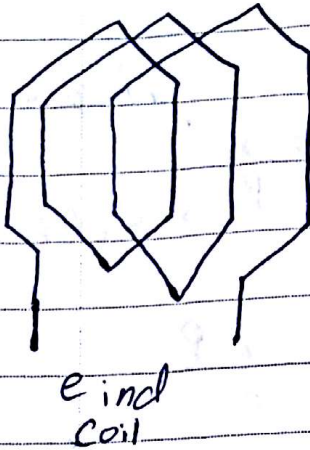Armature winding :- (usually drawn in a diamond shape)




$$e_{ind} = e_{ba} + e_{cd}$$

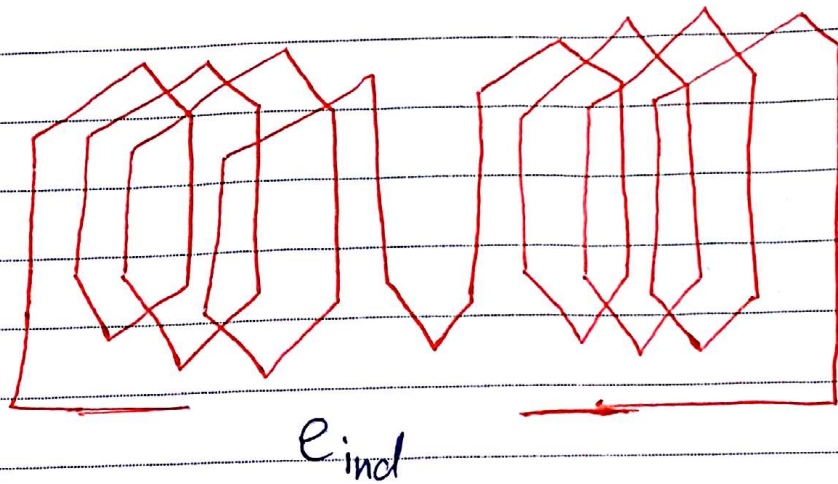


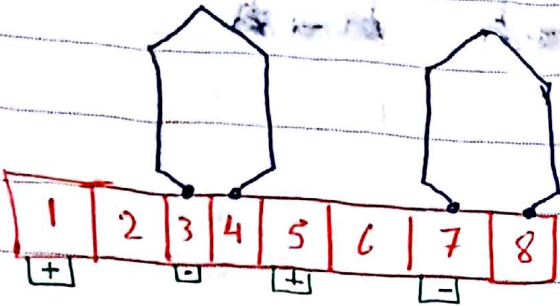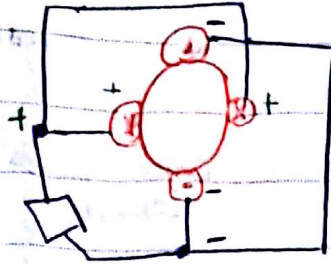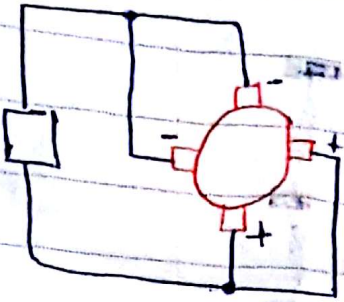

Lap winding

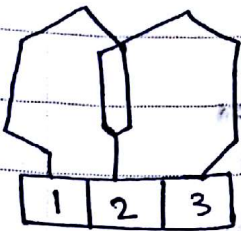


Wave winding

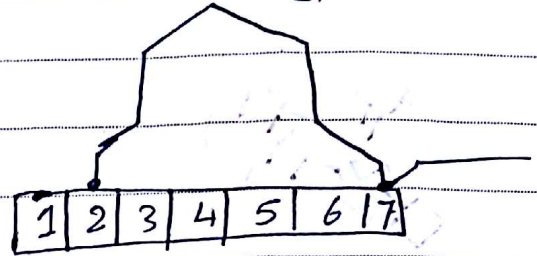



* Coil containing one or more turns of wire with the two ends of each coil coming out at adjacent commutator segment

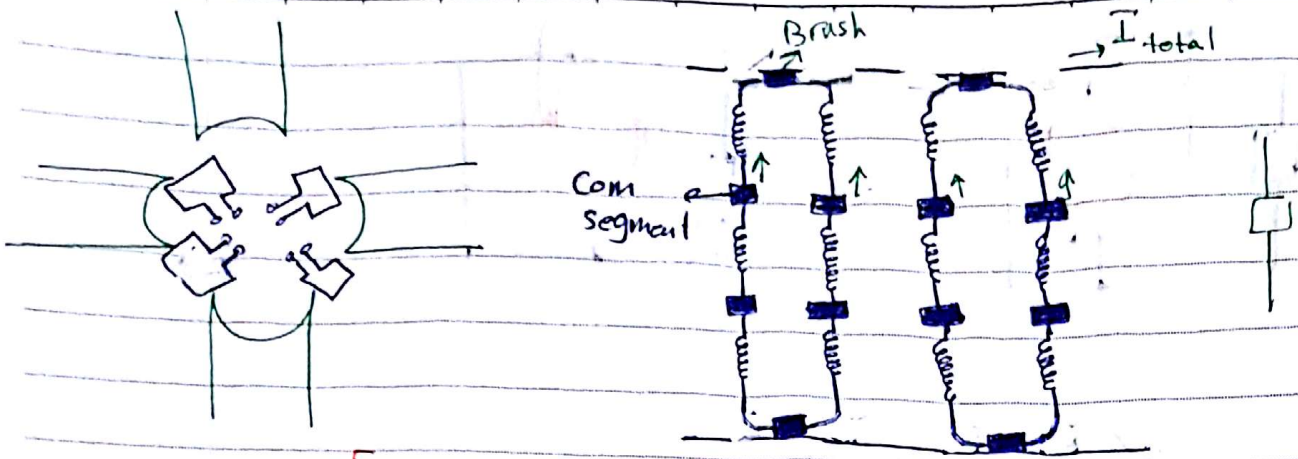* the end of the coil must be connected just before or just after the mid point of the electric circuit.




lap winding

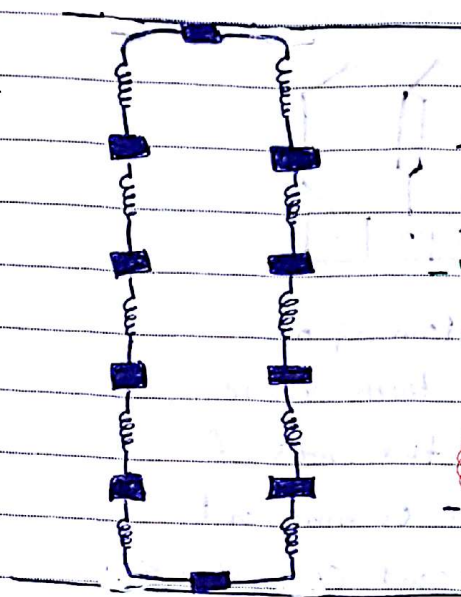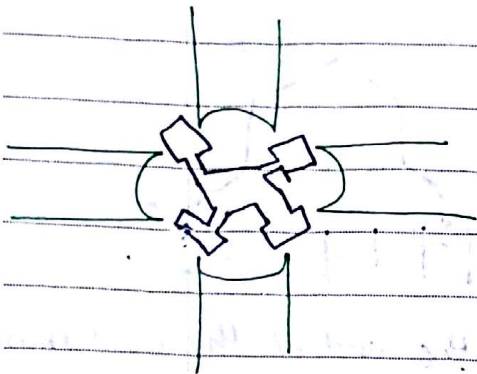low voltage / high current
because of parallel connection



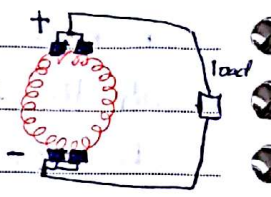- We need at least 2 brushes
- We can add extra brushes



wave winding

high voltage / low current


\times of parallel current paths (a) = 2

\times of current paths = \times of poles = \times of brushes

2/7/2017

No.

The simplest DC machine ever

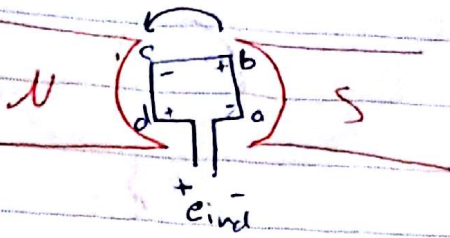


$$e_{ind} = V_{ba} + V_{cb} + V_{dc} + V_{da}$$

$$e_{ind} = (\mathbf{v} \times \mathbf{B}) \cdot \mathbf{l}$$

↓ thumb → fingers
 The perp. to the hand

* عند مرور ال Flux في ال air gap
 سيحدث عن اقصر طريق للوصل بين القطبين
 ال اقصى مساحة ممكنة لذلك يحدث الانعكاس.
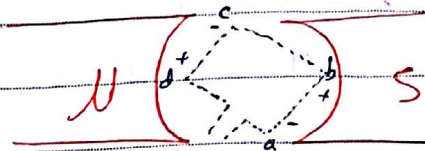
$$e_{ba} = (\mathbf{v} \times \mathbf{B}) \cdot \mathbf{l} = \begin{cases} VB l & , \text{ into the page, under pole face} \\ 0 & , \text{ beyond the pole face} \end{cases}$$




$$e_{cb} = 0$$

$$e_{dc} = (\mathbf{v} \times \mathbf{B}) \cdot \mathbf{l} = \begin{cases} VB l & , \text{ out of the page, under pole face} \\ 0 & , \text{ beyond pole face} \end{cases}$$

$$e_{ad} = 0$$

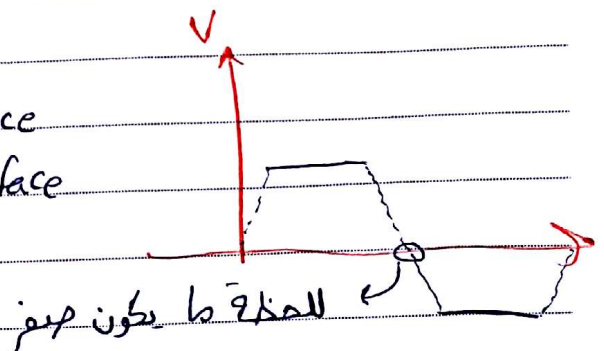
$$e_{ind \text{ total}} = \begin{cases} 2VB l & , \text{ under pole face} \\ 0 & , \text{ beyond pole face} \end{cases}$$



tangential velocity

$$v = r \omega$$

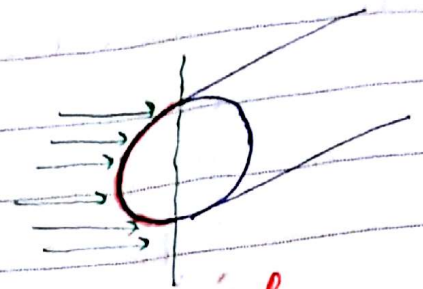radius \leftarrow \rightarrow angular velocity




$$e_{ind} = \begin{cases} 2r\omega Bl & , \text{under} \\ 0 & , \text{beyond} \end{cases}$$

$$e_{ind} = 2r\omega \frac{\phi}{A} l = \frac{2r\omega \phi l}{\pi r^2} = \frac{2}{\pi} \omega \phi$$

$$e_{ind} = \begin{cases} \frac{2}{\pi} \omega \phi & , \text{under} \\ 0 & , \text{beyond} \end{cases}$$

\rightarrow magnetic intensity (Flux)


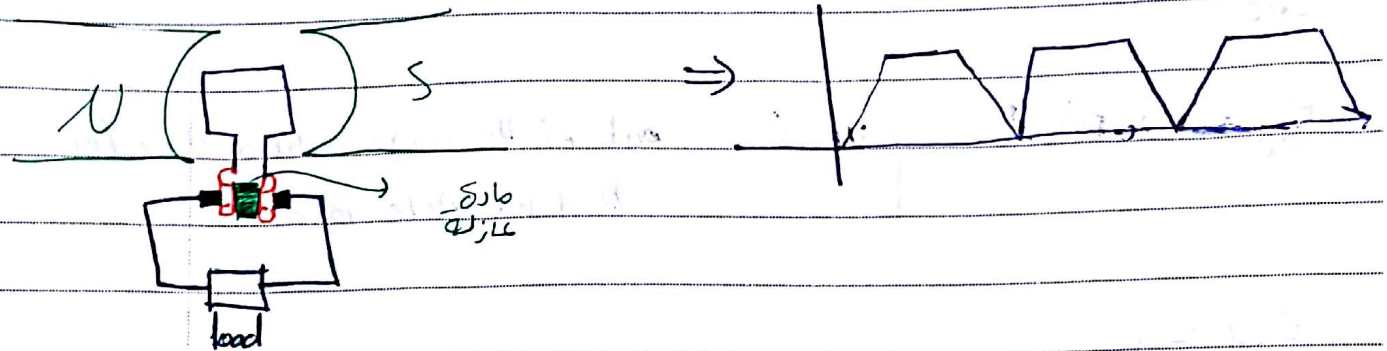
Constant depend on the dimensions and physical structure of prime mover



3/7/2017

No.

Motors :-

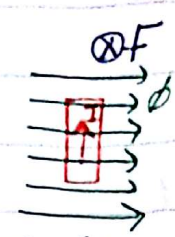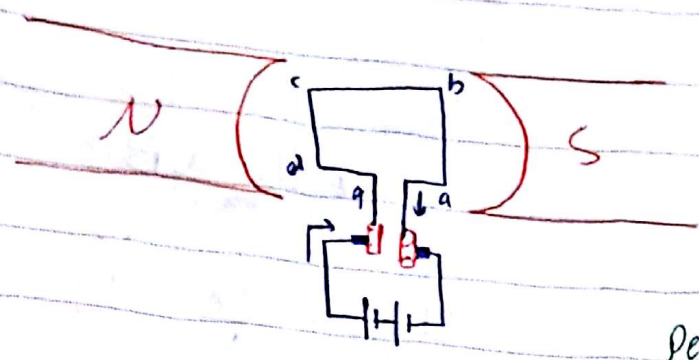

$$F = (l \times B) \cdot i$$


Perp. to the hand

Thumb fingers

$$\tau = r F \sin \theta \quad , \quad \theta \equiv \text{angle between } r \text{ and } F$$

$$\tau = \tau_{ab} + \tau_{bc} + \tau_{cd} + \tau_{da}$$
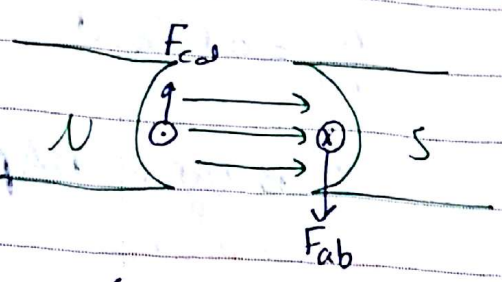
$$\tau_{ab} = \frac{i l B}{0} \quad \tau_{bc} = \frac{i l B}{0} \quad \tau_{cd} = \frac{i l B}{0} \quad \tau_{da} = \frac{i l B}{0}$$



$$\tau_{ind} = \begin{cases} 2 i r l B & , \text{ under} \\ 0 & , \text{ beyond} \end{cases}$$

$$\phi = B A_p = B (\pi r l)$$

$$\tau_{ind} = \begin{cases} \frac{2}{\pi} \phi i & , \text{ under} \\ 0 & , \text{ beyond} \end{cases}$$

depends on :-

- ① magnetic Flux .
- ② electric source .
- ③ Constant depends on the dimension and physical structure .


No. _____

Generator

$$E_a = k \phi \omega$$

$$e_{ind} = v B l$$

[voltage per conductor
under pole face]

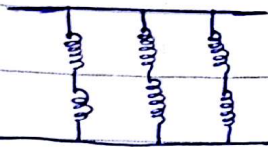

$$E_a = \frac{Z}{a} v B l$$

Z → # of conductors
 a → # of // current paths

$$E_a = \frac{Z}{a} r \omega m B l$$


Motor

$$T_a = k \phi I$$

$$T = r I_{cond} l B$$

$$I_{cond} = \frac{I_a}{a}$$

Total Armature current

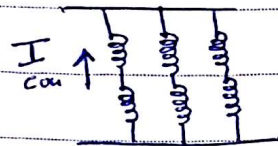

$$T_{cond} = r \frac{I_a}{a} l B$$

$$T_{ind} = \frac{Z}{a} r I_a l B$$

$$\phi = B \frac{2\pi r l}{p} = B A_p$$

flux per pole face

$$\phi = B A_p$$

$$I_{ind} = \left(\frac{ZP}{2\pi a}\right) \phi I_A$$

$$\phi = B \times \frac{2\pi r l}{p}$$

$$= k \phi I_A$$

$$E_a = \frac{Z r \omega_m B l}{a} \times \frac{p}{p} \times \frac{2\pi}{2\pi}$$

$$k = \frac{ZP}{2\pi a}$$

$$E_a = \left(\frac{ZP}{2\pi a}\right) \left(\frac{2\pi r l B}{p}\right) \omega_m$$

$$k' = \frac{ZP}{60a}$$

$$E_a = k \phi \omega_m \rightarrow \text{rad/sec}$$

$$k = \frac{ZP}{2\pi a}$$

$$E_a = k' \phi n_m \rightarrow \text{rev/min}$$

$$k' = \frac{ZP}{60a}$$

Example 8- Determine the induced voltage in the armature of a DC machine running at 1750 rpm and having 4 poles. The flux per pole is 25 mwb and the armature is lap wound with 36 coils with 13 turns on each coil. $a = p = \text{brushes}$

$$Z = 2 \times 36 \times 13 = 936 \text{ Conductor}$$



$$E_a = k \phi \omega_m = \frac{PZ}{60a} \times \phi \times \omega_m = \frac{936}{60} \times 25 \times 10^{-3} \times 1750 = 682.5 \text{ V}$$

$p = a = \text{brushes}$
Example 8- lap-wound armature has $\overbrace{567}^Z$ conductors and carries an armature current of $\overbrace{123.5}^{I_a}$ A. if the Flux per pole is $\overbrace{20}^{\phi}$ mwb, calculate the total produced torque

$$T_a = k \phi I_a$$
$$= \frac{pZ}{2\pi a} \phi I_a$$




$$= \frac{567}{2\pi} \times 20 \times 10^{-3} \times 123.5 = 226.43 \text{ Nm}$$

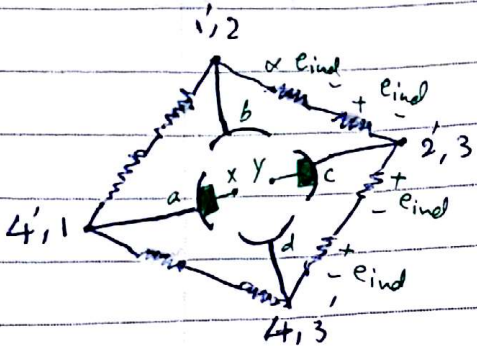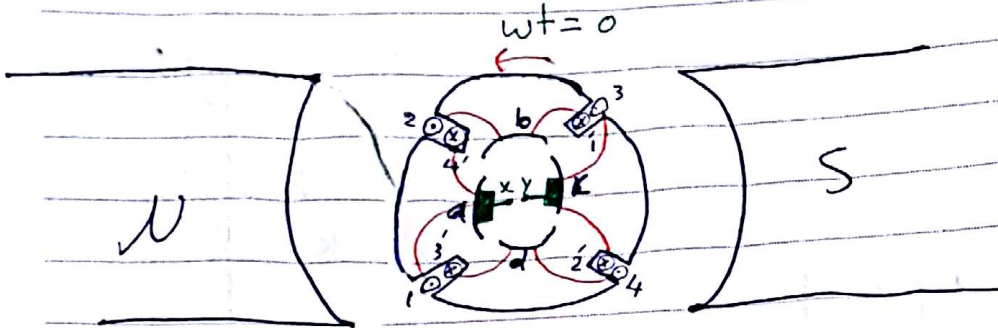x Commutation in a simple 4 loop DC machine a



$E_a = 4UBl$ when $wt = 0$


$wt = 45^\circ$

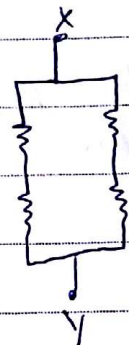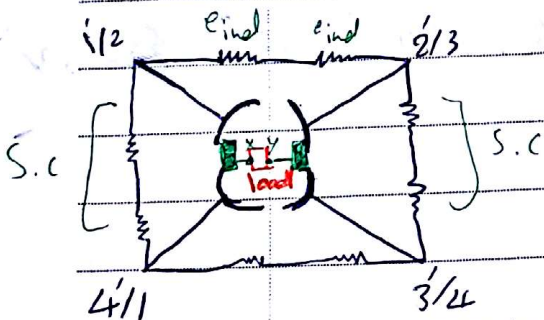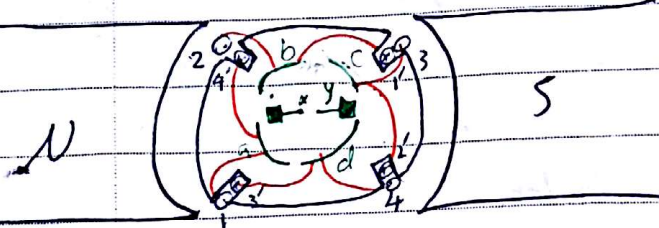


$E_a = 2UBl$
when $wt = 45^\circ$

No. _____

* $\omega t = 90^\circ$

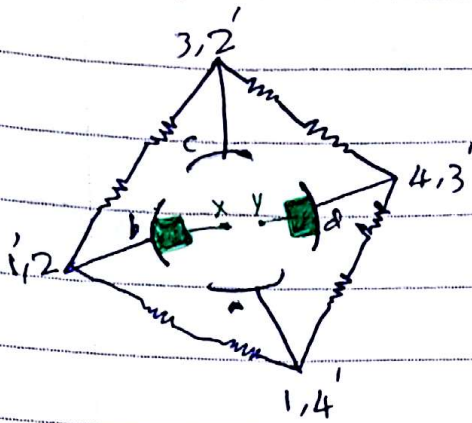

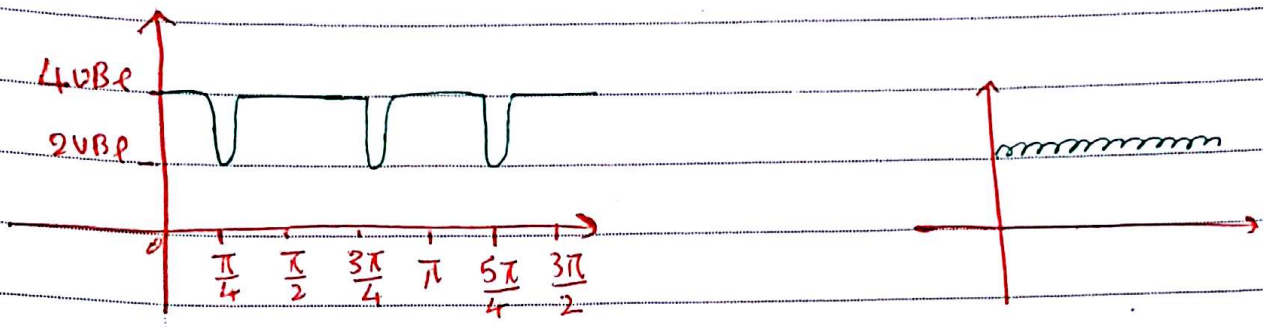$E_a = 4V_{BR}$ when $\omega t = 90^\circ$




~~End of Second Material~~

4/7/2017

problems with Commutation in Dc machine :-

(I) Armature reaction


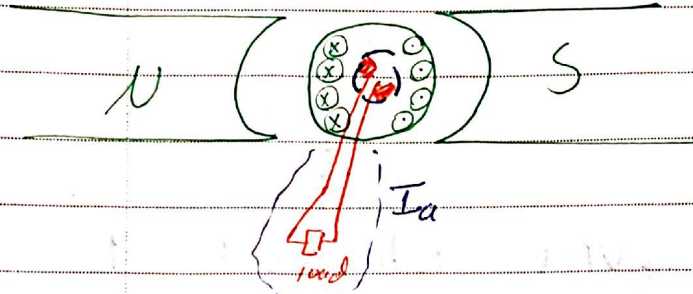



This current (I_a) produces it's own magnetic field that distorts the original magnetic field.

Armature reaction

neutral-plane shift flux weakening


A) Neutral-plane shift

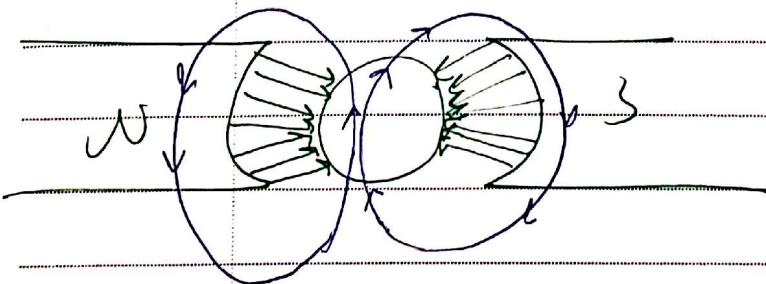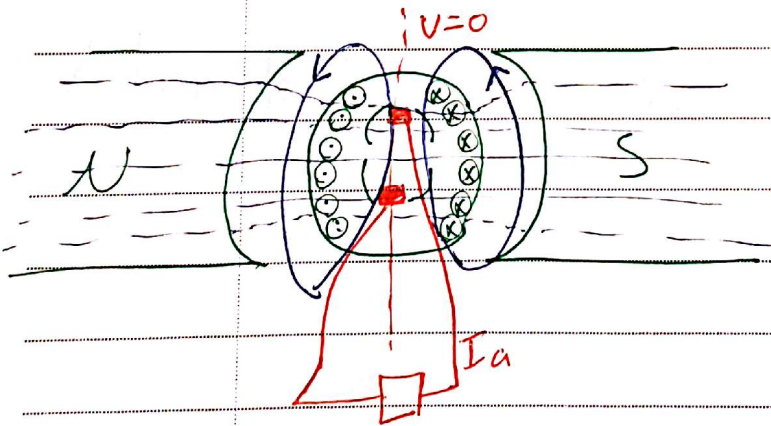


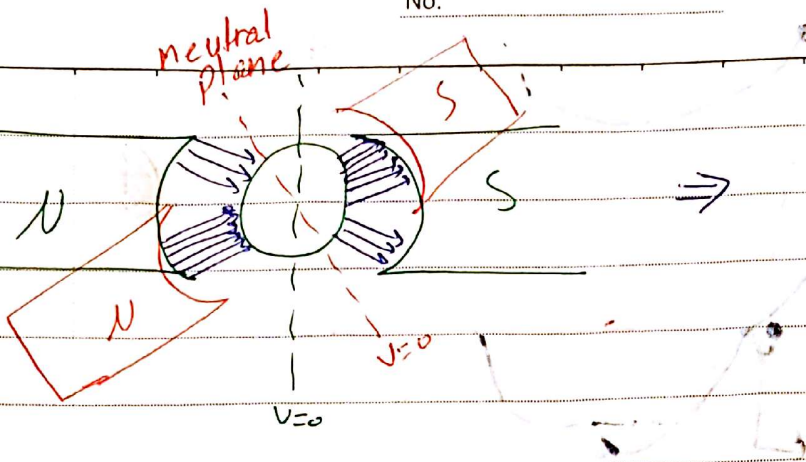


sparkling & arching
in the brushes


B) Flux Weakening

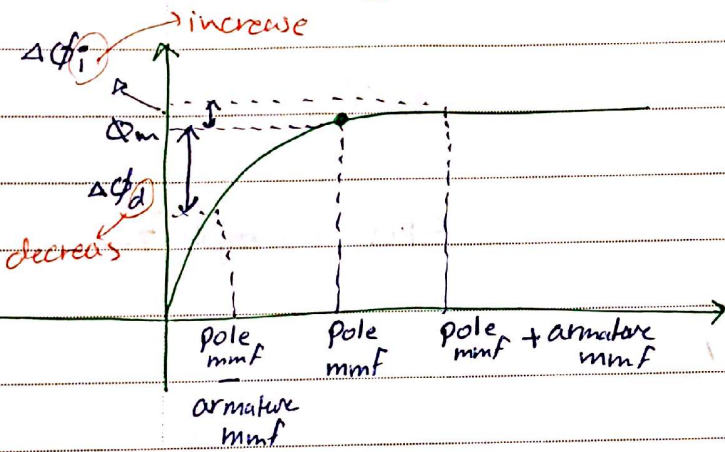

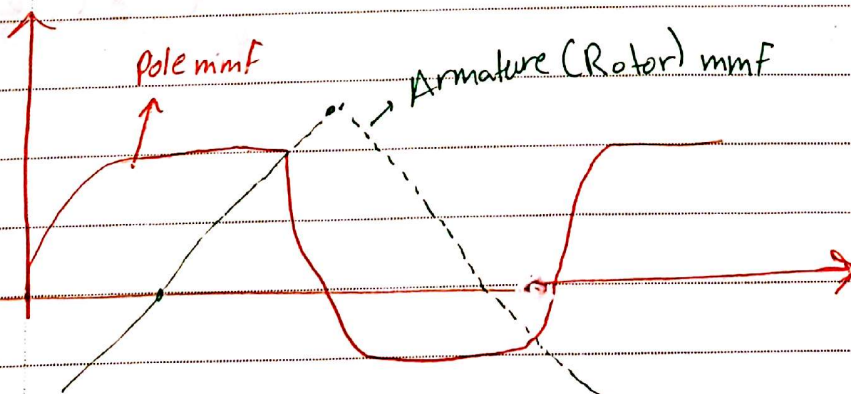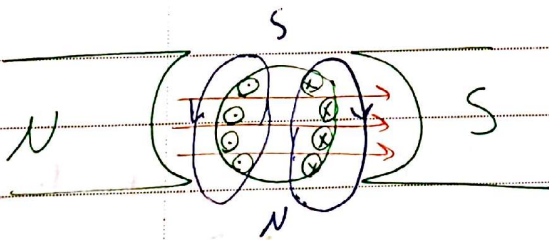The total coverage
flux under the pole
faces decreases.



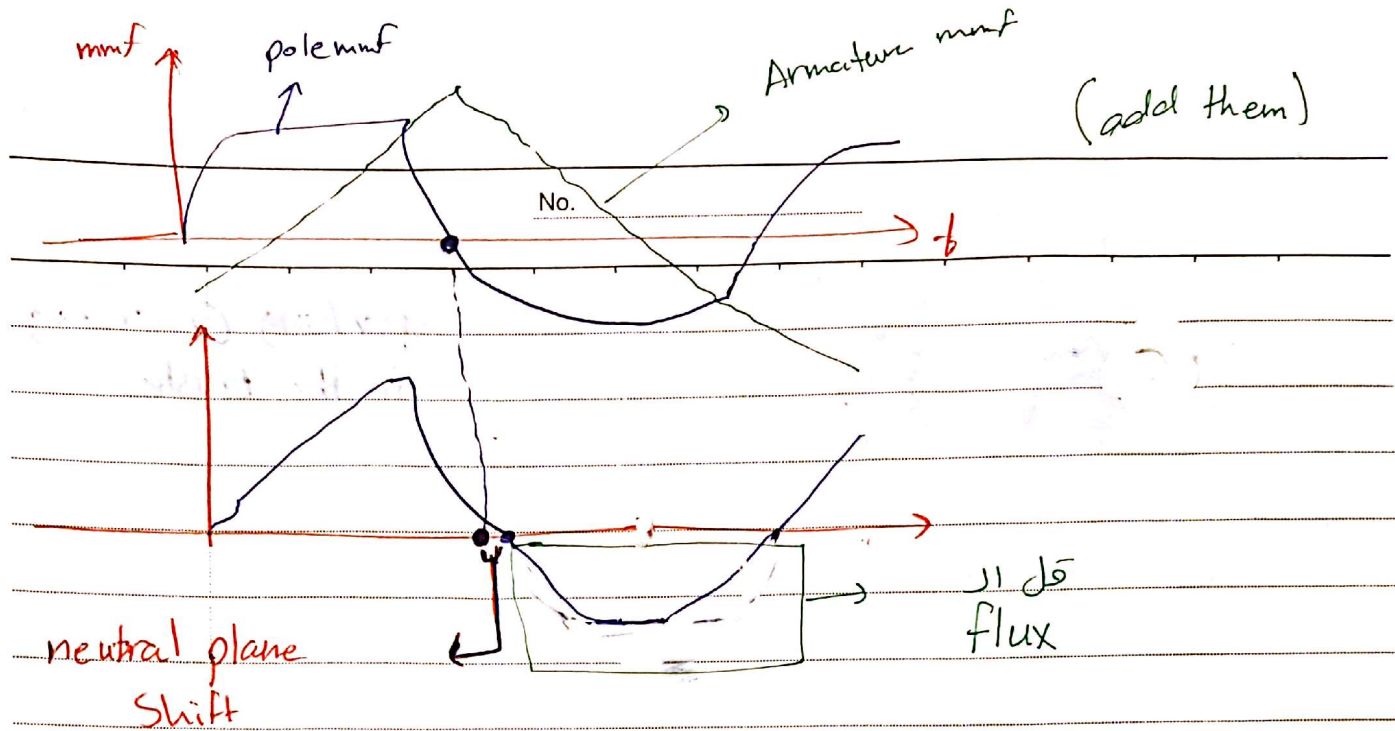when we add them we get \Rightarrow in the
next page




Generator

Motor

$$E_a = k \phi \omega_m$$

Study example 7.1

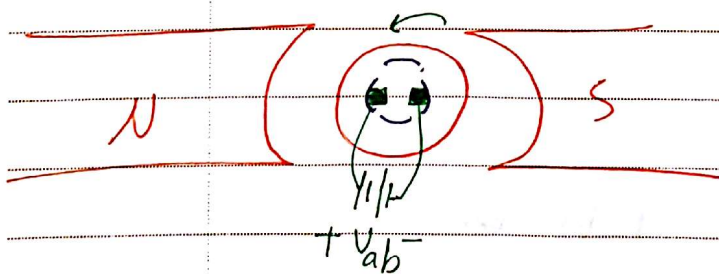- 1) reduces the voltage produced by the generator
- 2) leads to an increase in speed




when there is no load

$$\left[\begin{array}{l} I = 0 \\ V_{ab} = e_{ind} \end{array} \right]$$





$$e_{ind} = \frac{2}{\pi} \phi \omega$$

$$\uparrow \omega = \frac{e_{ind}}{\frac{2}{\pi} \phi}$$

② $L \frac{di}{dt}$ voltages

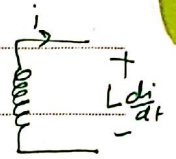
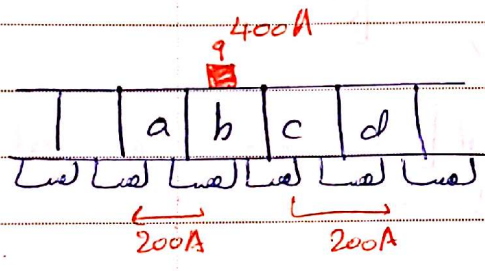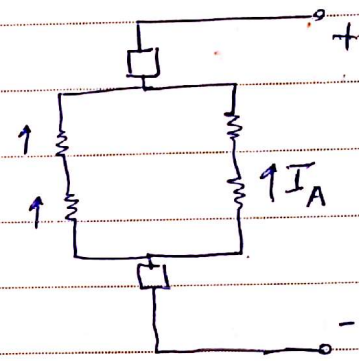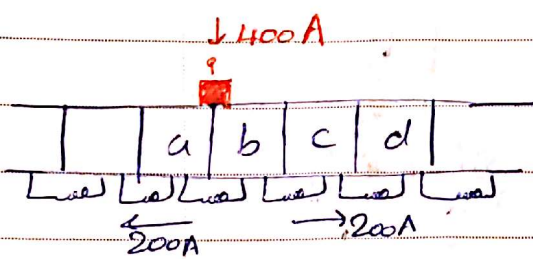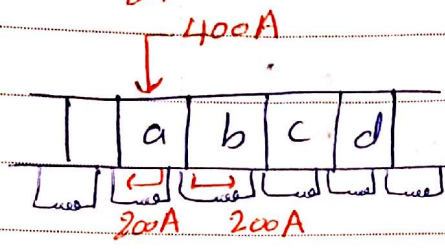
$$\infty \leftarrow V = L \frac{\Delta I}{\Delta t} \rightarrow \text{Zero}$$



DC machine running at 800 rpm and it has 50 Comm segments

$$\frac{800}{60} = 13.3 \text{ r per sec}$$


$$t = \frac{d}{\text{speed}} = \frac{1/50}{13.3} = 0.00155$$

$L * \frac{\Delta I}{\Delta t} = \frac{400}{0.0015} = 266667 \text{ A/s} \Rightarrow$ we will get a very large number
 \Rightarrow so there will be sparking and arcing



5/7/2017

1) Solution for neutral plane shift

→ Brush shift → X

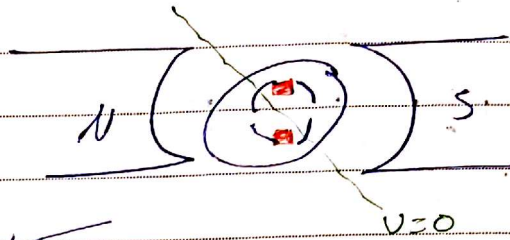


→ Commutating poles or inter poles →

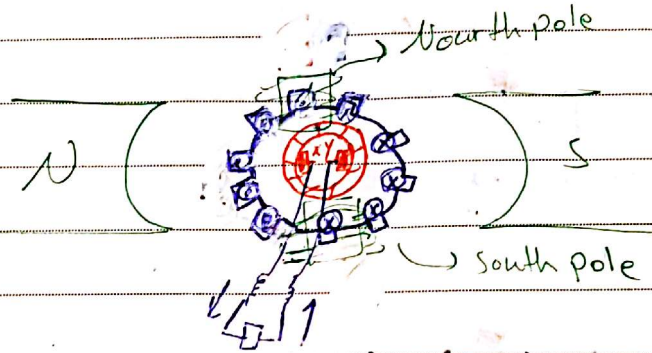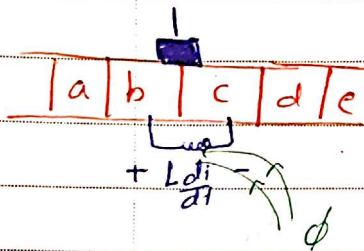


- * There won't be sparking on the brush if the voltage induced from the interpole equals and opposite the voltage $L \frac{di}{dt}$
- * The interpoles must be connected in series with the armature circuit.
- * The interpoles produce a tiny flux that won't affect the main flux.
- * The interpoles must be of the same polarity as the next upcoming main pole in a generator.
- * Interpoles must be of the same polarity as the previous main pole in a motor.
- * This solution can be done at low cost
- * Flux weakening problem still exist


No. _____

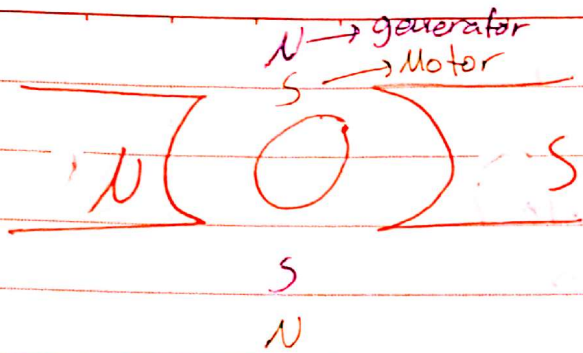

[2] Compensating winding.

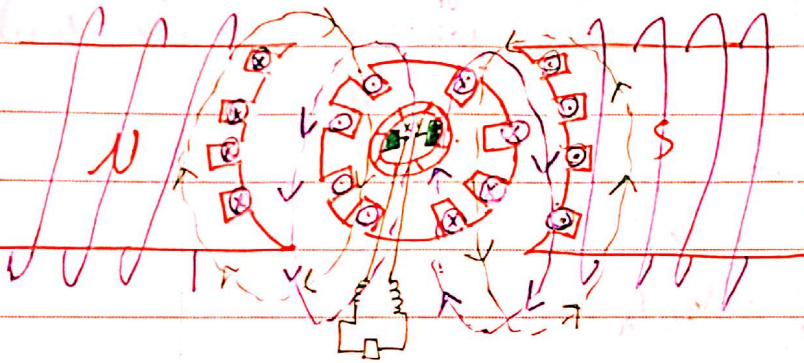

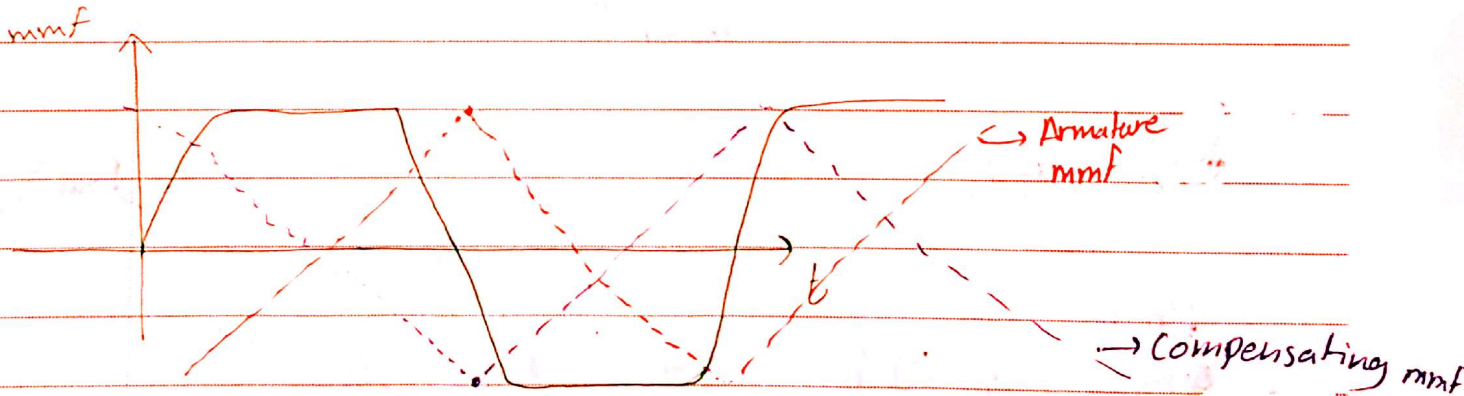
This solves phase shift and flux weakening




* The blue and the red one will cancel each other.

* Power flow and losses in Dc machines
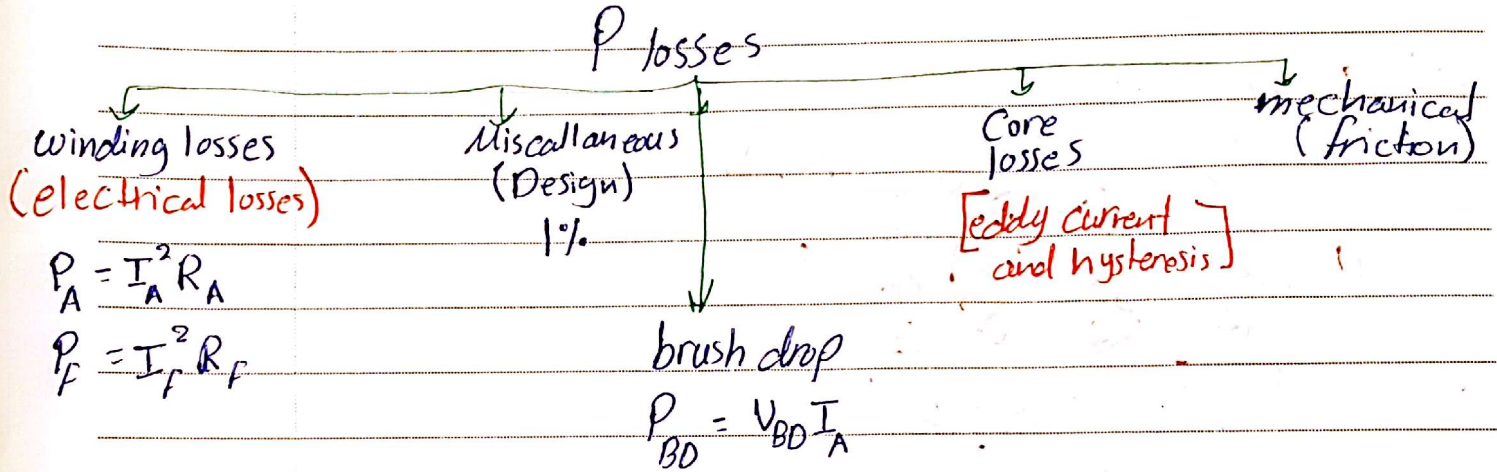
$$\eta = \frac{P_{out}}{P_{in}} \times 100\% = \frac{P_{out}}{P_{out} + P_{losses}} \times 100\%$$



" motor "

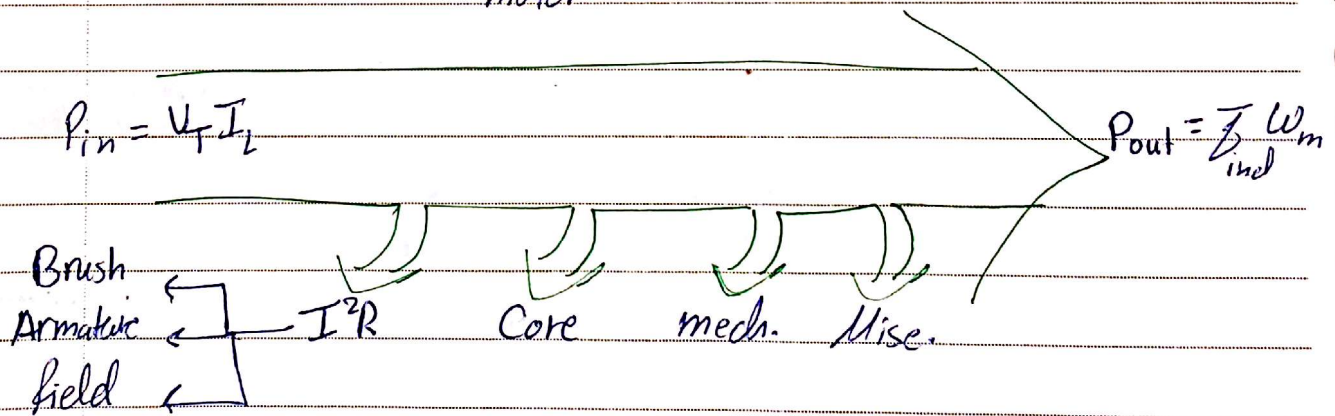


"chapter 8"

No. _____


DC machines

"Seperately excited Dc machine"

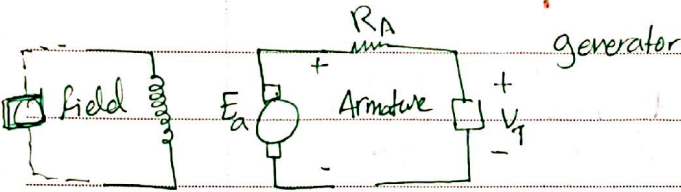[field winding is supplied by an external source]




"Permanant magnet"

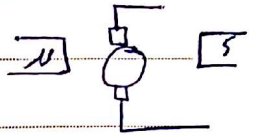


"Self excited Dc machine"

Shunt

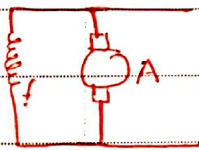


Seires

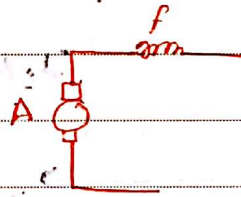


Compound


Comulative Compound

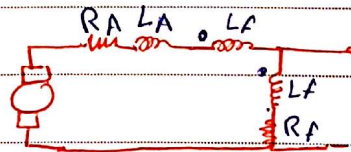


differential Compound

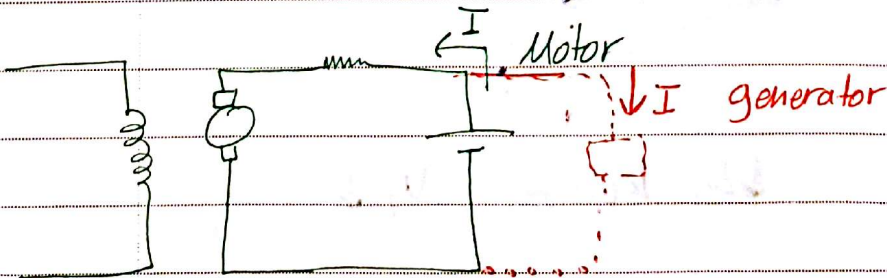

In general :-

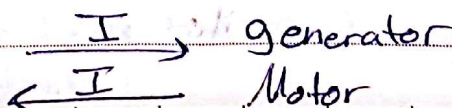

* Separately excited DC (generator)

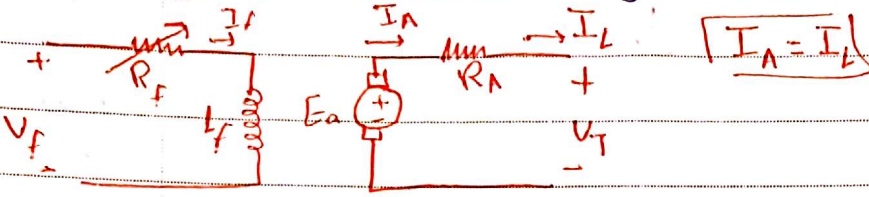

$$I_a = I_L$$


$$I_f = \frac{V_f}{R_f}$$

field voltage
field external resistance


field current

$$V_T = E_a - I_a R_a$$

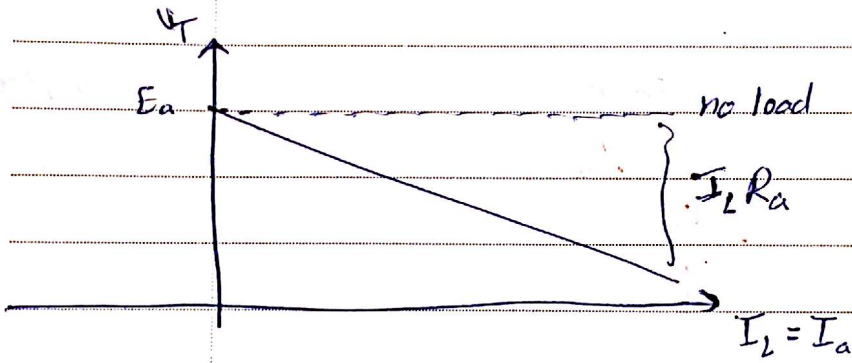terminal voltage applied to load
internal generated voltage
Armature



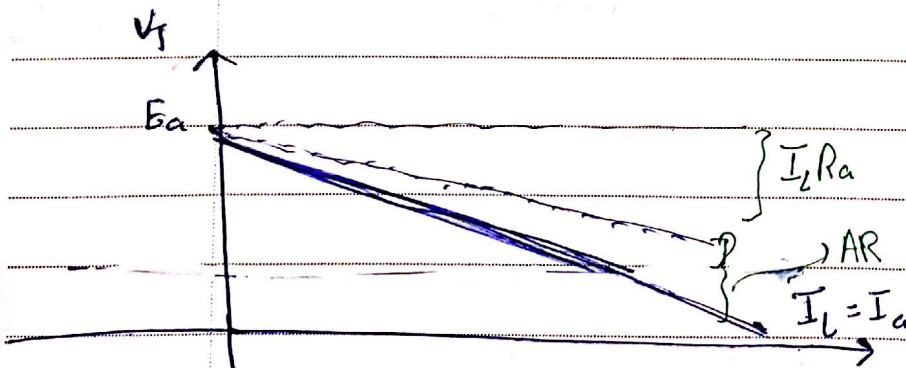" For a Compensated DC machine [no armature reaction]"



$I_a \uparrow$ $AR \uparrow$ $\phi \downarrow$ $E_a = k \phi \omega_m$ $V_T \downarrow$



" DC Separated excited machine with no Compensating winding"

6/7/2017


* The terminal voltage of a DC sep. excited generator can be controlled by :-

$$V_T = E_a - I_a R_a = k\phi\omega - I_a R_a$$

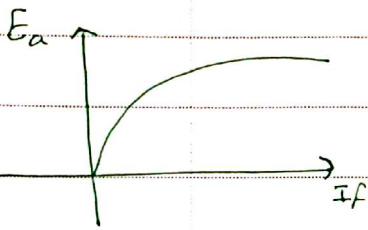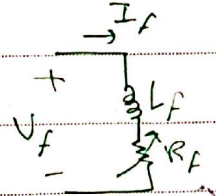- ① increase the speed of rotation
- ② decrease the field winding resistance





The DC shunt generator :-

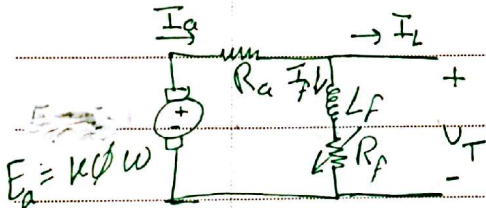

$$V_T = E_a - I_a R_a$$

$$I_a = I_L + I_f$$

$$I_f = \frac{V_T}{R_f}$$

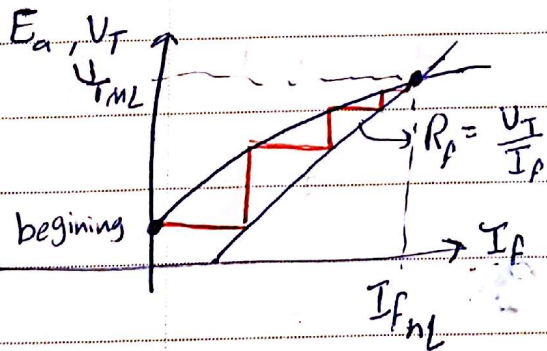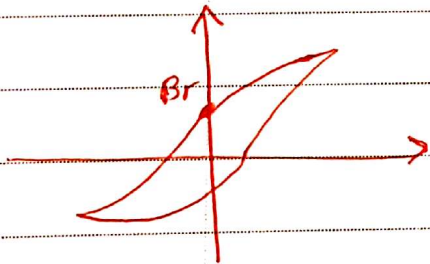


At the beginning $E_a = k\phi_{res}\omega$

problems 8-


① if there is $B_r \rightarrow$ there is no E_a
 \Rightarrow We need an external source. [Flashing the field].

② critical resistance 8-

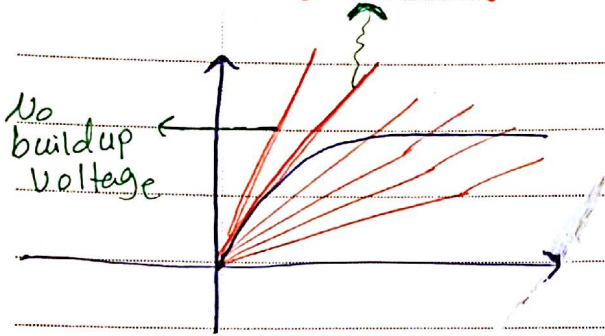


if $R_p > R_c$, there will be no buildup voltage.

③ Reverse the direction of rotation

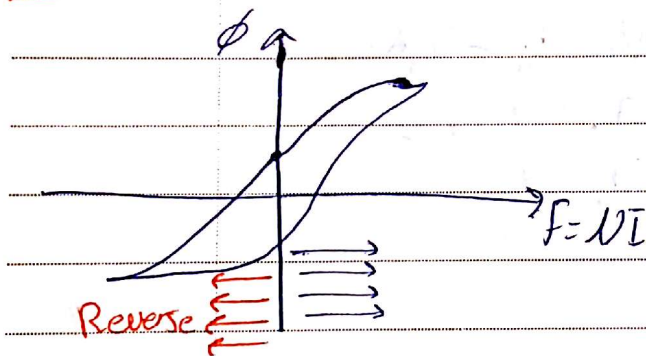

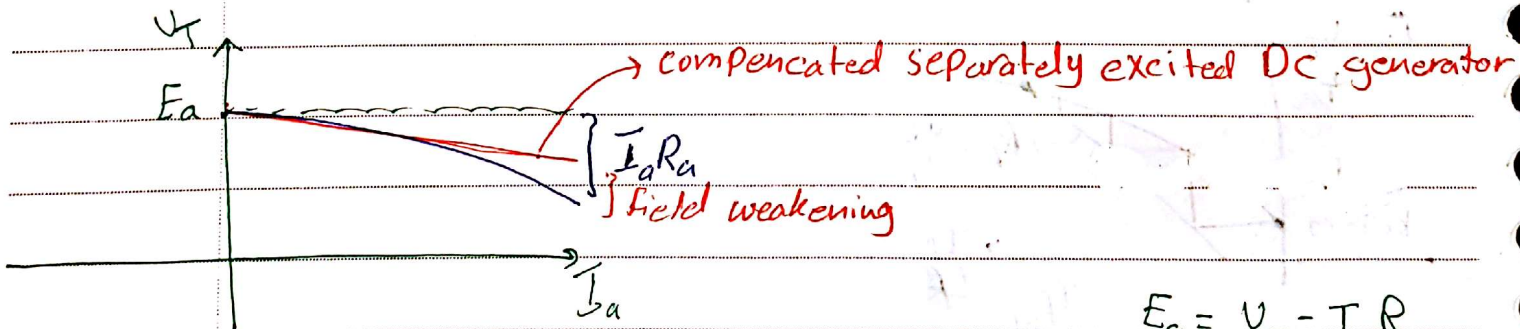no buildup voltage, we need external source.



$$E_a = V_T - I_a R_a$$

$$I_a \downarrow \rightarrow V_T \downarrow \rightarrow I_f \downarrow \rightarrow \phi \downarrow \rightarrow E_a \downarrow \rightarrow V_T \downarrow$$


$$V_T = I_f R_f$$

$V_R = \frac{E_a - V_T}{V_T}$, VR in short is worse than "Compensated Separated excited DC generator"

How to control V_T

$E_a = k \phi \omega$
 increase ϕ \rightarrow increase
 by changing R_f
 "decrease R_f "


* The DC Series generator :-

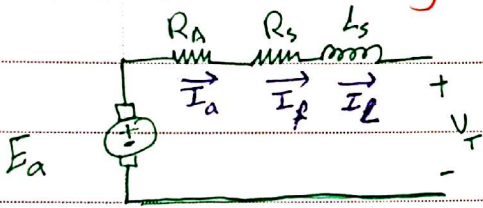

$$I_a = I_f = I_L$$

$$V_T = E_a - I_a (R_a + R_s)$$

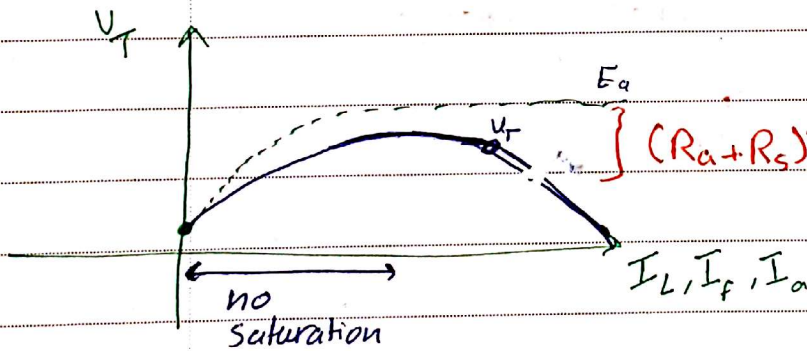
" R_s "; few turns with heavy wire \rightarrow should tolerate load current, don't make voltage drop.



$$V_T = E_a - I_a (R_s + R_a)$$


load $\rightarrow I_a \uparrow \rightarrow I_f \uparrow \rightarrow E_a \uparrow$ this one goes first

welding machines :-

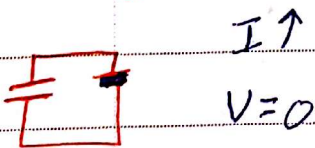

No. _____

* Cummutively Compound Dc generator :-

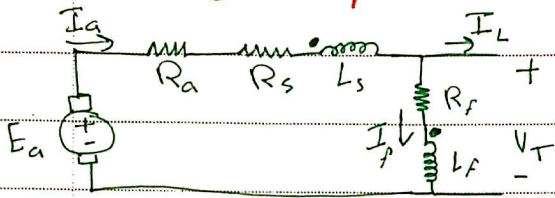

$$I_a = I_L + I_f$$

$$V_T = E_a - I_a (R_s + R_a)$$

$$V_T = I_f R_f$$

$$f_{net} = f_{SE} + f_f - f_{AR}$$

$$\downarrow V_T = E_a - \uparrow I_a (R_a + R_s)$$

① load increase $\rightarrow I_L \uparrow \rightarrow I_a \uparrow \rightarrow V_T \downarrow$

② load increase $\rightarrow I_L \uparrow \rightarrow I_a \uparrow \rightarrow f_{SE} = \frac{I_a}{3} N_s \uparrow \rightarrow E_a \uparrow \rightarrow V_T \uparrow$


8/7/2017

How to Control DC Compound generator :-

→ $\omega \uparrow$

→ $I_a \uparrow$ by $R_f \downarrow$

* Differentially compound DC generator.

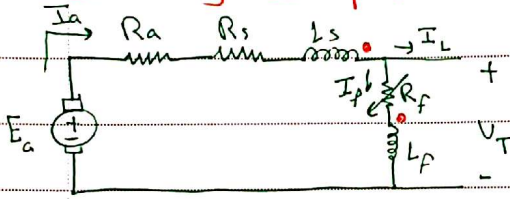

$$I_a = I_L + I_f$$

$$V_T = E_a - I_a(R_s + R_a)$$


$$V_T = I_f R_f$$

$$F_{net} = F_f - F_{SE} - F_{AR}$$


$$V_T = E_a - I_a(R_s + R_a)$$

① $I_L \uparrow \rightarrow I_a \uparrow \rightarrow V_T \downarrow$

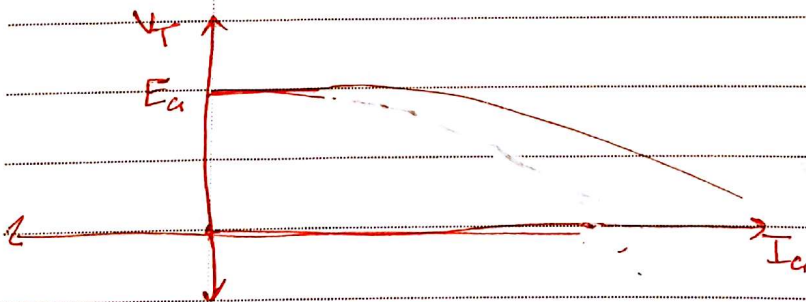② $I_L \uparrow \rightarrow I_a \uparrow \rightarrow \uparrow F_{SE} = N_{SE} I_a \rightarrow \downarrow F_{net} \rightarrow E_a \downarrow \rightarrow \downarrow V_T$




How to Control it? → ω → ϕ [F_f]

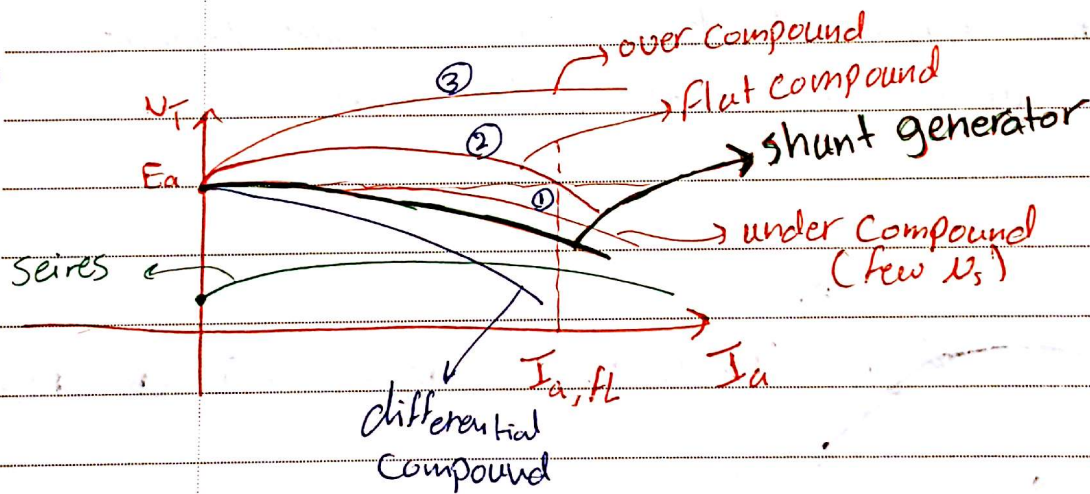


- N_s winding

①	few	⇒ under compound.
②	more	⇒ flat compound.
③	more and more	⇒ over compound.

Eg ckt for a Dc Motor :-

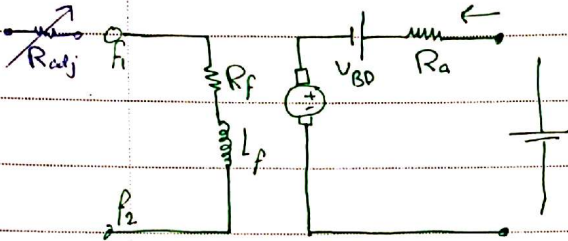

Simplified circuit :-

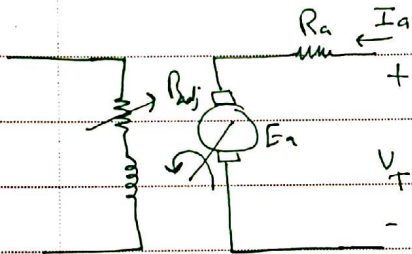


Dc motors types :-

- Separately excited
 - shunt
 - Series
 - permanent magnet
 - Compound
- > the same


↳ internal generated voltage

$$E_a = k \phi \omega_m$$
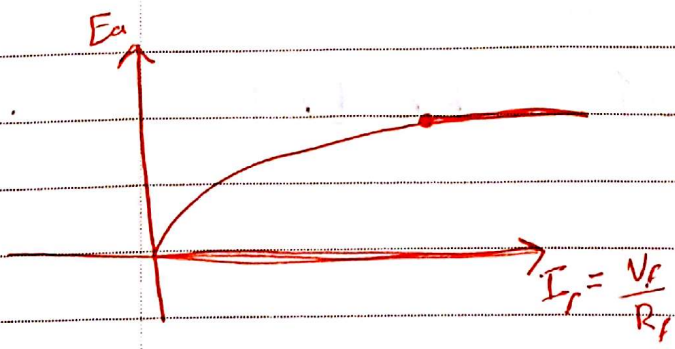
$$T_{ind} = k \phi I_a \quad / \quad T_{load}$$



1] Separately excited DC motor :-

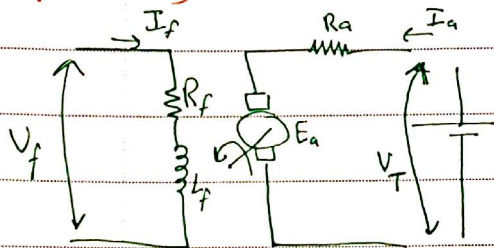


$$I_f = \frac{V_f}{R_f} \quad , \quad V_T = E_a + I_a R_a$$

$$E_a = k \phi \omega_m$$

$$T_{ind} = k \phi I_a$$

2] Shunt DC motor :-

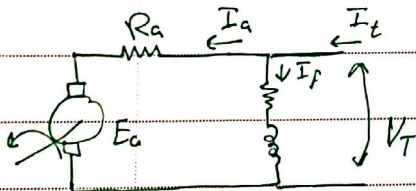

$$E_a = k \phi \omega_m$$


$$T_{ind} = k \phi I_a$$

$$I_f = \frac{V_T}{R_f}$$

$$I_t = I_f + I_a$$

$$V_T = E_a + I_a R_a$$

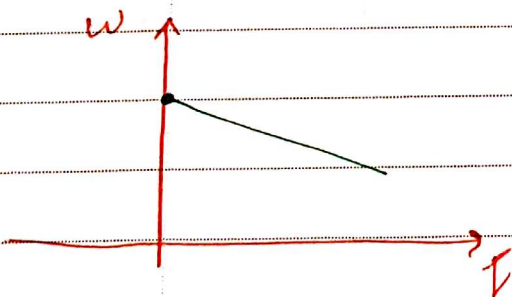Note :- for a generator \rightarrow external characteristics are (V_T, I_a)
 for motors \rightarrow external characteristics are (ω, T)



$$V_T = E_a + I_a R_a = k \phi \omega_m + \frac{T}{k \phi} R_a$$

$$\omega = \frac{V_T}{k \phi} - \frac{R_a T_{ind}}{(k \phi)^2}$$

Before $[T_{load} = T_{ind}]$


load $\uparrow \rightarrow T_{load} > T_{ind}$

$\omega \downarrow \rightarrow E_a = k \phi \omega$

$$\uparrow I_a = \frac{V_T - E_a}{R_a}$$

$$\uparrow T_{ind} = k \phi I_a$$


$T_{load} = T_{ind}$, but at lower mechanical speed.

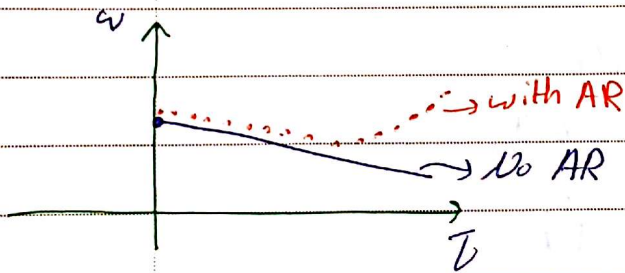

Example 8.1 :-

A 50 Hp ($1 \text{ Hp} = 746 \text{ W}$), 250 V, 1200 rpm Dc shunt motor with compensating winding. with $R_a = 0.06 \Omega$. its field circuit has $R_f = 50$ which produces a no load speed of 1200 rpm. The shunt field winding has 1200 turns per pole.

- (A) Find motor speed when input current is 100 A
 (B) when input current = 200 A
 (C) $I_f = 300 \text{ A}$

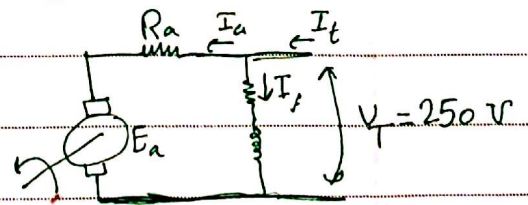

Solution 8- $E_{a1} = k\phi\omega$

$$\frac{E_{a1}}{E_{a2}} = \frac{\omega_1}{\omega_2} = \frac{n_1}{n_2}$$

$$n_2 = \frac{E_{a2}}{E_{a1}} n_1$$

At no load 8- $V_T = E_a = 250$
 $n = 1200 \text{ rpm}$

① $I_t = 100 \text{ A}$

$$I_a = I_t - I_f = 100 - \frac{250}{50} = 95 \text{ A}$$

$$E_a = V_T - R_a I_a = 250 - 95(0.06) = 244.3 \text{ V}$$

$$n_2 = \frac{244.3}{250} \times 1200 = 1173 \text{ rpm}$$

$$E_{a1} = 250 \rightarrow 1200 \text{ rpm}$$

$$E_{a2} = 244.3 \rightarrow 1173 \text{ rpm}$$

② $I_t = 200$

$$I_a = 195$$

$$E_{a3} = 250 - 0.06(195) = 238.3$$


$$n_3 = \frac{238.3}{250} \times 1200 = 1144 \text{ rpm}$$

③ $I_t = 300$

$$I_a = 295$$

$$E_{a4} = 250 - 0.06 \times 295$$

$$n_4 = 1115 \text{ rpm}$$

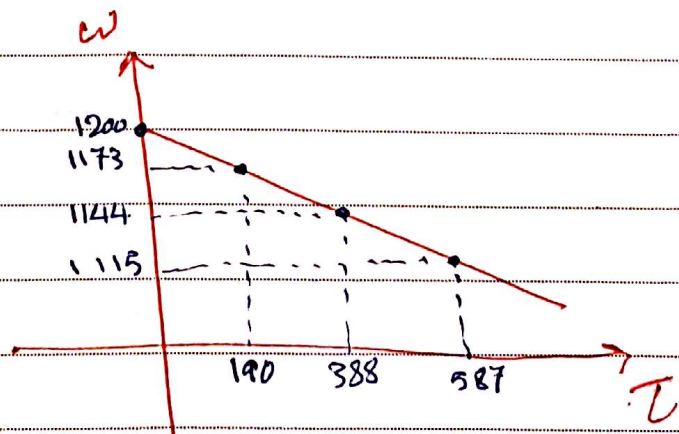

$$P = E_a I_a = T_{ind} \omega$$

$$T_{ind} = \frac{E_a I_a}{\omega}$$

$$T_2 = \frac{244.3 \times 95}{1173 \times \frac{2\pi}{60}} = 190 \text{ N.m}$$

$$T_3 = \frac{238.3 \times 195}{1144 \times \frac{2\pi}{60}} = 388 \text{ N.m}$$

$$T_4 = \frac{232.3 \times 295}{1115 \times \frac{2\pi}{60}} = 587 \text{ N.m}$$

* Speed Control :-

→ Adjusting the field (R_f)

→ Adjusting the [terminal voltage].

① Adjusting the field resistance.

① $R_f \uparrow \rightarrow I_f \downarrow$

⑤ $T_{ind} \uparrow = k \phi I_a$

② $\phi \downarrow$

③ $E_a \downarrow = k \phi \omega$

⑥ $T_{ind} > T_{load}$

④ $I_a \uparrow = \frac{V_t - E_a}{R_a}$


⑦ $\omega \uparrow$

⑧ $\uparrow E_a = k \phi \omega$

⑨ $I_a \downarrow$

⑩ $T_{ind} = T_{load}$ / at higher speed

Example 8-

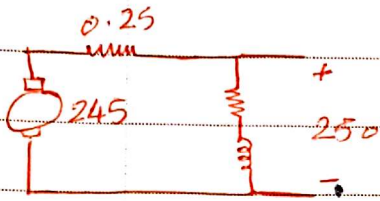



$$I_a = \frac{250 - 245}{0.25} = 20 \text{ A}$$

* $\phi \downarrow 1\% \rightarrow E_a = k\phi\omega \rightarrow E_a \downarrow 1\%$

$$E'_a = 245 - 0.01 \times 245 = 242.55$$

$$I'_a = \frac{250 - 242.55}{0.25} = 29.8 \text{ (49\%)} \quad \frac{29.8 - 20}{20} = 49\%$$

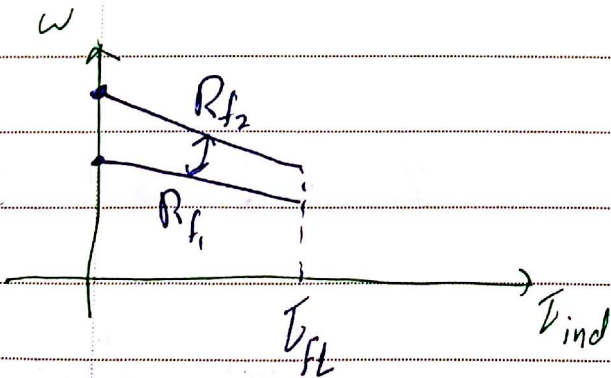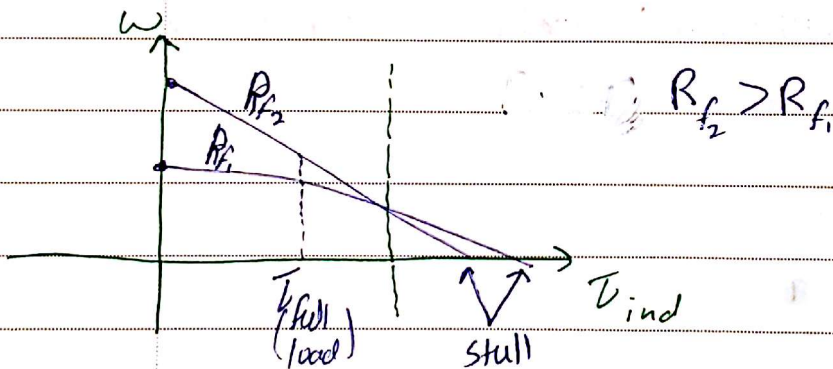* $T_{ind} = k\phi I$; I_a increase dominate ϕ decrease.




Explanations :-

(I doesn't dominate)


$$① T_{ind} = k \phi I_a$$

$$② \omega = \frac{V_T}{k\phi} - \frac{R_a}{(k\phi)^2} T_{ind}$$

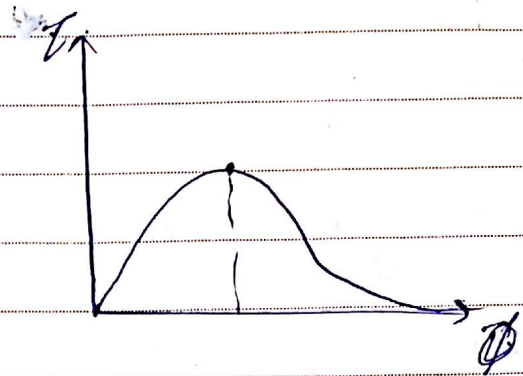
$$\omega = \frac{\alpha}{x} - \frac{\beta}{x^2}$$



II changing the armature voltage.

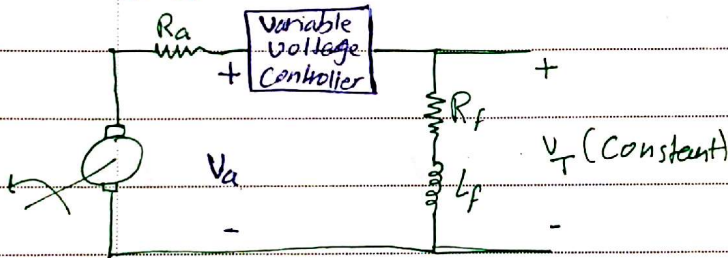

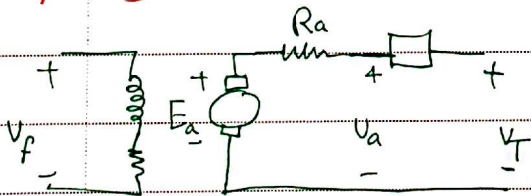⇒ to maintain voltage stability, this technique is used for separately excited DC motors.



$$① V_a \uparrow \rightarrow I_a \uparrow = \frac{V_a - E_a}{R_a}$$

$$② I_a \uparrow \rightarrow T_{ind} \uparrow = k \phi I_a$$


$$③ T_{ind} > T_{load}$$

$$④ \uparrow E_a = k \phi \omega \uparrow$$


$$⑤ \downarrow I_a = \frac{V_a - E_a}{R_a}$$

$$⑥ I_a \downarrow \rightarrow T_{ind} \downarrow$$

$T_{ind} = T_{load}$
at higher ω


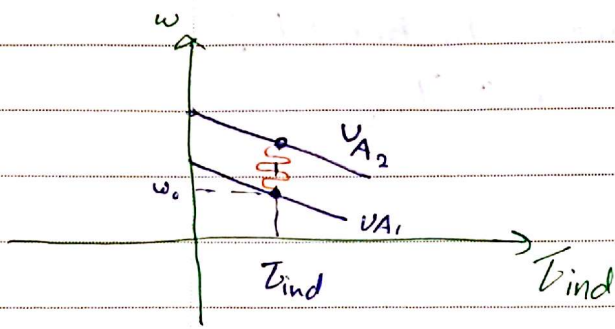


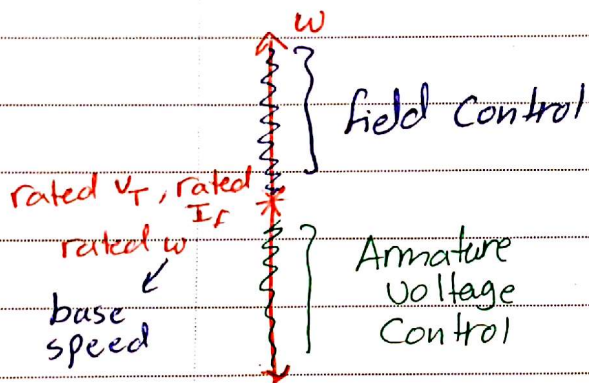- They are parallel, the slope doesn't change.
- these two methods have different safe ranges of operations.
- those methods are complementary



* if we used field control to make "ω" lower, the wire could burn because I_a increases to a very high value.

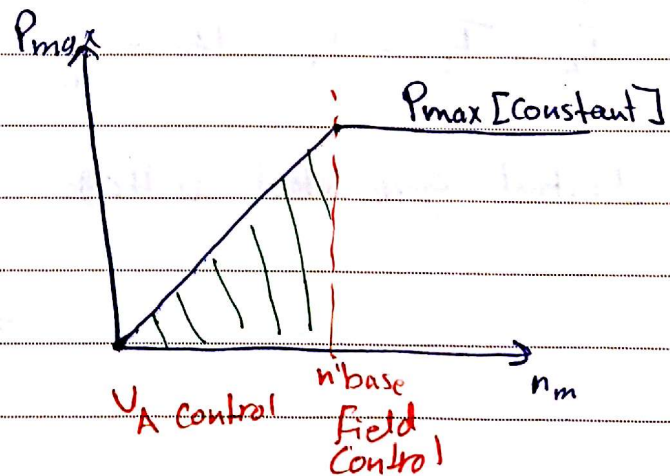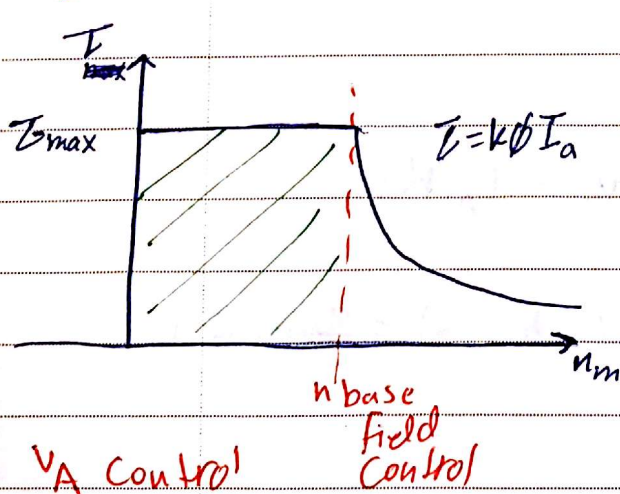⇒ shunt motors have excellent speed control characteristics.



$$P_{max} = T_{max} \omega$$

The limiting factor is Armature winding heating [I_a]


$$E_{ind} = k \phi I_a$$

$$E_{ind \text{ max}} = k \phi I_{a \text{ (max)}}$$

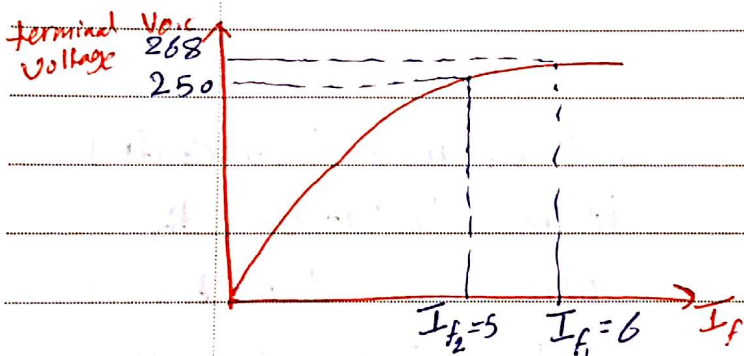Example 8.3 :-

100 hp, 250 v, 1200 rpm, DC shunt motor with $R_a = 0.03 \Omega$ and $R_f = 41.67 \Omega$. No AR. The motor is driving a load with a line current 126 A [I_t], and initial speed of 1103 rpm.

Assume that I_a is constant and magnetization curve is as follows



① What is the motor speed if the field resistance is increased to 50Ω :-

I_{A_1} → before increasing R_f to 50Ω

$$I_{A_1} = I_t - I_f = 126 - \frac{250}{41.67} = 120 \text{ A}$$

$$\text{Initial generated voltage} = E_{A_1} = V_T - I_{A_1} R_a$$

$$= 250 - (120)(0.03) = 246.4 \text{ V}$$

$$I_{A_2} = I_t - I_{f_2} = 126 - \frac{250}{50} = 121 \text{ A}$$

$$E_{A_2} = V_T - I_{A_2} R_a = 250 - (121)(0.03) = 246.37 \text{ V}$$

$$\frac{E_{A_1}}{E_{A_2}} = \frac{k \phi_1 n_1}{k \phi_2 n_2}$$


$$E_{A_1} \approx E_{A_2}$$

$$n_2 = \frac{\phi_1}{\phi_2} n_1 = \frac{268}{250} \times 1103 = 1187 \text{ rpm}$$

$$\phi(I_{f_1} = 6) = 268$$

$$\phi(I_{f_2} = 5) = 250$$

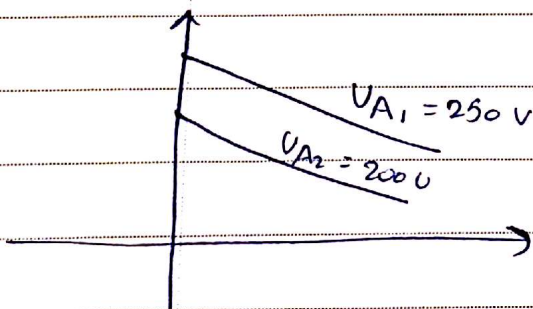② If the motor, then, is connected as separately excited DC motor and it is initially running at $V_A = 250 \text{ V}$, $I_a = 120 \text{ A}$, $n = 1103 \text{ rpm}$, while supplying a constant torque load, find the motor speed if $V_A = 200 \text{ V}$



$$\frac{E_{A_2}}{E_{A_1}} = \frac{k \phi_2 n_2}{k \phi_1 n_1}$$

$$E_{A_1} = V_A - I_a R_a = 250 - (120)(0.03)$$

$$E_{A_2} = 200 - (120)(0.03)$$

$$n_2 = \frac{E_{A_2}}{E_{A_1}} n_1 = \frac{200 - (120 \times 0.03)}{250 - (120 \times 0.03)} \times 1103 = 879 \text{ rpm}$$

No. _____

→ what happens if there is an open circuit in the field winding in a shunt or separately excited DC motor.

$$\omega = \frac{V_T}{k\phi} - \frac{R_a}{(k\phi)^2} I_{ind}$$

runway
motor
(when $\phi=0 \rightarrow \omega=\infty$)

We need a solution
[braking]

→ If the motor is not comp

AR → weakening the field

$\omega \uparrow \rightarrow$ load increase $\rightarrow I_a \uparrow \rightarrow AR \uparrow \rightarrow \omega \uparrow \uparrow \uparrow$

braking

9/7/2017

No. _____

* the previous example (a better solution)

$$E_{a2} = V_T - I_{A2} R_a$$


$$\frac{E_2}{E_1} = \frac{k \phi_2 I_{a2}}{k \phi_1 I_{a1}}$$

I_{load} is constant then $\frac{E_2}{E_1} = 1$

$$\Rightarrow 1 = \frac{I_{f2} I_{a2}}{I_{f1} I_{a1}}$$

$$I_{a2} = 144 \text{ A}$$

$$E_{a2} = 250 - (144)(0.03) = 245.7$$

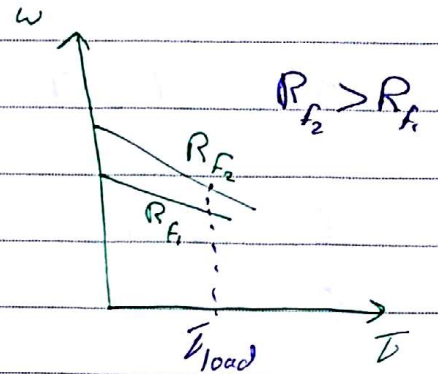

$$\frac{245.7}{246.4} = \frac{6}{5} \frac{n_2}{1103}$$


$$n_2 = 1320 \text{ rpm}$$

* Permanent magnet Dc motor 3- advantages :-

- 1] No field circuit copper losses.
- 2] The structure is smaller in size.


disadvantages :-

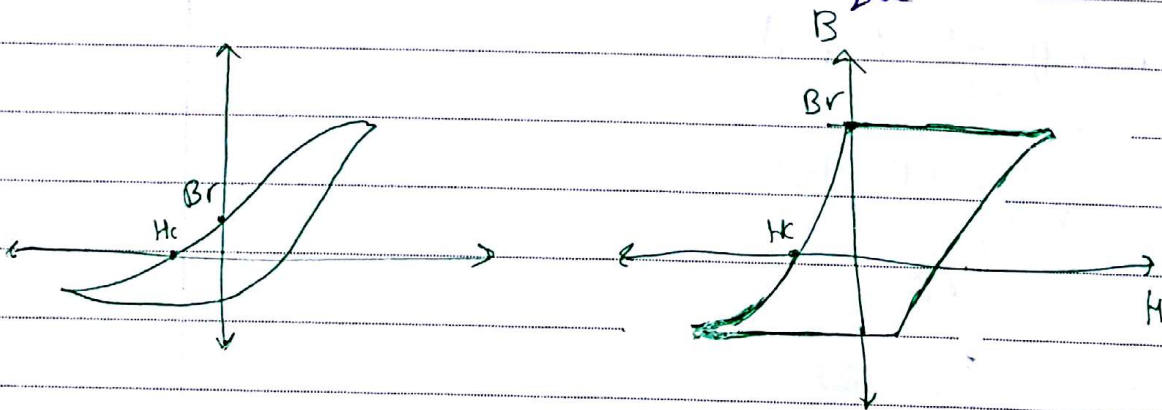- 1] There is always a risk of demagnetization due to heat AR.
- 2] produce weaker flux → less induced torque



"for permanent magnet"

* The series Dc motor

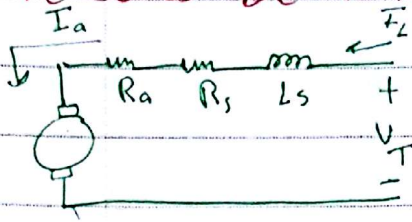

$$I_L = I_a = I_s$$

$$V_T = E_a + I_a (R_a + R_f)$$

$$T_{ind} = k \phi I_a$$

$$\phi = F(I_a)$$

$$\phi = C I_a$$

→ Constant

$T_{ind} = k C (I_a)^2$ → as T depends only on the square of I_a , we use this T in elevators. Also, ω is constant.

$$E_a = k \phi \omega$$

$$I_a = \sqrt{\frac{T_{ind}}{k C}}$$

$$V_T = E_a + I_a (R_a + R_f)$$

$$V_T = k \phi \omega + \sqrt{\frac{T_{ind}}{k C}} (R_a + R_f)$$


$$\omega = \frac{V_T}{k \phi} - \frac{\sqrt{\frac{T_{ind}}{k C}} (R_a + R_f)}{k \phi}$$

$$\phi = C I_a = C \sqrt{\frac{T_{ind}}{k C}}$$

$$\omega = \frac{V_T}{k_c \sqrt{\frac{I_{ind}}{k_c}}} - \sqrt{\frac{I_{ind}}{k_c}} \frac{(R_a + R_s)}{k_c \sqrt{\frac{I_{ind}}{k_c}}}$$

$$\omega = \frac{V_T}{\sqrt{k_c}} \frac{1}{\sqrt{I_{ind}}} - \frac{R_a + R_s}{k_c}$$
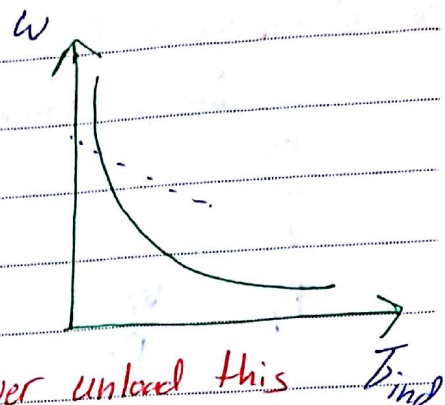
$$y = \frac{1}{\sqrt{x}} \alpha + \beta$$



Never unload this type of motors as I_{ind} goes to zero, ω goes to ∞ .

* to control the speed :-
 → change the terminal voltage.


Example 8.5 or 8.6 :-

250 V series DC motor with Compensating winding has $R_a + R_s = 0.08 \Omega$ and a series field of 25 turns per pole. Find the speed and induced torque of this motor, when it's armature current = 50 A and has 1200 rpm.

$$I_f = 50 \text{ A} \quad N = 25 \quad NI = 1250 = 25 \times 50$$

[No load condition]

$$T_{load} = 0$$

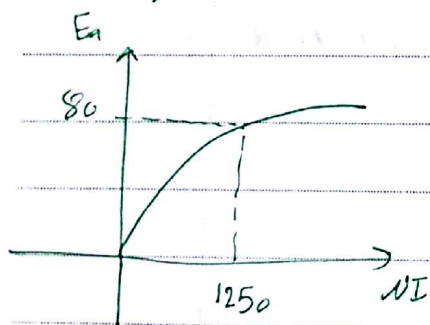


→ what happens when $I_a = 50$?

$$E_{a2} = V_T - I_a (R_a + R_s) = 250 - 50 \times 0.08 = 246$$

$$n_2 = \frac{E_2 n_1}{E_1} = \frac{246}{80} \times 1200 = 3690 \text{ rpm}$$

$$T_{ind} = \frac{P_{conv}}{\omega} = \frac{VI}{\omega} = \frac{246 \times 50}{\frac{3690 \times 2\pi}{60}} = 31.8 \text{ N.m}$$

* Compound DC motors

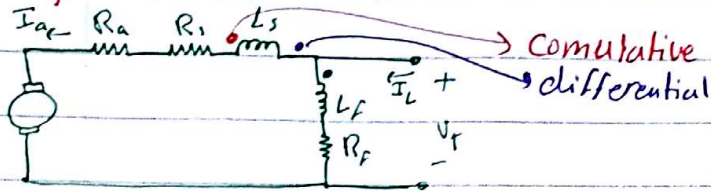

$$I_f = \frac{V_T}{R_f}$$

$$V_T = E_a + I_a (R_a + R_s)$$


$$I_L = I_a + I_f$$

$$F_{net} = F_f \pm F_{SE} - F_{AR}$$


→ Cumulative
→ differential

$$V_T = k\phi\omega + \frac{T_{ind}}{k\phi} (R_a + R_s)$$
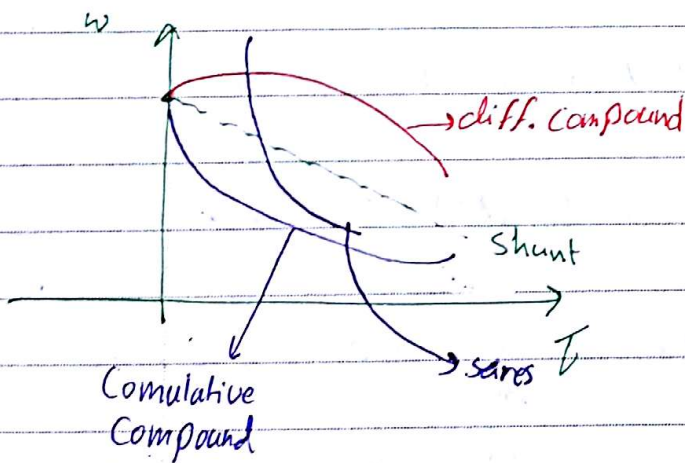
$$\omega = \frac{V_T}{k\phi} - \frac{(R_a + R_s)}{(k\phi)^2} T_{ind} \quad \left[\text{just like shunt motor} \right]$$



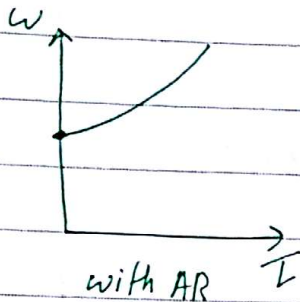DC cliff compound motors are not recognized internationally as stable motors



$$I \uparrow \rightarrow I_a \uparrow \rightarrow AR \uparrow$$

How to control it ?!

① field

② terminal voltage controller

$$I_f = \frac{V_T}{R_f} \rightarrow \begin{array}{l} \text{decrease } V_T \text{ to} \\ \text{decrease } I_f \\ \text{increase } R_f \text{ to} \\ \text{decrease } I_f \end{array}$$

* DC motor starting

→ we need protection and control devices.

- ① protect the motor from long-term overload.
- ② protect against high starting currents.
- ③ control the speed.
- ④ protect it from equipment short circuit.

At starting the motor is not running [$n_m = 0$]

$$\rightarrow E_a = 0$$

→ R_a is very low


$$I_a = \frac{V_T - E_a}{R_a} = \frac{V_T}{R_a}$$

ex) 50 hp, 250v Dc motor with $R_a = 0.06$, $I_a = 200A$ is the rated armature current.

$$I_{a(\text{start})} = \frac{250}{0.06} = \underline{\underline{4167 A}}$$


very high value

at starting :-

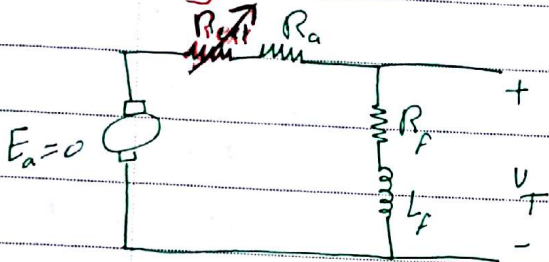


Solution :- ① R_{ext}
 ② V_T

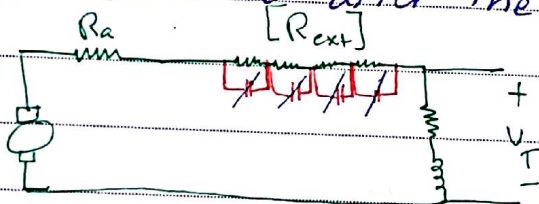R_{ext} must be removed after the motor runs on its rated speed.



10/10/2017

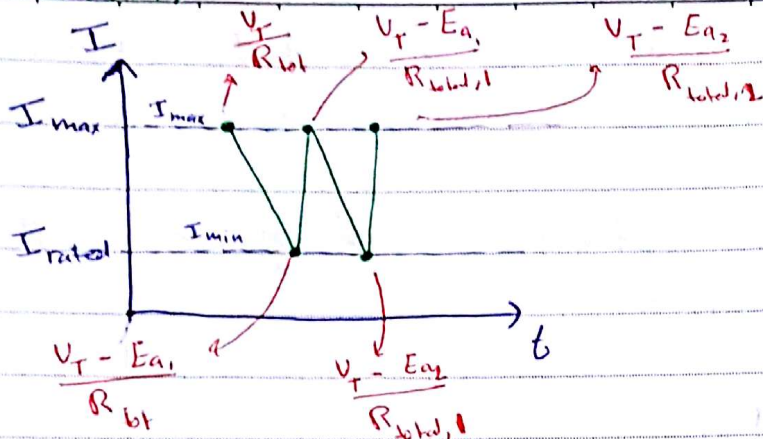

$$R_{bt,1} = R_a + R_2 + R_3 + R_4 \quad R_{tot,2} = R_a + R_3 + R_4$$

$$\rightarrow I_{min} R_{bt} = I_{max} R_{tot,1} = V_T - E_{a1}$$

$$R_{bt,1} = \frac{I_{min}}{I_{max}} R_{tot}$$

$$\rightarrow I_{min} R_{tot,1} = V_T - E_{a2} = I_{max} R_{tot,2}$$

$$R_{tot,1} = \frac{I_{max}}{I_{min}} R_{tot,2}$$

$$\frac{I_{max}}{I_{min}} R_{tot,2} = \frac{I_{min}}{I_{max}} R_{tot}$$

$$R_{tot,2} = \left(\frac{I_{min}}{I_{max}} \right)^2 R_{tot}$$

$$R_{tot,n} = \left(\frac{I_{min}}{I_{max}} \right)^n R_{tot}$$

(ex) 8- 100hp, 250V, 350A, shunt Dc motor with $R_a = 0.05 \Omega$, needs a starter, that will limit the max starting current ($I_r \times 2$) = 700

A) How many stages (n) of starting R will be required to limit the current to the value specified.


$$R_a \leftarrow R_{tot/n} = \left(\frac{I_{min}}{I_{max}} \right)^n R_{tot}$$

$$\frac{R_a}{R_{tot}} = \left(\frac{I_{min}}{I_{max}} \right)^n$$

$$n = \frac{\log(R_a/R_{tot})}{\log(I_{min}/I_{max})} = \frac{\log(0.05/0.357)}{\log(350/700)} = 2.85 \quad \text{Always round up} \\ \approx 3$$

$$R_T = \frac{V_T}{I_{max}} = \frac{250}{700} = 0.357$$

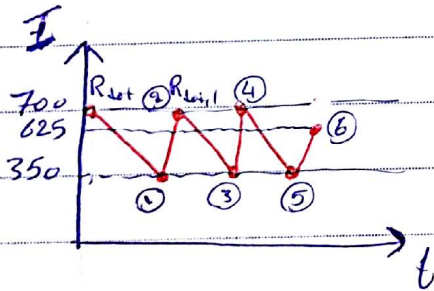B) what is the value of each segment and when (I) have to cut it out.



$$\textcircled{1} I_{min} = \frac{V_T - E_a}{R_{tot}}$$

$$\textcircled{2} R_{tot/1} = \frac{250 - 125}{700} = 0.1786 \Omega$$

$$E_a = V_T - I_{min}(R_{tot}) \\ = 250 - (350)(0.357) = 125 \text{ V}$$

$$\textcircled{3} \quad V_T - E_{a_2} = R_{\text{tot},1} (I_{\text{min}})$$

$$E_{a_2} = 187.5 \text{ V}$$

$$\textcircled{4} \quad R_{\text{tot},2} = \frac{250 - 187.5}{700} = 0.0893 \Omega$$

$$\textcircled{5} \quad E_{a_3} = V_T - I_{\text{min}} (R_{\text{tot},2})$$

$$= 250 - (350)(0.0893)$$

$$= 218.75 \Omega$$

$\textcircled{6}$ When R_3 is disconnected, only R_a exist.

$$I_a = \frac{250 - 218.75}{0.05} = 625 \text{ A}$$

$$R_3 = R_{\text{tot},2} - R_a = 0.0393$$

$$R_2 = R_{\text{tot},1} - R_a - R_3 = 0.1786 - 0.05 - 0.0393 = 0.0893 \Omega$$

$$R_1 = R_{\text{tot}} - R_a - R_2 - R_3 = 0.1786 \Omega$$


disconnect $\Rightarrow R_1$ when $E_a = 125$

R_2 when $E_a = 187.5$

R_3 when $E_a = 218.75$

No.

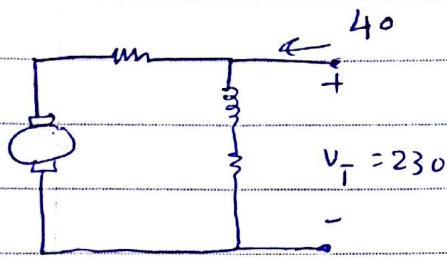(ex) :- A 12 hp, 230 v Shunt motor takes full load current = 40 A. The armature and field windings are 0.25 and 230 Ω resp. The total brush contact drop $V_{BD} = 2$, and core and friction losses = 380 w, calculate the efficiency of the motor.



$$P_{in} = 230 \times 40 = 9200 \text{ W}$$

$$I_f = \frac{V_T}{R_f} = \frac{230}{230} = 1 \text{ A}$$

$$I_a = 39 \text{ A}$$

$$E_a = V_T - I_a(R_a) - V_{BD} = 230 - (39 \times 0.25) - 2 = 218.25 \text{ V}$$


$$P_{out} = E_a I_a - P_{c+f} = 218.25 \times 39 - 380 = 8131.75$$

$$\eta = \frac{P_{out}}{P_{in}} \times 100\% = \frac{8131.75}{9200} \times 100\% = 88.39\%$$

(ex) 8. 230V shunt motor has $R_a = 0.05 \Omega$, $R_f = 75 \Omega$, the motor draws 7 A of line current while running at 1120 rpm.

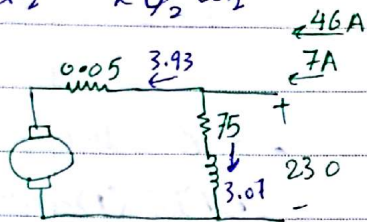A) What is the motor speed when it is loaded and $I_f = 4.6 \text{ A}$

$$\frac{E_{a1}}{E_{a2}} = \frac{k \phi_1 \omega_1}{k \phi_2 \omega_2} \quad [\phi_1 = \phi_2]$$



$$I_f = \frac{230}{75} = 3.07$$

$$E_{a1} = 230 - (0.05)(3.93)$$

$$E_{a2} = 230 - (0.05)(42.93)$$

$$\frac{E_{a1}}{E_{a2}} = \frac{n_1}{n_2} = \frac{229.8}{227.85} = \frac{1120}{n_2}$$

$$n_2 = \frac{(227.85)(1120)}{229.8} = 1110.5 \text{ rpm}$$

B) At this load, if the field circuit $R = 100 \Omega$, what is the new speed of the motor.

$$\frac{E_{a2}}{E_{a3}} = \frac{k \phi_2 \omega_2}{k \phi_3 \omega_3} = \frac{I_{f2} n_2}{I_{f3} n_3} \quad \Rightarrow I_{f3} = \frac{230}{100} = 2.3 \text{ A}$$

$$n_3 = I_{f2} n_2 \frac{E_{a3}}{E_{a2}} = \frac{(3.07)(1110.5)(227.815)}{229.8}$$

$$E_{a3} = 230 - I_{a3} R_a = 230 - (46 - 2.3)(0.05) = 227.815$$



$$n_3 = 1483 \text{ rpm}$$

11/7/2017

AC machines

↓
generators

↓
motors

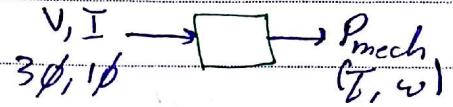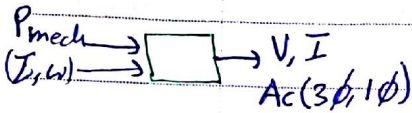

→ Synchronous


→ induction

(mainly as motors)

→ IG (Induction generator)

→ DFIG (Doubly fed induction generator)

* Synchronous machine structure :-

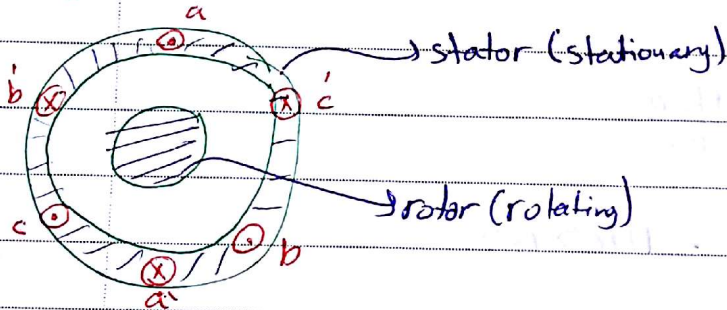

Winding


Field

Armature


[the ones that create the magnetic field]

[winding where the voltage is induced]



① slip rings and brushes

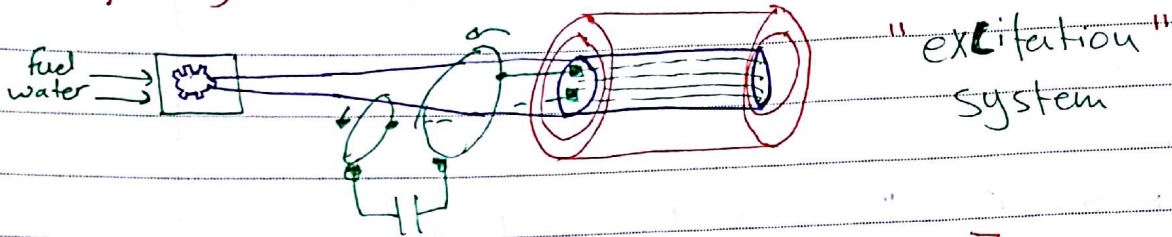

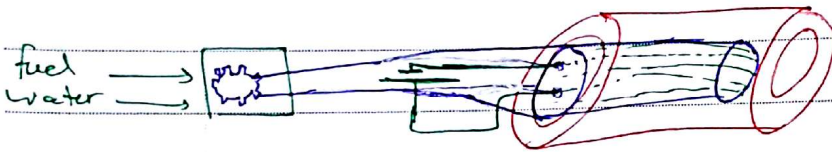② DC source [may be an AC source + rectifier] is mounted directly on the shaft



* Rotating magnetic field :-

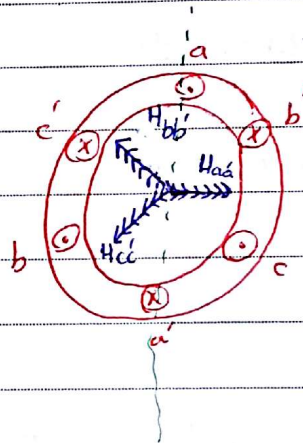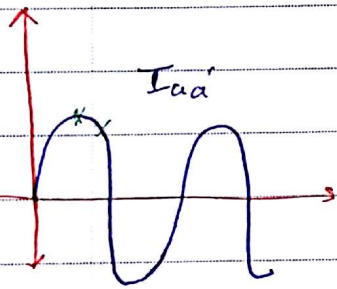

Suppose :-

$$i_{aa'} = I_m \sin \omega t$$

$$i_{bb'} = I_m \sin(\omega t - 120^\circ)$$

$$i_{cc'} = I_m \sin(\omega t + 120^\circ)$$

$$B = \mu H$$

$$H_{aa'} = H_m \sin \omega t \angle 0^\circ$$

$$H_{bb'} = H_m \sin(\omega t - 120^\circ) \angle -120^\circ$$

$$H_{cc'} = H_m \sin(\omega t + 120^\circ) \angle +120^\circ$$

$$B_{aa'} = B_m \sin(\omega t) \angle 0^\circ$$

$$B_{bb'} = B_m \sin(\omega t - 120^\circ) \angle -120^\circ$$

$$B_{cc'} = B_m \sin(\omega t + 120^\circ) \angle +120^\circ$$

$$B_{net} = B_{aa'} + B_{bb'} + B_{cc'}$$

→ $\omega t = 0$

$$B_{aa'} = 0$$

$$B_{bb'} = B_m \sin(-120) \angle 120 = -\frac{\sqrt{3}}{2} B_m [\cos 120 + j \sin 120]$$

$$B_{cc'} = B_m \sin(120) \angle -120 = \frac{\sqrt{3}}{2} B_m [\cos -120 + j \sin -120]$$

$$B_{net} = 1.5 B_m \angle -90^\circ$$


→ $\omega t = \frac{\pi}{2} = 90^\circ$

$$B_{aa'} = B_m \angle 0$$

$$B_{bb'} = B_m \sin(-30) \angle +120$$


$$B_{cc'} = B_m \sin(210) \angle -120$$

$$B_{net} = 1.5 B_m \angle 0$$

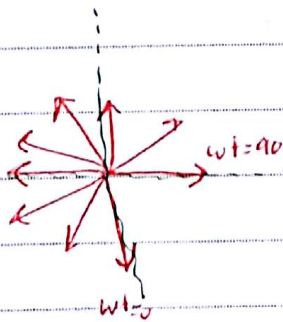

⇒ This is called rotating magnetic field


Cylindrical

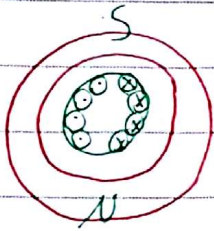

2 pole structure

* 2 or 4 poles

Salient pole

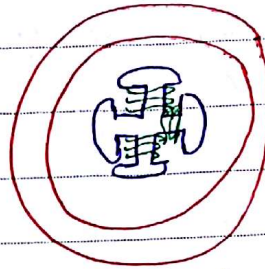


* 4 poles and up



180 electric degree

180 mech degree

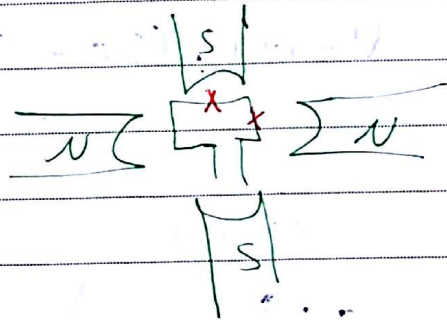

$\theta_{mech} = 90^\circ$

$\theta_e = 180^\circ$


$$\theta_e = \frac{P}{2} \theta_m$$

pole pairs $\frac{P}{2}$

12/7/2017

TR paralleling conditions :-

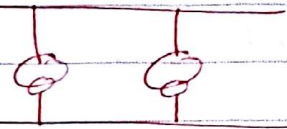
- ① Same voltage level.
- ② Same phase sequence.
- ③ Same vector group.
- ④ Same Z %.



In motors :-

$$SR \text{ (Speed regulation)} = \frac{n_{NL} - n_{FL}}{n_{FL}} \times 100\%$$

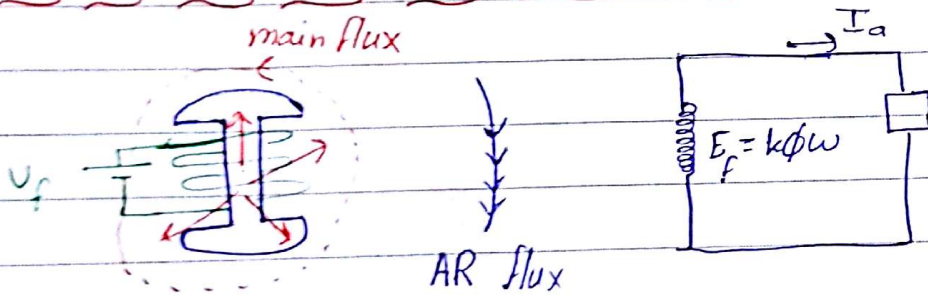Suggested problems for ch. 8 :-
(1-17), (20-23), (27)




$$\phi_g = \phi_f + \phi_s \downarrow \text{AR}$$









$$n_s = \frac{60 f}{P} \rightarrow \text{pole pairs}$$

$$E_{rms} = 4.44 f N_{ph} \phi_p k_w$$



$$k_w = k_p k_d \rightarrow \text{distribution factor}$$

pitch factor

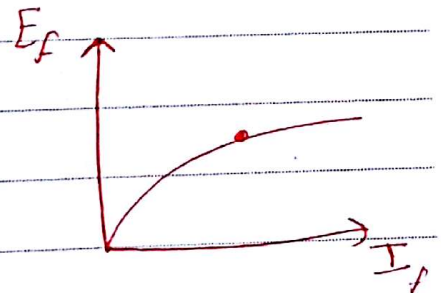

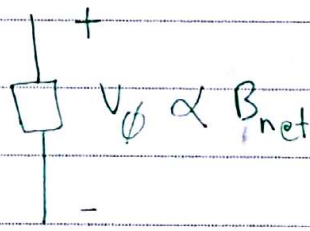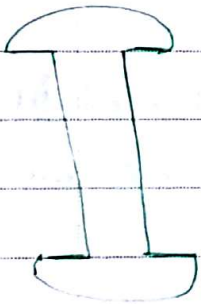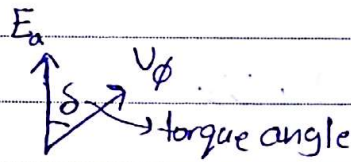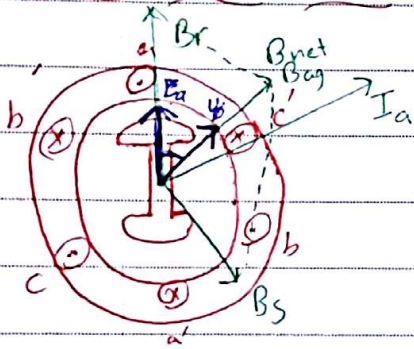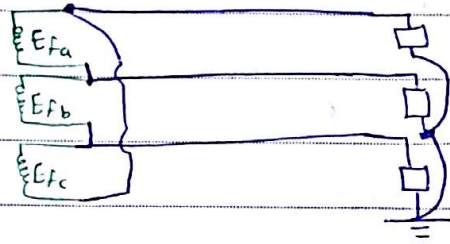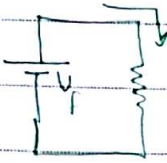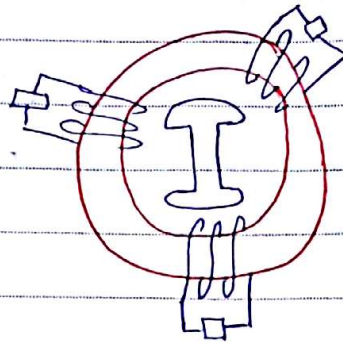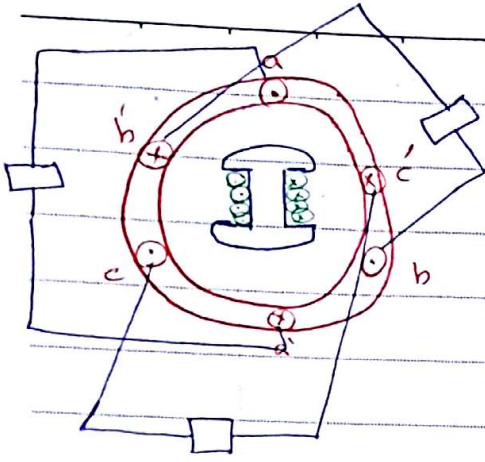


No.

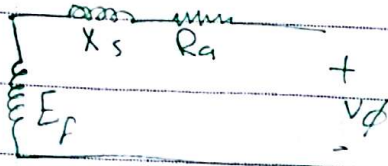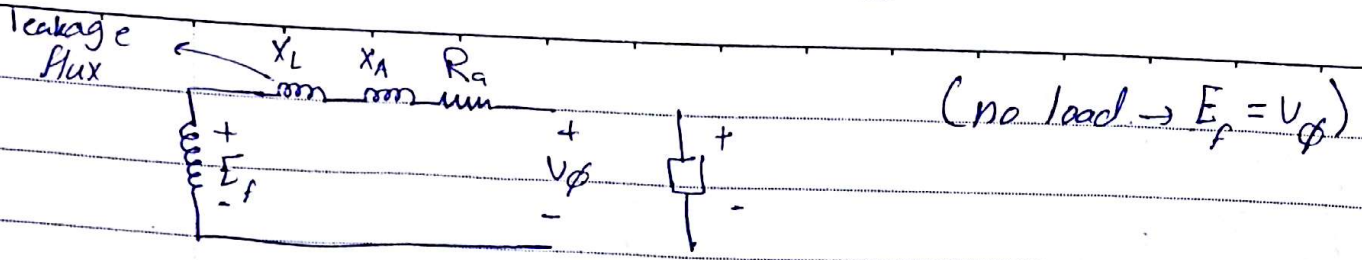

$$X_s = X_L + X_A$$

$X_s =$ synchronous reactance

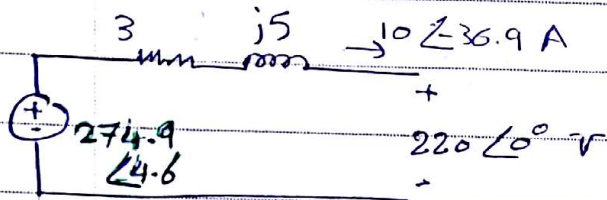
$$E_f = I_a (X_s + R_a) + V_\phi \rightarrow \angle 0^\circ$$




$$E_f = I_a (X_s + R_a) + V_\phi$$

$$= 220 + 10 \angle 36.9 (3 + j5)$$


$$= 274.9 \angle 4.6^\circ$$

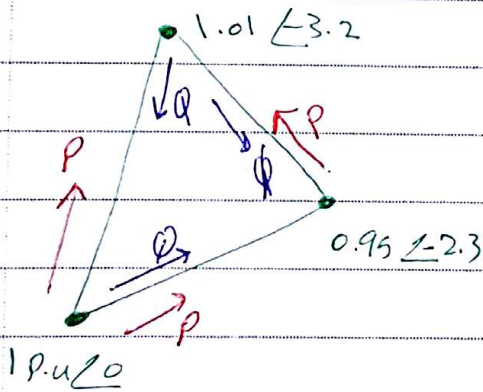

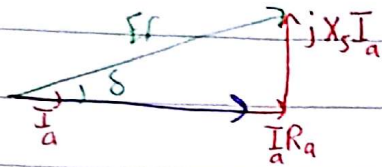
الأنواع هي التي تبعد الطاقة.
تعتمد على القولية الأعلى.



Unity p.f

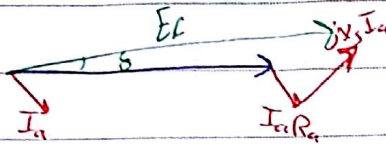

lagging p.f
smallest δ

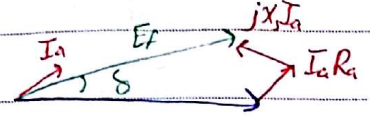

leading p.f
biggest δ

* power and torque in synchronous generator

power \rightarrow prime mover


mechanical power \leftarrow

$$P_{in} = T_{app} \omega_m$$

$$P_{out} = \sqrt{3} V_T I_L \cos \theta$$

line to line voltage \quad line current of the stator

$$P_{in} = 3 E_A I_A \cos \gamma$$

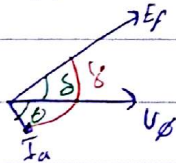

$$\gamma = \delta + \theta$$

$$P_{in} = T \omega_m = 3 E_A I_A \cos \gamma$$

$$3 V_\phi I_\phi \cos \theta$$

stray losses

friction

core losses

$I^2 R$ copper losses

$$Q_{out} = \sqrt{3} V_T I_L \sin \theta$$

13/7/2017


$$P_{out} = \sqrt{3} V_T I_L \cos \theta \rightarrow \text{line}$$

$$= 3 V_\phi I_\phi \cos \theta \rightarrow \text{phase}$$

$$Q_{out} = \sqrt{3} V_T I_L \sin \theta \rightarrow \text{line}$$


$$= 3 V_\phi I_\phi \sin \theta \rightarrow \text{phase}$$

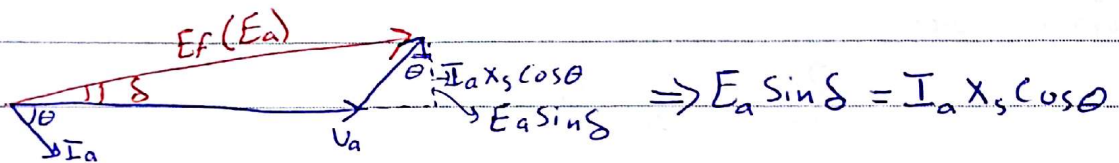In real synch gen. $\Rightarrow R_a \lll X_s$




$$P_{out} = 3 V_T I_a \cos \theta = 3 V_T \frac{E_a \sin \delta}{X_s}$$

$$P_{max} = \frac{3 V_T E_a}{X_s}$$

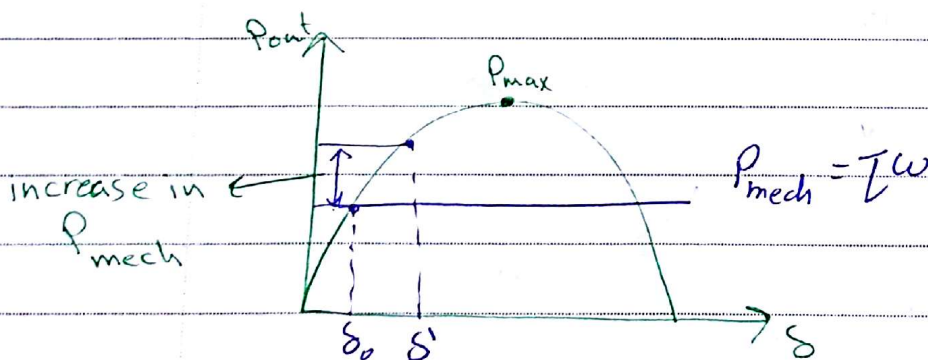


$$T = \frac{3 V_T E_a \sin \delta}{X_s \omega_m}$$

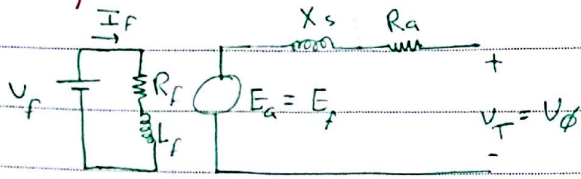
* parameter determination in a synchronous gen.



① o.c Test @ rated speed

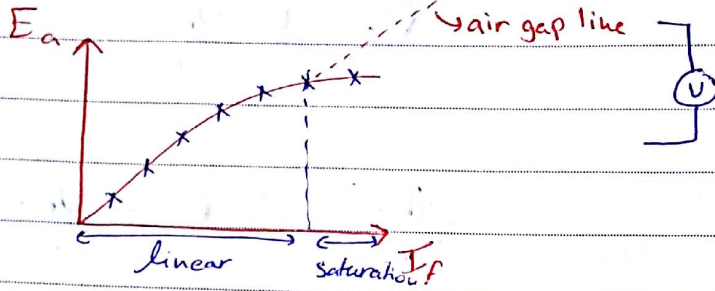

② S.c test @ rated speed

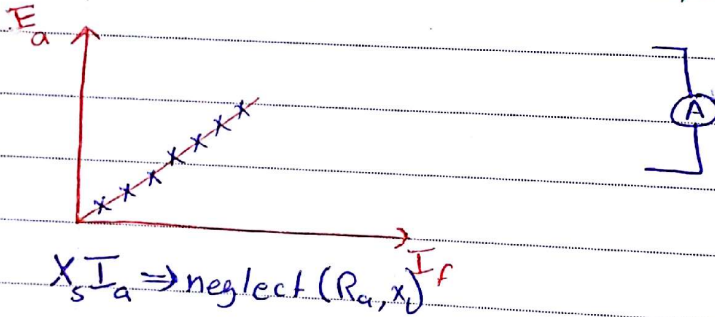


At any value of IR

$$jX_s + R_a = Z_s = \frac{V_{o.c}}{I_{s.c}}$$

X_s دلتا، في الجناح


Find R_a using DC test [generator is not running]

$\omega = 0 \Rightarrow E_a = 0$

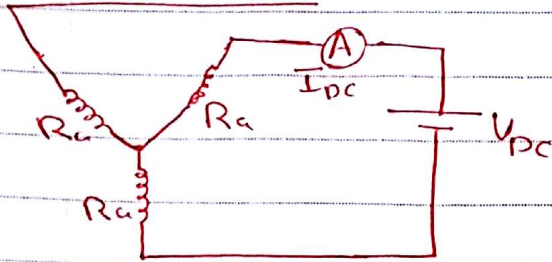

$$2R_a = \frac{V_{dc}}{I_{dc}}$$
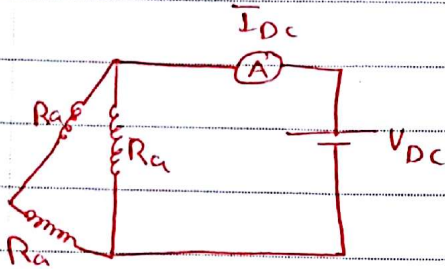
$$R_a = \frac{1}{2} \frac{V_{dc}}{I_{dc}}$$




$$\frac{2(R_a)^2}{3R_a} = \frac{2}{3} R_a = \frac{V_{dc}}{I_{dc}}$$

$$R_a = \frac{3}{2} \frac{V_{dc}}{I_{dc}}$$

$$|Z_s| = \frac{V_{o.c}}{I_{s.c}}$$

$$R_a = R_{DC}$$

$$X_s = \sqrt{Z_s^2 - R_a^2}$$

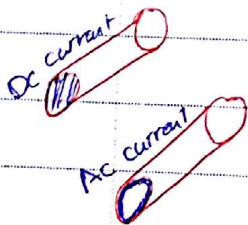


$$R_{AC} > R_{DC}$$

V_L و I_L بقراء V_{LL} و I_{LL} في الجناح

$\frac{V}{\sqrt{3}}$ و I في الجناح

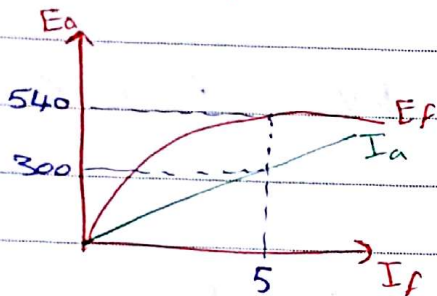Example 4.1 a - 200 kVA, 480V, 50 Hz, Δ connected synch gen. with rated field current $I_f = 5A$, was tested and following results obtained


- ① $V_{T, o.c} = 540 V$ at rated I_f
- ② $I_{L, s.c} = 300 A$ at rated I_f
- ③ when a DC source of 10V was applied to two of the terminals, $I_a = 25 A$



$$Z_s = \frac{540/\sqrt{3}}{300} = 1.039 \Omega$$

$$2R_{DC} = \frac{V_{DC}}{I_{DC}} = \frac{10}{25} = 0.4 \Rightarrow R_a = 0.2 \Omega$$
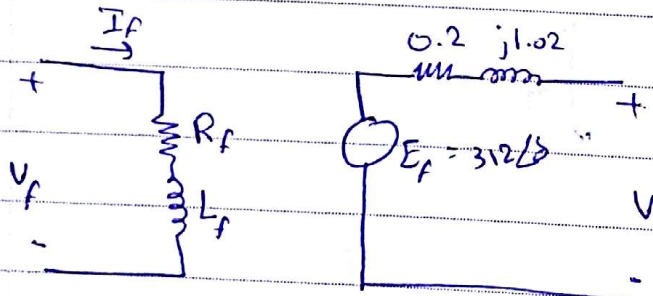
$$X_s = \sqrt{(1.039)^2 - (0.2)^2} = 1.02 \Omega$$



The behaviour of a synch. generator is mainly affected by :-

- ① load [PF and magnitude]
- ② Is the generator connected to a system or not.

* Synch. gen. working alone :-
 \Rightarrow speed is constant


① \Rightarrow if the field is not changed $E_a = k\phi\omega$, E_a is constant

② $\Rightarrow E_a = V_\phi + jX_s I_a$


change of the load $\Rightarrow E_a$ is constant

$$E_a = \underbrace{V_\phi}_{\substack{\downarrow \\ \text{decrease} \\ \text{as} \\ \text{load} \\ \text{increase}}} + jX_s \underbrace{I_a}_{\uparrow}$$

$$V_\phi = V_T = V_{\text{load}}$$

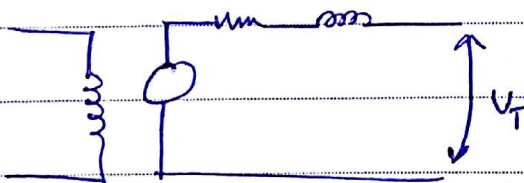

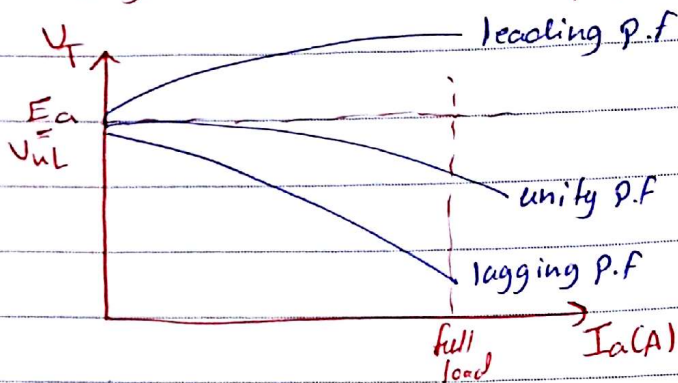
To adjust the value of V_T , increase the field.




$$UR = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$

$$V_{NL} = E_a$$
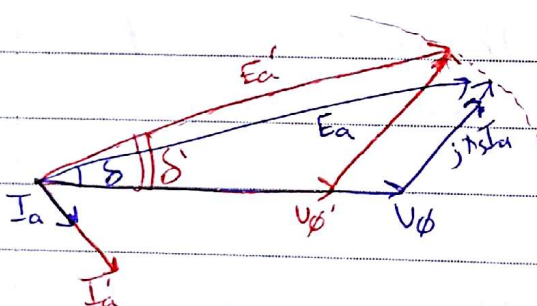
$$UR = \frac{E_a - V_{FL}}{V_{FL}} \times 100\%$$




$$|E_a| = |E_a'|$$

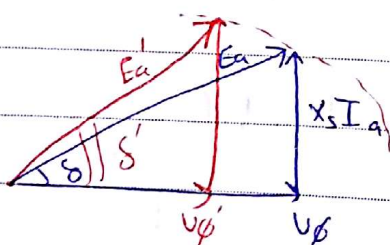

Stand alone 8-
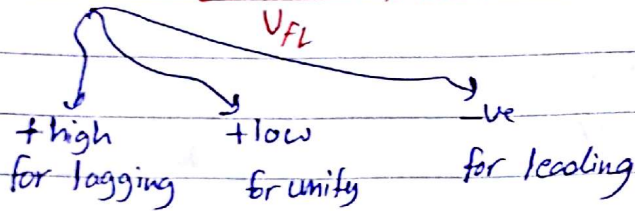
$$VR = \frac{E_a - V_T}{V_T} \times 100\%$$



$V_T \downarrow$ with $I_a \uparrow$

→ to increase V_T , $E_a \uparrow$ → by increasing ϕ → by decreasing R_f

** Study example 4.2


Example 8- 480 V, 60 Hz, Y connected 6-pole synch. gen.
per phase synch. reactance $X_s = 1 \Omega$, with full load current $I_a = 60$
at 0.8 lag p.f, friction and winding losses = 1.5 kW, $P_{core} = 1$ kW
at 60 Hz, $P_{copper} = 0$, The field current has been adjusted
such that the no-load terminal voltage is 480.

(A) speed of rotation


$$n_m = \frac{60 \times f}{P_{pairs}} = \frac{60 \times 60}{3} = 1200 \text{ rpm} \Rightarrow \omega_m = 125.7$$

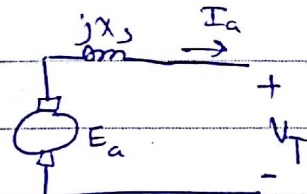(B) V_T at i) rated current 0.8 lag p.f

$$E_a \angle \delta = V_T \angle 0^\circ + jX_s I_a$$


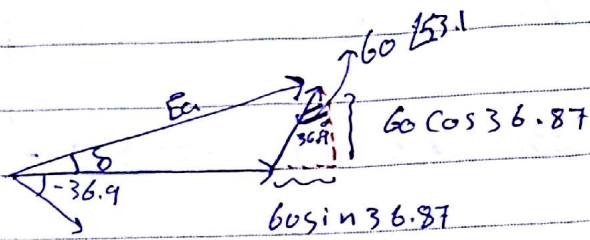
$$\frac{480}{\sqrt{3}} \angle \delta = V_T \angle 0^\circ + j 60 \angle -36.9^\circ \times 1$$




$$\left(\frac{480}{\sqrt{3}}\right)^2 = (V_T + 60 \sin 36.87)^2 + (60 \cos 36.87)^2$$

$$V_T = 236.8 \text{ V} \rightarrow \text{phase neutral}$$

$$V_T = 410 \text{ V}_{LL}$$

2) unity p.f

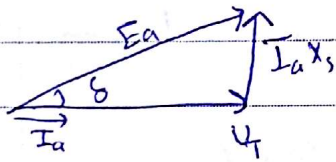

$$E_a \angle \delta = V_T \angle 0^\circ + 60 \angle 90^\circ$$

$$E_a^2 = V_T^2 + 60^2$$

$$V_T = 270.4 \text{ V}$$

$$V_T = 468.4 \text{ V}_{LL}$$

3) leading 0.8 p.f

$$\left(\frac{E_a}{\sqrt{3}}\right)^2 = (V_T - \sin I_a X_s)^2 + (I_a X_s \cos \theta)^2$$

$$V_T = 308.8 \text{ V}$$

$$V_T = 535 \text{ V}_{LL}$$

(B) for 0.8 lagging p.f find η

$$P_{out} = 3V_{\phi} I_{\phi} \cos\theta = 3 \times 236.8 \times 60 \times \cos(36.87) = 34.1 \text{ kW}$$

$$P_{in} = P_{out} + P_{core} + P_{copper} + P_{mech} = 34.1 + 0 + 1.5 = 36.6 \text{ kW}$$

$$\eta = \frac{P_{out}}{P_{in}} \times 100\% = \frac{34.1 \text{ k}}{36.6 \text{ k}} = 93.2\%$$

$$(C) T_{ind} = \frac{P_{in}}{\omega_m} = \frac{36.6}{125.7} = 291.2 \text{ Nm}$$


$$T_{load} = \frac{P_{out}}{\omega_m} = \frac{34.1}{125.7} = 271.2 \text{ Nm}$$

$$(D) UR = \frac{480 - 410}{410} \times 100\% = 17.1\% \rightarrow (0.8 \text{ lagging p.f.})$$

$$\text{Unity p.f.} \Rightarrow UR = \frac{480 - 468}{468} \times 100\% = 2.6\%$$


$$\text{Leading p.f.} \Rightarrow UR = \frac{480 - 535}{535} \times 100\% = -10.3\%$$

generator is connected to a system 8-

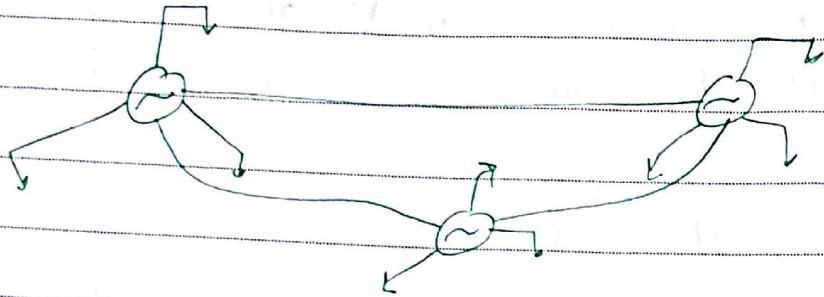

⇒ reliability, maintenance

N-1 contingency

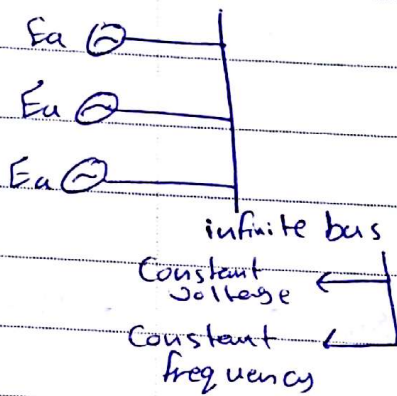


gen connected to a system V_T is constant

E_f is a function of I_f

magnitude and phase of I_a are dependent variables 3-

$$E_f = V_T + jX_s I_a$$

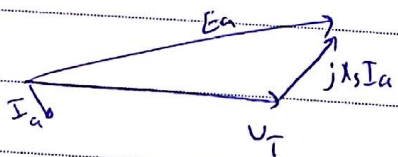

$$E_a \angle \delta = V_T \angle 0^\circ + I_a X_s \angle 90^\circ \pm \theta$$

Example 2: 60 Hz, 4 pole, Synchron. gen. has a synch reactance of 5Ω . The stator is connected in Δ and its line-line voltage is 15 kV. The line current of the generator is 1 kA and 0.9 lagging p.f.

(a) The equiv. field voltage (E_a)


$$E_a = \frac{15}{\sqrt{3}} \angle 0^\circ + 1k \angle -\cos^{-1} 0.9 \times j5 = 11.74 \angle 22.54 \text{ kV}$$

(b) The power delivered to the system.

$$P = \sqrt{3} \frac{V_{T.L.L.}}{1} I_a \cos \theta \quad \rightsquigarrow \quad \theta \text{ is the angle between } V_{\phi} \text{ and } I_{\phi} \text{ phase}$$

$$= \sqrt{3} \times 15 \times 10^3 \times 10^3 \times 0.9 = 23.38 \text{ MW}$$

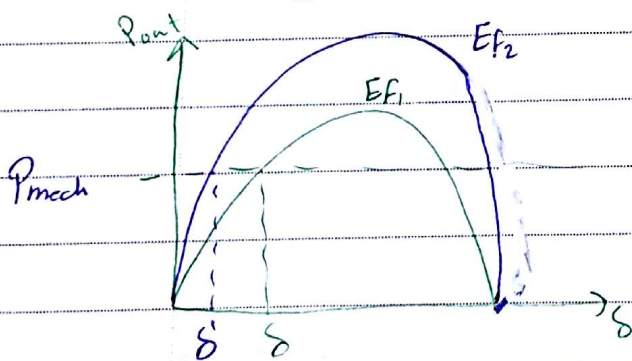
$$Q = \sqrt{3} \frac{V_{T.L.L.}}{1} I_a \sin \theta = \sqrt{3} \times 15 \times 10^3 \times 10^3 \times \sin(\cos^{-1} 0.9) = 11.32 \text{ MVAR}$$



$$P_{out} = \frac{3 V_T E_a \sin \delta}{X_s}$$

$$I_f \uparrow \rightarrow \phi \uparrow \rightarrow E \uparrow = k \phi \omega \rightarrow P_{out} \uparrow$$

$$E_{f1} < E_{f2}$$

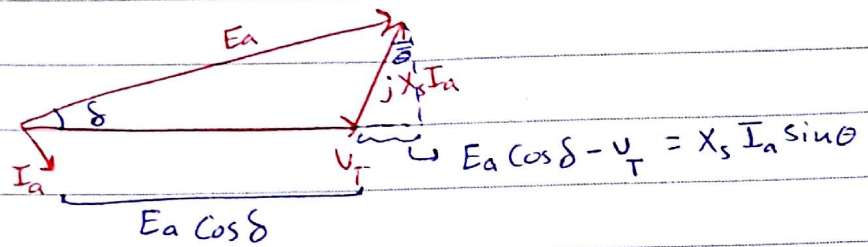


$$Q_t = 3 V_T I_a \sin \theta$$

$$X_s I_a \sin \theta = E_a \cos \delta - V_T$$

$$Q_t = 3 V_T \frac{(E_a \cos \delta - V_T)}{X_s}$$

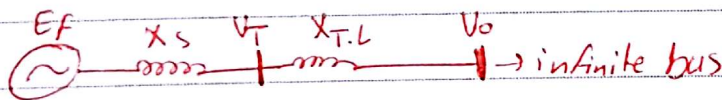- ① $E_a \cos \delta - V_T > 0 \Rightarrow (Q +ve)$ Q is delivered to the system
- ② $E_a \cos \delta - V_T = 0 \Rightarrow Q = 0$ Q is not being delivered or consumed by the system
- ③ $E_a \cos \delta - V_T < 0 \Rightarrow (Q -ve)$ The system delivers Q to the generator



$$P_{out} = \frac{3 E_f V_0 \sin \delta}{X_s + X_{T.L}}$$

* good luck *