

14
25

Q	Mark
1	1 / 10
2	3 / 8
3	5 / 5
4	8 / 15
5	12 / 12
SUM	29 / 50

University of Jordan

Electrical Eng. Dept

93371 Electrical Machines(1)

Prof. D.Dalabeih

First Exam.

24-10-2013

0127430

رقم التفتد: 53 الرقم الجامعي:

الاسم: تميم حسن القطيس

Q1) Fill in the following blanks:

[10]

1-The quantity that drives flux in magnetic circuit is called:

2-One of the assumptions in calculating Reluctance is:

3-The permeability of a core drops to a low value when:

4-The coercive force is defined as:

5-The area of the hysteresis loop is proportional to: magnitude of amplitude of the current and mmf

6-Eddey current losses are reduced by: heat in the core



7-The construction of transformer which has the windings wrapped around the central leg is called:

8-Flux linkage is defined as: ~~That flux can be out the core~~ flux out the core $\frac{d\phi}{dt}$

9-The two components of the no-load current of a transformer are: eddy and hysteresis

10-The shape of the transformer excitation current is:

1/2

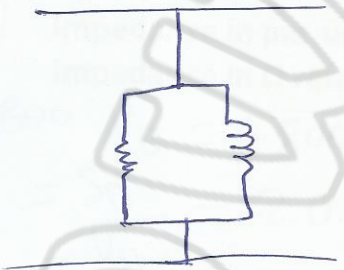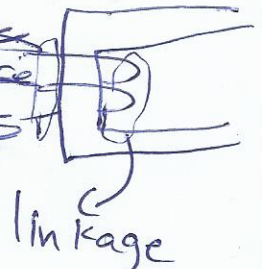

PRO

Q2) The construction shown in Fig. 1 has a depth of 8 cm and the following magnetization curve data:



B(T)	0.15	0.25	0.3	0.4	0.5	0.6
H(A.t/m)	40	50	55	65	70	85

$\Phi = BA = \phi$ $HL = Ni$ $B = \mu H$

Evaluate the current required to produce $B = 0.25$ T in the right leg. Assuming that right and left legs are symmetrical. [6]

$B = \frac{\phi}{A} \rightarrow \mu H$ from the slope $\mu = 0.01$
 $B = 0.25 \rightarrow H = 50$

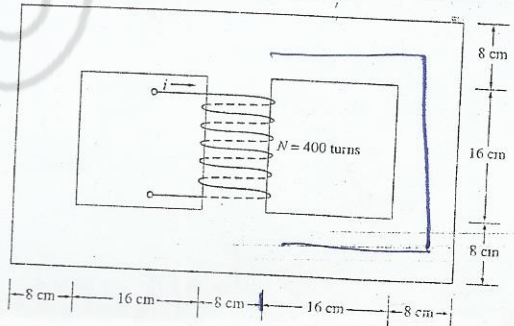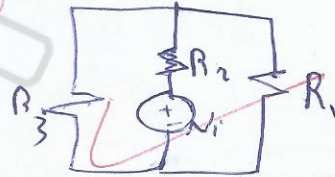$H = Ni \rightarrow Ni = 32$
 $L_{leg} = 0.56$ $R_1 = R_3 = \frac{0.56}{0.01 \times 0.64}$
 $R_1 = R_3 = 87.5$



$\Phi = 0.25 \times 0.64 = 0.16$
 $\Phi + \Phi_2 = 0.32$

$\text{mmf} = \phi \times R = 28 \rightarrow i = \frac{28}{400} = 0.07$ Fig. 1

b-Evaluate μ_r of the core according to the data of central leg. [2]

$\mu = \mu_0 \mu_r = \frac{\Delta B}{\Delta H} = \frac{0.4 - 0.15}{65 - 40} = 0.01$
 $\mu_r = \frac{0.01}{4\pi \times 10^{-7}} = 7957.75$

Q3) A (480/4800) V, 10 kVA transformer has a series equivalent impedance in per-unit as (0.0087 + j 0.026). Find the equivalent impedance in Ω referred to HV side. [5]

$V_B = 4800$ $S_B = 10 \text{ kVA}$

$I_B = \frac{S_B}{V_B} = 2.083$ $Z_B = \frac{V_B^2}{S_B} = 2304$

$(0.0087 + j0.026) \times 2304 = (20.0448 + 59.904j) \Omega$

Q4) A 20 kVA, (8000/240) V, 60 Hz transformer has the following parameters referred to HV side:

$$R_c = 159 \text{ k}\Omega \quad X_m = 38.4 \text{ k}\Omega \quad R_{eq} = 38.4 \Omega \quad X_{eq} = 192 \Omega$$

If an O/C test was performed with the LV as the primary, what would be the READINGS of its measuring instruments. [15]

$$V_{oc} = 240 \text{ V}$$

$$Z_c = R_c + X_m$$

$$Z_c = R_c \parallel X_m$$

$$|Z_c| = \frac{I_{oc}}{V_{oc}}$$

$$Z_c = 159000.0 \angle -0.0138$$

$$Y_c = 6.289 \times 10^{-6} \angle -0.0138$$

$$6.289 \times 10^{-6} \times 240 = I_{oc}$$

$$I_{oc} = 1.5094 \times 10^{-3} \text{ A}$$

$$\cos^{-1}(0.0138)$$

$$\cos^{-1}\left(\frac{P_{oc}}{V_{oc} I_{oc}}\right) = 0.0138$$


$$P_{oc} = 0.99971 \times 240 \times 1.5094 \times 10^{-3}$$

$$P_o = 362.15 \times 10^{-3} \text{ W}$$

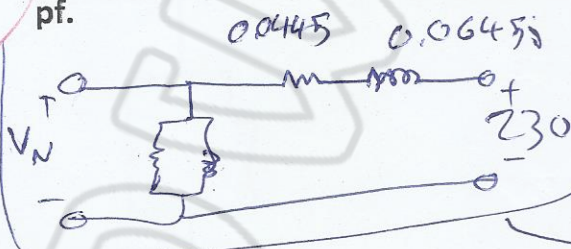Q5) A 15 kVA, 2300/230 V transformer has the following parameters

Referred to LV side: $R_{eq} = 0.0445 \Omega$ $X_{eq} = 0.0645 \Omega$

If this transformer is used as step-down, find its PU equivalent circuit and then use it to find the full load voltage regulation at 0.8 lagging pf.



$$V_B = 230 \text{ V} \quad S_B = 15 \times 10^3 \text{ VA}$$

$$Z_B = 3.5266$$

$$R_{eq} = 0.012618$$

$$X_{eq} = 0.01829$$

$$I = \frac{15 \times 10^3}{2300} \angle -\cos^{-1}(0.8) = 6.5217 \angle -36.869^\circ \text{ A}$$

$$I_B = \frac{S_B}{V_B} = 65.217 \rightarrow I = 1 \angle -36.869^\circ$$

$$V_N = 230 - 36.869 \times (0.012618 + 0.01829j) + 230$$

$$V_N = 0.02222 \angle 18.5298 + 1 = 1.02109 \angle 0.39624$$

$$VR = \frac{V_N - 1}{1} = 0.02109 = 2.1\%$$