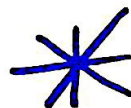


Electrical Machines (I)

Second
Semester
(2017)

Dr. Daifallah Dalabeih.

* Mohammad
Abu Hashia. *



Electrical Machines (I)

Summary

* First Material:

CHAPTER (1):

Amper's law: $\oint \vec{H} \cdot d\vec{l} = Ni$

$H L_c = Ni$

Total Flux: $\phi = \int B \cdot dA$

$\phi = BA$

$B = \mu H$

$Ni = \phi R$, $R = \frac{l}{\mu A}$

* Magnetic ccts using airgap:


$B_g = \frac{\phi}{A_g}$, $B_c = \frac{\phi}{A_c}$

$A_g = \text{factor} * A_c$

if $A_c = a * b$

$A_g = [a+g] * [b+g]$

* Magnetization curve "B-H curve":

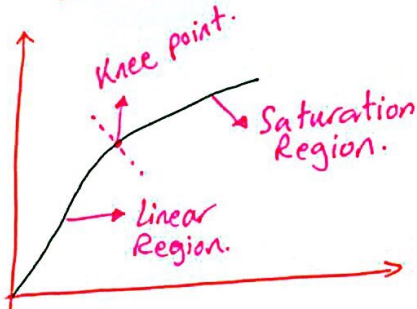

* Area of Hysteresis loop represent: Energy Density

$A_h \equiv J/m^3$

* Core Losses:

$P_c = P_h + P_e$

Hysteresis losses.

Eddy current losses.

⇒

$P_h = f A_h V$

$A_h = B_m^n K_h$

$P_e = V K_e B_m^2 f^2 \tau^2$

Stacking Factor: ≡

$\frac{\text{Volume of ferromagnetic material}}{\text{Total volume of the core.}}$

* Self Inductance:

$$e = -N \frac{d\phi}{dt}$$

$$L = \frac{N^2}{R} = \frac{N^2 \mu A}{l}$$

* For a 4-poles Machine:

$$NI = H_p L_p + H_g L_g + \frac{1}{2} H_R L_R + \frac{1}{2} H_Y L_Y$$

$H_p, H_R, H_Y \Rightarrow$ From B-H curve.
 $H_g \Rightarrow B_g \text{ given} \Rightarrow B_g = \mu_0 H_g.$


CHAPTER (2):



* Turns Ratio $(a) = \frac{V_p}{V_s} = \frac{e_p}{e_s} = \frac{i_s}{i_p} = \frac{N_p}{N_s}$

* $|S_s| = |S_p|$
 $P_p = P_s$
 $\eta = \frac{P_{out}}{P_{in}} = \frac{P_p}{P_s} = \frac{P_s}{P_p} = 1 = 100\%$

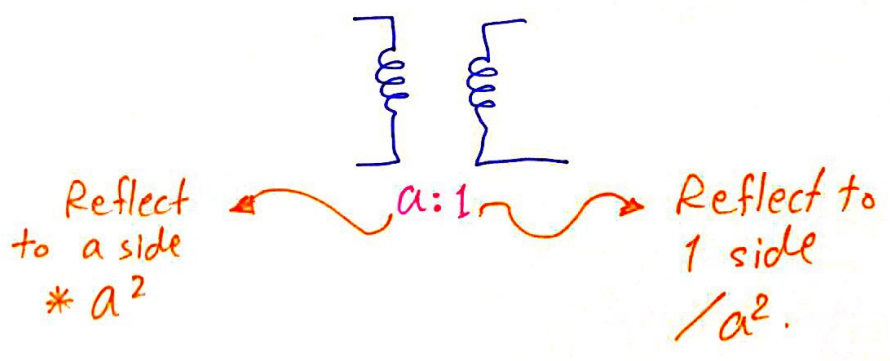$Z_p = \frac{V_p}{I_p}$, $Z_s = \frac{V_s}{I_s}$, $Z_p = a^2 Z_s$



Linkage flux $(\lambda) = \sum_{i=1}^N \Phi_i$

Average flux $\bar{\Phi} = \frac{\lambda}{N}$

$\Rightarrow e = \frac{d\lambda}{dt} = N \frac{d\bar{\Phi}}{dt}$

for primary:

$\bar{\Phi}_p = \Phi_m + \Phi_{LP}$
 $e_p = N_p * \frac{d\Phi_m}{dt} + N_p * \frac{d\Phi_{LP}}{dt}$

e_{pm}

e_{pL}

$e_p = e_{pm} + e_{pL}$

for secondary:

$\bar{\Phi}_s = \Phi_m + \Phi_{LS}$
 $e_s = N_s \frac{d\Phi_m}{dt} + N_s \frac{d\Phi_{LS}}{dt}$

e_{sm}

e_{sL}

$e_s = e_{sm} + e_{sL}$

$\frac{e_{pm}}{e_{sm}} = \frac{N_p}{N_s}$

*No-load:

*losses in practical transformer:

Losses = $P_h + P_e + i_p^2 R_p$

$i_p = i_m + i_c$

* P_e is max. when $\Phi = 0$.

$i_{ext} = I_{m1} \cos \omega t + I_{m2} \cos 2\omega t + I_{m3} \cos 3\omega t + \dots$

if +ve & -ve cycles identical:

$i_{ext} = I_{m1} \cos \omega t + I_{m3} \cos 3\omega t + I_{m5} \cos 5\omega t + \dots$

if we have: $a \neq 1$

reflect to primary:

$$R_{eq} = R_p + a^2 R_s$$

$$X_{eq} = X_p + a^2 X_s$$

$$Z_{eq} = R_{eq} + j X_{eq}$$

reflect to secondary:

$$R_{eq} = R_s + \frac{R_p}{a^2}$$

$$X_{eq} = X_s + \frac{X_p}{a^2}$$

* S/C Test:

we find R_{eq} & X_{eq} .

find R_{eq} from:

$$P_{sc} = I_{sc}^2 R_{eq}$$

find X_{eq} from:

$$|Z_{eq}| = \frac{|V_{sc}|}{|I_{sc}|} = \sqrt{R_{eq}^2 + X_{eq}^2}$$

or using:

$$Z_{eq} = |Z_{eq}| \angle \theta \rightarrow \cos^{-1} \left(\frac{P_{sc}}{I_{sc} V_{sc}} \right)$$

$$= R_{eq} + j X_{eq}$$

* O/C Test:

we find R_c & X_m .

find R_c from:

$$P_{oc} = \frac{V_{oc}^2}{R_c}$$

find X_m from:

$$|Y| = \frac{|I_{sc}|}{|V_{oc}|} = \sqrt{\left(\frac{1}{R_c}\right)^2 + \left(\frac{1}{X_m}\right)^2}$$

or using:

$$Y = |Y| \angle -\theta \rightarrow \cos^{-1} \left(\frac{P_{oc}}{I_{sc} V_{oc}} \right)$$

$$= \frac{1}{R_c} + j \frac{1}{X_m}$$

* PU system:

$$PU \text{ value} = \frac{\text{Actual value}}{\text{Base value}}$$

usually we select V & S as a base values.

$$Z_{new} (PU) = Z_{old} (PU) * \left(\frac{V_{old}}{V_{new}} \right)^2 * \left(\frac{S_{new}}{S_{old}} \right)$$

** Second Material:

* voltage regulation:

$$V_R\% = \frac{|V_L(NL)| - |V_L(FL)|}{|V_L(FL)|} * 100\%$$

* for inductive & resistive:
 $|E_s| > |V_s| \Rightarrow V_R +ve.$

* for capacitive:
 $|E_s| < |V_s| \Rightarrow V_R -ve.$


* efficiency:

$$\eta = \frac{\text{output}}{\text{input}} = \frac{\text{output}}{\text{output} + \text{losses}}$$


→ electrical
→ core.

* AutoTransformer:

step-up:

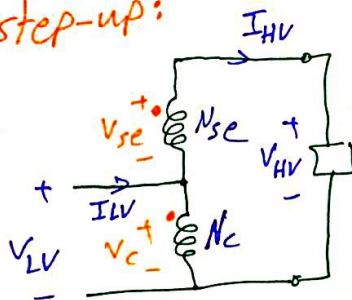

step-down:

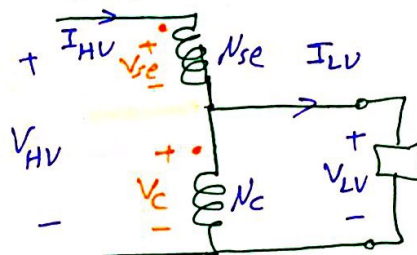

$$I_{LV} = I_{se} + I_c$$

$$S_i = S_o$$

$$I_c N_c = I_{se} N_{se}$$

$$\frac{V_c}{V_{se}} = \frac{N_c}{N_{se}}$$

$$\frac{V_{HV}}{V_{LV}} = \frac{I_{LV}}{I_{HV}} = \frac{N_{se} + N_c}{N_c}$$

$$\frac{S_{io}}{S_w} = \frac{N_c + N_{se}}{N_{se}}$$

* relation between $Z_{eq}(pu)_{conv.}$ & $Z_{eq}(pu)_{Auto}$:

$$Z_{eq}(pu)_{Auto} = Z_{eq}(pu)_{conv.} / \left(\frac{N_c + N_{se}}{N_{se}} \right)$$



* inrush current:

very high current $\gg I_{rated}$

under condition:

$$\phi = 2\phi_m ; \phi_m = \frac{V_m}{N\omega}$$

@ $V=0$ when $t=0$.

* 3 phase:

Y-Y $\frac{V_L}{V_\phi} = 1$
 $\Delta-\Delta$

Y- Δ $\frac{V_L}{V_\phi} = \sqrt{3}$

Δ -Y $\frac{V_L}{V_\phi} = \frac{1}{\sqrt{3}}$

\Rightarrow 4 possible cases of phase shift: $0, 180, -30, 30$
12:00 6:00 1:00 11:00

in +ve seq.: HV leads by 30° LV.

in -ve seq.: HV lags by 30° LV.

* ratio of line voltages:

effective turns ratio: $a_{eff} = \frac{V_{LL}}{V_{\phi\phi}} = \frac{N_H}{N_L/\sqrt{3}}$ in Y- Δ .

* O/C Test: $P_{oc} = \frac{W_1 + W_2}{3}$, $V_{oc} = \frac{V}{\sqrt{3}}$, $I_{oc} = \text{Ammeter reading}$

* S/C Test: $P_{sc} = \frac{W_1 + W_2}{3}$, $V_{sc} = \frac{V}{\sqrt{3}}$, $I_{sc} = |I|_{rated} = \text{Ammeter reading}$

Conventional: \rightarrow o/c : rated voltage = V_{oc} .
 \rightarrow s/c : rated current = I_{sc}


* 3-ph PU:

$S_{1\phi} = \frac{S_{3\phi}}{3}$


$V_{1\phi} = \frac{V_{LL}}{\sqrt{3}}$

$Z_b = \frac{V_{LL}^2}{S_{3\phi}}$

* Parallel operation:

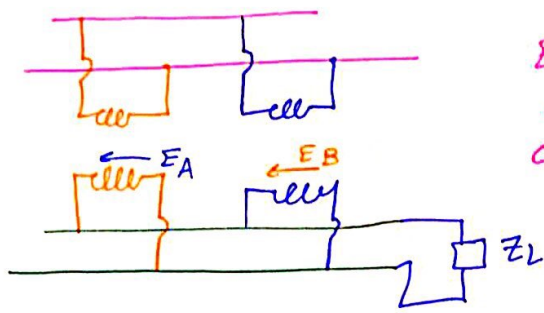

Equivalent circuit

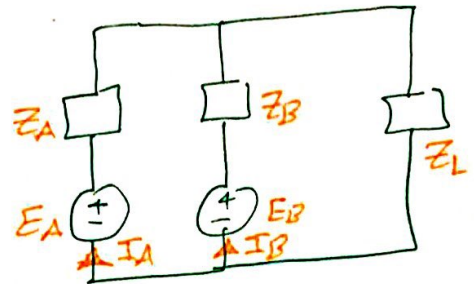

$$V = \frac{\frac{E_A}{Z_A} + \frac{E_B}{Z_B}}{\frac{1}{Z_A} + \frac{1}{Z_B} + \frac{1}{Z_L}}$$

$$I_A = \frac{E_A - V}{Z_A}$$

$$I_B = \frac{E_B - V}{Z_B}$$

* if $E_A = E_B$:


$$I_A = I_L \frac{Z_B}{Z_A + Z_B}$$

$$I_B = I_L \frac{Z_A}{Z_A + Z_B}$$

CHAPTER(3):

$$e \triangleq (\mathbf{v} \times \mathbf{B}) \cdot \mathbf{l}$$

for a loop

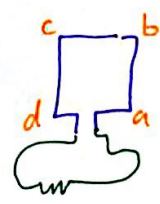


$$e = 2vBl \sin \theta_{ab}$$

$$v = \omega \cdot r \quad \& \quad \phi = BA$$


$$e = \omega \phi \sin \theta_{ab}$$

$$E_m = 2vBl = \omega \phi_m$$

* Armature circuit:

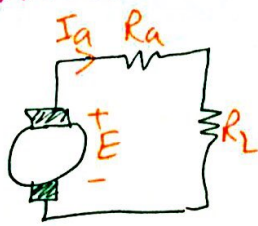

* Field circuit:

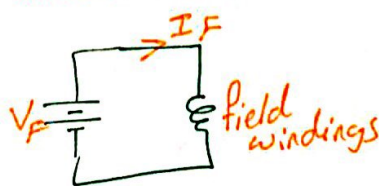

$$\tau = A B_s I_a \sin \theta = K (B_s \times B_r)$$

where K:

$$K = \frac{A l}{\mu N}$$

* Rotating Magnetic Field:

$$\begin{aligned} i_a &= I_m \sin \omega t \\ i_b &= I_m \sin(\omega t - 120) \\ i_c &= I_m \sin(\omega t - 240) \end{aligned}$$

$$\begin{aligned} H_{aa'} &= H_m \sin \omega t \angle 0^\circ \\ H_{bb'} &= H_m \sin(\omega t - 120) \angle 120^\circ \\ H_{cc'} &= H_m \sin(\omega t - 240) \angle 240^\circ \end{aligned}$$

$$\begin{aligned} B_{aa'} &= B_m \sin \omega t \angle 0^\circ \\ B_{bb'} &= B_m \sin(\omega t - 120) \angle 120^\circ \\ B_{cc'} &= B_m \sin(\omega t - 240) \angle 240^\circ \end{aligned}$$

$$B_p = 1.5 B_m (\sin \omega t - j \cos \omega t)$$

$$f_e = P f_m$$

* Final Material:

* synch. AC gen.:

$$e_{total} = 2 B_m l v \cos(\omega_m t)$$

$$\Rightarrow A_p = \frac{2\pi r l}{P}$$

$$\begin{aligned} E_m &= N \Phi \omega_e \\ E_{rms} &= 4.44 \Phi N f_e \end{aligned}$$

$$K_w = K_p K_d$$

$$E_{rms} = 4.44 K_d K_p \Phi N f_e$$

$$\begin{aligned} K_p &= \sin\left(\frac{P}{2}\right) \\ K_d &= \frac{\sin\left(\frac{18}{2}\right)}{n \sin\left(\frac{18}{2}\right)} \end{aligned}$$

coils pitch.
slot pitch. $\left(\frac{360}{\# \text{ of slots}}\right)$
 n : number of phase belts.

$$= \frac{\# \text{ of slots}}{P \times P}$$

number of poles.

$$\begin{aligned} \text{Pole pitch} &= 180^\circ \text{ elec.} \\ \text{Pole pitch} &= \frac{360}{P} \text{ mech.} \end{aligned}$$

of poles.

* synch. Reactance:

$$X_s = X + X_a$$

* when R_a is neglected:

$$\begin{aligned} P_{in} &= P_{mech} = T_{app} \omega_m \\ P_{out} &= 3 V_\phi I_\phi \cos \delta = \sqrt{3} V I_\phi \cos \delta \\ P_{conv} &= 3 E I_\phi \cos \delta = \sqrt{3} E I_\phi \cos \delta \end{aligned}$$

$$\begin{aligned} P_{out} &= P_{conv} \\ P_{out} &= \frac{3 V_\phi E \sin \delta}{X_s} \end{aligned}$$

$$P_{conv} = T_{ind} \omega_m$$

from it find T_{ind} :
 $T_{ind} = P_{out} / \omega_m$

* R_a & X_s :

DC/ Test: $R_{a(DC)} = \frac{1}{2} \left(\frac{V}{A} \right) \Rightarrow R_{a(AC)} = \text{factor} * R_{a(DC)}$

O/C Test: \rightarrow vary I_f & take the voltmeter reading \equiv Generated voltage. (E)

S/C Test: \rightarrow vary I_f & take the Ammeter reading $\equiv (I_a) \equiv \frac{E}{Z_{eq}}$

we obtain X_s from: $X_s = \sqrt{|Z_{eq}|^2 - R_a^2}$

* SCR:

$\Rightarrow SCR = \frac{I_f(OC)}{I_f(SC)}$

also: $SCR = \frac{1}{X_s(PU)}$

speed Drop = $\frac{n_{NL} - n_{fL}}{n_{fL}} * 100\%$

$P = S_p (f_{NL} - f_{fL})$

* Housing Diagram:

$P_L = P_1 + P_2$

$\Rightarrow P_L = S_{p1} (f_{NL1} - f_{sys}) + S_{p2} (f_{NL2} - f_{sys})$

* Gen. Connected to ∞ -system:


$P_{\infty} = P_L - P_1$

$f = \frac{n P}{2}$
pair pole.

* Armature windings:

Lap winding: $a = m P$

wave winding: $a = 2 m$

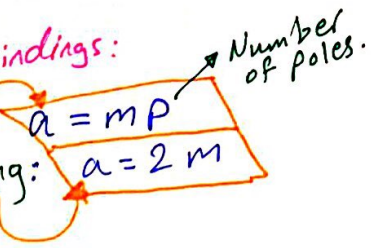

- simplex $\rightarrow m=1$
- duplex $\rightarrow m=2$
- Triplex $\rightarrow m=3$

* Voltage induced in DC gen.:

in a single turn:

$e = \frac{P \phi \omega}{\pi}$

for voltage per path:

$e = \frac{n P \phi Z}{a}$

*
$$T_{ind} = \frac{P\phi I}{\pi}$$

$$T_{total\ Torque} = \frac{P\phi Z I_a}{2\pi a}$$

* For shunt Motor:

$$E I_a = I V - (I_a^2 R_a + I_F V_F)$$

↓ ↓ ↓
 Converted input electrical
 power. power. losses.

$$P_{conv} = E I_a = T_{ind} \cdot \omega_m$$

$$T_{ind} = \frac{E I_a}{\omega_m}$$

* speed Equation:

$$\omega = \frac{V - I_a R_a}{K\phi}$$

$$\omega = \frac{V}{K\phi} - \frac{R_a}{K\phi^2} T$$

* speed Regulation:

$$SR = \frac{\omega_{NL} - \omega_{FL}}{\omega_{FL}}$$

* * *

Good * * *
* * * Luck.