


MACHINES I NOTEBOOK

**DR. ZAKIE KHADER
SPRING - 2014**


BY : RANIA DARAGHMEH



Topic 1: Electromagnetics

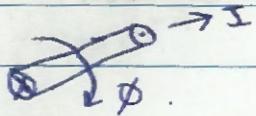
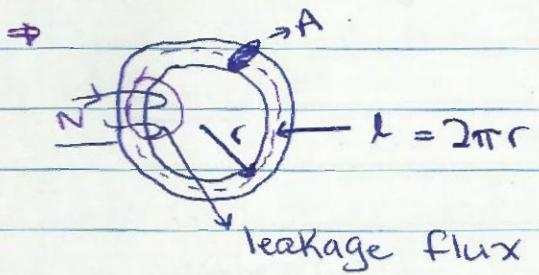
$$i = \oint H \cdot dL \quad H = \text{Magnetic Intensity}$$



Φ = magnetomotive force
Reluctance

$$= \text{flux} = \frac{F}{R} \quad [\text{Wb}]$$

$$F = Ni \quad (\text{Ampere turn} = AT) \quad R = \frac{l}{MA} \quad [AT/Wb]$$

M = permeability $[\text{Wb/Atm}]$

M = permeability of free space $= 4\pi \times 10^{-7}$

$M_r = \frac{M}{M_0}$ = relative permeability



⇒ In electric circuits:

$$R = \rho \frac{l}{A}, \quad I = \frac{E}{R}$$


$$\Rightarrow \Phi = \frac{Ni}{R} = \frac{Ni}{\frac{l}{MA}} = \frac{Ni}{2\pi r} \quad MA$$

$$\Rightarrow B = \text{flux density} = \frac{\Phi}{A} = \frac{Ni}{2\pi r} M. \quad [\text{Wb/m}^2 = \text{Tesla} = T]$$
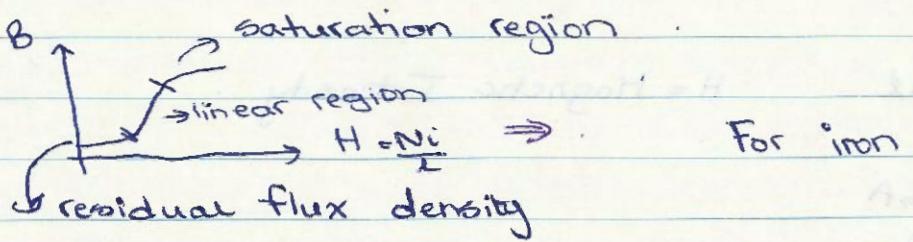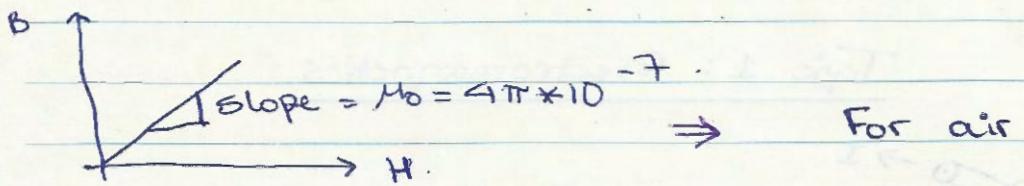
$$\Rightarrow Ni = \sum Hl, \quad Ni = Hf, \quad H = \frac{Ni}{l} \Rightarrow H = \frac{B}{M}, \quad B = MH$$



⇒ example :-

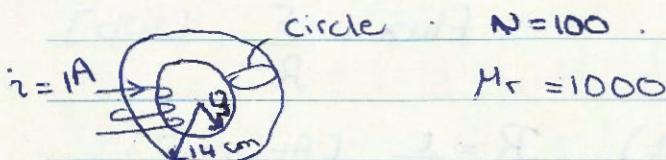

circle : $N = 100$

$H_f = 1000$

Solve :-

$$A = \pi * 0.01^2 = \pi * 10^{-4} \text{ m}^2$$

$$l = 13 * 2 * \pi * 10^{-2} = 0.26\pi \quad , \quad H = 1000 M_0$$

$$R = \frac{0.26\pi}{1000 * 4\pi * 10^{-7} * \pi * 10^{-4}}$$

$$= \frac{10^8 * 0.26}{4\pi} = 2.1 * 10^6$$

$$\phi = \frac{Ni}{R} = \frac{100 * 1}{2.1 * 10^6} = 0.05 \text{ mwb}$$

$$B = \frac{\phi}{A} = \frac{0.5 * 10^{-4}}{\pi * 10^{-4}} = 0.15 \text{ T}$$

\Rightarrow If I add an air gap of 1mm;

$$R_g = \frac{1 \times 10^{-3}}{4\pi \times 10^{-7}} = 0.5 \times 10^6$$

$$\Phi = \frac{100 \times 1}{(2.1 + 2.5) \times 10^6} = 0.027 \text{ wb} \text{ (Half the flux)}$$

\Rightarrow Electric

Magnetic

Current (A)

Flux (wb), Φ

Emf in voltage (V)

MMF F (AT)

R (Ω)

R (reluctance) (AT/wb)

$$I = \frac{E}{R}$$

$$\Phi = \frac{F}{R}$$

$$R = g \frac{l}{A}$$

$$R = \frac{l}{MA}$$

$\sum i = 0$ at a junction

$\sum \Phi = 0$


~~$$\sum i = 0$$~~

$\sum V = 0$ around a loop.

$\sum f = 0$ • (MMF \rightarrow $\mu_0 A$ (AT))

voltage drop, $i R$, drop of R

⇒ example :-

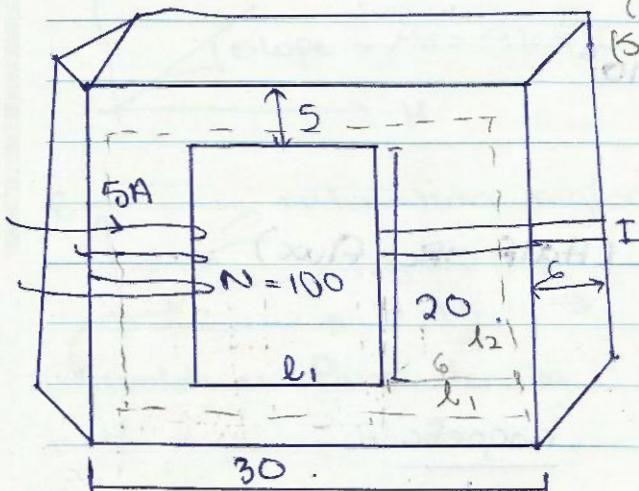


(Linear Relationship)

(Solve like this)

$$M_r = 2000$$

Find R_g in air gap

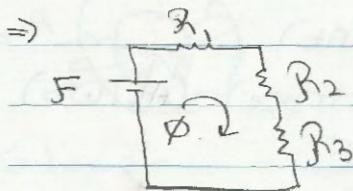

$$l_1 = 24 \times 2 = 48 \text{ cm}$$

$$(24 \text{ from } (30 - \frac{6}{2} - \frac{6}{2}))$$

$$l_2 = 25 \times 2 = 50 \text{ cm} = 0.5 \text{ mm}$$

$$A_2 = 4 \times 6 = 24 \text{ cm}^2 = 24 \times 10^{-4} \text{ m}^2$$

$$A_1 = 4 \times 5 = 20 \text{ cm}^2 = 20 \times 10^{-4} \text{ m}^2$$

$$l_3 = 0.001 \text{ cm}^2, A_3 = A_2 = 24 \times 10^{-4} \text{ m}^2$$

$$\frac{R_1 = 0.48}{2000 M_0 \times 20 \times 10^{-4}} = \frac{0.12}{\mu_0} \Rightarrow \Phi = \frac{5000}{\frac{0.12}{\mu_0} + \frac{0.104}{\mu_0} + \frac{0.416}{\mu_0}}$$

$$\frac{R_2 = 0.5}{2000 M_0 \times 24 \times 10^{-4}} = \frac{0.104}{\mu_0} \Rightarrow \frac{5000 M_0}{0.64} = \frac{5000 \times 4\pi \times 10^{-7}}{0.64}$$



$$= 9.81 \text{ mwb}$$

$$\Rightarrow R_3 = \frac{0.001}{M_0 \times 24 \times 10^{-4}} = \frac{0.416}{M_0}$$

$$B_g = \frac{9.81 \times 10^{-3}}{24 \times 10^{-4}} = 4.1 T$$

$$f = 5 \times 1000 = 5000$$


⇒ example :

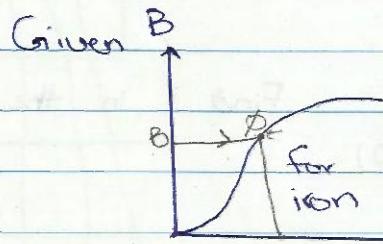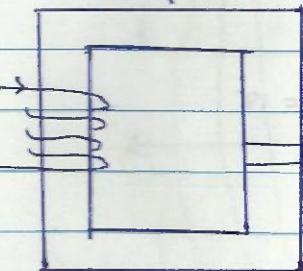

Non-linear
Relationship
can't solve
(like before, M_0 not
constant).

Given ϕ Required R_3 .

Given B , I_i , I_g , & A .

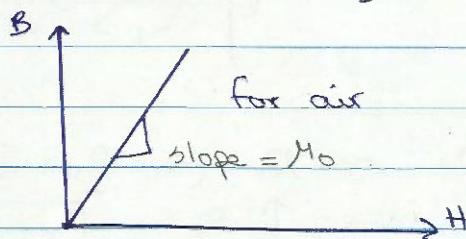

⇒ I find $B_g = \frac{\phi}{A}$

$$H_g = \frac{B}{M_0}$$

From graph:- H_i


$$N_i = S, H_i$$

$$= H_i I_i + H_g I_g$$

⇒ Now the given is : i & Required ϕ .


$$N_i = H_i I_i + H_g I_g$$

$$N_i = H_i I_i + \frac{B}{M_0} I_g$$

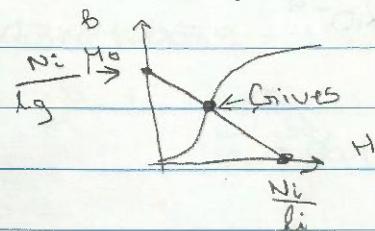

$$\Rightarrow \frac{N_i}{I_i} = H + \frac{B}{M_0} \frac{\lg}{I_i}$$


⇒ example :-

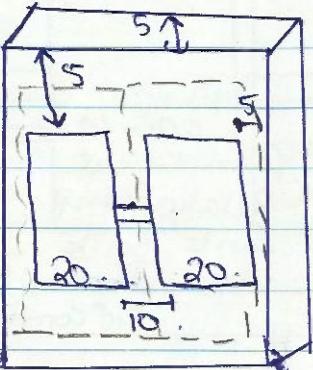

Find i in the $B_g = 1T$.

$$H_r = 1500$$

→

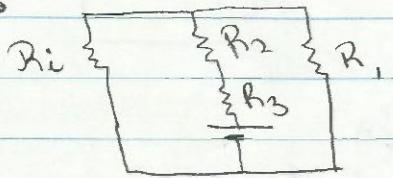

$$l_1 = (20 + \frac{10}{2} + \frac{5}{2}) \times 2 + \left(\frac{30+5}{2} + \frac{5}{2} \right)$$

$$= 90 \text{ cm} = 0.9 \text{ m}$$

$$l_2 = \left(\frac{30+5}{2} + \frac{5}{2} \right) = 33 \text{ cm} = 0.33 \text{ m}$$

$$A = 25 \times 10^{-4} \text{ m}^2$$

$$A_2 = A_3 = 50 \times 10^{-4} \text{ m}^2$$

$$\Rightarrow R_t = R_2 + R_3 + R_i // R_t$$


$$= \frac{0.9}{1500 M_0 \times 25 \times 10^{-4}} + \frac{0.35}{1500 M_0 \times 50 \times 10^{-4}} + \frac{0.001}{M_0 \times 50 \times 10^{-4}}$$

$$= 291784 \text{ A/m}$$

$$\Phi = 1 \times 50 \times 10^{-4} = 5 \times 10^{-3}$$


$$N_i = 1000 i = \Phi R = 5 \times 10^{-3} \times 291784$$

Fringing
Iron. $i = 1.45 A$

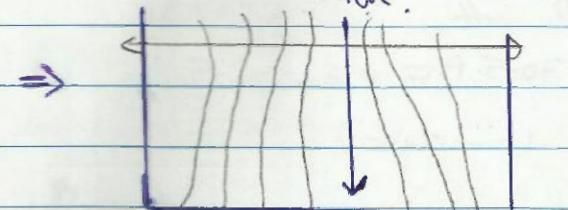

$$\text{Fringing factor} = \frac{A_i}{A_g}$$


≈ 1

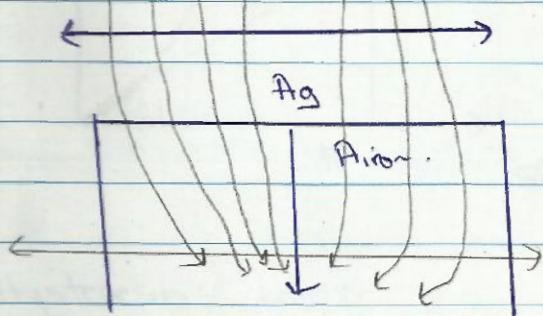


(Area of air) $>$ Area of iron)

(The greater the area the greater the fringing)

⇒ example:-

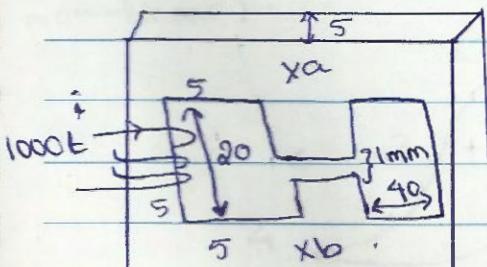

Given.

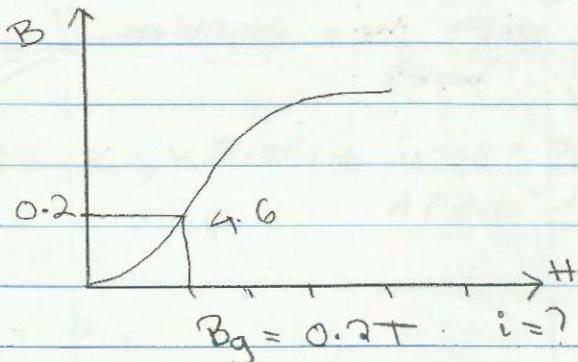


⇒ Linear.

⇒ Non-linear:

$$A_m = 10 \times 5 \times 10^{-4} = 0.005 \text{ m}^2$$
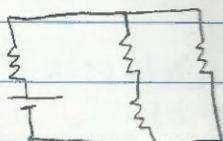
$$\Phi_m = 0.2 \times 0.005 = 1 \text{ mwb}$$



$$F_{lab} = H_m l_m + H_g l_g$$

from graph

$\Phi_m B_g$

for $B_m = 0.2$

$$H_m = 4.6$$

$$l_m = 25 \text{ cm} = 0.25 \text{ m}$$

$$R_g = \frac{0.001}{4\pi \times 10^{-7} \times 0.005} = 159000$$

$$f_{ab} = 4.6 \times 0.25 + 159000 \times 10^{-3} = 70.5 \text{ AT} = 1 \text{ m}$$

$$l_r = 47.5 \times 2 + 25 = 120 = 1.2 \text{ m} \quad (r \rightarrow \text{right})$$

$$H_r = \frac{170.5}{1.2} = 142 \text{ AT/m}$$

$$B_r = 0.9 \text{ T}$$

$$A_r = 5 \times 5 \times 10^{-4}$$

$$\Phi = 0.9 \times 25 \times 10^{-4} = 2.25 \text{ mWb}$$

$$\Phi_L = 2.25 \times 10$$

$$B_L = \frac{3.25 \times 10^{-3}}{2.5 \times 10^{-4}} = 1.3 \text{ T}$$


From graph $H_L = 200 \text{ AT/wb}$
(in book)

$$1000E = 300xi + 170.5$$

$$i = 0.59 \text{ A}$$


→ We defined $B = MH$

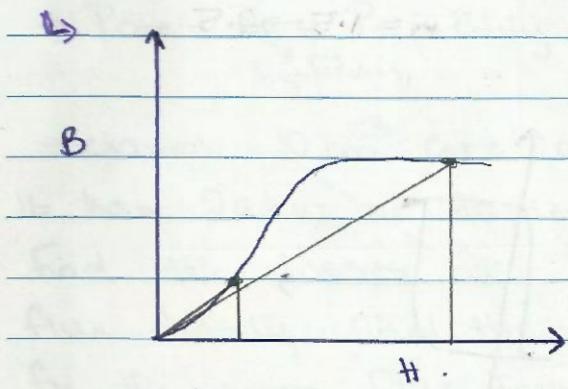↳ $M = \frac{B}{H}$ (note that this is not the slope of the curve, it's dividing the B -coordinate over the H -coordinate).




⇒ Hysteresis's Loop:-

(makes the current non-linear)

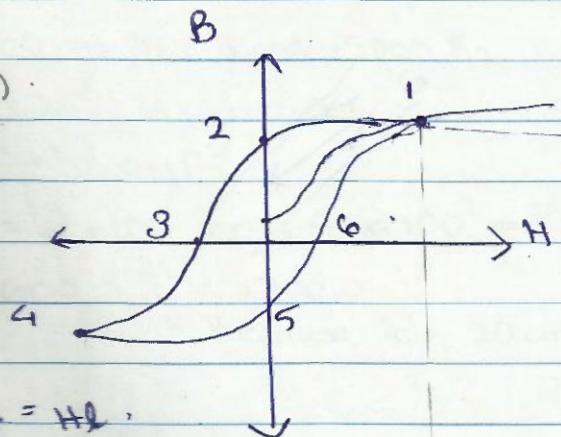

$$F = Ni = HL$$


$$H = \frac{Ni}{L}$$

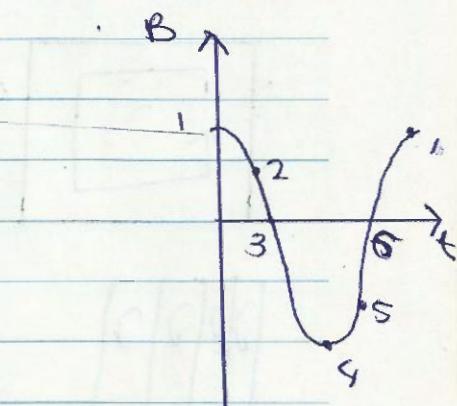

$$(H + \Delta i)$$

$$\cos^2 \theta = \frac{N d\phi}{dt}$$

IF this
is sine

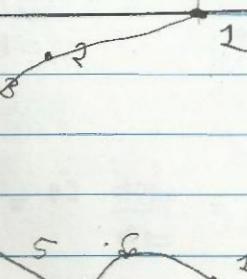



↳ Distorted f phase shift of 90° .

⇒ Hysteresis's Loss:

(The greater the B_{max} , the more the power loss)

For ac $\rightarrow P_h = k_h B_{max}^n F T$ where n is usually with frequency.




$$n = 1.5 \rightarrow 2.5.$$

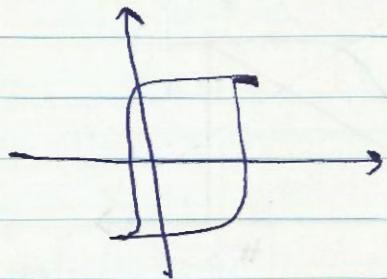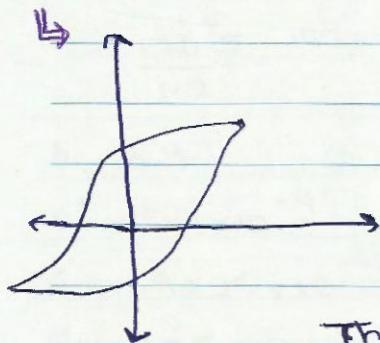

The difference n makes.

{Volume $\uparrow \rightarrow$ losses \uparrow }.

⇒ Eddy Current Loss :-

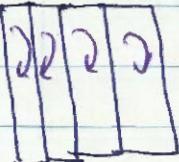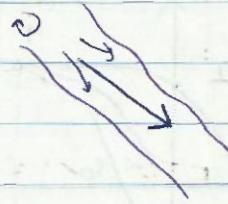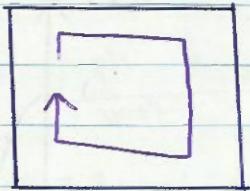

$$* P_h = K_h B_{max}^n f \cdot v \quad (n = 1.5 \rightarrow 2.5)$$

$$P_c = K_c B^2 \max F^2 t^2 \cdot v$$

total hysteresis loss + Eddy Current loss (from core loss) + Jc loss

$$* P_{core} = P_h + P_e \rightarrow \text{eddy hysteresis}$$

example: 10 cm³ core at 50 Hz, total loss = 200 W.

It has 264 W at 60 Hz & Contains Flux density.

Find the losses for 20 cm³ at 100 Hz for same flux density. Find the losses for 20 cm³ at 100 Hz for the same flux density.

$$P = K_1 f + K_2 f^2$$

$$200 = 50K_1 + 2500 K_2 \times 6$$

$$264 = 60K_1 + 3600 K_2 \times 5$$

$$\hookrightarrow 1200 = 300K_1 + 15000 K_2$$


$$K_1 = 2, K_2 = 0.04$$

$$P = 2f + 0.04f^2$$


$$P_{100} = 2 * 100 + 0.04 * 100^2 = 600 \text{ W}$$

$$P = 600 \times 2 = 1200 \text{ W}$$

Because it's 20 cm³

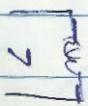

$$V = L \frac{di(t)}{dt}$$

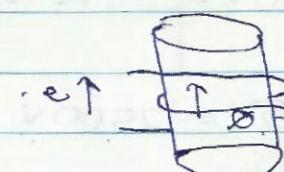


$$e = N \frac{d\phi}{dt}$$

$$\phi = \frac{1}{N} \int e \cdot dt$$


$$\therefore L = \frac{di(t)}{dt} = N \frac{d\phi}{dt} = \frac{d(N\phi)}{di}$$

$$L = N \frac{d\phi}{di}$$

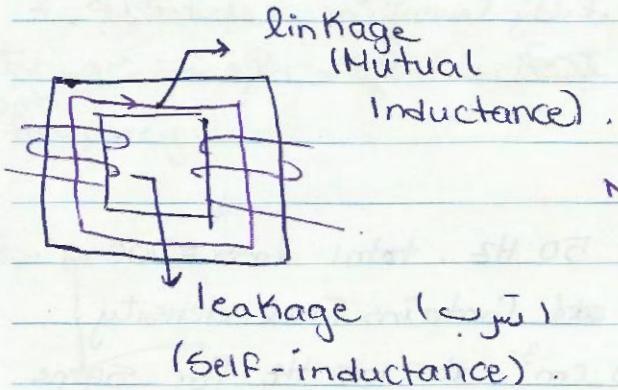
$$\lambda = N\phi \rightarrow \text{Flux linkage}$$



No.

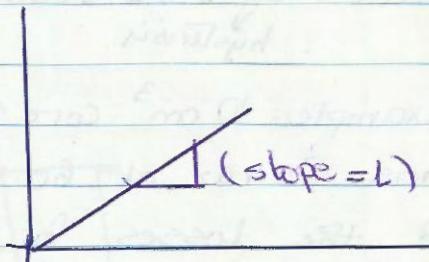

(1-16)

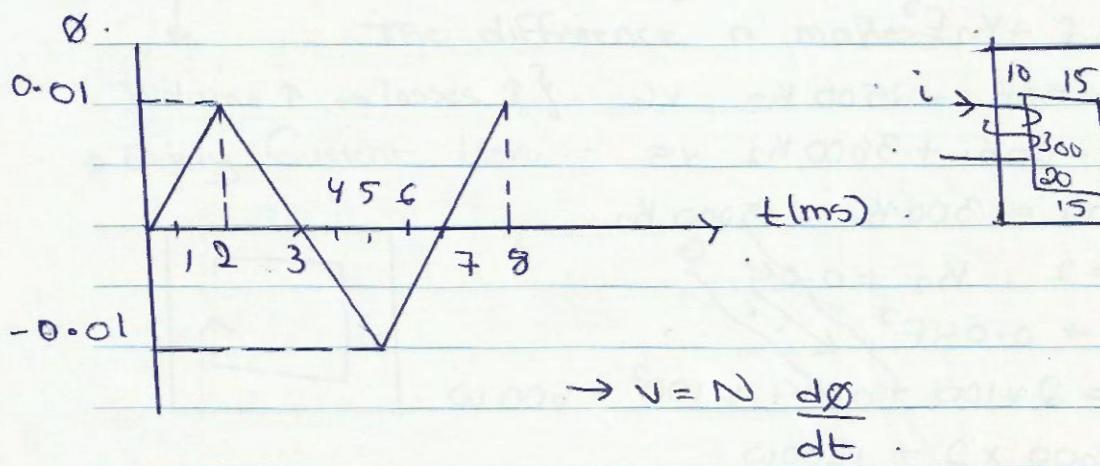

$$\rightarrow V = N \frac{d\phi}{dt}$$

$$\phi = kt$$

$$= \frac{0.01}{0.002} t = 5t \quad (t: 0 \rightarrow 2 \text{ ms})$$

$$V = 500 * 5 = 2500V$$

$$\phi = At + B$$

$$0.01 = A * 0.002 + B$$

$$-0.01 = A * 0.005 + B$$

$$0.02 = -0.003A$$

$$A = -6.67 \rightarrow$$

$$B = 0.01 + 6.67 * 0.002 = 0.023$$

$$\phi = -6.67t + 0.023$$

$$e = 500 * (-6.67) = -3330 \text{ V}$$

$$\phi = At + B$$

$$0 = A * 0.007 + B \quad (t: s \rightarrow 7 \text{ ms})$$

$$-0.01 = A * 0.005 + B$$

$$0.01 = 0.002A$$

$$A = 5, B = -0.35$$

$$\phi = 5t - 0.35$$

$$v = 500 * 5 = 2500 \text{ V}$$

$$\phi = At + B$$

$$0 = A * 0.007 + B$$



$$0.001 = A * 0.008 + B$$

(t: 7 → 8 ms)


$$A = 10$$

$$B = 0.007$$

$$v = 500 * 10 = 5000 \text{ V}$$

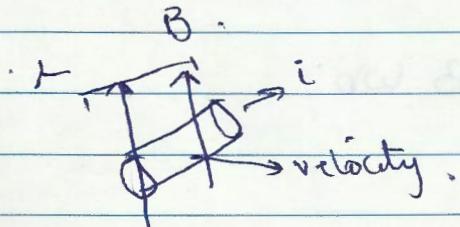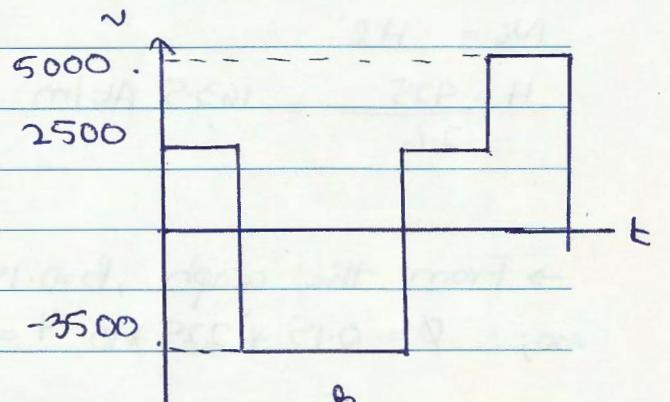

* Generator. $e = Blv$.

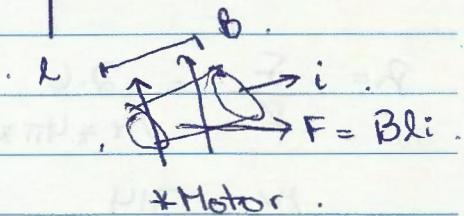

$$1-7) \quad l = (50 + \frac{15}{2} + \frac{15}{2}) * 2 + (50 + \frac{15}{2} + \frac{15}{2}) * 2$$

$$= 2.6 \text{ m}$$

$$A = 15 * 15 * 10^{-4}$$


$$R = 2.6$$

$$\frac{100 * 4\pi * 10^{-7}}{225 * 10^{-4}}$$

$$= 91960 \text{ At} \text{ wb.}$$


$$i_1 = 0.5 \text{ A}$$

$$400t$$

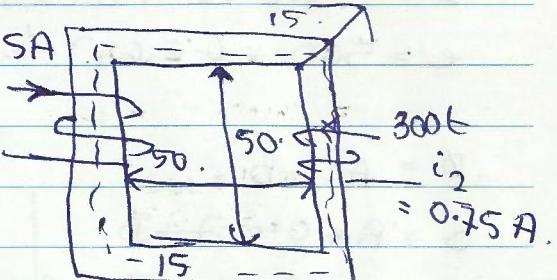

$$\mu_r = 1000$$
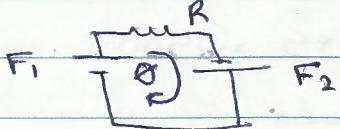
$$\Phi = \frac{400 * 0.5 + 300 * 0.75}{91960} = 4.62 \text{ mwb}$$




1-12)

$$F_{\text{tot}} = 400 * 0.5 + 300 * 0.75 \cdot B$$

$$= 425 \text{ At}$$

$$N_i = Hl.$$
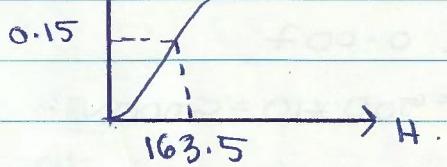
$$H = \frac{425}{2.6} = 163.5 \text{ At/m.}$$



→ From the graph, $b = 0.15 \text{ T}$

$$\text{so; } \Phi = 0.15 * 225 * 10^{-4} = 0.0033 \text{ wb.}$$

$$R = \frac{F}{\Phi} = \frac{2.6}{\mu_r * 4\pi * 10^{-7} * 225 * 10^{-4}}$$

$$\mu_r = 714.$$


$$1-14) \quad B = 0.5 T$$

$$A_g = 5 \times 5 \times 10^{-4} \times 1.05$$

$$\emptyset = 0.5 + 25 \times 10^{-4} \times 1.05$$

$$= 0.00131 \text{ Wb}$$

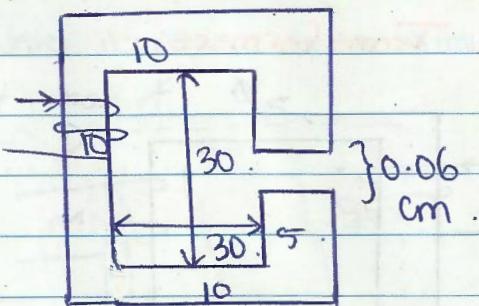
$$B_i = \frac{0.00131}{5 \times 5 \times 10^{-4}} = 0.524 T$$




$$B_{\text{upper}} = B_{\text{left}} = \frac{0.00131}{5 \times 10 \times 10^{-4}} = 0.262 T$$

$$F = 160 \times 0.24 + 70 \times 0.72 \\ = 88.8$$

$$i = \frac{88.8}{400} = 0.22 A$$

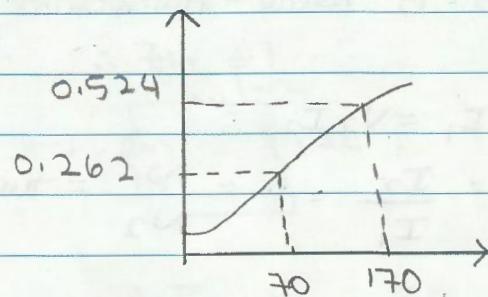

* Transformers:-

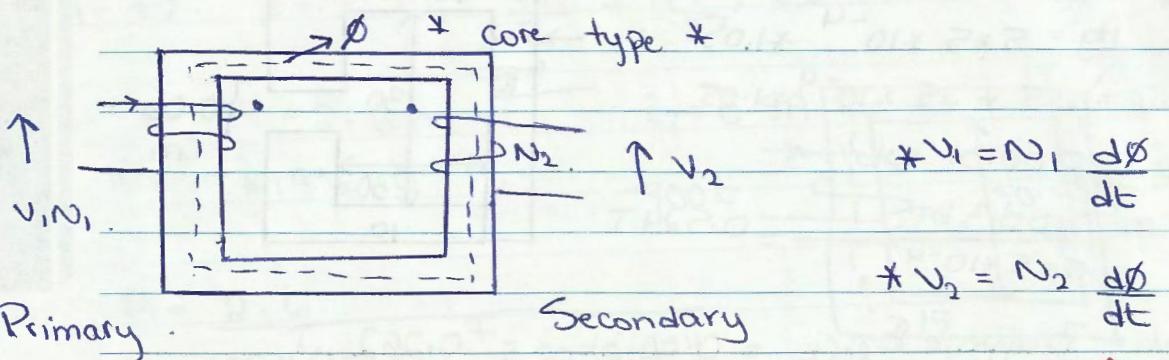

$$* V_1 = N_1 \frac{d\phi}{dt}$$

$$* V_2 = N_2 \frac{d\phi}{dt}$$

$$\therefore \frac{V_1}{V_2} = \frac{N_1}{N_2}$$

→ This is ideal transformer.

$$V_1 I_1 = V_2 I_2$$


$$\frac{V_1}{V_2} = \frac{I_2}{I_1} = a = \frac{N_1}{N_2} = \text{turns-ratio}$$

⇒ a > 1 ... step down $V_1 > V_2$.

a < 1 ... step up $V_1 < V_2$.

$$\boxed{\frac{I_1}{I_2} = \frac{1}{a}}$$

$$\therefore Z_L = \frac{V_2}{I_2}$$

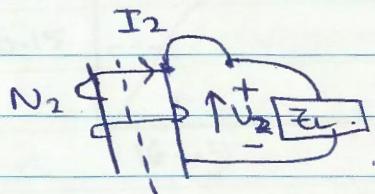


$$\rightarrow V_1 = a V_2$$

$$\rightarrow I_1 = \frac{I_2}{a}$$

$$\therefore Z_{in} = a^2 Z_L$$

$$\boxed{\frac{V_1}{I_1} = \frac{a^2 V_1}{I_2} = a^2 Z_L}$$

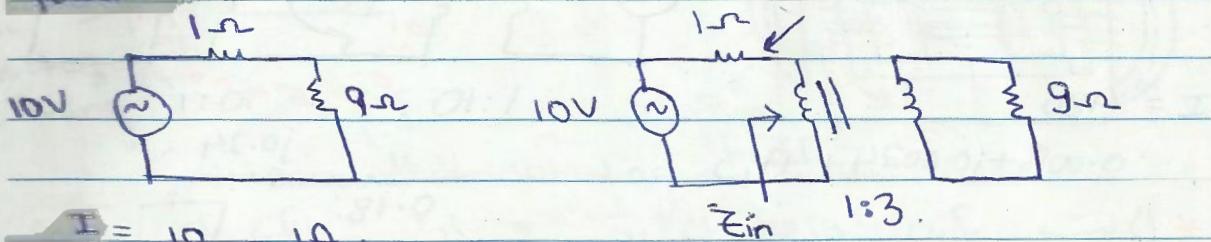→ Impedance matching:- we use it give a maximum power.



$$I = \frac{10}{1+9} = 1A$$

$$P = I^2 * g = 9W$$

$$\alpha = \frac{1}{3}$$

$$\alpha * Z_L = 9 * (1/3)$$

→ P_B > P_A.

$$\therefore Z_{in} = \frac{1}{1-j2}$$

$$|Z_L| = |Z_{in}|, \angle Z_L = -\angle Z_{in}$$



النواتي المترافق تحقق اذا

maximum -ji use جي

للتوصيل يتحقق تحقق

-ji و j


$$\therefore I = \frac{10}{1+j1} = 5A$$

$$P_B = 5^2 * 1 = 25W$$


→ example: $I = \frac{480 \angle 0}{0.18 + j0.24 + 4 + j3}$

$$V_{load} = 90.8 \angle -37.8^\circ * (4+j3) * 480 \angle 0^\circ$$

$$= 454 \angle -0.90^\circ$$

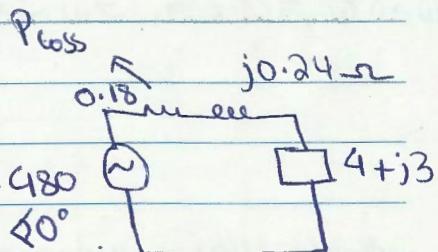
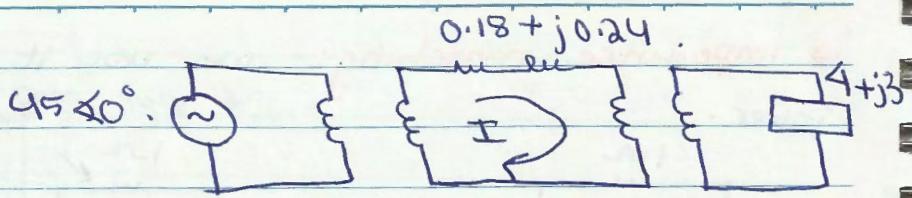
$$P_{loss} = I^2 R_L = 90.8^2 * 0.18 = 1484 W$$



$$I = 480$$

$$0.0018 + j0.0024 + 4 + j3$$

$$1:10 \quad 10:1$$

$$\frac{0.18}{0.18} \quad 10:1$$

$$j0.24$$


$$Z_{in}$$


$$P = 95.94^2 * 0.0018 = 16.7 \text{ W}$$

$$Z_{in} = 10^2 * (4 + j3)$$

$$= 400 + j300$$

$$0.0018 \quad j0.0024$$

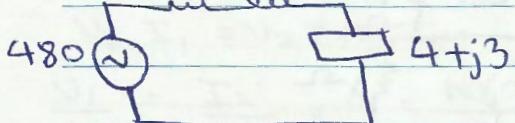

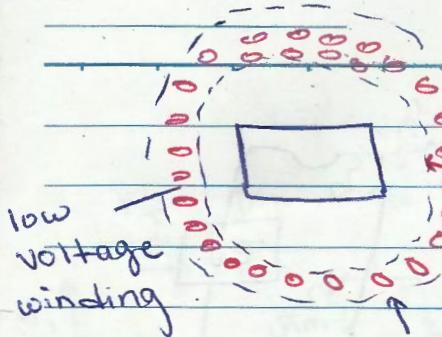


insulators

H.V. winding

* الائچيت يكون ماحفظ ايجاره وعوارض الالكتريكيات

(3-Φ)

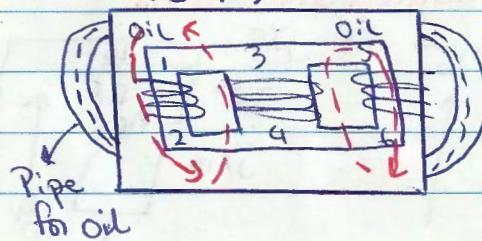

* اذا ازتمحنت درجة الحرارة فتؤدي ذلك
إلى تغير مادة السفع المغناطيسي فيها العازل
وعند تغير درجة الحرارة تؤدي ذلك
مادحة السفع إلى حدوث تسرب
"winding" - إلإ في "short chrt" gives وذلك

* losses in core depends on voltage.


* losses in Copper depends on current.

$$L = N \frac{d\phi}{dt}, e = N \frac{d\phi}{dt}, \phi = \phi_m \sin \omega t, e = N \phi_m \omega \cos \omega t.$$

$$\boxed{\phi_{tot} = \phi_{residual} + \phi_{linkage}}$$

* the current between primary & secondary will make a phase shift by 90° .

* Equivalent Circuit

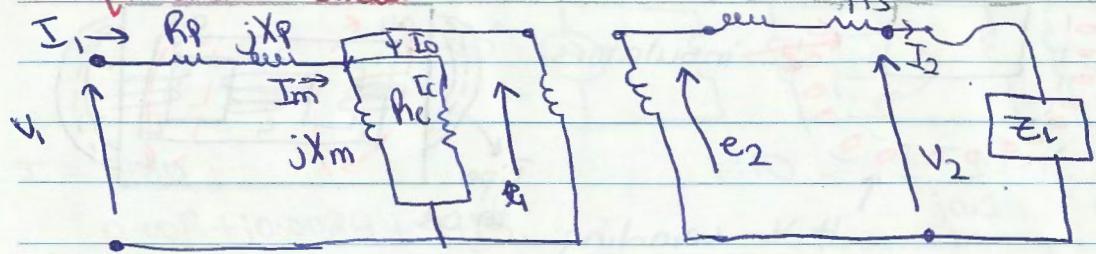

$N_1:N_2$

$\alpha:1$

$V \uparrow \rightarrow I \downarrow \rightarrow A \downarrow$




High \rightarrow very thin
otherwise it will be low.

* This is the exact equivalent circuit, *


* R_c : Core resistance

* X_m : magnetizing reactance


* I_0 : no load current

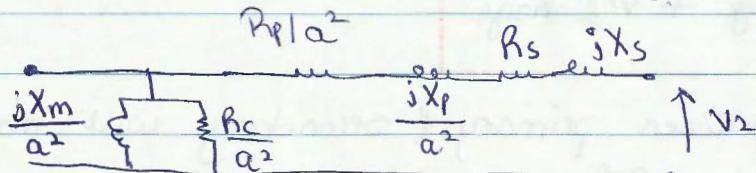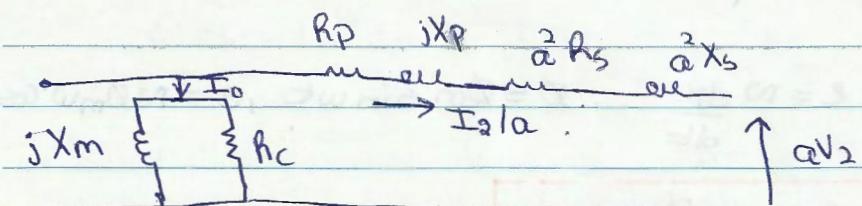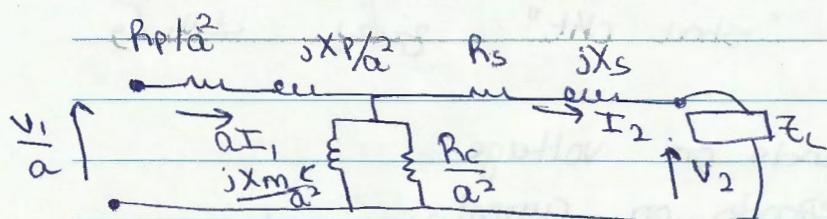

Monday
10th of March, 2013.

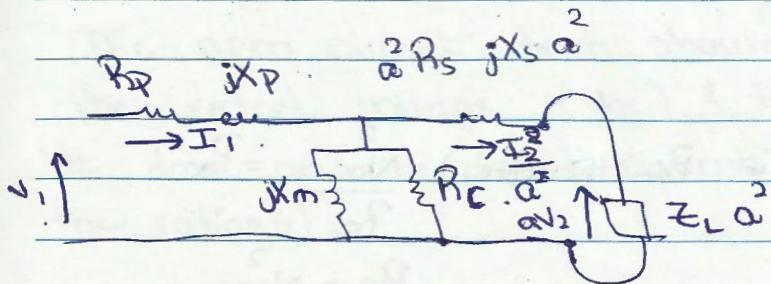

$$R_{eq} = R_p + \alpha^2 R_s$$

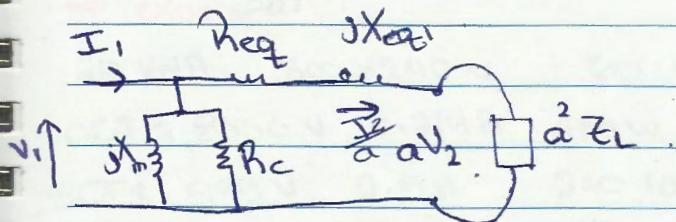


$$X_{eq} = X_p + \alpha^2 X_s$$

* Ratings :

1) 100 KVA · 2) 1100/400 (the first is the first voltage decided, but this doesn't mean that we can't use it 400/1100 → it becomes a step-down transformer).

3) freq. = 50 Hz.

* Testing of Transformers:

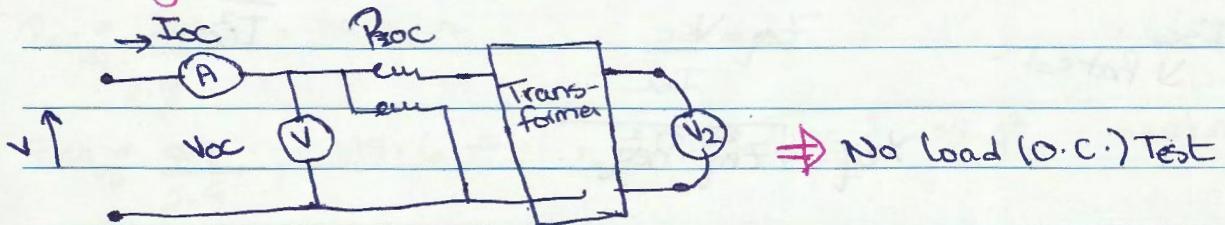

⇒ No Load (O.C.) Test

$$\alpha = \frac{V_{oc}}{\sqrt{2}}$$

* Note :-

The open circuit test should be done on the rated voltage (V_{oc}) & the s.c. test should be done on the rated current ($I_{sc} \Rightarrow$ from the ratings)

⇒ example :-

20 kVA 3000/240 V 60 Hz

OCT: 3000 V 0.214 A 400 W

SCT: 489 V 2.5 A 240 W

$$I_{\text{Rated H}} = \frac{20,000}{8000} = 2.5 \text{ A}$$

$$400 = \frac{8000^2}{R_c}, R_c = 160 \text{ k}\Omega$$

$$I_c = \frac{8000}{160,000} = 0.05 \text{ A}$$

$$I_m = \sqrt{0.214^2 - 0.05^2} = 0.21 \text{ A}$$


$$X_m = \frac{8000}{0.21} = 38.4 \text{ k}\Omega$$

These values are referred to high voltage.

$$R_{eq} = \frac{240}{2.5^2} = 38.4 \Omega$$

$$Z_{eq} = \frac{489}{2.5} = 195.6 \Omega, X_{eqH} = \sqrt{195.6^2 - 38.4^2} = 192 \Omega$$

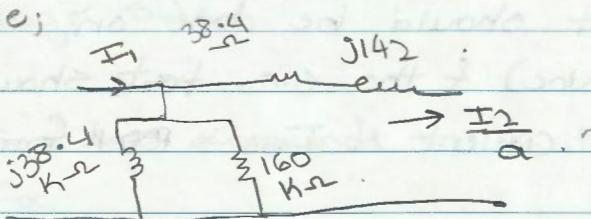So the equivalent circuit, referred to the high voltage side;



$$a = \frac{8000}{240} = 33.3$$

$$R_{CL} = \frac{160 \cdot 1000}{33.3^2} = 144.3 \Omega$$

$$X_{WL} = \frac{38400}{33.3^2} = 34.6 \Omega$$

$$R_{eq_L} = \frac{38.4}{33.3^2} = 0.034 \Omega$$

$$X_{eq_CL} = \frac{192}{33.3^2} = 0.17 \Omega$$

* Per Unit Systems:-

per unit value = Actual Value

(It doesn't have a unit)

Rated Value. (or Base Value).

If this applies to all values in transformer I have 4 values: I_1, V, P, Z

(I'm given two values, & I calculate the other two).

Since I have high voltage & low voltage, I get 4 values, \rightarrow current high & current low.

⇒ examples

$$P_{base} = 20 \text{ kVA}$$

$$\sqrt{V_{base}} H = 8000 \text{ V}$$

$$I_{base} H = \frac{20,000}{8000} = 25 \text{ A}$$

$$Z_{base} H = \frac{8000}{2.5} = 3200 \text{ Ω}$$

$$\sqrt{V_{base}} L = 240 \text{ V}$$

$$I_{base} L = \frac{20,000}{240} = 83.3 \text{ A}$$

$$Z_{base} L = \frac{240}{83.3} = 2.88 \text{ Ω}$$

$$\hookrightarrow \text{Now; } R_{Cpu} = \frac{160,000}{3200} = 50$$

$$X_m pu = \frac{38.4 \text{ k-Ω}}{3200} = 12$$

$$R_{eq. pu} = \frac{38.4 \text{ Ω}}{3200} = 0.012$$

$$X_{eq. pu} = \frac{192}{3200} = 0.06$$

⇒ Now taking the low values:

$$R_{Cpu} = \frac{144.3}{2.88} = 50$$

$$X_m pu = \frac{34.6}{2.88} = 12$$

$$R_{eq. pu} = \frac{0.034}{2.88} = 0.012$$

$$X_{eq. pu} = \frac{0.17}{2.88} = 0.06$$

*Note:

Therefore the






per unit values

for high & low
are the same

so the per unit
values are independent
of high & low.

* Voltage Regulation:-
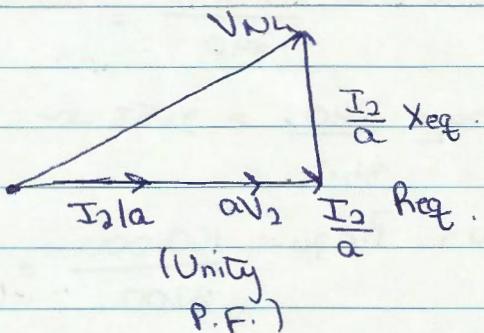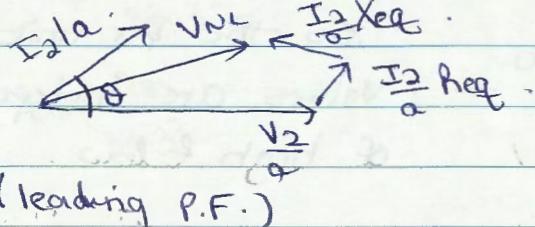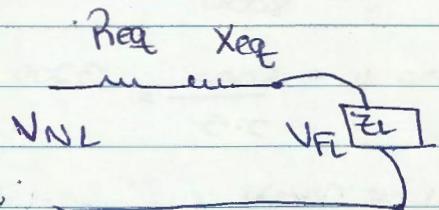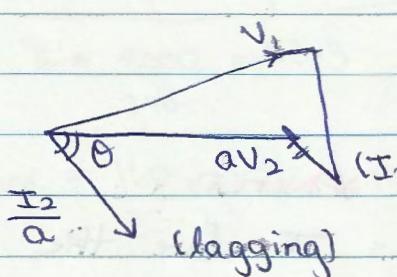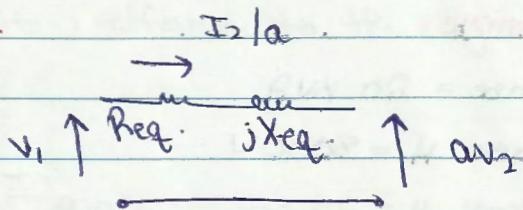
$$\frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$



$$V_1 \approx aV_2 + \frac{I_2}{a} R_{eq} \cos\theta + \frac{I_2}{a} X_{eq} \sin\theta$$

$$V.R. = \frac{V_{NL} - V_{FL}}{V_{FL}} = \frac{\frac{I_2}{a} R_{eq} \cos \theta + \frac{I_2}{a} X_{eq} \sin \theta}{a V_2}$$

$$= I_{P.U.} [R_{eq} p.u. \cos\theta + X_{eq} \sin\theta] .$$

Find V_R at full load : 0.8 p.f. lagging
 $3000/240$ 1 p.f.

R_{eq} 38.4Ω

0.8 p.f. leading

X_{eq} 192Ω

$R_{eq} P.U. = 0.012$

$X_{eq} P.U. = 0.06$

$$I_{FLH} = 2.5 A, I_{FLL} = \frac{20,000}{240} = 83.3 A$$


$$I_{FL} \rightarrow I_{P.U.} = 1$$

$$V.R_1 = 1 [0.012 * 0.8 + 0.06 * 0.6] = 0.0456 = 4.56\%$$

$$V.R_2 = 1 [0.012 * 1 + 0] = 0.012 = 1.2\%$$

$$V.R_3 = 1 [0.012 * 0.8 + -0.06 * 0.6] = -0.0026 = -2.6\%$$
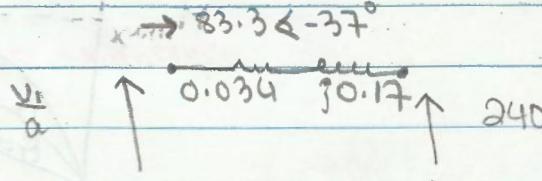
$$V.R.1 = \frac{83.3}{240} \left[\frac{38.4}{33.3} * 0.8 + \frac{192}{33.3^2} * 0.6^2 \right]; a = \frac{8000}{240}$$



$$\frac{V_1}{a} = 240 + 83.3 [0.8 - j0.6] (0.34 + j0.17)$$


$$= 250.9 \angle 5.5^\circ$$

$$\frac{250.9 - 240}{240} = 0.0454 V$$

$$V_1 = 250.9 * 33.3 = 8354 V \quad (\text{Original voltage})$$

$$V.R_3 = 1 [0.012 * 0.8 - 0.06 * 0.6] = -0.026 = -2.6\%$$

* Efficiency :

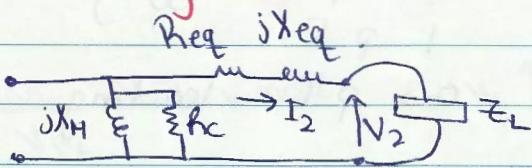

$$*\eta = \frac{P_{out}}{P_{in}} * 100\%.$$

$$* P_{in} = P_{out} + P_{loss}$$

$$* P_{out} = V_2 I_2 \cos \theta .$$

* air gap \rightarrow no losses .

* the losses are in the core f ~~Copper~~

$$* P_{loss} = I_2^2 R_{req} + P_C$$


$\stackrel{\text{depends}}{=}$ Power constant (P_{NL})

on load .

$$\eta = \frac{V_2 I_2 \cos \theta}{V_2 I_2 \cos \theta + P_{NL} + I_2^2 R_{req}} * 100\%.$$

$$\frac{dM}{dI_2} = 0$$

$$\frac{dM}{d\theta} = 0 .$$

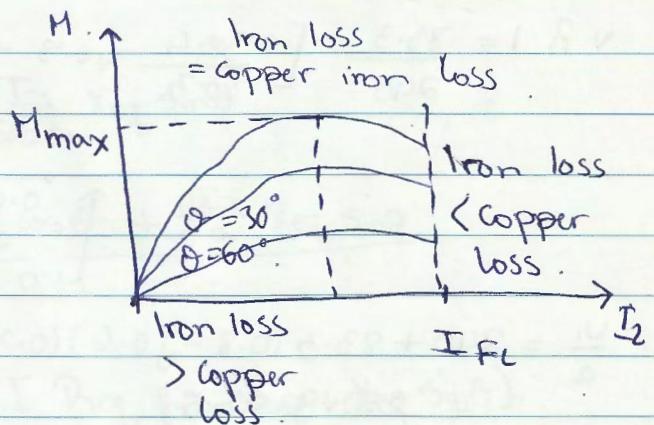

* For max. M


$$\theta = 0 .$$

$$I_2^2 R_{req} = P_{NL} .$$

* Iron loss is copper

$$*\eta_{\max}$$
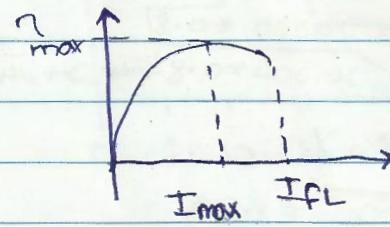
$$\eta = \frac{VI \cos \theta}{\sqrt{I^2 \cos^2 \theta + P_i + I^2 R_{\text{req}}}}$$



$$\eta = \frac{VI \cos \theta}{\sqrt{I^2 \cos^2 \theta + 2P_i}} = \frac{K \cos \theta}{K \cos^2 \theta + 2P_i}$$

$$\frac{VI \cos \theta}{\sqrt{I^2 \cos^2 \theta + 2P_i}} = \frac{K \cos \theta}{K \cos^2 \theta + 2P_i}$$

$$= K I_F L$$

$$+ \frac{P_i}{K} = P_U$$

Max η occurs when: $P_i = P_{cc}$

$$P_i = I_{\max}^2 R_{\text{req}}$$

$$P_i = P_{cc} = I_{\max}^2 R_{\text{req}}$$

$$I_{\max} \eta = \sqrt{\frac{P_i}{R_{\text{req}}}}$$

$$P_{sc} = I_F L R_{\text{req}}$$

$$\frac{I_{\max} \eta}{I_F L} = K = \sqrt{\frac{P_{cc}}{P_{sc}}}$$

$$\frac{I_{\max} \eta}{I_F L} = K = \sqrt{\frac{P_{cc}}{P_{sc}}}$$

η
full
load

values from previous example:-

$$KVA = 20$$

$$P_{sc} = 240$$

$$P_{cc} = 400$$

$$R_{eqH} = 38.4$$

$$R_{eqL} =$$

$$R_{eqL} = 0.034$$

$$X_{eqL} =$$

η at 0.8 p.f.

$$I_{FL} = 2.5 \text{ A}$$

$$\hookrightarrow \eta_{FL} = \frac{20000 * 0.8}{20000 * 0.8 + 400 + 240} \\ = 96\%$$

$$K = \sqrt{\frac{400}{240}} = 1.29$$

$$\eta_{max} = \frac{20000 * 0.8 * 1.29}{20000 * 0.8 * 1.29 + 2 * 400} = 96.3\%$$

$$P_{max} = 20000$$

$$P_{pu} = \frac{400}{20000} = 0.02$$

$$* P_{CLFL} = I_{FL}^2 R_{req}$$


↓
Copper
loss

$$* P_{Cpu} = R_{req} \cdot pu$$

$$* R_{pu} = \frac{V_{pu}}{I_{pu}} = \frac{1}{R_{req} \cdot pu}$$

* All day efficiency :-
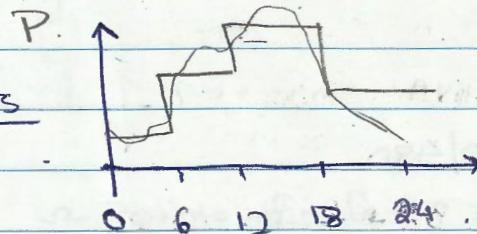
$$\% = \frac{\text{Output of energy in 24 hrs}}{\text{input " " " "}}$$



\Rightarrow 6 hours at no load.

7 hours at $\frac{1}{2}$ full load 0.9 P.F.

6 hours at $\frac{3}{4}$ full load 0.85 P.F.

5 hours at full load 0.8 P.F.

$$P_{cplu} = \frac{240}{20,000} = 0.012$$

$$P_{cplu} = \frac{400}{20000} = 0.02$$

\Rightarrow All day $\eta = \frac{\sum \text{output 24 hrs}}{\sum \text{input energy} + \sum \text{losses in 24 hrs}}$
in 24 hrs

\hookrightarrow Back to example :-

$$\eta = \frac{0 + 0.5 \times 0.9 \times 7 + \frac{3}{4} \times 0.85 \times 6 + 5 \times 0.8 \times 1}{10.97 + 24 \times 0.02 + 0.012 [0 + (\frac{1}{2})^2 \times 7 + (\frac{3}{4})^2 \times 6 + 1^2 \times 5]} \times 100\%$$

$$= 94.8\%$$

* Problems :

2.1

20 kVA .

8000 / 480 :

$$R_p = 32 \Omega \quad R_s = 0.05 \Omega$$

$$X_p = 45 \Omega \quad X_s = 0.06 \Omega$$

$$R_c = 250 \text{ k}\Omega \quad X_m = 30 \text{ k}\Omega$$

Solve: \downarrow impedance .

$$\frac{\alpha}{\alpha} = \frac{8000}{480} = 16.67$$

$$\alpha^2 R_s = 0.05 \times 16.67^2 = 13.9 \Omega$$

$$\alpha^2 X_s = 0.06 \times 16.67^2 = 16.7 \Omega$$

$$P_{base} = 20,000$$

$$V_{base H} = 8000$$

$$I_{base H} = \frac{20,000}{8000} = 2.5$$

$$Z_{base H} = \frac{8000}{2.5} = 3200 \Omega$$

$$\frac{32}{3200} = 0.01$$



$$\frac{16.7}{3200} = 0.0052$$

$$\frac{45}{3200} = 0.0141$$

$$R_{pu} = \frac{250000}{3200} = 78.125 \text{ p.u.}$$

$$\frac{13.9}{3200} = 0.0043$$
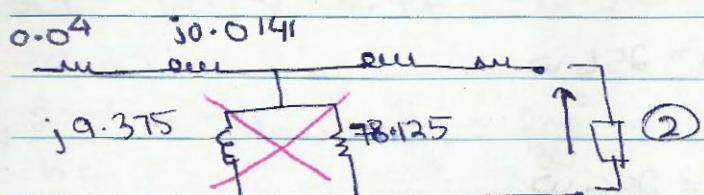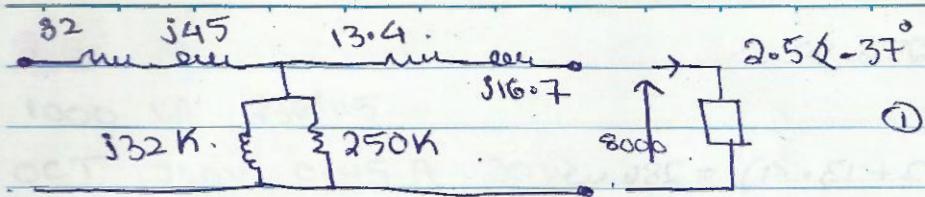
$$X_m = \frac{30,000}{3200} = 9.375 \text{ p.u.}$$



"PU equivalent circuit"

*Note: We found the

p.u. values from
the original equation

Circuit & drew the second
circuit

* After approximation (when I approximate the R & L inside
are crossed out X)

$$\begin{aligned} \rightarrow V_R &= R_{eq} \text{ pu} \cos \theta + X_{eq} \text{ pu} \sin \theta \\ &= 0.0143 * 0.8 + 0.0143 * 0.6 \\ &= 0.023 \end{aligned}$$

\leftarrow Voltage
Regulation.

$$\begin{aligned} \text{where: } R_{eq} \text{ pu} &= 0.01 + 0.0043 \\ &= 0.0143 \end{aligned}$$

$$\begin{aligned} X_{eq} \text{ pu} &= 0.0141 + 0.0052 \\ &= 0.0193 \end{aligned}$$

$$V_R \text{ can also} = \frac{V_{NL} - V_{FL}}{V_{FL}} = \frac{V_{NL}}{V_{FL}} - 1 = 0.023$$

$$\text{where } V_{NL} = (1 + 0.023) V_{FL} = 8000$$

$$V_P = (1 + 0.023) 8000 = 8184$$

$$P_C = \frac{8000^2}{250,000} = 256 \text{ W}$$

$$P_{CL} = 2.5^2 \times (32 + 13 \cdot 4) = 286 \text{ W}$$

$$P_{IPU} = \frac{1}{78.125} \times 20,000 = 256 \text{ W}$$

$$P_{CL} \eta_u = 20,000 \times 0.143 = 286 \text{ W}$$

$$\rightarrow \eta = \frac{20,000 \times 0.8}{20,000 + 0.8 + 256 + 286} \\ = 96.7\%$$

$$\eta = \frac{1 \times 0.8}{1 \times 0.8 + \frac{1}{78.125}} + 0.0143 = 96.7\%$$

* If told to find half the efficiency : the $\frac{1}{78.125}$ doesn't change because it's iron, the 0.0143 is * by $\frac{1}{4}$ ($\frac{1}{2}$)² since it's I^2 & 1×0.8 is * by $1/2$!

$$\rightarrow K = \sqrt{\frac{1}{78.125}} = \sqrt{\frac{256}{286}} = 0.946$$

$$\eta_{max} = 0.946 \times 0.8 = 96.73\% \\ \frac{0.946 \times 0.8 + 2 \times \frac{1}{78.125}}{1}$$

2.6

1000 VA 230/115

OCT 230V 0.45 A 30W

SCT 19.1V 8.7A 42.3W

Solve:

$$a) \frac{230^2}{R_C} = 30, \quad R_C = \frac{230^2}{30} = 1763\Omega$$

$$I_C = \frac{230}{1763} = 0.13$$

(If I want to take
the low values, I
divide by 4).

$$X_H = \frac{230}{I_H} = 534\Omega$$

$$R_{eq} = \frac{42.3}{8.7} = 0.558\Omega$$

$$Z_{eq} = \frac{19.1}{8.7} = 2.2\Omega \quad X_{eq} = \sqrt{2.2^2 - 0.558^2}$$

$$= 2.128\Omega$$

$$b) \frac{1000}{230} = 4.3$$

$$V.R. = \frac{4.3}{230} [0.558 \times 0.8 + 2.128 \times 0.6] = 3.3\%$$

$$\frac{4.3}{230} [0.558 \times 1] = 1.1\%$$

$$\frac{4.3}{230} [0.558 \times 0.8 - 2.128 \times 0.6] = -1.5\%$$

$$n = \frac{1000 \times 0.8}{1000 \times 0.8 + 30 + \frac{4.3^2 \times 0.558}{4.3 \times 0.558}}$$

2.7

$$15 \text{ kVA} \quad 8000/230.$$

$$Z_{eq} = 80 + j300.$$

$$R_c = 350 \text{ ohm}.$$


$$X_m = 70 \text{ ohm}.$$

$$N_p = 7967 / Z_L = 32 + j3 \text{ ohm}.$$

Answer:

$$\alpha = \frac{8000}{230} = 34.8.$$
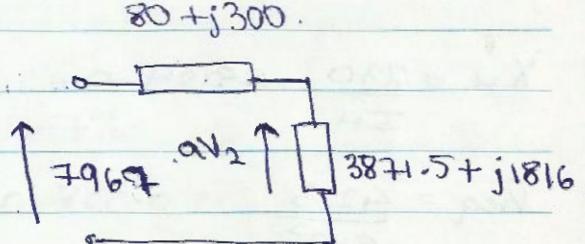
$$Z_{LP} = (3 \cdot 2 + j1.5) \times 34.8^2 \\ = 3871.5 + j1816.$$



$$\alpha V_2 = \frac{7967 * (3871.5 + j1816)}{(3871.5 + 80) + j(1816 + 300)} = 7610.$$

$$\text{V.R.} = \frac{7967 - 7610}{7610} = 4.7\%.$$

$$V_2 = \frac{7610}{34.8} = 218.8 \text{ V}$$

$$X_{ch} = -j3.5 \times 34.8^2 = -j4234$$

$$\alpha N_2 = \frac{7967 (-j4234)}{80 + j300 - j4234} = 8573.$$

$$\text{v.p.} = \frac{7967 - 8573}{8573} = -7.07\% \rightarrow (\text{Current lagging})$$

Q.9

5000 KVA.

230/13.8 KV.

$$Z_{pu} = +j0.05$$

$$\{ V_{ac} = 13.8 \text{ KV}$$

$$\text{L.W. } I_{ac} = 15.1 \text{ A}$$

$$P_{ac} = 44.9 \text{ KW}$$

Answers:

$$R_{CL} = \frac{(13.8 \times 10^2)^2}{44900} = 4240 \Omega$$

$$I_{CL} = \frac{13800}{4240} = 3.25 \text{ A}$$

$$I_{ML} = \sqrt{15.1^2 + 3.25^2} = 14.75 \text{ A}$$

$$X_{ML} = \frac{13800}{14.75} = 936 \Omega$$

$$P_{base} = 5000 \text{ KVA}$$

$$V_{base} = 13.8 \text{ KV}$$


$$I_{base} = \frac{50,000}{13.8} = 362 \text{ A}$$

$$Z_{base} = \frac{13800}{362} = 38.09 \Omega$$

$$Z_{eqL} = (0.01 + j0.05) + 38.09$$

$$= 0.38 + j1.9 \sim$$

$$0.38 + j1.9$$

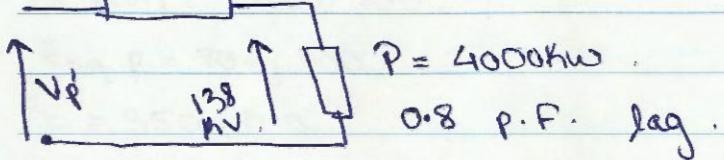

$$I = \frac{4000}{13800 * 0.8} = 362.8 \angle -37^\circ$$

$$V_p = 13800 + 362.8 (0.8 - j0.6) (0.38 + j1.9)$$

$$= 14.33 \angle 1.9^\circ \text{ kV}$$

$$\eta \cdot R = \frac{14.33 - 13.8}{13.8} = 3.84\%$$

$$\eta = \frac{4000}{\frac{4000000 + 14300^2}{4240} + 362.8^2 * 0.38} = 97.6\%$$

Find the max n?




$$K = \sqrt{\frac{44900}{362.8^2 * 0.38}} = 0.94$$

$$\eta_{\max} = \frac{4000000 * 0.94}{4000000 * 0.94 + 49900 * 2}$$

$$= 97.66\%$$



*Note: If I take a device from one country to the other with another frequency :- I multiply the voltage by the freq. ratio ($\frac{230 \times 50}{60}$)

* Auto transformer :

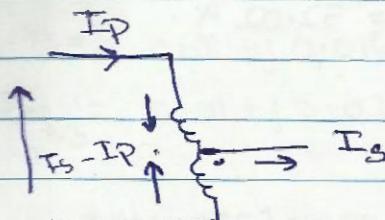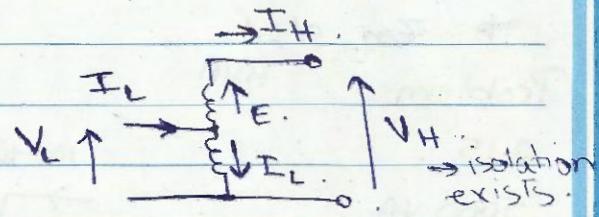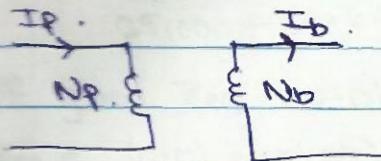


→ this transformer doesn't have isolation


4 Cases :- For every two winding transformer I can get 4 cases:-

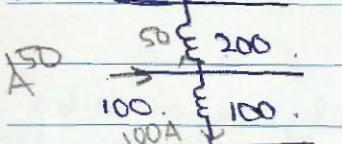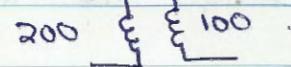1)  $150 \times 100 = 15,000 \text{ VA}$  $\frac{400}{10,000} = 4\%$ losses. therefore $\eta = 96\%$


$$* \text{I rated H} = \frac{10,000}{200} = 50 \text{ A}$$

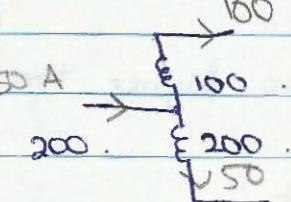2)  $200 \times 150 = 30,000 \text{ VA}$ $= 50 \text{ A}$

$$* \text{I rated L} = \frac{10,000}{100} = 100 \text{ A}$$

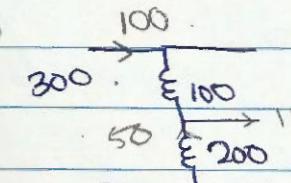3)  $300 \times 100 = 30,000 \text{ VA}$ $\frac{400}{30,000} = 1.33\%$

$$\eta = 98.66\%$$

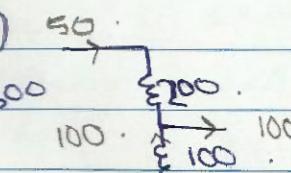4)  $100 + 50 = 150 \text{ A}$

$$10 \text{ A} = 50 \times 300 = 15,000 \text{ VA}$$

$\Rightarrow \text{Zeq} \propto \frac{1}{\text{KVA}}$


Problems

2.15 :

5000 VA.

480/120 V.

600 → 120 V.

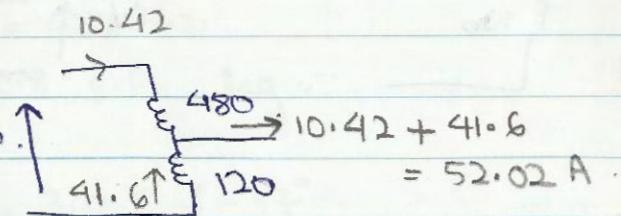


$$\frac{5000}{480} = 10.42 \text{ A}$$

$$\text{KVA} = 52.02 * 120 = 6250 \text{ VA}$$

$$\frac{5000}{120} = 41.6 \text{ A}$$

→ If we change the transformer to this:

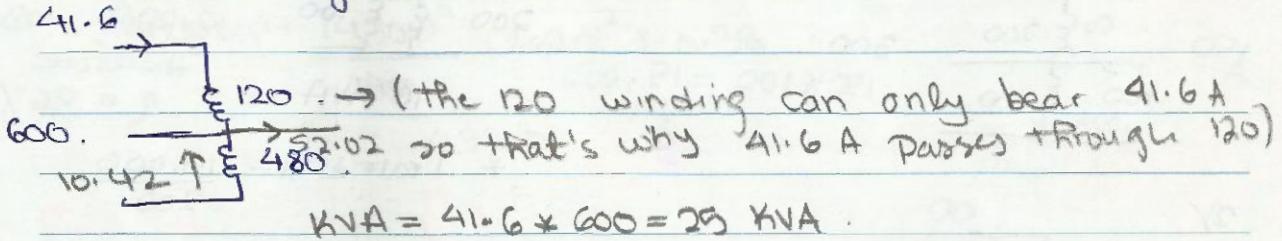

* The closer the percentage is to 1, the higher the profit.

η_{FL} of 2 winding transformer = 97%.

assuming PF = 1;

→ 2 windings $\frac{5000}{5000 + P_{loss}} = 0.97$, $P_{loss} = 154.64 \text{ W}$.

$5000 + P_{loss}$

$$\eta_2 = \frac{6250}{6250 + 154.64} = 97.6\%$$

$$\eta_3 = \frac{25,000}{25,000 + 154.64} = 99.4\%$$

If given $Z_{eq} = 0.01 + j0.02$ p.u.

$$Z_{eq} = (0.01 + j0.02) * \frac{5000}{6250}$$

$$= 0.008 + j0.016 \text{ p.u.}$$

$$Z_{eq_{t3}} = (0.01 + j0.02) * \frac{5000}{25,000}$$

$$= 0.002 + j0.004 \text{ p.u.}$$

Solution to 1st exam:-

$$\textcircled{1} \quad Z_{eq} = 0.015 + j0.025$$

$$R_{CH} = 4000 \Omega$$

$$X_{base H} = 1000$$

$$I_{base} = \frac{100,000}{400} = 250 \text{ A}$$

$$T_{base} = \frac{400}{250} = 1.6 \Omega$$

$$\begin{aligned} Z_{eq_{T2}} &= 1.6(0.015 + j0.025) \\ &= 0.024 + j0.04 \end{aligned}$$

$$\frac{2000}{400} = 5 = \alpha$$

$$R_{CL} = \frac{4000}{5^2} = 160 \Omega$$

$$X_{ML} = \frac{1000}{5^2} = 40 \Omega$$

$$\begin{aligned} V_R &= I_{pu} (R_{eq pu} \cos \theta + X_{eq pu} \sin \theta) \\ &= 1 (0.015 \times 0.8 + 0.025 \times 0.6) \\ &= 2.61 \end{aligned}$$


$$P_{iron} = \frac{2000^2}{400} = 1000 \text{ W}$$

$$P_{SG} = 250^2 \times 0.024$$

$$K = \sqrt{\frac{1000}{1500}} = 0.816$$


$$\begin{aligned} \gamma_{max} &= \frac{1 \times 0.9 \times 0.816}{1 + 0.9 + 0.816 + 2 \times 0.01} \\ &= 97.31 \end{aligned}$$

$\frac{1000}{10,000}$

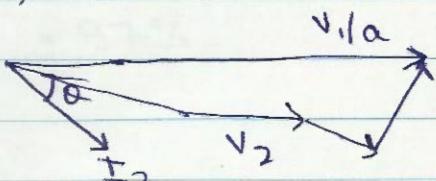

$$\text{all day } \eta = \frac{0.5 + 0.9 + 8 + 0.8 + 6 + 6 * \frac{1}{4} \times 1}{() + 24 \times 0.01 + 0.015 (- - -)} =$$

②

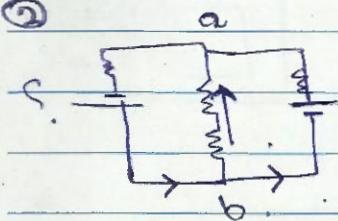


$$B_i = \frac{4 \times 10^{-3}}{15 \times 5 \times 10^{-4}} = 0.5033 \text{ T}$$

$$B_g = \frac{0.5033}{1.05}$$

$$B_{rg} = \frac{0.04 \times 10^{-3}}{4\pi \times 10^{-7} \times 5 \times 15 \times 1.05 \times 10^{-4}}$$
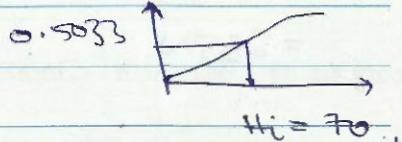
$$H_{rg} l_g = \Phi_{rg} R_{rg} = 0.004 \times B_{rg} \\ = \frac{0.004 \times 0.5033}{1.15}$$



$$185 - 100 = 85 = H_a$$

$$F_{ab} = 70 + 115 \\ = 185$$

$$H_r \Rightarrow B * A = 4.5 \text{ mWb} \\ \text{from graph}$$

$$\Phi = 4 + \frac{2.45}{2.45} = 8.5 \text{ mWb} \rightarrow B_L =$$


$$F = Ni$$

$$H_L L_L$$

$$= F_{ab} + H_{el} L$$

$$= 200i$$

$$i = 3.9 \text{ A}$$

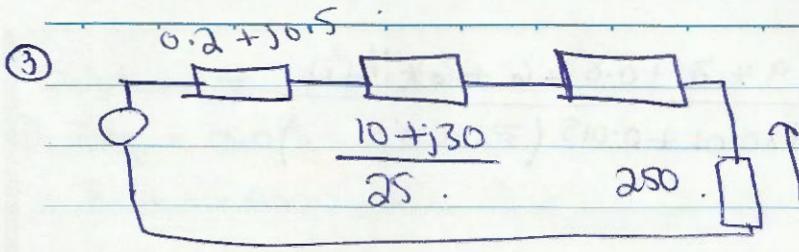

$$\frac{5000}{250} = 20.$$




$$\frac{250}{20} = 12.5 \quad 12.5 (0.01 + j0.02)$$

$$V_s = \frac{250}{10 + j5} (10 + j5 + \dots) \\ = 285 \text{ V}$$


$$I = \frac{250}{10 + j5} = 22.36$$

$$n = \frac{22.36^2 * 10}{(?) + 100 + 200 + 25} = 93.2$$

* Three phase Transformers:-

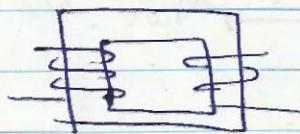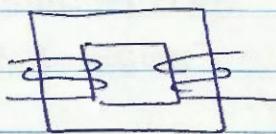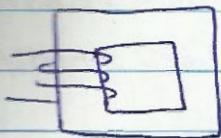

OR

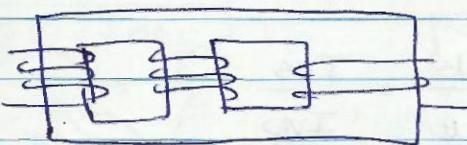

(Both are three phase, two different representations)

(The sum of the flux of the 3 transformers = 0 at a junction)

* I have 4 ways of connecting the Primary & secondary:-


Y Y (y-y) .

$\text{Y } \Delta$ (y-delta) :


$\Delta \text{ Y}$

$\Delta \Delta$.

* 1st connection: (Y-Y) (Rarely used) .

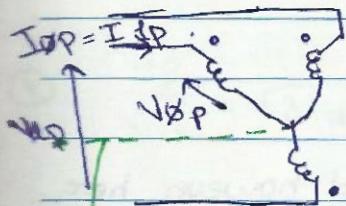

Primary

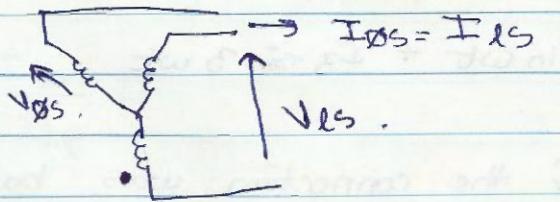


Secondary

$$\frac{V_{\phi P}}{V_{\phi S}} = a$$

$$V_{\phi P} = \sqrt{3} V_{\phi S} \angle 30^\circ$$

this is a neutral connection .

⇒ why 60° ?

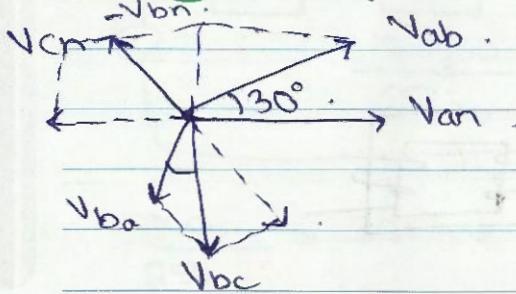

$$\Rightarrow a = \frac{V_{lp}}{V_{ls}} = \frac{\sqrt{3} V_{op} \times 30^\circ}{\sqrt{3} V_{os} \times 30^\circ} = \frac{I_{ls}}{I_{lp}} = \frac{I_{os}}{I_{op}}$$

* Note :
 $I_{ls} \rightarrow I_{line}$ secondary
 $I_{lp} \rightarrow I_{line}$ primary
 $I_{os} \rightarrow I_{phase}$ secondary
 $I_{ls} \rightarrow I_{line}$ secondary.

⇒ from the phasor diagram:-

$$V_{an}(t) = V_m \sin \omega t$$

$$V_{bn}(t) = V_m \sin(\omega t - 120^\circ)$$

$$V_{cn}(t) = V_m \sin(\omega t - 240^\circ)$$

$$i(t) = I_1 \sin \omega t + I_3 \sin 3\omega t$$

* $I_n = 0$ if the connection was balanced, however here I_n is the summation of the 3 currents. (If we get a really high voltage as we have distortion)


for the 3rd harmonic :-

$$V_{an3} = \sqrt{3}m \sin 3\omega t$$


$$V_{bn3} = \sqrt{3}m \sin 3\omega t + 120 \times 3 \quad (\text{In phase})$$

$$V_{cn3} = \sqrt{3}m \sin 3\omega t + 240 \times 3$$

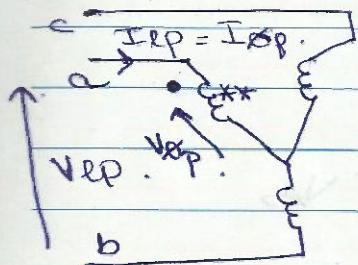* 2nd connection (Y - Δ) (Important; mostly used)


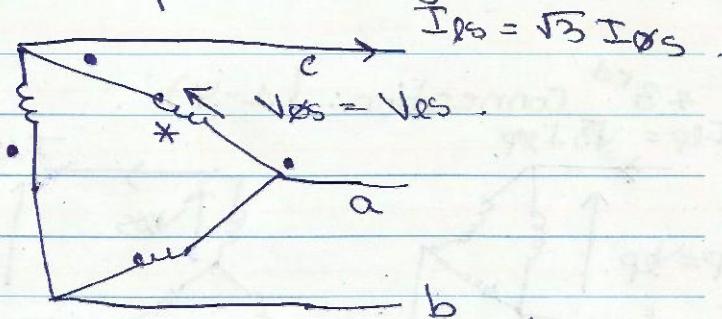
$$\therefore V_{aP} = \sqrt{3} V_{\phi P}$$



① (Note: the * & ** are a single phase transformer, (secondary & primary) (no phase) the V_{aP} & $V_{\phi P}$ however have a 30° phase in the primary)

$$\textcircled{1} \quad \frac{V_{aP}}{V_{ls}} = \sqrt{3} \quad a = \frac{I_{\phi S}}{I_{aP}}$$


② (Y-Y with Y-Y can be connected; but Y-Δ with Y-Δ only if they're in phase) & the vector group has a phase shift $+30^\circ$ or -30°)

④ the 1st harmonic (+/-) 3rd harmonic.

$3\sqrt{3} \sin 3\omega t$ → Current in the secondary A coil



→ the voltage

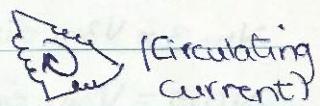


(circulating current)


here is zero (I get rid of the 3rd harmonic).

* 3rd Connection: (Δ-4) .

$$I_{LP} = \sqrt{3} I_{OP}$$

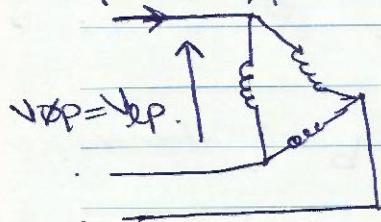

$$I_{LS} = I_{OS}$$

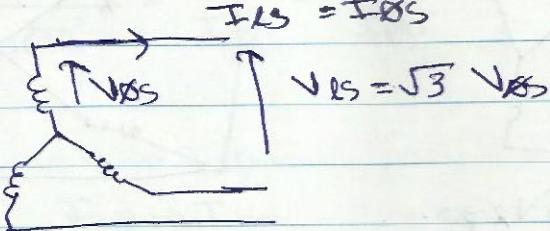

$$\frac{V_{LP}}{V_{OS}} = \alpha = \frac{V_{LP}}{\sqrt{3} V_{OS}} = \frac{V_{LP}}{V_{OS}} \sqrt{3}$$

$$\frac{V_{LP}}{V_{OS}} = \frac{\alpha}{\sqrt{3}} = \frac{I_{LS}}{I_{OP}}$$

Jean Hamdan
Hamedan

$$S_{\phi \text{ base}} = \frac{S_{\text{base}}}{3}$$

$$I_{\phi \text{ base}} = \frac{S_{\phi \text{ base}}}{U_{\phi \text{ base}}} = \frac{S_{\text{base}}}{3 U_{\phi \text{ base}}}$$

$$Z_{\phi \text{ base}} = \frac{U_{\phi \text{ base}}}{I_{\phi \text{ base}}} = 3 \frac{U_{\phi \text{ base}}^2}{S_{\text{base}}}$$

50 kVA

13800 / 208 Δ Y

$$Z_{PU} = 0.01 + j0.07$$

$$Z_{\text{base}} = \frac{3 * 13800^2}{50000} = 11426 \text{ } \Omega$$


$$Z_{\text{eq}} = 11426 (0.01 + j0.07) = 114.2 + j800$$

$$V.R \approx I.P.U (R_{\text{eq}} P.U \cos \theta + X_{\text{eq}} P.U \sin \theta)$$

$$\approx 1 [0.01 * 0.8 + 0.07 * 0.6] P$$

$$\approx 0.05 \text{ } S_f \text{ -- P.U}$$

$$I_P = \frac{50000}{3 * 13800} = 1208$$

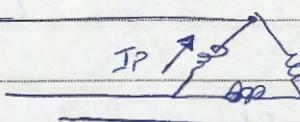

$$V.dP = 13800 + 1.208 (0.8 - j0.6) (114.2 + j800)$$

$$\approx 14506$$

$$VR = \frac{14506 - 13800}{13800} = 5\%$$

*Problems .

2.10 :

Given :

600 KVA .

34.5 / 13.8 KV .

YY .

Answer :

Connection

YY

$$\frac{V_p}{\sqrt{3}} = \frac{34.5}{\sqrt{3}} = 19.9$$

$$\frac{V_b}{\sqrt{3}} = \frac{13.8}{\sqrt{3}} = 7.97$$

	V _p	V _b	KVA	a (of single phase)
YY	$\frac{34.5}{\sqrt{3}}$	$\frac{13.8}{\sqrt{3}}$	200	$\frac{19.9}{7.97} = 2.5$

YΔ

$$\frac{34.5}{\sqrt{3}} = 19.9 \cdot 13.8 \quad 200 \quad \frac{19.9}{13.8} = 1.44$$

ΔY

$$34.5 \cdot \frac{13.8}{\sqrt{3}} = 7.97 \quad 200 \quad \frac{34.5}{7.97} = 4.33$$

ΔΔ

$$34.5 \cdot 13.8 \quad 200 \quad \frac{34.5}{13.8} = 2.5$$

2.13 Given:

15000 / 400 V .

3Δ YΔ

34100 KVA .

7967 / 480

Answer:

$$V_{sc} = \frac{560}{P_{sc}} = 3350$$

$$I_{sc} = 12.6 A .$$

$$P_{\phi SC} = \frac{3300}{3} = 1100 \text{ W}$$

$$V_{\phi S} = \frac{560}{\sqrt{3}} = 323.2$$

~~$$P_{\phi SC} = \frac{3300}{3} = 1100 \text{ W}$$~~

~~1100 W~~

~~5~~

$$I_{\phi SC} = 12.6 \text{ A}$$


$$R_{eq} = \frac{1100}{12.6^2} = 6.94 \Omega$$

$$Z_{eq} = \frac{323.2}{12.6} = 25.66 \Omega$$

$$X_{eq} = \sqrt{25.66^2 - 6.94^2} = 24.7 \Omega$$

~~5~~
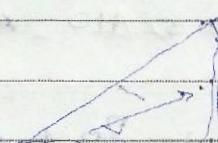
$$\frac{100000}{7667} = 12.55 \angle -31.79^\circ$$



$$VR = \frac{12.55}{7667} (6.94 * 0.85 + 24.7 * 0.6)$$

~~5~~

$$= 3.01 \%$$

~~5~~

2.11 100 000 kVA

230 / 115 kV

$\Delta - \Delta$


$$Z_{PV} = 0.02 + j0.055$$



$$R_C = 110 \text{ PV}$$

$$X_m = 20 \text{ PV}$$
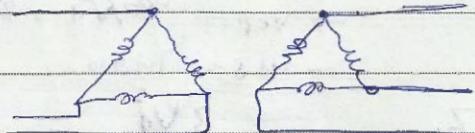
$$80 \text{ MVA} \quad 0.85 \text{ P.F. lagging}$$



$$I_{LS} = \frac{80000 \text{ kVA}}{\sqrt{3} * 230 \text{ kV}} = 402 \text{ A}$$

$$I_{PV} = \frac{402}{502} = 0.8 \angle -31.8^\circ$$

$$I_{LB} = \frac{100000}{\sqrt{3} * 115} = 502$$

$$P_{D1} = P_{R1}$$

8.61

$$\delta_{EP} = \delta_{DF}$$

+0.4

$$\delta_{DF} = \delta_{DE}$$

8.61

→ 2.11 Given: 100,000 kVA

230/115 kV (ΔΔ)

$$Z_{p.u.} = 0.02 + j0.055$$

$$R_c = 110 \text{ p.u.}$$

$$X_m = 20 \text{ p.u.}$$

80 MVA 0.85 p.f. lag.

(Note:- the per-unit values are irrelevant to primary & secondary).

Answer:

$$\frac{80,000 \text{ kVA}}{\sqrt{3} \times 115 \text{ kV}} = 402 \text{ A} = \text{Line secondary.}$$



$$I_{\text{base}} = \frac{10,000}{\sqrt{3} \times 115} = 502 \text{ } -31.8^\circ$$

$$I_{\text{P.U.}} = \frac{402}{502} = 0.8 \angle \cos^{-1}(0.85)$$

$$VR = 0.8 [0.02 \times 0.85 + 0.055 \times 0.52]$$

$$Z_{\text{base}} = \frac{3 \sqrt{3} s_{\text{base}}^2}{S_{\text{base}}}$$

$$Z_{\text{base}} = \frac{3 \times 115^2}{100} \frac{\text{kW}^2}{\text{MVA}}$$

$$= 397$$


$$Z_{\text{eq}} = 397 (0.01 + j0.055)$$

$$= 7.94 + j21.8$$

$$R_c = 110 \times 397 = 43.7 \text{ k}\Omega$$

$$X_m = 20 \times 397 = 7.94 \text{ k}\Omega$$

224

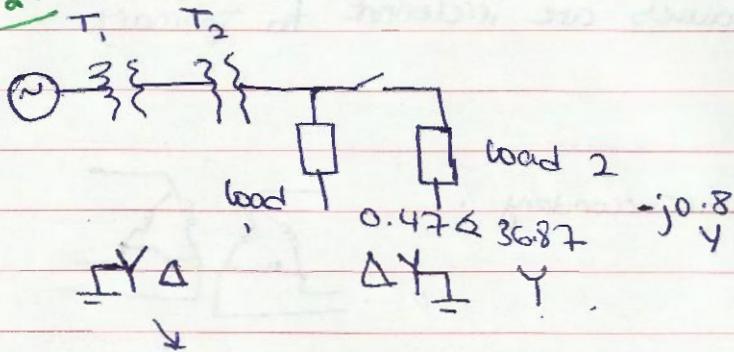

480V.

$$480/14000$$

$$14400/480$$

base value of system $\leftarrow \text{1900 kVA}$

$$R = 8.01 \text{ p.u.}$$

$$S = 500 \text{ kVA}.$$

$$V_{op} = \frac{480}{\sqrt{3}}$$

$$X = 0.04 \text{ p.u.}$$

$$R = 0.02 \text{ p.u.}$$

$$V_{bs} = 14,000.$$

$$X = 0.085 \text{ p.u.} \leftarrow V_{op} = 14400.$$


$$X = 0.085 \text{ p.u.} \leftarrow V_{bs} = 207.$$

Answer:-

$$Z_{base} = \frac{3V_{op}^2}{S_{base}} = \frac{3 \times 14400^2}{1000} = 0.238$$

$$Z_{base\ 2} = \frac{14400^2}{1000} = 207.4.$$

$$Z_{base\ 3} = Z_{base\ 1}$$

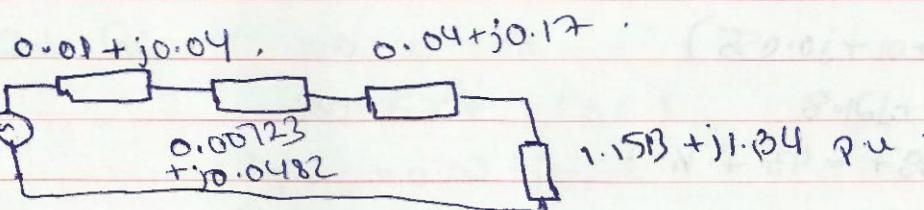

$$S_{base} = 1000 \text{ kVA}.$$

$$\frac{1.5 + j10}{207} = 0.00723 + j0.0482.$$

$$(Z_{p.u.})_2 = (0.02 + j0.085) * \frac{1000}{500}.$$

$$\frac{0.45 \angle 36.87}{0.258} = 1.513 + j1.134$$

$$I = \frac{1}{\{ \dots \}} = 0.4765 \angle -41.6^\circ$$

$$V_L = 0.4765 \angle -41.6^\circ \times (1.513 + j1.134)$$

P.U.



$$= 0.901 \text{ p.u.}$$

$$V_1 = 480 \times 0.901 = 432$$

(To get the losses multiply $I^2 \times$ each value)

$$PF = \cos(41.6)$$

* Open Δ - Open Δ :-

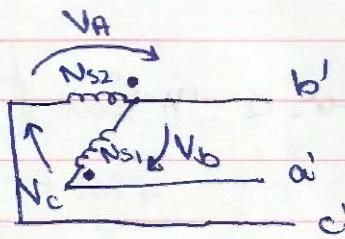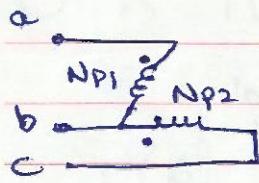

$$V = -V_A - V_B.$$

$$= -V_60^\circ - V_6-120^\circ$$

$$V_B = V_120^\circ.$$

$$= -V - \sqrt{-0.5 - j0.866}$$

$$= -0.5V + j0.866V$$

$$= V_120^\circ.$$

$$\rightarrow P = 3V\phi I\phi \cos \theta.$$

$$* P_1 = 3V\phi I\phi \cos(150^\circ - 120^\circ)$$

$$= 3V\phi I\phi \cos 30^\circ$$

$$= \frac{\sqrt{3}}{2} V\phi I\phi$$

$$* P_2 = 3V\phi I\phi \cos(30^\circ - 60^\circ).$$

$$= 3V\phi I\phi \cos(-30^\circ)$$

$$= \frac{\sqrt{3}}{2} V\phi I\phi$$

$$P = \frac{\sqrt{3}}{2} V\phi I\phi.$$

$$\frac{P_{\text{Apper}}}{P_{3\phi}} = \frac{\frac{\sqrt{3}}{2} V\phi I\phi}{3V\phi I\phi} = \frac{1}{\sqrt{3}} = 0.577.$$

$$\sum Q = 0.$$

$$Q_1 = 3V\phi I\phi \sin(150^\circ - 120^\circ)$$



$$= 3V\phi I\phi \sin 30^\circ = \frac{1}{2} V\phi I\phi.$$

$$Q_2 = 3V\phi I\phi \sin(30^\circ - 60^\circ)$$




$$= 3V\phi I\phi \sin(-30^\circ) = -V_2 V\phi I\phi.$$

$$\frac{P}{3\sqrt{2}} * \frac{\sqrt{3}}{2} \Rightarrow \frac{1}{\sqrt{3}}$$

→ Open Y - open Δ

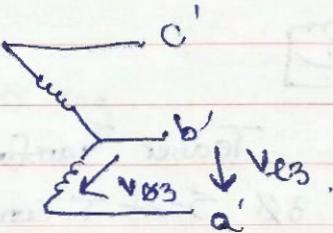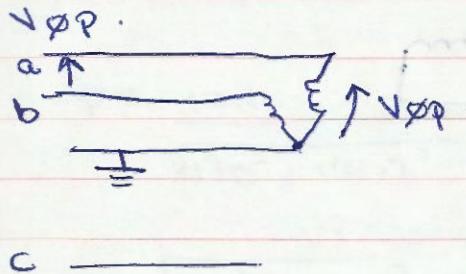

* Scott Connection:-

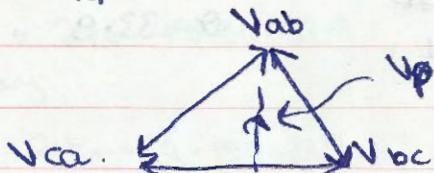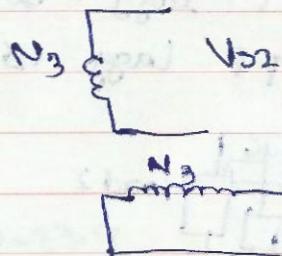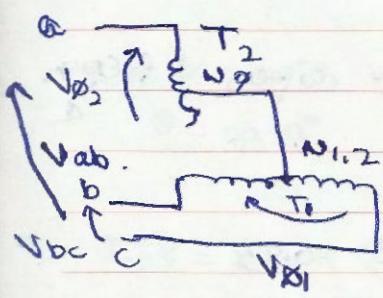

$$V_{B2} = 0.866 V \angle 90^\circ$$

$$V_{ab} = V \angle 120^\circ$$



$$V_{bc} = V \angle 0^\circ$$

$$V_{ca} = V \angle -120^\circ$$

$$V_{B2} = \frac{V}{\alpha} \angle 90^\circ$$

$$V \angle 60^\circ$$

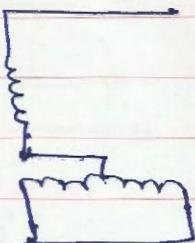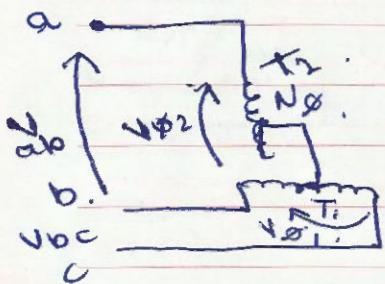→ Making the Secondary of the Scott Connection:
3 phase:-



Teaser Transformer.



" 3Ø Scott T Connection "

→ Example:

$$2 \times 13.8 \text{ kVA}$$

$$480V \quad 120 \text{ kW} \quad 0.8 \text{ p.f. lagg. } 30^\circ$$
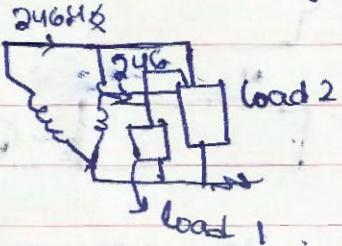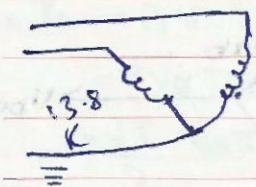
$$\text{,,} \quad 50 \text{ kW} \quad 0.9 \text{ p.f. lagg. } 10^\circ. \sim \text{open Y & open A}$$



$$\cos \theta = 0.83$$

$$\theta = 33.9^\circ$$

→ Solution:-

$$P_1 = 120 \text{ kW}$$

$$\text{KVA}_1 = \frac{120}{0.8} = 150 \text{ KVA}$$

$$Q_1 = 150 \times 0.6 = 90 \text{ KVAR}$$

$$P_2 = 50 \text{ kW}$$

$$P_{\text{Total}} = 50 + 120 = 170$$

$$\text{KVA}_2 = \frac{50}{0.9} = 55.5$$

$$Q_2 = 55.5 \sin 25.84^\circ \\ = 24.2 \text{ KVAR}$$

$$Q_{\text{tot}} = Q_1 + Q_2 = 114.2 \text{ KVAR}$$

$$\text{PF} = \frac{170}{\sqrt{170^2 + 114.2^2}} = 0.83 \text{ lag.}$$

$$I = \frac{\sqrt{170^2 + 114.2^2} \text{ A}}{\sqrt{3} * 480} = 246.4 \text{ A}$$

$$\cos \theta = 0.83$$

$$\theta = 33.9^\circ$$

$$I_{AS} = 246.4 \angle -30 - 33.9^\circ$$

$$I_{CS} = 246.4 \angle 90 - 33.9^\circ$$

secondary

$$I_{BS} = 246.4 \angle -150 - 33.9^\circ$$



$$P_n = V_A S I_A \cos \theta = 480 *$$

$$Q_A = 480 \times 246.4 \sin 63.9^\circ \\ = 106.2 \text{ KVAR}$$

$$P_2 = 480 \times 246.4 \cos(56.1 - 120^\circ) \\ = 118 \text{ kW.}$$

$$Q_2 = 480 \times 246.4 \sin(56.1 - 120^\circ) = 8.04$$

→ Example:

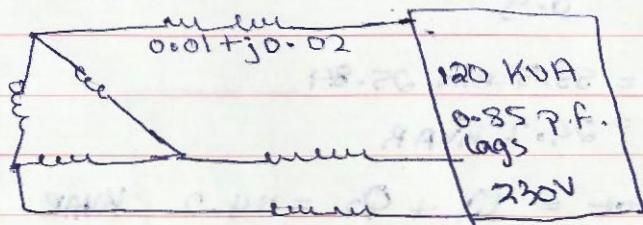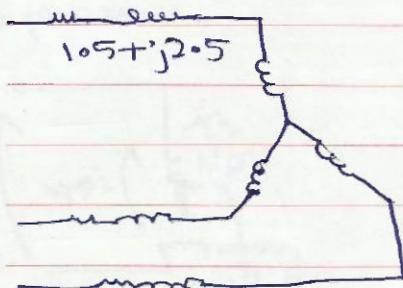

$$Z_{eq1} = 0.012 + j0.016$$

3 transformers each 2300/230 V.

Find the supply voltage $V_{sp} = 2300\sqrt{3}$.

→ Solution:


↳ Transformation Ratio (a): $10\sqrt{3} : 1$

$$Z_{eqH} = (0.012 + j0.016) * 10^2 = 1.2 + j1.6 \text{ ohms}$$

$$a = \frac{V_{sp}}{V_{es}} = \frac{2300\sqrt{3}}{230} = 10\sqrt{3}$$

Z_{eqH} from Z_{eq1} :
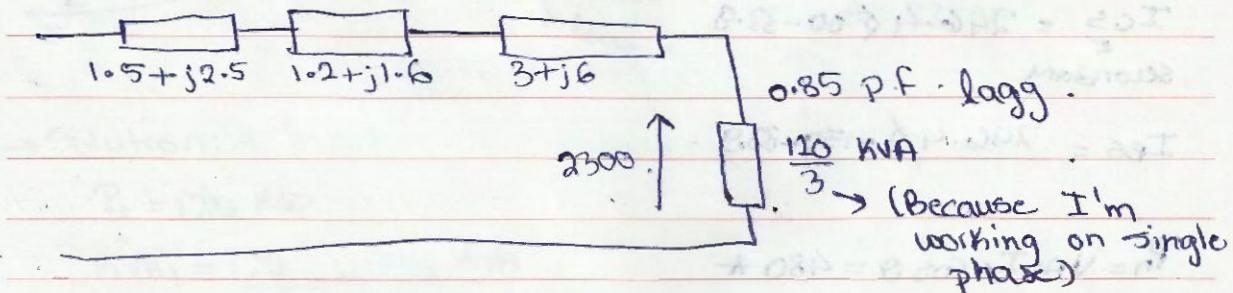
$$Z_{T2H} = (0.01 + j0.02)(10\sqrt{3})^2 = 3 + j6$$



$$I = \frac{40,000}{2300} = 17.34 \angle -31.78$$

$$= 17.39(0.85 - j0.5267) \text{ A}$$

$$V_1 = 2300 + 17.39(0.85 - j0.5267)(1.05 + j2.5 + 1.2 + j1.6 + 3 + j6)$$

$$= 2478.68 \text{ V}$$

$$\sqrt{10} = 2478 \cdot 68\sqrt{3} = 4296$$

$$VR\% = \frac{2478.0 - 2300}{2300} = 7.7\%$$

$$\eta = \frac{40,000 * 0.85}{40,000 * 0.85 + 17.38^2 * (1.3 + 1.2 + 1.3)} = 95.2\%$$


* Inrush current :-

$$v(t) = V_m \sin(\omega t + \phi)$$



$$\Phi_{max} = \frac{V_{max}}{\omega N_p}$$

$$v(t) = V_m \sin(\omega t)$$
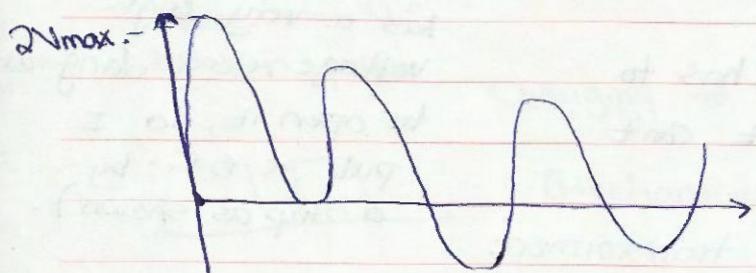
$$\Phi_{max} = \frac{2V_{max}}{\omega N_p}$$



Voltage & Flux
• (90° -> 90°)

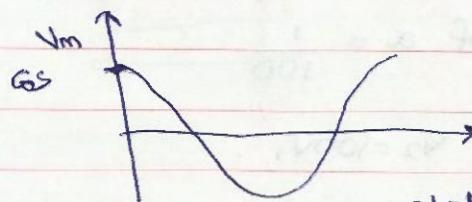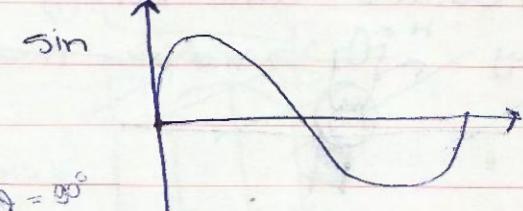

$$i = N \frac{d\phi}{dt}$$

$$\phi = \frac{1}{N} \int \omega dt$$

$$\phi = \frac{1}{N} \int_0^t I_m \sin(\omega t) dt = \frac{I_m}{\omega} \left[\cos \omega t \right]_0^t = \frac{I_m}{\omega} (\cos \omega t - 1)$$

$$V_m \cos \theta - \cos \theta$$


$$-V_m \frac{-1 - 1}{\omega N} = +2V_m \frac{1}{\omega N}$$

$$\frac{\sin \omega t}{\omega N} + K$$



Potential Transformers:-

Instruments Transformers:-

(1) Potential Transformer:

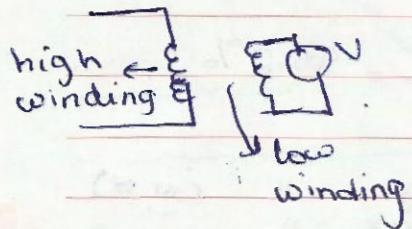

(2) Current Transformer:-

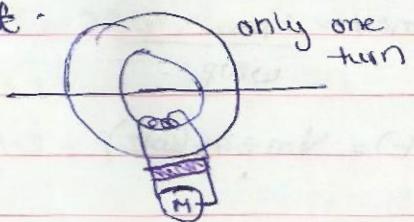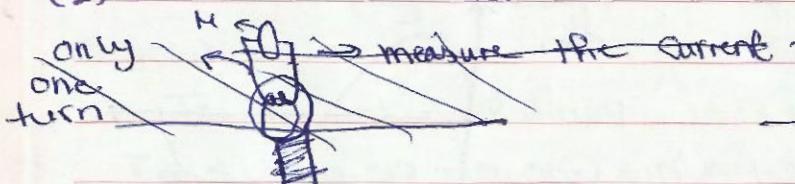

$$\text{if } a = \frac{1}{100}$$

$$V_2 = 100V,$$

* Rule: the secondary has to be short circuited, if it can't have a fuse!

(Note that this has a very high voltage, very dangerous to open it, so I put a S.C. by a strip as shown)

Standard to the current transformer:

600:5

800:5


1000:5

(The problem with current is you have to make it series, & I can't make series without cutting the wire, this is why we use the current transformer).


Chapter 8

DC machines:


Orientation & speed

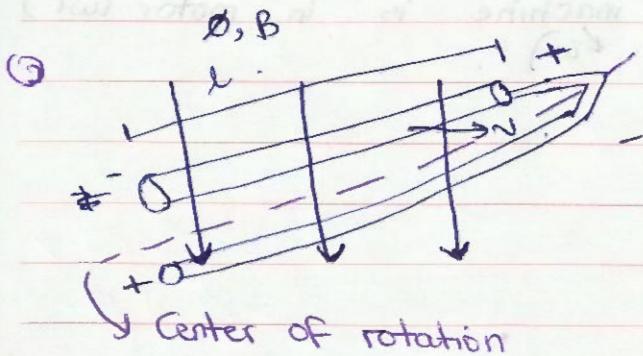

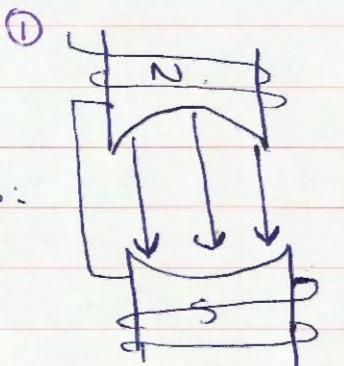$e = Blv$
Since they are in series $e = 2Blv \propto \omega r$




So the emf will look like this:

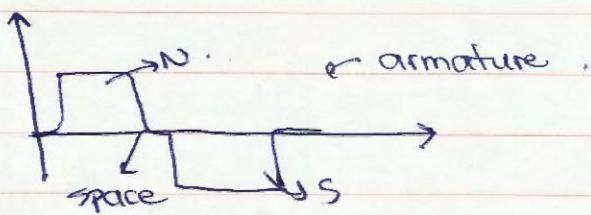

space between poles

Changing to DC

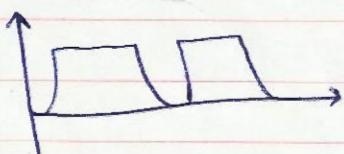

(Mechanical Cutting)



* I need 3 things to change to DC:- (numbered above).

(1) Field (Poles).

(2) Winding (Armature)

(3) Commutator (for the mechanical cutting)

Motors


$$F = Bl_i$$

$$T = 2(Bli) \cdot V(2 \text{ wires})$$


(the difference between motor & machine is in motor (wr) i)

Practically:

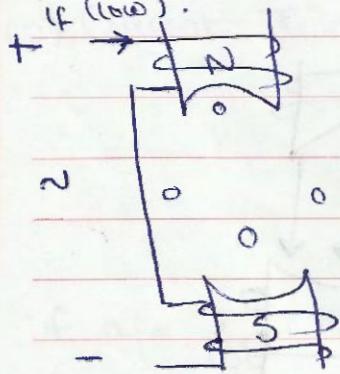I induce the flux by an external winding given a current if (loop).





the commutator:-

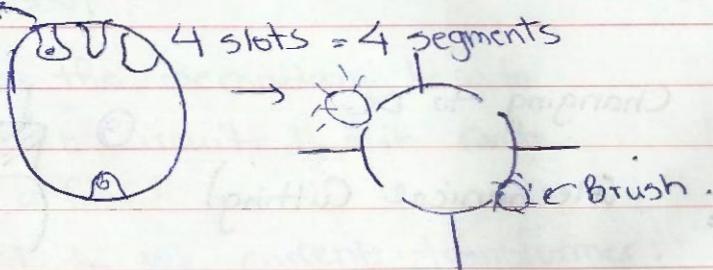

(For a good DC machine, I want the maximum # of slots.)


→ Armature Winding:-

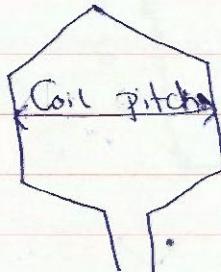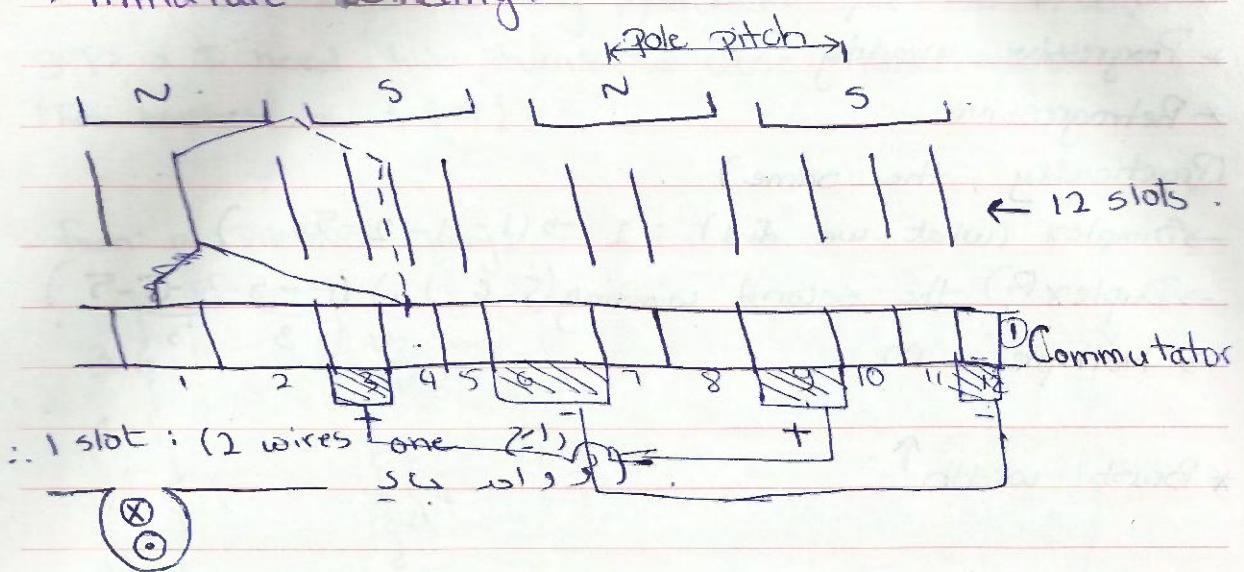

- ∴ \Rightarrow Pole pitch: the distance from half the pole to half the pole (3 in this case)
- \Rightarrow Coil pitch: the beginning to the end of the coil
- ∴ They are supposed to be equal

* Lap winding

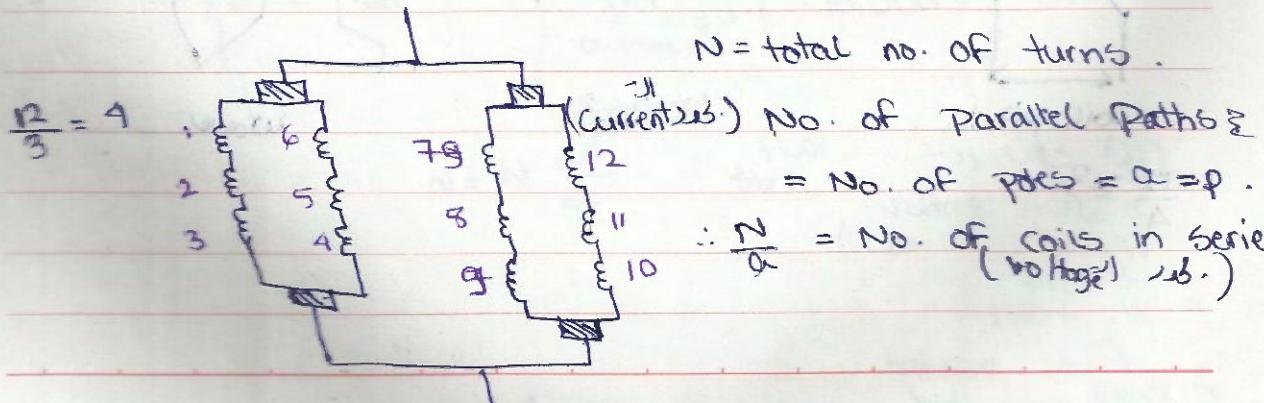The drawing above, I continue the same way up to 12 (each 3 slots connected) after 12 I return to 1. Every end is connected to the beginning (No end).



→ Properties of lap winding:

* Progressive winding :

* Retrogressive

(Practically, the same) .



→ Simplex (what we did) : $1 \rightarrow (1-4-2-5-\dots)$.

→ Duplex (2) the second winding $(5-6)$ $\rightarrow (1-4-3-\underbrace{6-5}_{3})$.


→ Multiplex, m .

* Brush width ↑

→ Wave Winding:

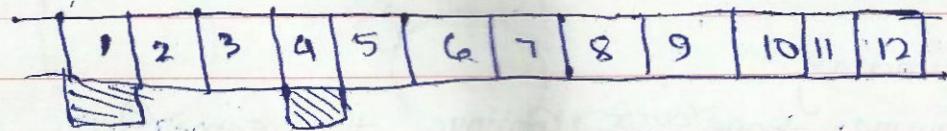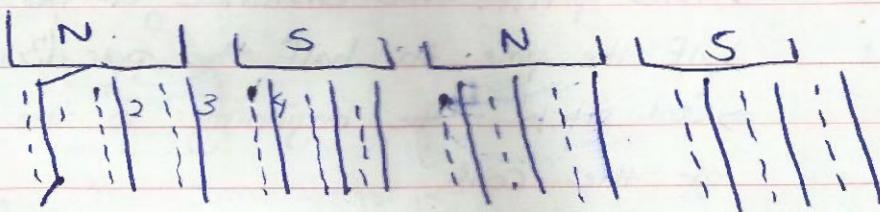


Pole pitch = 3.25 .

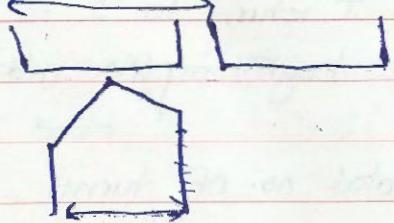

coil pitch .


$$\frac{12}{4} = 3 .$$

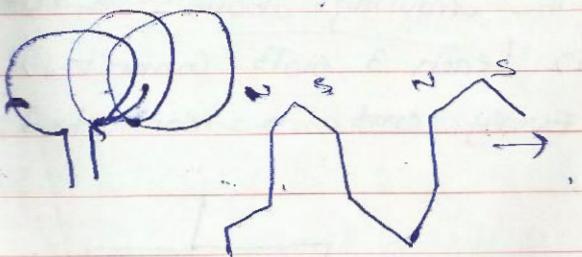

wave .




*Note: In wave winding, between 1 & 4 I have two gaps \rightarrow I need two turns to close these gaps
 (Two brushes, on 1 & 4)

from a practical way:

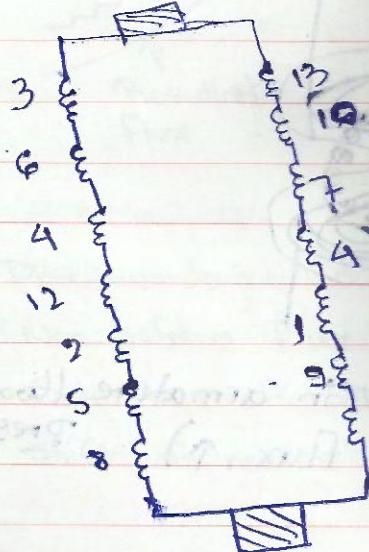

$$\text{No. of parallel paths} = 2 \div a \\ = 2m$$

(In loop = pm)

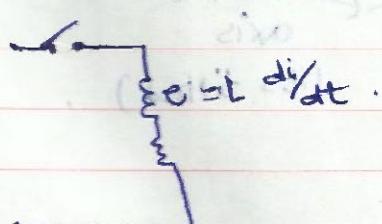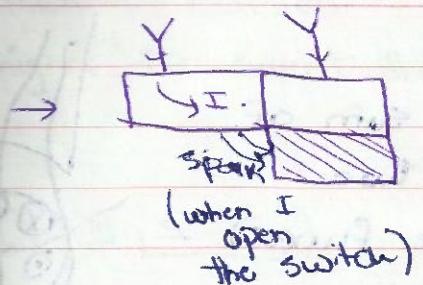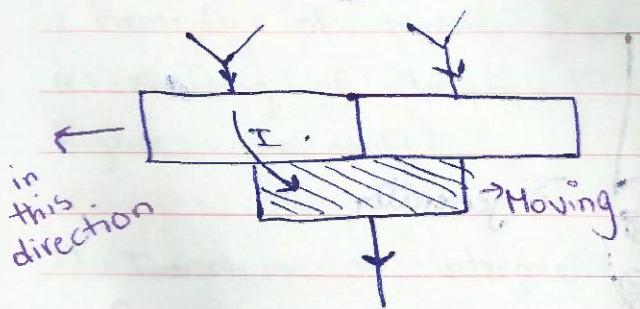

$$\frac{100}{0.001} \times 0.1 = 10,000 \text{ V}$$

$$N = N \frac{di}{dt}$$

flux \rightarrow (ES 15)
 sin


voltage \rightarrow 16
 (cos which means there is a phase shift between flux & voltage).

* The brushes are to be located on the neutral axis between poles.

→ Armature Reaction.





No load

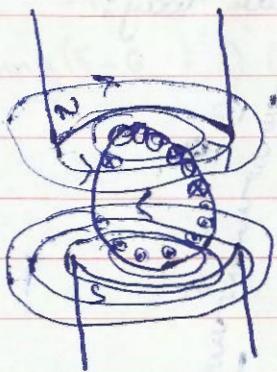

(Current in armature (load has a flux, ↑) Present)

(The sum of the two above fluxes)

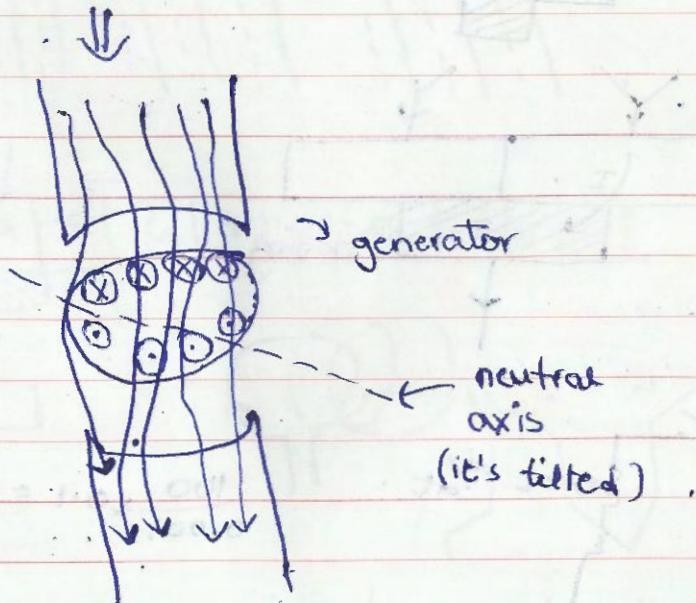

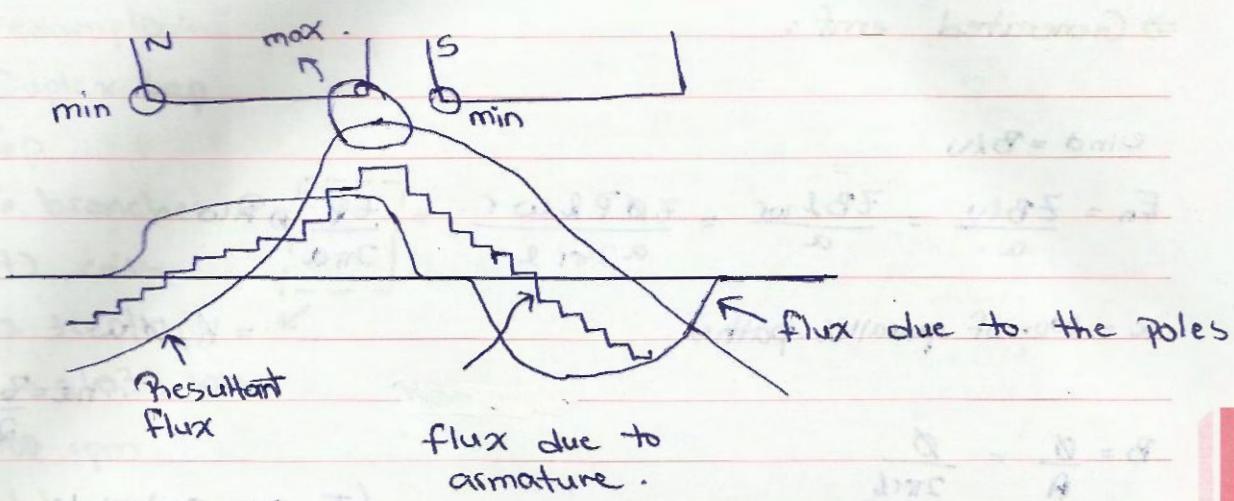


* Disadvantages of armature reaction:

- (1) Non-uniform flux distribution
- (2) Saturation of pole tips
- (3) Shift of neutral axis

* Remedy of problems of armature reaction:

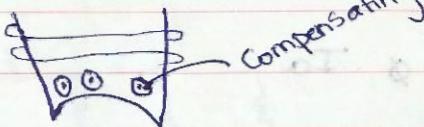- (1) Shifting of brushes (the higher the current the higher the shift)
- (2) Insertion of interpoles (
- (3) Compensating winding :



⇒ Generated emf:

$$e_{ind} = Blv$$

$$E_a = \frac{ZBlv}{a} = \frac{ZBlwr}{a} = \frac{Z\Phi P l w r}{a 2\pi r} = \boxed{\frac{ZP}{2\pi a} \phi \cdot w}$$

a = No. of parallel paths.

$$= K_a \phi \cdot w$$

$$\therefore K_a = \frac{ZP}{2\pi a}$$

$$B = \frac{\phi}{A} = \frac{\phi}{2\pi r l}$$

P → (no. of poles).

(I can control the machine by the flux & speed (ϕ & w) as K_a is a constant)
(w in rad/sec).

→ If I have a motor, I have:

$$f = Blz \quad \text{total current}$$

$$i = \frac{I_a}{a} \quad \leftarrow \text{(One conductor)}$$

$$T = \frac{ZBl \cdot I_a}{a} \quad (\tau \rightarrow \text{torque})$$

(In motor,
I give the
torque (mechanical
torque by rotation))

$$= \frac{ZP}{2\pi a} \phi \cdot I_a$$

$$= K_a \phi \cdot I_a$$

$$T = \frac{P}{w} \quad , \quad P = TW = \frac{K_a \phi \cdot w}{2\pi} I_a$$

$$\text{Power} = E_a I_a \quad (\text{Induced emf} + \text{Armature current})$$

(This is an ideal generator, no resistors).

⇒ example :

Duplex Lap

6P

6 branches

72 coils

12 turn/coil

$$\phi = 0.039 \text{ Wb}$$

400 rpm

Solution:

$$a' = pm = 6 \times 2 = 12$$

(because it's duplex)

$$Z = 72 * 12 * 2 = 1728 \text{ Conductor turns}$$

(2 legs, turn 15)

$$Ra = \frac{1728 * 6}{2\pi * 12} = 137.5$$

$$w = 400 * \frac{2\pi}{60} = 41.8$$


$$E_a = 137.5 * 0.039 * 41.8 =$$

Given:

⇒ each turn is 0.011Ω

Solution:

$$Ra = \frac{0.011}{2}$$

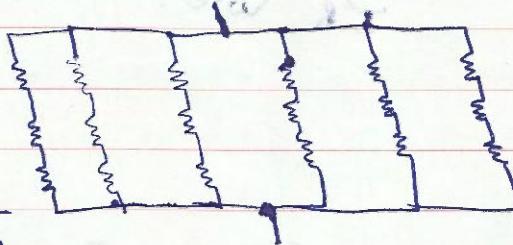

$$Ra = \frac{1728}{6} * \frac{0.011}{2} * \frac{1}{6}$$

$$= 0.26 \Omega$$

$$\Rightarrow \eta = \frac{P_{out}}{P_{in}} + 100\%.$$


$$= P_{in} - P_{loss}$$

$$P_{loss} = \left\{ \begin{array}{l} I^2 R \xrightarrow{\text{Brush}} I_a^2 R_a \\ I^2 R \xrightarrow{\text{Core}} I_p^2 R_F \\ \text{Mechanical} \\ \text{Stray} \end{array} \right.$$

$$\Rightarrow \text{Brush losses: } V_{brush} \cdot I$$


$$P_{in} = TW$$

\Rightarrow For machine generator

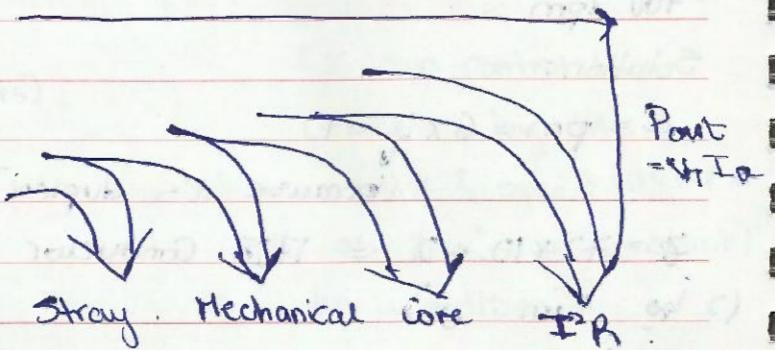

\Rightarrow For motor

$$P_{in} = VT I_L$$

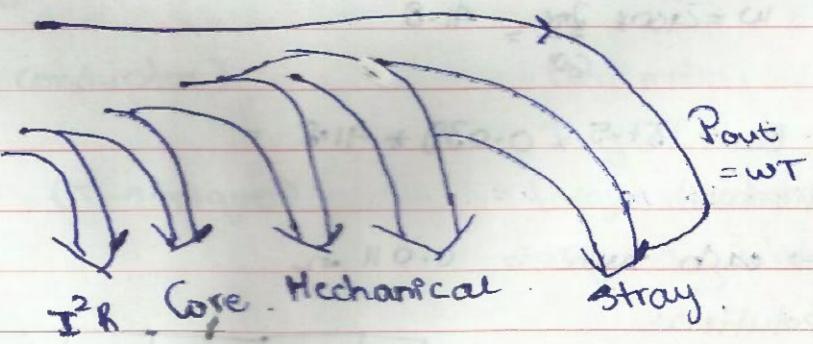

→ Problems:

7.1 Given:

$$B = 0.8 \text{ T}$$


$$V_A = 24 \text{ V}$$

$$l = 0.5 \text{ m}$$

$$h = 0.4 \text{ m}$$

$$\omega = 250 \text{ rad/s}$$

$$T = 0.125 \text{ m}$$

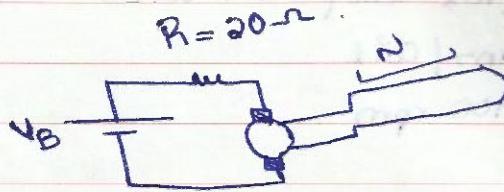

Solution:-

$$E = 2BL\omega r = 2BL\omega$$

$$= 2 * 0.8 * 0.5 * 250 * 0.125$$

$$= 25 \text{ V}$$

$$I = \frac{25 - 24}{0.4} = 2.5 \text{ A} \quad \therefore \text{It is a generator}$$

→ Question:

$$8 \text{ p}$$

$$100 \text{ A} = I_a$$

Simplex lap $\alpha = 8$

$$I = \frac{100}{8} = 12.5$$

$$\text{duplex lap} = 2 * 8 = 16$$

$$I = \frac{100}{16} = 6.25 \text{ A}$$

$$\text{Simplex wave } \alpha = 2 \quad I = \frac{100}{2} = 50 \text{ A}$$

$$\text{Quadruplex wave } 4 * \alpha = 4 * 2 = 8 \rightarrow I = \frac{100}{8} = 12.5 \text{ A}$$

8-7) $p = 8$ 25 kW 120V
 duplex loop 64 coils
 16 turns / coil
 $= 2400 \text{ rpm}$

Solution :

$$E_a = 120 = \frac{Z_p}{2\pi a} \phi w$$

$$\Rightarrow \frac{64 * 16 * 2 * 8 * \phi * 2400 * 25}{60} = 2400$$

$$a = 16$$

$$\phi = 0.00293 \text{ wb}$$

$$I_{a \text{ rated}} = \frac{25000}{120} = 208 \text{ A}$$

$$T = \frac{P}{w} = \frac{25000}{2400 * \frac{25}{60}} = 93.47 \text{ Nm.}$$

$$i = \frac{20P}{16} = 13 \text{ A}$$

→ If the resistance of armature is 0.011 ohm / turn

$$r_z = \frac{0.011}{2}$$

per

$$\text{No. of conductor paths} = \frac{64 * 16 * 2}{2 * 8} = 128.$$

$$R_{\text{per}} = \frac{128 * 0.011}{16} = 0.044 \text{ ohm}$$

⇒ DC motors:

Separately excited

Shunt

Series




Permanent magnet

Compound



⇒ Speed regulation:

$$\frac{n_{NL} - n_{FL}}{n_{FL}} * 100\%$$

↳ i) Separately Excited:

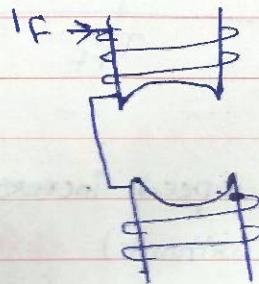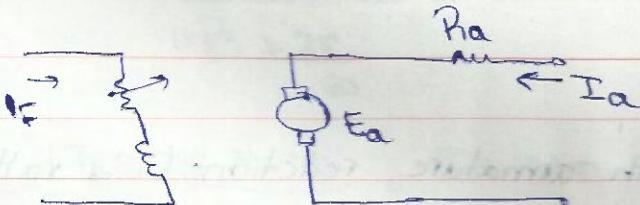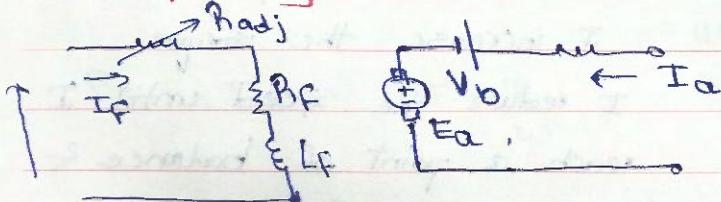


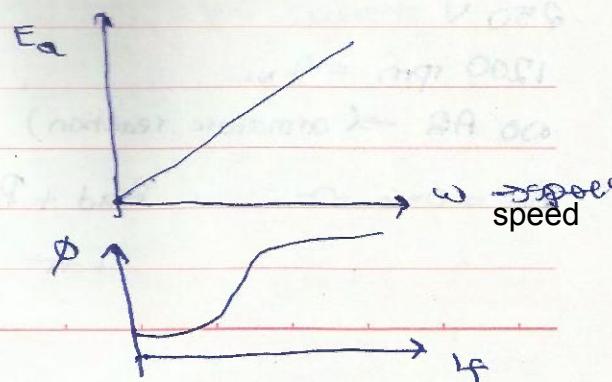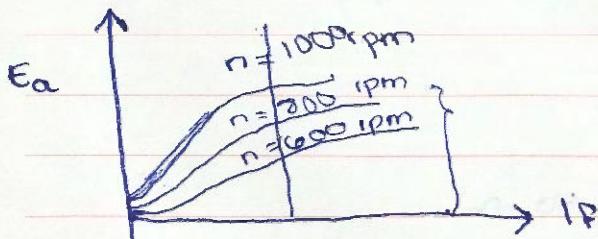$E_a = K_a \Phi \omega$. (the emf is proportional to the flux in B_{FL})



(n & w are both speeds; $n \times \frac{2\pi}{60} \rightarrow w$)

b2) Shunt :

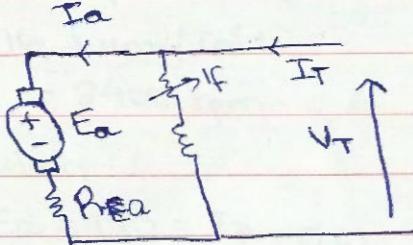

$$E_a = V_T - I_a R_a$$


$$T = K_a \Phi I_a$$

$$I_a = \frac{I}{K_a \Phi}$$

$$K_a \Phi w = V_T - \frac{I}{K_a \Phi} R_a$$

$$\uparrow \quad \frac{V_T}{K_a \Phi} - \frac{R_a}{(K_a \Phi)^2} T$$

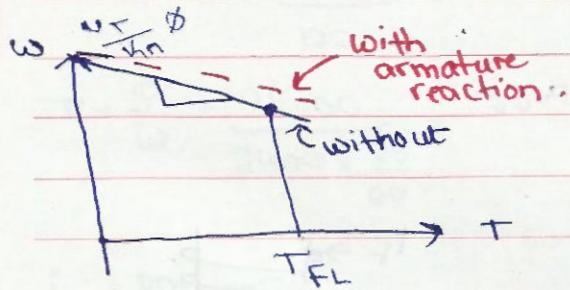(the higher the torque, the less the speed; if



I increase the torque
I reduce the speed until I
reach a point of balance &
vice versa).

⇒ The speed increases with armature reaction (I'd rather have without)

* example:

50 HP

250 V

$$1200 \text{ rpm} = n_{NL}$$

NO AR → (armature reaction)

$$R_a = 0.6 \Omega \quad R_{ad} + R_F = 50 \Omega$$

$$I_{eff} = 100A \quad 1200 \text{ turns}/pole$$

→ Solution:

$$E_a = 250 - 95 + 0.06 \\ = 244.3 \text{ V}$$

(95, because I_T is divided
on load $\Rightarrow I_a = 100 - \frac{250}{50} = 95$)

no load :

$$\frac{E_{a1}}{E_{a2}} = \frac{n_1}{n_2}, \quad \frac{250}{244.3} = \frac{1200}{n_2}$$

$$n_2 = 1173 \text{ rpm.}$$

$$200 - 5 = 195$$

$$E_{a3} = 250 - 0.06 * 195$$

$$= 238.3$$

$$n_3 = \frac{1200}{250} + 238.3$$

$$= 1144 \text{ rpm.}$$

$$P = E_a I_a, \quad T = \frac{P}{\omega}$$

$$T_2 = \frac{244.3 * 95}{1173 + \frac{2\pi}{60}} = 190 \text{ Nm}$$

$$T_3 = \frac{238.3 * 195}{1144 + \frac{2\pi}{60}} = 388 \text{ Nm}$$

$$I_F^* = I_F - \frac{F_{AR}}{N_F}$$

* Note:

(Armature reaction
reduces from the
field current).


* Taking the same previous example but with armature reaction:

Given $FAR = 840 \text{ AT}$ 200A

→ Solution:

$$I_F^* = 5 - \frac{840}{1200} = 4.3 \text{ A} \quad E_a^* = 238.3 + \frac{4.3}{5}$$

Given:

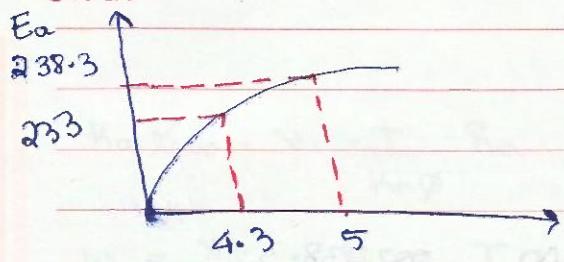

$$n = \frac{238.3}{233} * 1200 = 12.27 \text{ rpm}$$


From graph $E_a = 233$.

E_a & ω are related to flux - (is linear)

* Speed Control of DC shunt motor.

$$\omega = \frac{V_T}{K_a B} - \frac{R_a}{(K_a B)^2} T$$


1) Variation of supply voltage V_T .

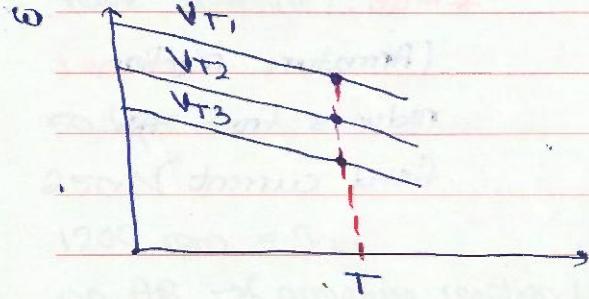

$$V_{T1} > V_{T2} > V_{T3}$$

Same slope.


2) By changing field current.

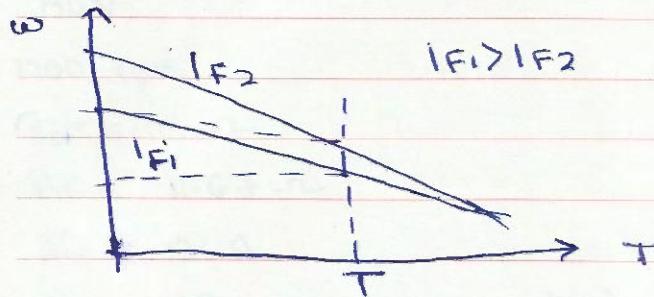

(Reducing flux reduces field current).

*Note:

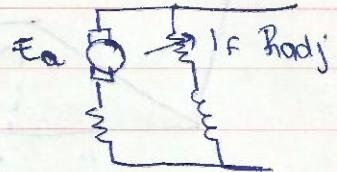To stop the motor, the armature circuit should be switched off before the field circuit (if not the opposite or else the speed increases to ∞ & the motor breaks).



$$E_a = k_m \Phi \omega$$

⇒ example:

$$E_a = 245$$

$$V_T = 250 \text{ V}$$

$$I_a = 20 \text{ A}$$

$$R_a = 0.25 \Omega$$


Reduction of I_F by 1%

$$E_a = 245 \times 0.99$$



$$= 242.55 \text{ V}$$

$$I_{a2} R_a = I_{a2} + 0.25 = 250 - 242.55 \Rightarrow I_a = 29.8 \text{ A}$$

3) Changing $R_a \cdot \omega$



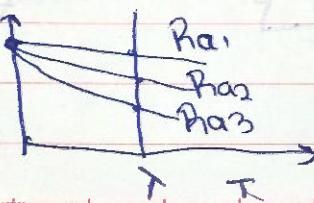


$R_{a3} > R_{a2} > R_{a1}$.

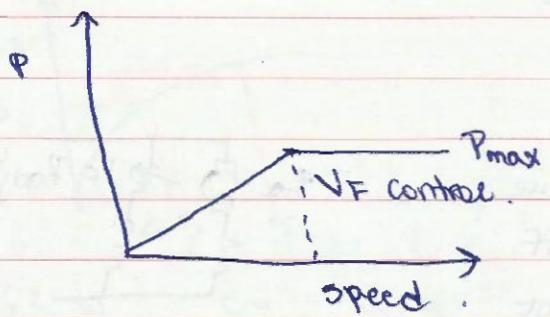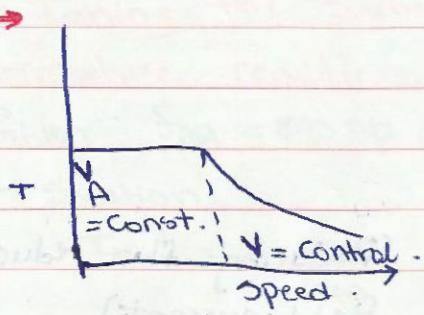

$$T = \frac{P}{\omega}$$
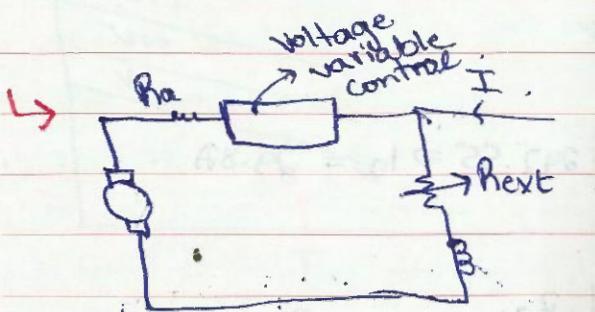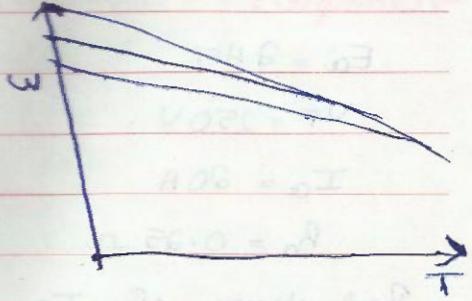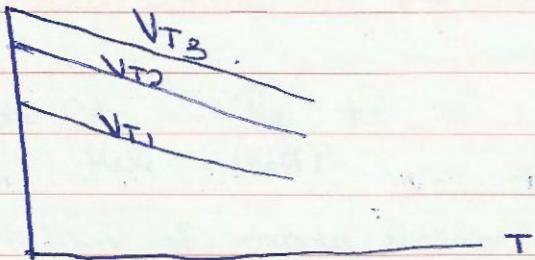
$$\omega = \frac{V_T}{(k_n s)} - \frac{R_A}{(k_n s)^2} T_n$$



\therefore The voltage variable control is used to change the 1st graph & R_{ext} for the 2nd.

→ Example :

100 hp

250 V

1200 rpm


$R_{sh} = 0.03 \Omega$

$R_F = 41.67 \Omega$

$I_L = 126 A$

$n_0 = 1103 \text{ rpm}$ $I_a = \text{constant}$

$R_F = 50 \Omega$

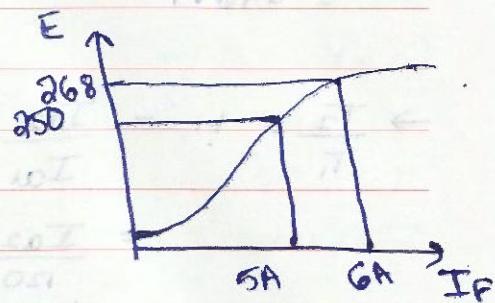

Solution:

$$I_F (\text{armature current}) = \frac{250}{41.67} = 6 A$$

$$I_a = 126 - 6 = 120 A$$

$$E_a = 250 - (120 * 0.03) = 246.4 V$$

$$I_{F2} = \frac{250}{50} = 5 A$$

$$\frac{n_1}{n_2} \times \frac{\Phi_1}{\Phi_2} = \frac{E_{a1}}{E_{a2}} = 1 \quad = \frac{1103}{n_2} \times \frac{268}{250} \quad \therefore n_2 = 1187 \text{ rpm}$$

⇒ ~~Assuming~~ Assume Linear region of saturation curve
if the torque on the motor is increased by 10%.
if the field current changed from 6 to 5 A. Find the speed.

Td $I_a \Phi$ ← Key to solution

E_a & $\omega \Phi$

$$\frac{T_2}{T_1} = 1.1 = \frac{I_{a1}}{I_{a2}} \cdot \frac{I_{F1}}{I_{F2}}$$
$$= 120 \times \frac{6}{5}$$
$$I_{a2} = \frac{120 \times 6}{5 \times 1.1} = \frac{144}{1.1} A$$

$$\begin{aligned} E_{d2} &= 250 - 150 + 130 \cdot 9 \cdot 0.03 \\ &= 246.1 \end{aligned}$$


$$\begin{aligned} \rightarrow \frac{T_2}{T_1} &= 1.1 = \frac{I_{d2}}{I_{d1}} \cdot \frac{I_{F2}}{I_{F1}} \\ &= \frac{I_{d2}}{120} \cdot \frac{5}{6} \end{aligned}$$


$$I_{d2} = \frac{120 + 6 \cdot 1.1}{5} = 158.4$$

$$\begin{aligned} E_{d2} &= 250 - 158.4 + 0.03 \\ &= 245.25 \end{aligned}$$


$$\begin{aligned} \frac{E_{d2}}{E_{d1}} &= \frac{n_2}{n_1} \cdot \frac{I_{F2}}{I_{F1}} \Rightarrow n_2 = \frac{245.25 + 1103 + 6}{246.4 \cdot 5} \\ \frac{245.25}{246.4} &= \frac{n_2}{1103} \cdot \frac{5}{6} \\ &= 1317 \text{ rpm} \end{aligned}$$

\Rightarrow Permanent Magnetic Motors:

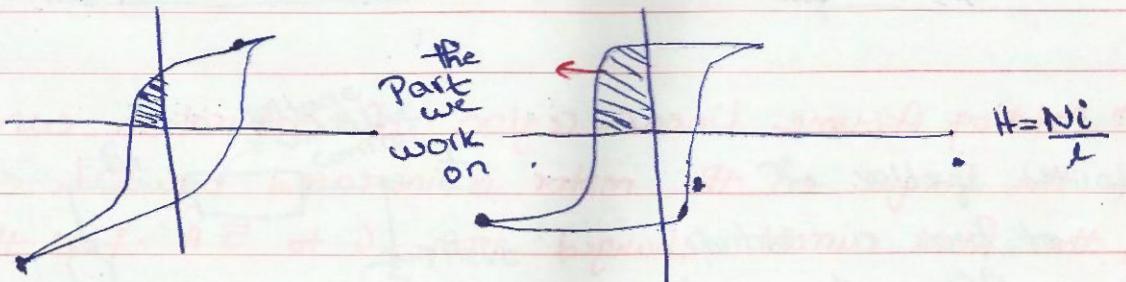

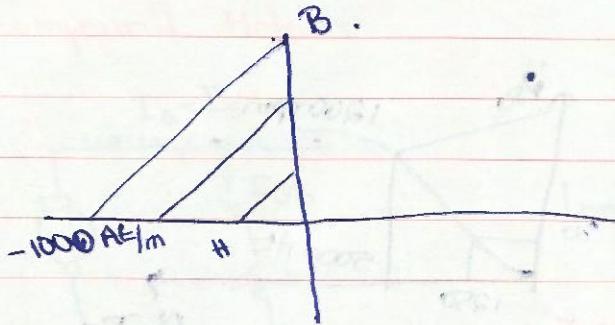

⇒ Series Motors:

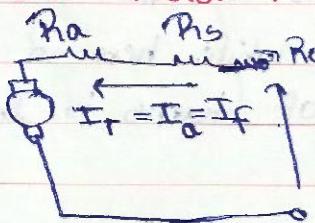

$$T \propto I_a \theta$$

$$T \propto I_a^2$$

$$I_a \propto \sqrt{T}$$

$$E_a \propto \theta \omega$$

$$E_a \propto I_a \omega$$


$$\omega \propto \frac{E_a}{I_a}$$

$$E_a = V_T - I_a (R_a + R_s + R_{ext})$$

$$K_i I_a \omega = V_T - I_a (R_a + R_s + R_{ext})$$

$$K_i \cdot \omega = \frac{V_T}{I_a} - \frac{(R_a + R_s + R_{ext})}{K_i}$$
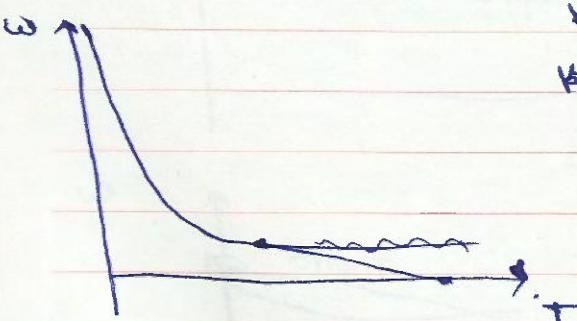
$$= \frac{V_T}{K_i I_a} - \frac{R_a + R_s + R_{ext}}{K_i}$$



If we switch on the motor with no load, speed is theoretically ∞ .

⇒ example:


250V.

$$R_a + R_s = 0.08$$

25 turns / pole

$$I_a = 50 \text{ A}$$

1200 rpm.

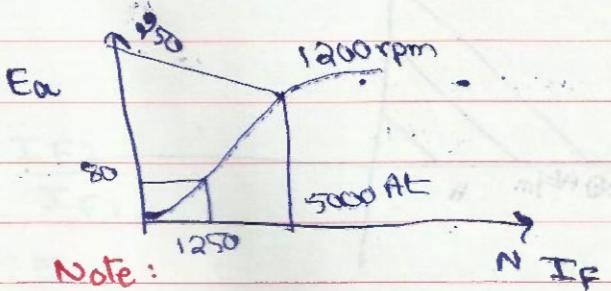

(In shunt I need a very high number of turns as the current is low while here in series the no. of turns is low)

Solution:

$$E_a = 250 - 50(0.08) = 246 \text{ V}$$

$$50 * 25 = 1250 \text{ AT}$$


From graph 1250 AT → 80V

$$\frac{n_1}{n_2} = \frac{E_1}{E_2}$$


$$\frac{246}{80} = \frac{1250}{100} \rightarrow n_2 = \text{rpm}$$

$$T = \frac{E_a I_a}{\omega} = \frac{246 * 50}{\frac{2\pi}{60}} =$$

→ Compound Motor:

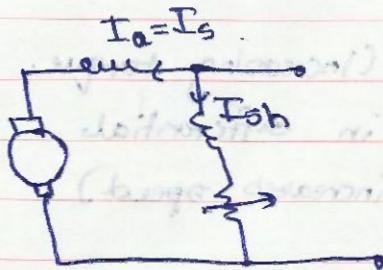

Long Shunt

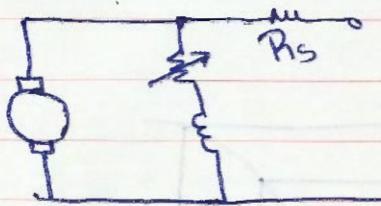

Short Shunt


$$\Phi_T = \Phi_{sh} + \Phi_s$$

→ Cumulative


$$\Phi_T = \Phi_{sh} - \Phi_s$$

→ Differential

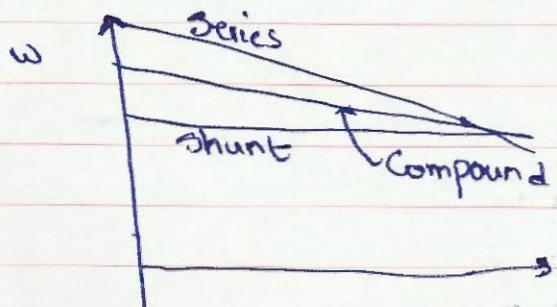* Therefore, I can have 4 types of compound motor.




at different speed

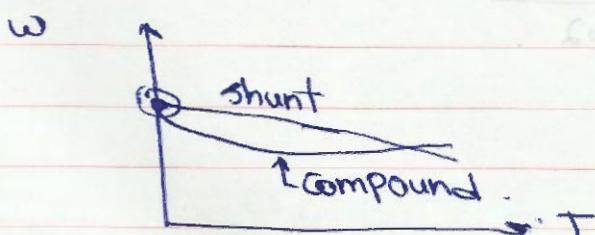

at the same speed

w

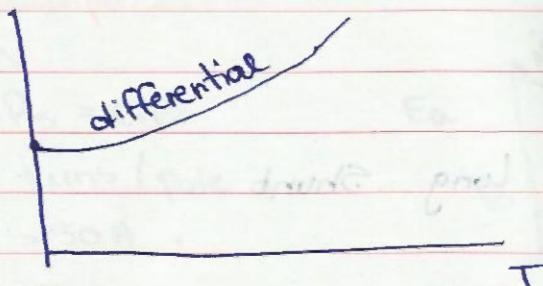

(Increasing torque
in differentials
increases speed)

→ Example :

$$100 \text{ hp}$$


$$250V$$

$$R_s + R_a = 0.04 - n$$

$$N_{sh} = 1000 \text{ turns}$$

$$N_{as} = 3 \text{ turns}$$

$$n_o = 1200 \text{ rpm}$$

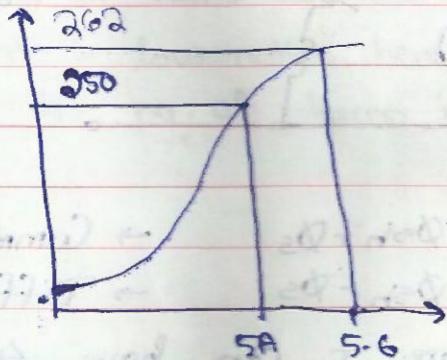

$$I_a = 200A$$

Solution :



$$E_a = 250 - 200 * 0.04$$

$$= 2. \quad \therefore 2V$$

$$I_F^* = 5 * \frac{3}{1000} * 200 = 5.4A$$

$$\frac{n_1}{n_0} = \frac{E_{a1}}{E_{a0}} \rightarrow \frac{n_1}{1200} = \frac{242}{262}$$

→ Starting of shunt DC motor

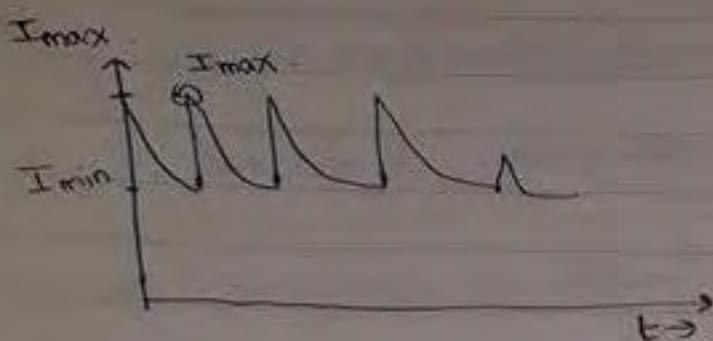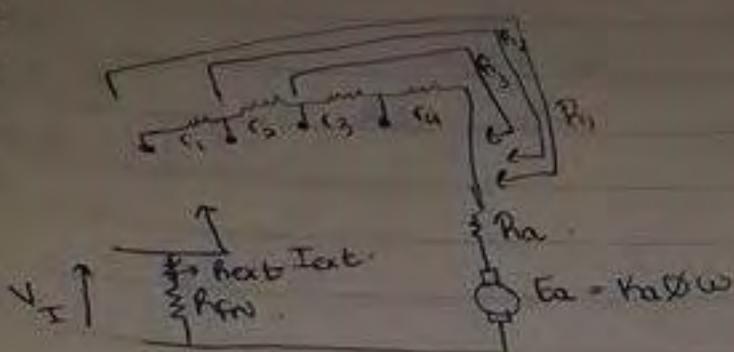

* $I_{\min} \leq I_{\text{rated}}$

→ At starting $E_a = 0$

$$I_{\max} = \frac{V_T}{R_T}$$

$$V_T = E_{a1} + I_{\min} R_1$$

$$E_{a1} = V_T - I_{\min} R_1 \quad \left. \right\} \quad I_{\min} R_1 = I_{\max} R_2$$

$$= V_T - I_{\min} R_2$$

$$\frac{I_{\max}}{I_{\min}} = \frac{R_1}{R_2} = \frac{R_2}{R_3} = \frac{R_3}{R_4} = \dots = \frac{R_n}{R_a}$$

$$\left(\frac{I_{\max}}{I_{\min}} \right)^n = \frac{R_1}{R_a}$$

$$n = \frac{\log \frac{R_1}{R_a}}{\log \frac{I_{\max}}{I_{\min}}}$$

→ Example

$$V_T = 200 \text{ V}$$

$$\text{Rated speed} = 1800 \text{ rpm}$$

$$I_{\max} = 1.6$$

$$F_{\min}$$

$$R_a = 0.2 \Omega$$

$$I_{\text{rated}} = 100 \text{ A}$$

Solution:

$$I_{\max} = 1.6 * 100 = 160 \text{ A}$$

$$R_1 = \frac{200}{160} = 1.25 \quad \left. \begin{array}{l} \\ \end{array} \right\} r_1 = 1.25 - 0.78 = 0.47 \Omega$$

$$R_2 = \frac{1.25}{1.6} = 0.78 \Omega \quad \left. \begin{array}{l} \\ \end{array} \right\} r_2 = 0.78 - 0.488 = 0.292 \Omega$$

$$R_3 = \frac{0.78}{1.6} = 0.488 \quad \left. \begin{array}{l} \\ \end{array} \right\} r_3 = 0.488 - 0.345 = 0.143 \Omega$$

$$R_4 = \frac{0.488}{1.6} = 0.305 \quad \left. \begin{array}{l} \\ \end{array} \right\} r_4 = 0.305 - 0.2 = 0.105 \Omega$$

$$R_5 = \frac{0.305}{1.6} = 0.193 \quad \left. \begin{array}{l} \\ \end{array} \right\}$$




$$E_{a1} = 200 - (100 * 1.25) = 75 \text{ V}$$


$$E_{a2} = 200 - (100 * 0.788) = 121.2 \text{ V}$$

$$E_{a3} = 200 - (100 * 0.488) = 151.2 \text{ V}$$

$$E_{a4} = 200 - (100 * 0.305) = 169.5 \text{ V}$$
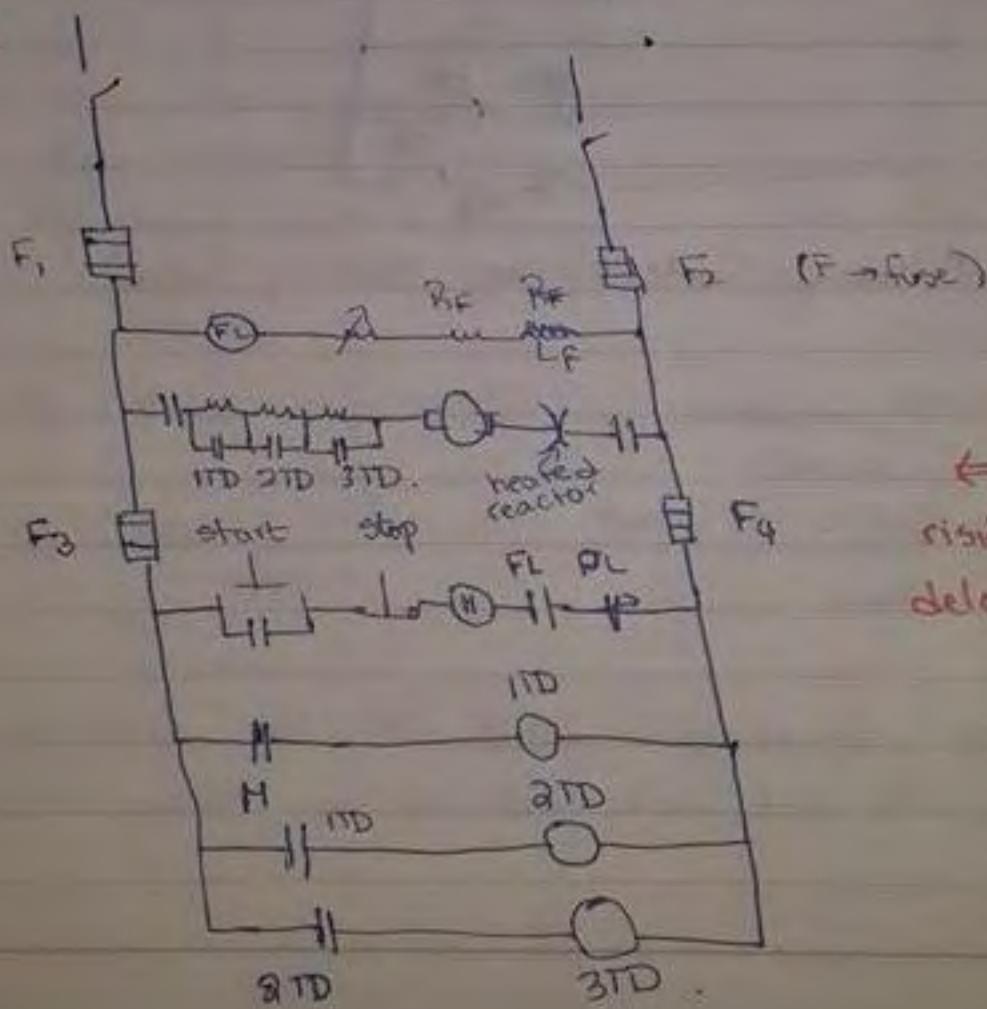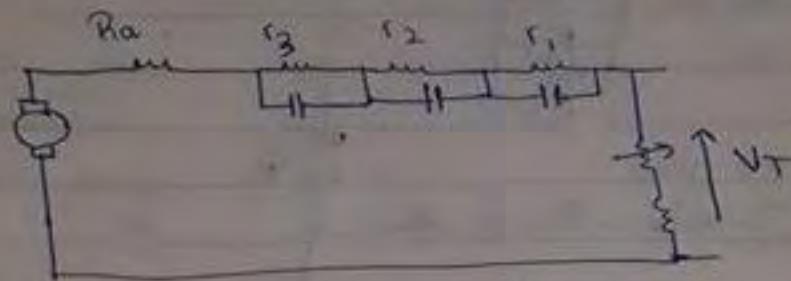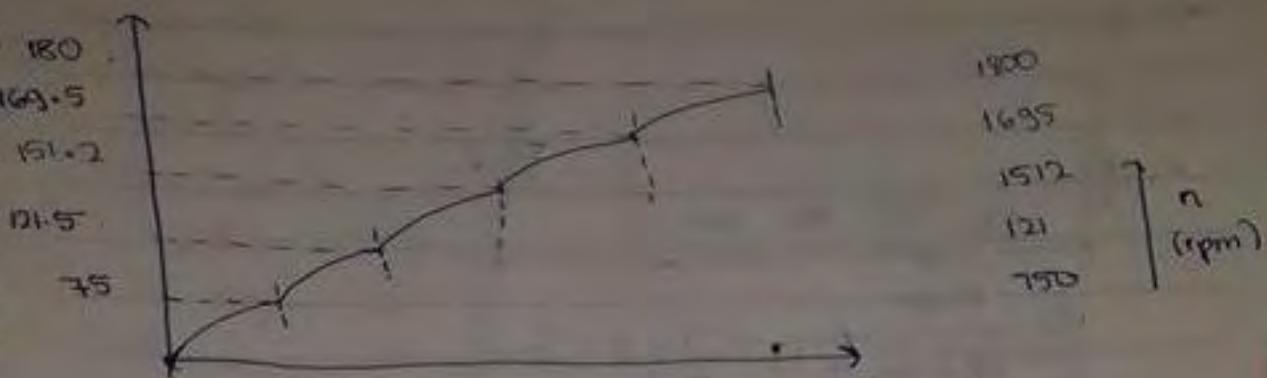
$$E_{a5} = 200 - (100 * 0.193) = 180 \text{ V}$$



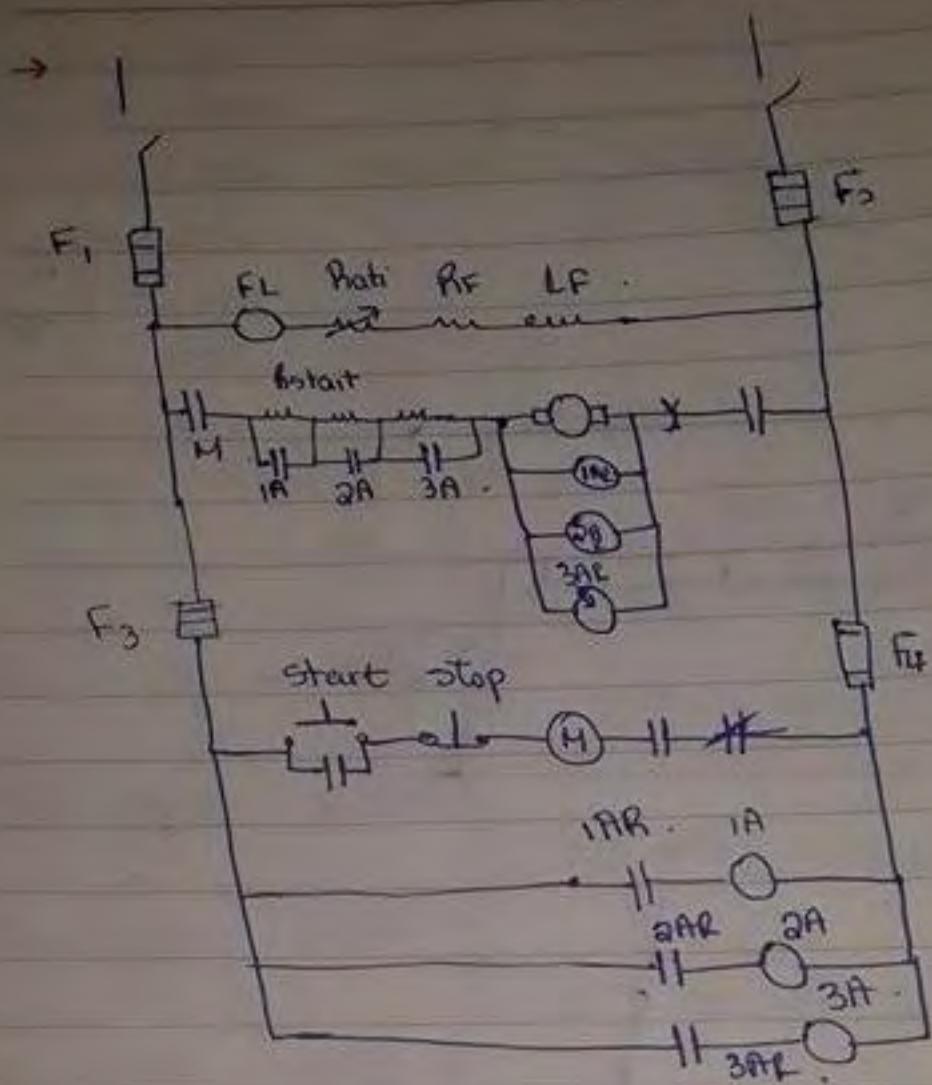

"Using Counter Voltage Sensing Relay"

* Losses:

Cu loss armature
 field.

Brush drop loss

Mechanical loss

Core loss

Stray loss

→ Example:

58 hp

250 V

1200 rpm

$$I_{\text{rated}} = 170 \text{ A}$$

$$I_{\text{F rated}} = 5 \text{ A}$$

$$\text{Blocked} = 10.2 \text{ V} \cdot 170 \text{ A}$$

$$250 \text{ V} \cdot 5 \text{ A}$$

$$N = 24 \text{ brushes}$$

$$V_{NL} = 240 \text{ V} \quad 1170 \text{ rpm} \quad 13.2 \text{ A} \quad 4.8 \text{ A}$$

↳ Solution:

$$P_R = \frac{10.2}{170} = 0.06 \text{ W}$$

$$R_F = \frac{250}{5} = 50 \text{ m}\Omega$$

$$P_R = 170^2 * 0.06 = 1734 \text{ W}$$

$$P_F = 5^2 * 50 = 1250 \text{ W}$$

$$P_{\text{brushes}} = 2 * 170 = 340 \text{ W}$$

$$I_{\text{total}} = 170 + 5 = 175 \text{ A} \quad (\text{input})$$

$$P_{\text{stray}} = \frac{1}{100} * 43750 = 437.5 \text{ W}$$

$$P_{NL} = 240 * 13.2 = 3168 \text{ W}$$

$$P_{in} = 250 * 175 = 43750 \text{ W}$$

$$\frac{240 * 13.2}{50 * 175} = 240$$


$$\eta = \frac{43750 - 1734 - 1250 - 340 - 3168 - 437.5}{43750} = 79.2 \%$$

(we don't take the 4.8A in consideration as it is the field current in no load & we have the Pf already)

→ Parallel operation of Synchronous Generators
(Synchronization)

3-lamp method:

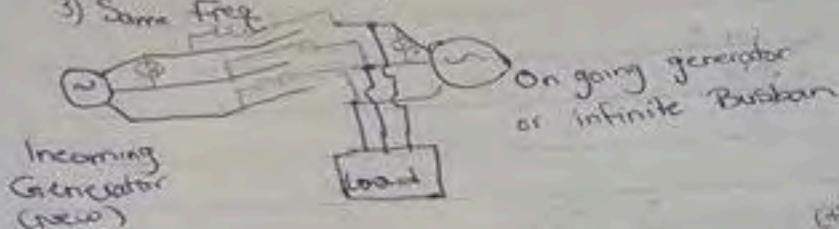- 1) Same Voltage
- 2) Same phase sequence
- 3) Same freq



4 same phase

(the voltmeter
to achieve the
first condition (same V))



$$f_2 = 51 \text{ Hz}$$

light - 11 توقف (stop)
مثلاً pattern (pattern)
phase shift - 11
- 20



→ For second condition of same phase sequence

Not in
phase seq

All ON & OFF at the same time


One lamp OFF + 2 ON

→ For 3rd condition → (the lamp)

Different freq = 2 * No. of ON & OFF / second

→ For 4th condition → All lamps are OFF & stay off

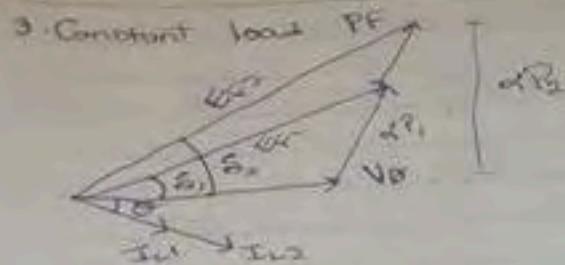(At the moment the 3 lamps are OFF, I close
the switch & connect the lamps in parallel)



\Rightarrow Torque (or Power) angle $\sim 53^\circ$ (approx)

5-28

20 MVA

12.2 kV

0.8 pf lag

γ

$X_d = 1.1 \text{ p.u}$

12.2 kV Bus

$$Z_{bus} = \frac{\delta V_d^2}{\delta}$$

$$V_d = \frac{12.200}{\sqrt{3}} = 7044 \text{ V}$$


$$Z_{bus} = \frac{3 \times 7044^2}{20,000,000} = 7.44 \text{ } \Omega$$

$$X_d = 1.1 * 7.44 = 8.18 \text{ } \Omega$$

$$I_{rated} = \frac{20,000,000}{53 + j2200}$$

$$= 946 + j -36.87$$
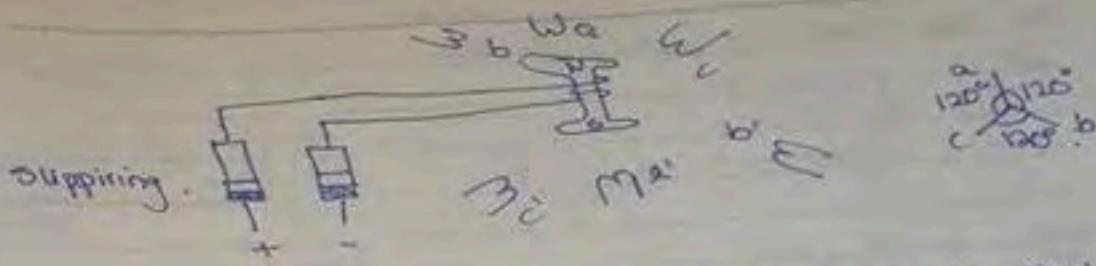
$$\begin{aligned} E_f &= V_d + I_{rated} Z_d \\ &= 7044 + 946(0.8 - j0.6) \\ &= 13230 \text{ } \angle 27.9^\circ \end{aligned}$$




(Here, the slipping is one piece & the brush is attached & when the piece moves, the brush touches the piece)

→ Infinite Busbar :-

$$V_T = \text{Constant}$$

$$R_S \approx 0$$

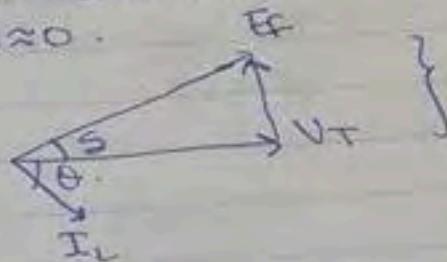

$$\left\{ X_s I_L \cos \theta = E_f \sin S \right\} d\theta$$




$$\frac{3V_T}{X_s} + X_s I_L \cos \theta = E_f \sin S * \frac{3V_T}{X_s}$$

$$= 3V_T I_L \cos \theta = \frac{3V_T E_f \sin S}{X_s} = ?$$

Power \rightarrow $\frac{3}{2} V_T^2 \sin^2 S = \frac{3}{2} V_T^2 \cos^2 \theta$

If \rightarrow کم ویس بفردا
 $P \rightarrow$ امکانیک " "

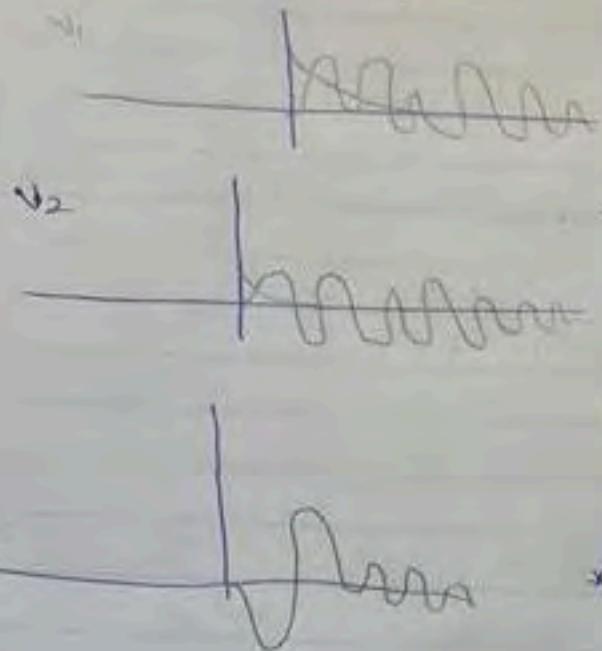- * same before & same after equation EQ instead of P3
- * Transient of Synchronous Generators:
Sudden change into the load



- * short happened $\rightarrow I$ will pass until something happened
- * The short is dependent on the impedance

* Protection \rightarrow $\bar{O}^{\prime \prime} \bar{S}^{\prime \prime} \bar{A}^{\prime \prime}$ $\bar{U}^{\prime \prime} \bar{U}^{\prime \prime} \bar{U}^{\prime \prime}$
use all three phases


* Protection on all the systems

40-50 cycle
 $T' = 15$

$T'' = 0.045$
sec
2 cycles

Subtract Transient
 X_S''

Final State
 X_S'

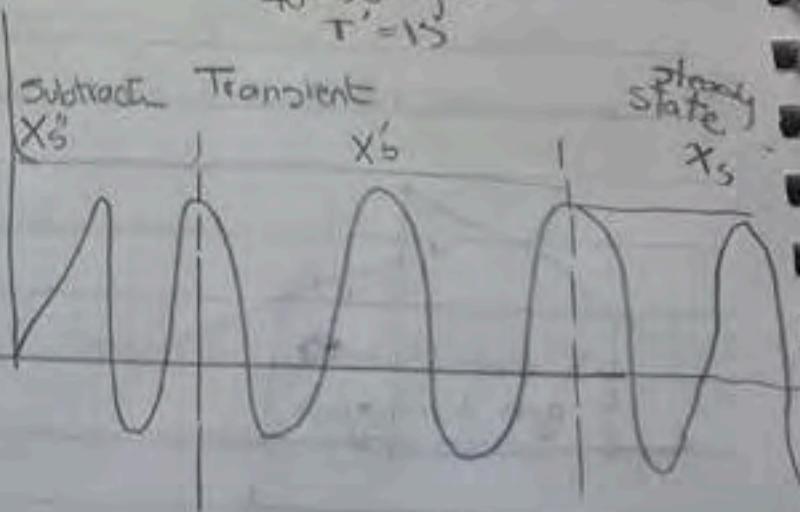

→ If the power is increased by 10%.

$$E_P = 0.75 \times 13230 = 9922.5$$

$$\sin S_1 = \frac{13230}{9922.5} \sin 27.9^\circ = 0.816$$

$$I_L = \frac{13230 \times 0.816 - 7704}{38.18}$$

$$= 262 \angle -6.6^\circ$$

⇒ If the power is increased by 10%. Keeping I_C the same.

$$\frac{P_2}{P_1} = \frac{E_P \sin S_2}{E_P \sin S_1} = 1.1$$

$$\sin S_2 = 1.1 \sin 27.9^\circ$$

$$I_L = \frac{13230 \times 0.97 - 7704}{38.18}$$

$$= 915 \angle -32.27^\circ$$




$$I_a = 50 \text{ A}$$

$$P_{700}$$


$$106 + 50 + 0.18 = 157 \text{ V}$$

$$\frac{157}{1800} = 121 \text{ V}$$

* Series Generators:

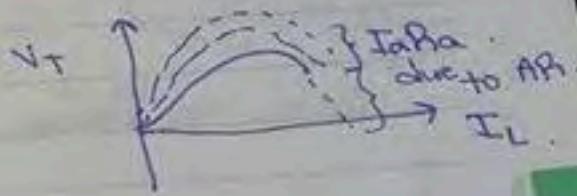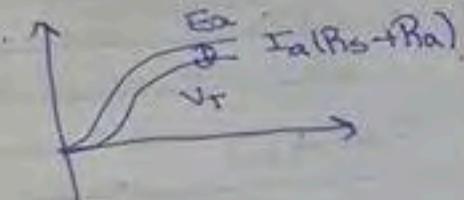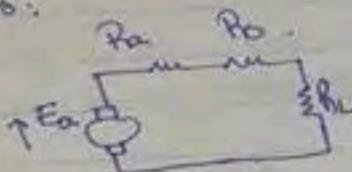

↳ Compound DC generator:

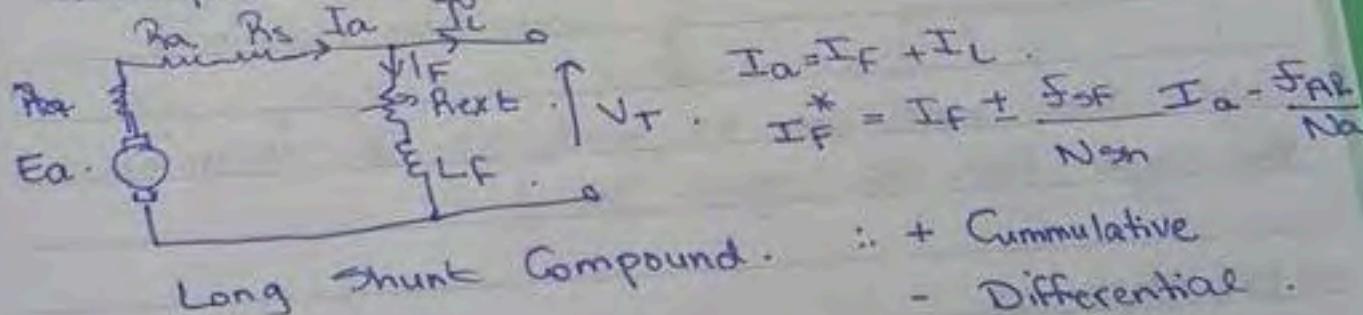

$$I_a = I_F + I_L$$

$$I_F^* = I_F + \frac{S_{SF}}{N_{sh}} I_a - \frac{S_{AR}}{N_b}$$


\therefore + Cumulative
- Differential

$$\phi_{AB} + \phi_{Sh} + \phi_{Sh} * \phi_T \quad \text{Cumulative}$$

$$\phi_{AB} + \phi_{Sh} + -\phi_0 = \phi_T \quad \text{differential}$$

$$I_a = I_L + I_F$$
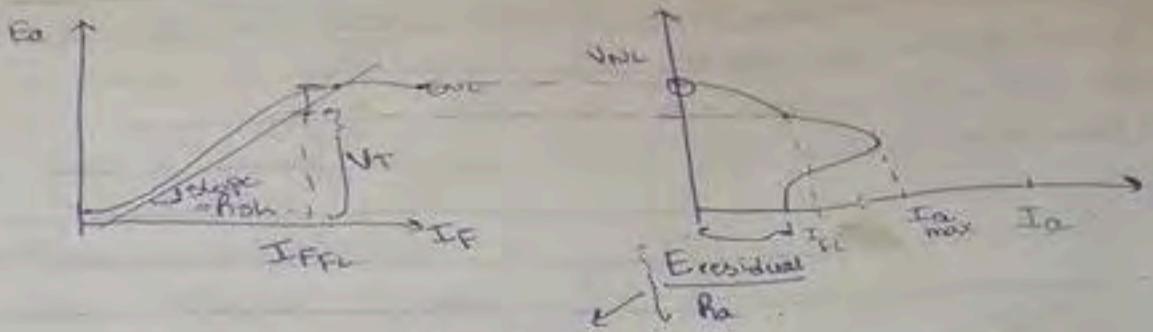
$$I_F^* = I_F + \frac{S_{SF}}{N_{sh}} I_a - \frac{S_{AR}}{N_b}$$




we get this
from making R_a a s.c.

Δ ← the
generator
practically
works
here
only (base FL)

External Characteristics

→ Example: (9-22)

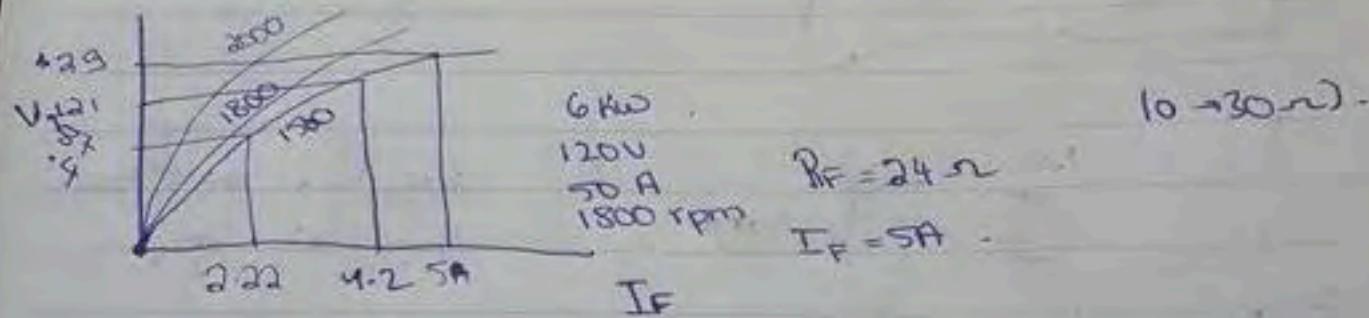

Solution:

$$\frac{120}{24} = 5 \text{ A}$$


$$\frac{120}{24+30} = 2.22 \text{ A}$$

$$I_{F\ min} = \frac{87.4 * 1500}{1800} = 72.8 \text{ A}, \quad I_{F\ max} = \frac{129 * 2000}{1800}$$


$$(1500 \text{ rev } \omega_s) = 143 \text{ A}$$

$$(2000 \text{ rev } \omega_s)$$


Frequency Power:

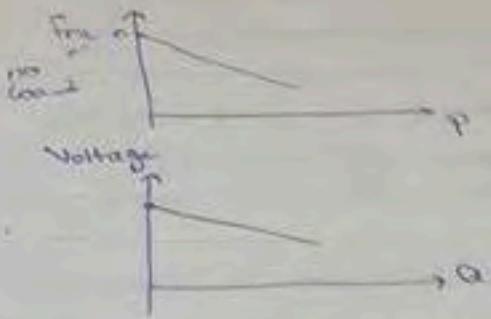


$$\alpha = \frac{120f}{V}$$

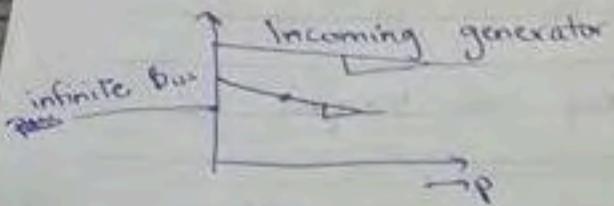

f vs. P (slope = HZ/kW)


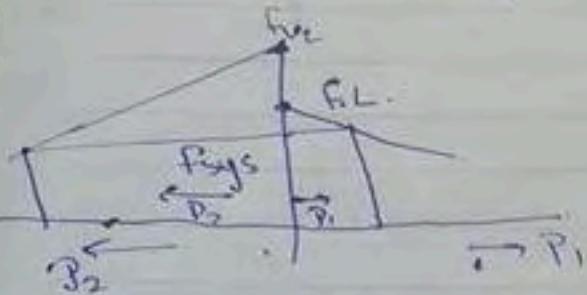


$$P_2 + P_1 = P_{\text{total}}$$

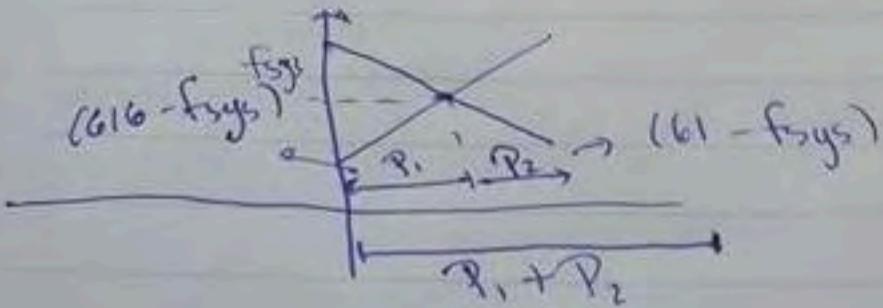

Frequency Power:


$$\Delta f = \frac{V_{sys}}{X}$$

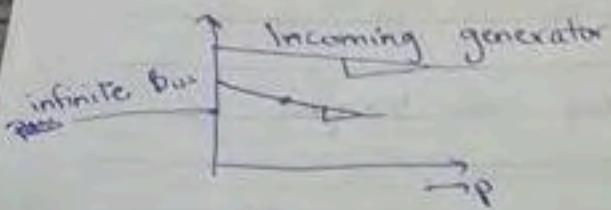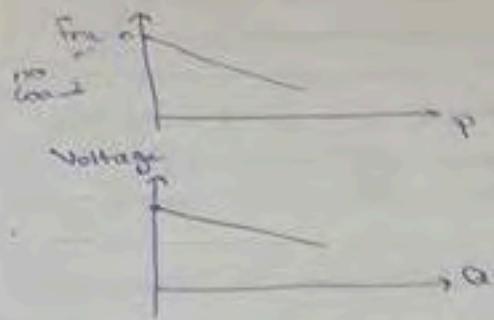

$\Delta f \leftarrow f_{ini} - f_{sys}$
slope = H_2 / X_{bus}



$$P_2 + P_1 = P_{total}$$

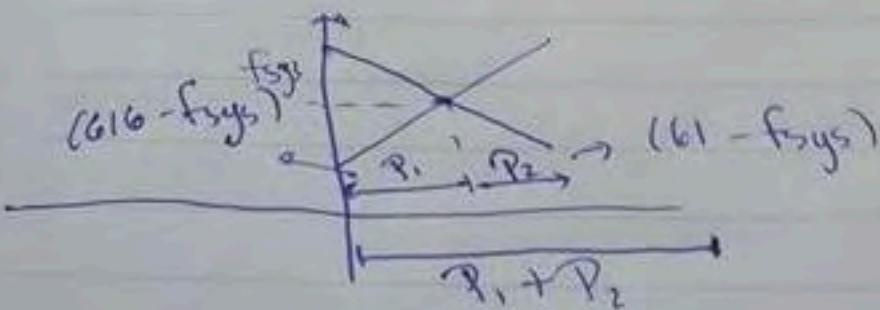


$$I(\omega) = (2 - \omega^2) + \frac{1}{\omega^2} + (2 - \omega^2)c \frac{\omega^2}{\omega^2 + \omega_0^2}$$


$$\omega_0^2 = 16300 - 16700 = \frac{1}{\omega_0^2} + (16300 - \omega_0^2)c$$

$$= 400 \Rightarrow \omega_0 = 20\sqrt{2}$$

→ Capability Curve: C.P.Q

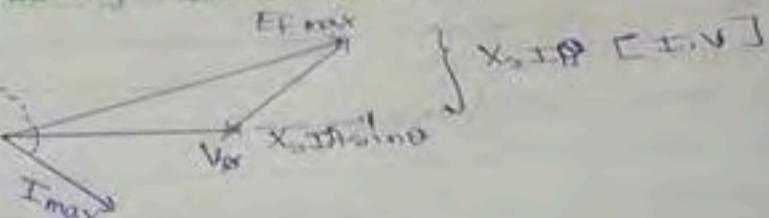

Phasor Diagram

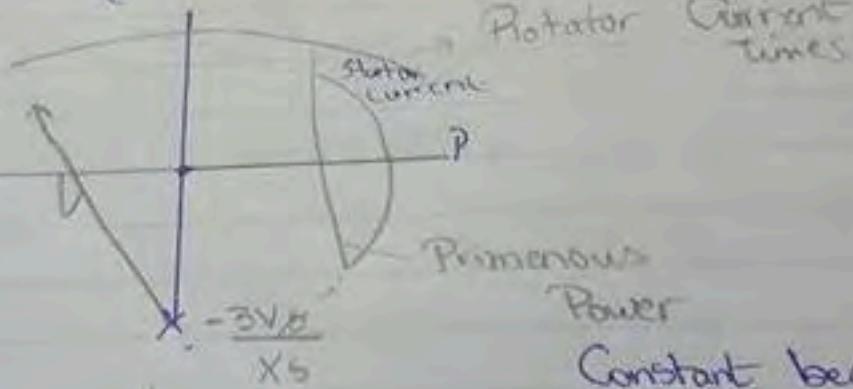

Power
Constant because
it doesn't
depend on I
excitation nor Q

$$Q = 3V_B I_A \sin \phi$$

$$S = 3V_B I$$

$$P = 3V_B I_A \cos \theta$$


$$= \frac{3V_B}{X_B} (X_B I_A \sin \theta)$$

$$= \frac{3V_B}{X_B} (X_B I_A \cos \theta)$$


$$Q = \frac{3V_B}{X_B} (-V_B) = -\frac{3V_B^2}{X_B}$$

- Q axis

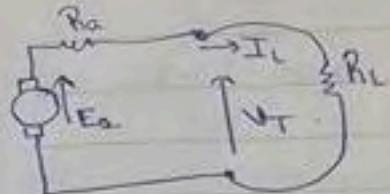
- * DC generator:
- 1. Separately excited
- 2. Shunt
- 3. Series
- 4. Compound \rightarrow Cumulative
 \hookrightarrow Differential



$$E_a = K_a \phi w$$

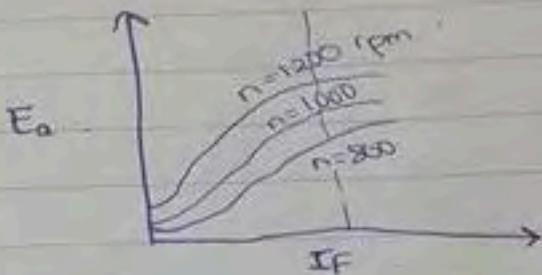


$$V_T = E_a - I_a R_a$$

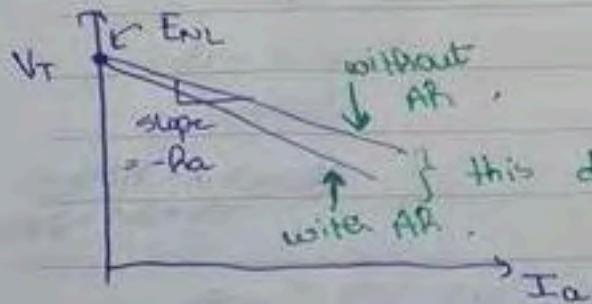

this difference is due to AR
 (armature reaction)

$$I_f^+ = I_f - \frac{f_{AR}}{N_A}$$

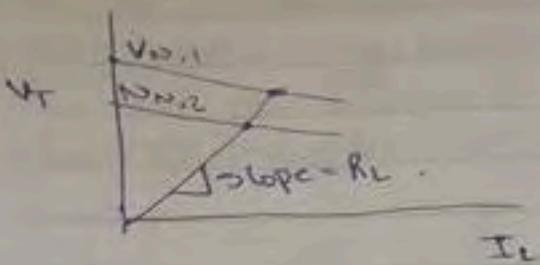

→ Example :-

$$172 \text{ k} \omega$$

$$430 \text{ V}$$

$$400 \text{ A}$$

$$1800 \text{ rpm}$$

$$R_{\text{adj}} = 0.05 \text{ } \Omega$$

$$V_F = 430 \text{ V}$$

$$Z_F = 20 \text{ } \Omega$$

$$N_F = 1000 \text{ turns/pole}$$

$$R_{\text{adj}} = 0 \rightarrow 300 \text{ } \Omega$$

→ 63 Ω

$$1600 \text{ rpm}$$

→ Solution:-


$$I_F = \frac{430}{20 + 63} = 5.2 \text{ A}$$

$$E_{\text{as}} = \frac{1600}{1800} \times 430 = 382 \text{ V}$$

$$V_r = 382 - 360 \times 0.05 = 364 \text{ V}$$

$$I_F^* = 5.2 - \frac{450}{1000} = 4.75 \text{ A}$$

Given Graph

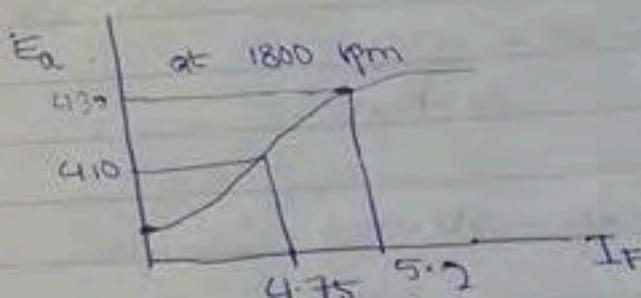

→ Example:

$$Q_1 = 50 \text{ MVar}$$

$$Q_2 = 60 \text{ MVar}$$

$$P_{\text{tot}} = 2.5 \text{ MW}$$

$$\omega_1 = 1 \text{ rad/sec}$$

$$\omega_2 = 1 \text{ rad/sec}$$

$$0.87 \text{ f lag}$$

Solution:

$$\textcircled{1} \quad P_1 = 1 \text{ MW} = (G1) \omega_1 - F_{\text{avg}}$$


$$P_2 = 1 \text{ MW} = (G2) \omega_2 + F_{\text{avg}}$$

$$P_1 + P_2 = 2.5$$

$$P_1 = 1 \text{ MW}$$

$$P_2 = 1 \text{ MW}$$

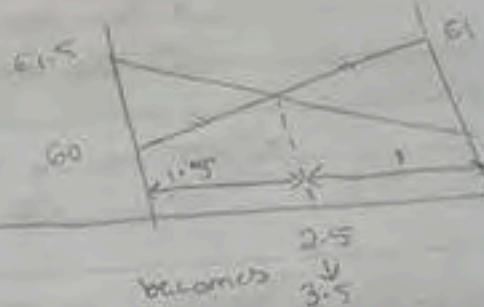
$$\Rightarrow F_{\text{avg}} = 0.0 \text{ Hz}$$



$$\textcircled{2} \quad P_1 + P_2 = 3.5 \quad f_{\text{avg}} = 59.75 \text{ Hz}$$

$$P_1 = 2 \text{ MW} \quad P_2 = 1.5 \text{ MW}$$

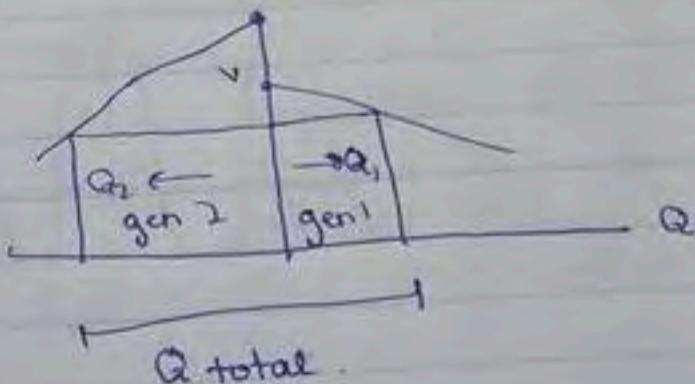\textcircled{3} Some stop & some fNL, so they're equally the same



P → $\frac{dP}{dQ}$
 V → $\frac{dV}{dQ}$
 I → $\frac{dI}{dQ}$
generators → load

→ Example:

$$Q_1 = 50.5 \text{ MVar}$$

$$Q_2 = 61 \text{ MVar}$$

$$P_{\text{tot}} = 2.5 \text{ MW}$$

$$\Delta f = 1 \text{ Hz/MW}$$

$$\Delta P_2 = 1 \text{ MW/Hz}$$

$$0.875 \text{ f lag}$$

Solution:

$$\textcircled{1} \quad P_1 = 1 \text{ MW} = (G_1) \cdot 5 - (\text{f lag})$$


$$P_2 = 1 \text{ MW} = (G_2) \cdot 61 - (\text{f lag})$$

$$P_1 + P_2 = 2.5$$

$$P_1 = 0.875 \text{ MW}$$

$$P_2 = 1 \text{ MW}$$


→ f_{sys} = 59.75 Hz

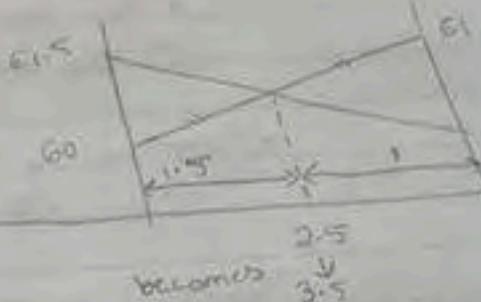





$$\textcircled{2} \quad P_1 + P_2 = 2.5, \quad f_{\text{sys}} = 59.75 \text{ Hz}$$

$$P_1 = 0.875 \text{ MW} \quad \therefore P_2 = 1.5 \text{ MW}$$

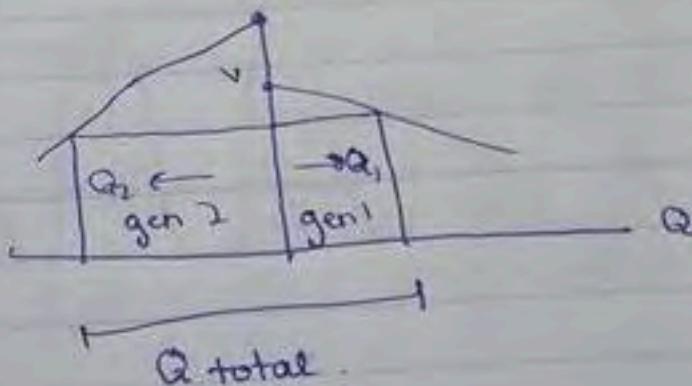$\textcircled{3}$ Same step & same f_{NL}, so they're equally far from f_{sys}



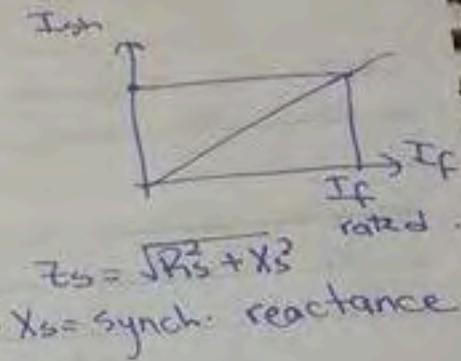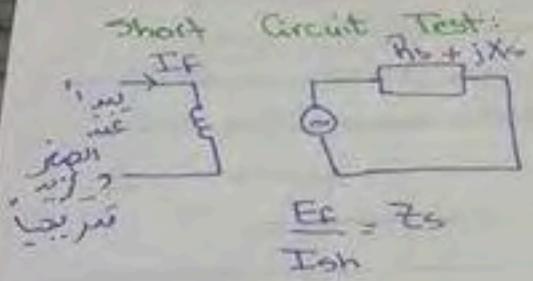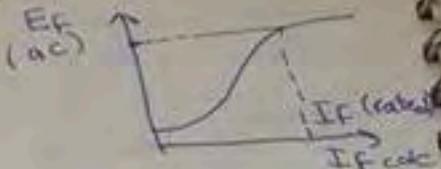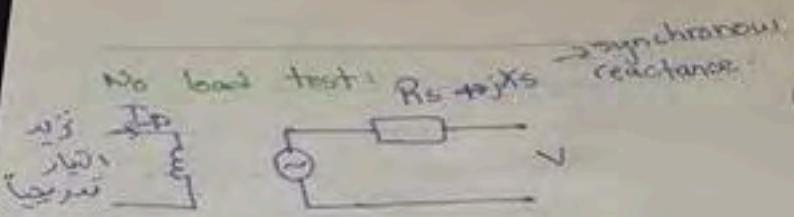P $\frac{dP}{dQ}$
 V $dQ_d I$
generators \rightarrow load





# of poles P	f	n
2	50	3000
4		1500
6		1000
8		750
12		583

$$V_T = E_F - I_L Z_S$$

$$E_F = V_T + I_L Z_S$$

$$E_F$$

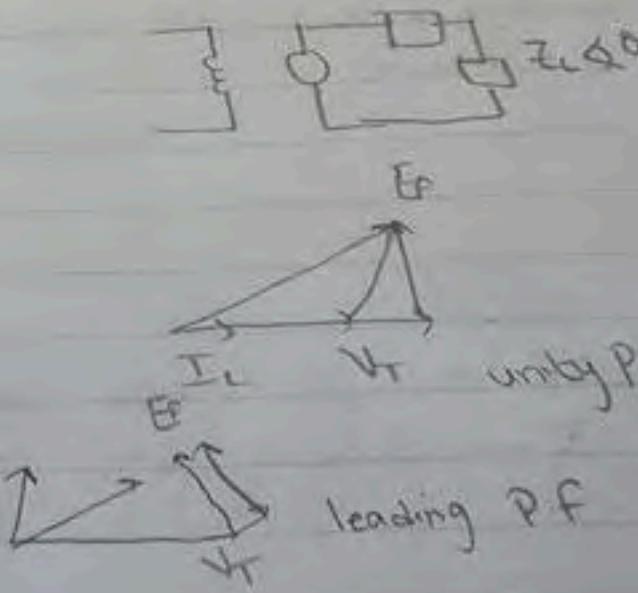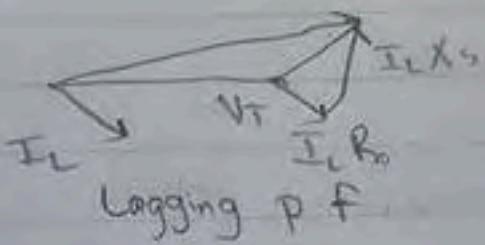


For the 3rd condition,
if I switch the direction
of emf, the graph will
look like this



- 1) residual flux 157.3
 - 2) practical
 - 3) the direction of short
circuit current in the same
direction of residual flux
- page 157 all ab 17
(flux ab 18)

therefore, no intersection with the flux

→ adding a load

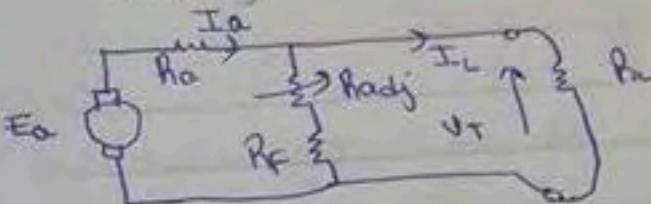

Graphically
non-linear
load



we find V_T & E_a
from this graph

From graph, you find E_a at 4.75A, $E_{ai} = 910V$
 Correcting it with speed: $E_{a2} = \frac{910 * 1600}{1800} = 364V$.

$$V_T = 364 - 360 * 0.05 = 346$$

$$382 + 0.05 * 360 = 400V$$


$$E_{a4} = 400 * \frac{1800}{1600} = 480V$$

From graph $I_F = 6.15$

$$6.15 = \frac{430}{20 + R_{ext}}$$

$$R_{ext} = 50\Omega$$

\Rightarrow 2) Shunt DC generator:

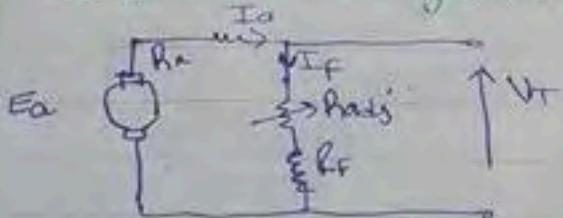


$$I_a = I_L + I_{sh}$$

$$V_T = E_a - I_a R_a$$

$$V_T = I_{sh} (R_F + R_{adj})$$


$$E_a = K_a \phi_0 \omega \quad R_{sh}$$

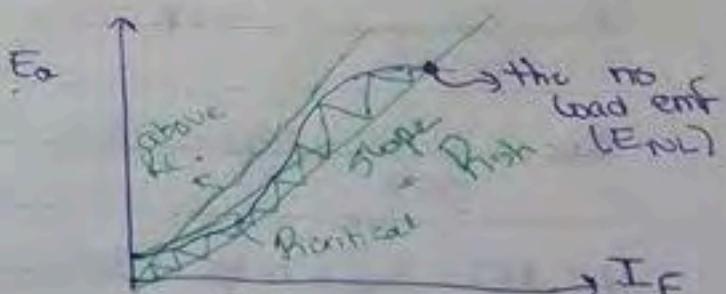We ignore R_a here, we divide E_a by $R_{adj} + R_F$ which $\rightarrow \ggg R_a$.






Practical is the resistance above which there will be no induced current, below which there will be induced current.

Equivalent Circuit :-

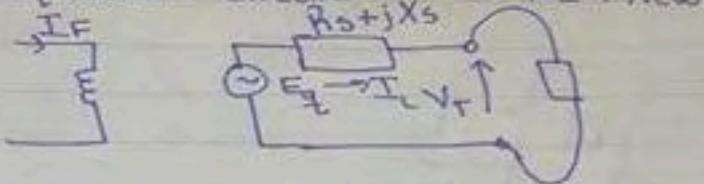

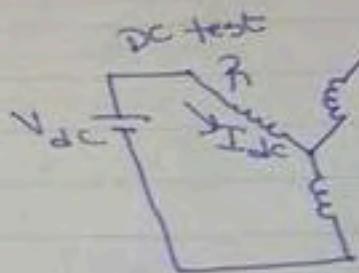
$$\frac{V_{DC}}{I_{DC}} = \frac{R_L + jX_L}{3R} = \frac{a_R}{3}$$



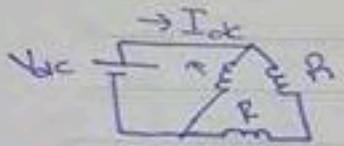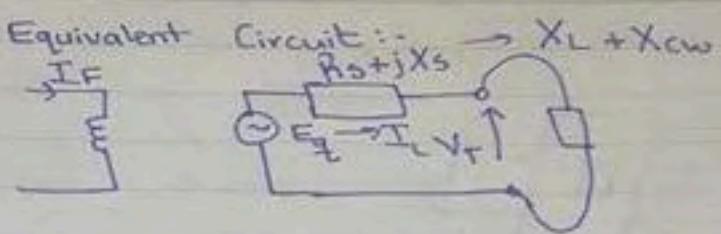
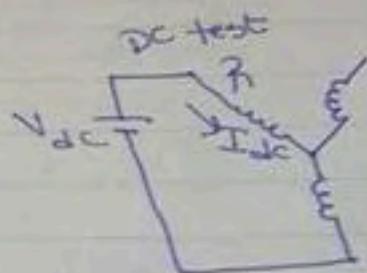
$$\frac{V_{AC}}{I_{AC}} = \frac{R_{12} + jX_{12}}{3R} = \frac{a_R}{3}$$



Decreasing E_F by 5%.

$$E_{F2} = 0.95 \times 13230 = 12570 \text{ V}$$


$$E_{F1} \sin 21^\circ = E_{F2} \sin 22^\circ$$

$$\frac{\sin 21^\circ}{\sin 22^\circ} = \frac{E_{F2}}{E_{F1}} = 0.95$$

$$22 = \sin^{-1} \frac{13230}{12570} \sin 21.9^\circ = 23.5^\circ$$


$$I_L = \frac{E_F - V_D}{Z_S}$$
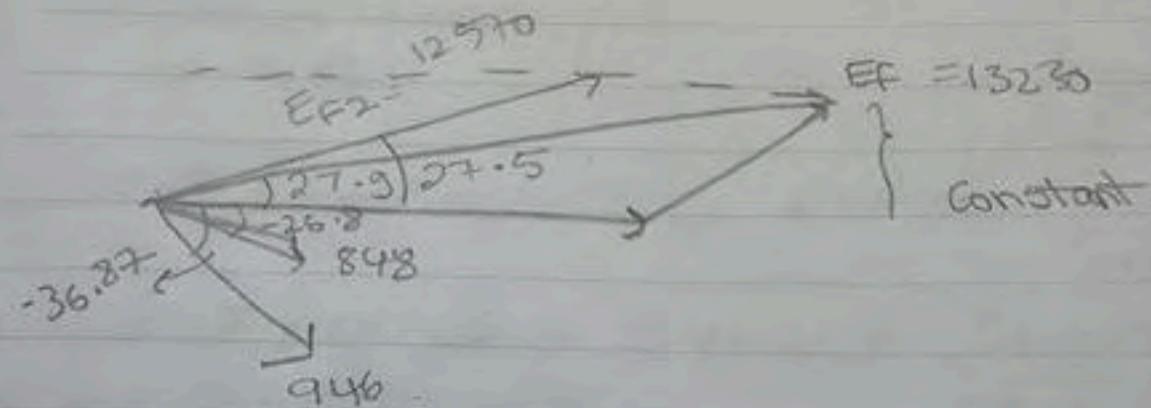
$$I_L = \frac{12570 \angle 23.5^\circ - 7044}{j 8.16} = 848 \angle -26.8^\circ$$



→ Hence there is a source.

Rotor

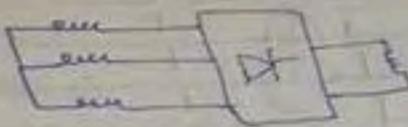

Stator

field coil





Exciter → DC source

DC source

main generator



Here there is no source

Rotor

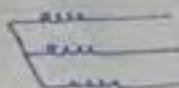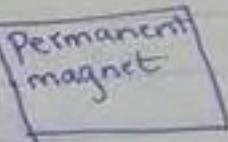

main generator

synchronous generator

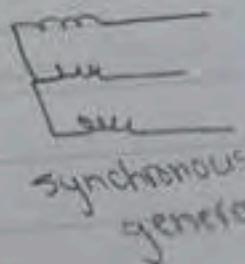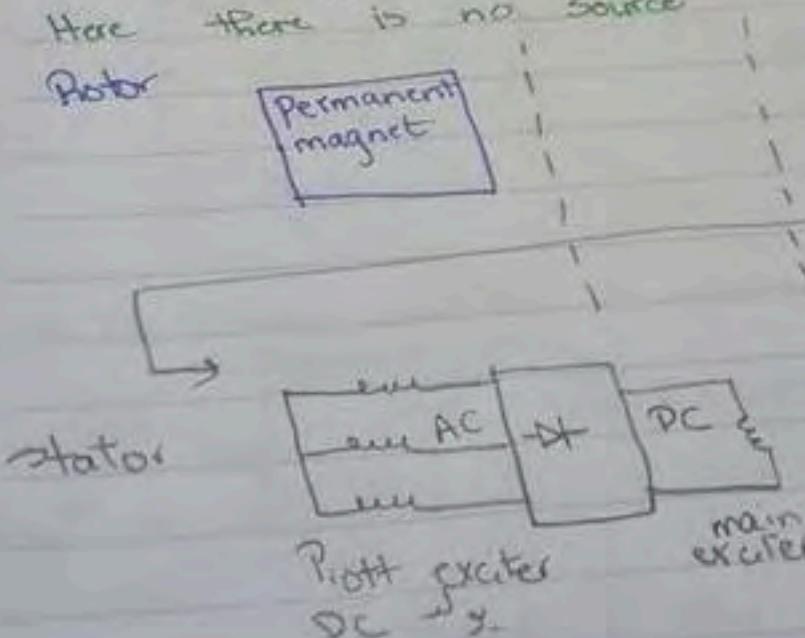

Example:

100 MVA

13.5 kV

Y

60 Hz

$$X_b = 1.2$$

$$X_b' = 0.25 \text{ m}, T' = 1.13$$

$$X_b'' = 0.12 \text{ m}, T'' = 0.095$$

$$I_{base} = 50 / \text{transient}$$

$$I_{base}$$

$$\rightarrow I_{base} = \frac{S_{base}}{\sqrt{3} V_{base}} = \frac{100 \text{ MVA}}{\sqrt{3} \times 13.5} = 4184 \text{ A}$$

$$\rightarrow I'' = \frac{E_p}{X_b} = \frac{1.0}{0.12} = 8.33 \text{ p.u.}$$

$$= 8.33 \times 4184 = 34950 \text{ A}$$

$$\rightarrow I' = \frac{1}{0.25} = 4 \text{ p.u.}$$

$$= 4 \times 4184 = 16700 \text{ A}$$

$$I_0 = \frac{1}{1} = 1 \text{ p.u.}$$

$$= 1 \times 4184 = 4184 \text{ A}$$

$$I_{dc} = \frac{50}{150} \times 34950$$

$$I_{tot} = 1.5 \times 34950 = 52375 \text{ A}$$




$$Y_0 T \cos \theta = E_F \sin \delta$$



$$\times \frac{3V_{ph}}{X_0} + \frac{3V_{ph}}{X_0}$$




$$3V_{ph} T \cos \theta = \frac{3V_{ph} E_F \sin \delta}{X_0} - P$$

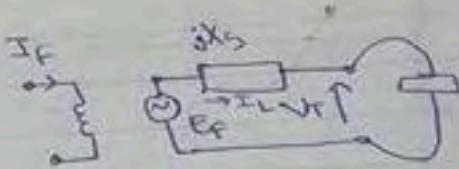1- Constant P Variable I_F
 (Real component of
 the current is constant)



2- Constant I_F variable P

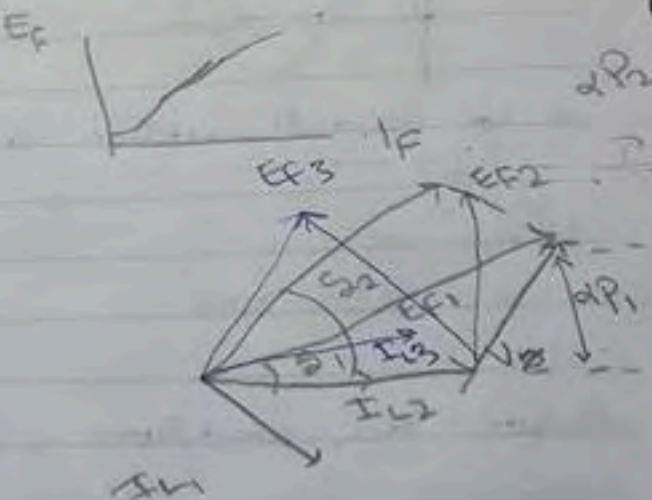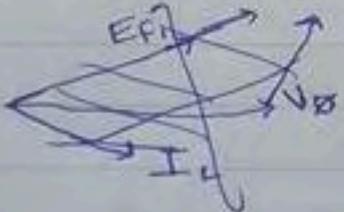

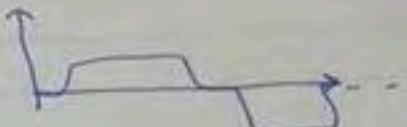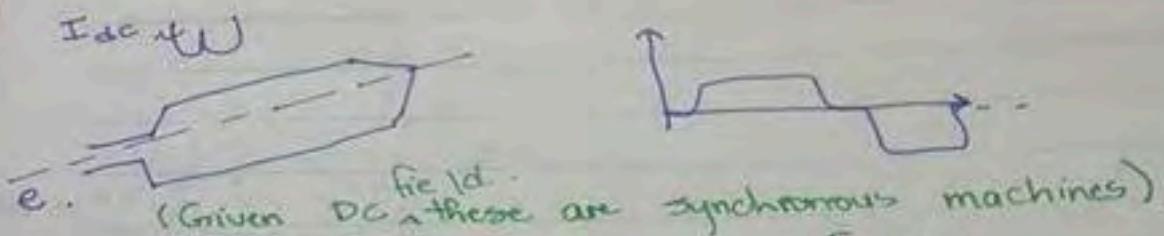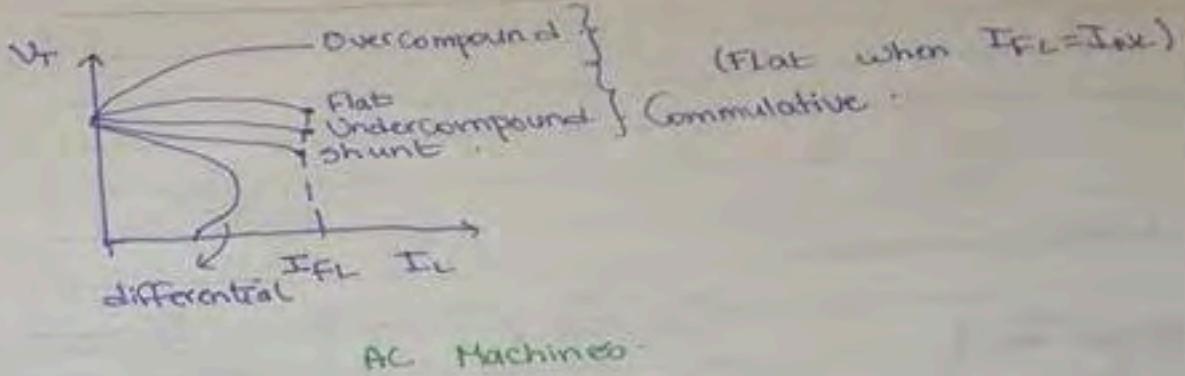

∴ Note that both are AC machines, I determine the type from the given field.

⇒ AC Machines

Synchronous.
Synch. Motor. Synch. Generator

Induction
Induction Generator

Induction *
Motor

→ * The most important & most used.