

Machines1

By: Sara Audeh

Dr.Aldalabezeh

POWER UNIT

Fall 2016

Magnetic Field and electric Circuits :-

What? magnetic Field

why? Because magnetic Field is Fundamental for the operation of Transformers, Generators, and motors as follows :-

[1] any Current (i) in a Conductor generates Magnetic Field (ϕ) around it. [The direction of ϕ can be found by using Right hand Rule \rightarrow (RHR)
 (ϕ is $\propto i$)

[2] time varying magnetic field passing through a coil or a Conductor will induce a voltage in this coil or Conductor. This is the concept of transformer operation.


[3] If a conductor cut a magnetic field then a voltage will be reduced in it. This is the concept of generator operation.

[4] A current carrying conductor in a magnetic field will experience a force. This is the concept of motor operation.

How?? The objective is to find ϕ for a given i
 OR to find i for a given ϕ

* This can be solved approximately by the concept of magnetic ckt. and introduced as follows :-

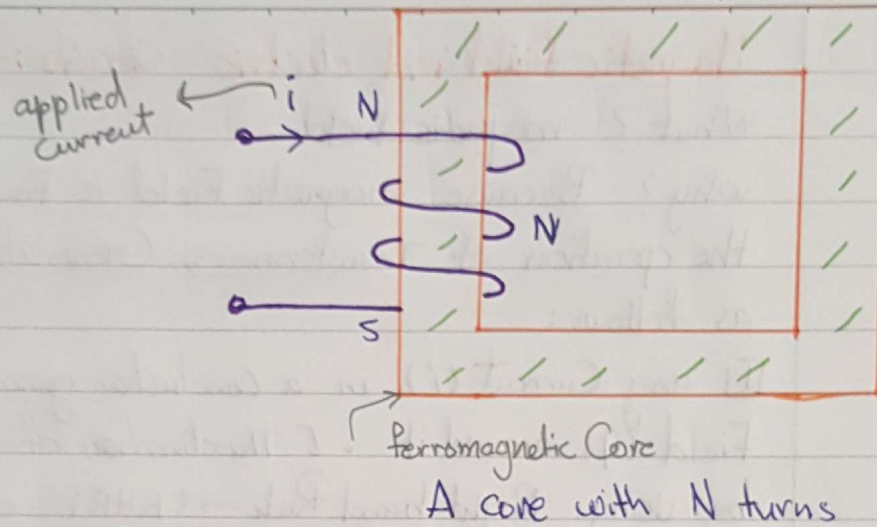Basic mathematical Laws and Relationships
 Consider the following system



Amper's Law:-

$$\oint H \cdot dl = I$$

المجال المغناطيسي

التيار الكلي المحاط بالحلقة

$H \equiv$ Magnetic Field strength or intensity.

شدة المجال المغناطيسي

$l \equiv$ a closed path or loop.

مسار مغلق

$I \equiv$ Total current enclosed by the loop.

التيار الكلي المحاط

\therefore For Uniform Magnetic Field, and for the mean length of Flux path \rightarrow

$$Hl = Ni \dots \textcircled{1}$$

القوة الدافعة

$l \equiv$ Mean length of Flux path (m)

$$H \equiv \frac{A \cdot t}{l \text{ m}}$$

Relation ship between flux density B and H is

$$B = \mu H$$

* Unit of B is wb/m^2 or

$\mu \equiv$ Called permeability (H/m)

Tesla.

of ferromagnetic material or Core.


$$\mu = \mu_0 \mu_r$$

\rightarrow for free space or air = $4\pi \times 10^{-7}$

$\mu_0 \equiv$ Permeability of free space.

$\mu_r \equiv$ Relative permeability of the material cores (2000-8000)

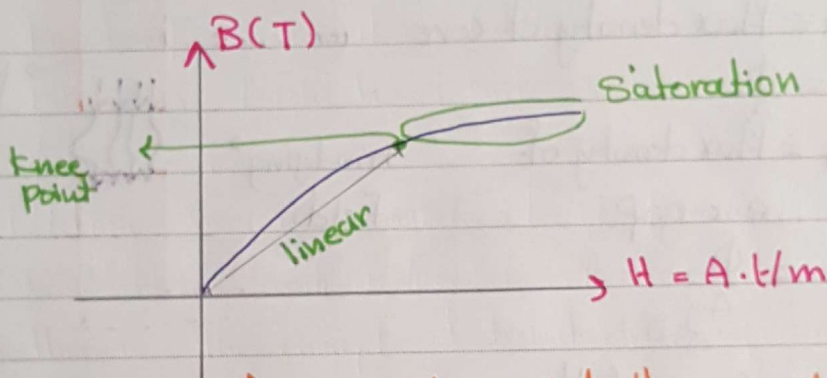* However in practice the relationship between B and H is nonlinear as follows:-



↑ This is also called the magnetization curve

$\therefore B = \frac{\Phi}{A}$ $A \equiv$ cross sectional Area of the core

$Ni = Hl = \frac{B}{\mu} l = \frac{\Phi}{\mu A} l$

$\therefore \boxed{Ni} = \frac{l}{\mu A} \Phi$


$Ni = R\Phi$

magnetomotive force (mmf) ρ

$\therefore \rho = R\Phi$

I want Reluctance as small as possible

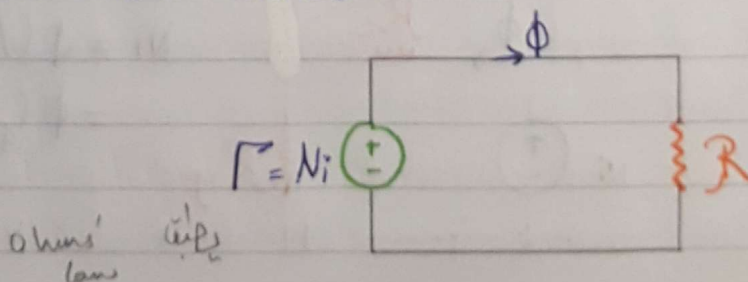By using Analogy with electrical circuits, the equivalent magnetic circuit will be :-



All circuit laws (ohm's, KVL, KCL) are applicable to magnetic circuit with $\text{mmf} \equiv \text{emf}$
 $\phi \equiv i$

Magnetic structure with air gap:-


$B_c \equiv$ flux density of core

$$= \frac{\phi}{A_c}$$

$B_g \equiv$ flux density of air gap

$$= \frac{\phi}{A_g}$$

Fringing Field

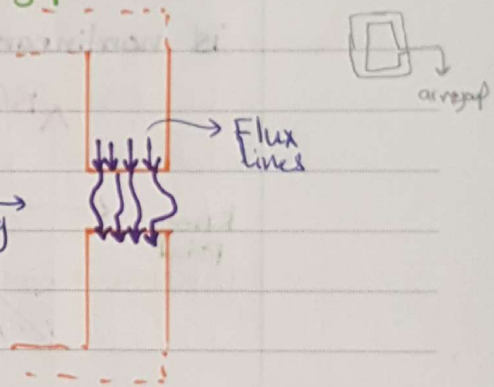

$A_g \equiv$ Area of the air gap

if the length of the air gap very small


Note:- A_g can be found approximately compare with the core + length of the gap
 for example: if $g \ll l_c$

Then all g to the sides of the core

OR multiply A_c by correction factor.

* If the fringing field is neglected then $A_g = A_c$
 $B_g = B_c$

Equivalent magnetic circuit

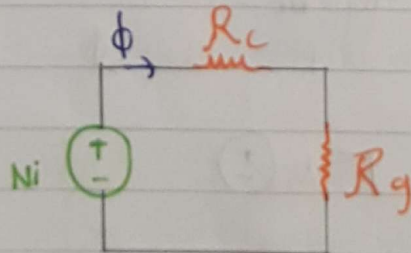


$$N_i = \phi (R_c + R_g)$$

$$= \phi \left(\frac{l_c}{A_c \mu_0 \mu_r} + \frac{g}{A_g \mu_0} \right)$$

Since air gap have high reluctance, then in electrical Machines, the air gap between the stator and the Rotor should be as small as possible (i.e just a clearance)

Illustration:-

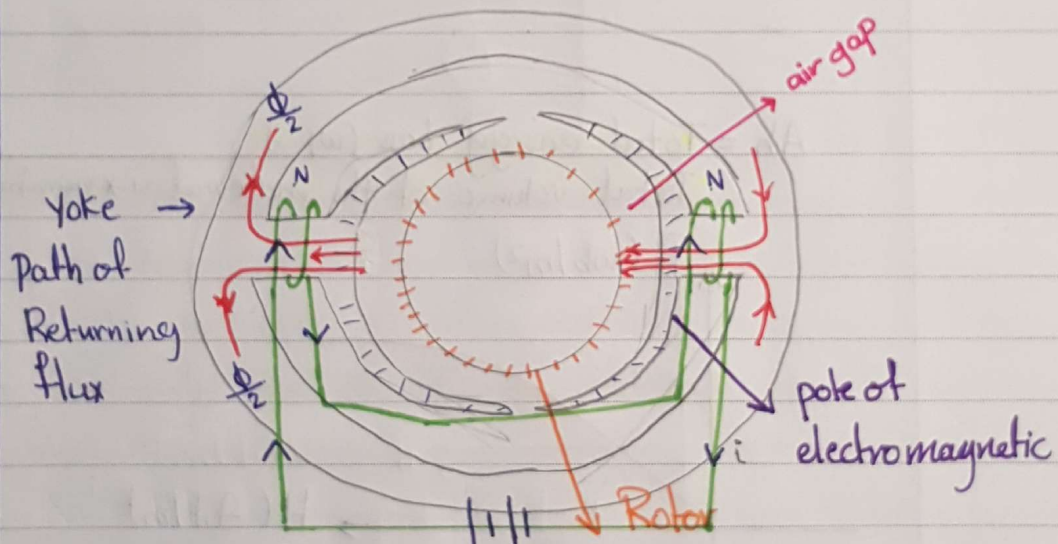
Find the equivalent Magnetic circuit of a 2-pole machine



yoke: path of Returning Flux

Nx: number of Turns

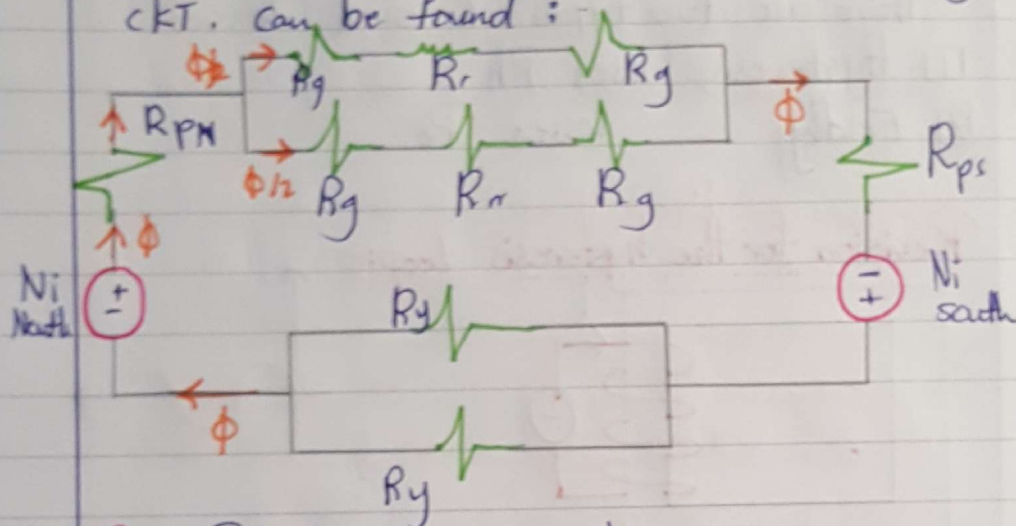Hence from the machine structure the following magnetic CKT. can be found :



- R_{pm} : Reluctance of the **North pole**
- R_g : Reluctance of the **air gap**
- R_r : Reluctance of the **rotor**
- R_{ps} : Reluctance of the **South pole**
- R_y : Reluctance of the **yoke**

By applying the Magnetic circuit laws:
By KVL:

$$-N_i + \Phi [(R_g + R_r + R_g) \parallel (R_g + R_r + R_g)] + \Phi [R_{ps}] - N_i + \Phi [R_y \parallel R_y] = 0 \dots \textcircled{1}$$





- hence by using equation (1) we can calculate Φ for a given N_i or N_i for a given Φ .

* there are some examples in the text Book

Losses in Ferromagnetic Materials:

- There are two types of such losses.
- 1] Hysteresis losses P_h
- 2] Eddy losses P_e


Revision for the hysteresis loop:

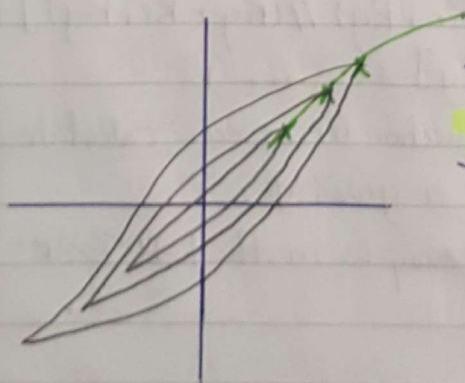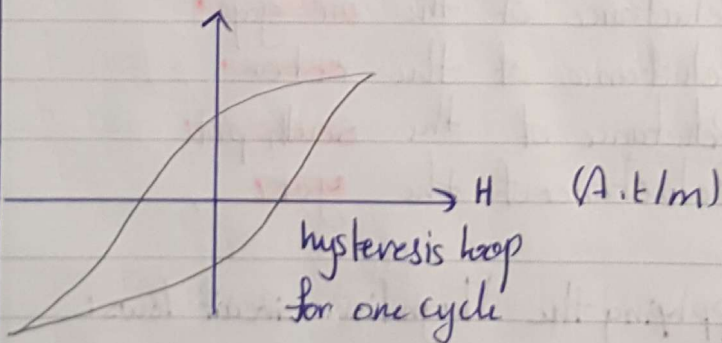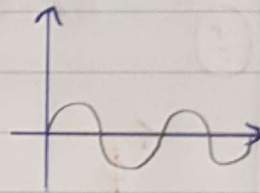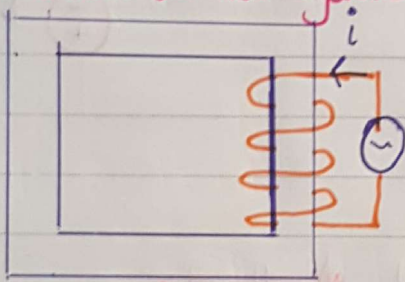

* The area of hysteresis loop $(B \cdot H) = \text{J/m}^3$
This is called energy density

* The area of H. loop is Energy Density / cycle (Ah)
جسٹاپ جو 2022

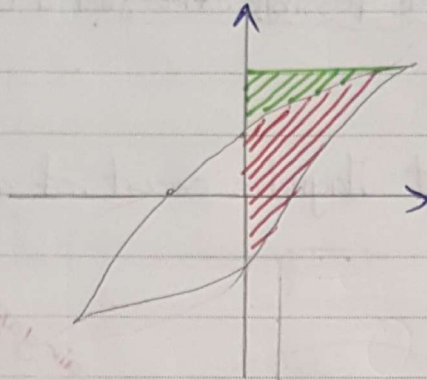
* the area of the hysteresis loop ($B \times H$) = J/m^3 this is called energy density.



Area in red: Supplied energy
 Area in Green: Area returned
 Area of H-loop: Ah = energy density per cycle

$$A_h = \text{Total energy loss (w) J}$$

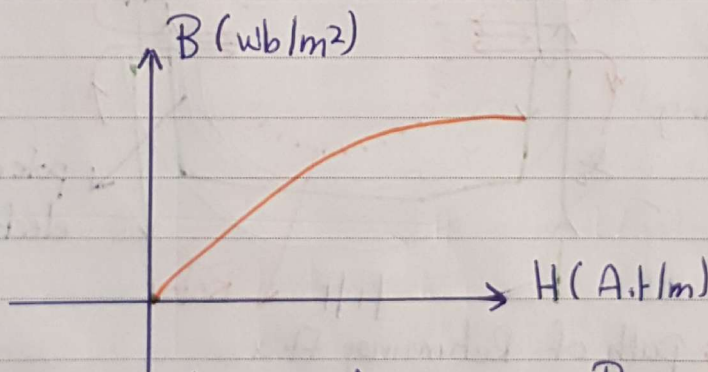Total volume of the material $v \times$ number of cycles



$$A_h = \frac{w}{v} \times \# \text{ of cycles} = \frac{P_h \times \text{time}}{v \times \# \text{ of cycles}}$$

P_h = Power losses (watt)

$$A_h = \frac{P_h}{v \times \frac{\text{number of cycles}}{\text{Time}}} \rightarrow \text{frequency.}$$

* An Empirical formula was found for A_h

$$A_h = k_h B_m^n \quad n = \text{constant} \quad 1.5 \leq n \leq 2.5$$

k_h = An constant its value depends on the type of the material

B_m = Maximum value of flux density.

$$\text{So } P_h = k h B_m^n \cdot V \cdot f$$

P_c : Eddy Current losses

** To reduce the Eddy Current losses we make the coil from laminations (تسليخ) they should be isolated and parallel to the flux.

** i applied generate $\phi \rightarrow \phi \propto i \rightarrow$ Since it's AC ϕ is AC $\rightarrow \phi$ generate voltage (e) in the core, since the core is conducting. generate i_e
 i_e will flow in such direction (according to Lenz's) to generate ϕ_e opposing $\phi \rightarrow i_e$ flow in circular direction so it's called **eddy current** \rightarrow This i_e causes P_c .

$P_c \rightarrow$ reduced by using lamination for the core. (تسليخ)

Since lamination are used then the total volume of the core is going to increase. (تسليخ)

Hence, Stacking factor \triangleq

$$\triangleq \frac{\text{Volume of the ferromagnetic material}}{\text{Total volume of the core}}$$

$$= \frac{\text{Area of the ferro material}}{\text{Total Area of the core}}$$

Expression of P_c

$$P_c \propto i_e^2, \text{ since } i_e \propto e$$

$$\therefore P_c \propto e^2$$

$$\text{since } e \propto B_m f$$

$$\therefore P_c \propto B_m^2 f^2$$

$e \rightarrow$ for voltage

frequency

maximum flux density

Hence P_c can be expressed as:

$$P_e = k_e B_m^2 f^2 TV$$

k_e \equiv Constant depends on the type of ferromagnetic material

T \equiv Lamination Thickness

V \equiv Volume of the ferromaterial.

Core losses, $P_c \Rightarrow$

$$P_c \cong P_e + P_h$$

* **Example:** The total core losses for a given magnetic sheet steel is found to be 1800 W at 60 Hz, when the frequency is increased by 50% the core losses is found to be 3000 W. 96 = 60 + 30

$$P_c = P_e + P_h \quad \begin{array}{l} \nearrow \text{constant } k_b \\ \searrow \text{constant } k_a \end{array}$$

$$= k_e f^2 B_m^2 TV + k_h B_m^n f$$

for the same flux density B_m

$$P_c = k_b f^2 + k_a f$$


$$\therefore 1800 = k_b 60^2 + k_a 60 \quad \dots \textcircled{1}$$

$$3000 = k_b 90^2 + k_a 90 \quad \dots \textcircled{2}$$

Solving $\textcircled{1}$ and $\textcircled{2}$ it can be found:



$$k_b = \frac{1}{9}$$

f	P_e	P_h
60	$\frac{1}{9} \times 3600 = 400$	$1800 - 400 = 1400$
90	$\frac{1}{9} \times 90 \times 90 = 900$	$3000 - 900 = 2100$

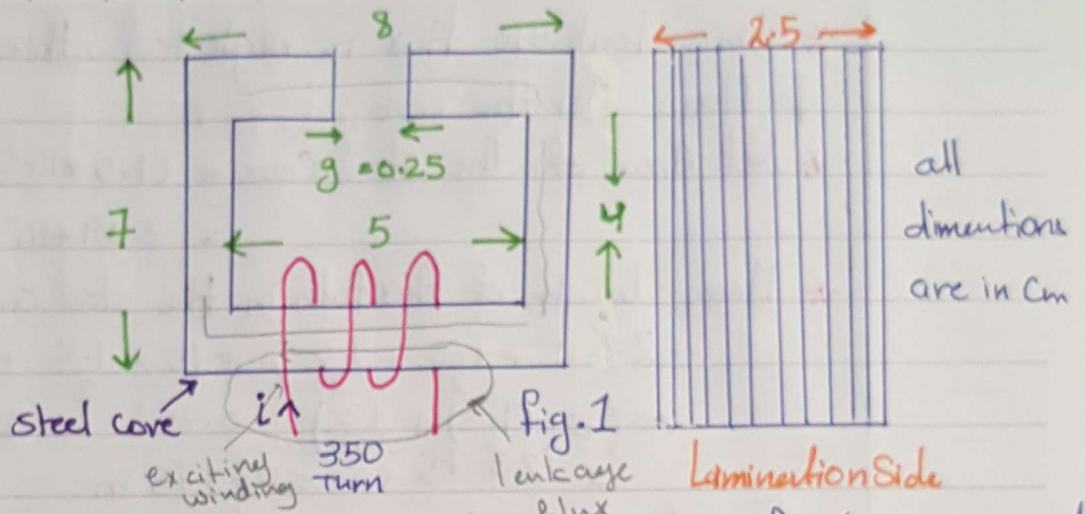

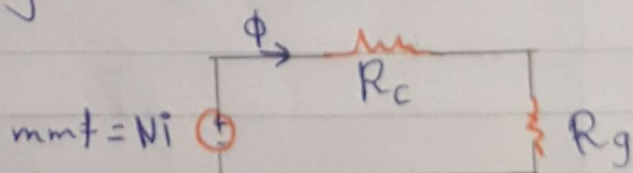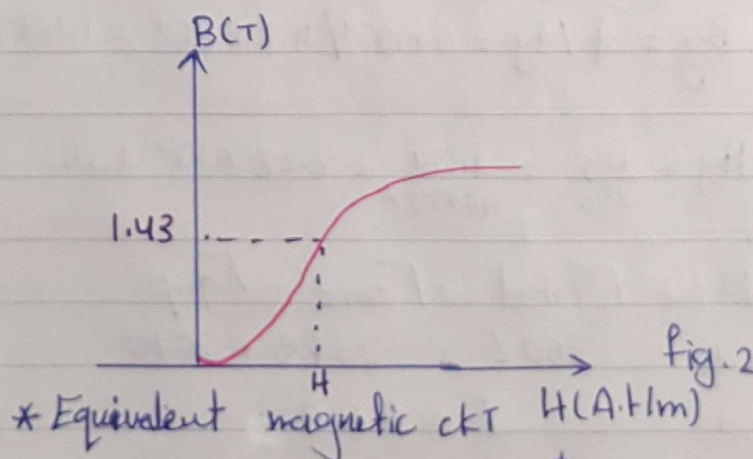Example: The magnetic ckt shown in fig. 1 is composed of a laminated core of steel with air gap g and has an exciting winding of 350 turns. The magnetization curve of steel is shown in fig. 2. The presence of laminations is taken into account by assuming stacking factor 0.93.

Neglect leakage flux, but take in to account fringing and calculate the required exciting current to produce a flux of 5×10^{-4} wb in the core.



* Equivalent magnetic ckt

Fig. 2

* Since leakage flux is neglected, then all the flux ϕ flows in the core.

$$\begin{aligned} \text{* Net Area of the steel Core} &= (1.5 \times 10^{-2} \times 2.5 \times 10^{-2} \times 0.93) \\ &= 3.49 \times 10^{-4} \text{ m}^2 \end{aligned}$$

$$\begin{aligned} \text{* Mean length of flux path in the steel core} &= \\ &= 2 \left(4 + \frac{1.5}{2} + \frac{1.5}{2} \right) + \left(5 + \frac{1.5}{2} + \frac{1.5}{2} \right) \\ &+ \left(5 + \frac{1.5}{2} + \frac{1.5}{2} - 0.25 \right) \\ &= 23.75 \text{ cm} = 0.2375 \text{ m} \end{aligned}$$

$$\text{* Flux density in the core} = \frac{\phi}{A_c} = \frac{5 \times 10^{-4}}{3.49 \times 10^{-4}} = 1.43 \text{ T}$$

By using Fig. 2: it can be found that for $B = 1.43$
 $H_{\text{core}} = 10^3$

* Correction for air gap, add g to the side of the gap

$$\begin{aligned} A_g &= (1.5 + 2.5) (2.5 + 0.25) \times 10^{-4} \\ &= 4.81 \times 10^{-4} \text{ m}^2 \end{aligned}$$

$$\therefore B_g = \phi / A_g = 5 \times 10^{-4} / 4.8 \times 10^{-4} = 1.04 \text{ T}$$

$$H_g = \frac{B_g}{\mu_0} = \frac{1.04}{4\pi \times 10^{-7}} = 8.28 \times 10^5 \text{ A.t/m}$$

$$\begin{aligned} \text{By KVL: } \Gamma_{\text{total}} &= \Gamma_{\text{core}} + \Gamma_{\text{gap}} \\ 350 i &= 237.5 + 2070 \\ i &= 6.6 \text{ A} \end{aligned}$$

Inductance L :

Flux linkage, $\lambda \cong N\phi$

$$\lambda \cong Li$$

$$L = \frac{N\phi}{i}$$

Since $Ni = R\phi$

$$\therefore L = \frac{N\phi}{\frac{R\phi}{N}} = \frac{N^2}{R} = \frac{N^2 \mu A}{l}$$

the end of the
concept of magnetic
ckts.

Chapter (2) :-

Transformer :

what? Definition it's a device or Equipment which can be used to change the level or magnitude of Ac voltage

why? It is used in the process of electrical energy transfer by ¹stepping up the voltage and ²reducing the current

↳ Consequently

* Hence power losses will be decreased

How? Analysis


* Construction ^{البناء} → ^{التركيب}

Transformer consist of a core with two or more windings _{cks}

* Classification ^{التصنيف}

- According to their application they can be classified into :-

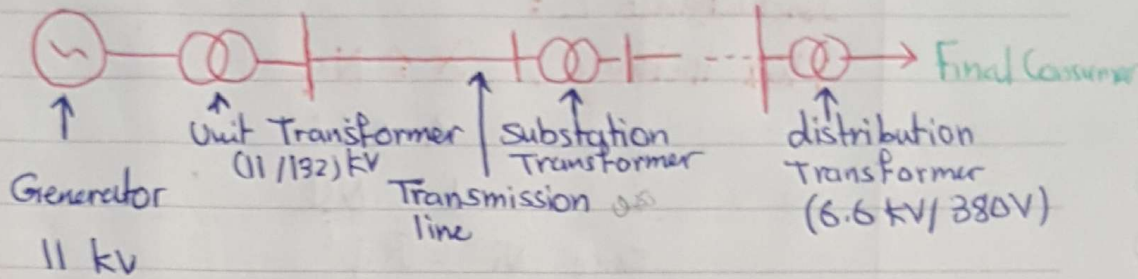□ **Power Transformer** : This is the one used in the process of Generator Transmission and distribution of electrical energy.



[2] Instrument Transformer: These are the ones which are used in the process of electrical measurement of voltage and current:

- A. Potential Transformer PT
- B. Current Transformer CT

This course concerned with **Power Transformer:**

Single Phase Transformer

Objective: To find Voltage, Current and power relationship

$N_s, N_p \equiv$ Primary and Secondary turns.



i_p : applied primary current

V : Applied primary voltage

e_p, e_s : Primary, Secondary

Included voltage.

Primary coil or winding

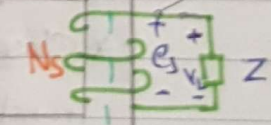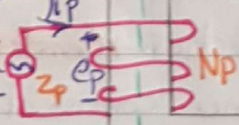

Core

Secondary winding

V_L : Load voltage

** Assume **Ideal Transformer**

Assumption

- 1 No Losses (electrical and core)
- 2 $\mu_r \rightarrow \infty$
- 3 No Leakage flux (ie. all generated flux flow in the core)

تسرب

3. No.

$$e_p = N_p \frac{d\phi}{dt} \quad e = N \frac{d\phi}{dt}$$
$$e_s = N_s \frac{d\phi}{dt}$$

$$\frac{e_p}{e_s} = \frac{N_p}{N_s} = a = \text{turns ratio}$$

$$i_p N_p = i_s N_s$$

$$\therefore \frac{i_p}{i_s} = \frac{N_s}{N_p} = \frac{1}{a}$$

V_s : Secondary terminal voltage

Since a is a real number then e_p and e_s are in phase

Also i_p and i_s are in phase

* for Ideal Transformer

$$e_p = V_p \quad \text{and} \quad V_s = e_s$$

* The voltage and the current relationships can be written in phasor form:

$$\frac{V_p}{V_s} = \frac{I_s}{I_p} = a$$

$$\therefore V_p I_p = V_s I_s$$

\therefore Apparent power of primary and secondary is the same (KVL)

Power:

$$P_{\text{supplied by primary}} = P_p = V_p I_p \cos \theta_p$$

$$P_{\text{taken by the secondary}} = P_s = V_s I_s \cos \theta_s \quad \rightarrow \text{phase shift}$$

* for ideal transformer $\rightarrow \theta_p = \theta_s = \theta$

$$\therefore P_p = (a V_s) * \left(\frac{I_s}{a}\right) * \cos \theta = V_s I_s \cos \theta = P_s$$

$$\therefore \eta \text{ of Transformer} = 100\%$$

$$\text{efficiency } \eta = \frac{P_{\text{out}}}{P_{\text{in}}} = \frac{P_{\text{out}}}{P_{\text{out}} + P_{\text{losses}}}$$

Impedance


$$Z = \frac{V}{I} \text{ for Transformer}$$

$$\rightarrow Z_p = \frac{V_p}{I_p} = \frac{a V_s}{\frac{I_s}{a}} = a^2 \frac{V_s}{I_s} = a^2 Z_s$$

$$\text{OR } Z_s = \frac{Z_p}{a^2}$$

turns
ratio

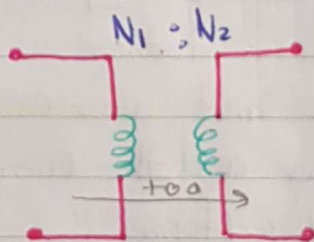- ∴ To Reflect Z_s to primary * by a^2
- ∴ To Reflect Z_p to secondary ÷ by a^2



$$1 : \frac{N_2}{N_1} = a_1 \quad \text{OR} \quad \frac{N_1}{N_2} = 1 = a_2$$


In general To reflect an impedance Z to the a side, multiply Z by a^2

To reflect an impedance Z to 1 side ÷ Z by a^2

* Real Transformer: (Practical)

Here:

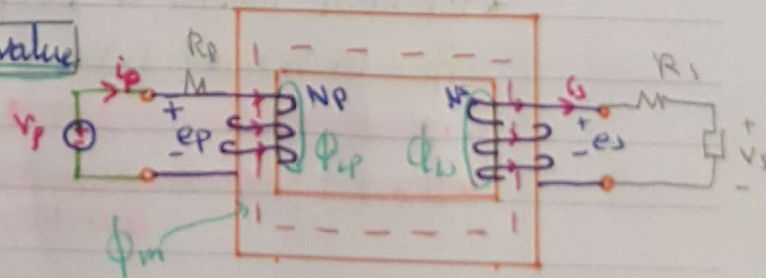- 1) losses will be taken into account
- 2) leakage flux
- 3) k_r has a high value



ϕ_m = Mutual flux

ϕ_{lp} = leakage flux of primary

ϕ_{ls} = Leakage flux of Secondary

$$\phi_p = \phi_m + \phi_{lp}$$

$$e_p = e_{mp} + e_{lp}$$

$$\phi_s = \phi_m + \phi_{ls}$$

$$e_s = e_{ms} + e_{ls}$$

$$\therefore e_p = N_p \frac{d\phi_p}{dt} = N_p \frac{d\phi_m}{dt} + N_p \frac{d\phi_{lp}}{dt}$$

$$e_s = N_s \frac{d\phi_s}{dt} = N_s \frac{d\phi_m}{dt} + N_s \frac{d\phi_{ls}}{dt}$$

$$\therefore \frac{e_{mp}}{e_{ms}} = \frac{N_p}{N_s}$$

For Practical iron Core transformer $\phi_m \gg \phi_l$

$$\therefore \phi_m \approx \phi$$


$$\therefore \frac{e_p}{e_s} = \frac{N_p}{N_s}$$

* If the resistance of the winding is reflected then:

$$V_p \approx e_p$$

$$V_s \approx e_s$$

* Current Relationship Equivalent CKT

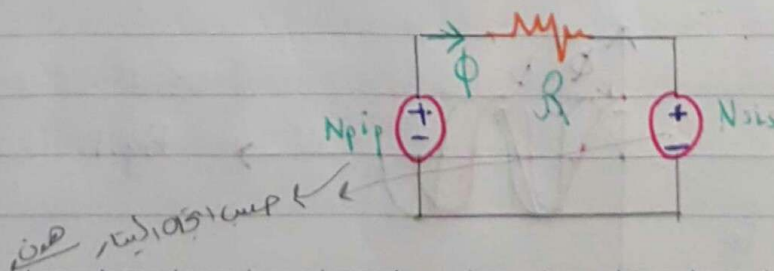

No.

Flux مقدار ال
في الحدة الكهرومغناطيسية

دائما ثابت (بزيادته Current وبتغيره voltage) كما يوضح ϕ للمغناطيسية (المغناطيسية)

∴ By KVL $\rightarrow N_p i_p - N_s i_s = R \phi$


Since R is very small $\therefore R \approx 0$

$$N_p i_p = N_s i_s$$

$$\therefore \frac{i_p}{i_s} = \frac{N_s}{N_p}$$

Excitation Current:

This is the primary current at no-load

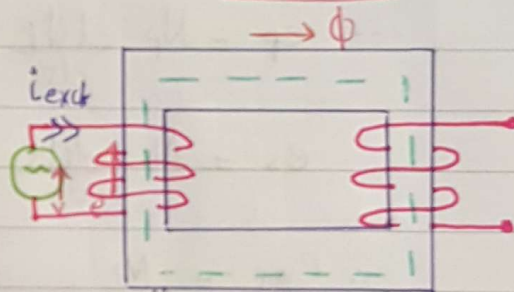

i_{ext} has 2 functions or 2 components:-

i) to supply the magnetizing current (i_m) for flux generation

ii) to account for the core losses (i_c)


*objective To find by qualitative means the shape of i_{ext}

Since $v = N \frac{d\phi}{dt}$

$$\therefore \phi = \frac{1}{N} \int v dt$$

if $v = \sqrt{V_m} \cos \omega t$
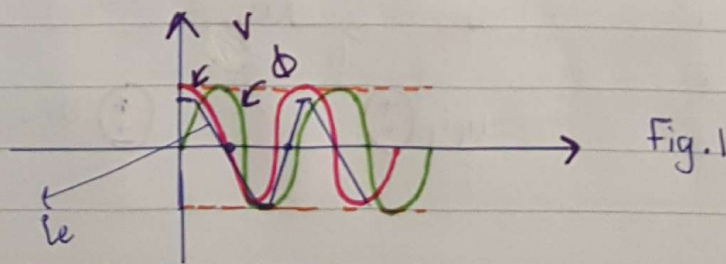
$$\therefore \phi = \phi_m \sin \omega t$$



i_m

If the magnetization curve of the core is given,


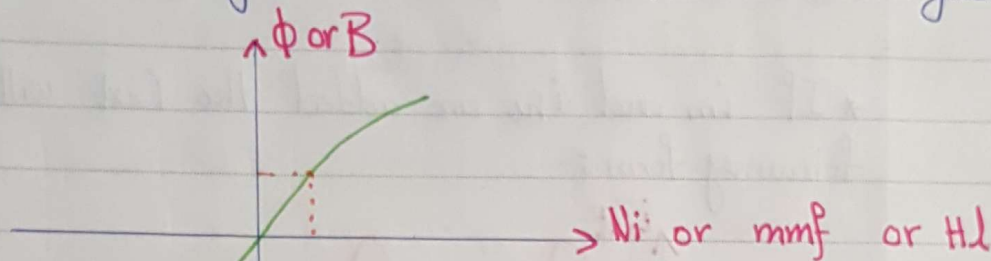


Fig. 2

* For each value of ϕ in Fig. 1, then by projecting it in Fig. 2, the corresponding value for i_m can be found.

* The shape of i_m will be as follows:-

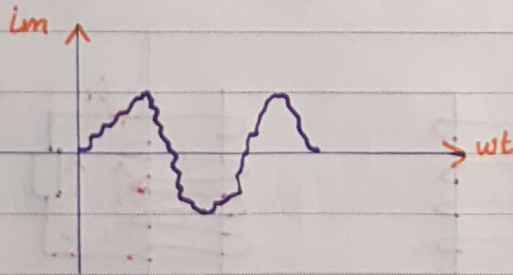

$\therefore i_m$ is a distorted sinusoidal, and by using Fourier Series it can be analysed into fundamental + Harmonics

 i_c


$$i_c = i_e + i_h \equiv i_{he}$$

$$i_e \propto e \propto \frac{d\phi}{dt}$$


$\therefore i_e$ is non sinusoidal, but it is periodic by Fourier Series

it can be decomposed into Fundamental + harmonic
 [it is non linear function of voltage]

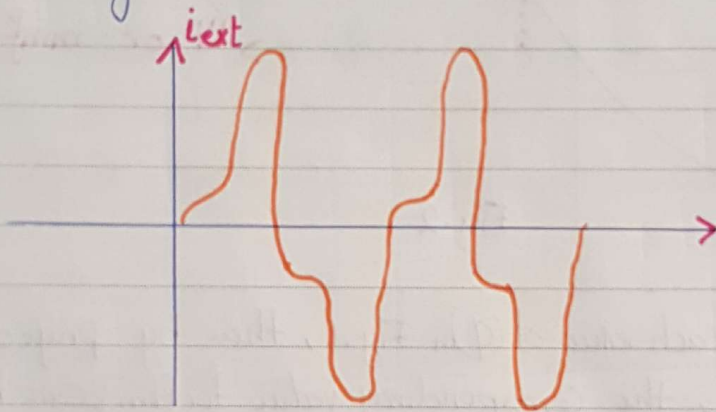* If i_m and i_{he} are added the i_{ext} will have the following form :-



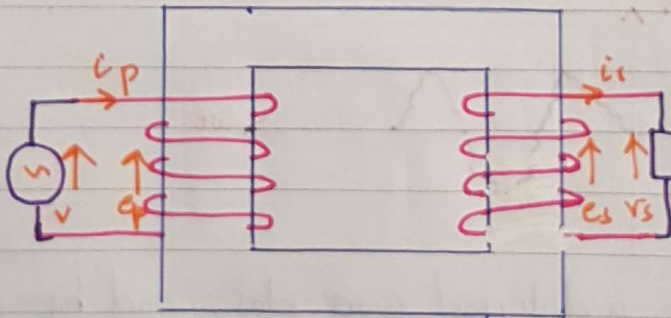* Equivalent Circuit of Real Transformer :- (model)



The Equivalent circuit model should take into account the following :

□ Copper losses in the primary and secondary windings (i.e. heating losses)

The losses are represented by resistance in the primary and secondary circuits (i.e. R_p and R_s)

2] leakage flux in the primary and secondary windings (ϕ_{lp} and ϕ_{ls})

$$e_{lp} = N_p \frac{d\phi_{lp}}{dt}$$

$$e_{ls} = N_s \frac{d\phi_{ls}}{dt}$$

$$= N_p \frac{d}{dt} \left(\frac{N_p i_p}{\mathcal{R}} \right)$$

$$= N_s \frac{d}{dt} \left(\frac{N_s i_s}{\mathcal{R}} \right)$$

self inductance $L_p = \frac{N_p^2}{\mathcal{R}} \frac{di_p}{dt}$

$L_s = \frac{N_s^2}{\mathcal{R}} \frac{di_s}{dt}$


** leakage flux in the primary and secondary windings (ϕ_{lp} and ϕ_{ls}) are represented by self inductance in the primary and secondary circuits (L_p and L_s)

3] iext : 1. i_m
 Represented by a reactance X_m
 generate ϕ
 Because i_m lags applied voltage by 90°

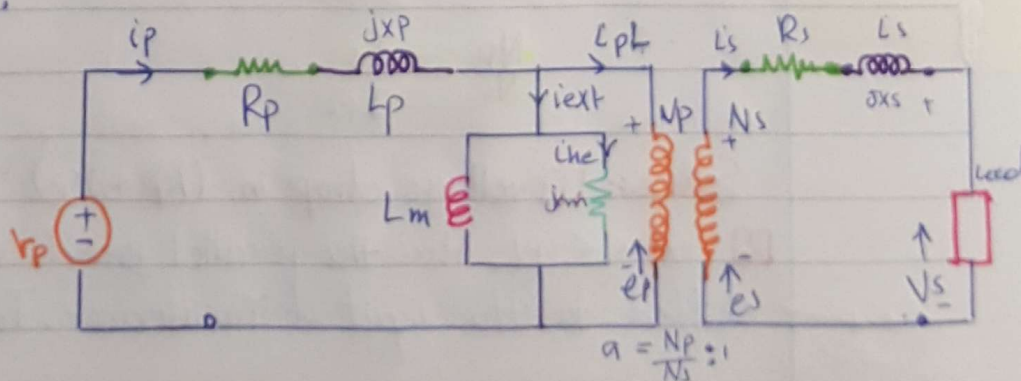2. i_{htc}


\rightarrow this Represented by a resistance R_c

* Consequently the equivalent circuit can be deduced as follows:




- $i_p \equiv$ Total Primary Current
- $i_{ext} \equiv$ No-load Component of i_p
- $i_{pl} \equiv$ Load component of i_p

Reflect $s \rightarrow P$

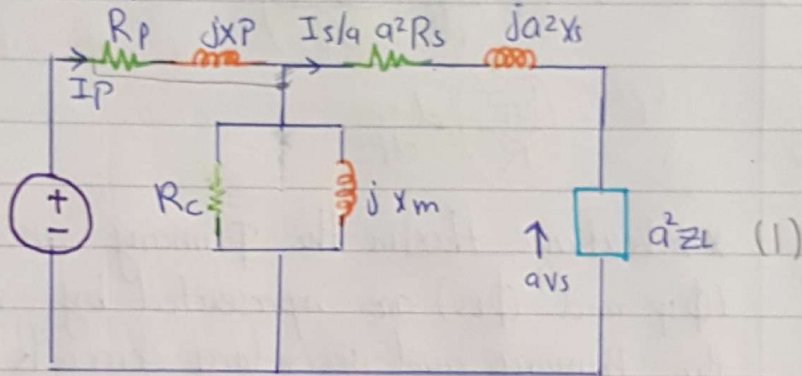

Reflect $P \rightarrow s$

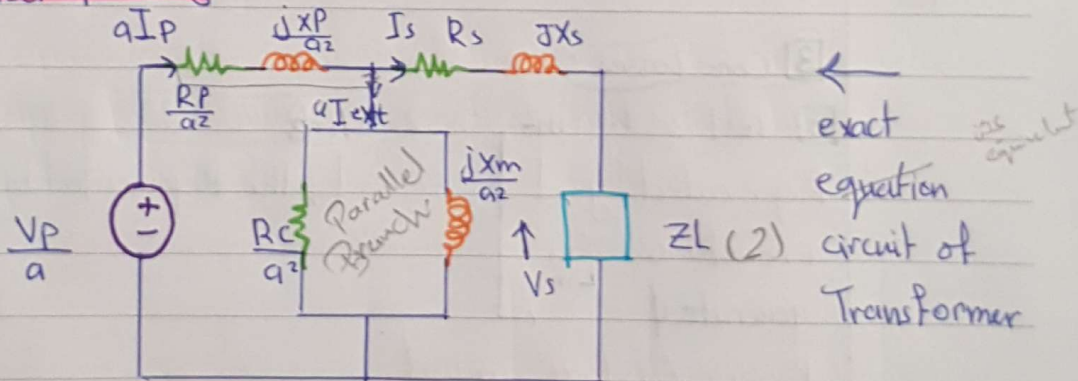

$$\therefore a I_{pl} = I_s$$

$$a = \frac{I_s}{I_{pl}}$$

$$\frac{N_p}{N_s} = \frac{I_s}{I_{pl}}$$

Since:- \square voltage drop in $(R_p + jX_p)$ is very small and \square $i_{ext} \ll i_{pl}$ then the parallel branch of $(R_c \parallel X_m)$ can be shifted to the input of Transformer, To produce an approximate

equivalent circuit.


$$R_{eqp} = R_p + a^2 R_s$$

$$X_{eqp} = X_p + a^2 X_s$$

$$R_{eqs} = \frac{R_p}{a^2} + R_s$$

$$X_{eqs} = \frac{X_p}{a^2} + X_s$$

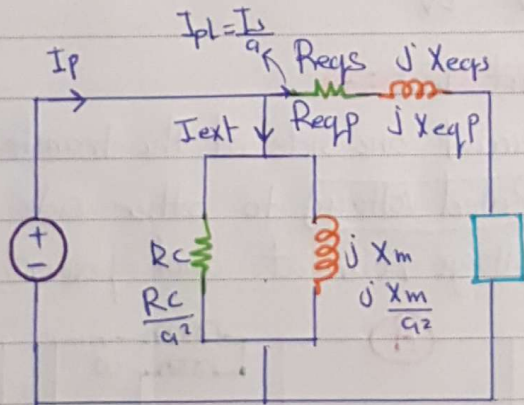
X_{eqp}, R_{eqp} = Called the equivalent Series Resistance and Reactance of the transformer.



Since: $I_{ext} \ll I_p$

Then parallel branch from current voltage relationship can be neglected.


∴ equivalent circuit will be :-

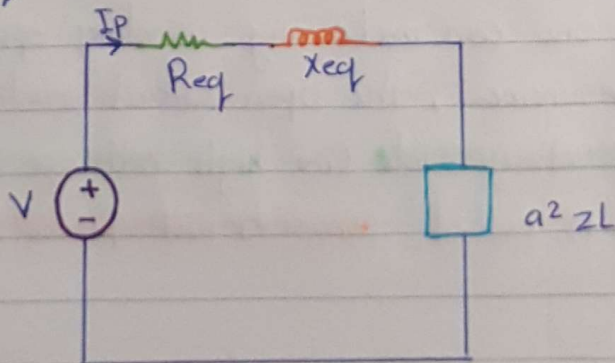

Measurement of Transformer Parameters (R_c , X_m , R_{eq} and X_{eq})

Why?! These parameter are used in the performance analysis of Transformer as will be shown later

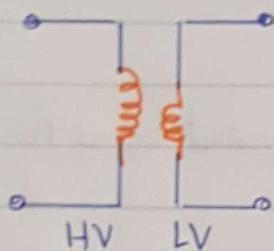
How?! Procedure By performing open circuit and short circuit as follows.



high and low voltage

Open circuit Test :-

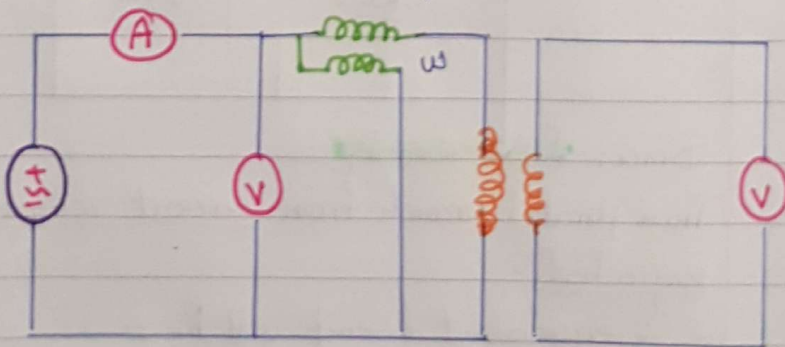- 1] open circuit one side of the transformer (i.e. LV or HV)
- 2] Apply Rated voltage to other side and take the readings of input voltage, current and power.




Although one can make any winding open circuit, but for easy measurement, the open circuit readings are taken on the low voltage side (i.e. high voltage is open circuit)

→ This is called conventional procedure

By using the equivalent circuit :-

Since I_{oc} is very small, then drop in R_p and X_p is very small

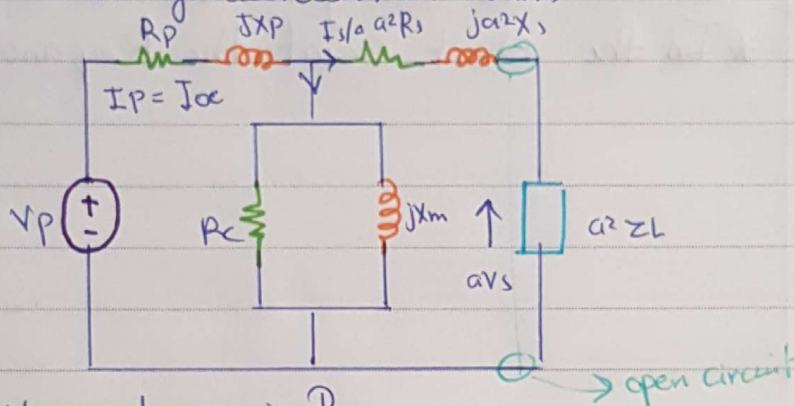$\therefore V_{oc} =$ Voltage across ($R_m // X_m$)



$\therefore W_{oc} =$ Losses in R_c

\therefore In the open circuit test one can determine X_m and R_c
As follows:-

$$W_{oc} = I_{oc}^2 R_c$$

$$\therefore R_c = \frac{W_{oc}}{I_{oc}^2} = \frac{W. \text{ Reading}}{(A. \text{ Reading})^2}$$

$$Y = \frac{1}{R_c} + \frac{1}{jX_m}$$

$$\text{But } |Y| = \frac{I_{oc}}{V_{oc}} = \sqrt{\left(\frac{1}{R_c}\right)^2 + \left(\frac{1}{X_m}\right)^2}$$

$$\therefore \frac{1}{X_m} = \sqrt{\left(\frac{1}{R_c}\right)^2 + \frac{1}{Y^2}} = \sqrt{\left|\frac{1}{Y}\right|^2 - \left(\frac{1}{R_c}\right)^2}$$

Short Circuit Test:


- 1] short circuit one side of the transformer
- 2] Apply Rated Current to the other side.

Since:- High voltage has a lower rated current.

Then as the convention, the readings are taken on the high voltage side.

Then take the readings of V, A and W.

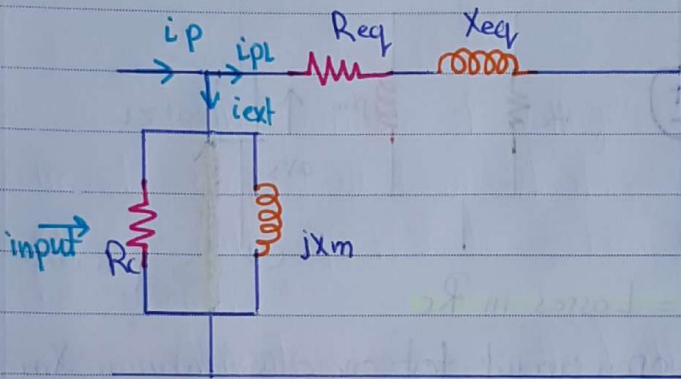* In the short circuit the R_{eq} and X_{eq} are measured.



Since $i_{pL} \gg i_{ext}$

$$i_p = i_{pL}$$

$$\therefore P_{sc} = I_{sc}^2 R_{eq}$$

$$\therefore R_{eq} = \frac{P_{sc}}{I_{sc}^2}$$

$$\therefore X_{eq} = \sqrt{Z_{eq}^2 - R_{eq}^2}$$

$$Z_{eq} = R_{eq} + jX_{eq}$$

$$|Z_{eq}| = \sqrt{R_{eq}^2 + X_{eq}^2}$$

$$|Z_{eq}| = \frac{V_{sc}}{I_{sc}}$$

* Example:- 1380 VA, (230/115) V transformer has been tested to determine its equivalent circuit. The results were as follows:-

O/C

$$V = 230 \text{ V}$$

$$I = 0.45 \text{ A}$$

$$P = 30 \text{ W}$$

S/C

$$V = 13.2 \text{ V}$$

$$I = 6 \text{ A}$$

$$P = 20.1 \text{ W}$$

* Find the equivalent circuit referred to Low volt side:-

Since open circuit Rated voltage applied.

Then in this example measurement were taken on the high voltage side

$$P_{oc} = \frac{V_{oc}^2}{R_c} \therefore R_c = \frac{V_{oc}^2}{P_{oc}} = \frac{(230)^2}{30} = 1763.3 \Omega$$

$$M = \frac{I_{oc}}{V_{oc}} = \frac{0.45}{230} = 0.001957$$

$$M = \sqrt{\left(\frac{1}{R_c}\right)^2 + \left(\frac{1}{X_m}\right)^2} \quad \text{By substitution} \quad X_m = 533.9 \Omega$$

Short Circuit Test Rated current is applied

$$I_{LV} = \frac{1380}{115} = 12 \text{ A}$$

$$I_{HV} = \frac{1380}{230} = 6 \text{ A}$$

\therefore Readings are taken on the high voltage side

$$P_{sc} = I_{sc}^2 R_{eq}$$

$$\therefore R_{eq} = \frac{20.1}{6^2} = 0.558$$


$$|Z_{eq}| = \frac{V_{sc}}{I_{sc}}$$

$$= 13.2 / 6$$


$$= 2.2$$

$$\therefore Z_{eq} = \sqrt{|Z_{eq}|^2 - |R_{eq}|^2} = 2.128 \Omega$$

Refer all parameters to LV side

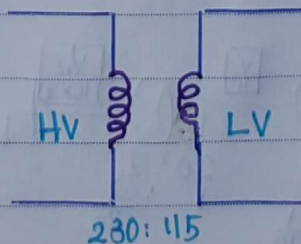

$$a = \frac{230}{115} = 2$$

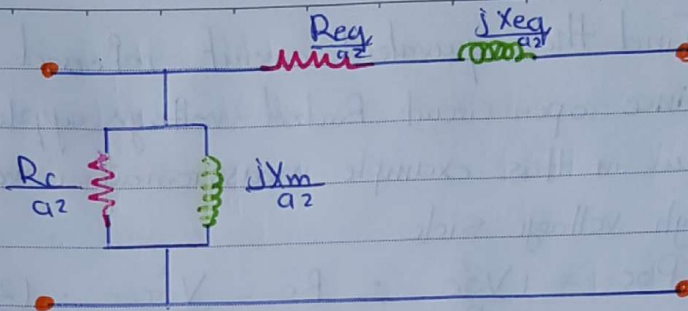

Per-Unit System (PU)

What?! The variables of voltage, Current, Power and Impedance are not expressed in terms of its SI Unit. However they are expressed with respect to certain Reference values as will be shown

Why?! Advantages → see the textbook or any other reference.

Quantity in PU \triangleq $\frac{\text{Actual value}}{\text{Base or Reference value}}$ → could be real or complex
 ↳ This is always a real value


∴ PU value and actual value have the same phase angle

Since there are 4 variables V, I, S, Z , any two are selected to be the Base values (usually the Base values of V and S are selected V_b and S_b)

And the base values of the other two are calculated from the selected ones as follows:-

$$S_b = V_b I_b \quad \therefore I_b = \frac{S_b}{V_b}$$
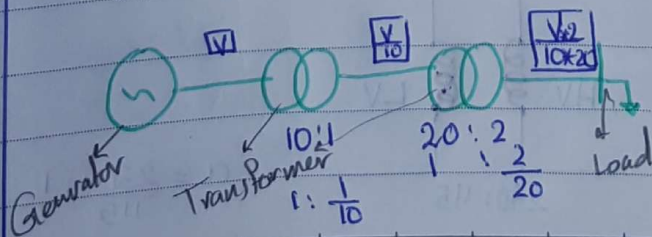
$$Z_b = \frac{V_b}{I_b} = \frac{V_b}{S_b/V_b} = \frac{V_b^2}{S_b}$$




* Since S for the high voltage and low voltage does not change, the S_b remain the same for the system. However the Base value of voltage change according to transformer Ratio.

Procedure

- 1] Select S_b, V_b for the system
- 2] Identify V_b by using transformer ratio for each section
- 3] Find Z_b for each section
- 4] evaluate PU system

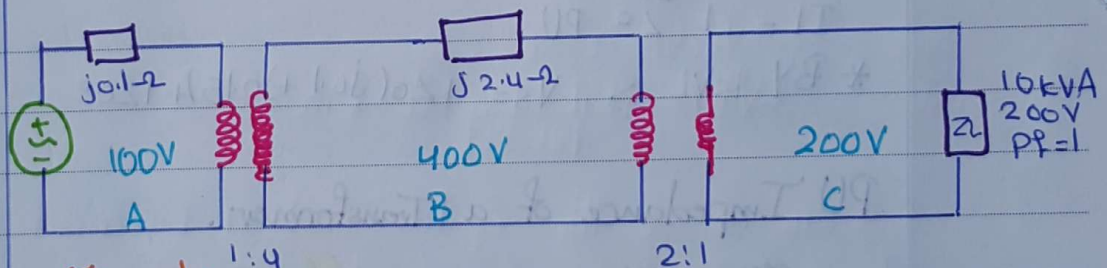* As a convention usually the Rating of the largest component are selected to be base value



→ Example:-

Find the PU equivalent system

$$\text{let } S_b = 10 \text{ kVA}$$

$$\text{let } V_b = 200 \text{ V}$$

$$Z_b \triangleq V_b^2 / S_b$$

$$Z_{bA} = \frac{(100)^2}{10 \times 10^3} = 1 \Omega$$

$$Z_{bB} = \frac{(400)^2}{10 \times 10^3} = 16 \Omega$$

$$Z_{bC} = \frac{(200)^2}{10 \times 10^3} = 4 \Omega$$


$$Z_{PUA} = j0.1 = j0.1$$

$$Z_{PUB} = j0.15 = j0.15$$

$$Z_{PUC} = \frac{16}{4} = \frac{4}{4} = 1$$

$$|Z_L| = \frac{V^2}{S} = \frac{(200)^2}{10 \times 10^3} = 4$$
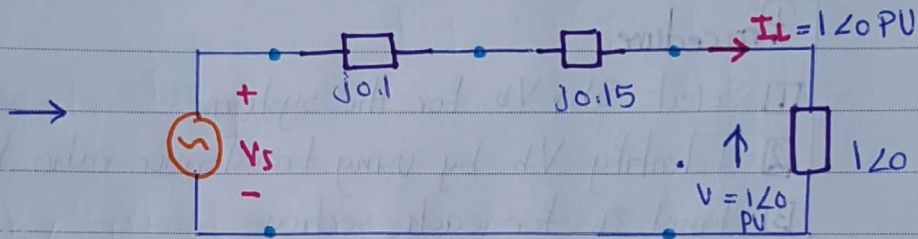
$$\therefore Z_L = 1 \angle 0^\circ \text{ PU}$$



$$Z_L \rightarrow |I_L| = \frac{10 \times 10^3}{200} = \frac{10^4}{200} \text{ A}$$


$$I_b = \frac{S_b}{V_b} = \frac{10^4}{200} \text{ A}$$

$$|I_L, \text{ PU}| = \frac{I_L}{I_b} = 1$$

$$I_L = 1 \angle 0^\circ \text{ PU}$$

* BY KVL $\rightarrow V_s = 1 \angle 0^\circ (j0.1 + j0.15) + 1 \angle 0^\circ$

PU Impedance of a Transformer.

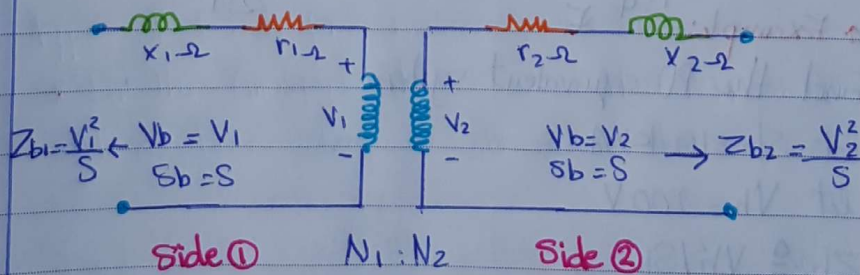

$$a = \frac{N_1}{N_2}$$

Reflect Side 1 \rightarrow Side 2

$$\therefore R_{eq 2} = r_2 + \frac{r_1}{a^2}$$

$$X_{eq 2} = X_2 + \frac{X_1}{a^2}$$

$$Req_2 (PU) = \frac{Req_2}{Z_{b2}}$$

$$Req_2 (PU) = \frac{S}{V_2^2} (r_2 + \frac{r_1}{a^2})$$

$$\text{But } \frac{V_1}{V_2} = \frac{N_1}{N_2} = a$$

$$\therefore V_2 = \frac{V_1}{a}$$

$$\therefore Req_2 (PU) = \frac{S a^2}{V_1^2} (r_2 + \frac{r_1}{a^2})$$

$$Req_2 (PU) = \frac{S^2 V_1^2}{V_1^2} (r_2 a^2 + r_1) \dots 1$$

→ Similarly

$$Xeq_2 (PU) = \frac{S}{V_1^2} (a^2 X_2 + X_1) \dots 2$$

Reflect Side 2 → Side 1

$$\therefore Req_1 = r_1 + a^2 r_2$$

$$Xeq_1 = X_1 + a^2 X_2$$


$$\therefore Req_1 (PU) = \frac{Req_1}{Z_{b1}} = \frac{S}{V_1^2} (r_1 + a^2 r_2) \dots 3$$

→ Similarly

$$Xeq_1 (PU) = \frac{S}{V_1^2} (X_1 + a^2 X_2) \dots 4$$


Hence it can be observed that 1 = 3 2 = 4

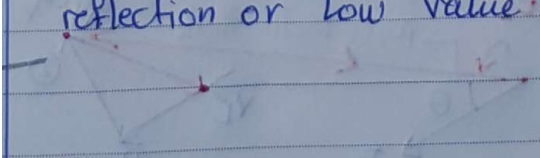∴ PU Req and Xeq are the same for high value reflection or low value reflection.



Voltage Regulation VR

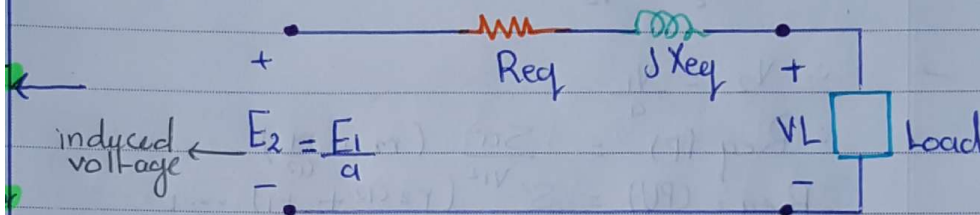* This measures the difference between input and output voltage at a given load. and defined as follows by using the equivalent circuit



$$VR\% \triangleq \frac{|V_{L,NL}| - |V_{L,FL}|}{|V_{L,FL}|} \times 100\%$$

NL = No Load

FL = Full Load

$$\frac{E_1}{E_2} = \frac{N_1}{N_2} = a$$

$$E_2 = I_L (R_{eq} + jX_{eq}) + V_L$$

Z_{eq}

$$\therefore E_2 = \frac{E_1}{a}$$

$$\therefore V_{L,NL} = E_2 = \frac{E_1}{a}$$

$$\therefore VR\% = \frac{|E_1| - |V_{L,FL}|}{|V_{L,FL}|} \times 100\%$$

* One can see the significance of VR by considering various types of loads (i.e. Inductive, Resistive and capacitive)


* In the Analysis, it's assumed that $|V_L|$ and $|I_L|$ are fixed.

* Here phasor diagram will be used.


Inductive

1: $I_L R_{eq}$

2: $I_L X_{eq}$

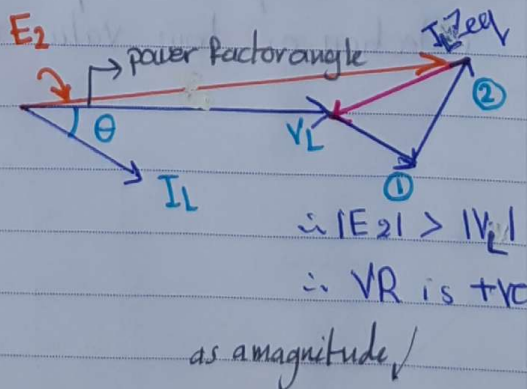


Resistive

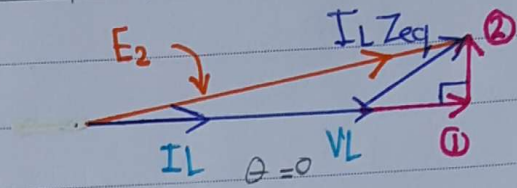

V_R is +ve


$|E_2|_{\text{Resistive}} < |E_2|_{\text{inductive}}$

Capacitive

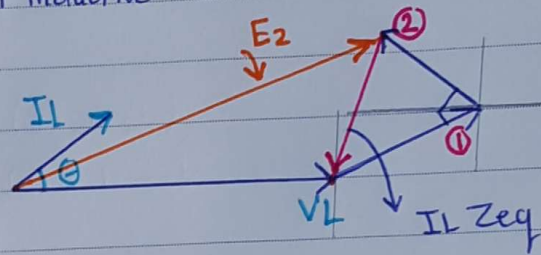

$|E_2| < |V_L|$

$\therefore V_R$ is -ve

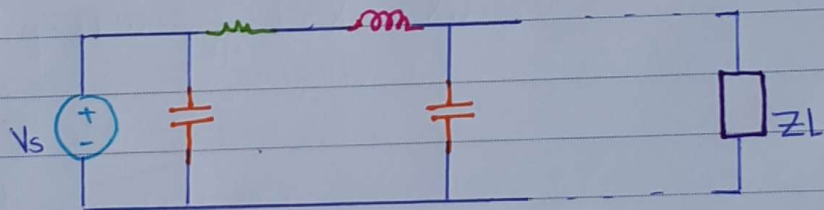

π -equivalent circuit

Efficiency η

$$\eta \triangleq \frac{\text{output}}{\text{input}} = \frac{\text{output}}{\text{output} + \text{Losses}}$$

$$\text{output} = |V_L| |I_L| \cos \theta \text{ watt}$$

$\theta \equiv$ PF angle of the load

losses \equiv electrical or Copper losses + Core losses

$$\downarrow I_L^2 R_{eq}$$

$$P_e \quad P_h$$


are evaluated from O/C test

Example: A 10 kVA (4800/240)V transformer was tested by o/c and s/c Test, and the results were as follows:-

o/c: 240V 1.5A 60W ← LV (Readings)

s/c: 180V 2.083A 180W ← HV (Readings)

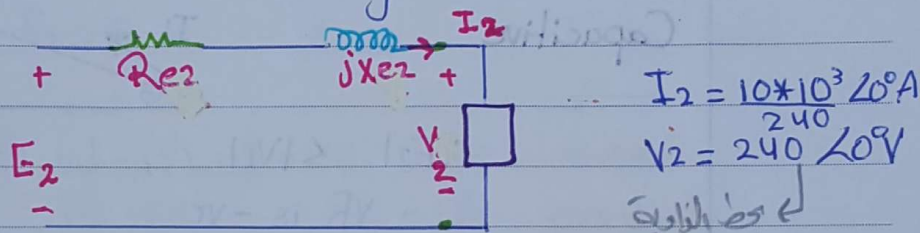1 Evaluate VR of the stepdown transformer at unity PF with full-load. ∴ secondary is LV.



From the given data it can be found

$$R_{e2} = 0.104 \Omega$$

$$X_{e2} = 0.19 \Omega$$

$$VR = \frac{|E_2| - |V_2|}{|V_2|}$$

$$E_2 = I_2(R_{e2} + jX_{e2}) + V_2 = (244.167 + j7.92) V$$

$$\therefore VR = \frac{244.3 - 240}{240} \times 100\% = 1.79\%$$

$$|E_2| = 244.3 V$$

2 Evaluate η of the step down transformer at full-load at 0.9 PF Lagging.

$$\eta = \frac{V_2 I_2 \cos \theta}{V_2 I_2 \cos \theta + \text{electrical losses} + \text{core losses}}$$

$$V_2 = 240 V$$

$$I_2 = 41.67 A$$

$$\cos \theta = 0.9$$

No. _____

electrical losses : $I_2^2 R_{e2}$
↳ OR from short circuit data = 180 w
Core losses → from open circuit Test.


$$\eta = \frac{[240 \times 41.67 \times 0.9]}{() + 180 + 60} \times 100\% = 97.4\%$$

* Autotransformer :-

* This type is used when the required change in voltage is very small. example $110 \rightarrow 120$

$13.2 \rightarrow 13.8$ KV

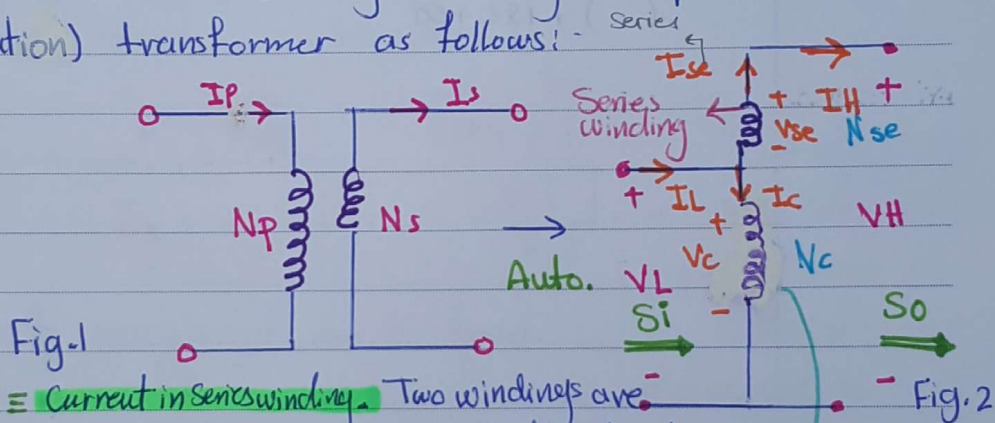* This is introduced by considering the previous conventional (isolation) transformer as follows:-



$I_{se} \equiv$ Current in series winding. Two windings are

$I_c \equiv$ Current in common winding. connected electrically

$V_C \equiv$ Voltage in common winding.

$V_{se} \equiv$ Voltage in series winding.

common winding: because it is common between HV and LV sides

* Voltage and current in the windings are related by turns Ratio as follows:-

$$\frac{V_C}{V_{se}} = \frac{N_c}{N_{se}} \quad \dots 1$$

$$I_c N_c = I_{se} N_{se}$$

$$\frac{I_c}{I_{se}} = \frac{N_{se}}{N_c} \quad \dots 2$$

* Voltage and Current Relationship :-

objective: To find $\frac{V_H}{V_L}$ and $\frac{I_H}{I_L}$

No. _____

Procedure :-

From fig. 2

$$V_H = V_C + V_{se} \quad \dots 3$$

$$\begin{aligned} &= V_C + V_C \frac{N_{se}}{N_C} \quad \text{by sub. (1) in (3)} \\ &= V_C \left(\frac{N_C + N_{se}}{N_C} \right) = V_L \left(\frac{N_C + N_{se}}{N_C} \right) \end{aligned}$$

$$\therefore \frac{V_H}{V_L} = \frac{N_C + N_{se}}{N_C} \quad \dots 5$$

From Fig. 2

$$I_L = I_C + I_{se} \quad \dots 4$$

Substitute (2) in (4)

$$\begin{aligned} I_L &= I_{se} \frac{N_{se}}{N_C} + I_{se} \\ &= I_{se} \left(\frac{N_C + N_{se}}{N_C} \right) \end{aligned}$$

$$\therefore \frac{I_L}{I_H} = \frac{N_{se} + N_C}{N_C} \quad \dots 6$$

* Apparent power Relationship :-

$S_i \equiv$ input apparent power

$S_o \equiv$ output apparent power


$$S_i = V_L I_L \quad \dots 7$$

$$S_o = V_H I_H \quad \dots 8$$

Find relation between S_i and S_o

Substitute (5) and (6) in (7)
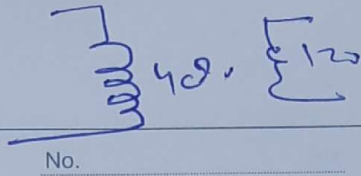
$$S_i = V_L \left(\frac{N_C}{N_C + N_{se}} \right) * \left(\frac{N_C + N_{se}}{N_C} \right) * I_H$$



No.

$$S_i = V_H I_H$$


$$\therefore S_i = S_o = S_{io}$$

$$I_L = I_c + I_{se}$$

$$\therefore I_c = I_L - I_{se}$$

* Apparent Power advantage of Autotransformer:-

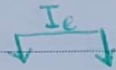Apparent power of the winding, $S_w = V_c I_c$ OR $S_w = V_{se} I_{se}$



$$\therefore S_w = V_L (I_L - I_{se})$$

$$= V_L (I_L - I_H)$$


$$= V_L \left(I_L - I_L \frac{N_c}{N_s + N_c} \right) = \frac{V_L I_L}{S_{io}} \left(\frac{N_s}{N_c + N_s} \right)$$

$$\frac{S_{io}}{S_w} = \frac{N_c + N_s}{N_s}$$

$$\therefore S_{io} > S_w$$

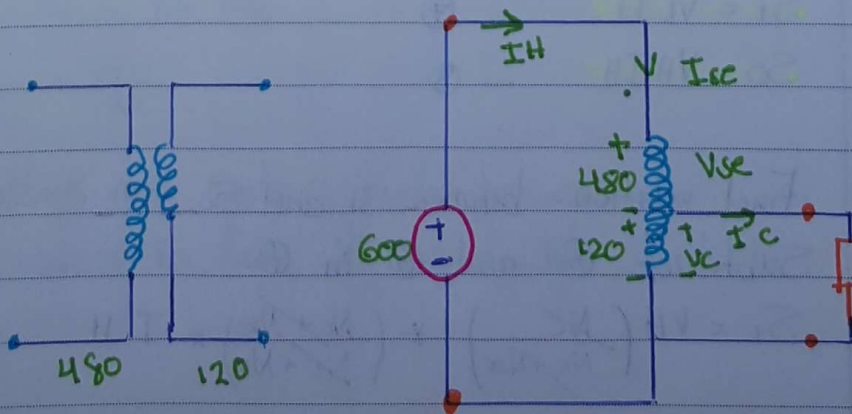* Example: A 5000VA, (480/120V) conventional transformer is to be used to supply Power from 600V source to 120V load. Consider that the transformer to be ideal and all insulation can handle 600V

- Sketch the transformer connection that will do the job.
- Find the kVA Rating of the Produced Autotransformer.



$$\frac{S_{10}}{S_w} = \frac{N_c + N_{se}}{N_{se}}$$

$$N_c \propto V_c = 120$$


$$N_{se} \propto V_{se} = 480$$

$$\begin{aligned} \therefore S_{10} &= S_w \left(\frac{N_c + N_{se}}{N_{se}} \right) \\ &= 5000 \left(\frac{120 + 480}{480} \right) = 6250 \text{ VA} \end{aligned}$$

[C] Find the max. primary and secondary current which may flow.

$$\therefore I_{p, \max} = \frac{6250}{600} = 10.4 \text{ A}$$
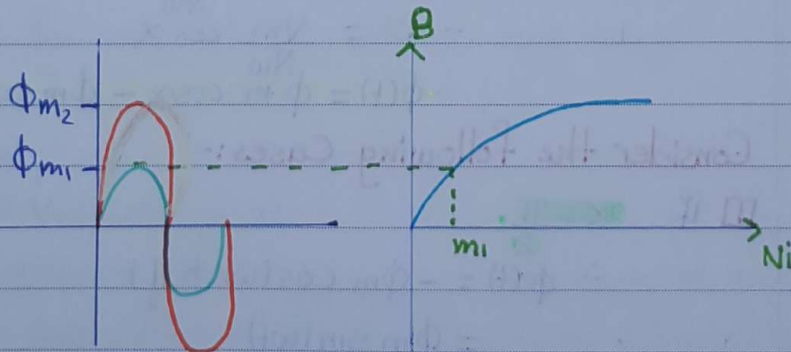
$$I_{s, \max} = \frac{6250}{120} = 52.1 \text{ A}$$




$$I_{m_2} \gg I_{m_1}$$

I_{m_2} can exceed Rated current of Transformer.

* Current Inrush

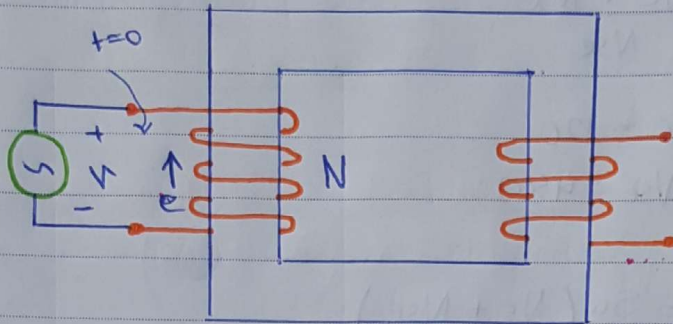This is a very high magnetizing current which may flow in the primary of a transformer when it is connected to the supply.



$$\text{Let } v = V_m \sin(\omega t + \alpha) \quad \alpha \equiv \text{phase angle of the voltage.}$$

$$e = V = V_m \sin(\omega t + \alpha)$$

$$\text{Since } e = N \frac{d\phi}{dt}$$

$$\therefore \phi = \frac{1}{N} \int e dt = \frac{1}{N} \int V_m \sin(\omega t + \alpha) dt$$

$$\phi(t) = -\frac{V_m}{N\omega} \cos(\omega t + \alpha) + C \quad \leftarrow \text{constant of integration}$$

ϕ_m : the Peak value of ϕ

$$\therefore \phi(0) = 0 = -\frac{V_m}{N\omega} \cos \alpha + C$$

$$\therefore C = \frac{V_m}{N\omega} \cos \alpha$$

$$\therefore \phi(t) = \phi_m \cos \alpha - \phi_m \cos(\omega t + \alpha)$$

Consider the following Cases:-

III if $\alpha = \frac{\pi}{2}$

$$\therefore \phi(t) = -\phi_m \cos(\omega t + \frac{\pi}{2})$$

$$= \phi_m \sin(\omega t)$$

$\therefore \phi(t)$ has its normal Peak of ϕ_m

$$\text{Since } v = V_m \sin(\omega t + \frac{\pi}{2})$$


\therefore at $t=0$

$$v = V_m \sin(\frac{\pi}{2}) = V_m$$

Hence the voltage is applied at a value = +ve maximum then there is no problem in magnetizing Current.

$$\boxed{2} \quad \alpha = 0$$
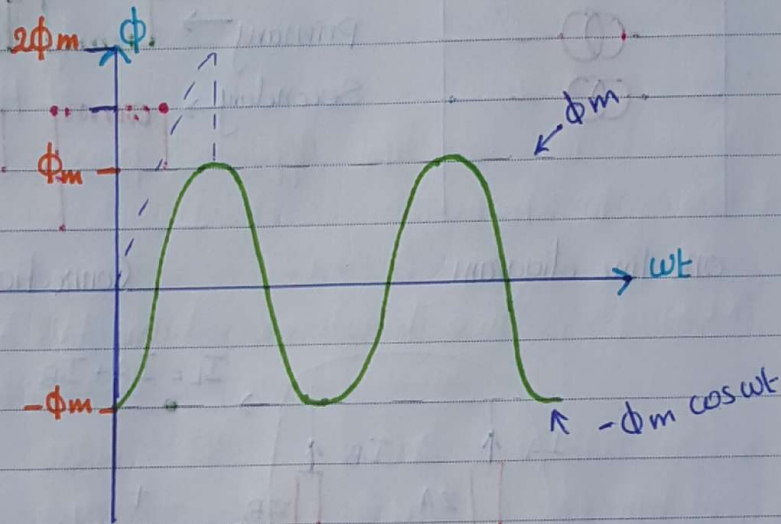
$$\therefore \phi(t) = \phi_m - \phi_m \cos(\omega t)$$




* In this case flux is twice the normal flux.
 Hence the required I_m will be very large
 and $I_m \gg I_{rated}$



$$V = V_m \sin(\omega t + 0^\circ)$$

$$= V_m \sin \omega t$$

$$\text{at } t=0, V=0$$

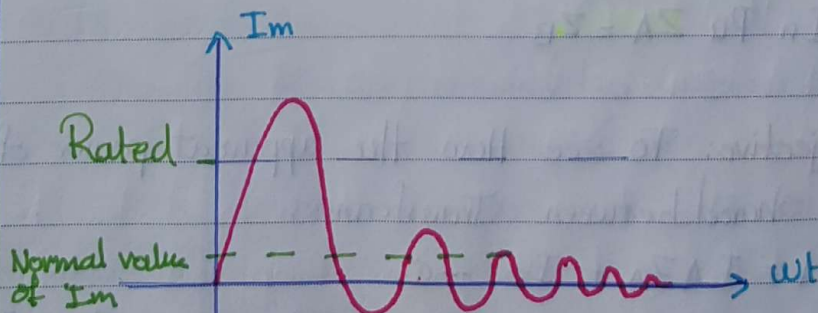

Parallel Operation of Transformer

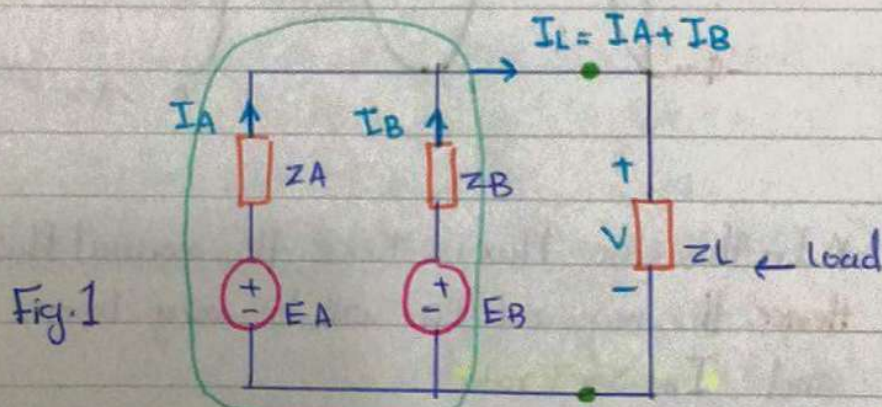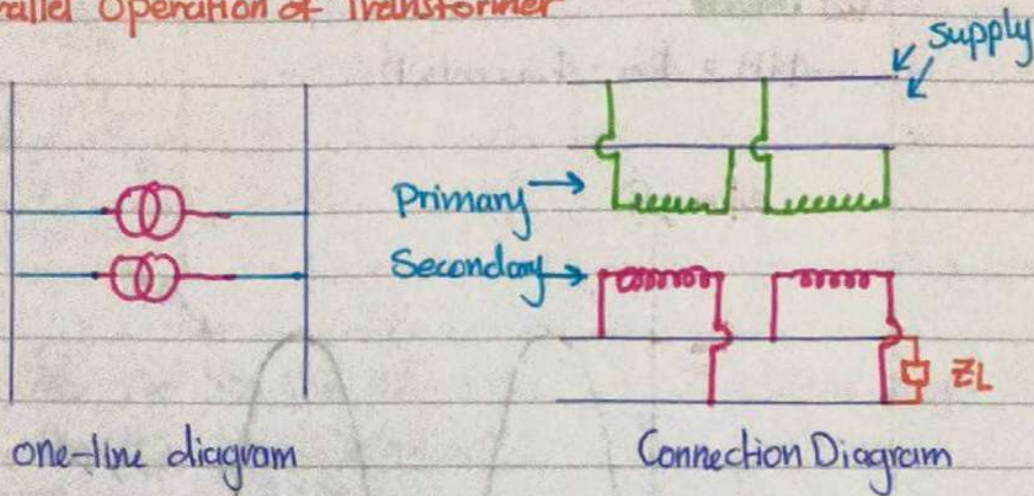

* Among the major consider for Parallel operation:-

1. $E_A = E_B$
2. In Pu $Z_A = Z_B$

* Objective: To see How the apparent power of the load is shared between transformer.

$$E_A = I_A Z_A + I_Z \quad \text{--- (1)}$$

$$E_B = I_B Z_B + I_Z \quad \text{--- (2)} \quad \text{where } I = I_A + I_B$$

$$V = I Z \quad \text{--- (3)}$$

By using these equations it can be found that:-

$$I_A = \frac{E_A}{Z_A + Z + \frac{2Z A}{Z_B}} + \frac{E_A + E_B}{Z_A + Z_B + \frac{Z A Z_B}{Z}} \quad \dots (4)$$

representing the circulating current in the source

Similar expression for I_B can be found by replacing A by B in (4)

$$I_B = \dots (5)$$

Since $V = I Z = (I_A + I_B) Z \dots (6)$ Then by substituting (4) and (5) into (6) it can be found that:

$$V = \frac{E_A}{Z_A} + \frac{E_B}{Z_B} \dots (7)$$

$$\frac{1}{Z_A} + \frac{1}{Z_B} + \frac{1}{Z}$$

The advantage of (7) that it can be modified when more transformers are added in parallel

For example:- if transformers C and D are added. then: (1) Add the terms E_C/Z_C and E_D/Z_D to numerator in (7)

(2) Add the terms $1/Z_C$ and $1/Z_D$ to Denominator in (7)

* If $E_A = E_B$

Then By KVL: around the Green Loop in Fig. 1 ←

$$-E_A + I_A Z_A - I_B Z_B + E_B = 0$$

$$\therefore I_A Z_A = I_B Z_B \quad (8)$$

Since $I = I_A + I_B \quad (9)$

\therefore By Using (8) and (9) it can be found:-

$$I_A = I \left(\frac{Z_B}{Z_A + Z_B} \right) \quad I_B = I \left(\frac{Z_A}{Z_A + Z_B} \right)$$

$$\therefore \text{Apparent Power of (A)} \quad S_A = V I_A = V I \left(\frac{Z_B}{Z_A + Z_B} \right) \quad \text{--- (10)}$$

$$\text{Apparent Power of (B)} \quad S_B = V I_B = V I \left(\frac{Z_A}{Z_A + Z_B} \right) \quad \text{--- (11)}$$

Apparent Power
of the Load

(10) and (11) Give the Apparent power sharing (distribution) between transformers.

***Example:-** Two Transformers have the Following Data:-

	Transformer A	Transformer B
Rated Current (A)	200	600
E ← No load Voltage (V)	245 = E_A	240 = E_B
Req (PU)	0.02	0.025
Xeq (PU)	0.05	0.06

*Find the terminal voltage when they are connected in Parallel to supply a load $Z = (0.25 + j0.1) \Omega$

$$V = \frac{E_A / Z_A + E_B / Z_B}{1/Z_A + 1/Z_B + 1/Z}$$

$$\therefore E_A = 245 \angle 0^\circ \text{ V}$$

$$E_B = 240 \angle 0^\circ \text{ V}$$

- Note: The Base values which used for R_{pu} , X_{pu} are the Rating of the Given components.

$$\therefore Z_{Ab} = \frac{245}{200} \Omega$$

$$Z_{Bb} = \frac{240}{600} \Omega$$

No. _____

$$Z_A = (0.02 + j0.05) * \frac{245}{200} \Omega$$

$$Z_B = (0.025 + j0.06) * \frac{240}{500} \Omega$$

By substitution it can be found $\rightarrow V = 230 \angle -3^\circ \text{ V}$

*Solve this example By using PU concept.

$$Z_{\text{new}}(\text{PU}) = Z_{\text{old}}(\text{PU}) * \left(\frac{V_{\text{b,old}}}{V_{\text{b,new}}} \right)^2 * \left(\frac{S_{\text{b,new}}}{S_{\text{b,old}}} \right)$$




3-Phase Transformer:-

Why?? because electrical energy is Generated, transmitted and distributed as a 3-phase.

Construction:

It could be one of two types:-

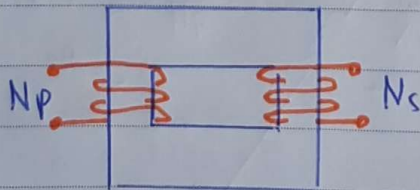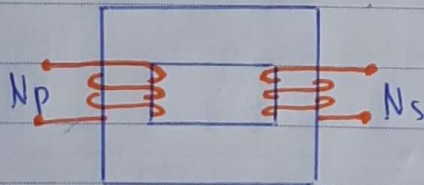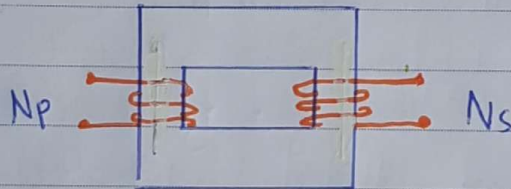- 1] Using 3 Single phase (1-ph) transformers, so called 3-phase transformer Bank



- more reliable:


Reserve = 1-ph terms

* IF one Transformer fail. still 3 phase can be supplied by the other 2 transformers

So called V-connection

But with a reduced Apparent power Capability

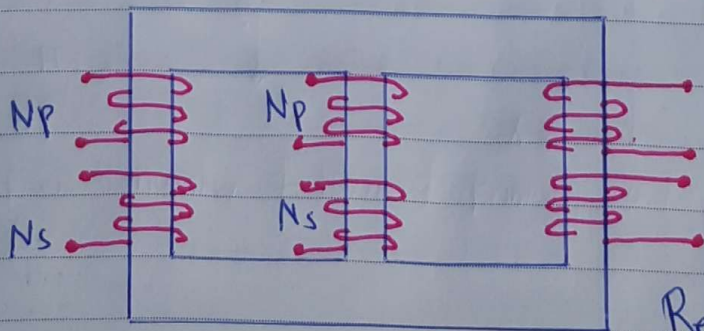- 2] Single core with 3 pairs of windings:-



- lighter

- cheaper

- more efficient

Reserve = 3-ph - Terms

Connections:-

* Since a 3-phase winding can be connected as Y or Δ then there are 4-types of 3-phase transformer from connection point to view:-

1. Y-Y
2. Y- Δ
3. Δ -Y
4. Δ - Δ

* Objective

1. Ratio of voltage magnitude
2. phase shift in Transformer
3. Per phase equivalent circuit.

Convention


1. The phase of the HV side is represented by capital letters ABC
2. The phase of the LV side is represented by small letters abc

* See how various standards represent the HV and LV windings


2. Terminals of HV side are represented by letters H_1, H_2, H_3
Terminals of LV side are represented by letters X_1, X_2, X_3

3. In Graphical representation the windings of each phase are drawn parallel to each other.

Y-Y connection

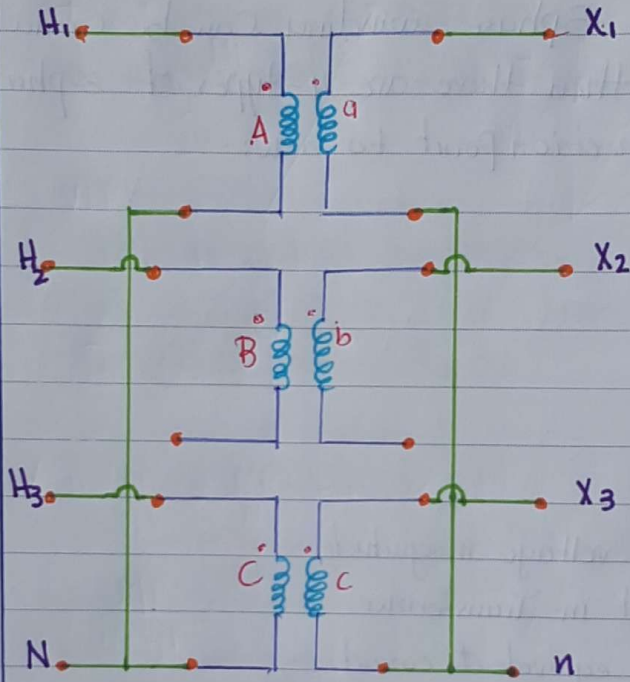

Graphical representation:-

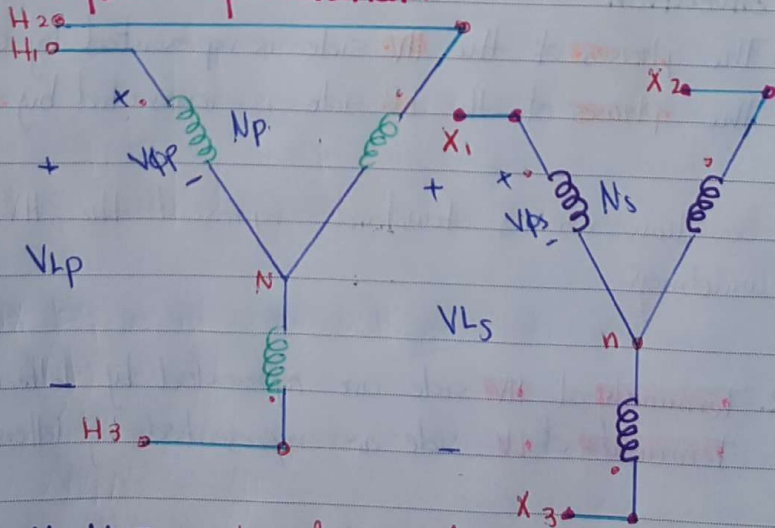

$N_p, N_s \equiv$ number of turns of Primary and secondary.


Objective:

Ratio of voltage magnitude.


$$\frac{V_{\phi P}}{V_{\phi S}} = \frac{N_P}{N_S} = a$$

$$\frac{V_{LP}/\sqrt{3}}{V_{LS}/\sqrt{3}} = \frac{N_P}{N_S} = a$$



$$\therefore \frac{V_{LP}}{V_{LS}} = a$$

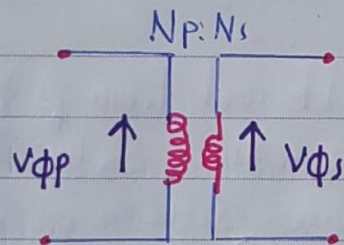

Y-Δ Connection

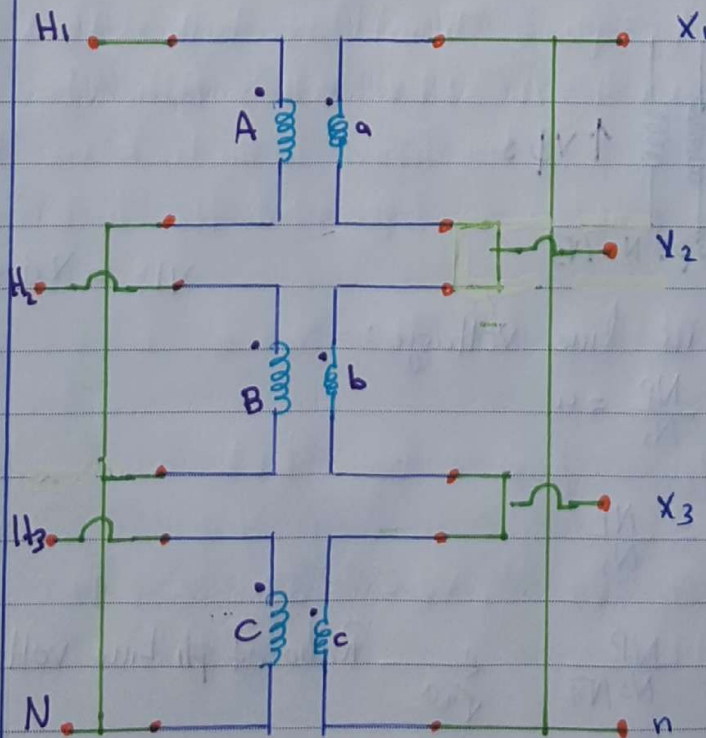

No. _____

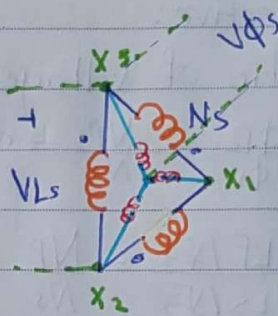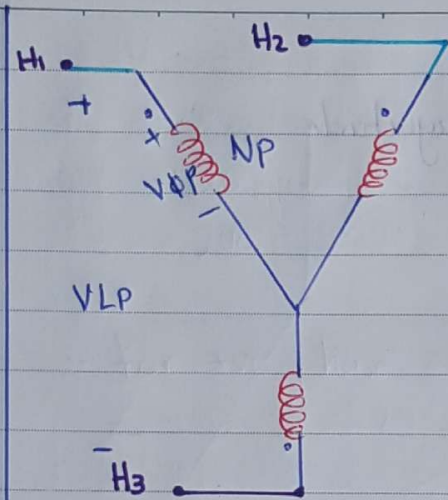


$$\frac{V_{\phi P}}{V_{Ls}} = \frac{N_P}{N_s} = a$$

$$\frac{V_{\phi P}}{\sqrt{3} V_{\phi S}} = \frac{N_P}{N_s}$$

$$\frac{V_{\phi P}}{V_{\phi S}} = \frac{N_P}{N_s / \sqrt{3}}$$

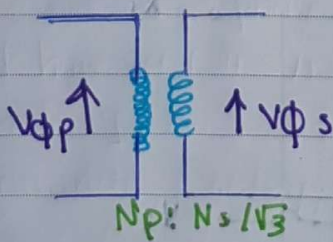← Ratio of phase voltage.
→ effective turns Ratio



$$V_{Ls} = \sqrt{3} V_{\phi S} \leftarrow \Delta$$

* Express in line voltage :-

$$\frac{V_{\phi P}}{V_{Ls}} = \frac{N_P}{N_s} = a$$

$$\frac{V_{LP} / \sqrt{3}}{V_{Ls}} = \frac{N_P}{N_s}$$

$$\frac{V_{LP}}{V_{Ls}} = \frac{N_P}{N_s / \sqrt{3}}$$

← Ratio of Line voltage
← $\sqrt{3} a$

By similar Procedure it can be shown for Δ -Y and Δ - Δ :-

The effective turns Ratio = line voltage Ratio.


* Phase shift in 3-phase Transformer :-

* Y-Y and Δ - Δ do not introduce phase shift between corresponding voltage. (e.g. V_{AB} and V_{ab} are in phase)

* However Δ -Y and Y- Δ create a phase shift of 30°

→ As a convention the terminal markings (H_1, H_2, H_3 and X_1, X_2, X_3) are made in such a way that HV leads LV by 30° in the case of +ve phase sequence.

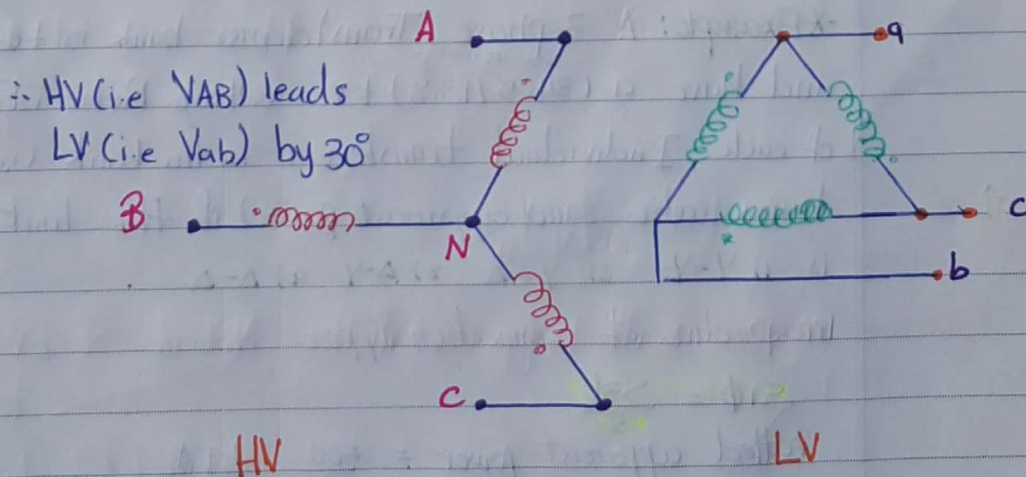* To illustrate consider the following Y- Δ connection.



* V_{AN} is in phase with V_{ab}

if $\angle V_{AN} = 0^\circ$, then $\angle V_{ab} = 0^\circ$

In the positive phase sequence

In the +ve Phase Sequence

$$\angle V_{an} = 0^\circ \quad \angle V_{ab} = 0^\circ + 30^\circ$$

$$\angle V_{bn} = 120^\circ \quad \angle V_{bc} = 120^\circ + 30^\circ$$

$$\angle V_{cn} = 240^\circ \quad \angle V_{ca} = 240^\circ + 30^\circ$$

∴ For +ve phase sequence

$$\angle V_{AB} = \angle V_{AN} + 30^\circ$$

$$\angle V_{AB} = 0^\circ + 30^\circ = 30^\circ$$

* The same Result can be obtained from Δ -Y

Note the \rightarrow HV \uparrow LV \uparrow

letters on the terminal should be in such a way that VAB leads Vab by 30°

* Example: A 3-phase Transformer bank is to handle 500 kVA and have a ^{line voltage} (34.5/13.8) kV voltage Ratio. Find the rating of each individual transformer in the bank (i.e. its HV, LV, turns ratio and apparent power) if the bank is connected

is 1) Y-Y 2) Y- Δ 3) Δ -Y 4) Δ - Δ

irrespective of connection type:-

$$S_{1\phi} = \frac{S_{3\phi}}{3}$$

$$\text{rated apparent power} = \frac{500}{3} \text{ kVA}$$

1) Y-Y

$$V_{\phi HV} = 34.5/\sqrt{3} \quad , \quad V_{\phi LV} = \frac{13.8}{\sqrt{3}} = 7.97$$

$$= 19.93$$

$$a = \frac{V\phi_{HV}}{V\phi_{LV}} = 2.5$$

2) $\gamma - \Delta$

$$V\phi_{HV} = 19.92$$

$$V\phi_{LV} = 13.8 = V_{LLV}$$

$$a = 1.44$$

3) $\Delta - \gamma$

$$V\phi_{HV} = 34.5$$

$$V\phi_{LV} = 13.8 \sqrt{3}$$

$$a = 4.33$$

4) $\Delta - \Delta$

$$V\phi_{HV} = 34.5$$


$$V\phi_{LV} = 13.8$$

$$a = 2.5$$


Voltage Groups :-

Although the 3-phase winding, As seen before, can be connected as Δ or γ

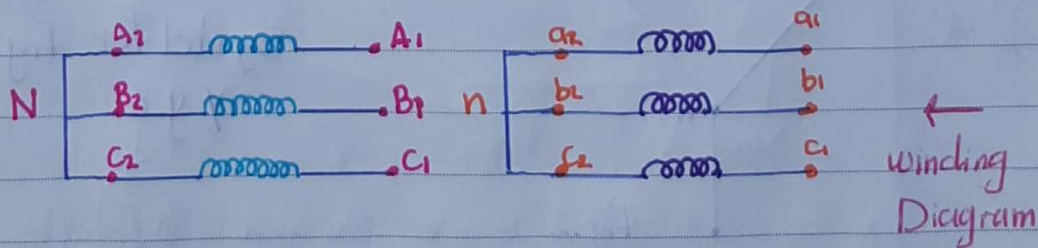
Also the connection of these windings can be reversed as illustrated below:-



∴ Corresponding phasor Diagram:-

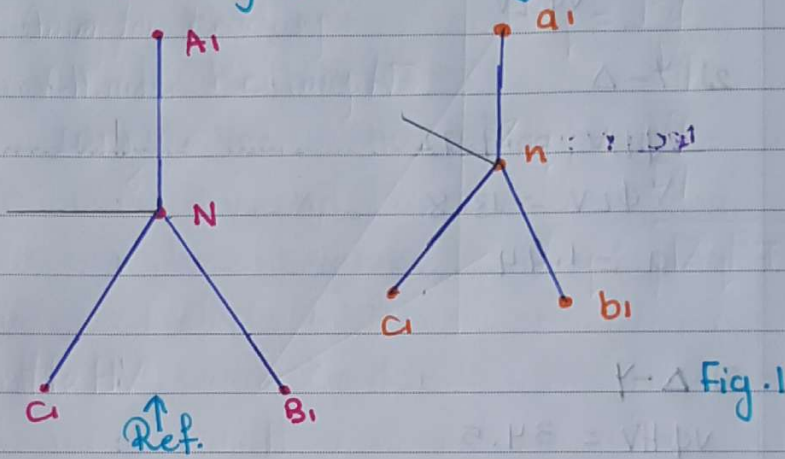


* Vector Diagram Symbol:-

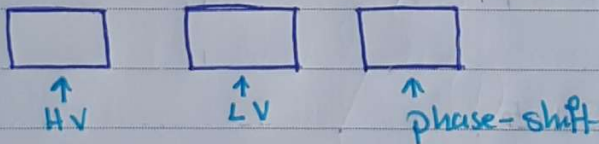


By means at the clock hour:-
 How **hour arm** at 12 → HV
minute arm represent LV

Symbol = $Y_N y_n$ ← from Fig. 1

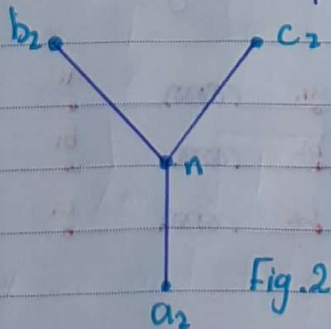* what will happen if the Neutral of LV is reversed?



Symbol for Fig. 2 =

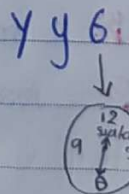


Conclusion: If all possible connections of the LV windings are considered then the phase shift can be $0^\circ, 180^\circ, -30^\circ, +30^\circ$. Summarized in the following table

Vector Symbol	Phase Shift	Main Group
Yy_0	0°	1
Dd_0	0°	1
Yy_6	180°	2
Dd_6	180°	2
Dy_1	-30°	3
Yd_1	-30°	3
Dy_{11}	30°	4
Yd_{11}	30°	4

Final Comment:- All calculation of 1-phase transformer (O/C, S/C, V.R., η and P.U) are applicable to 3-phase transformers **but** using Per-Phase circuit.

Illustration:-

Consider O/C and S/C Tests.

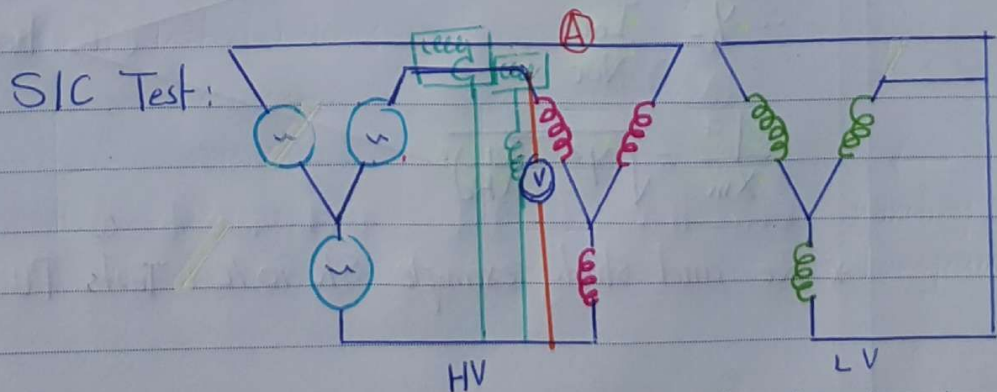

From the Readings:-

$$I_{\phi} = \text{Ammeter Reading}$$

$$V_{\phi} = \text{Voltmeter Reading} / \sqrt{3}$$

$$P_{\phi} = \frac{W_1 + W_2}{3}$$


$$R_{eq} = \frac{P_{\phi}}{I_{\phi}^2}$$

$$|Z_{eq}| = \frac{V_{\phi}}{I_{\phi}}$$

$$\therefore X_{eq} = \sqrt{|Z_{eq}|^2 - R_{eq}^2}$$

Referred to HV

O/C Test:-

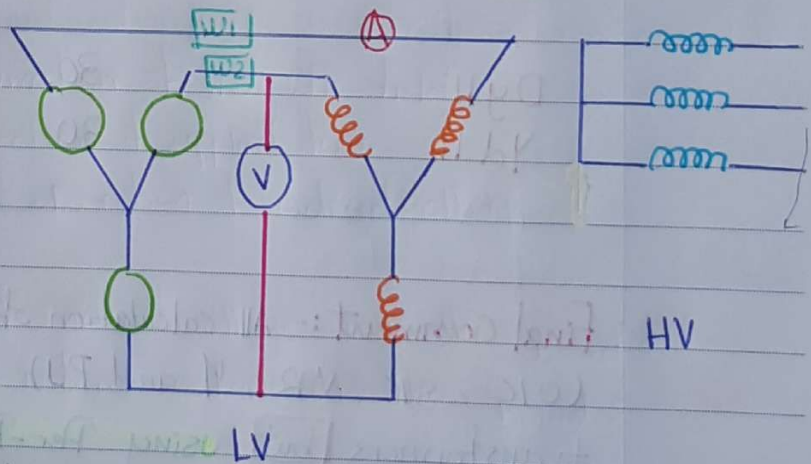

$$\therefore P_{oc} = V_{oc}^2 / R_c$$

$$\therefore R_c = V_{oc}^2 / P_{oc}$$

$$I_{oc} = V_{oc} Y$$

$$\therefore Y = \frac{I_{oc}}{V_{oc}}$$

$$\frac{1}{X_m} = \sqrt{Y^2 - \left(\frac{1}{R_c}\right)^2}$$

Referred to LV

* See and study example SIC 10/1C, Tests PU, VR and Y

AC Machines :- ↔ Generators ↔ Motors

* These machines can be classified in general into:

1. Synchronous machines: Magnetic Field winding is supplied by a dc current from an external source
2. Induction machines: Magnetic Field winding current is supplied by induction action (i.e transformer action)



* In this course, one is concern with 3-phase Synchronous.

AC Machines Fundamental :-

Voltage induced in a coil

* Consider a stationary magnetic field, within which a coil is rotating.

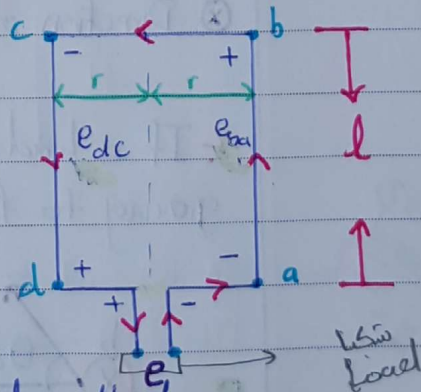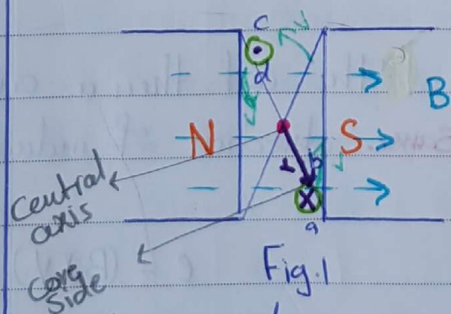Objective: To find the magnitude and shape of the induced voltage in the coil.



Voltage induce in a conductor of length l :

$$e = (B \times V) l$$

$B \equiv$ flux density

$V \equiv$ linear velocity of the conductor

$l \equiv$ length of the conductor

* The coil is rotated by means of an external mechanical force
let the applied rotation is ccw

* Induced voltage across the coil terminals = Sum of voltages induced in a b, bc, cd, da.

* Usually bc (called Back end connection) and da (called Front end connection) are outside the magnetic field. Hence no induced voltage in them.

Direction of induced voltage can be found by using RHR:-

Forefinger \equiv Direction of magnetic field


Thumb \equiv Direction of applied force

Middle finger \equiv Direction of induced voltage.

⊙ Direction of induced voltage out of the Board.


⊗ Direction of induced voltage into the Board.

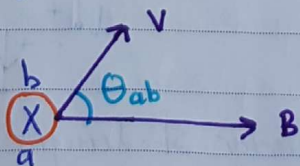* If a load is connected to the coil then a current is going to flow in the **same** direction of induced voltage



$$e = (B \times v) \cdot l$$
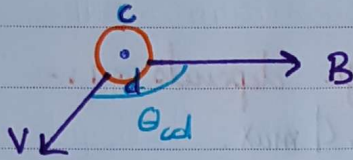
$$e_{ba} = (Bv \sin \theta_{ab}) l = Bvl \sin \theta_{ab} \quad \text{--- (1)}$$



$$\therefore e_{dc} = (BV \sin \theta_{cd}) l$$

$$e_{dc} = BV l \sin \theta_{cd} \dots (2)$$

\therefore Induced voltage $e = e_{ba} + e_{dc}$

$$\therefore e = BV l \sin \theta_{ab} + BV l \sin \theta_{cd} \dots (3)$$


But $\theta_{cd} = 180 - \theta_{ab}$

$$\therefore e = BV l \sin \theta_{ab} + BV l \sin (180 - \theta_{ab})$$

$$= 2BV l \sin \theta_{ab}$$

* if let $\theta_{ab} = \theta$
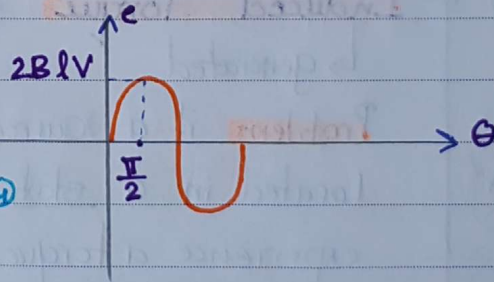
$$\therefore e = 2BV l \sin \theta \dots (4)$$



\therefore The shape of induced voltage in a **single turn coil** is sinusoidal with a magnitude = $2BlV$

* (4) can be Rewritten as follows:-

if Rotational Speed = ω (Rad/s)

$$\therefore \theta = \omega t \dots (5) \quad t \equiv \text{time}$$

$$\omega r = V \dots (6) \quad r \equiv \text{distance between coil side and central axis}$$

Sub. (5), (6) into (4)

$$e = 2B (\omega r) l \sin \omega t = \boxed{[2rl]} BW \sin \theta$$

\rightarrow Area of the core plane = A

$$\therefore e = AB \omega \sin \omega t \quad * \text{ when } A \text{ is } \perp \text{ to flux lines then}$$

$$AB = \phi_{\max}$$

$$e = \phi_{\max} \omega \sin \omega t \dots \textcircled{7}$$

* In general induced voltage depends on :-

1. Flux in the machine, ϕ_{\max} .
2. Speed of machine, ω .
3. Structure of the machine.


* Note:- This structure (Fig.1) is used in dc machines.

Induced Torque

↳ generated

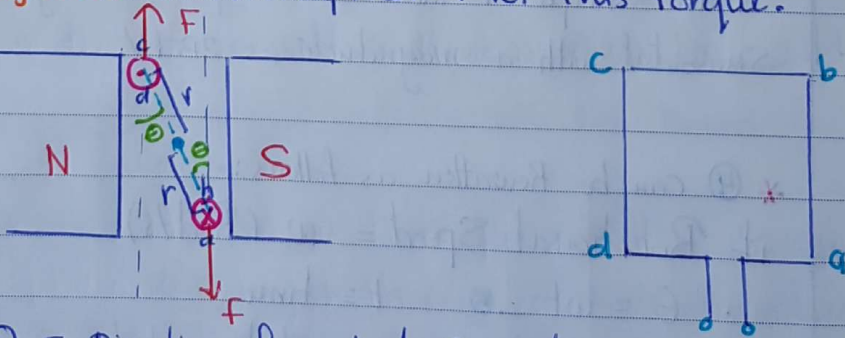Problem if a current is applied to a single-turn coil located in a stationary magnetic field, then it will experience a torque.

Objective Find the expression for this torque.



$\otimes \odot \equiv$ Direction of applied Current


Direction of developed force, F can be found by means of LHR \rightarrow as follows:-

For Finger \equiv Direction of magnetic field.

Middle \equiv Direction of applied Current.

Thumb \equiv Direction of Developed force

$$\phi = \mu NI$$

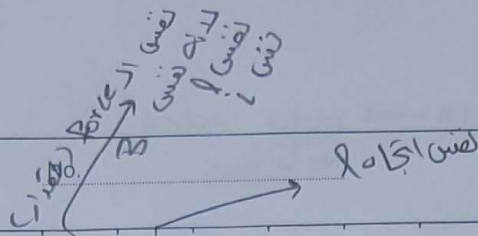

By definition, $f = i (B \times l)$

* Back and front end connections will not experience any torque. $T = r \times F$

$$F_{ab} = F_{cd} = B i l$$

$$T_{ab} = F_{ab} r \sin \theta$$

$$= B i l r \sin \theta$$

$$T_{cd} = F_{cd} r \sin \theta$$

$$= B i l r \sin \theta$$

$$\therefore \text{Total Torque } T = T_{ab} + 0 + T_{cd} + 0$$

$$T = 2 B i l r \sin \theta$$

$$= (2 r l) B i \sin \theta$$

$$\textcircled{1} \dots T = A B i \sin \theta$$


$A =$ coil's plane

$\textcircled{1}$ can be Rewritten as follows:-

\therefore Area.

where B is flux density of stationary (i.e. stator) magnetic field Rewrite as B_s

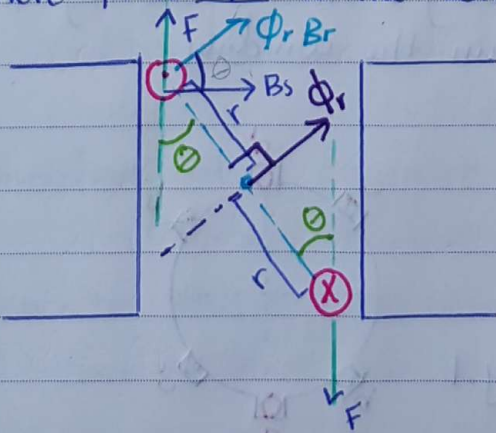* Current i in the rotating coil (i.e. Rotor) generate flux ϕ_r , whose direction can be found by means of RHR where ϕ_r is \perp to the coil's plane.



$$* Ni = R \phi_r$$

$$Ni = \frac{l'}{A' \mu} \phi_r$$

$l' \rightarrow$ mean length

$A' \rightarrow$ cross sectional Area.

Since $B_r \propto \phi_r$

$$\therefore i = \frac{k}{N} B_r \dots \textcircled{2}$$

$k = \text{Constant}$

Substitute $\textcircled{2}$ into $\textcircled{1} \rightarrow$

$$T = AB_s \frac{k}{N} B_r \sin \theta = G B_s B_r \sin \theta \dots \textcircled{3}$$

$G(B_s \times B_r) \leftarrow \sin \theta$

Also it can be found that Angle between B_r and $B_s = \theta$

$$\therefore T = G (B_s \times B_r)$$

Comment:-

In a generator action there is a motor action and in the motor action there is a generator action

Rotating Magnetic field

Definition: If a balance three phase voltage is applied to a 3-phase winding, then a rotating magnetic field is produced within the winding

Proof:-

3 coils
6 slots



Fig. 1

a, a' \equiv Terminals of coil a

b, b' \equiv Terminals of coil b

c, c' \equiv Terminals of coil c

In Fig. 1, coil span = 180° mechanical degrees

* let the currents be:-

$$i_a = I_m \sin \omega t$$

$$i_b = I_m \sin(\omega t - 120^\circ)$$

$$i_c = I_m \sin(\omega t - 240^\circ)$$

where:

i_a enter terminal a and leave through a'

i_b enter terminal b and leave through b'

i_c enter terminal c and leave through c'

ωt	i_a	i_b	i_c	Direction of generated ϕ
0	0	\otimes -ve	\odot +ve	\uparrow
90	+ve	-ve	-ve	\leftarrow
180	0	+ve	-ve	\downarrow
270				
360				



Convention +ve current \odot

-ve current \otimes


* Hence in this type of winding (2 pole - winding) when the current make one cycle The magnetic field make one mechanical Rotation $\therefore f_e = f_m$

electrical frequency $\nearrow f_e = f_m \nwarrow$ mechanical frequency.

* when $\omega = 0$ This type of stator winding is called 2 pole-winding



* when $\omega = 90$

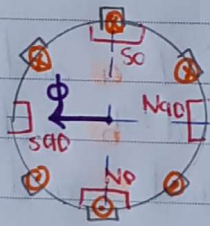

* when $\omega = 180$

↑


→

↓

* If the coil span and phase span are changed then one may change the number of winding-poles as follows:-

* let coil span = $180^\circ = 40^\circ$
 phase span = $\frac{120^\circ}{2} = 60^\circ$ connected

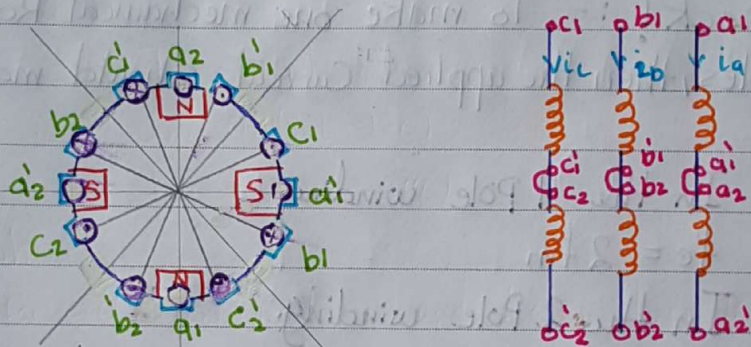* let each phase represented by 2 coils in series:-




this when $\omega t = 0$

let: $i_a \equiv I_m \sin \omega t$
 $i_b \equiv I_m \sin (\omega t - 120^\circ)$
 $i_c \equiv I_m \sin (\omega t - 240^\circ)$

+ve Current \odot

-ve Current \otimes

ωt	i_a	i_b	i_c	
0	0	-ve	+ve	← Represent 4-pole winding
90	+ve	-ve	-ve	
180				
270				

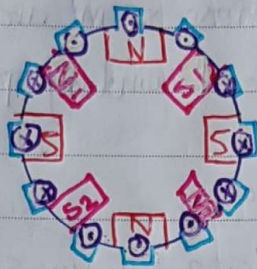

← this when $\omega t = 90$

Check! :- To make one mechanical Rotation for the Poles, then the applied Current should make 2 cycles.

∴ In the 4 Pole winding
 $f_e = 2 f_m$

In the 2 Pole winding
 $f_e = f_m$

∴ In General :-

$$f_e = P f_m$$

f_e → electrical frequency (HZ)
 f_m → mechanical frequency (Rotation Per Second (r.p.s))
 P → No. of pole Pairs


Induced or Generated voltage in AC Machines:-

As a Balanced 3-phase voltage applied to stator windings Produce Rotating field. Then an applied Rotating magnetic Field within stator windings will induced a balanced 3-phase voltage in the stator.

Objective :- To find an expression for the generated voltage in the stator winding due to the Rotating magnetic field.


* In Ac machines, the Rotor windings are designed in such way to Produce a flux whose magnitude changes in Sinusoidal manner.

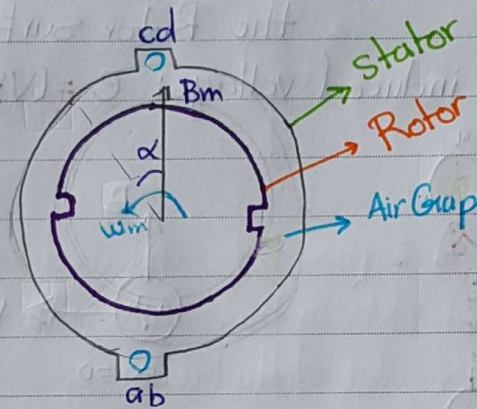Procedure :- Consider a single turn coil on the stator.



Rotor are of two types:-

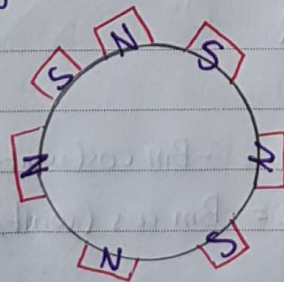
1. Cylindrical or non-salient.
2. noncylindrical or salient.



$$B = B_m \cos \alpha$$

$\alpha \equiv$ the angle from the direction B_m

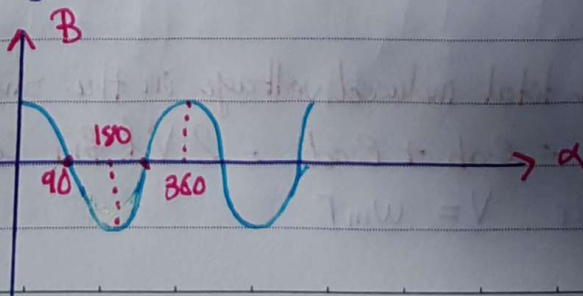flux is sinusoidal but the direction of maximum flux density (B_m) along +ve y-direction




Since the Rotor is Rotating with angular speed ω_m (rad/s) Then the flux at a point on the stator with angle α is

$$B = B_m \cos(\omega_m t - \alpha)$$

↳ This for flux Radially outward from the Rotor surface.

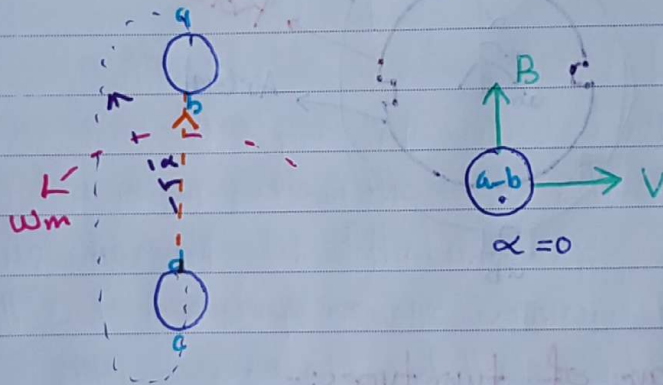* To find induced voltage: $e = (V \times B) l$




$B = B_m \cos(\omega_m t - \alpha)$ ← always assumes that the flux is

$$e = (B \cdot v) \cdot l$$

outward from Rotor surface.

$$e_{ab} = (B_m \cos \omega_m t) V l$$

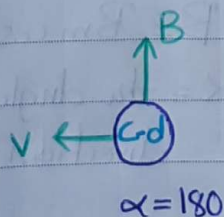

$$e_{cd} = -B_m \cos(\omega_m t - \alpha) V l$$

$$e_{cd} = B_m \cos(\omega_m t) V l$$

* There is no induced voltage in bc and cd because $(B \times v)$ is \perp on their length

∴ The total induced voltage in the single turn coil is

$$e = e_{ab} + e_{cd} = 2 \cdot V l \cdot B_m \cos \omega_m t \quad \text{--- ①}$$

$$\text{Since } V = \omega_m r$$

$$\begin{aligned} \therefore e &= 2wr l B_m \cos \omega_m t \\ &= (2r l) B_m \omega_m \cos \omega_m t \\ &= A B_m \omega_m \cos (\omega_m t) \end{aligned}$$

$2r.l \equiv$ Area of the plane

$$\therefore e = \phi_m \omega_m \cos (\omega_m t)$$

\therefore For N turns coil \rightarrow

$$e = N \phi_m \omega \cos (\omega t)$$

For a 2-pole stator winding $\omega_s = \omega_m = \omega$

$$e = \underbrace{N \phi_m \omega}_{E_m} \cos \omega t$$

* Comments: -

- ϕ_m is called flux per pole.
- Peak or maximum value of Induced voltage,
 $E_m = N \phi_m \omega$

$\therefore E_m$ depends on: speed of rotor

- magnetic field of Rotor (i.e. ϕ_m)
- Construction of Machine (i.e. N)

$$3. E_{RMS} = E_m / \sqrt{2}$$

$$\begin{aligned} \therefore E_{RMS} &= \frac{1}{\sqrt{2}} N \phi_m \omega \\ &= \frac{1}{\sqrt{2}} N \phi_m 2\pi f \end{aligned}$$

$$E_{RMS} = 4.44 N \phi_m f$$

\hookrightarrow frequency of Induced voltage.


4. Hence for 3-phase Ac generator a Balanced 3-phase voltages will be generated

$$E_{an} = E_m \sin \omega t$$

$$E_{bn} = E_m \sin (\omega t - 120)$$

$$E_{cn} = E_m \sin (\omega t - 240)$$



*usually the generator is γ -connected.

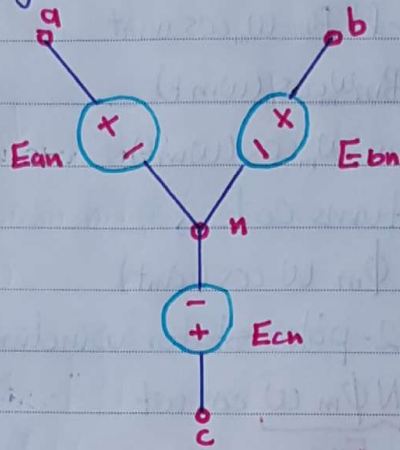

\therefore line voltage
 $= \sqrt{3} (N\phi_m \omega)$

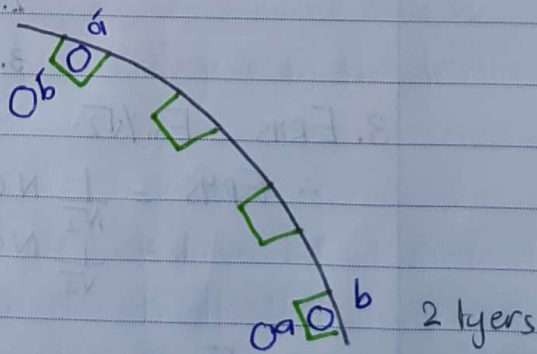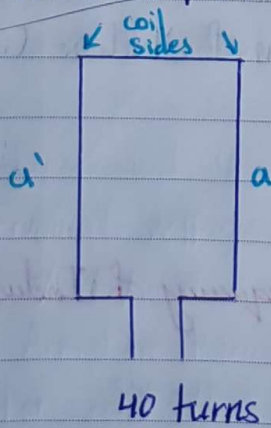* **Example:-** A 3-phase, γ -connected, 4 pole winding is installed in 24 slots in the stator. There are 40 turns of wire in each slot of the windings.

All coils in each phase are connected in series. The flux per pole is 0.06 wb and the speed of Rotation of magnetic field 1800 rpm.



1. what is the frequency of generated or induced voltage?

$$f_e = P \frac{f_m}{2} = \left(\frac{4}{2}\right) * \frac{1800}{60} = 60 \text{ Hz}$$

\uparrow pole pairs \uparrow ps

2. what are the resulting phase and terminal voltages?

$$E_{\phi} = 4.44 N \phi_m f$$

$$= 4.44 * \left(\frac{24}{3}\right) * 40 * 0.06 * 60$$

$$= 3617.28 \text{ V} \leftarrow \text{Phase voltage}$$

$$\text{terminal, line voltage} = \sqrt{3} E_{\phi} = 6265.3 \text{ V}$$

* See the rating of generated voltage of 3-phase generator in power stations \rightarrow (11-25) رطل تقريبا

$$E_{\phi} = 4.44 N \phi_m f * k_p * k_d \rightarrow \begin{matrix} \text{Distribution} \\ \text{factor.} \end{matrix}$$

\hookrightarrow Pitch factor

* See Appendix B. in your textbook.

Machines: Chapter

No. _____

3-phase Synchronous Generator:-

Construction

Rotor

(Carry the **main** magnetic field circuit)

Stator

(Carry the Armature windings)

↳ this is the 3-phase winding (As explained before)

* Main magnetic field circuit:-

- Usually the field current is supplied from external DC source to the field windings through brushes and sliprings.

- other types of supplying field current are:-

1. Brushless exciters.
2. Pilot exciters (use permanent Magnet)

* see the introduction and Block diagram in the textbook.

* Equivalent circuit of the 3-phase generator →

Terminal voltage, $V\phi =$ generated voltage $E\phi$ at No-load.

$V\phi \neq E\phi$ at load condition due to the following Reasons:-


A) Armature Reaction: Interaction between main flux of the rotor and the flux produced by Armature current.

- This armature Reaction is represented by a reactance, jX


B) Self induced of Armature windings, jX_a

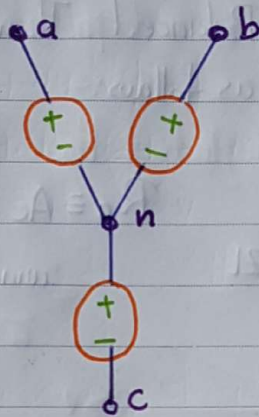C) Resistance of Armature windings, R_a


two electromagnetic
1. main
2. exciter magnet



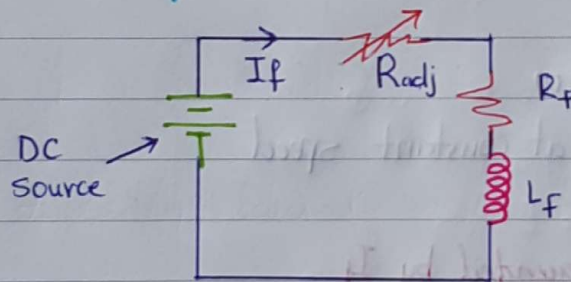∴ The equivalent circuit can be deduced as follows:




Field circuit

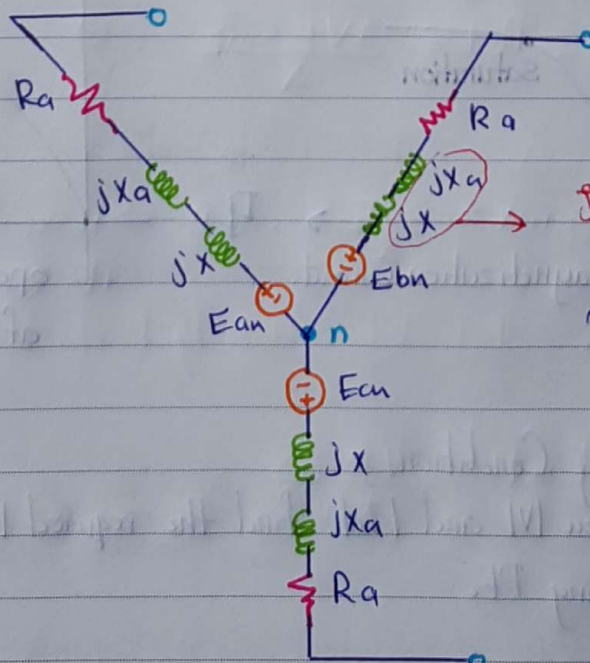

$jX + jX_a = jX_s$
Synchronous Reactance.

Armature Circuit

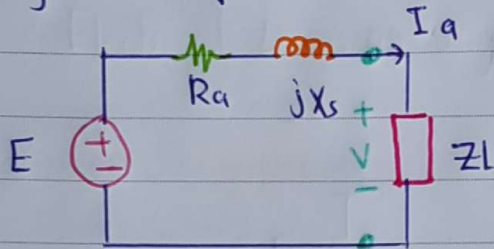* Since the system is Balanced Then it can be represented by Per-phase circuit as follows:-



$R_a \equiv$ Ac Resistor of Armature windings.

* Performance of the generator Under Various loading Condition:-



1) No-Load

$$V = E = N\phi\omega$$

Running Rotor at constant speed

$$E = k\phi$$

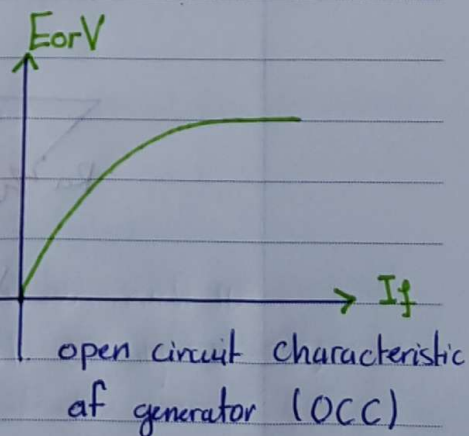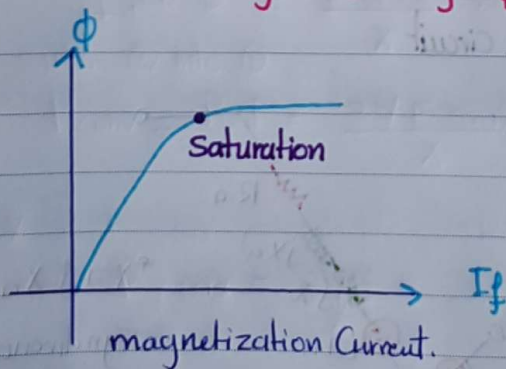
constant \leftarrow \rightarrow generated by I_f




2) Loading Condition

For a given $|V|$ and $|I_a|$ find the required $|E|$ for lagging, Unity and Leading PF.


Lagging (Inductive)

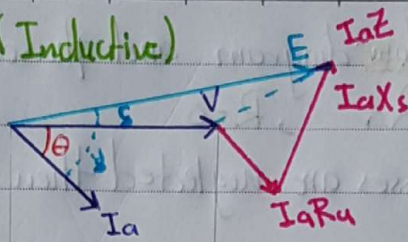

Resistive (Unity PF)

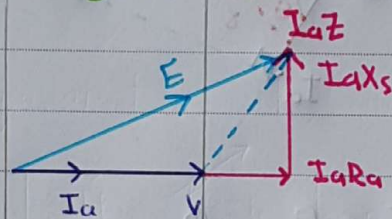


Capacitive (Leading PF)

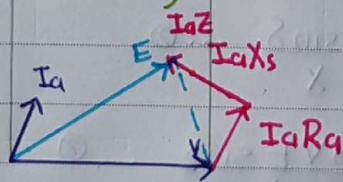

*Power and Torque Relationship of 3-phase Synchronous generator:-

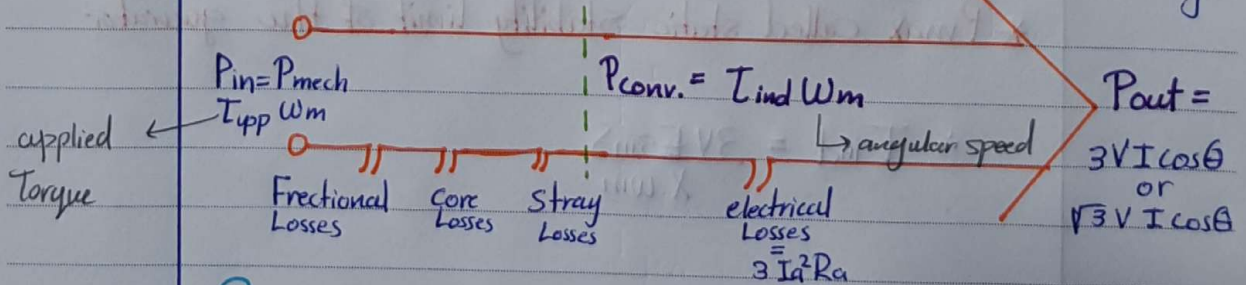
This can be explained and derived in terms of Power flow Diagram



$P_{conv.} \equiv$ Amount of input power which is converted to electrical.

* Using power flow diagram and phasor diagram, Assuming that $X_s \gg R_a$, $R=0$

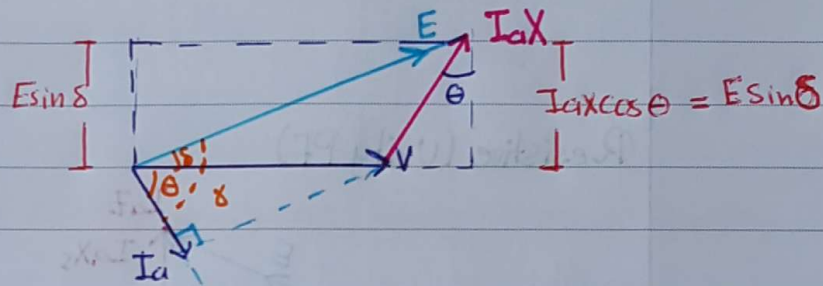\therefore Electrical losses are neglected then $P_{conv} = P_{out}$



$$P_{conv} = P_{out} = 3VI \cos \theta \quad \dots ①$$

From phasor diagram

$$I_a X \cos \theta = E \sin \delta$$

$$I_a \cos \theta = \frac{E \sin \delta}{X} \quad \dots ②$$

sub. ② into ①

$$P_{conv} = P_{out} = \frac{3VE \sin \delta}{X} \quad \dots ③$$

* $P_{out, max}$ is when $\delta = 90^\circ$

$$P_{out, max} = \frac{3VE}{X} \quad \dots ④$$

δ never reach 90°

it's usually $(20^\circ - 30^\circ)$


* P_{max} called static stability limit of the generator

$$\therefore T_{ind} = \frac{3VE \sin \delta}{X \omega_m}$$

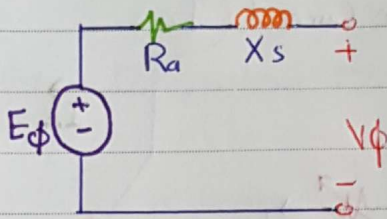***Measurement of Generator Parameters:-**


Objective: To measure R_a and X_s .

Procedure: This can be performed by means of \boxed{OIC} , \boxed{SIC} and \boxed{dc} Tests as follows:-




***Open circuit Test:-**

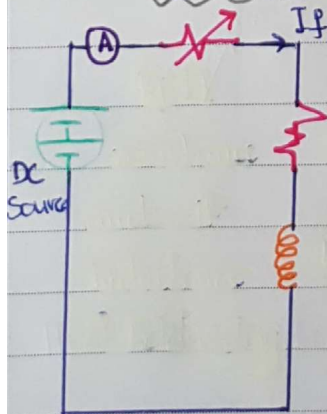1. open circuit The terminals of the armature
2. Run the **rotor** at a constant speed
3. Vary the field current, (I_f) , in steps and take the corresponding Readings of $V\phi$.
4. Plot $V\phi$ vs I_f




Field

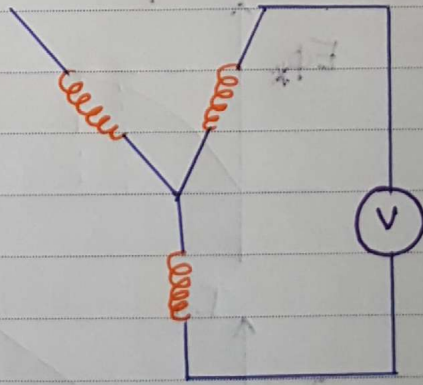




Armature


I_f [A. reading]	$V\phi = \frac{V}{\sqrt{3}}$
I_{f1}	$V\phi_1$
I_{f2}	$V\phi_2$
⋮	⋮

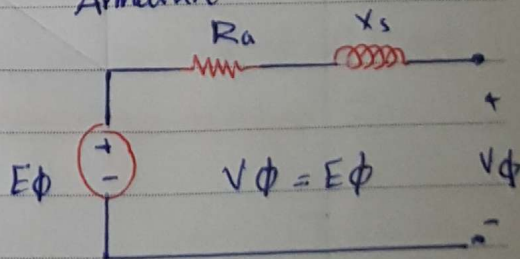

*** Short circuit test :-**

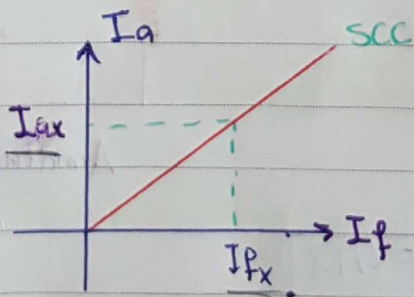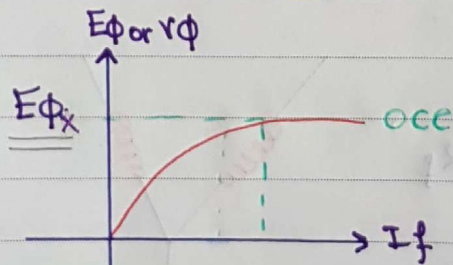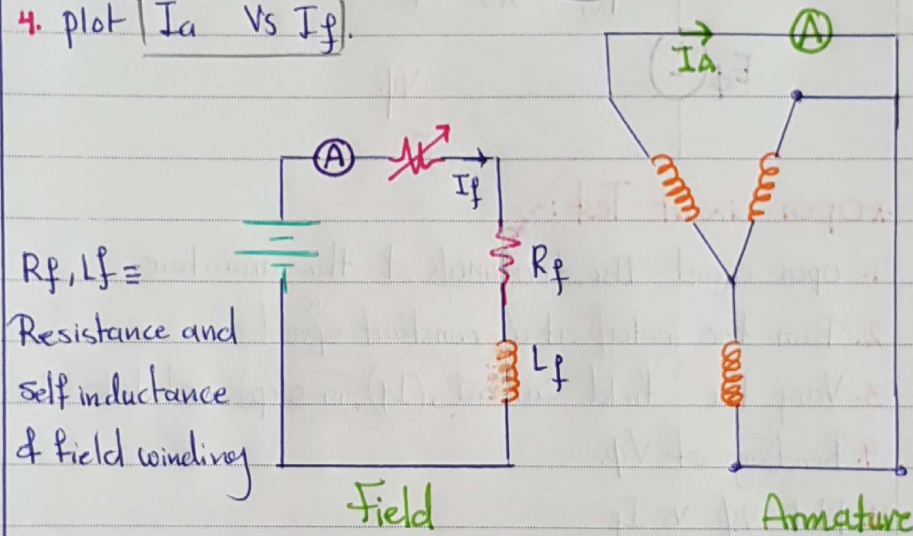1. Short circuit the terminals of the Armature.
2. Run the rotor at a constant speed.
3. Vary the field current (I_f) in steps and take the corresponding Readings of Armature Current (I_a).
4. plot I_a Vs I_f .



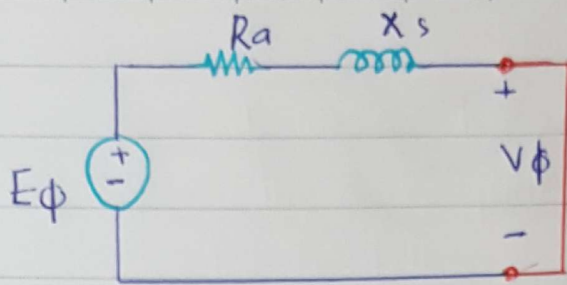


$V\phi = \text{zero in s/c} \therefore$ for a given field current I_f , then from the OCC, one can find the generated voltage $E\phi_x$ and from SCC, one can find corresponding I_{ax} .

$$\therefore \frac{E\phi_x}{I_{ax}} = |Z|, \text{ where } |Z| = \sqrt{R_a^2 + X_s^2} \dots (1) \quad Z = R_a + jX_s$$

* Now if R_a is neglected then $X_s = E\phi_x / I_{ax}$ **Unsl.**

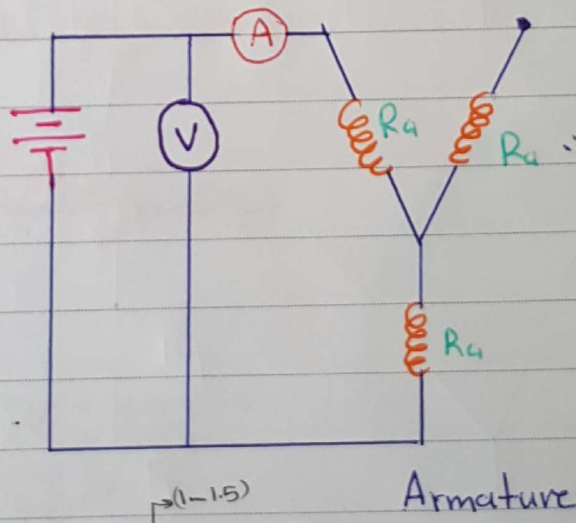* If R_a is not neglected then it can be measured by means of **DC Test** as follows:-



$$\therefore R_A = \frac{1}{2} \frac{\text{Voltmeter Reading}}{\text{Ammeter Reading}}$$

↳ DC resistance

$$\therefore R_{A,ac} = a \text{ factor} * R_{A,dc} \dots (2)$$


* Substitute (2) in (1) to find X_s

* If X_s is calculated a long linear portion of the OCC, it called **Unsat. Synchronous Reactance**.

* **Short circuit Ratio (SCR)** \triangleq Field Current which produces Rated voltage at (O/C) divided by Field Current which produces Rated Armature Current at (S/C)

$$(\text{SCR}) = \frac{I_{fv}}{I_{fI}}$$

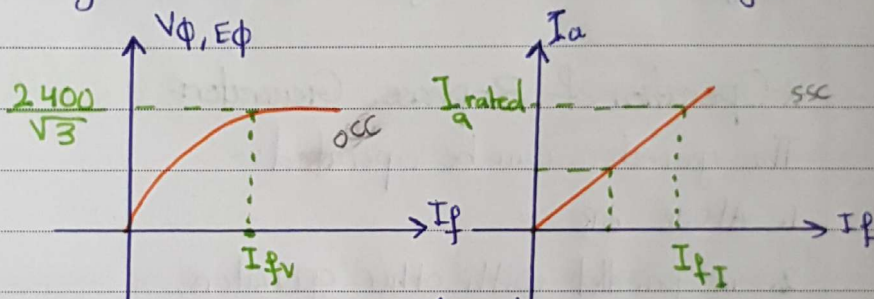* **Illustration** Consider a 9375 kVA, 2 pole, 60 Hz, 2400 V 3 phase generator. The occ and scc are given. ↑
Rated voltage
↓
line voltage



from the occ, it can be found that $I_{fv} = 116 \text{ A}$

$$I_{\text{rated}} = \frac{9375 \text{ k}}{\sqrt{3} \times 2400} = 2255 \text{ A} \quad I_{fI} = 131 \text{ A}$$

$$\therefore \text{SCR} = \frac{116}{131} = 0.89$$

* **Significance of SCR:-**

- $\text{SCR} = \frac{1}{X_s}$... ①

- at short circuit if R_a is neglected then $E\phi = I_a X$

$$\therefore X = \frac{E\phi}{I_a} \dots ②$$

- It was found that $E\phi = 4.44 k_p k_d N \phi_f$

since $\Gamma = R\phi$

mmf \uparrow Reluctance \uparrow Flux

$$E\phi = 4.44 k_p k_d N \frac{\Gamma}{R} f$$

→ constant

$$E\phi = k\Gamma \dots (3) \quad \text{when } k \propto \frac{1}{R}$$

substitute (3) into (2)

$$X = \frac{k\Gamma}{I_a} \dots (4)$$

* Large SCR \rightarrow Smaller $X_s \rightarrow$ smaller $k \rightarrow$ Larger R
 \rightarrow Longer Air gap between stator and rotor \rightarrow Hence
 a larger mmf is required from field windings \rightarrow larger size
 of generator \rightarrow higher cost per **KVA** Rating.

* Operation of 3-phase Generator:-

The generator can be operated:-

1. Alone OR
2. in parallel with other generators.

* **Alone**:- Assume that **1** Rotor running at constant speed (ω constant)

2 I_f is constant, (ϕ constant)

3 R_a is neglected

\therefore Since $E = k\phi\omega$ \therefore E remain **Constant**


Objective:- what will happen to $(V\phi)$? when the load is changed keeping the **power (PF) constant** for the three types Inductive Resistive and capacitive.

* Inductive :-

* let $|I_a|$ increases to $|I_a'|$


then $I_a'x > I_ax$

$\therefore V\phi < V\phi$

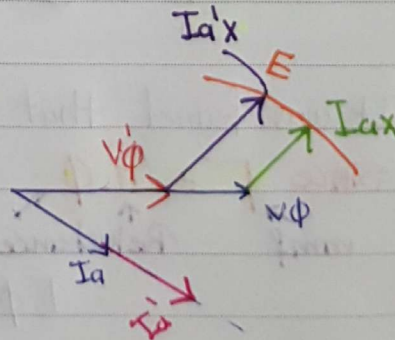


*** Resistive :-**

$V\phi' < V\phi$

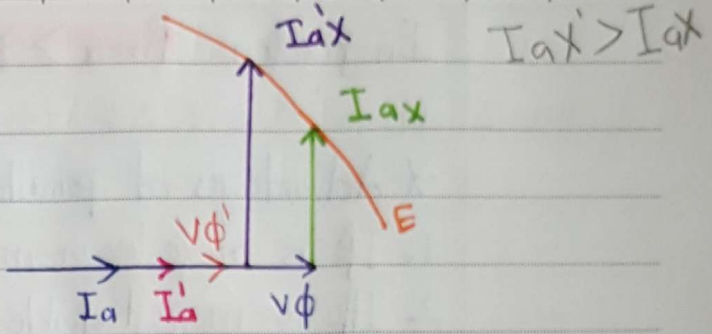

*** Capacitive :-**

$V\phi' > V\phi$

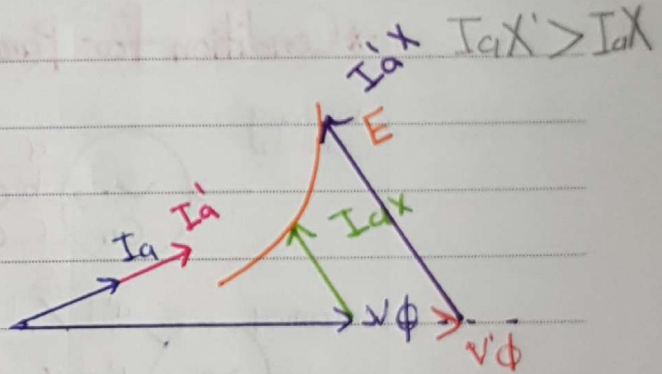


* However in practice $V\phi$ is kept constant, Hence E is changed to achieve that. Since $E = k\phi\omega$

Since ω can not be changed in order to maintain f constant, that E is controlled by changing ϕ , through the adjustment of I_f

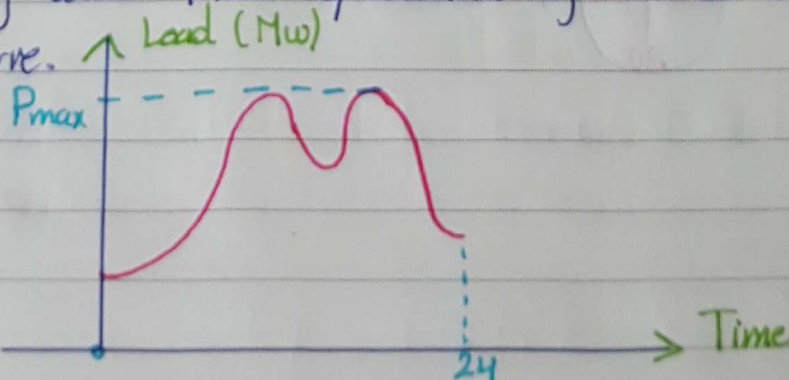*** Parallel operation of generators :-**

- Generator are used to supply a load, and this load is changing with time represented by the so called Daily Load curve.



Load curve

No.

عدد المولدات

إذا خرب واحد
تطبق كل الطاقة

In Jordan $P_{max} > 3000 \text{ Mw}$

1 * 3000 Mw


3 * 1000 Mw

better

* Advantages of parallel operations:-

1. It is more economical.
2. It is more Reliable.

* Condition for Parallel Operations:-

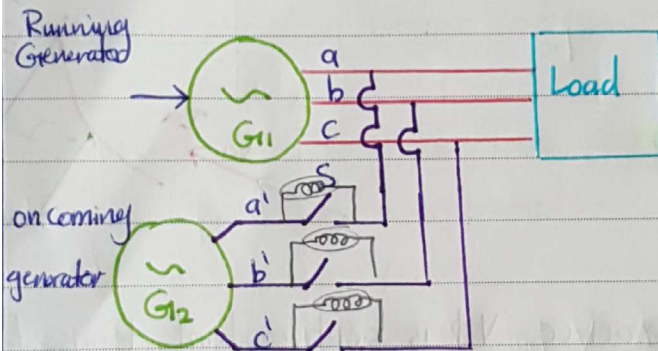

This process is called synchronization.


* what are the conditions to be satisfied before closing the switch

S.

1] G_1 and G_2 should have the same voltage (i.e. magnitude and phase). i.e. $V_{an} = V_{a'n}$, $V_{bn} = V_{b'n}$, $V_{cn} = V_{c'n}$

2] G_1 and G_2 should have the same phase sequence.

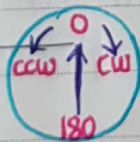3] frequency of G_2 should be slightly higher than that of G_1
 $f_{G_2} > f_{G_1}$



* Procedure of synchronization :-

1] Adjust I_{f2} (ie field current of G_2) until its terminal voltage equal that of G_1

2] check the phase sequence by using :-

A. a small 3-phase Induction motor (مثل التوضيح على الرسم)

OR

B. 3 bulbs method. عشان افقد الازدواج
التقريب

3] Let f_2 to be slightly higher than f_1 , hence her the phase angles of G_2 is changing slowly with respect to G_1 , Then when the phase shift equal to zero, close S.

* phase shift can be checked by :-

1. Synchroscope.


2. 3 bulbs method.

* Relationships between Active Power - Frequency and Reactive Power - Voltage :-

* Relation between P and F :-

Since the Rotor is driven by a prime mover (P_m), then as the load in the generator \uparrow , then the speed of PM \downarrow .

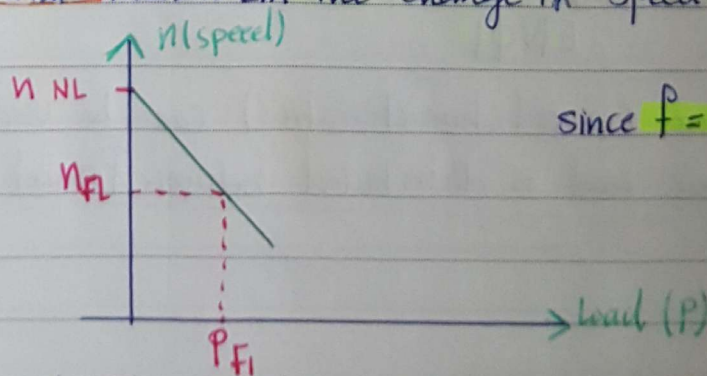
This decreases is usually non-linear. However by using a Governor mechanism the change in speed is made linear.



$$\text{since } f = nP \therefore f \propto n$$


$$\text{Speed droop, } SD = \frac{n_{NL} - n_{FL}}{n_{FL}}$$

Typical values, $SD = (2\% - 4\%)$

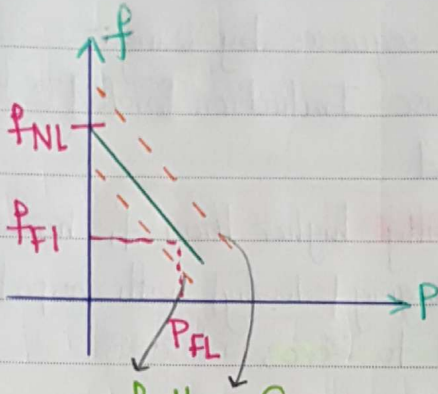

* By means of the Governor one may change the setting of NO-Load point.

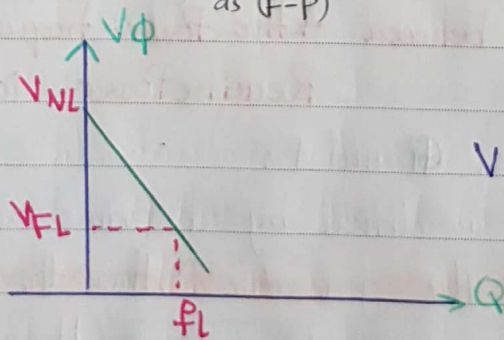* Relationship between ϕ and V As explained before, when $Q \uparrow$ then $V \downarrow$ By using inductive load
Hence the same Relationship exists between V and Q
as $(P-P)$



$$VR = \frac{|V_{NL}| - |V_{FL}|}{|V_{FL}|}$$

$$VR = \frac{|E\phi| - |V\phi_L|}{|V\phi_L|} \times 100\%$$

* These curves (characteristics) can be used to find how a given load is distributed between Parallel generators


* Amount of Load sharing This could be between

1. A Generator and the whole system
- OR
2. 2 parallel Generators


* Procedure It can be solved by means of the Haws diagram as follows

Case II :-

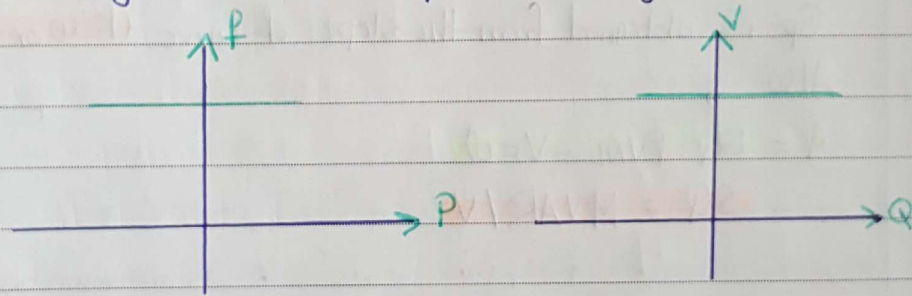The system can be represented by the following characteristics:-




* This is called ∞ system

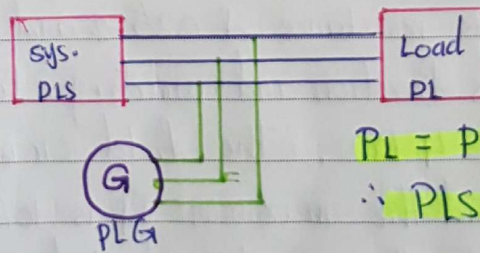


$$P_L = P_{LG} + P_{LS}$$

$$\therefore P_{LS} = P_L - P_{LG}$$

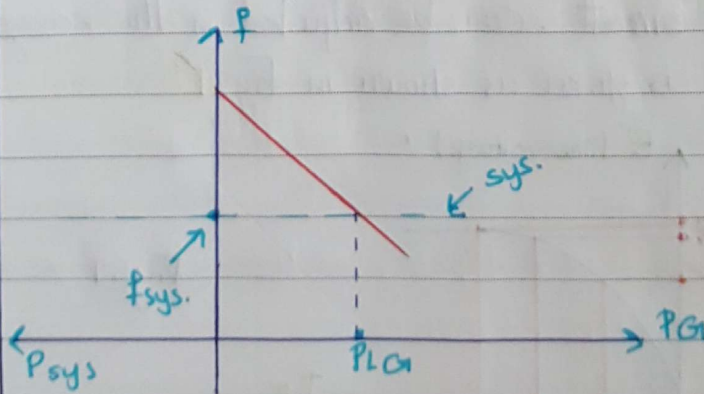

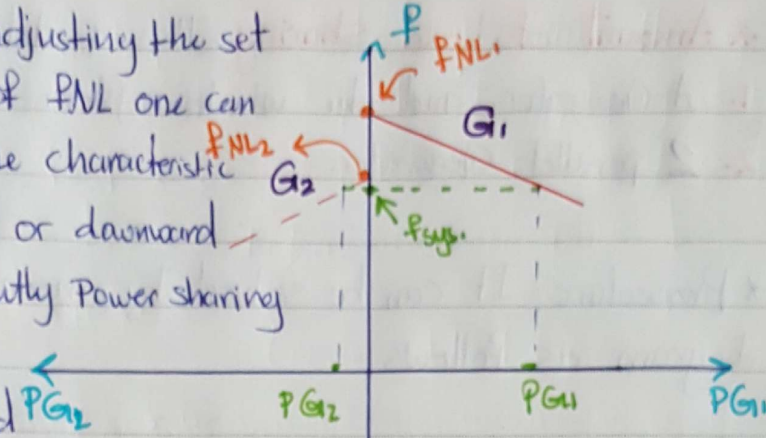* by adjusting the set point of PNL one can shift the characteristic upward or downward. Consequently Power sharing can be controlled



* In general:-

$$P = S_p (f_{NL} - f_{FL} \text{ or } f_{sys})$$

S_p is obtained from the slope of curve (KW or MW) / Hz

Also \rightarrow

$$Q = S_Q (V_{NL} - V_{FL})$$

$$\therefore S_Q = \text{MVAR/V}$$

* Example:- A 480 V, 200 kVA, 0.8 PF lagging, 2-pole, Y-connected synch. generator, has synchronous reactance and armature resistance of 0.25Ω and 0.04Ω respectively. At 60 Hz its friction and windings losses = 6 kW and core losses = 4 kW. The field circuit has dc voltage of 200 V, and the maximum I_f is 10 A. The resistance of the field circuit can be adjusted in the range of (20-200) Ω . The OCC is given as shown in Fig. 1

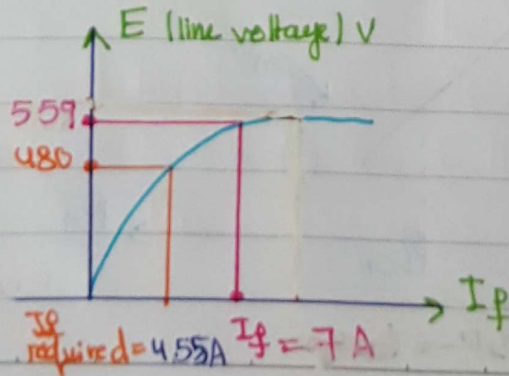



Fig. 1

1] How much I_f is required to generate terminal voltage V_T , equal to 480 V when the generator is running at NO-load.

$$\therefore V_T = E = 480 \text{ V}$$

\therefore by using given OCC, find I_f which correspond to $E = 480 \text{ V}$

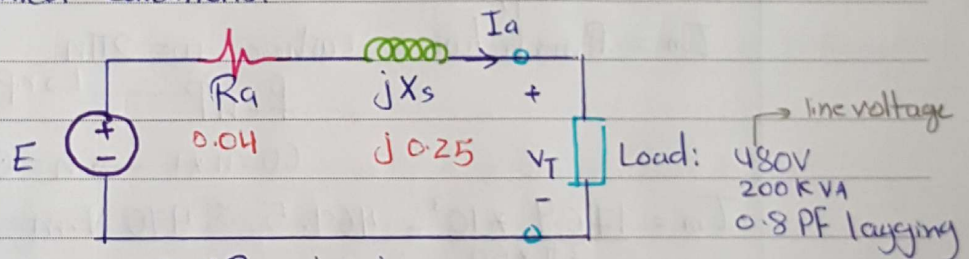2] what is the internal generated voltage of this machine at Rated conditions.



$$E = V_T + I_a(R_a + jX_s)$$

$$I_a = \frac{200 \times 10^3}{\sqrt{3} \times 480} \quad \angle -\cos^{-1}(0.8) \rightarrow \angle -36.87^\circ$$

$V_T = \frac{480}{\sqrt{3}} \angle 0^\circ$

\therefore By substitution

$$E\phi = 322.7 \angle 7.4^\circ$$

$$E_L = \sqrt{3} \times E\phi = 559 \text{ V}$$

3] How much I_f is required to make $V_T = 480$ when the generator is running at rated conditions.

Rated Conditions

V_T	E
(V)	559 (V)

\therefore from open circuit characteristic can be found, $I_f =$

4] How much power and Torque must the generator's Prime mover must be capable of supplying at Rated conditions

$$P_{\text{mech input}} = P_{\text{out}} + \text{electrical Losses} + \text{Core Losses} + \text{Friction Losses}$$

$$200 \times 10^3 \times 0.8 \quad 3I_a^2 R_a = 3(240.6)^2 0.04 \quad 4 \times 10^3 \quad 6 \times 10^3$$

$$T_{\text{mech}} = 176.9 \text{ kW}$$

$$P_{\text{mech}} = T_m \times \omega$$

or
 T_{app}

$$T_m = P_{\text{mech}} / \omega$$

$$\text{where } \omega = 2\pi n$$

$$f = nP$$

→ r.p.s

$$60 = n \times 1 \rightarrow n = 60 \text{ r.p.s}$$

$$T_m = \frac{176.9 \times 10^3}{2\pi \times 60} = 469.5 \approx 470 \text{ N.m}$$

5] find η

$$\eta = \frac{\text{output}}{\text{input}} = \frac{200 \times 10^3 \times 0.8}{176.9 \times 10^3} = 90.4\%$$

* Example:- A 480 V, 200 kW, 2 pole, 3-phase, 50 Hz synchronous generator prime mover has $n_{NL} = 3040 \text{ rpm}$ and $n_{FL} = 2975 \text{ rpm}$

a] Find the SD of this generator

$$SD = \frac{n_{NL} - n_{FL}}{n_{FL}} \times 100\% = 2.18\%$$


b] This generator is connected to other generator with the following Data:-

480 V, 150 kW, 4 pole, 50 Hz with prime mover of $n_{NL} = 1300$, $n_{FL} = 1485 \text{ rpm}$

The Load to be shared between the generator is 200 kW at 0.85 PF lagging.

b.1 Find SD of this generator ← By substitution $SD =$ ^{12.45}

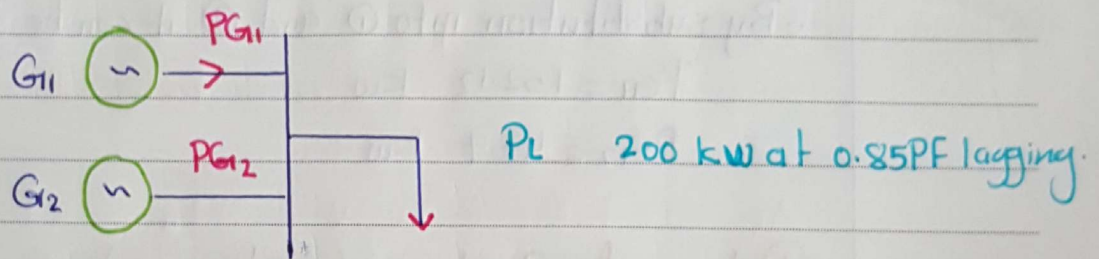b.2 Find the System's Frequency and the amount of Load Sharing



Single-Line Diagram.

$$\therefore P_{G1} + P_{G2} = P_L$$

$$P_{G1} = S_{P1} (f_{NL1} - f_{sys})$$

$$P_{G2} = S_{P2} (f_{NL2} - f_{sys})$$

$$\rightarrow S_{P1} \quad \text{since } f = nP$$

$$f_{NL1} = \frac{3040}{60} \times 1 = 50.67 \text{ Hz}$$

$$f_{FL} = \frac{2475}{60} = 49.58$$

$$S_{P1} = \frac{200}{50.67 - 49.58} = 183.5 \text{ kW/Hz}$$

$$\rightarrow S_{P2}$$

$$f_{NL} = \frac{1500}{60} \times 2 = 50 \text{ Hz}$$

$$f_{FL} = \frac{148}{60} \times 2 = 49.5 \text{ Hz}$$

$$\therefore SP_2 = \frac{150}{50 - 49.5} = 300 \text{ kW/Hz}$$

$$\therefore \underbrace{18.5 (50.67 - P_{\text{sys}})}_{P_{G1}} + \underbrace{300 (50 - P_{\text{sys}})}_{P_{G2}} = 200$$

$$\therefore P_{\text{sys}} = 49.841 \text{ Hz}$$

\(\therefore\) By substitution into ① and ② it can be found:

$$P_{G1} = 152.12 \text{ kW}$$

$$P_{G2} = 47.7 \text{ kW}$$

* Ratings of 3-phase (synchronous) generator: -

- Since the generator is going to be used in a given country when its frequency is specified (i.e. 50 or 60 Hz)
- what type of prime mover to be used (i.e. steam, hydro, gas, ... etc) Then the speed n is fixed.
- Since $E = k\phi\omega$, ϕ can be increased to a certain max. limit and since $\phi \propto I_f$ then here is a limit for I_f (i.e. $I_f \text{ max}$). In order to limit Rotor losses to a certain max. level.

\(\therefore\) There is a limit on E (i.e. E_{max})

\(\rightarrow\) consequently Rated voltage, V_ϕ , is specified

- To limit the heating in the Armature circuit (i.e. $3I_a^2R_a$) Then I_a is set at max. or rated value (i.e. I_{rated})
- Having specified V_ϕ and I_ϕ then apparent power is specified.


$$S = 3 V_\phi I_\phi$$

$$= \sqrt{3} V_L I_L$$

$$AB = I_a X \cos \theta$$

$$BC = I_a X \sin \theta$$

$$AC = I_a X$$

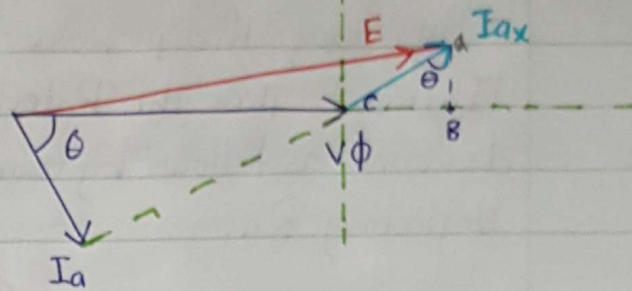

* Introduce perpendicular axis as at the tip of $V\phi$

Objective: To convert phasor diagram into a power diagram, by multiplying voltage by a certain factor.

$$AB \rightarrow I_a X \cos \theta * \frac{3V}{X} = 3V I_a \cos \theta = P$$

$$BC \rightarrow I_a X \sin \theta * \frac{3V}{X} = 3V I_a \sin \theta = Q$$

$$AC \rightarrow I_a X * \frac{3V}{X} = 3V I_a = |S|$$

\therefore Triangle ABC is a power triangle


\rightarrow The new axis become power axis.


\rightarrow Also the origin of the phasor diagram, with respect to origin of power diagram = $-V\phi$

$$\therefore \text{This origin becomes } -V\phi * \frac{3V}{X} = -\frac{3V^2\phi}{X}$$

$$\text{Also } E \rightarrow E = \frac{3V\phi}{X}$$

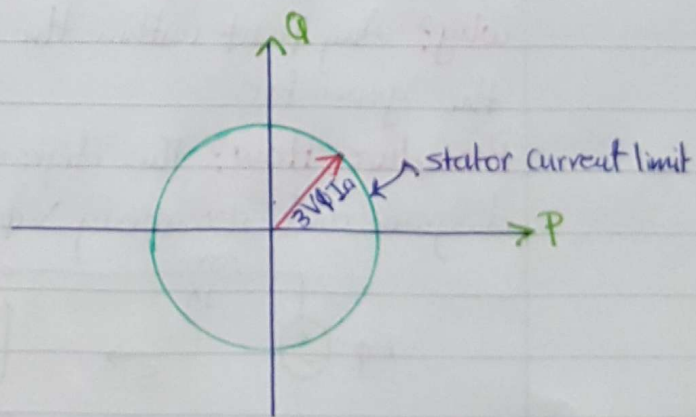So \rightarrow By using the previous information draw on the Power axis, a diagram which take into account the limits on I_a and I_f



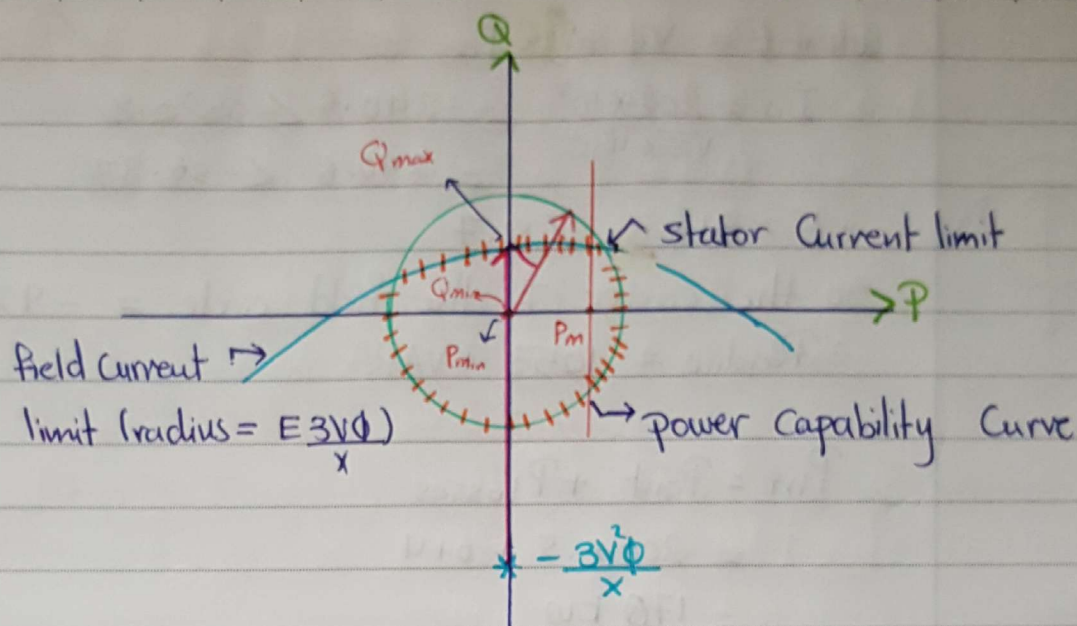

- * any point within the 2 circles is a safe operating point
- * one may add another constraints, for example: the max. power supplied by the turbine, say P_m

$$P_{gmin} \leq P_G \leq P_{gmax}$$

$$Q_{gmin} \leq Q_G \leq Q_{gmax}$$

* **Example:-** A 480 V, 200 kVA, 0.8 PF lagging, 60 Hz 2 pole Y-connected generator, has $X = 0.25 \Omega$, $R_a = 0.04 \Omega$, at 60 Hz it's friction and windings losses = 6 kW it's core losses = 4 kW $V_f = 200$ V, $I_f = 10$ A. Construct the Power Capability Curve.

Stator Circle

Origin = (0,0) center
Radius = 200 kVA

field Circle

Center = $Q = -\frac{3V^2}{X}$
 $V_f = 480$
 $X = 0.25$
Radius = $E * \frac{3V^2}{X}$

where $E = V\phi + jX I_a$

$$I_a = \frac{200 \times 10^3}{\sqrt{3} \times 480} = 240.6 \angle -\cos^{-1} 0.8$$
$$= 240.6 \angle -36.87$$

$$\therefore E = 316.8 \angle 8.7$$

So the center of the field circle = -920.7 kVAR

$$\therefore \text{Radius} = 1053 \text{ kVAR}$$

$$P_m = P_{out} + P_{losses}$$

$$= 200 \times 0.8 + 6 + 4$$

$$= 170 \text{ kW}$$

* Pitch, distribution and winding Factor:-

It was found that

$$E_{\phi} = 4.44 (k_p k_d) N \phi f$$


k_w
 \rightarrow distribution factor
 \rightarrow Pitch factor

- winding factor:- $k_w = k_p k_d$

These are defined as follows:-

$$k_p \triangleq \sin\left(\frac{P}{2}\right)$$

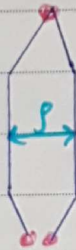$P \equiv$ coils Pitch in electrical degree




Fractional Pitch coil \equiv its Pitch is $<$ Pole's Pitch

$$k_d \triangleq \frac{\sin\left(\frac{n\delta}{2}\right)}{n \sin\left(\frac{\delta}{2}\right)}$$


$\delta \equiv$ space between adjacent slots
 slots per phase belts

$n \equiv$ number of

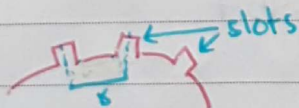

of phase or groups = $3 \times P$

$P \equiv$ number of poles

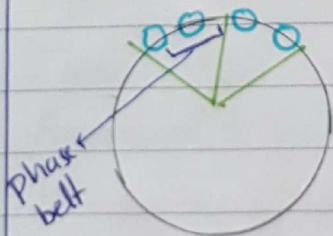

* Example:- 13.8 kV, 60 Hz, 12 Poles, 3-phase Y generator

has:- 180 stator slots

Double layer winding

8 turns/coil

The coil pitch = 12 slots

→ Find k_p , k_d and k_w .

$$P = 12 \text{ slots}$$

$$\text{Pole Pitch} = \frac{180}{12} = 15 \text{ slots}$$

$$\therefore \rho = \frac{12}{15} \times 180^\circ = 144^\circ$$

$$\therefore k_p = \sin\left(\frac{144^\circ}{2}\right) = 0.95$$

$$\gamma = \frac{180^\circ}{15} \left(\frac{\text{Pole Pitch}}{\text{slots/Pole pitch}} \right) = 12^\circ$$

$$n = \frac{180 \text{ slots}}{3 \times 12} = 5$$





$$\therefore k_d = \frac{\sin(5 \times 12)}{5 \times \sin\left(\frac{12}{2}\right)} = 0.957$$

$$k_w = k_p k_d = 0.95 \times 0.957$$

1. I_f is supplied from external sources, hence it is called Separately Excited DC machines.
2. Self excited DC machines In this case the field windings are connected to Armature windings, In order to utilize the Residual magnetism in the Field poles, Connection is made through Brushes and commutator segments.

* According to the method of connection there are 3 types of self excited DC Machines:-

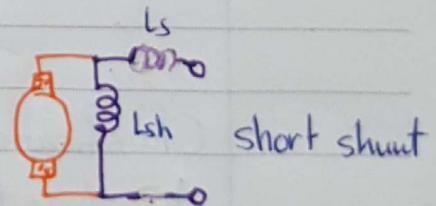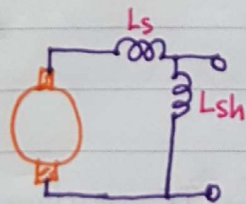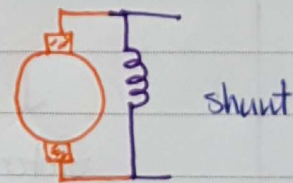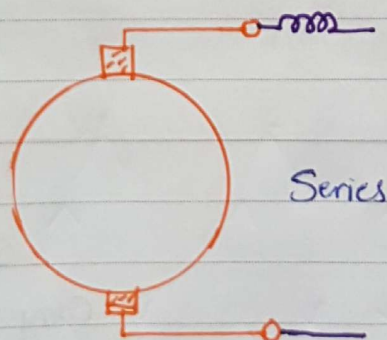1. Series DC Machines.
2. Shunt DC Machines.
3. Compound DC Machines.
 - a. long shunt
 - b. short shunt



* Also Compound can be classified into:-

- 27 ← A. **Commutative Compound** Series field aid shunt field.
- 28 ← B. **Differential Compound** Series field opposes shunt field.

* Operation:-

Operation of DC Machines was explained Before, during the Fundamental of AC Machines:-


1. An applied mechanical input to the rotor generated an internal sinusoidal voltage, and by using Commutator and Brushes this AC voltage converted to DC voltage. (i.e DC generator action)
2. An applied DC current to Armature (through Brushes and commutator) a torque was produced (i.e DC Motor action)

* Commutation:-


It is the process of converting the internal generated AC voltage to DC voltage by using Commutators and Brushes.

* Procedure:-

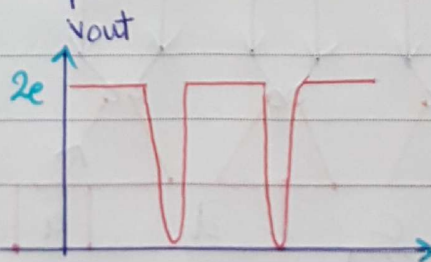1. Previously one coil with a single turn was considered. The Brushes output:-


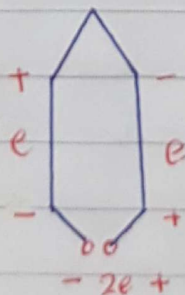
$$e = B l v = \text{voltage per conductor}$$



* The dc output can be improved by increasing number of Armature coils.

2. Let the Armature has 4 coils, with a double layer winding commutator segments.


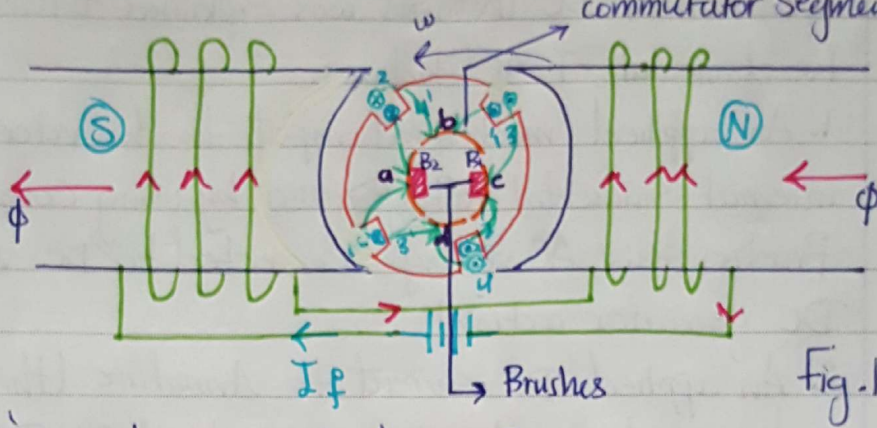


Fig. 1


- 1, 2 → b
- 3, 2' → c
- 4, 3' → d
- 1, 4' → a
- 1, 3', 4', 2 → ⊗
- 4, 2', 1', 3 → ⊙


* these are 2 parallel paths

* Fig. 1 can be Redrawn as follows:-

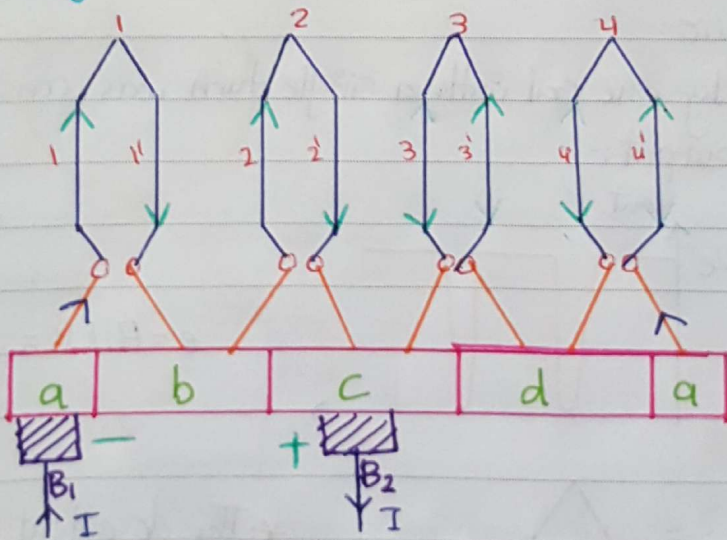

Commutator System.

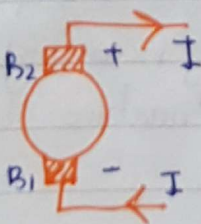

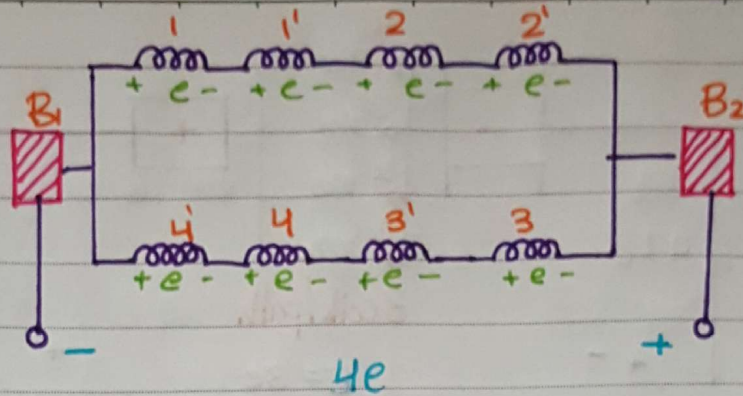

$1-1'-2-2' \equiv \text{path}$

$4'-4-3'-3 \equiv \text{path}$

* There are two types of Armature Windings:-

- Lap winding
- wave winding

* Number of parallel paths = a

For lap winding, $a = mp$

For wave winding, $a = 2m$

$P \equiv$ number of Poles

$m \equiv$ multiplicity of winding

$\equiv 1$ for simplex winding

$= 2$ for duplex winding


$= 3$ for Triplex winding

Illustration For 12 slots, double layer winding, number of coils = 12


* if the machine has 4 poles.

\therefore for simplex lap winding, $a = 1 \times 4 = 4$

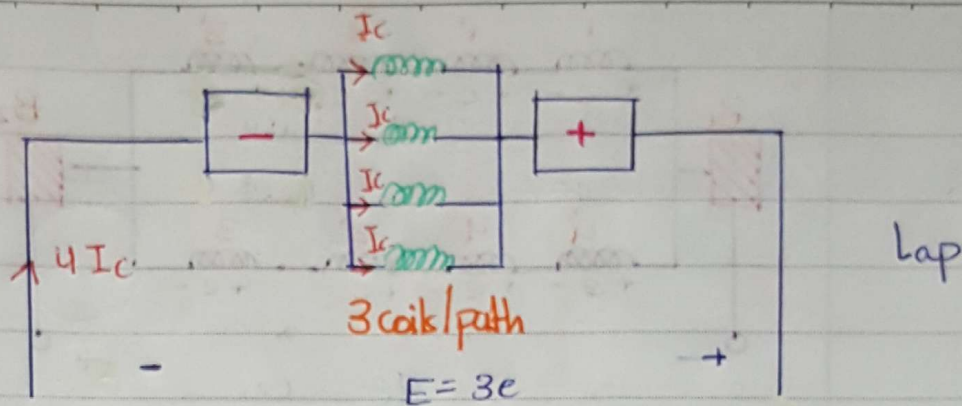for simplex wave winding, $a = 2 \times 1 = 2$



$$P = 3e \times 4 I_c = 12eI_c$$

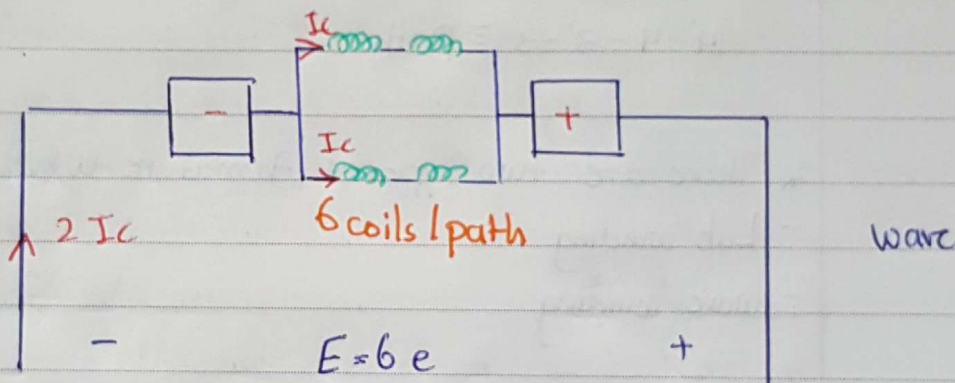

$$P = 6e \times 2 I_c = 12eI_c$$

* if voltage / coil = e * if Coils Current = I_c

* Expression for the generated voltage, E . (i.e. voltage across Brush)

if e_c = voltage generated per conductor. = $B \cdot l \cdot v$

* Single turn has 2 conductors.

if C = Number of Armature coils,

N \equiv Number of Turns per coil.

Z \equiv Total number of Armature conductors.

$$Z = 2 * N * C$$

$$E = \frac{Z}{a} * e_c = \frac{Z}{a} * B l v$$

$$E = \frac{Z}{a} B l v = \frac{Z B l \omega r}{a}$$

if flux per pole = ϕ

Number of poles = P

$$\therefore B = \frac{P \phi}{\text{Area}} = \frac{P \phi}{2 \pi r l}$$

$$E = \frac{Z P \phi}{2 \pi r l} \frac{l \omega r}{a} = \frac{Z P \omega \phi}{2 \pi a}$$

But $\omega = 2 \pi n$ $n = \text{Rotation speed (rps)}$


$$\therefore E = \frac{Z P \phi n}{a}$$

* For a given generator Z , P and a are constants.

$$\therefore E = k \phi n \quad k = \frac{Z P}{a}$$


* Comment 1:- For a constant speed (n)

$$\therefore E \propto \phi$$

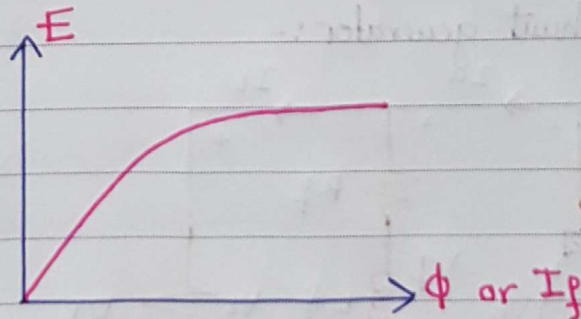

OR
magnetization Curve
No-load characteristic of DC generator

* Equivalent Circuit :-

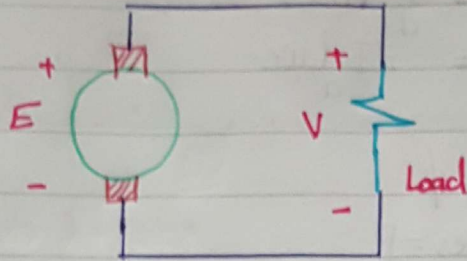


$V =$ Terminal or Load voltage.

Relation between E and V depends on the type of generator.

* For Example :-

① Separately excited :-

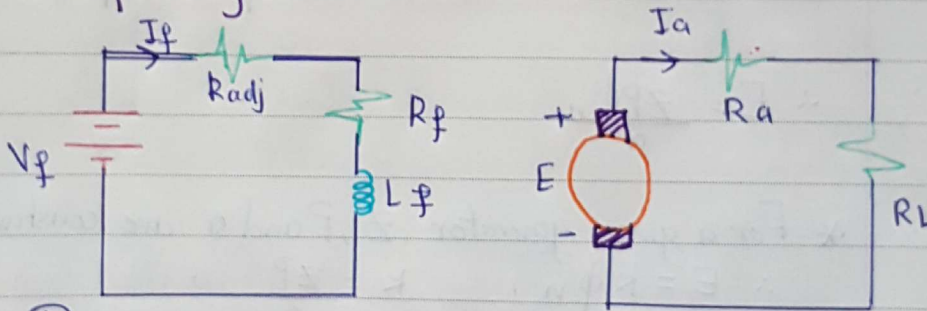


$R_a \equiv$ Armature Circuit Resistance.

$$\therefore E = I_a R_a + V$$

$I_a \equiv$ Armature Current.

② Shunt generator :-

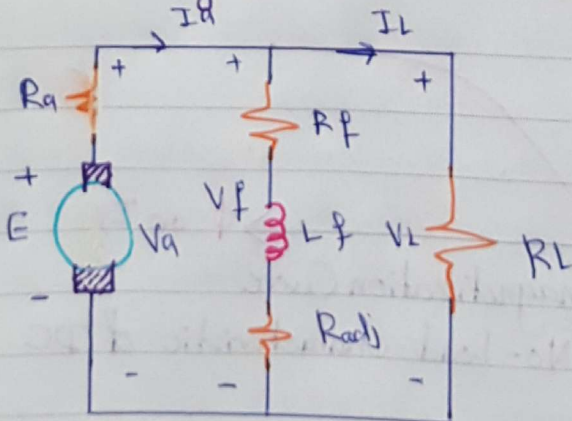


$$\therefore V_L = V_a = V_f$$

$$I_a = I_f + I_L$$

$$\therefore E = I_a R_a + V_a$$

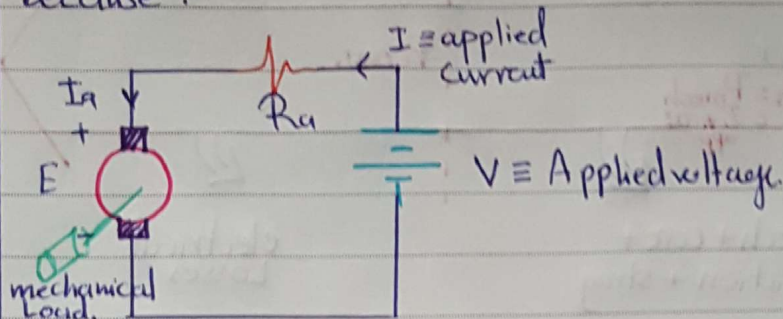*** Note :-** E in the case of DC motor is called Back emf, because :-



E opposing applied voltage V

$$\therefore V = E + I_a R_a$$

*** Developed Torque By DC motor :-**

let $T_c \equiv$ Torque developed by a conductor $= B I_c l r$
 $I_c \equiv$ conductor current

\therefore Developed Torque, $T = T_c Z$

$$\therefore T = B I_c l r Z = \frac{P\phi}{2\pi l r} * \frac{I_a}{a} * l r * Z$$

$$\therefore T = \frac{P\phi I_a Z}{2\pi a}$$

\rightarrow for a given motor P, Z and a are constant


$$\therefore T = k \phi I_a$$

$$k = \frac{P Z}{2\pi a}$$

*** Note :-** in the case of generator T is called T_{ind} or
 retarding Torque

$\omega \rightarrow$

***Power flow diagram:-**

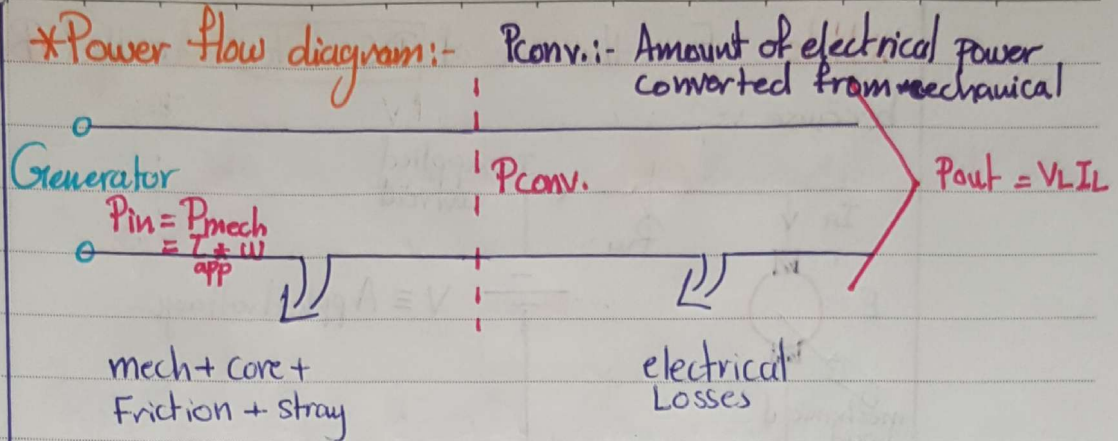


Various Types of DC Motors

Objective:

To find their voltage and Current Relationships:-

Sep. excited

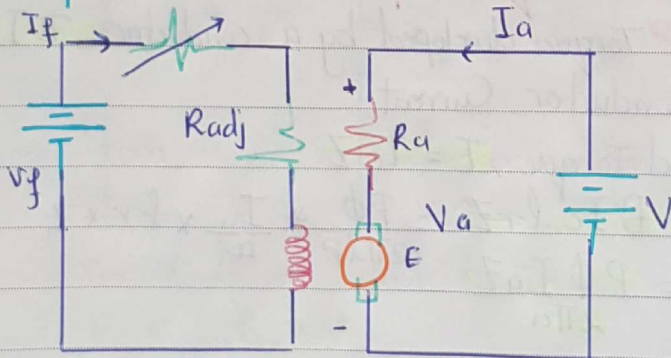

$V_f \equiv$ Applied field voltage

$I_f \equiv$ field current

$R_f \equiv$ field circuit Resistance

$V \equiv$ Applied voltage to Armature.

$I_a \equiv$ Armature current

$E \equiv$ Back emf


$V_a \equiv$ Armature Terminal voltage.

$$I_f = V_f / R_f$$

$$V = E + I_a R_a$$

$$V = V_a$$

Shunt

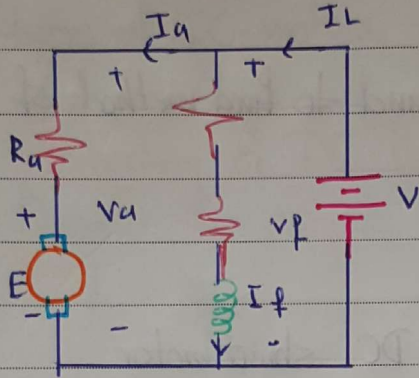


$$V = V_f = V_a$$

$$I_L = I_f + I_a$$


Series

Series field

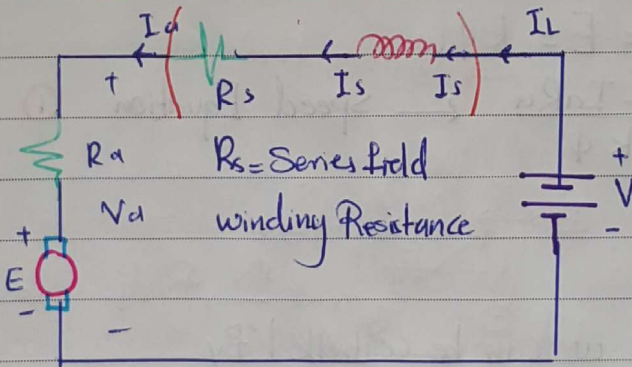

$R_s =$ Series field winding Resistance

Compound

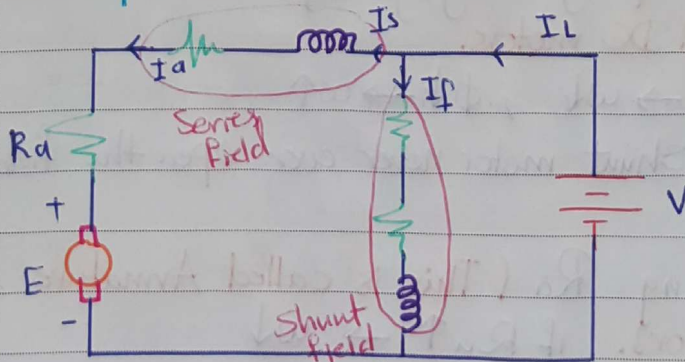

Long Compound DC motor

$$I_s = I_a$$

$$I_L = I_f + I_a$$

$$V = I(R_s + R_a) + E$$

* Speed Equation of DC Motors:-

Objective

To find such equation and to find method of controlling its speed

Procedure

Consider for Example a DC shunt motor

$$E \triangleq k \phi \omega$$

$$V - I_a R_a = E = k \phi \omega$$

$$\therefore \omega = \frac{V - I_a R_a}{k \phi} \quad \text{Speed Equation (1)}$$

applied voltage \leftarrow V \leftarrow $I_a R_a$ \leftarrow Amature Resistance \rightarrow

flux \rightarrow $k \phi$ \rightarrow Field Current \rightarrow Radj. \rightarrow ϕ

\therefore From (1) ω can be controlled By

1. Varying V (if $V \uparrow \rightarrow \omega \uparrow$)
2. Varying ϕ by changing I_f . This is called field controlled DC motors.

* if $\phi \uparrow \rightarrow \omega \downarrow$, $\phi \downarrow \rightarrow \omega \uparrow$

\rightarrow For shunt motor never ever open the field circuit suddenly.

3. Changing R_a (This is called Armature Controlled DC motor). if $R_a \uparrow \rightarrow \omega \downarrow$

\rightarrow most widely used are 1. and 2.

*The same conclusions can be applied to the other types of DC motors.

*Starting of DC Motors:-

Consider for example DC shunt motor:-

$$I = \frac{V - E}{R_a}$$

* Initially at starting because of the Inertia of the Rotor the motor does not rotate, Hence initially $E = k\phi\omega = 0$
 $\therefore I_{\text{starting}} = \frac{V}{R_a}$ which is much greater than Rated I_a .

\therefore **AT Starting:** I_a should be limited by using starting Resistance in series with R_a .

*Characteristics of DC motors:-

This gives Relationship between its 2 outputs:- ω and T

Procedure:-

$$E = k\phi\omega$$

$$E = V - I_a R_a = k\phi\omega$$

$$\therefore \omega = \frac{V - I_a R_a}{k\phi} \quad \dots \textcircled{1}$$


$$\text{But } T = k'\phi I_a$$

$$\therefore I_a = \frac{T}{k\phi} \quad \dots \textcircled{2}$$

Sub. 2 into 1


$$\omega = \frac{V}{k\phi} - \frac{R_a T}{(k\phi)^2}$$

← speed
→ Torque

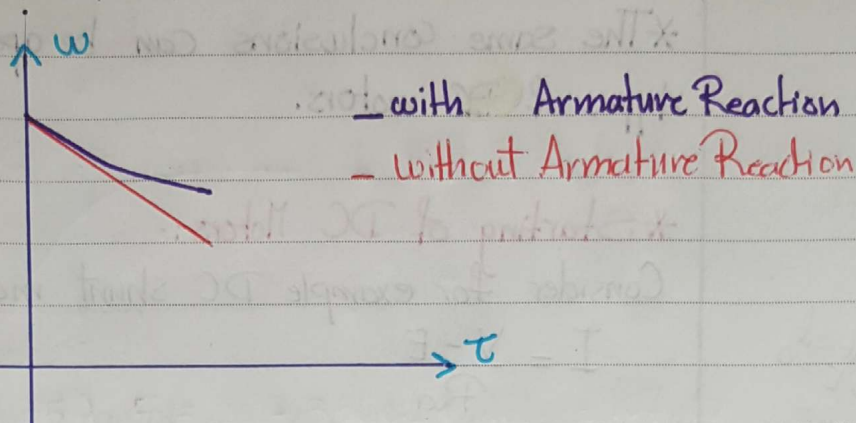

* Methods of Reducing or Eliminating Armature Reaction

1] Compensating Winding

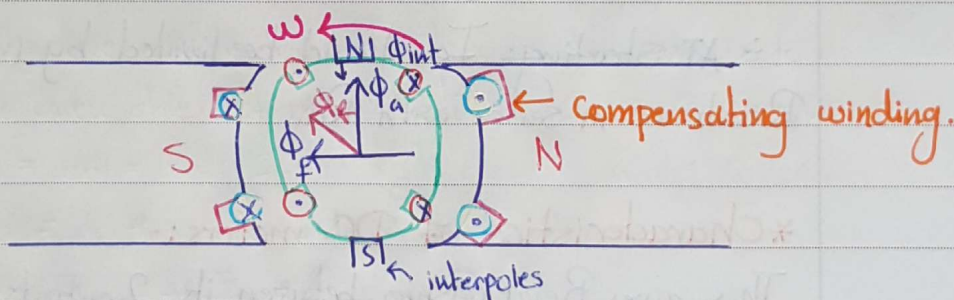

DC Motor

* The Compensating windings are connected in Series with Armature, in such a way that flux cancels the armature flux.

OR


2] Using Interpoles

→ Polarity of Interpoles:-

In the case of motor it's equal to that to the previous main pole.

In the case of generator it's equal to the coming main pole.

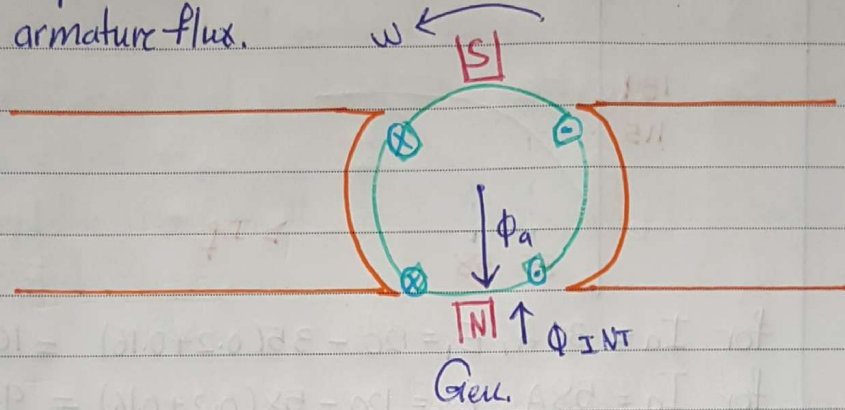
* Interpoles are introduced in order to produce a flux to cancel the armature flux.




* Example:- A 7.5 hp, 120V, Series dc motor has $R_a = 0.2 \Omega$ and $R_{se} = 0.16 \Omega$. At full load the current input is 58A at the rated speed of 1050 rpm. The core losses are 200 watt and the mech. losses are 240 watt at full load. Assume the mech. losses vary as the cube of motor's speed, where core losses are constant. Given in the magnetization Curve at $n = 1200$ rpm, from which

I_f (A)	E (V)
35	115
58	134

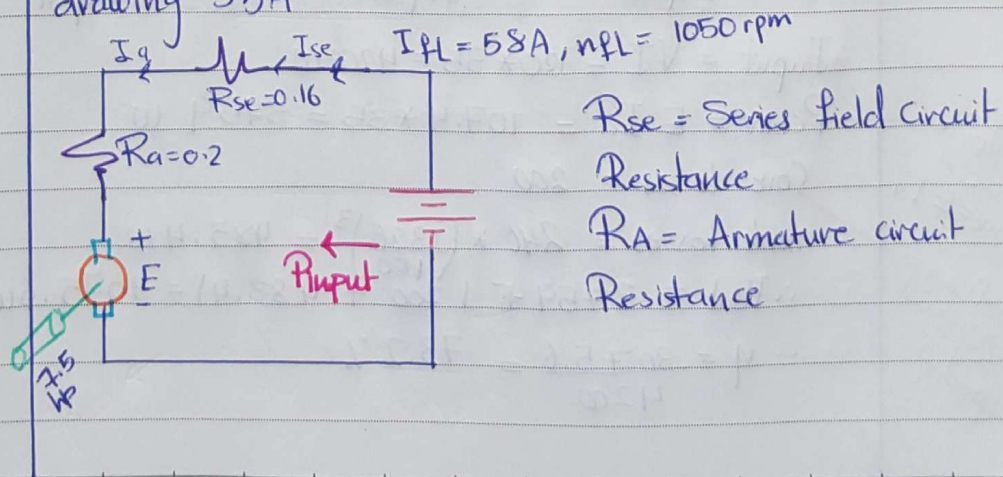→ Find the speed and efficiency of the motor if it is drawing 35A



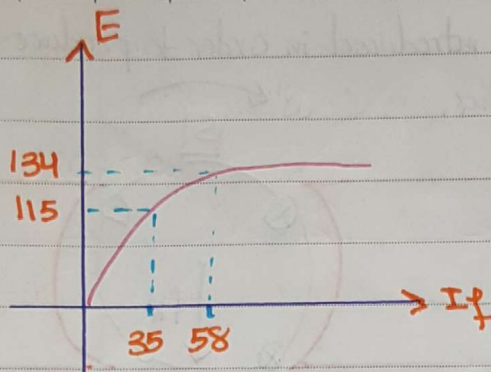

$$\text{for } I_a = 35 \text{ A, } E_1 = 120 - 35(0.2 + 0.16) = 107.4 \text{ V}$$

$$\text{for } I_a = 58 \text{ A, } E_2 = 120 - 58(0.2 + 0.16) = 99.1 \text{ V}$$

Since $E = k\phi n$

$$\therefore \frac{E_1}{E_2} = \frac{k\phi_1 n_1}{k\phi_2 n_2} \quad \text{①} \quad n_1 \equiv \text{required speed at 35 A}$$

$$n_2 = 1050 \text{ rpm}$$

Objective now is to find $\phi_1 \rightarrow$ This can be found from the given data of magnetization curve at $n = 1200 \text{ rps}$

$$E_1' = 115 = k\phi_1 1200$$

$$E_2' = 134 = k\phi_2 1200$$

$$\therefore \frac{E_1'}{E_2'} = \frac{115}{134} = \frac{\phi_1}{\phi_2} \quad \text{②}$$

Sub. ② in ① $\rightarrow n = 1326 \text{ rpm}$

$$\eta = \frac{\text{output}}{\text{Input}} = \frac{\text{Input} - \text{losses}}{\text{Input}} = \frac{P_{\text{conv}} - (\text{mech} + \text{core})\text{losses}}{\text{Input}}$$

$$\text{Input} = VI = 120 \times 35 = 4200 \text{ W}$$

$$P_{\text{conv}} = E I_a = 107.4 \times 35 = 3759 \text{ W}$$

$$\text{Core losses} = 200$$

$$\text{mech losses} = 240 \times \left(\frac{1326}{1050}\right)^3 = 483.4 \text{ W}$$


$$\therefore P_{\text{out}} = 3759 - (200 + 483.4) = 3075.6 \text{ W}$$

$$\therefore \eta = \frac{3075.6}{4200} = 73.2\%$$

* **Example:** when connected to a source of Rated voltage, a 25 hp, 230V shunt motor draw 6.1A at no-load. The field current is 1A at no-load at a speed of 1300 rpm.

$$R_a = 1 \Omega$$

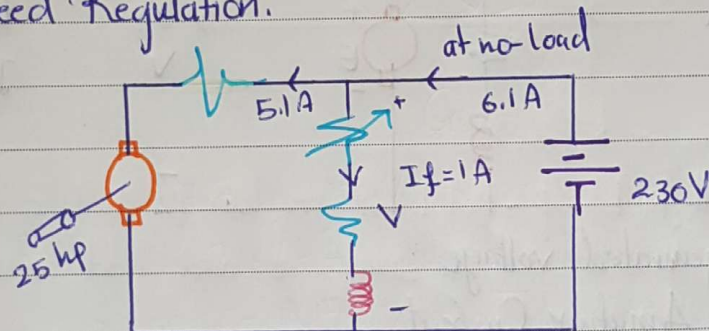1. Find the speed of the motor when $I_a = 80 \text{ A}$ (rated value).
2. Speed Regulation.



$$E = V - I_a R_a$$

$$k\phi n = V - I_a R_a$$

$$n = \frac{V - I_a R_a}{k\phi}$$

$$\therefore \frac{n_1}{n_2} = \frac{V - I_{a1} R_a}{V - I_{a2} R_a}$$


$$\frac{1300}{n_2} = \frac{230 - 5.1 \times 1}{230 - 80 \times 1} \rightarrow 867 \text{ rpm}$$

$$\text{Speed Regulation} = \frac{n_{nl} - n_{fl}}{n_{fl}} = \frac{1300 - 867}{867} \times 100\% = 50\%$$

DC generators:-

Voltage - Current Relationship.

Sep. excited

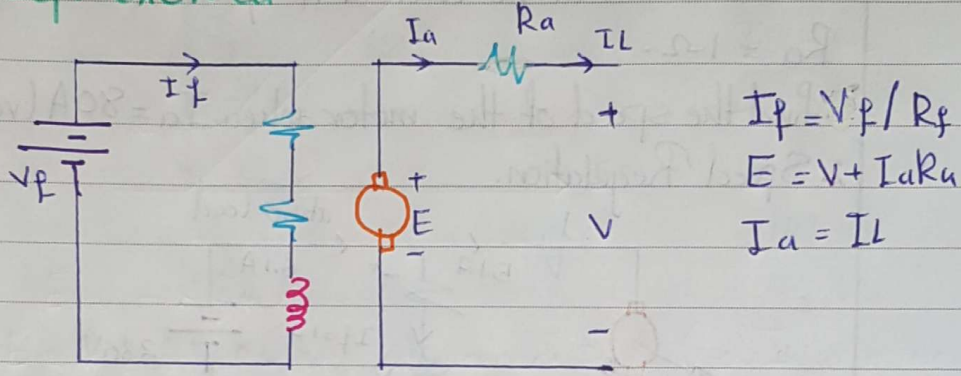


$$I_f = V_f / R_f$$

$$E = V + I_a R_a$$

$$I_a = I_L$$

- $E \equiv$ generated voltage
- $I_a \equiv$ Armature Current
- $V_f \equiv$ field voltage
- $I_f \equiv$ Field Current
- $I_L \equiv$ line or load Current

Shunt

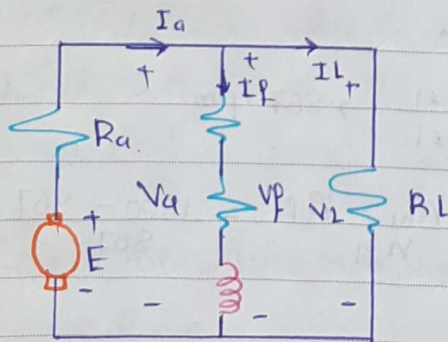


$$I_a = I_f + I_L$$

$$V_a = V_f = V_L$$

$$E = V_a + I_a R_a$$


Series

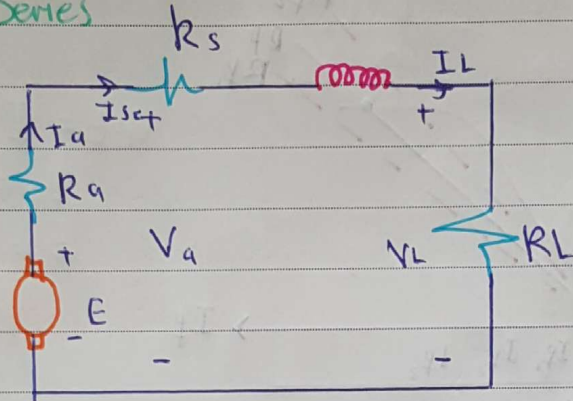

$$I_a = I_{se} = I_L$$

$$E = V_a + I_a R_a$$

Compound

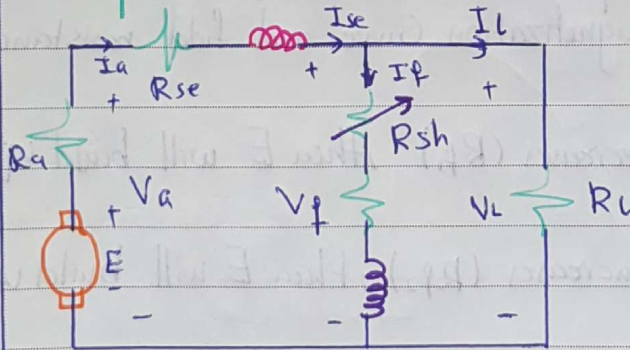

$$I_a = I_{se} = I_f + I_L$$

$$V_L = V_f$$

$$E = I_a R_a + V_a$$


$$-V_a + I_{se} R_{se} + V_L = 0$$

Long shunt

Build-up of voltage in self excited generator

The generation of voltage depends on the Existence of Residual Magnetism in the Pole.


Consider for example a shunt generator.

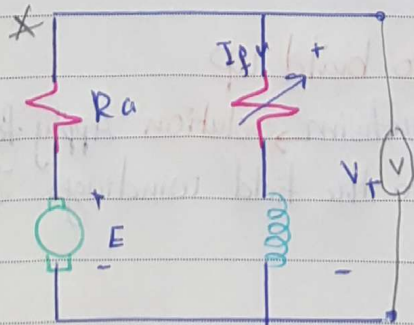

$$I_f = \frac{V_T}{R_f}$$

$$V_T = E - I_a R_a$$

$$I_f = \frac{V_T}{R_f}$$

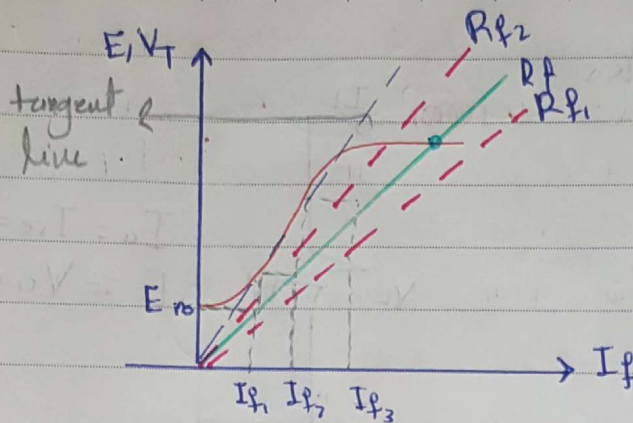

$$E_{res} = k \phi_{res} N$$

E will build up until it reaches point (i.e. Intersective between magnetization Curve and field resistance line)

- * If R_f decreases (R_{f1}), then E will build up to higher value.
- * If R_f Increases (R_{f2}), then E will build up to lower value.

→ If R_f is increase to a higher value, then the generator may fail to build up. This is called the **Critical field resistance (R_{fc})**

* R_{fc} is tangent to magnetization Curve.


* Causes of failure to build up

1. lack to Residual Magnetism → **Solution** Apply for a while and external dc current to the field windings. This is called "Flashing Out"

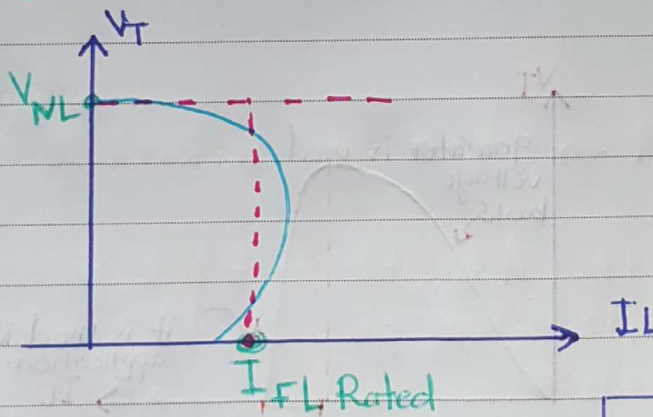2. Field windings connection are in such a way that I_f cancels ϕ_{res} . → **Solution** Reverse the Connections
3. $R_f >$ critical field resistance (e.g. o/c in the field windings)
4. o/c in the Armature windings

* **Load characteristic of shunt generator :-**

→ **Objective:** to find Relationship between V_T and I_L




$$I_a = I_f + I_L$$


$$V_T = E - I_a R_a$$

$$I_f = V_T / R_f$$

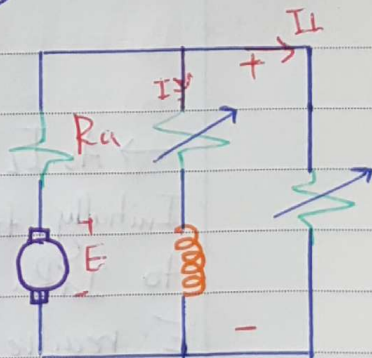
$$E = k\phi\omega \quad \phi \propto I_f$$



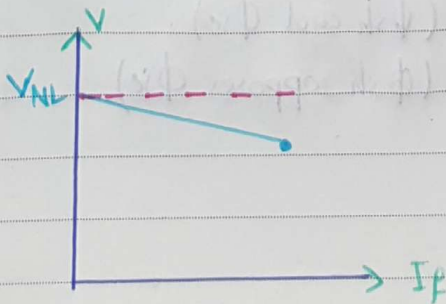$I_L \uparrow \rightarrow I_a R_a \uparrow \rightarrow V_T \downarrow \rightarrow I_f \downarrow \rightarrow \phi \downarrow \rightarrow E \downarrow$
 after a certain loading point V_T is going to collapse



* Series Generator R_s, L_s

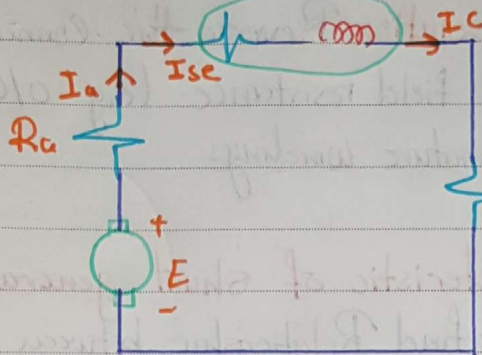


$$+ V_T = E - I_a(R_a + R_s)$$

$$I_a = I_L = I_{se}$$

$$E = k \phi n$$

$$\phi \propto I_{se}$$

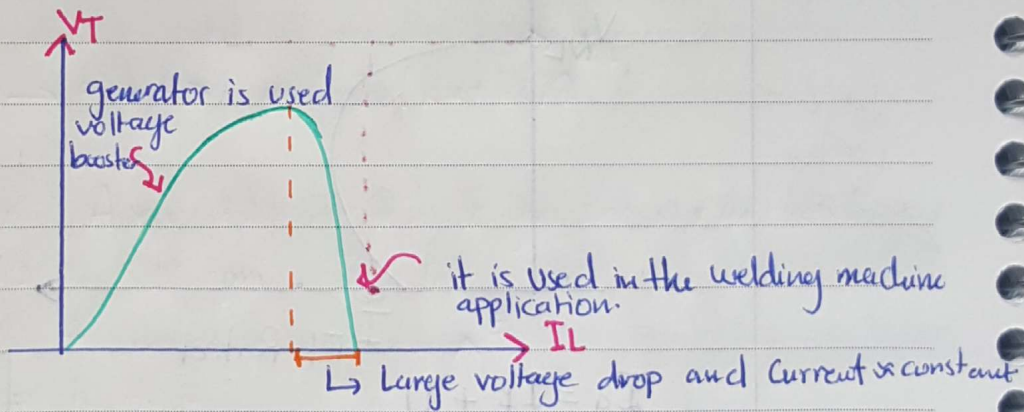


→ As $I_L \uparrow$ ($I_L = I_a = I_{se}$) → $E \uparrow$ and $I_a R_a \uparrow$ → However Initially the Increase in E is greater than Reduction due to $I_a R_a$, Consequently V_T is going to increase. → when E reaches saturation value, then after that the increase in $I_a R_a$ will be greater than increase in E

* Compound Generator:-

- Cumulative (ϕ_{sh} and ϕ_{se})
- Differential (ϕ_{sh} opposes ϕ_{se})

1. Cummulative

Consider Long Shunt Comp. Generator

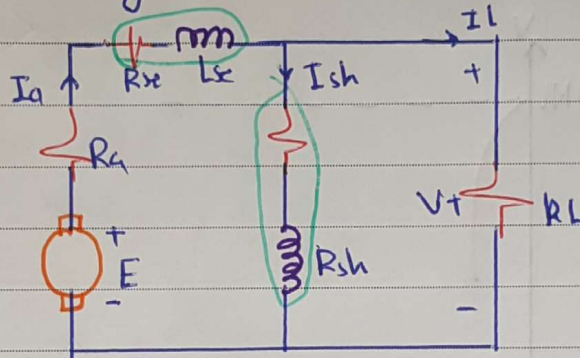


$$V_T = E - I_a(R_s + R_a)$$

$$I_a = I_L + I_{sh}$$

$$I_a = I_{sc}$$

Two mmf :- shunt $I_{sh} N_{sh}$
Series $I_{se} N_{se}$
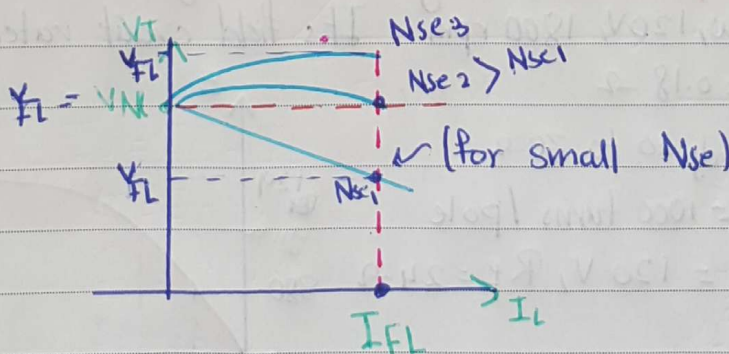
$$E = k(\Phi_{sh} + \Phi_{se}) \times n$$




$$N_{se3} > N_{se2} > N_{se1}$$

→ Depending on the Number of turns of Series Field winding one may obtain :-

- ① Under Compound
- ② Flat Compound
- ③ Over Compound

2. Differential

$$E = k(\phi_{sh} - \phi_{se}) n$$

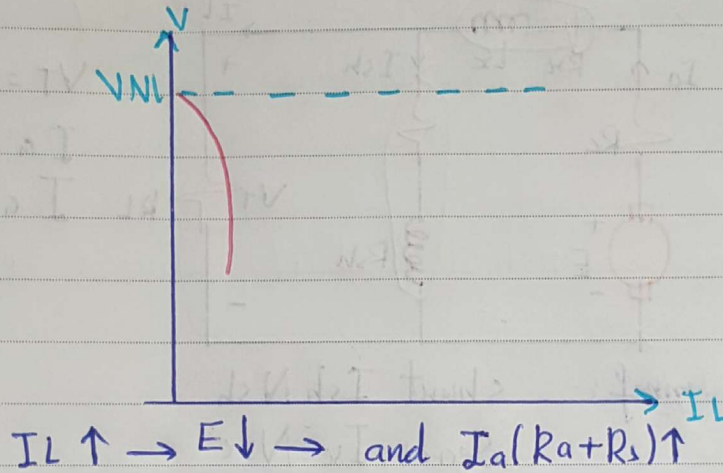



*Example:- A separately excited dc generator is rated at:-
6 kW, 120V, 1800 rpm. Its field circuit rated at 5A

$$R_a = 0.18 \Omega$$

$$R_{f \text{ adj}} = 0 \text{ to } 30 \Omega$$

$$N_f = 1000 \text{ turns / pole}$$

$$V_f = 120 \text{ V}, R_f = 24 \Omega$$

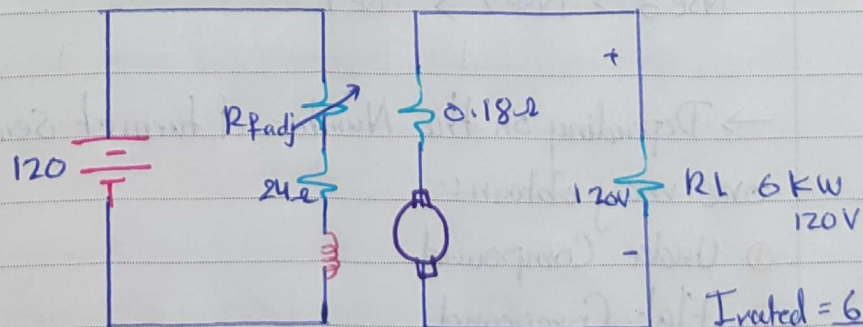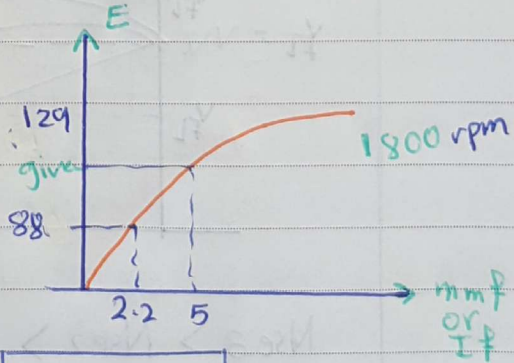

$$I_{\text{rated}} = \frac{6 \times 10^3}{120} = 50 \text{ A}$$

a. If generator operating at no-load what is the range of voltage adjustments that can be made or achieved by changing R_{adj}

$$R_{adj}=0, I_f = \frac{120}{24} = 5 \text{ A} \rightarrow 5 \times 1000 = 5000 \text{ A-t}$$

$$R_{adj} = 30 \Omega, I_f = \frac{120}{24+30} = 2.2 \rightarrow 2.2 \times 1000 = 2200 \text{ A-t}$$

b. If R_{adj} is allowed to vary from $(0 \rightarrow 30) \Omega$ and generator speed allowed to vary from $(1500 - 2000) \text{ rpm}$ what are the max. and min. no-load voltages?

Assuming ϕ to be constant, $E = kn$

$$\frac{E_1}{E_2} = \frac{n_1}{n_2} \rightarrow E_2 = E_1 \frac{n_2}{n_1}$$

$$\text{for } 1500 \text{ rpm, } E_{\min} = 88 \frac{1500}{1800} = 73.3 \text{ V}$$

$$E_{\max} = 129 \frac{1500}{1800} = 107.5 \text{ V}$$

$$\text{for } 2000 \text{ rpm, } E_{\min} = 88 \frac{2000}{1800} = 97.8 \text{ V}$$

$$E_{\max} = 129 \frac{2000}{1800} = 143.3 \text{ V}$$