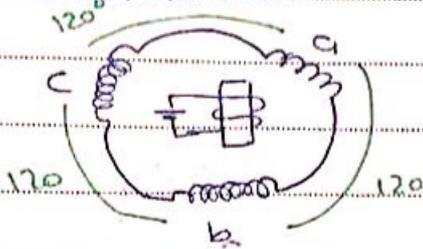



* Topics of synch Gen:-

- Construction:-



Spatial distribution

DC source: excitation

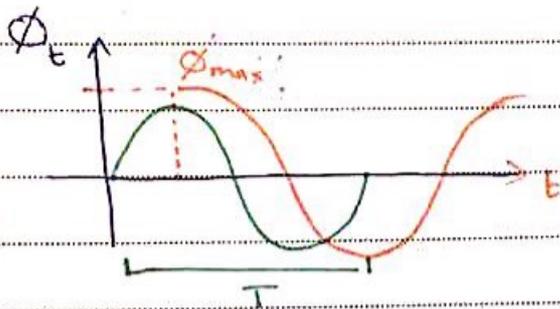

- Principles:-

- 1] moving charges generator magnetic fields
- 2] Faraday's law $e = -N \frac{d\phi}{dt}$


$$\phi = \phi_m \sin(\omega t) \quad (\text{wb}) \Rightarrow \text{unit}$$

$$e = N \phi_m \omega \cos(\omega t) = E_m \cos \omega t \quad (\text{V})$$

$$E_{rms} = \frac{E_m}{\sqrt{2}} = \frac{N \phi_m \omega}{\sqrt{2}} = \frac{2\pi f N \phi_m}{\sqrt{2}} = 4.44 f N \phi_m \quad (\text{approx})$$

$$\mu \propto \phi$$



$$\mu = \mu_0 \mu_r$$

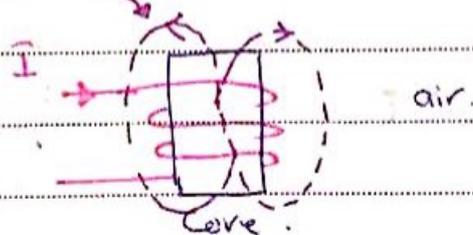

$$e_a = E_m \cos \omega t$$

$$e_b = E_m \cos (\omega t - 120^\circ)$$
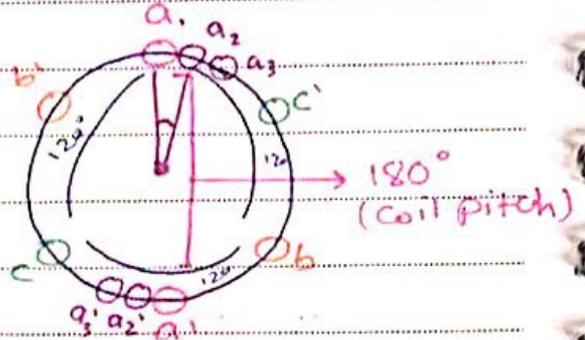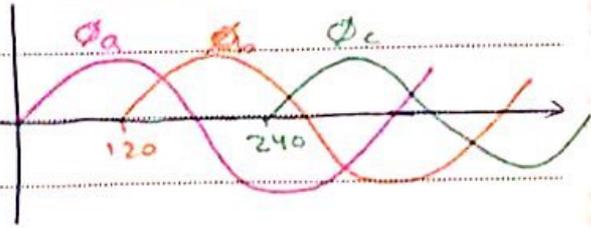
$$e_c = E_m \cos (\omega t + 120^\circ)$$



* To increase ϕ we have some space so we can
 1) increase # of slots.

if we have 30 slot then:

→ 10 slot / phase and 120° between slots.




2) have them parallel in the core



"لا تتركوا عيني قلوبكم انما لادعوا لهدى الله واولئك هم السالكين"



* 2-poles machine:

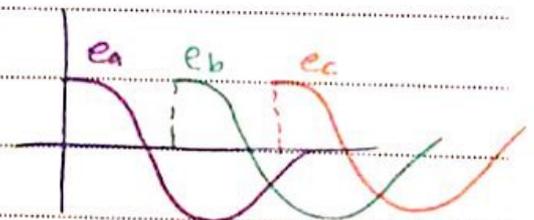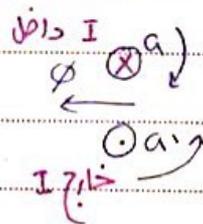
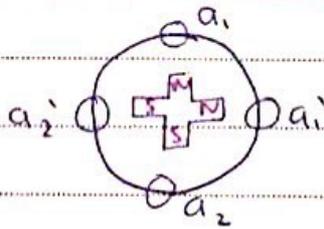


for 2 poles # of electric cycle = # of mech cycle

$$n_s = \frac{120}{P} f$$

P	$f = 50$	$f = 60$
2	3000	3600
4		
6		
8		
10	6000	7200

Synch Gen:-

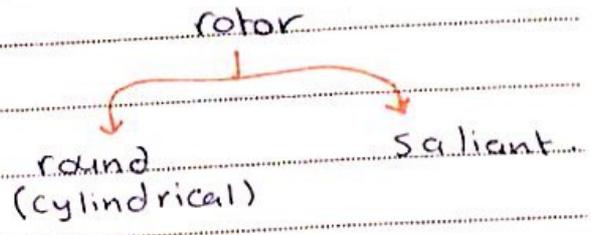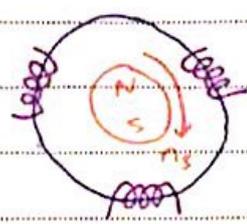


Prime-mover is driven "synch. speed" $n_s = \frac{120f}{P}$

P = poles


Steam turbines (thermal power plant)

P	n_s (rpm)	
	F = 50	F = 60 Hz.
2	3000	3600
4	1500	1800
6	1000	1200
8	750	900
10	600	720
12	500	600

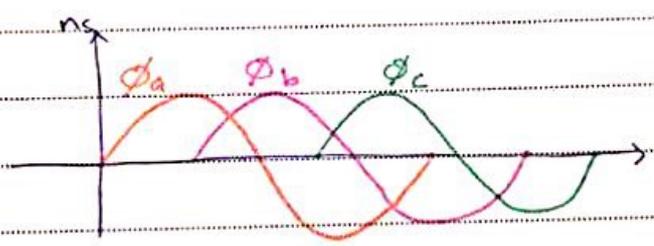


* Construction of rotor &

[1] cylindrical

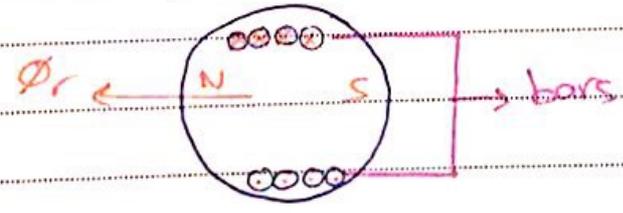


[2] salient rotor:-

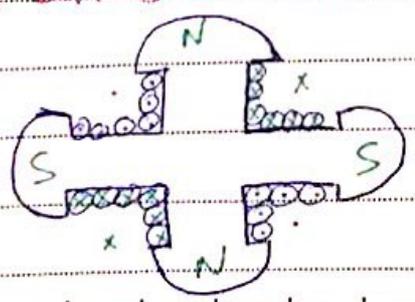

used with slow driven Gen.

[3]

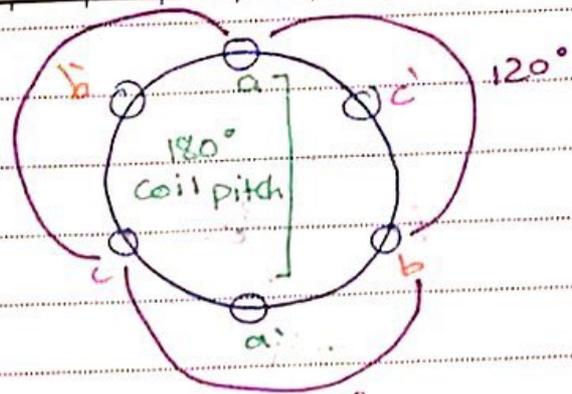for 2 pole machine.
 one mech cycle \rightarrow one electrical cycle




$$\Phi_m = \Phi_e \Rightarrow$$

$$f_m = f_e$$


50 Hz elec.

120°
 \downarrow
 mech. phase angle

50 Hz mech

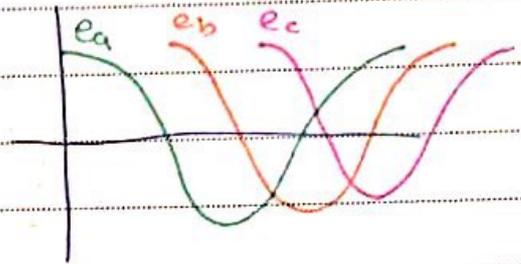

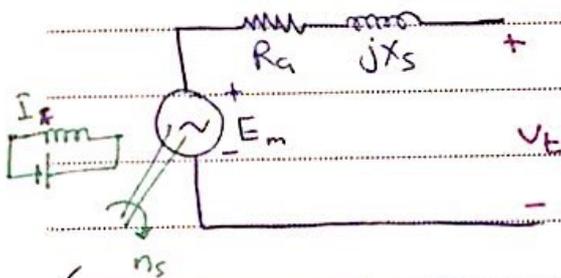* Parameter calculations of sench (m/G) :-




* induced e we need:
 Speed \leftarrow Flux

- ① o/c test
- ② SIC test
- ③ DC Resistance test


Single phase equivalent ckt:-

① O/C test :-

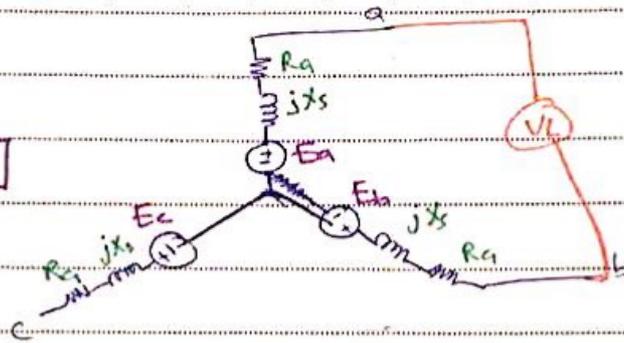

~~at rated speed~~


$n = n_s$

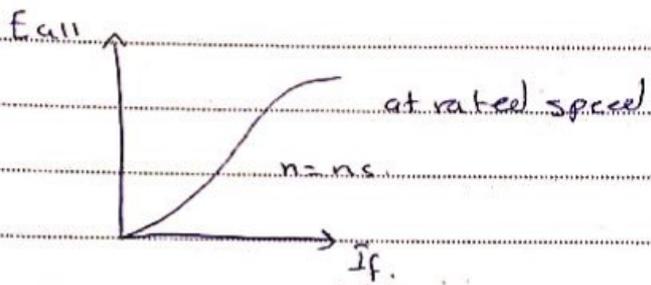


$E = 4.47 F N \Phi_m$

$I_f \propto \Phi_f$

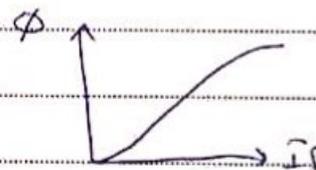
$E \propto \Phi$
 $\Phi \propto I_f$
 $E \propto I_f$




② S/C test :-

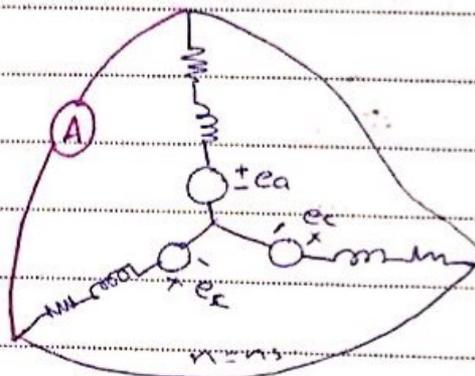

$I_{sc} \propto I_f$

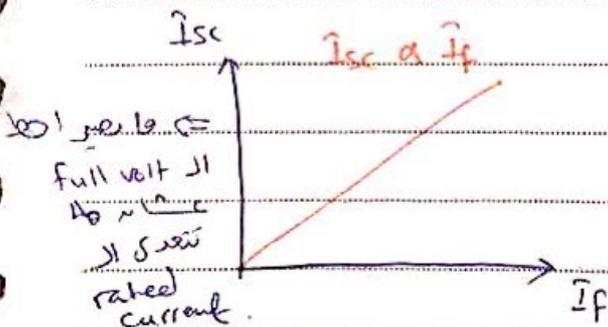

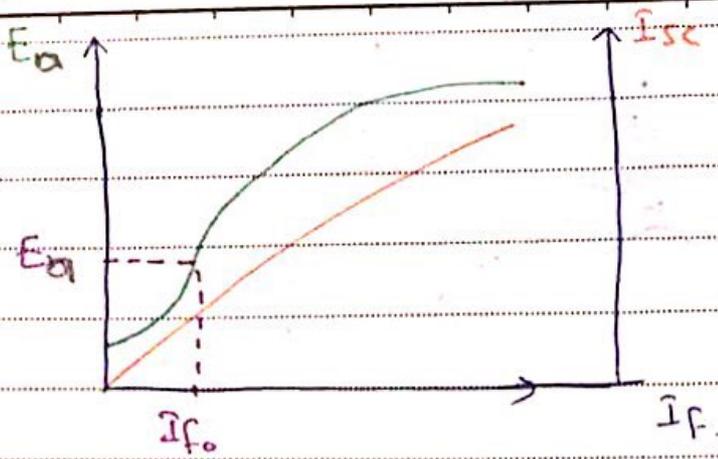

$$|Z_s| = \frac{|E_{aph}|}{I_{sc}}$$


$$|Z_s| = \sqrt{R_a^2 + X_s^2}$$

③ DC resistance test

$$\frac{V_{dc}}{I_{dc}} = 2 R_{dc}$$


$$R_{dc} = \frac{1}{2} \frac{V_{dc}}{I_{dc}}$$

ohmic resistance

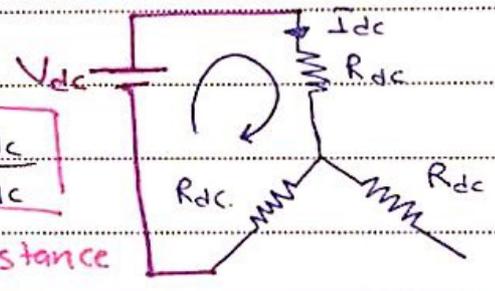


$$R_{eff} = R_a = (1.1 - 1.8) R_{dc}$$

$$X_s = \sqrt{Z_s^2 - R_a^2}$$



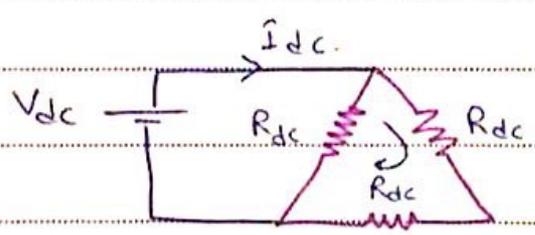


⇒

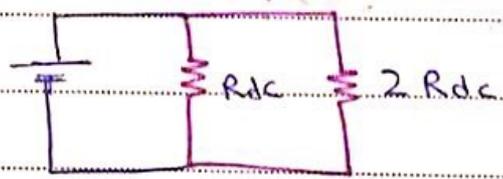



$$R_{dc} = \frac{V_{dc}}{I_{dc}} \times \frac{3}{2}$$

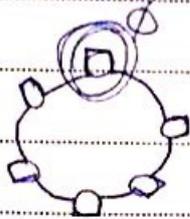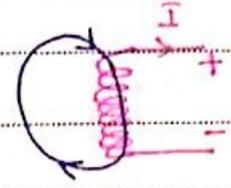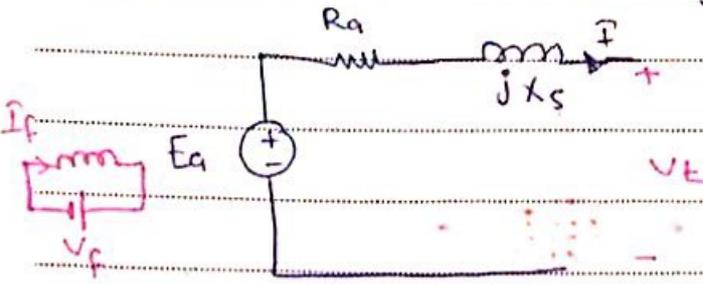under load condition E is different from V_t it cannot be measured directly.



jX_s : Synch reactance.


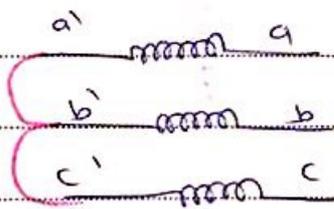
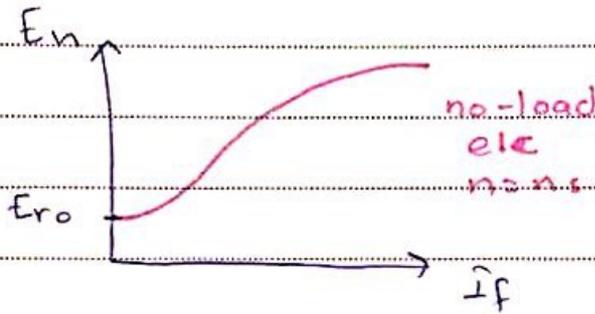
$$V = L \frac{di}{dt} = \omega L I_m \cos \omega t$$



Y-connection

$$V_{LL} = \sqrt{3} V_{Ln}$$



$$V_L = \sqrt{3} V_{ph}$$

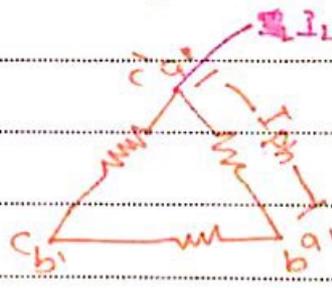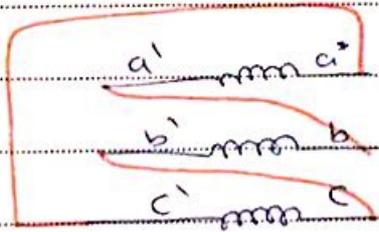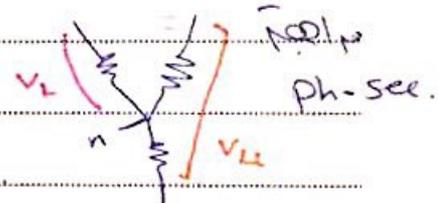

Δ connection

$$I_{ph} = I_L / \sqrt{3}$$

$$V_{ph} = V_L$$

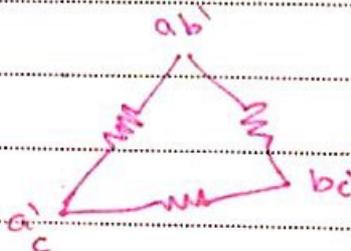
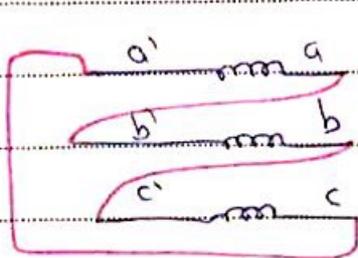


1 Hz = 1 cycle / s \Rightarrow rpm = f_m x 60

3000 rpm \Rightarrow 50 Hz elec


50 Hz mech

4-poles Gen:-

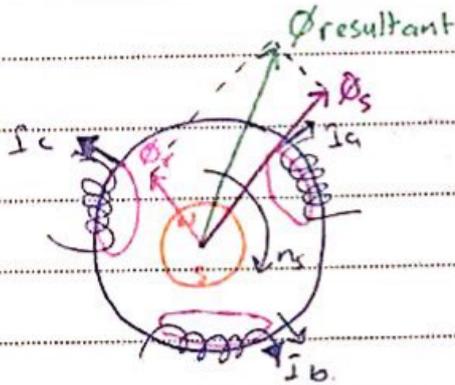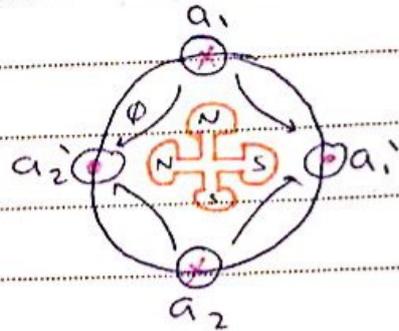

- 2 flux \rightarrow ① stator flux.
- \rightarrow ② main flux

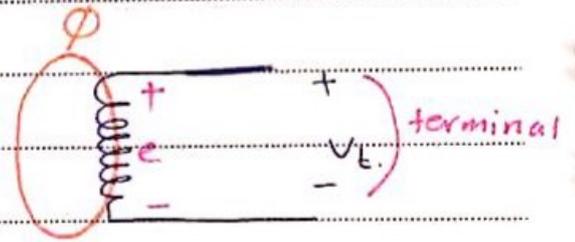- e = induced voltage
- $\phi = \phi_m \sin(\omega t)$
- $e = N \frac{d\phi}{dt} = \omega N \phi_m \cos \omega t$



- V = terminal voltage

at no-load \Rightarrow

$e = \underbrace{2\pi f N \phi_m}_{E_m} \cos \omega t$

$e = v_t$
 $E = V_t$


$E_m = 2\pi f N \phi_m$

$E_{rms} = \frac{E_m}{\sqrt{2}} = \frac{2\pi f N \phi_m}{\sqrt{2}}$

$E_{rms} = 4.44 f N \phi_m$

$E_{rms} = 4.44 f N B A$

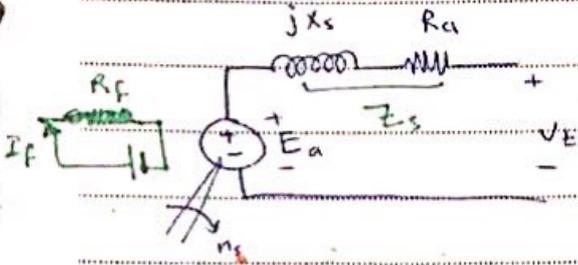Parameter calculations of synch Machine :-



→ rated terminal volt at rated current

Ex 1: 2000 KVA (2 MVA), 480V, 50 Hz, Y connected

S.G. $I_f \text{ rated} = 5 \text{ A}$

O.C test

s.c test

DC Res. test

$V_{L.O.C} = 540 \text{ V}$

$I_{L.S.C} = 300 \text{ A}$

$V_{dc} = 10 \text{ V}$

$I_f \text{ rated}$



$I_f \text{ rated}$

$I_{dc} = 25 \text{ A}$

Find R_a and X_s ?!




Sol:

O.C test :- $V_t = E$

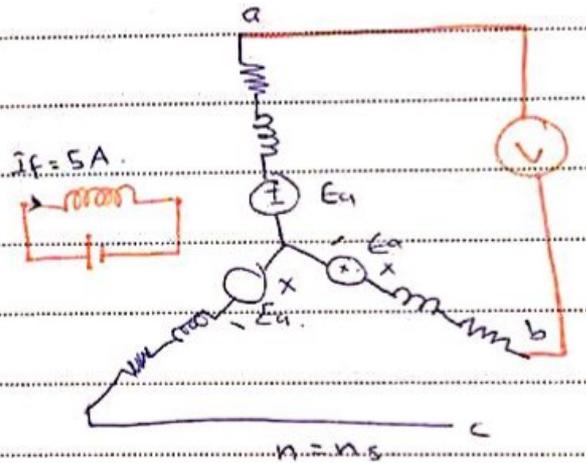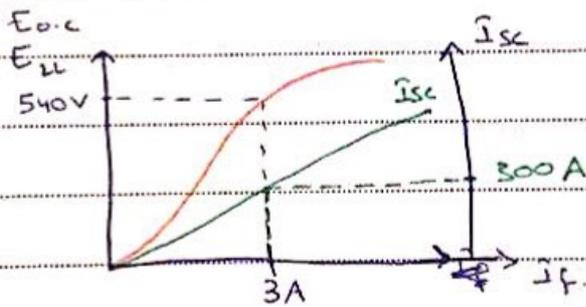

S.c test.

3-ph fault
3-ph s.c.

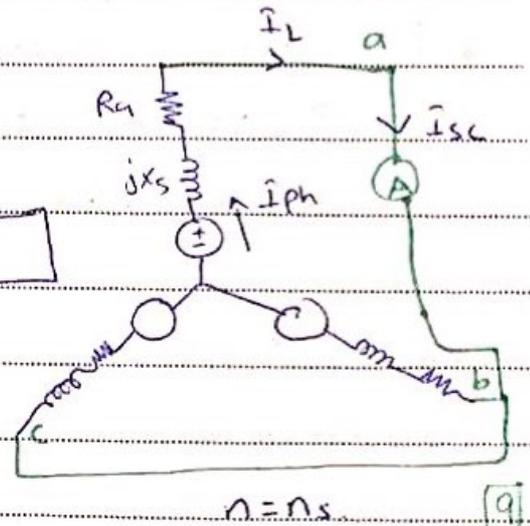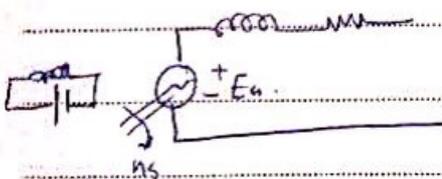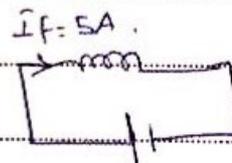


$$|Z_s| = \frac{E_{oc\text{ ph}}}{I_{sc\text{ ph}}} = \frac{540/\sqrt{3}}{300} = \frac{311.8}{300} = 1.04 \Omega$$

$$Z_s = \sqrt{R_a^2 + X_s^2} = 1.04 \Omega$$

③ DC test

$$R_{dc} = \frac{1}{2} \frac{V_{dc}}{I_{dc}}$$
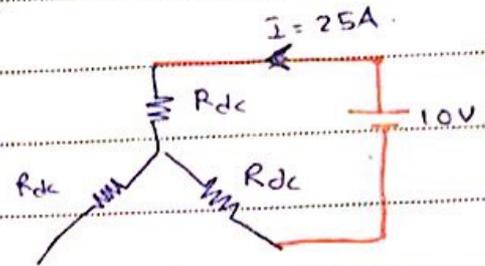
$$= \frac{1}{2} \left(\frac{10}{25} \right) = 0.2 \Omega$$



$$\eta = 0.0$$

$$R_a = (1.1 - 1.8) R_{dc}$$

$$\text{let } R_a = R_{dc} = 0.2 \Omega$$

$$X_s = \sqrt{|Z_s|^2 - R_a^2} = \sqrt{1.04^2 - 0.2^2}$$

$$X_s = 1.02 \Omega$$

$$I_{L\text{ rated}} = \frac{200 \times 10^3}{\sqrt{3} \times 480} = 240.5 \text{ A}$$

* Performance Evaluation of S.G :-

① voltage regulation.


② efficiency

* Modes of operation of S.G :-



① stand alone (isolated) "off-Grid"

② "on-Grid" Gen. connected to the Infinite Bus (Grid) [1]

① "off-Grid"

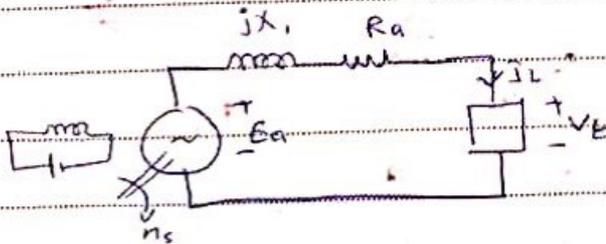


② "on-Grid"

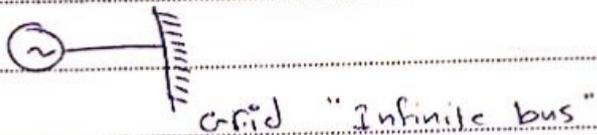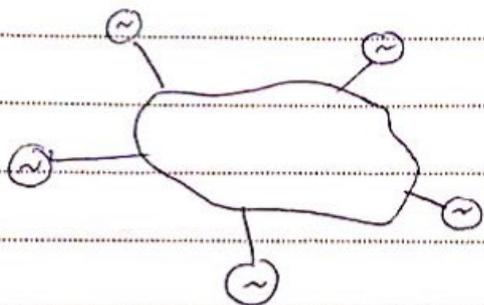

$f = \text{constant}$, $V_t = \text{const}$

□ Isolated Gen:

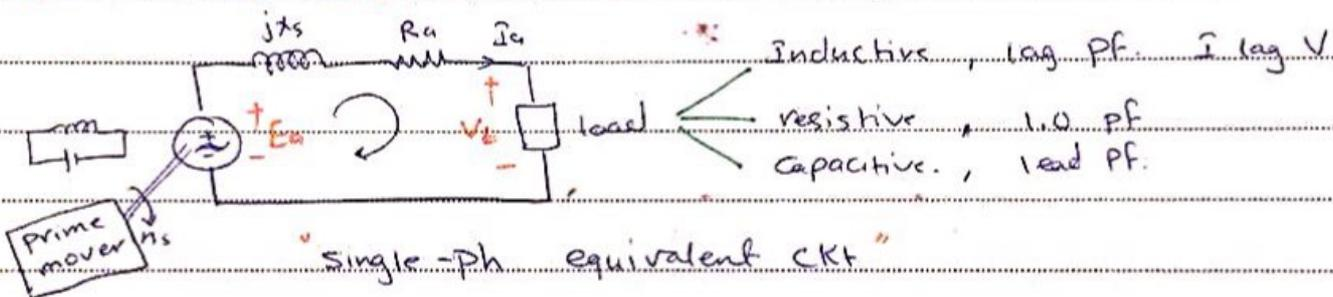

"single-ph equivalent ckt"


$$\vec{E}_a = \vec{V}_t + \vec{I}_a (R_a + jX_s)$$

~~phase shift~~

E_a // phase // V_t // phase shift // $\cos \phi$ // real power // \times magnitude // V_t // magnitude // E_a // $\sin \phi$ // Reactive power // \times

* Consider lagging pf load condition:


(I_a lags V_t by angle ϕ)

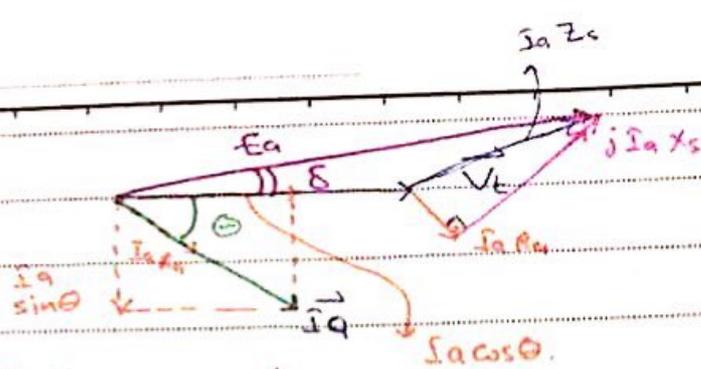


$\delta \equiv$ power angle

$\theta \equiv$ PF angle

E_a magnitude $> |V_t| \rightarrow$ Gen supplies VAR to the load

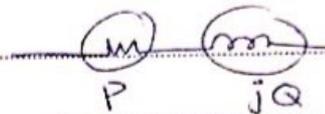


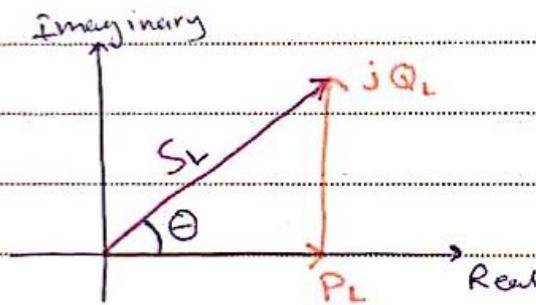E_a leads V_t by angle $\delta \Rightarrow$ Gen is over excited \Rightarrow VAR
 \Rightarrow Gen supplies watts to the load.



$$E_a = 4.44 f N \phi$$

$$\phi \propto I_f \rightarrow |E_a| \propto I_f$$

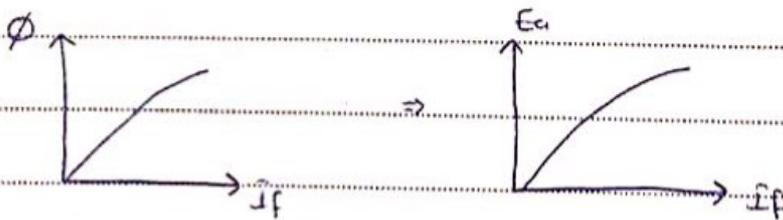


Gen magnitude $\downarrow \leftarrow$ more real power $\leftarrow \uparrow \delta$


$\uparrow T_{dev} \downarrow T_{mech} \rightarrow$ speed \downarrow

\leftarrow G \rightarrow $\downarrow \delta$ \rightarrow $\uparrow \delta$

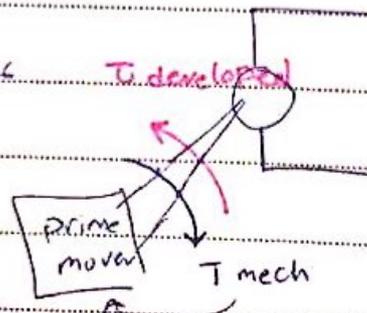$T_{mech} \uparrow \leftarrow \downarrow T_{dev}$



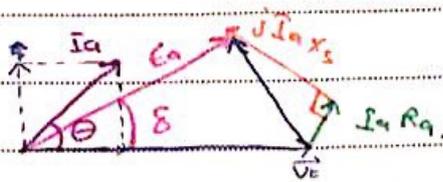② Capacitive load :- leading PF. (I_a leads V_t by θ)



$\theta, \delta = +ve$

$|E_a| < |V_t|$

E_a lead V_t by angle δ

\Rightarrow Gen. is under excited (absorbs VAR)

if V_t $\leftarrow E_a$ ال

capacitive load \leftarrow VAR $\leftarrow E_a$ ال


V_t ال \leftarrow excitation ال

unity pf \leftarrow Resist ال

VAR \leftarrow Capacitive bank ال


V_t ال \leftarrow E_a ال

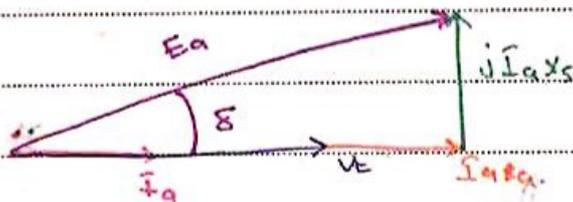③ Resistive load: 1.0 PF. E_a in phase V_t



$|E_a| > V_t$

"Normally excited."

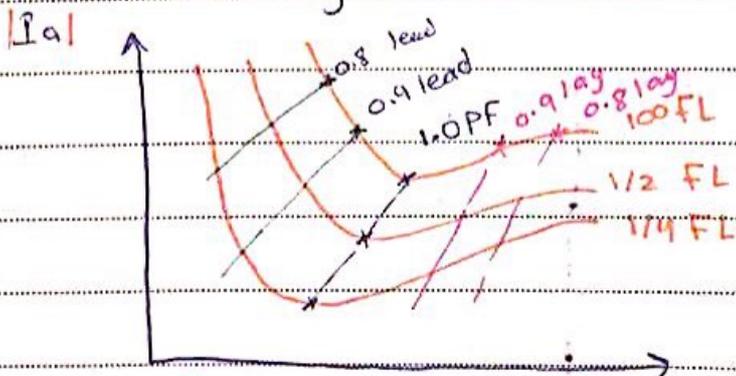

* over excited supply VAR

* under excited absorb VAR.


Capacitive load

"V curve of S.G" I_f

if \leftarrow ال

Subject

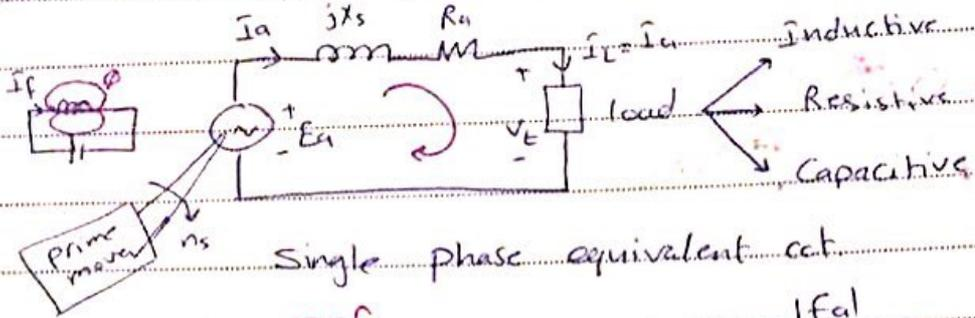I Stand-Alone operation (Isolated) of S.G




Single phase equivalent ckt

$$n_s = \frac{120F}{P}$$

power in watts



load → current
→ power watt
↑ load ↓ Z

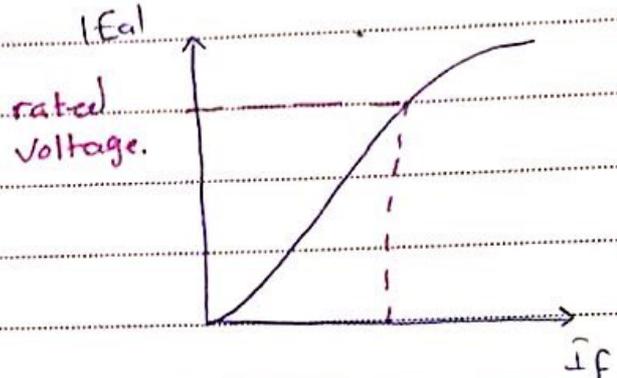

let assume that $|E_g|$ is fixed $\Rightarrow V_t ?$

$$\vec{V}_t = \vec{E}_g - \vec{I}_a (R_a + jX_s)$$

II Inductive load:

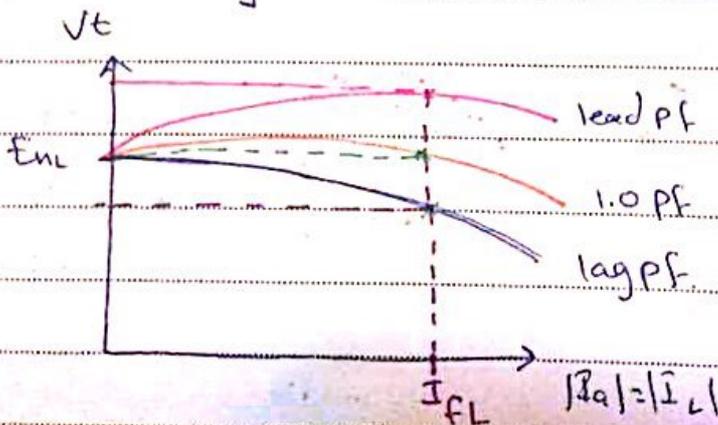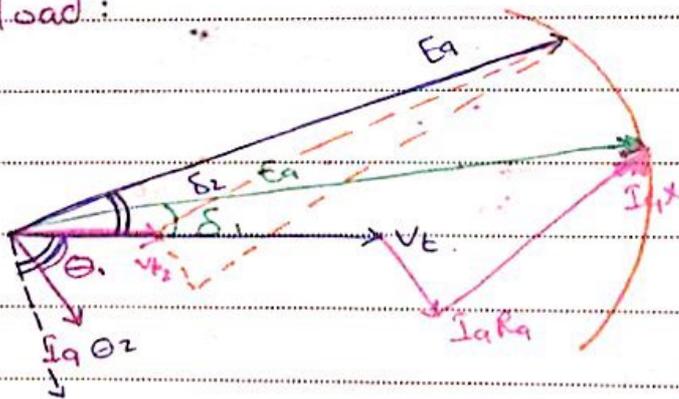

for ~~an unregulated~~ unregulated Gen | E_{af} = fixed

as the load increase $\rightarrow V_t$
 Increase load pf
 decrease lag pf.


%VR : voltage regulation.

$$VR_{FL} = \frac{V_{tNL} - V_{tFL}}{V_{tFL}} \times 100\%$$


$VR_{FL} > 0$ lag pf
 < 0 lead pf

To regulate the Gen (keeping $V_t =$ fixed) at rated voltage)

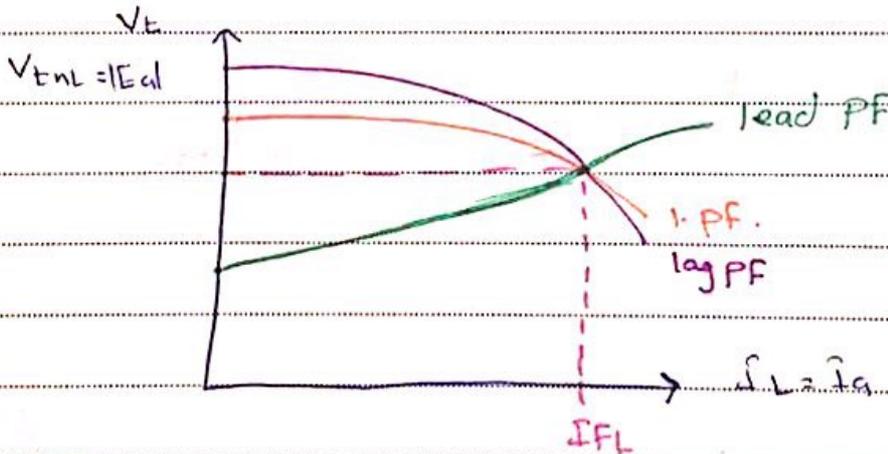E_a has to be regulated by means of adjusting the excitation (fixed current).



AVR (Automatic Voltage Regulator)

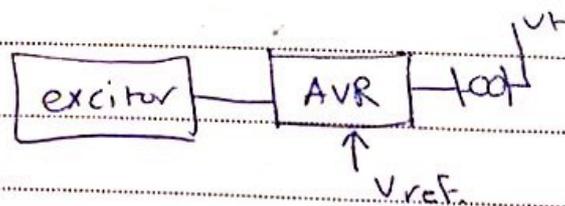

Efficiency

$$P_{in} = P_{mech} = T_{in} \omega_s$$

$$P_d = T_d \cdot \omega_s = 3 I_a E_{all} \cos \delta = P_{conv}$$

$$= \sqrt{3} E_{all} I_a = P_{conv}$$

$$P_{out} = 3 V_t I_a \cos \theta = \sqrt{3} V_L I_L \cos \theta$$

$$P_{rot} = \text{Friction} + \text{Core} + \text{winding}$$

$$P_{cu} = 3 I_a^2 R_a$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{out} + \sum \text{losses}} = \frac{3 V_t I_a \cos \theta}{3 V_t I_a \cos \theta + P_{rot} + P_{cu}} \times 100\%$$

Ex 480V, 60Hz, Y-conn S.O.G, P=6 (poles)

$$X_s = 1 \Omega / \text{ph.}$$

$I_a \text{ FL} = 60 \text{ A}$ at 0.8 PF lagging

$$P_{\text{friction}} = 1.5 \text{ kW}, P_{\text{core}} = 1.0 \text{ kW} \Rightarrow P_{rot} = 2.5 \text{ kW}$$

$R_a \approx 0.0$ (negligible), $V_{t, nL} = 480 \text{ V} = 1 E_{all}$

Find: (1) n_s

- (2) $V_t = ?$
- a. Full load and 0.8 PF lag.
 - b. " " " 1.0 PF
 - c. " " " 0.8 PF lead.

(3) η_{FL} | 0.8 PF lag.




4 $T_{in} - T_{mech}$

5 % V_{RFL} $\left\{ \begin{array}{l} 0.8 \text{ PF lag} \\ 1.0 \text{ PF} \\ 0.8 \text{ PF lead} \end{array} \right.$

Sol:

1 $n_s = \frac{120f}{P} = \frac{120 \times 60}{6} = 1200 \text{ RPM}$

2 $\vec{V}_t = |\vec{E}_a| - \vec{I}_a Z_s = \vec{E}_a - \vec{I}_a (jX_s) = \vec{E}_a - j\vec{I}_a X_s$

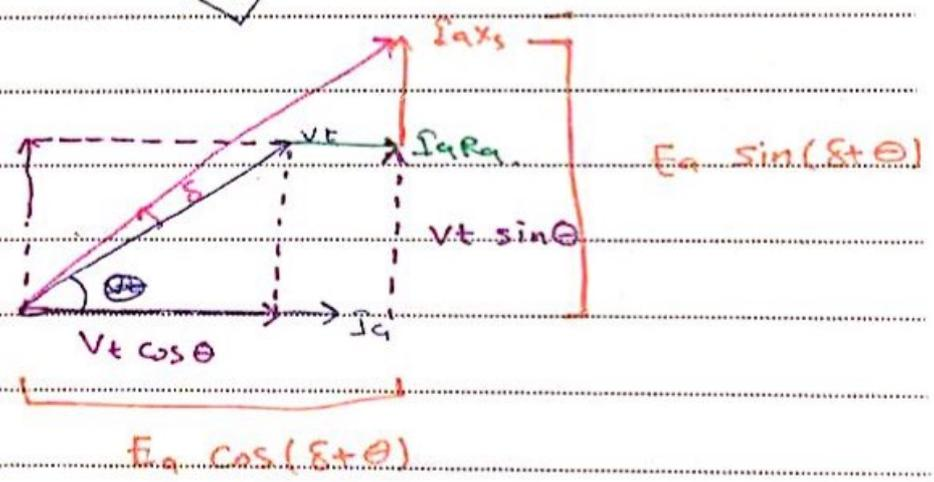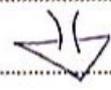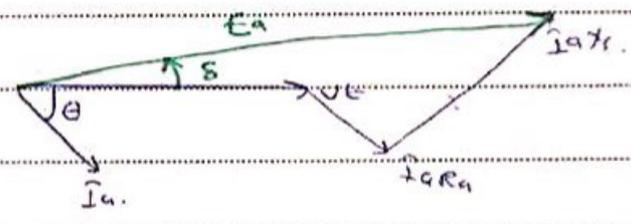

$|E_a| = \sqrt{(V_t \cos \theta + I_a R_a)^2 + (V_t \sin \theta \oplus I_a X_s)^2}$

lag PF $\leftarrow \oplus$ leading PF

$$\bar{I}_a = 60 \angle \theta$$

$$\theta = \begin{cases} -36.9^\circ \text{ lag PF} \\ 0 \text{ 1.0 PF} \\ +36.9^\circ \text{ lead PF} \end{cases}$$

$$V_t = \frac{480}{\sqrt{3}} \angle +8 - 60 \angle \theta * 1.0 \angle 90^\circ$$

① 0.8 PF lag:

$$|E_{af}|^2 = (V_t \cos \theta + I_a R_a)^2 + (V_t \sin \theta + I_a X_s)^2$$

$$\left(\frac{480}{\sqrt{3}}\right)^2 = (V_t (0.8))^2 + V_t (0.6)^2 + 1.60^2$$

$$\text{Solve for } V_t \Rightarrow V_t = 236.8 \text{ V (L-n)}$$

$$V_{tLL} = \sqrt{3} * 236.8 = 410 \text{ V}$$

$$VR\% \Big|_{0.8 \text{ PF lag}} = \frac{480 - 410}{410} * 100\%$$

$$= 17.1\%$$

② 1.0 PF $\rightarrow \theta = 0^\circ$

$$\left(\frac{480}{\sqrt{3}}\right)^2 = (V_t * 1)^2 + (0 + 60 * 1.0)^2$$

$$V_{tph} = 270.4 \text{ V}$$

$$\text{Solve for } V_t = 468 \text{ V}_{LL}$$

$$VR\% \Big|_{1.0 \text{ PF}} = \frac{480 - 468}{468} * 100\% = 2.6\%$$

③ 0.8 pf load :-


$$\left(\frac{480}{\sqrt{3}}\right)^2 = (V_L \times 0.8)^2 + (V_L \times 0.6 - 1.0 \times 60)^2$$

$$V_{L_{Ph}} = 308.8 \text{ V} \rightarrow V_{L_{LL}} = 535 \text{ V}$$

$$VR\% \Big|_{0.8 \text{ pf load}} = \frac{480 - 535}{535} = -10.3\%$$

" load at rated voltage $\rightarrow E_a$ " η

$$\eta = \frac{P_{out}}{P_{in}} \Big|_{0.8 \text{ pf load}}$$

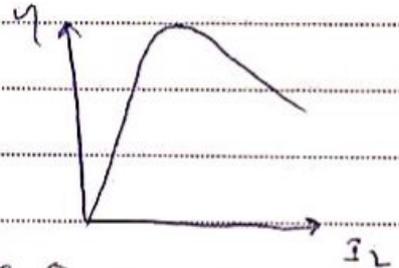

$$P_{out} \Big|_{0.8 \text{ pf load}} = 3 V_L I_a \cos \theta = \sqrt{3} \times V_L \times I_L \cos \theta$$

$$= 3 \times \frac{410}{\sqrt{3}} \times 60 \times 0.8 = \text{~~34.1 kW~~}$$

$$= \sqrt{3} \times 410 \times 60 \times 0.8 = 34.1 \text{ kW}$$

$$P_{in} = P_{out} + \text{losses}$$

$$= 34.1 \text{ kW} + 2.5 \text{ kW}$$

$$= 36.6 \text{ kW}$$

$$\eta \Big|_{0.8 \text{ pf load}} = \frac{34.1}{36.6} \times 100 = 93.2\%$$

0.8
PF
load


$$4) T_{in} = ?$$

$$P_{in} = T_{in} \cdot \omega_s$$

$$36.6 \times 10^3 = T_{ind} \cdot \frac{2\pi n_s}{60}$$

$$= T_{ind} \cdot \frac{2\pi \times 1200}{60}$$


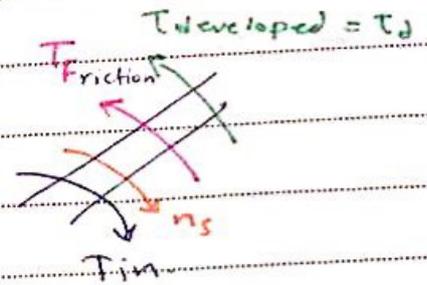
$$T_{ind} = 291.2 \text{ N}\cdot\text{m}$$



$$T_d = \frac{P_d}{\omega_s} = \frac{34.1 \text{ k}}{2\pi \times \frac{1200}{60}}$$


$$T_d = 271.3 \text{ N}\cdot\text{m}$$

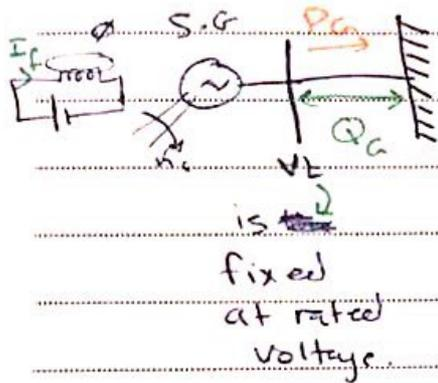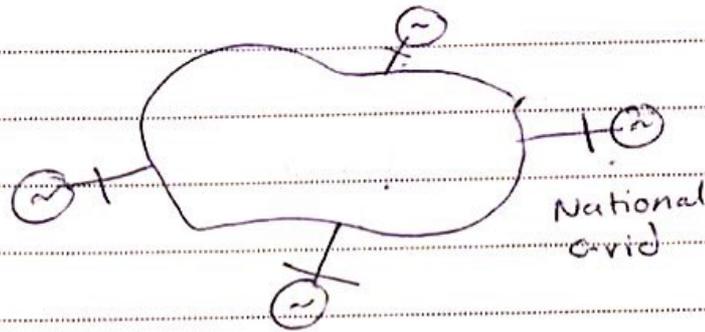[2] Synch Gen. connected to Infinite bus (Grid):-




- Infinite bus
- constant freq
- constant voltage

[a]

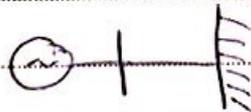


Gen connected to the Grid directly.

[b]

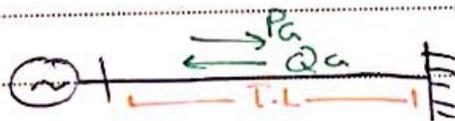

Gen connected to the Grid through T.L

[c]

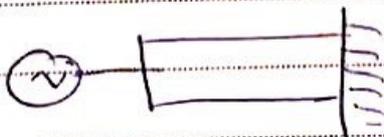


Gen connected to the Grid through double circuit.





[21]

x Equivalent circuit 8.4

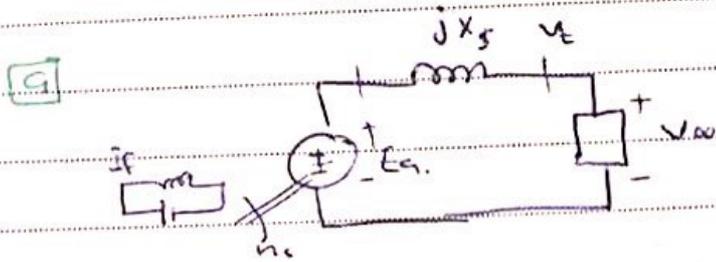

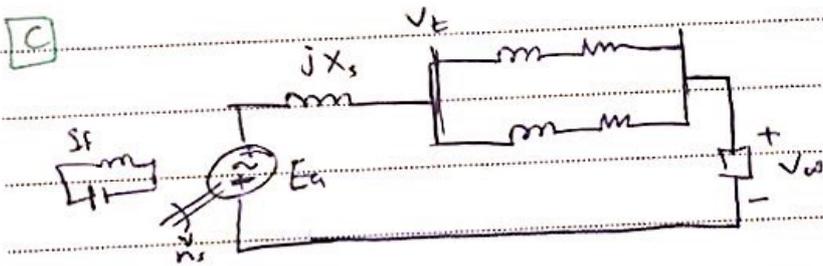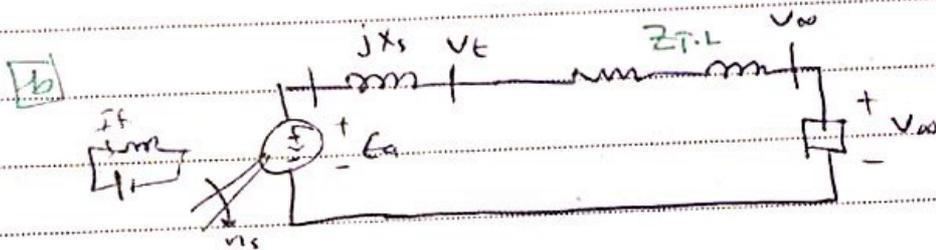
$$R_a \ll X_s \Rightarrow R_a \approx 0.0$$



$I_f \rightarrow$ Control Q_a

$n \rightarrow$ Control P_a

* S.G connected to infinite bus 8.4

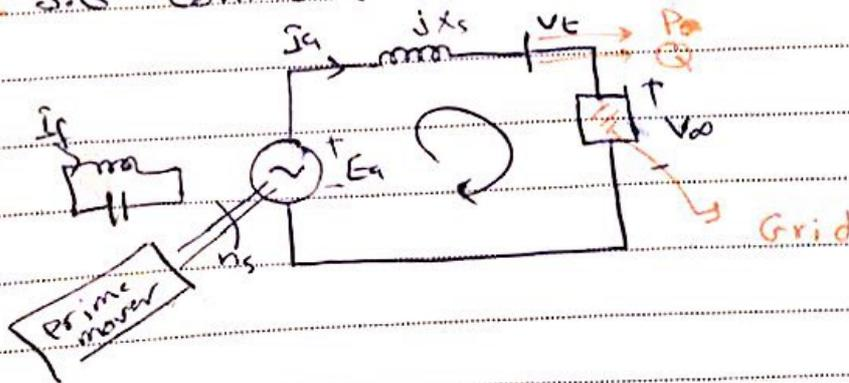


$$V_t = V_{\infty} = \text{constant}$$

$$R_a \approx 0.0 \text{ (negligible)}$$

$$\vec{E}_a = V_t + j \vec{I}_a X_s$$

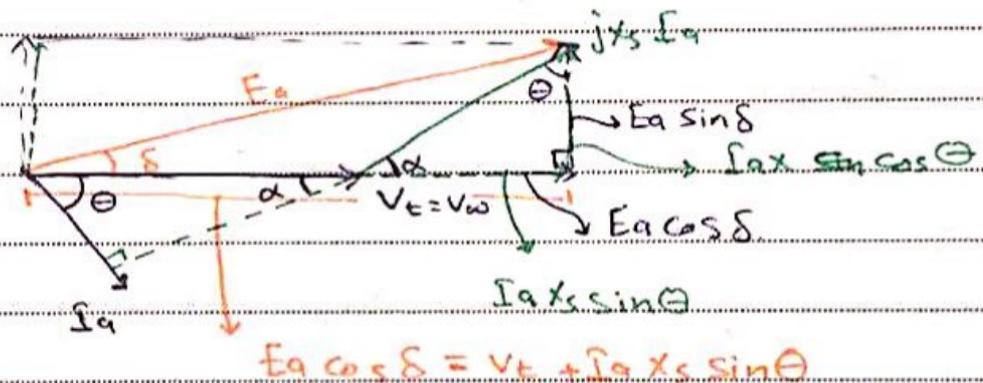□ Consider lagging PF $\rightarrow \vec{I}_a$ lags V_t (\vec{V}_{∞}) by angle Θ .



$$|E_a| > |V_t|$$

\vec{E}_a lead \vec{V}_t by angle δ

Gen supplies P and Q

$$P = 3 V_t I_a \cos \Theta < \frac{V_t}{I_a}$$

$$P = \sqrt{3} V_L I_L \cos \Theta < \frac{I_a}{V_t}$$

$$Q = 3 V_t I_a \sin \Theta < \frac{V_t}{I_a}$$

$$= \sqrt{3} V_L I_L \sin \Theta$$

Consider the vertical component.

$$E_a \sin \delta = I_a X_s \cos \Theta$$

$$E_a \sin \delta = I_a X_s \cos \theta$$

$$\frac{3 V_t E_a \sin \delta}{X_s} = 3 V_t I_a \cos \theta = P_{3\phi \text{ ph}}$$

$$P_{3\phi \text{ ph}} = 3 V_t |I_a| \cos \theta$$

$\underbrace{\quad \quad \quad}_{V_t} \quad \underbrace{\quad \quad \quad}_{I_a}$

$$P_{3\phi \text{ ph}} = \frac{3 |V_t| |E_a| \sin \delta}{X_s} \rightarrow \text{when } P_o \approx 0.0$$

consider the horizontal component

$$E_a \cos \delta = V_t + I_a X_s \sin \theta$$

$$E_a \cos \delta - V_t = I_a X_s \sin \theta$$

$$\frac{1}{X_s} [E_a \cos \delta - V_t] = I_a \sin \theta$$

$$\frac{3 V_t}{X_s} [E_a \cos \delta - V_t] = 3 V_t I_a \sin \theta = Q_{3\phi \text{ ph}}$$

$R_a \approx 0.0$


$$Q_{3\phi \text{ ph}} = \frac{3 V_t E_a \cos \delta - 3 V_t^2}{X_s}$$

$E_a \cos \delta > V_t \Rightarrow Q_{3\phi} > 0 \rightarrow Q$ is generated as "delivered" supplied

$E_a \cos \delta < V_t \rightarrow Q_{3\phi} < 0 \rightarrow Q_{3\phi}$ is absorbed

$\uparrow I_f \rightarrow \uparrow E_a$

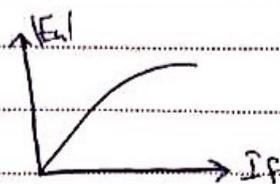"If \uparrow \rightarrow \uparrow E_a \rightarrow \uparrow P_o "




(24)

Capacitive $\rightarrow Q$

Generator $(\cos \phi) \rightarrow \vec{I}_a \cdot \vec{V}_t = Q \sin \phi \omega \leftarrow C$

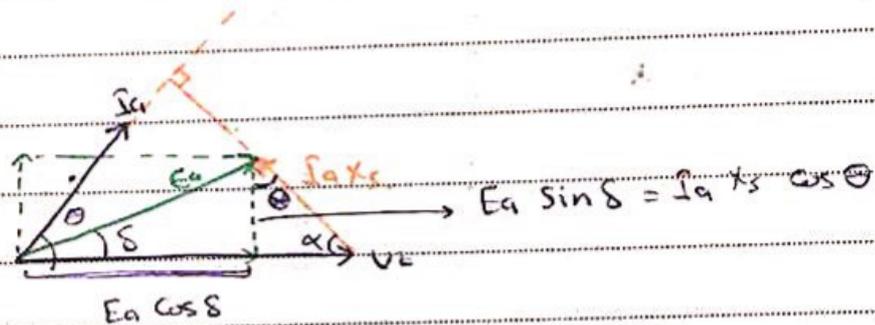2] Consider leading PF $\rightarrow \vec{I}_a$ lead $V_t (\vec{V}_t)$ by angle ϕ



$E_a \cos \delta < V_t$


$Q_{3\phi} = \frac{3V_t}{X_s} [E_a \cos \delta - V_t] \Rightarrow Q_{3\phi} < 0$

Gen absorbed VAR

\vec{E}_a lead $\vec{V}_t \Rightarrow$ Gen supplies P

" real power " MW

3] Consider unity PF:

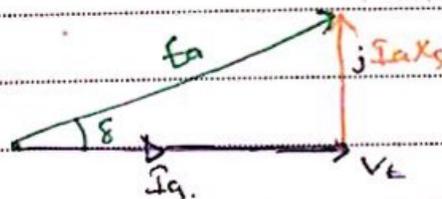



$|E_a \cos \delta| > |V_t|$

$Q_G = Q_C = 0$

$Q_G =$ just little to compensate $= 3 I_a^2 X_s$

- Power Angle Curve (P-δ Curve)
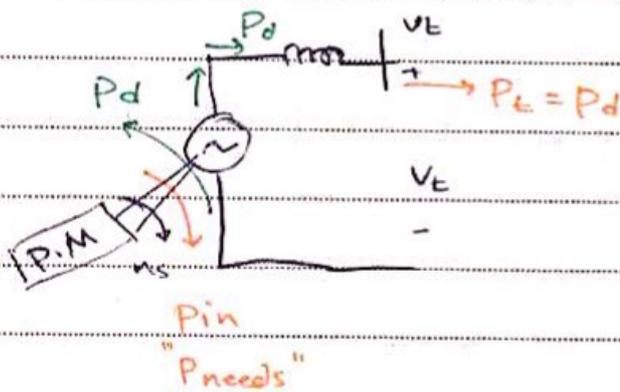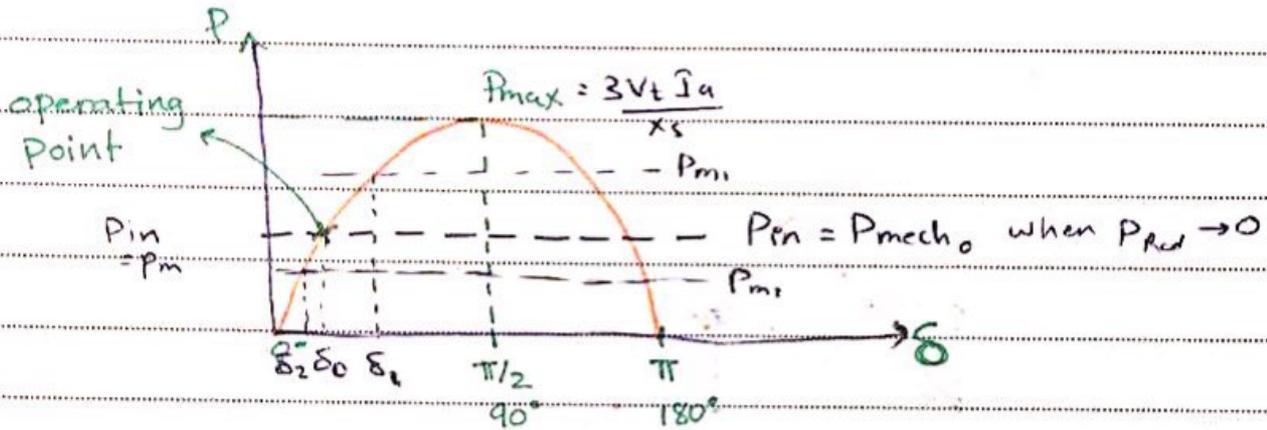
$$P_{3\phi} = \frac{3 V_b \cdot E_a}{X_s} \sin \delta = P_d \text{ "developed Power"}$$




$$P_{in} = T_{in} \cdot \omega_s$$

$$\begin{aligned} P_d &= P_{conv} \\ &= T_d \cdot \omega_s \\ &= 3 E_a \cos \delta \\ &= \frac{3 V_b \sin \delta E_a}{X_s} \\ &= P_{out} \end{aligned}$$

P_{red}

↑ P_G real machine → ↑ P_{electri} → P_{dev} > P_{in} → Slow down
 → δ ↑ → more steam → mech power ↑ (↓ δ₂ → ↓ P_{mech})

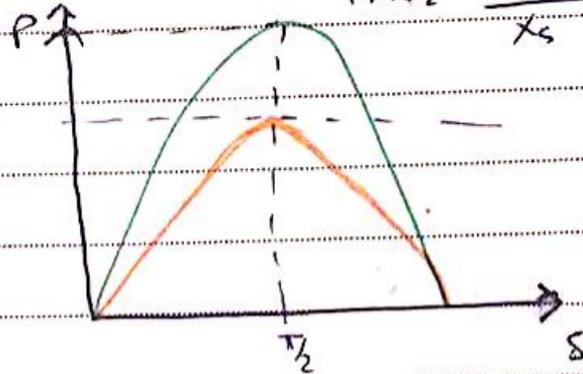$\uparrow E_a \rightarrow \uparrow P_{max}$



$$P_{max2} = \frac{3V_t E_a}{X_s}$$


$\uparrow P_{max} \Rightarrow P_{mech} / \text{electrical const.}$

$\uparrow E_a \rightarrow \downarrow \delta$ " $p = \text{const. } \frac{dE_a}{E_a} = \frac{d\delta}{\delta}$ "


* $\uparrow P_{mech} \text{ up to } P_{max} \Rightarrow P_{mech} = P_{max} \Rightarrow$

$P_{mech} > P_{max} \text{ elect} \rightarrow \text{machine will slip}$


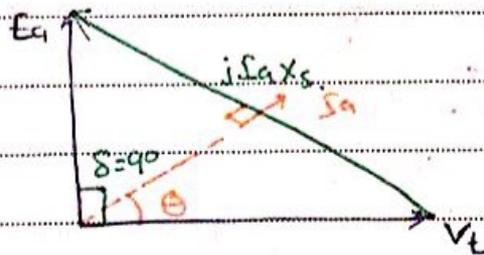
Operation at P_{max} is called ~~steady~~ steady, stable stability limit $\delta = 90^\circ$





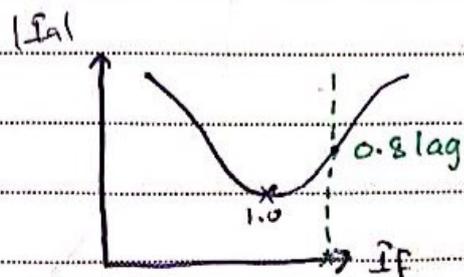
$$P_{max} = \frac{3V_t E_a}{X_s} \quad \delta = 90^\circ$$



* Process of Synchronization :-

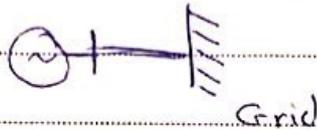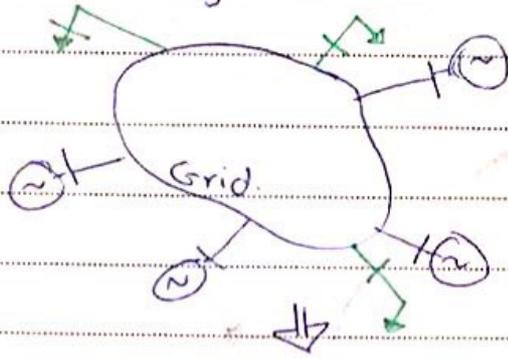


S.G. Connected to Infinite bus "Grid"

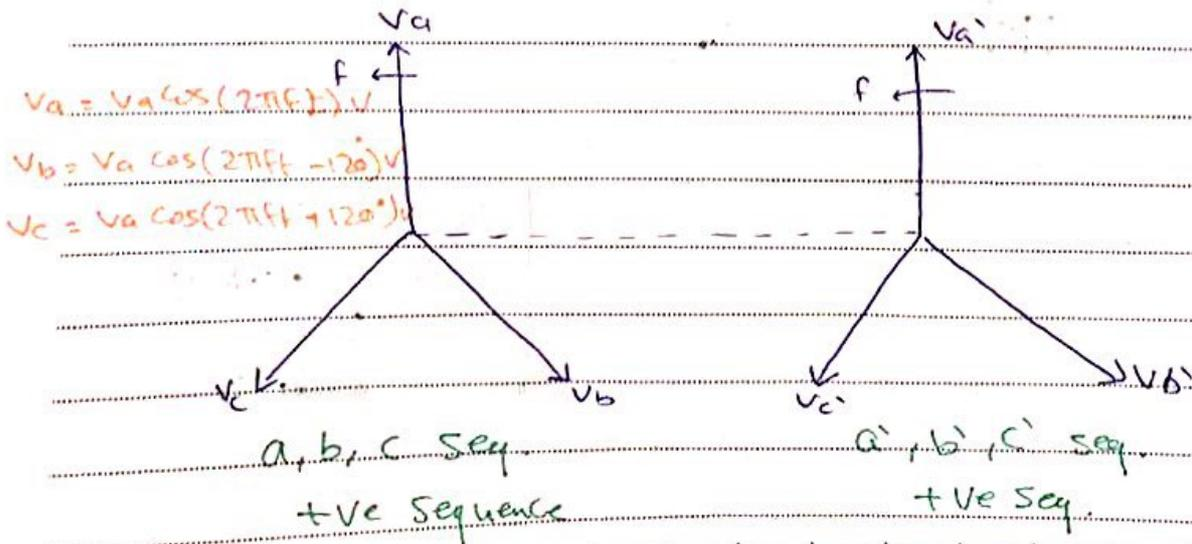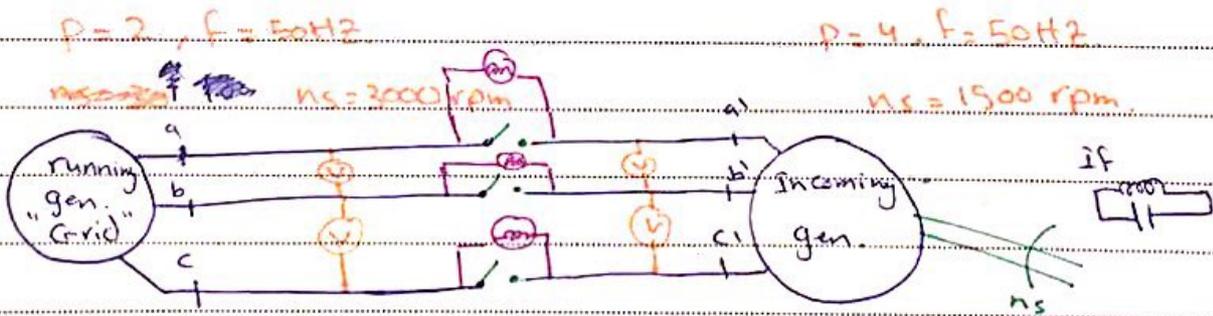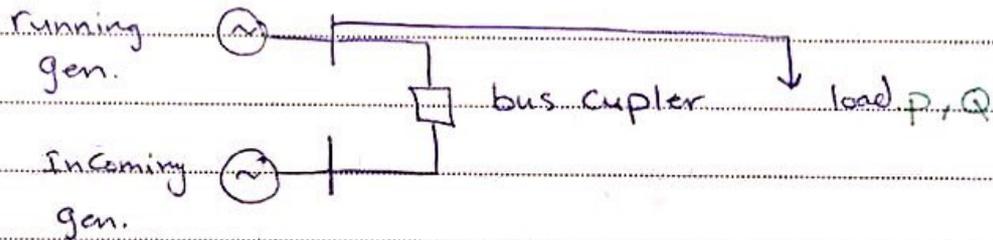


Condition of Successful Synchronization

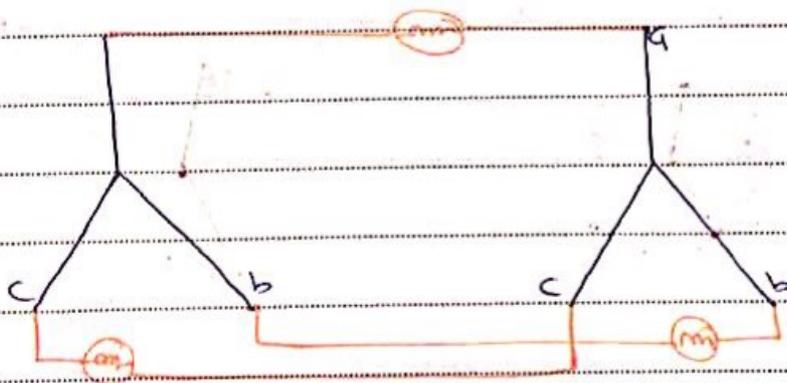
- ① Both running and Incoming Generator have the same voltage magnitude.
- ② Both machines must have the same frequency "Speed"
- ③ Both machines have the same phase sequence.
- ④ Both machines have the same phase position.



dark lamp ← bus

2 phases

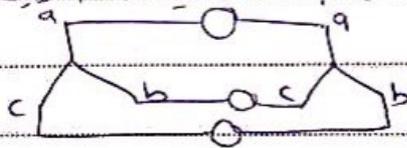

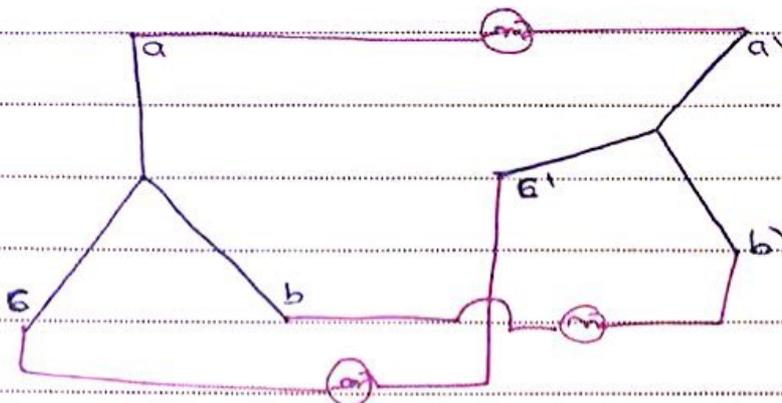


* ↑ phase ⇒
 ↑ V
 * ↑ difference between
 تيزيد الاضاه



$$V_a = V_a \cos(\omega t + f)$$

$$V_{a'} = V_a \cos(\omega t + f - 10^\circ)$$



الاضاه شدتها ~~تختلف~~ تتغير في الـ 3

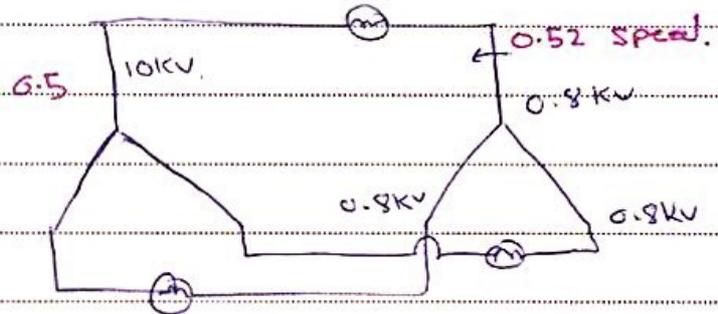

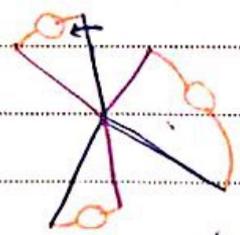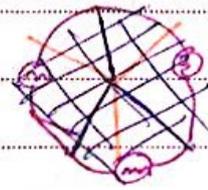* واحد اسرع من الثاني ← الـ 3 طرين () ← ليدري بلف و فو كلهم نفس الشكل.



ادت الـ ركة ← ريفو كلهم بنفس الشكل

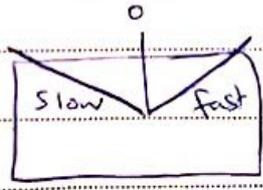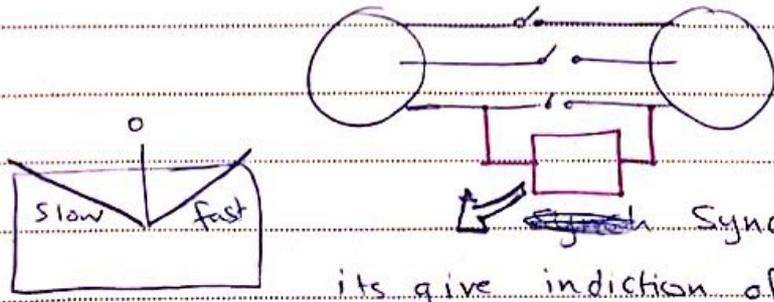


Synchron scope.
 its give indication of speed and phase position, its can controll by steam

اذا كان متغير ببطء السرعة، اذا كان متغير بقل السرعة

Solution Tutorial # 1 : Synch. Gen.

Q # 1-a :

Sol:

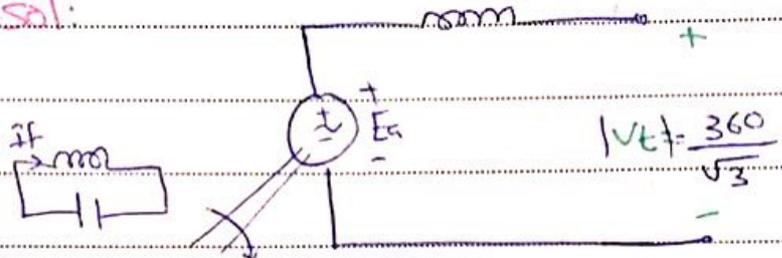

$$f_1 = 60 \text{ Hz}$$

$$I_{f1} = 3.6 \text{ A}$$

$$V_{tLL} = 360 \text{ V}$$

$$f_2 = 40 \text{ Hz}$$

$$I_{f2} = 2.4 \text{ A}$$

$$V_{tLL} = ?$$

$$E_g = V_t = 4.44 f N \Phi_{ph} m$$

$$\Phi_m \propto I_f$$

$$E_g \propto f \cdot I_f$$

$$V_{tLL} \propto I_f \cdot f$$

$$\frac{V_2}{V_1} = \frac{I_{f2} \cdot f_2}{I_{f1} \cdot f_1} \Rightarrow$$

$$V_2 = \frac{2.4 \times 40}{3.6 \times 60} \times 360$$

$$V_{2LL} = 160 \text{ V}$$

Q # 1-b :

Sol: $V_{t1} = E_g = 620 \text{ V}$ at Φ_1 and n_1

$$V_{t2} = ? \text{ at } \Phi_2 = 0.88 \Phi_1$$

$$n_2 = 1.1 n_1$$

$$\textcircled{1} \frac{V_2}{V_1} = \frac{\Phi_2 \cdot n_2}{\Phi_1 \cdot n_1}$$

$$V_2 = 0.85 \times 1.1 \times 620.$$

$$V_2 = 580 \text{ V}$$

$$\textcircled{2} n_s = \frac{120f}{P} \Rightarrow f_2 = \frac{n_2}{n_1} \cdot f_1$$

$$= 1.1 \times 60$$

$$f_2 = 66 \text{ Hz}$$

Q 2:

~~Q 2~~ $p = 8$, $n_s = 900 \text{ rpm}$, γ -connected
 $N_{ph} = 120 \text{ turn.}$, $K_w = 0.9$
 $\Phi = ?!$ if $V_{LL} = 2400 \text{ V (line volt)}$

Sol: $E_{ph} = \frac{V_{LL}}{\sqrt{3}} = 4.44 f N_{ph} \Phi_m \cdot K_w$


$$E_{LL} = V_{LL} = \sqrt{3} \cdot 4.44 f N_{ph} \Phi_m \cdot K_w = 2400$$

$$\Phi = \frac{2400/\sqrt{3}}{4.44 \cdot 60 \cdot 120 \cdot 0.9}$$

$$\Phi_m = 48.2 \text{ m wb}$$




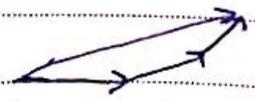- * $K < 1 \Rightarrow$
- ① Friction pitch.
- ② \vec{a} و \vec{a}' لا في ال vector ايجو ايجو في ال



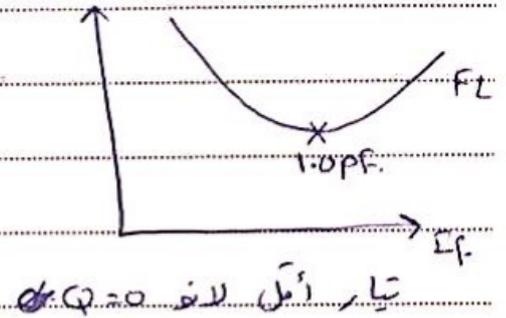Q 3.8 $S_{3\phi} = 1000 \text{ kVA}$, 12 kV $X_s = 30 \Omega$, $R_a = 0.02 \Omega$
 rated I_a


$P_{\text{supplied}} = 750 \text{ kW}$
 at 12 kV .
 at 0.8 PF lagging .



Find VR % ?!

Sol: $VR\% = \frac{V_{NL} - V_L}{V_L} \times 100\%$

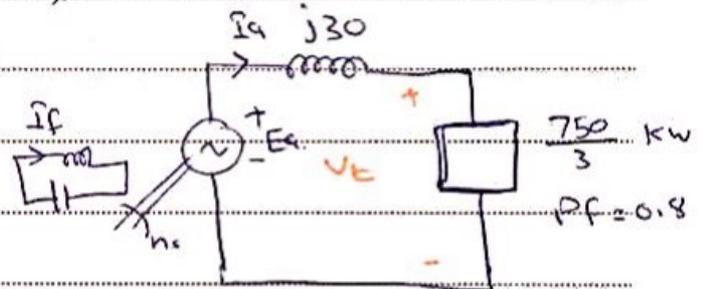$V_t = \frac{12 \text{ kV}}{\sqrt{3}} \angle 0$



$V_{NL} = |E_a|$
 load condition


$= \sqrt{(V_t \cos \theta + I_a R_a)^2 + (V_t \sin \theta \pm X_s I_a)^2}$

OR $\Rightarrow \vec{E}_a = \vec{V}_{NL} = \vec{V}_t + j I_a (R_a + j X_s)$
 $= \frac{12000}{\sqrt{3}} \angle 0 + j (45.1 \angle -36.9^\circ) \times (30 \angle 90^\circ)$

$= 7.74 \angle 7.9^\circ \text{ kV}$ $E_{aNL} = 13.5 \text{ kV}$

$I_a = \frac{P_{3\phi}}{\sqrt{3} \times V_{LL} \times PF}$

$|I_a|_{(I_L)} = \frac{S_{3\phi}}{\sqrt{3} \times V_{LL} \times PF} = \frac{750 \times 10^3}{\sqrt{3} \times 12 \times 10^3 \times 0.8} = 45.1 \text{ A}$

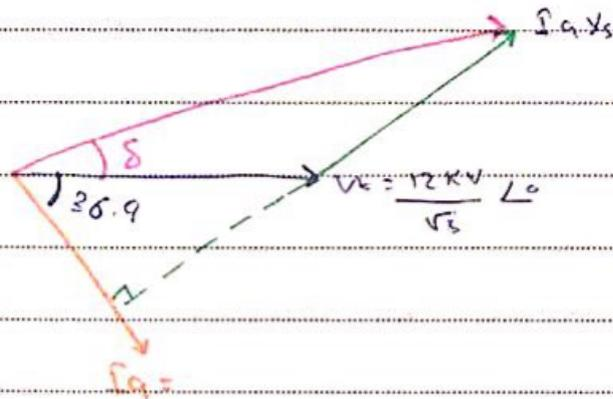

$$\begin{aligned} \text{VR}\% &= \frac{13.5 - 12}{12} \times 100\% \\ &= 12.5\% \end{aligned}$$

Question #1-a

$$V_t \text{ no load} = E_a$$

A synchronous generator on open-circuit generates 360 V at 60 Hz when the field current is 3.6 A. Neglecting saturation determine the open-circuit EMF when the frequency is 40 Hz and the field current is 2.4 A.

Question #1-b

A three-phase, 60 Hz synchronous generator operating at no load has a generated voltage of 620 V at rated frequency. If the pole flux is decreased by 15% and the speed is increased by 10%, determine:

- The induced voltage,
- The frequency.

Question #2

A 3-phase, 8-pole, 900-rpm, Y-connected synchronous generator has 120 turns per phase and a stator-winding factor of 0.90. A voltage of 2400 V is measured across the machine terminals on no load. Determine the flux per pole.

Question #3

A 3-phase, 1000-kVA, 12 kV, Y-connected, synchronous generator supplies 750 kW at 12 kV and 0.8 lagging power factor. The synchronous reactance is 30 Ω per phase, and the armature resistance is negligible. Calculate the voltage regulation.

Question #4

A 3-phase, Y-connected synchronous generator supplies a load of 10 MW at 11 kV (terminal voltage). Its resistance is $R_a=0.1 \Omega$ /phase and synchronous reactance $X_s=0.66 \Omega$ /phase. Calculate the line value of EMF generated and the percentage voltage regulation at:

- 1.0 *pf*.
- 0.8 *pf lagging*
- 0.8 *pf leading*.

Question #5

A 1200-kVA, 6600-V, 3-phase, Y-connected synchronous generator with a resistance R_a of 0.4 Ω and a reactance X_s of 6 Ω per phase delivers full-load current at *pf* 0.8 lagging and normal rated voltage. Estimate the terminal voltage for the same excitation and load current at 0.8 *pf leading*.

Question #6

The following test results are obtained from a 3-phase, 6000-kVA, 6,600 V, Y-connected, 2-pole, 50-Hz, synchronous generator. With a field current of 125 A, the open-circuit voltage is 8000V at the rated speed with the same field current and rated speed, the short-circuit is 800 A. At the rated full-load, the armature resistance voltage drop is 3% of the rated phase voltage. Find the regulation of the synchronous generator on full-load and at a *pf* of 0.8 lagging.

Question #7

A 3-phase, 10-kVA, 208-V, 4-pole, Y-connected synchronous generator has a synchronous reactance X_s of 2.0 Ω per phase and negligible armature resistance. The generator is connected to a three-phase, 208-V infinite bus. Neglect rotational losses.

- The field current and the mechanical input power are adjusted so that the synchronous generator delivers 6 kW at 0.85 lagging power factor. Determine the excitation voltage and the angle δ .
- The mechanical input power is kept constant but the field current is adjusted to make the power factor unity. Determine the percent change in the field current with respect to its value to part (a).

Question #8

A 25-kVA, 230-V, 3-phase, 4-pole, 60-Hz, Y-connected synchronous generator has a synchronous reactance X_s of 1.5Ω per phase and negligible armature resistance. The generator is connected to an infinite bus (of constant voltage magnitude and constant frequency) at 230 V and 60 Hz.

- Determine the excitation voltage E_a when the machine is delivering rated kVA at 0.8 pf lagging.
- The field excitation current I_f is increased by 20% without changing the power input from the prime mover. Find the stator current I_a , power factor, and reactive power Q supplied by the machine.
- With the field excitation current I_f as in part (a), the input power from the prime mover is increased very slowly. What is the steady-state limit? Determine stator current I_a , power factor, and reactive power Q .

Question #9

A 12-kV, 3-phase, 60-Hz, Y-connected synchronous generator has a synchronous reactance X_s of 15Ω per phase and negligible armature resistance. For a given field current, the open-circuit voltage is 13 kV.

- Calculate the maximum power developed by the generator.
- Determine the armature current and power factor for the maximum power condition.

Question #10

A 3-phase, 6-pole, 60-Hz synchronous generator has a synchronous reactance X_s of 4Ω per phase and a terminal voltage of 2300 V. The field current is adjusted so that the excitation voltage is 2300 V at a power angle of 15° . Find:

- Stator current.
- Power factor.
- Output real and reactive power.
- Maximum power developed by the generator.
- Armature current and power factor for the maximum power condition.
- The maximum torque applied to the shaft of the generator.

Question #11

The loss data for a 10-MVA, 12-kV, 2-pole, 60-Hz, 3-phase synchronous generator is as follows:

Open-circuit core loss at 12 kV = 75 kW

Short-circuit load loss at 480 A = 60 kW

Friction and windage loss = 55 kW


Calculate the efficiency at rated load and 0.8 pf lagging.

Question #12

Two identical 3-phase, Y-connected alternators work in parallel and supply a load of 1500 kW at 11 kV at a power factor of 0.866 lagging. Each alternator supplies half the total real power. The synchronous reactance of each is 50Ω per phase and the resistance is 4Ω per phase. The field excitation of the first machine is so adjusted that its armature current is 50 A lagging. Determine:

- The power factor of the first alternator.
- The armature current and power factor of the second alternator.
- The generated voltage and voltage regulation of the first alternator.

Tutorial Q4:

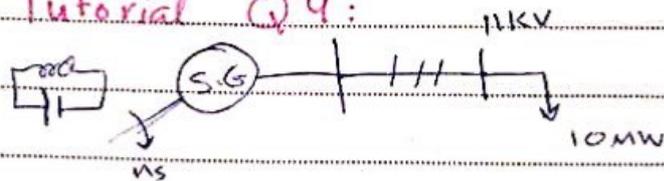

$$R_a = 0.1 \Omega / \text{ph}$$

$$X_s = 0.66 \Omega / \text{ph}$$


Find E_{eff} and VR% at the above load

0.8 PF lag
0.8 PF lead
1.0 PF

Condition.

For γ connection.

$$|I_L| = |I_{\text{ph}}|$$

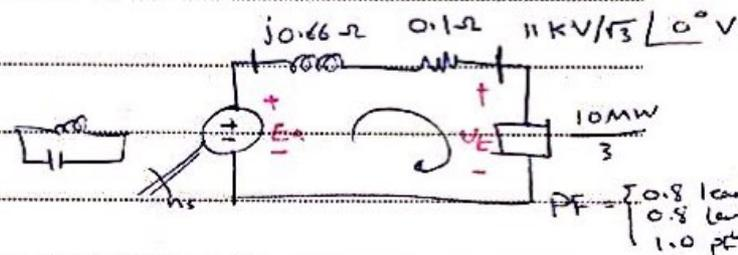

Sol:

$$\text{VR}\% = \frac{V_{\text{nl}} - V_L}{V_L} \times 100\%$$

$$V_{\text{nl}} = |E_g|$$

$$\vec{E}_g = \vec{V}_t + \vec{I}_a (R_a + jX_s)$$

$$= \frac{11 \times 10^3}{\sqrt{3}} \angle 0^\circ + (0.1 + 0.66j) |I_a| \angle \theta$$

$$|I_L| = \frac{P_{3\phi} / \text{PF}}{\sqrt{3} * V_{LL}} = \frac{S_{3\phi}}{\sqrt{3} V_{LL}}$$

a. 0.8 PF $\theta = 36.9^\circ$

$$|I_L| = \frac{10 \times 10^3 / 0.8}{\sqrt{3} * 11 \times 10^3} = 6.56 \text{ A} = |I_a|$$


35

b. ~~0.8~~ 1.0 pf $\theta = 0^\circ$

$$|I_L| = |I_a| = \frac{10 \times 10^6}{\sqrt{3} \times 11 \times 10^3} = 525 \text{ A}$$

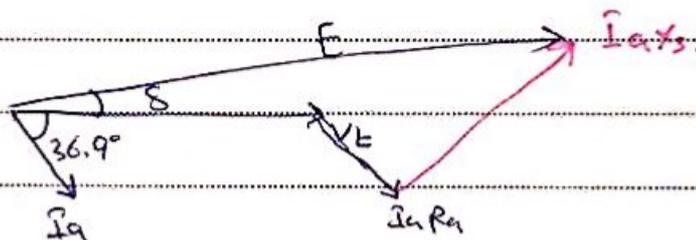q. 0.8 pf lag.


$$E_a = \frac{11 \times 10^3}{\sqrt{3}} \angle 0^\circ + (0.1 + j0.66) \times 656 \angle -36.9^\circ$$



$$E_a = 6670 \angle 2.6^\circ \text{ V (phase voltage)}$$

$$|E_{aLL}| = 6670 \times \sqrt{3} = 11552$$

b. 0.8 pf lead

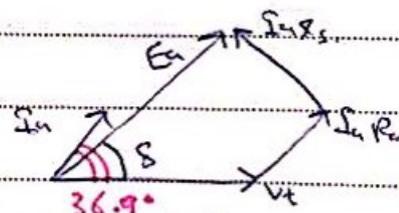

$$\vec{E}_a = \frac{11 \times 10^3}{\sqrt{3}} \angle 0 + 656 \angle +36.9^\circ (0.1 + j0.66)$$

$$= 6192.5 \angle \quad$$

$$|E_{aLL}| = 6192.5 \times \sqrt{3} = 10726 \text{ V}_{LL}$$

a. VR% at 0.8 pf lag

$$VR\% = \frac{11552 - 11000}{11000} \times 100\% = 5\%$$

b. VR% at 0.8 PF lead:

$$VR\% = \frac{10726 - 11000}{11000} \times 100\% = -2.5\%$$

c. 1.0 PF $\Rightarrow \vec{I}_g = 525 \angle 0^\circ$

$$|E_g| = 6413 \text{ Vph}$$

$$|E_{LL}| = \sqrt{3} \times 6413 = 11077 \text{ V}$$

$$VR\% = \frac{11077 - 11000}{11000} \times 100\%$$

$$= 1\%$$

rated load "Full load"

Q5: 1200 KVA (1.2 MVA), 6600V (6.6 KV), 3ph Y-conn.

S.G, $R_a = 0.4 \Omega/\text{ph}$, $X_s = 6 \Omega/\text{ph}$

Point = PFL at 0.8 PF at rated voltage.


Find V_t for the same excitation (lag PF) at 0.8 PF load.

lead \leftarrow lag no. just load *

Sol: a) $E_a = \sqrt{(V_t \cos\theta + I_a R_a)^2 + (V_t \sin\theta + I_a X_s)^2}$
 OR $E_a = V_t + I_a (R_a + jX_s)$

$|I_{FL}| = |I_{aFL}| = \frac{S_{FL}}{\sqrt{3} V_L} = \frac{1.2 \times 10^6}{\sqrt{3} \times 6.6 \times 10^3} = 105 \text{ A}$


$\theta = \cos^{-1}(0.8) = 36.9^\circ$

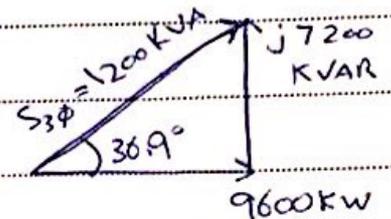

$E_a = \frac{6600}{\sqrt{3}} \angle 0 + 105 \angle -36.9^\circ (0.4 + j6)$


$\vec{E}_a = 4250 \angle 6.5^\circ \text{ V (Phase voltage)}$

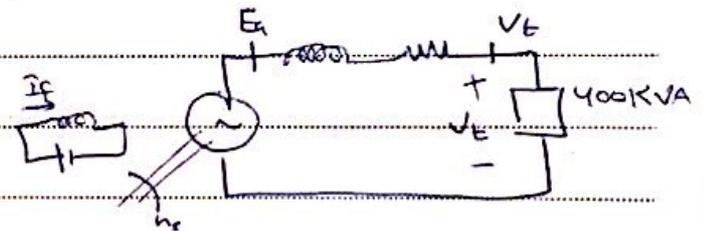$E_{all} = 4250 \times \sqrt{3} = 7.36 \text{ KV}$



((machine over excited))

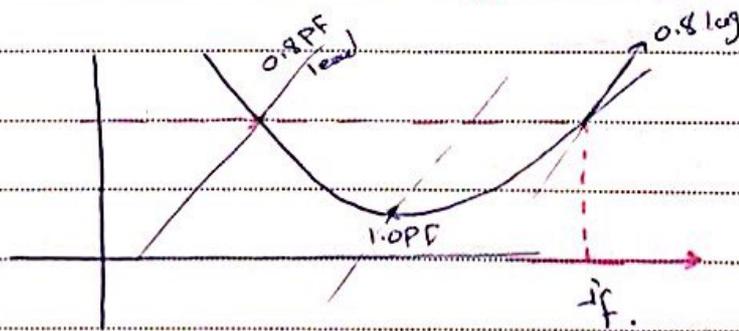$V_t = 3810.5 \text{ V}$
 $I_a = 105 \text{ A}$



b) $(4250)^2 = (V_t \times 0.8 + 105 \times 0.4)^2 + (V_t \times 0.6 - 105 \times 6)^2$

solve for $V_t \Rightarrow$ ~~4575.4 V~~

$V_t = 4575.4 \text{ Vph}$

$$V_L(L) = \sqrt{3} \times 4575.4 = 7.93 \text{ kV}$$

⇒ the terminal voltage excited the rated voltage ⇒ the Gen. Should be regulated to keep V_t at rated voltage by reducing the excitation.

Q6:

6000 KVA, 6.6 kV, Y-connected, P=2

f = 50 Hz S.G, $I_F = 125 \text{ A}$ ⇒

$V_{oc} = 8000 \text{ V}$ at rated speed

$I_F = 125 \text{ A} \rightarrow I_{sc} = 800 \text{ A}$ at rated speed.


at Full load and rated voltage.

$I_a R_a / \text{ph} = 3\%$ of the rated voltage.

Sol:

والتا لول الجهد المندرج هو
" R_a في كل طور، في"

(phase voltage).

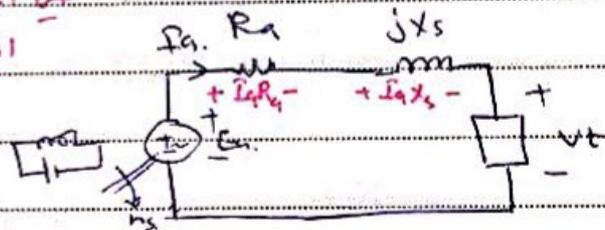

$$|Z_s| = \sqrt{R_a^2 + X_s^2}$$

$$= \frac{E_o \cdot \text{ph}}{I_{sc} \cdot \text{ph}}$$

$$= \frac{8000}{800}$$

$$= 10 \Omega$$

$$= 5.7 \Omega$$

$$= 5.7 \Omega$$



$$I_a \text{ rated} = \frac{6000 \times 10^3}{\sqrt{3} \times 6.6 \times 10^3} = 525 \text{ A}$$

$$\sqrt{3} \times 6.6 \times 10^3$$

$$I_a R_a = 525 \cdot R_a = 0.03 \times \frac{6600}{\sqrt{3}}$$

$$525 \cdot R_a = 114.3 \text{ V}$$

$$R_a = 0.21 \Omega$$


$$X_s = \sqrt{Z^2 - R_a^2}$$

$$= \sqrt{(5.7)^2 - (0.21)^2}$$



$$X_s = 5.69 \Omega$$

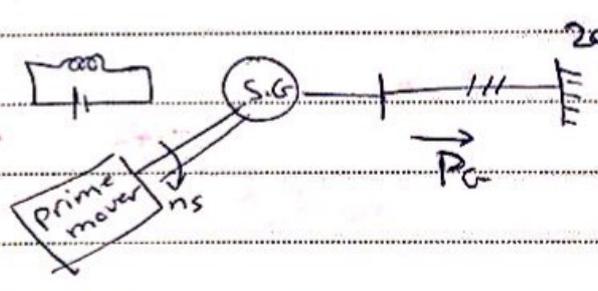Q7

10 KVA, 208V, $p=4$, $R_a \approx 0.0 \Omega$
 $X_s = 2 \Omega$, $P_{rot} \approx 0.0$ (rotational).



find $|E_a|$ and δ ?

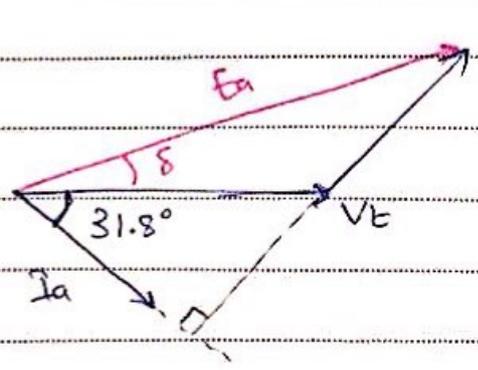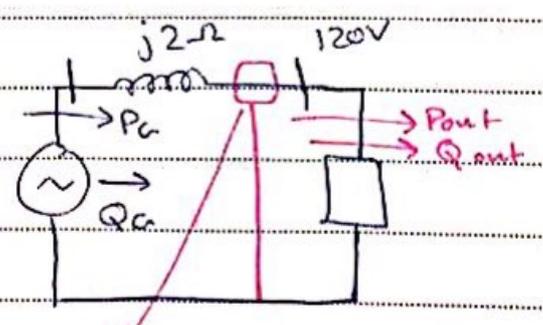

Power analyzer

power = 6 KW at 0.85 PF lag

$$\vec{E}_a = \vec{V}_t + j \vec{I}_a X_s$$

$$|I_a| = \frac{6000 / 0.85}{\sqrt{3} \times 208} = \frac{S_{3\phi}}{\sqrt{3} \times V_{LL}} = 19.6 \text{ A}$$

$$\vec{I}_a = 19.6 \angle -31.8^\circ$$


$$\vec{E}_a = \vec{V}_t + j \vec{I}_a X_s$$

~~$$|I_a| = \frac{6000}{\sqrt{3} \times 0.85}$$~~


$$\begin{aligned} \vec{E}_a &= 120 \angle 0^\circ + 19.6 \angle -31.8^\circ \times 2 \angle 90^\circ \\ &= 144.6 \angle 13.3^\circ \text{ V ph.} \end{aligned}$$

$$|E_{all}| = \sqrt{3} \times 144.6 = 250.5 \text{ V}$$


[b]

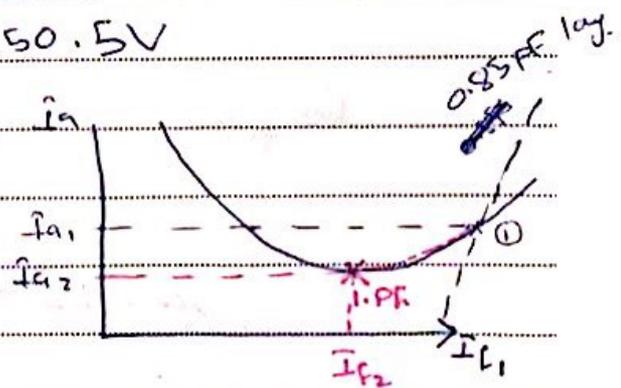

$$Q_{3\phi} = P_{3\phi} (31.8^\circ)$$

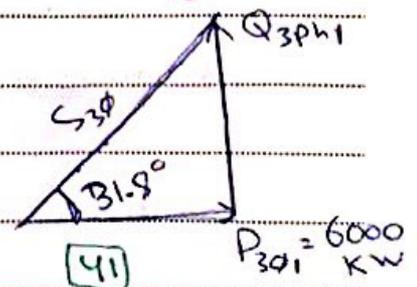

Q7:1

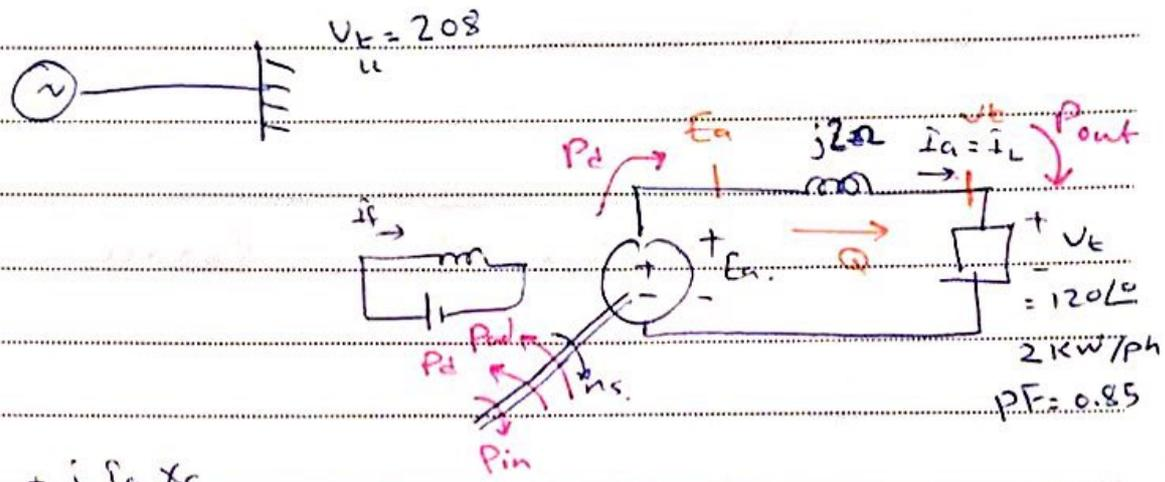


$$E_a = V_t + j I_a X_s$$

$$= 120 \angle 0^\circ + 19.6 \angle -31.8^\circ + 2 \angle 90^\circ$$

$$|I_a| = 19.6 \text{ A}$$

$$I_a = 19.6 \text{ A} \angle -31.8^\circ$$



$$E_a = 144.6 \angle 13.3^\circ$$

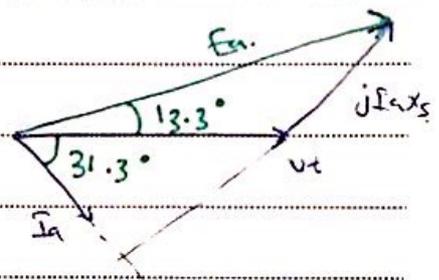

Since $R_a \approx 0.0$

$$P_{out} = P_d$$

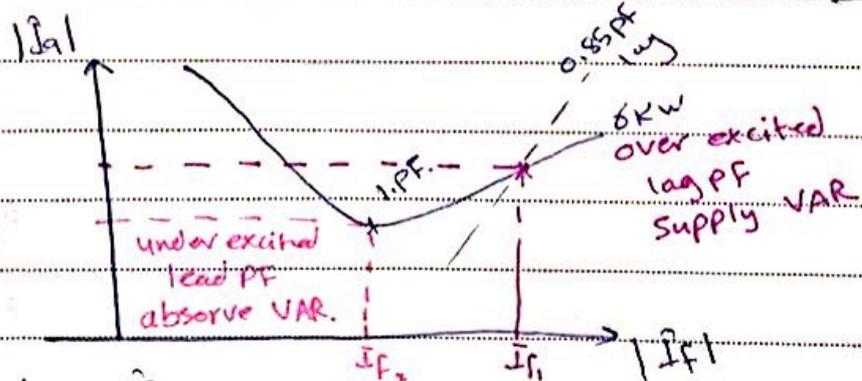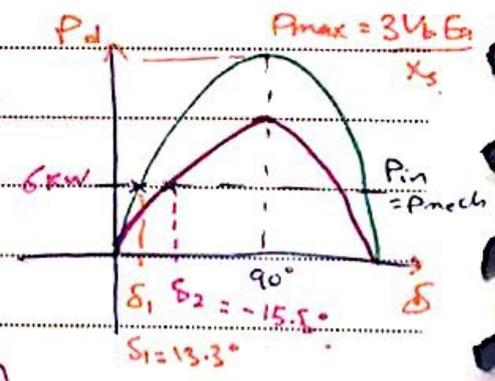
$$6 \text{ kW} = 3 V_t I_a \cos \theta = 3 V_t E_a \sin \delta$$



Find $\frac{\Delta I_f}{I_{f1}}$

$$\frac{\Delta I_f}{I_{f1}} = \frac{I_{f2} - I_{f1}}{I_{f1}} = \frac{I_{f2}}{I_{f1}} - 1 = \left| \frac{E_{a2}}{E_{a1}} \right| > 1$$

42

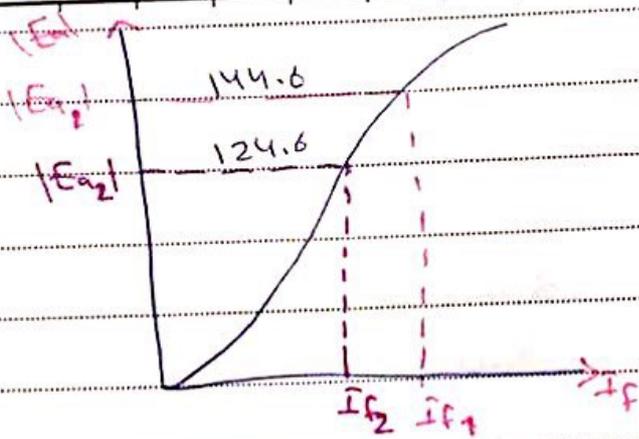

$$\frac{E_{a1}}{I_{f1}} = \frac{E_{a2}}{I_{f2}}$$

$$\frac{I_{f1}}{E_{a1}} = \frac{I_{f2}}{E_{a2}}$$

$$\frac{I_{f2}}{I_{f1}} = \frac{E_{a2}}{E_{a1}}$$

$$|E_{a2}| = \sqrt{(V_t \cos \theta_2 + I_{a2} R_a)^2 + (V_t \sin \theta_2 + I_{a2} X_s)^2}$$

$$3V_t I_{a1} \cos \theta_1 = 3V_t I_{a2} \cos \theta_2$$

$$3 \times 120 \times 19.6 \times 0.85 = 3 \times 120 \times I_{a2} \times 1.0$$

$$I_{a2} = \frac{19.6 \times 0.85}{1.0} = 16.7 \text{ A}$$

$$\vec{E}_{a2} = V_t + j I_{a2} X_s$$

$$= 120 \angle 0^\circ + 16.7 \angle 0^\circ \times 2 \angle 90^\circ$$

$$\vec{E}_{a2} = 124.6 \angle 15.5^\circ \text{ V}$$

$$\frac{\Delta I_f}{I_{f1}} = \frac{124.6}{144.6} - 1 = -0.1314$$




$$\% \frac{\hat{\Delta}F}{f_f} = -13.1\%$$

Q8

25KVA, 230V, 3ph, p=4, f=60Hz.

Y-connected S.C.

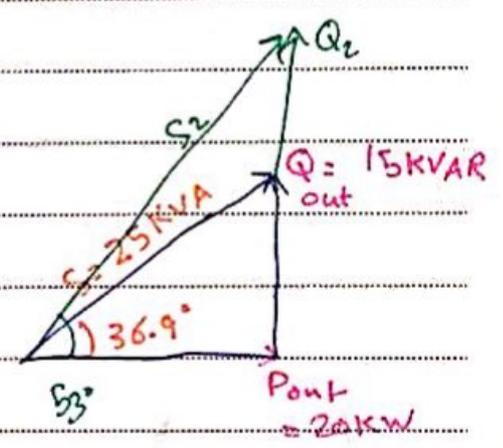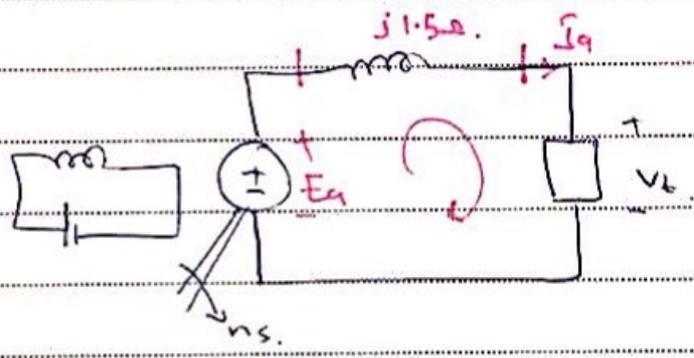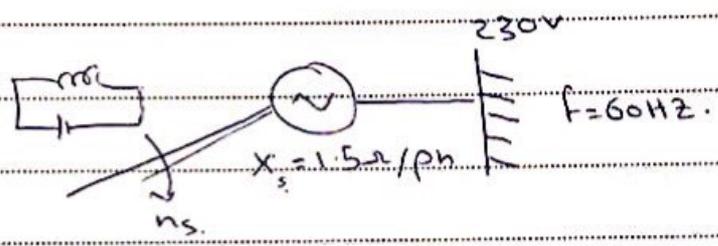$X_s = 1.5 \Omega / \text{ph}$ $\rightarrow R_a \approx 0$.



$$|I_{a \text{ ph}}| = I_L = \frac{S_{3\phi}}{\sqrt{3} V_{LL}}$$

$$= \frac{25 \times 10^3}{\sqrt{3} \times 230} = 62.7 \text{ A.}$$



$$I_a = 62.7 \angle -36.9^\circ \text{ A}$$

$$\vec{E}_a = \vec{V}_t + j I_a X_s$$

$$= \frac{230}{\sqrt{3}} \angle 0 + \left[j \left(62.7 \angle -36.9^\circ \right) \times 1.5 \angle 90^\circ \right] = 203.6 \angle 21.7^\circ$$

$$|\vec{E}_{aLL}| = \sqrt{3} \times 203.6 = 352.7 \text{ V}$$

44

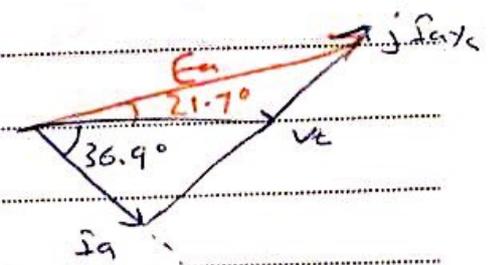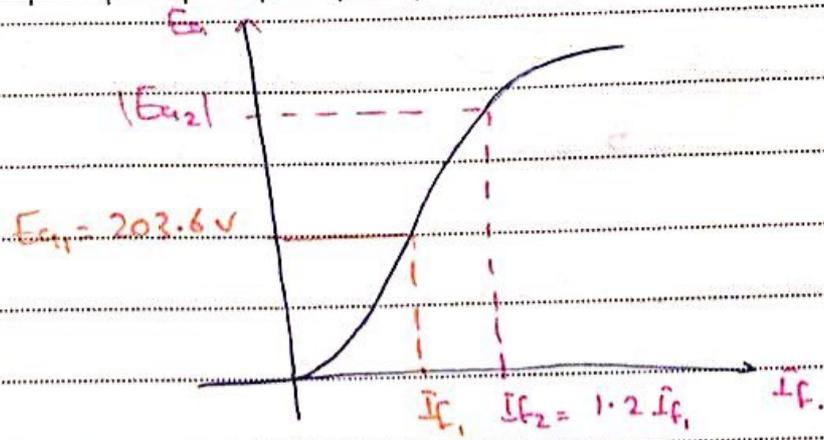



$E_a \propto I_f$ linear relation

$$E_{a2} = 1.2 E_{a1}$$

$$|E_{a2}| = 1.2 \times 203.6$$

$$|E_{a2}| = 244.3 \text{ V}$$

Steady-state stability limit

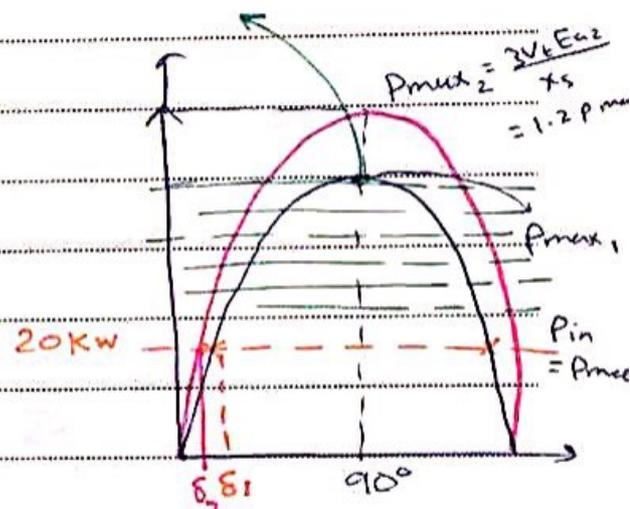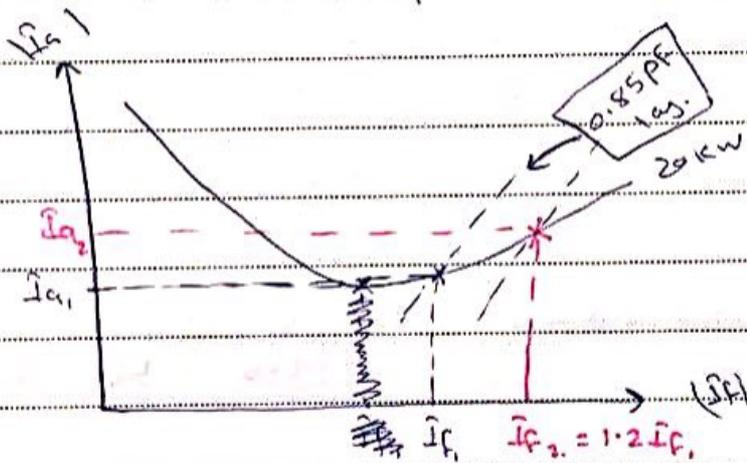

$S_{out} = S_{rated}$ at 0.8 PF lag

$$= 25 \text{ KVA}$$

$$\theta = \cos^{-1}(0.8) = 36.9^\circ$$

$$P = 3Vt I_{a1} \cos \theta_1 = 3Vt I_{a2} \cos \theta_2$$

$$P = \frac{3Vt E_{a1} \sin \delta_1}{X_s} = \frac{3Vt E_{a2} \sin \delta_2}{X_s}$$

$$E_{a2} \sin \delta_1 = E_{a2} \sin \delta_2 = 1.2 E_{a1} \sin \delta_1$$

$$I_{a2} = \frac{\vec{E}_{a2} - \vec{V}_E}{jX_s} = \frac{|E_{a2}| \angle \delta_2 - \frac{230}{\sqrt{3}} \angle 0^\circ}{1.5 \angle 90^\circ} = \frac{1.2 E_{a1} \angle \delta_2 - \frac{230}{\sqrt{3}} \angle 0^\circ}{1.5 \angle 90^\circ}$$

$$E_{a1} \sin \delta_1 = E_{a2} \sin \delta_2 = 1.2 E_{a1} \sin \delta_2$$

$$\sin \delta_2 = \frac{\sin \delta_1}{1.2} = \frac{\sin(21.7^\circ)}{1.2} = 0.30$$

$$\delta_2 = 17.9^\circ$$

$$I_{a2} = \frac{1.2 \times 203.6 \angle 17.9^\circ - \frac{230}{\sqrt{3}} \angle 0^\circ}{1.5 \angle 90^\circ} = 83.2 \angle -53^\circ \text{ A}$$

$$PF_2 = \cos \theta_2 = \cos(53^\circ) = 0.60 \text{ lag.}$$

$$Q_2 = 3V_b I_{a2} \sin \theta_2 = \frac{3V_b}{X_s} [E_{a2} \cos \delta_2 - V_E]$$

$$= 3 \times \frac{230}{\sqrt{3}} * 83.2 * 0.8 = 3 * \frac{230}{1.5 \sqrt{3}} \left[244.3 \cos \left[(17.9^\circ) - \frac{230^\circ}{\sqrt{3}} \right] \right]$$

$$Q_2 = 26.4 \text{ KVA}$$


$$S_2 = \frac{P_2}{PF_2} = \sqrt{P_2^2 + Q_2^2}$$

$$S_2 = \frac{20 \text{ k}}{0.6} = \sqrt{(20)^2 + (26.4)^2} \text{ k}$$


$$S_2 = 33.1 \text{ KVAR.}$$

Q10

3ph, s.g, $p=6$, $f=60\text{Hz}$, $X_s=4\Omega$, Y connec.
 $|V_{tLL}| = 2300\text{V}$, $|E_{aLL}| = 2300\text{V}$, $\delta = 15^\circ$

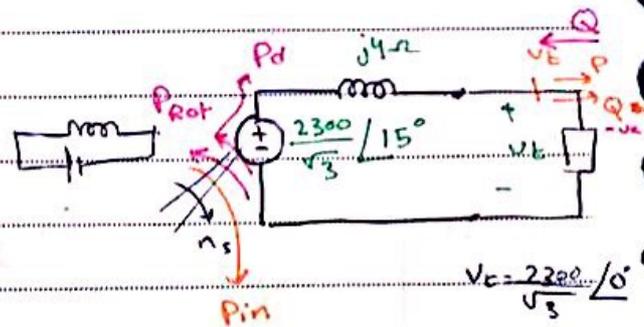

power is generated $\leftarrow \delta$

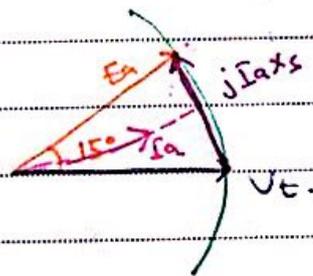

I_a lead!
 $(I_a \text{ h. } I_a X_s)$

$$E_a = \vec{V}_t + j I_a X_s$$

Find a) \vec{I}_a (Armature current phasor) ?!

$$\vec{I}_a = \frac{\vec{E}_a - \vec{V}_a}{jX_s} = \frac{\left(\frac{2300}{\sqrt{3}} \angle 15^\circ\right) - \left(\frac{2300}{\sqrt{3}} \angle 0^\circ\right)}{4 \angle 90^\circ}$$

$$\vec{I}_a = 86.6 \angle +7.5^\circ$$

b) PF = ?!

$$\text{PF} = \cos \theta = \cos(7.5) = 0.991 \text{ lead}$$

48

c) $P_{out}, Q_{out} = ?$

$$P_{out} = \sqrt{3} V_L I_L \cos \theta = 3 V_E I_a \cos \theta, T_d = \frac{P_{in}}{\omega_s}$$

$$= \sqrt{3} * 2300 * 86.6 * 0.991$$

$$= 342 \text{ kW}$$

$$T_d = 342 \text{ K} / 12$$

$$T_d = 2.74 \text{ KN}$$

$$Q_{out} = -\sqrt{3} V_L I_L \sin \theta$$

$$= -\sqrt{3} * 2300 * 86.6 \sin(7.5)$$

$$= -45 \text{ KVAR}$$

OR $Q = \frac{3V_E}{X_s} [E_a \cos \delta - V_E]$

$$= \frac{3 * \frac{2300}{\sqrt{3}}}{4} \left[\frac{2300}{\sqrt{3}} \cos 15 - \frac{2300}{\sqrt{3}} \right]$$


"Gen. 11 ac abla Q"

d) $P_d = ?$


$$P_{dmax} = \frac{3V_E \cdot E_a}{X_s} \Big|_{\delta=90^\circ}$$

$$= 3 * \frac{2300}{\sqrt{3}} * \frac{2300}{\sqrt{3}}$$

$$4$$

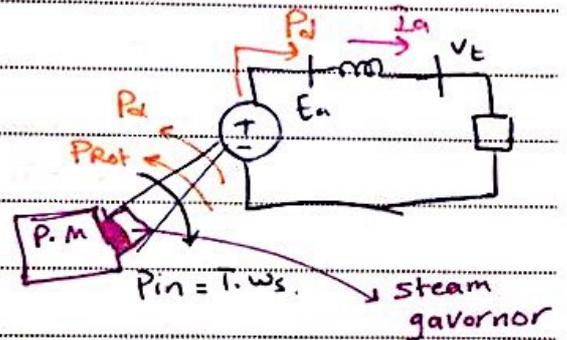

$$P_{dmax} = 1.32 \text{ MW}$$

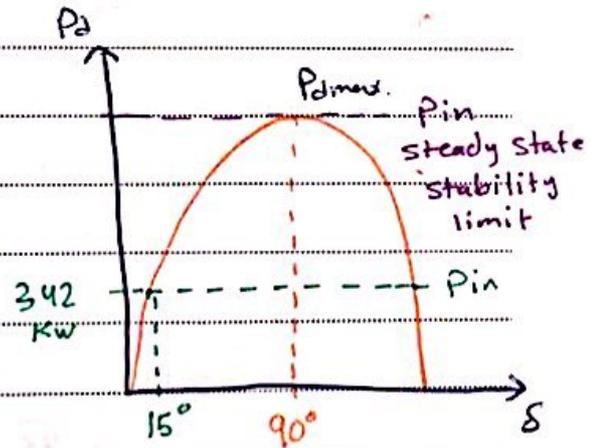


* Steady State stability limit occurs at $\delta = 90^\circ$

$$I_q = \frac{\vec{E}_a - \vec{V}_E}{jX_s} = \frac{\frac{2300}{\sqrt{3}} \angle 90^\circ - \frac{2300}{\sqrt{3}} \angle 0^\circ}{4 \angle 90^\circ} = 4.69 \angle 45^\circ \text{ A}$$

PF = $\cos 45 = 0.707$ "leading"

(49)

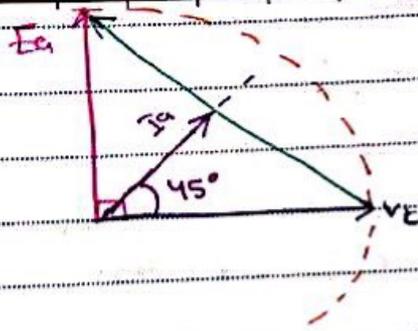

$$T_{in} = T_{mech} = T_d \quad (\text{Prot} \approx 0.1)$$

$$T_d = \frac{P_{in}}{\omega_s}$$

$$f = 60 \text{ Hz}, \quad p = 6, \quad n_s = 1200 \text{ rpm}$$

$$\omega_s = \frac{2\pi n_s}{60} = \frac{2\pi \times 1200}{60}$$

$$\omega_s = 40\pi = 125 \text{ rad/s}$$

$$T_d = \frac{P_{in}}{\omega_s} = \frac{1.32 \times 10^6}{125} = 10.5 \text{ kNm}$$

Q11

10 MVA, 12 kV, $p = 2$, $f = 60 \text{ Hz}$, S.G., γ -con.

→ rated volt is 10 MVA in 11.8 kV

$$S_{\text{rated}} = 3 V_{L \text{ rated}} I_{a \text{ rated}}$$

$$= \sqrt{3} V_{LL \text{ rated}} I_{L \text{ rated}}$$

$$I_{a \text{ rated}} = I_{L \text{ rated}} = \frac{S_{\text{rated}}}{\sqrt{3} * V_{LL \text{ rated}}}$$


50

$$I_{a, \text{rated}} = \frac{10 \times 10^6}{\sqrt{3} * 12 \times 10^3} = 481 \text{ A}$$

O.C test at \uparrow core losses rated voltage $\Rightarrow P_{\text{core}} = 75 \text{ KW}$


S.C test at $\underline{480 \text{ A}}$ rated current $\Rightarrow P_{\text{loss}} = 60 \text{ KW}$

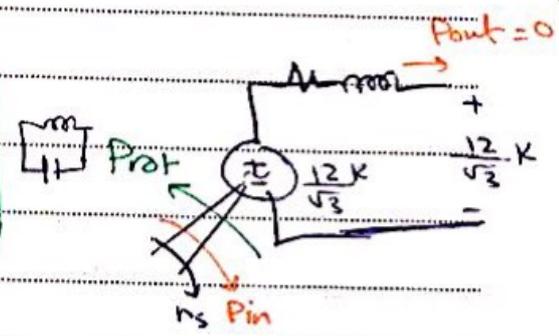if $P_{\text{in}} = P_{\text{rot}}$ run in constant speed
constant (constant speed)




$$P_{\text{Fandw}} = 55 \text{ KW}$$

Find $\eta = ?!$
PF 0.8

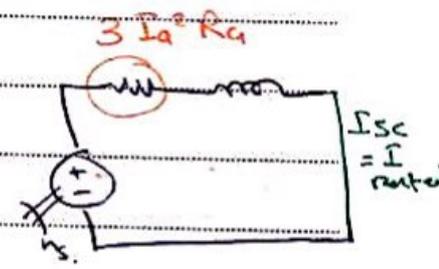
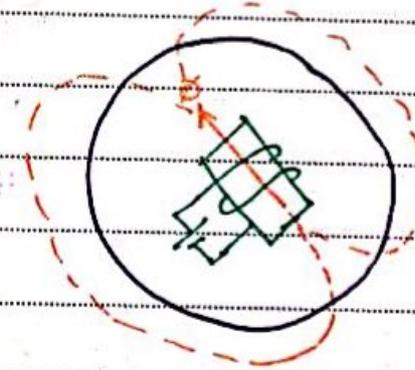
$$\eta = \frac{P_{\text{out rated}}}{P_{\text{out rated}} + P_{\text{rot}} + P_{\text{cu rated}}}$$




$$P_{\text{rot}} = S_{\text{rated}} * \text{PF}$$

$$= 10 \text{ M} * 0.8$$

$$= 8 \text{ MW}$$
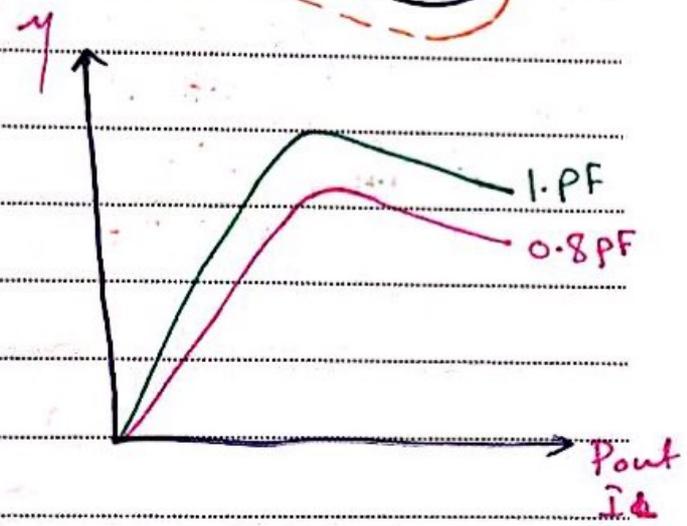
$$\eta = \frac{8 \times 10^6}{8 \times 10^6 + P_{\text{core}} + P_{\text{Fandw}} + P_{\text{cu}}}$$



$$\eta = \frac{8 \times 10^6}{8 \times 10^6 + 75 \times 10^3 + 55 \times 10^3 + 60 \times 10^3}$$


$$\eta = 97.7\%$$

$$\Sigma P_{\text{losses}} = P_{\text{core}} + P_{\text{Fandw}} + P_{\text{Cu}}$$


P_{Rob.}

P_{Cu} = ~~power~~ winding copper losses

Q12

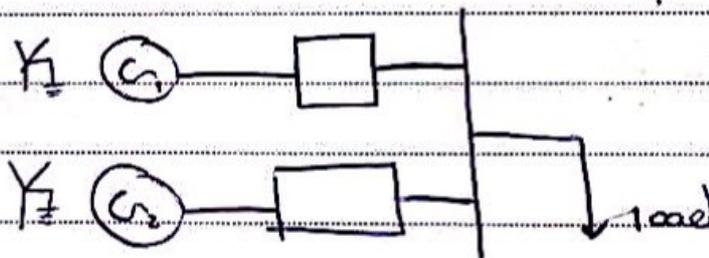

parallel operation

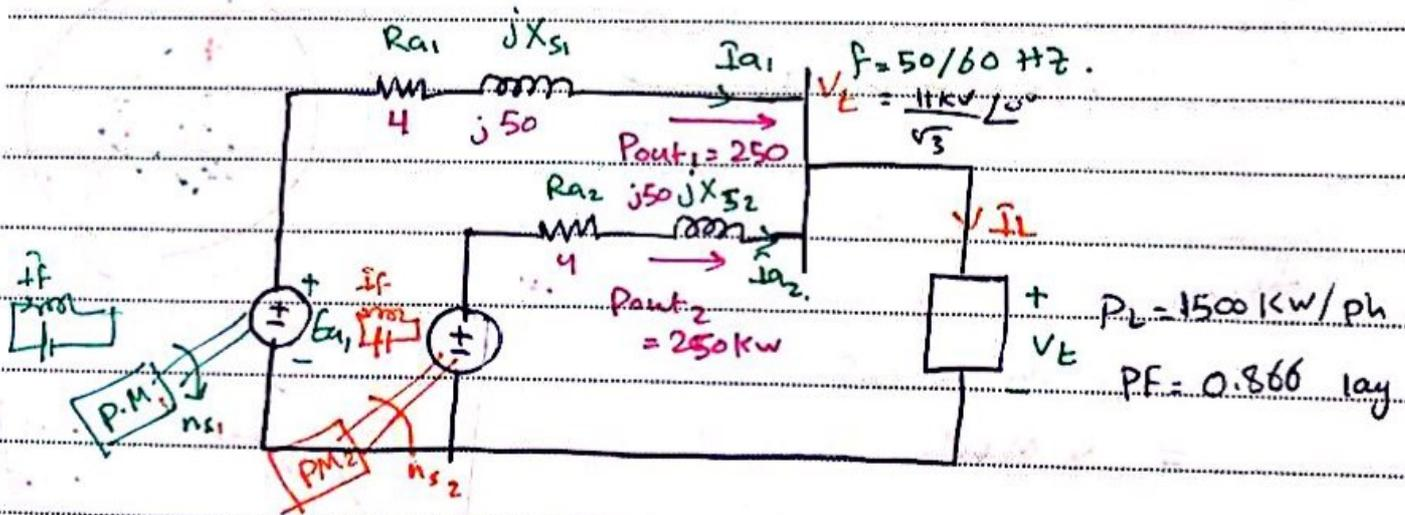

By KCL $\vec{I}_L = \vec{I}_{a1} + \vec{I}_{a2}$ "as a vector"

$$V_L = \frac{11 \text{ kV}}{\sqrt{3}} \angle 0^\circ$$

$$P_{out 1} = P_{out 2} = \frac{P_L}{2} = \frac{1500}{2} = 750 \text{ kW / Gen}$$

$$P_{out / phase} = \frac{750 \text{ kW}}{3} = 250 \text{ kW}$$

$$|I_{a1}| = 50 \text{ A at lag PF.}$$


$$\text{Find } PF_1 = \cos \theta_1 = ?$$

$$PF = 0.866 \text{ lag}$$

$$\cos \theta_L \rightarrow \theta_L = \cos^{-1}(0.866)$$

$$\theta_L = 30^\circ$$

load

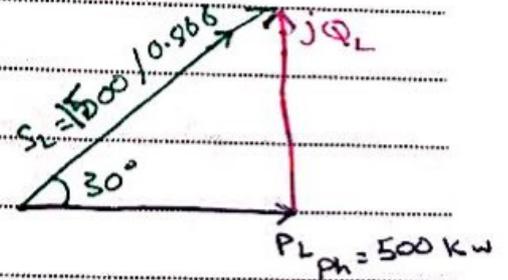

$$\begin{aligned} Q_L &= P_L * \tan \theta_L \\ &= 500 \text{ kW} * \tan(30) \\ &= 288 \text{ KVAR} \end{aligned}$$

$$P_L = P_{out 1} + P_{out 2}$$

$$Q_L = Q_{out 1} + Q_{out 2}$$

$$P_{out 1} = \sqrt{3} V_L I_{a1} \cos \theta_1 = V_{ph} \cdot I_{ph} \cos \theta$$

$$250 \times 10^3 = \frac{11 \times 10^3}{\sqrt{3}} \times 50 \times PF_1$$

$$PF_1 = \cos \theta_1 = 0.787 \rightarrow \text{lagging.}$$

$$\theta_1 = 38^\circ$$

$$\vec{I}_{a1} = 50 \angle -38^\circ \text{ A}, \quad \vec{I}_{a2} = \vec{I}_L - \vec{I}_{a1}$$

$$|\vec{I}_L| = \frac{P}{\sqrt{3} V_L * PF} = \frac{1500 \times 10^3}{\sqrt{3} * 11 \times 10^3 * 0.866}$$

$$\boxed{\vec{I}_L = 90.9 \text{ A}}$$

$$\vec{I}_{a2} = 90.9 \angle -30^\circ - 50 \angle -38^\circ$$

$$= 85.7 \angle +62^\circ \text{ A}$$

$$PF_2 = \because \cos \theta_2 = \cos^\alpha (62)$$

$$= 0.470 \text{ leading.}$$

$$Q_1 = \sqrt{3} V_L I_{L1} \sin \theta_1$$


$$= \sqrt{3} * 11 \times 10^3 * 50 * \sin(38^\circ) = 586 \text{ KVAR}$$

$$\vec{E}_{a1} = V_t + (R_{a1} + jX_{s1}) \vec{I}_{a1}$$

$$\vec{E}_{a2} = V_t + (R_{a2} + jX_{s2}) \vec{I}_{a2}$$

$$VR_1 = \frac{|E_{a1}| - |V_t|}{|V_t|} \times 100\%$$

$$VR_2 = \frac{|E_{a2}| - |V_t|}{|V_t|} \times 100\%$$

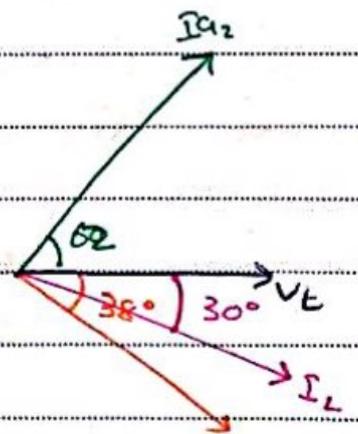




Example 5-2

480 V, 60 Hz, Δ -Connection SG
 $p=4$, $X_s = 6.1 \Omega$, $R_a = 0.015 \Omega$
 at full-load condition \Rightarrow

(Line) $I_{LFL} = 1200$ A at 0.8 pf lag.

$P_{F+W} = 40$ kW \Rightarrow $P_{core} = 30$ kW.

Sol:

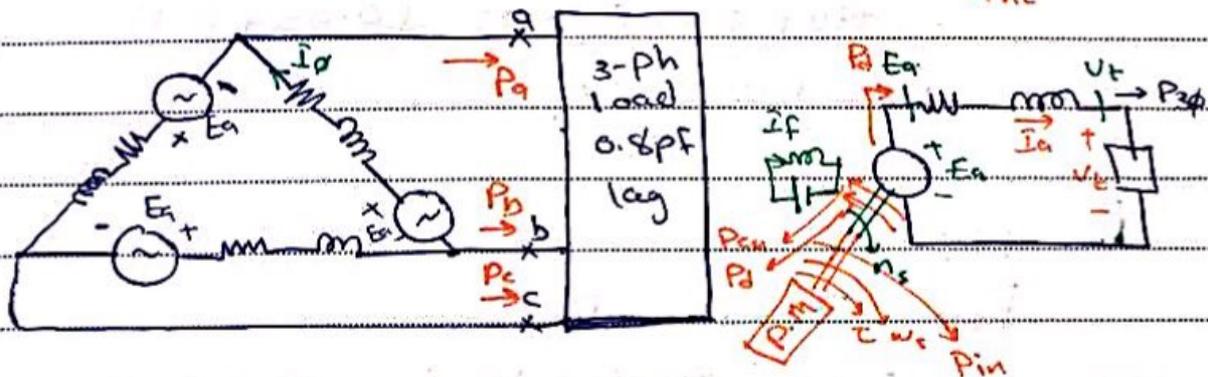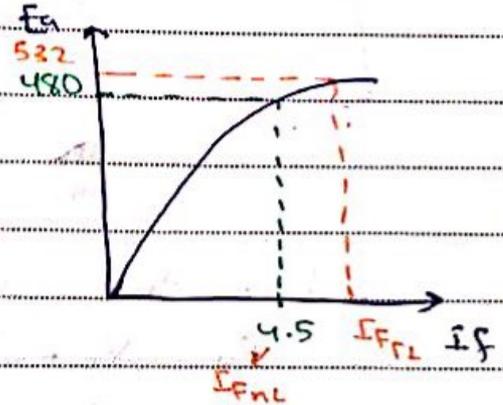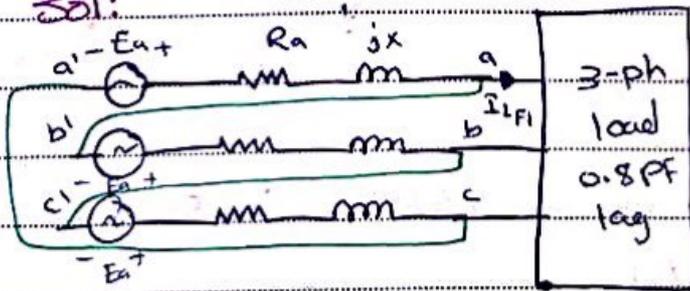

Find a) $n_s = ?!$

$$n_s = \frac{120f}{P} = \frac{120 \times 60}{4} = 1800 \text{ rpm}$$

b) $I_f = ?!$



$E_{aNL} = 480$ V ; from the O.C.C $\Rightarrow I_f = 54.5$ A

In Δ -connection:

$$V_\phi = V_{LL}$$

$$I_{ph} = \frac{I_L}{\sqrt{3}} = \frac{1200}{\sqrt{3}} = 692.8 \text{ A}, \theta = \cos^{-1}(0.8) = 36.9^\circ$$

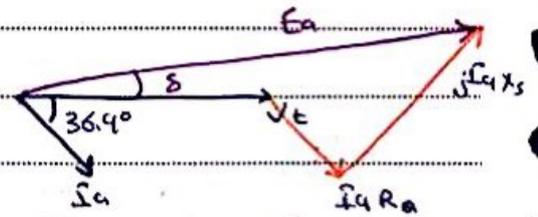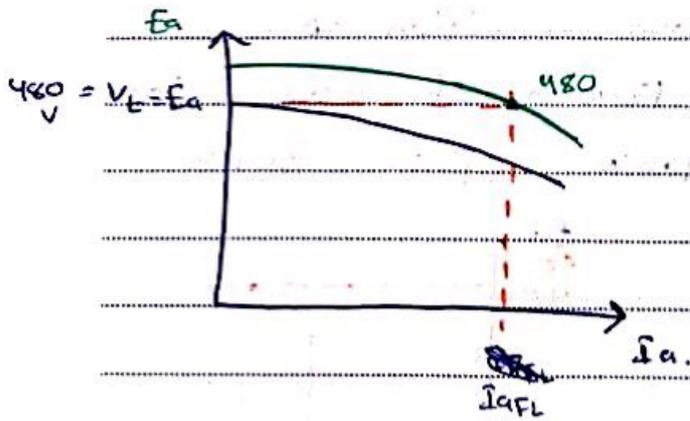c) under full-load condition, $I_L = 1200\text{ A}$, $p = 0.8$, lag
 $V_t = V_{\text{rated}}$ Find I_f ?



from the curve for $E_a = 532\text{ V} \Rightarrow I_f = 5.7\text{ A}$.

$$E_a = V_t + I_a(R_a + jX_s)$$

$$= 480 + 692.8 \angle -36.9^\circ (0.015 + j0.1)$$

$E_a = 532 \angle 5.3^\circ \text{ V}$

d) $P_{3\phi} = ?$

$$P_{3\phi} = P_a + P_b + P_c$$

$$= V_a I_a \cos\theta + V_b I_b \cos\theta + V_c I_c \cos\theta$$

$$= 3 V_a I_a \cos\theta$$

$$= 3 * 480 * 692.8 * 0.8$$


$$= \sqrt{3} V_L I_L \cos\theta = \sqrt{3} * 480 * 1200 * 0.8$$

$P_{3\phi} = 798 \text{ kW}$

$$P_{in} = T \cdot \omega_s$$

$$P_{in} = P_{out} + P_{\text{cwt}} + P_{\text{core}} + P_{F+W}$$
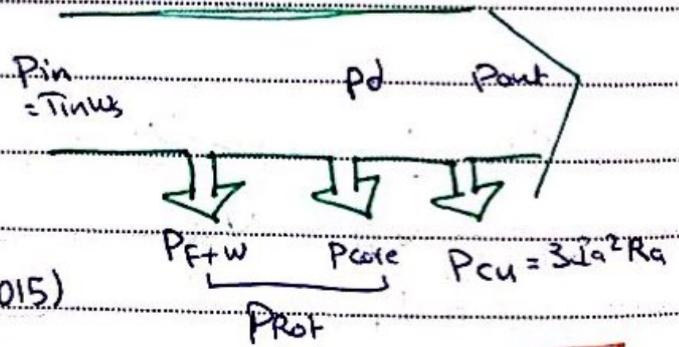
$$= 798 \times 10^3 + \underbrace{\sum P_{\text{losses}}}_{30 \times 10^3 + 40 \times 10^3}$$




561

$$P_{in} = 889.6 \text{ KW}$$

$$\eta_{FL} = \frac{P_{out}}{P_{in}} \times 100\% = \frac{798}{889.6} \times 100\% = 89.8\%$$

[E] if the terminal are open $\Rightarrow V_t = E_a = 532 \text{ V}$

$$\begin{aligned} \%VR &= \frac{|V_{nd} - |V_{FL}|}{|V_{FL}|} \times 100\% \\ &= \frac{532 - 480}{480} \times 100\% \\ &= 10.8\% \end{aligned}$$

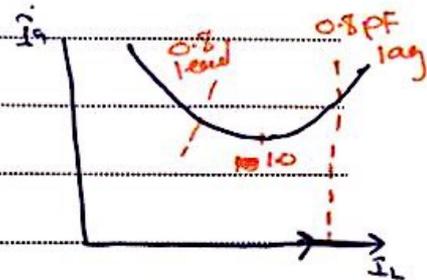


[F] for 0.8 PF leading, $I_2 = 1200 \text{ A}$ (excitation)

$$\begin{aligned} \vec{E}_a &= V_t + \vec{I}_a (R_a + jX_s) \\ &= 480 \angle 0^\circ + 692.8 \angle +36.9^\circ (0.05 + j0.15) \end{aligned}$$

$$E_a = 451 \angle 7.1^\circ \text{ V}$$

\Rightarrow from the curve $\Rightarrow I_f \Rightarrow 0.8 \text{ lead PF}$

$$\Rightarrow I_f = 4.1 \text{ A}$$

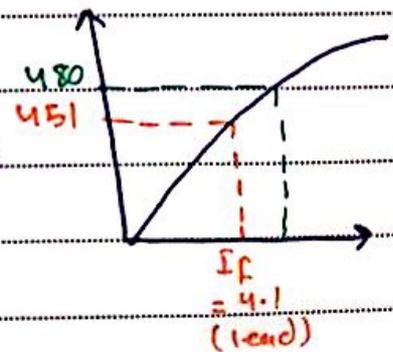

Q912 KV, $f = 60\text{ Hz}$, Δ connected S.G $X_s = 15 \Omega$, $E_{oc} = 13\text{ KV}$ **Q** Find $P_{max} = ?$


$$P_{max} = \frac{3 V_L E_a}{X_s} \quad \delta = 90^\circ = \frac{V_{LL} \times E_{LL}}{X_s}$$
$$= \frac{12\text{ K} \times 13\text{ K}}{15}$$

$$\vec{I}_a = \frac{\vec{E}_a - \vec{V}_L}{j X_s}$$


$$Q = \sqrt{3} V_L I_L \sin \theta$$

58

* Synchronous Motor $\delta \Delta$

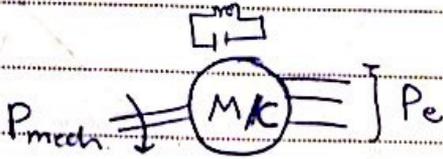


M/C \rightarrow generator

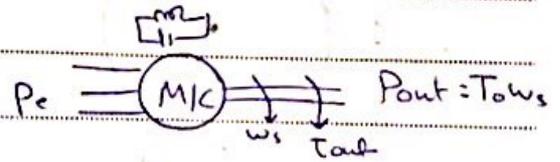


M/C \rightarrow motor


* Construction $\delta \Delta$

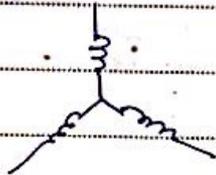

Y-connection
armature

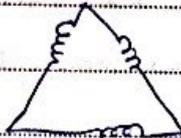

Δ -connection
armature

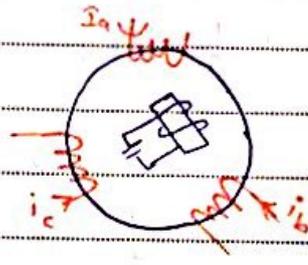


rotor \rightarrow field

\therefore Stator \rightarrow armature




* Synch Motor requires 2 electric supplies $\delta \Delta$

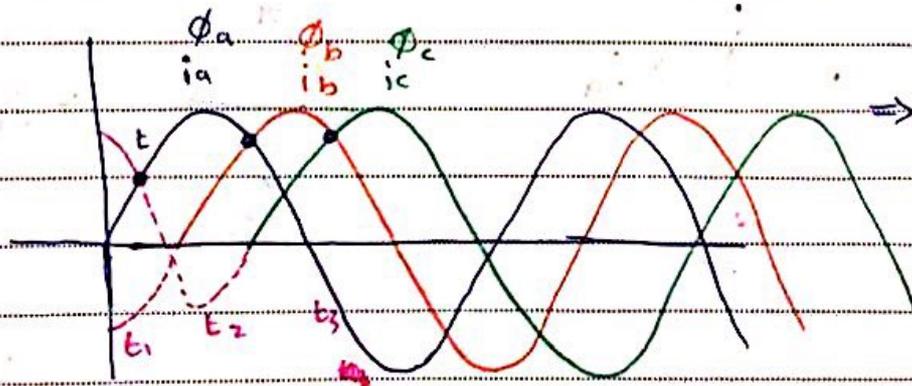- 1) AC 3 ϕ source to energize the armature
- 2) DC source to energize the field winding

Notes $\delta \Delta$ synch motor is not a self-starting motor, meaning when you supply AC and DC sources it won't move immediately.





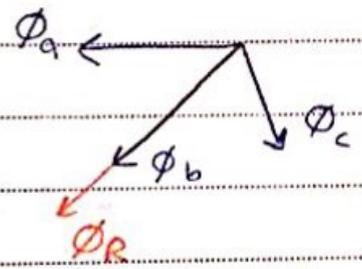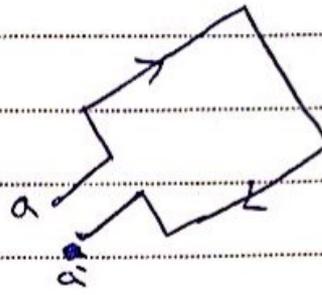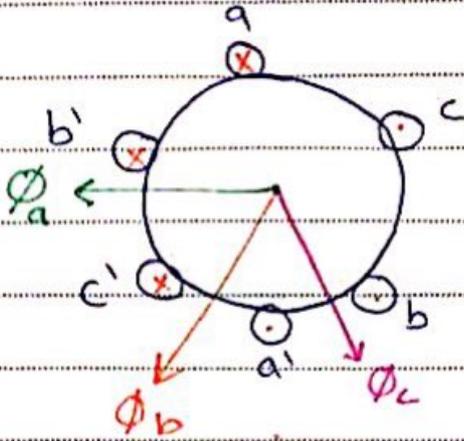\Rightarrow at instant t_1
 i_a, i_c are +ve
 i_b is -ve.





$t = t_1$

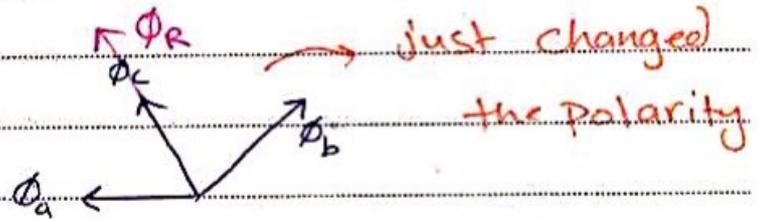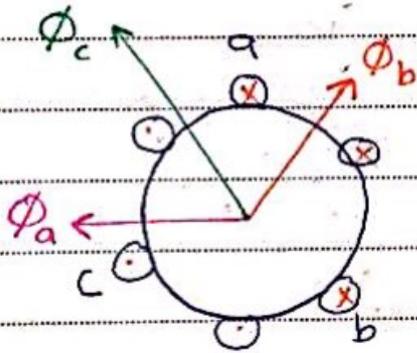* the flux generated is time varying and stationary \Rightarrow at instant $t_2 \Rightarrow$ i_a i_b $+ve$
 i_c $-ve$



$t = t_2$

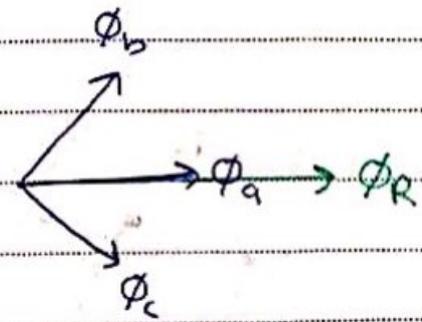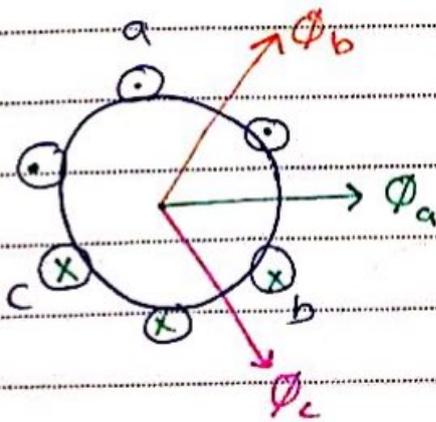\Rightarrow at instant $t_3 \Rightarrow$ i_b i_c $+ve$
 i_a $-ve$



its rotating clock wise (rotating field)

if we change the sequence reversing any 2-phases \rightarrow anti-clock wise

* the rotating flux runs at synch speed

$$n_s = \frac{120 f}{P}$$

ex. plains use frequency 400 Hz.

P	50 Hz	60 Hz
2	3000	3600
4	1500	1800
6	1000	1200
8	750	900
10	600	720



\Rightarrow Speed of motor ~~doesn't~~ doesn't depend on input voltage

$$E = 4.44 f N_p \Phi$$


just depend on f and Φ

$\uparrow f \rightarrow \Phi \downarrow$

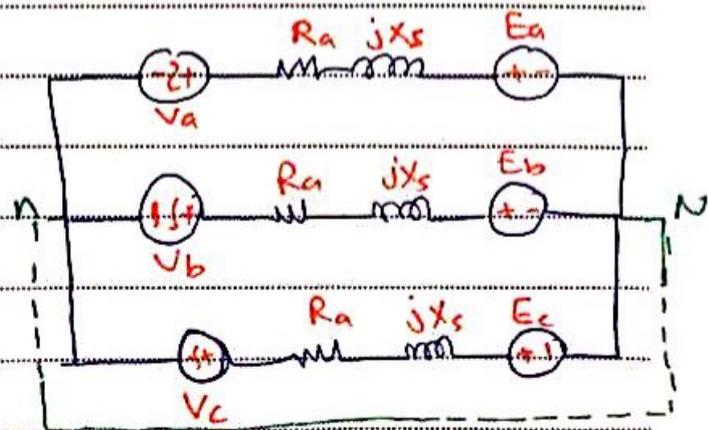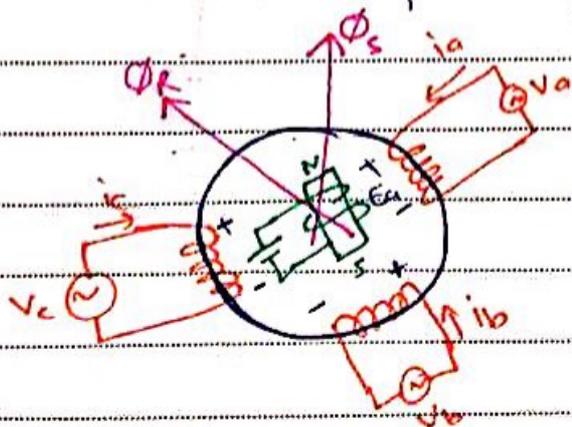Φ_s will induce voltage in the winding that has a polarity opposing to the source.




Per-Phase equivalent ckt.

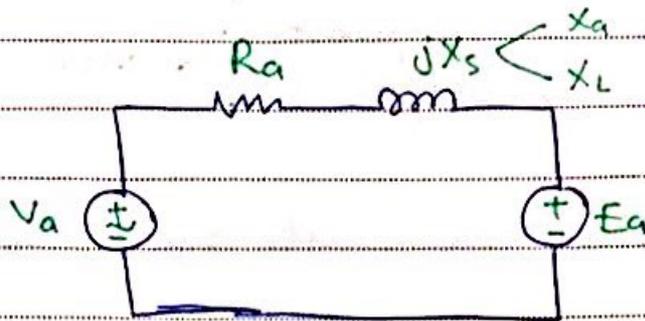


When we turn on DC excitation we create Φ_R i will have a pull in Φ_R Φ_s will move together (note: $\Phi_R \rightarrow$ constant, $\Phi_s \rightarrow$ changes sinusoidally) but after 10ms polarity will reverse Φ_R Φ_s will repulse causing the motor to keep alternating
 Sol \rightarrow we need a starting machines.

- ① reduced freq starting
- ② external prime mover
- ③ induction.

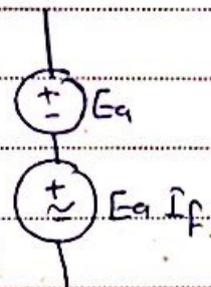note :- when Φ_R rotates it will also induce voltage is series with E_a



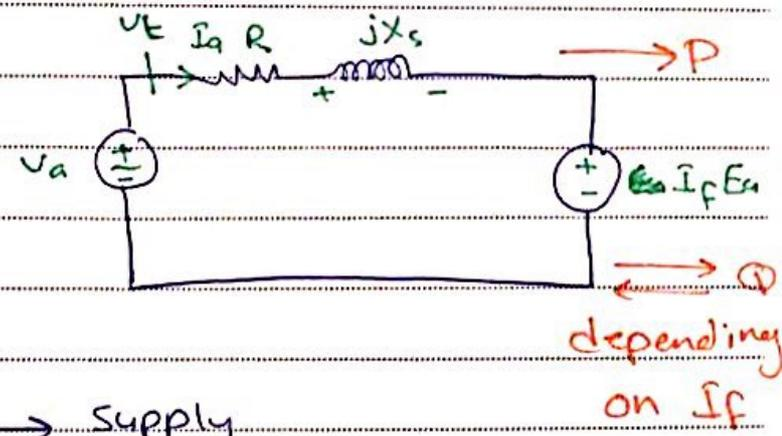E_a is represented with the voltage drop on jX_s



over excite motor \rightarrow supply


under excite supply \rightarrow motor (Synchronous Condens Capacit)

Adv of Synch motor \rightarrow acts as Synch capacitor or Synch inductor


$$n_s = \frac{120f}{P}$$

* Modes of operation of synchronous Motor:

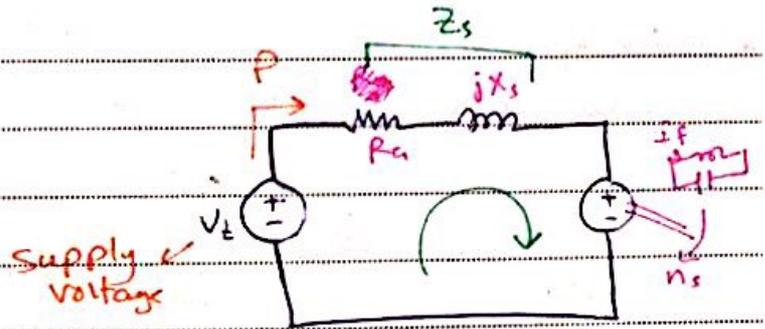- a- unity PF
- b- lagging PF
- c- leading PF



"Single phase equivalent circuit of S.M"

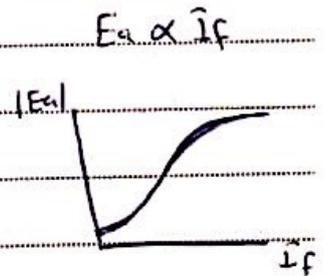


consider V_t as a reference.

a) unity PF

$$\vec{V}_t = \vec{I}_a (R_a + jX_s) + \vec{E}_a$$

$$\vec{E}_a = V_t - \vec{I}_a (R_a + jX_s)$$


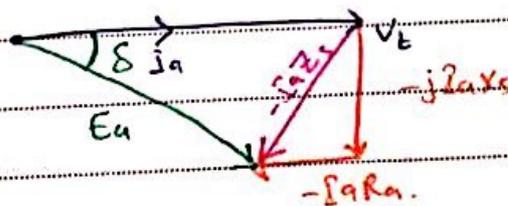
$$= \vec{V}_t - \vec{I}_a R_a - \vec{I}_a jX_s$$




E_a lags V_t by angle δ

(power angle torque angle)

δ is -ve

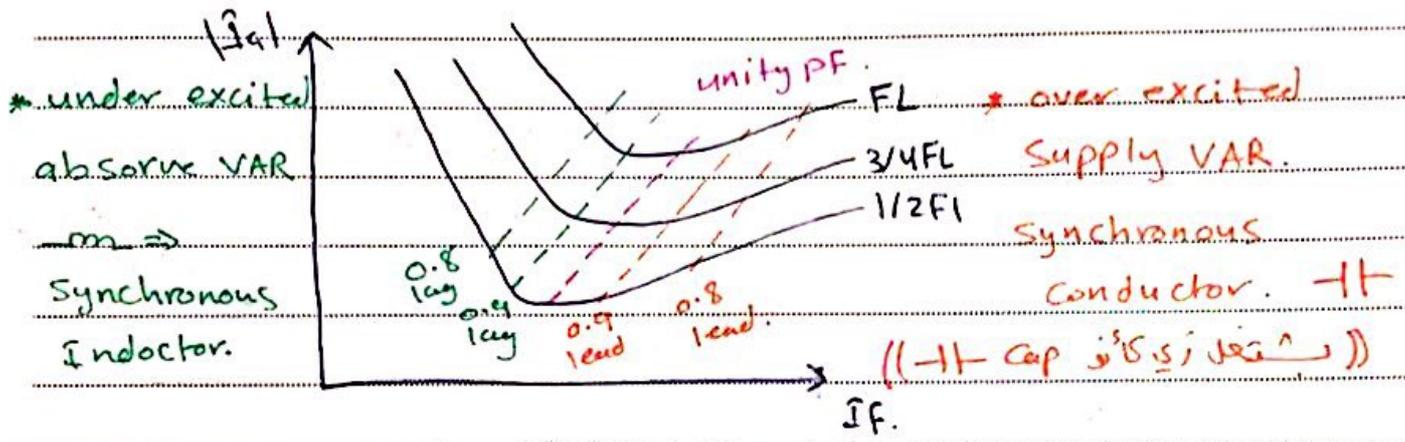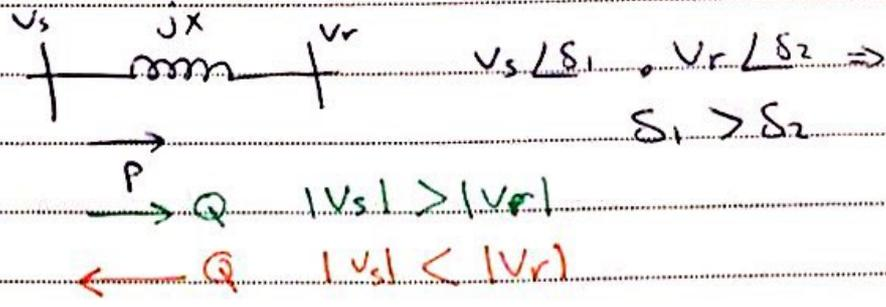


b) lag pf condition :-

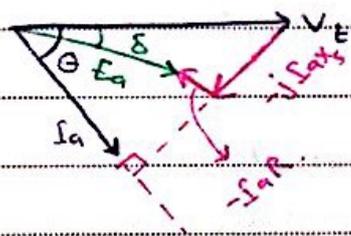

$E_a \cos \delta < V_t \Rightarrow$ M/C is under excited absorb VAR.

$\delta < \theta \Rightarrow$ P flow from V_t toward to M/C.

c) lead pf

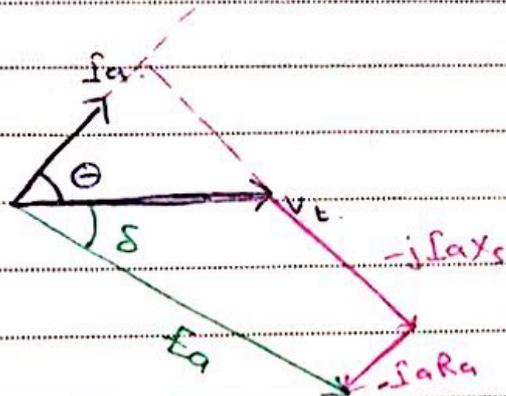

$$E_a \cos \delta > V_t$$


MIC is over excited

supply VAR


work as synchronous condenser (capacitor)

If R_a is negligible $R_a \approx 0.0$


a) unity pf:-

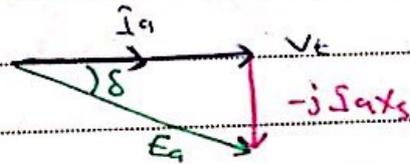

b) lagging pf:-

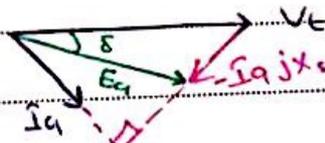

c) lead pf:-

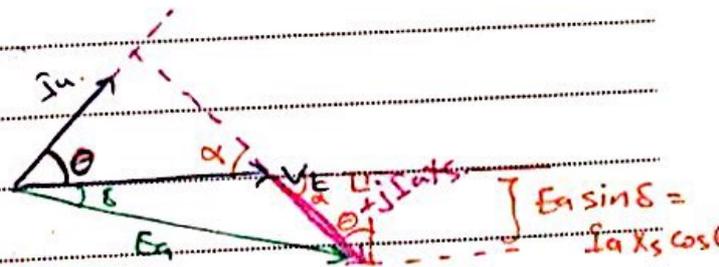

$$E_a \sin \delta = I_a X_s \cos \theta$$

$$\left(\frac{E_a \sin \delta}{X_s} = I_a \cos \theta \right) * 3V_t$$

$$3V_t I_a \cos\theta = \frac{3V_t E_a \sin\delta}{X_s}$$

$$P_{3\phi in} = P_{dev.}$$

$$P_{in} = \sqrt{3} V_t I_a \cos\theta$$



$$= 3 V_t I_a \cos\theta$$

$$P_d = P_{conv}$$

$$= 3 E_a I_a \cos\theta$$

$$P_{out} = T_m \omega_s$$


Steady state
stability
limit.

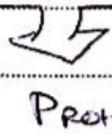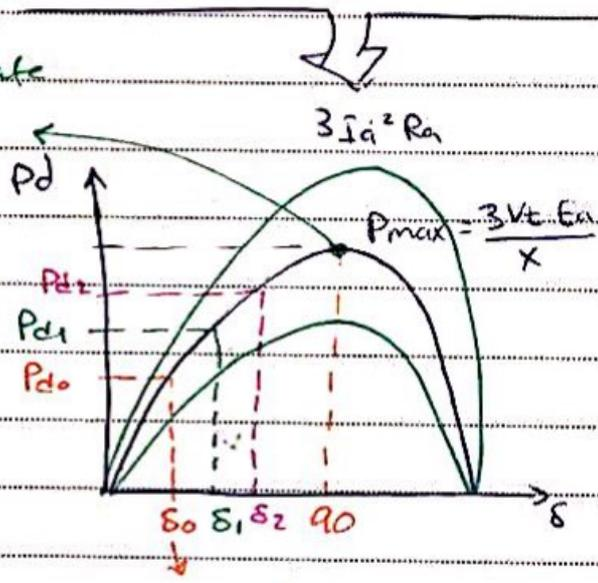

$$P_d = \frac{3V_t E_a \sin\delta}{X}$$



$$P_{max} |_{\delta=90^\circ} = \frac{3|V_t||E_a|}{X_s}$$

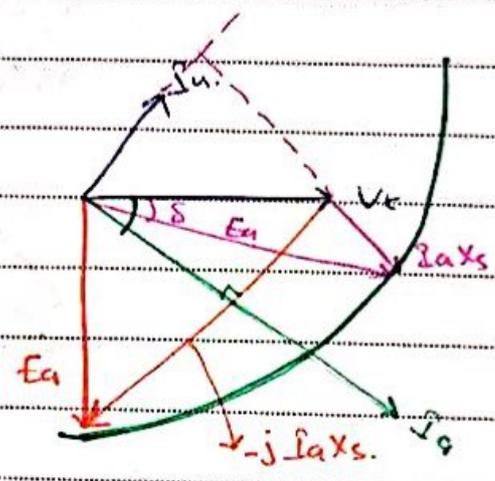$E_a \downarrow \rightarrow \delta \uparrow$



\uparrow load $\uparrow \delta \rightarrow$ machine \Rightarrow more power

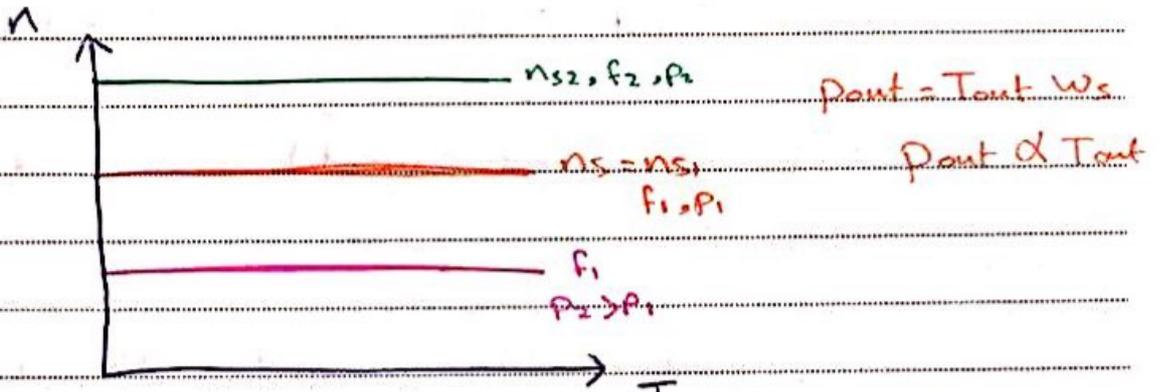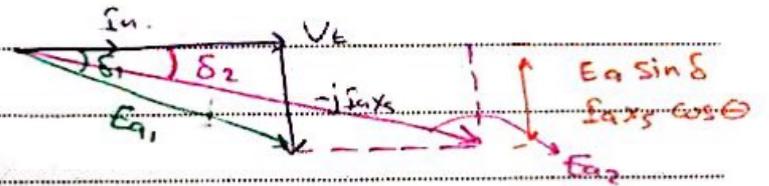$E_1 \uparrow \rightarrow \delta \downarrow$



- السعة بفض ثابتة لا تتغير مع nL ← FL
 - كثافة ال فرق بتزويد ال n

EX 18

208 V, 45 KVA, 0.8 PF leading

Δ -connected, 60 HZ S.M

$X_s = 1.5 \Omega$, $R_a = 0.0$

$P_{\text{Fandw}} = 2.5 \text{ KW}$, $P_{\text{core}} = 1.0 \text{ KW}$


$P_{\text{out}} = 15 \text{ hp}$ (mechanical output power)

PF = 0.8 leading.

Find: a) \vec{i}_A (phase current), \vec{i}_L (line current) and \vec{E}_a ?!

b) $P_{\text{out}} = 30 \text{ hp}$ sketch the behavior of the phaser diagram ?!

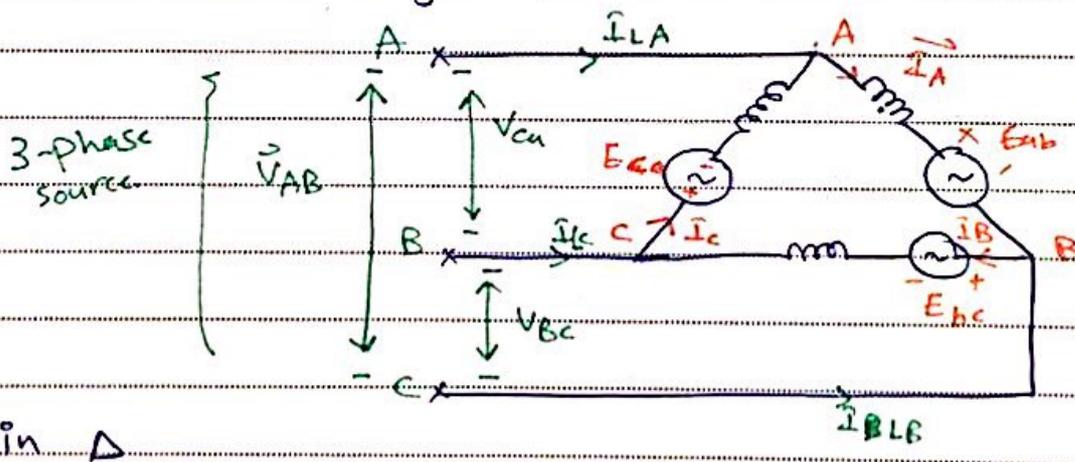c) Find \vec{i}_A , \vec{i}_L and \vec{E}_a after the load change ?!



Phase voltage = line voltage

Phase current = $\frac{\text{line current}}{\sqrt{3}}$

Subject

$$P_{out} = 15 \text{ hp}$$

$$= T_{out} \cdot \omega_s$$

$$= T_{sh} \cdot \omega_s$$

$$\vec{V}_t = 208 \angle 0^\circ$$

$$I_A \cdot jX_s$$

$$P_d$$

$$P_{Rot}$$

$$E_{cb}$$

$$P_{out} = 15 \text{ hp}$$

$$= 30 \text{ hp}$$

$$P_{in} = 3 V_{ph} I_{ph} \cos \theta$$
$$= \sqrt{3} V_L I_L \cos \theta$$
$$= 13.6 \text{ kW}$$

$$P_d = T_d \cdot \omega_s$$
$$= 3 E_{cb} I_A \cos \theta$$
$$= 13.69 \text{ kW}$$

$$P_{out} = T_{out} \cdot \omega_s$$
$$= 11.19 \text{ kW}$$

$$P_{air} = 0.0$$

$$P_{Rot} < P_{F+W}$$
$$= 2.5 \text{ kW}$$

$$1 \text{ hp} = 746 \text{ W} \approx 0.746 \text{ kW}$$

$$P_{out} = 15 \times 746 = 11190 \text{ W} \quad (11.19 \text{ kW})$$

$$P_{in} = P_{out} + \sum \text{losses}$$
$$= (11.19) \text{ kW} + (1.5 + 1.0 + 0.0) \text{ kW}$$
$$= 13.69 \text{ kW}$$

$$P_{in} = 3 |V_t| |I_A| \cos \theta$$
$$= \sqrt{3} V_L I_L \cos \theta$$
$$= \sqrt{3} \times 208 \times |I_L| \times 0.8$$

$$|I_L| = 47.5 \text{ A}$$

$$P_{in} = 3 \times V_L |I_A| \cos \theta$$


$$13.69 \times 10^3 = 3 \times 208 \times |I_A| \times 0.8$$

$$|I_A| = 27.4 \text{ A}$$

$$\vec{I}_A = 27.4 \angle +36.9^\circ \text{ A}$$

$$V_t = \vec{E}_{ab} + j \vec{I}_a X_s$$
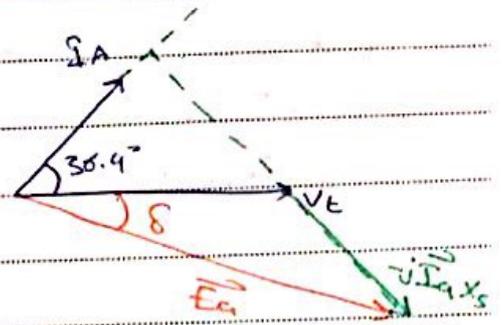
$$\vec{E}_{ab} = \vec{V}_t - j \vec{I}_a X_s$$





Since $\vec{E}_{ab} \cos \theta > V_t$
 the S.M is over excited
 SM supply VAR.


$$\vec{E}_{ab} = 208 \angle 0 - (\underbrace{27.4 \angle +38.9^\circ}_{I_a}) (\underbrace{2.5 \angle +90^\circ}_{X_s})$$

$$\vec{E}_{ab} = 255 \angle -12.4^\circ$$

$$|E_a| = 255$$

$$\delta = 12.4^\circ$$

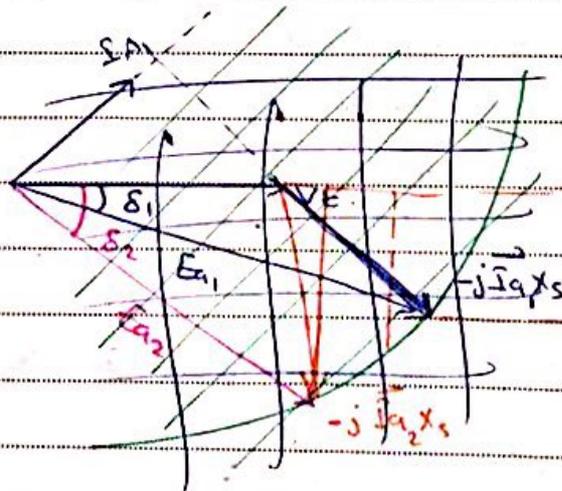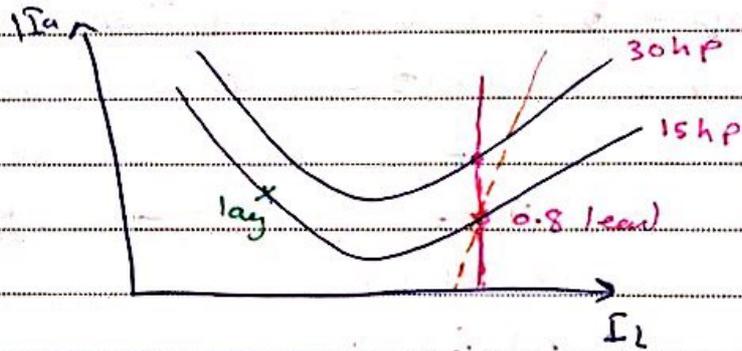

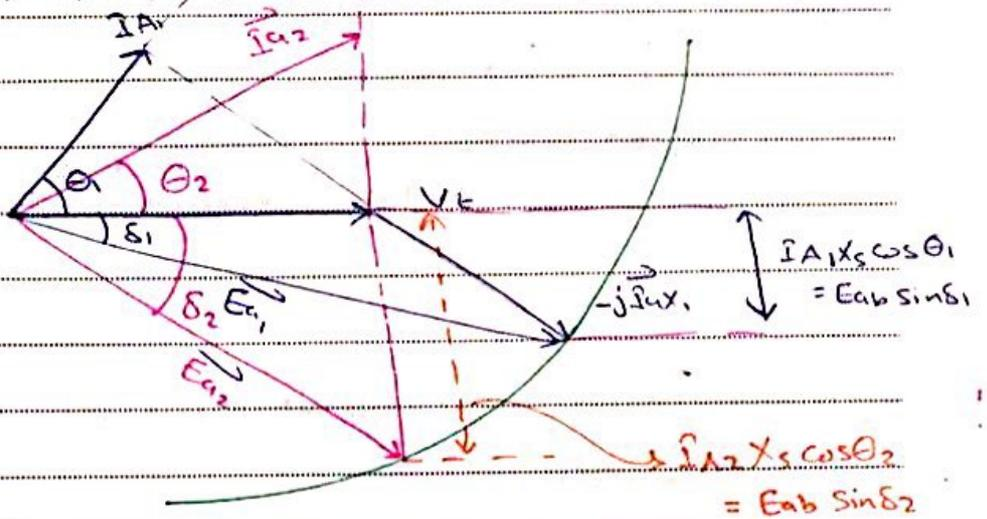

Port 2 = 30hp

= 30 x 746 = 22.38 kW

$P_d = 22.38 + 2.5 \text{ kW} = 24.88 \text{ kW}$

$R_a = 0.0$

$= \sqrt{3} V_L I_{L2} \cos \theta_2 = 3 V_t I_{A2} \cos \theta_2$

$= \sqrt{3} \times 208 \times I_{L2} \times \cos \theta_2$

$P_d = \frac{3 V_t E_a \sin \delta}{X_s}$

$P_{d2} = 22.38 \text{ kW} = \frac{3 \times 208 \times 255 \sin \delta_2}{2.5}$

$\delta_2 = \sin^{-1} \left[\frac{22.38 \times 10^3 \times 2.5}{3 \times 208 \times 255} \right]$

$\delta_2 = 23^\circ$


$I_{A2} = \frac{V_t - \vec{E}_{ab}}{jX_s} = \frac{208 \angle 0^\circ - 255 \angle -23^\circ}{2.5 \angle +90^\circ}$

$I_{A2} = 41.2 \angle 15^\circ \text{ A}$


$$|\vec{I}| = \sqrt{3} * 41.2 = 71.4 \text{ A}$$

$$\text{PF} = \cos \theta_2 = \cos 15^\circ$$

$$\text{PF} = 0.966 \text{ leading}$$

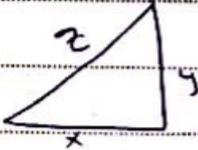

$$|z| = \sqrt{x^2 + y^2}$$

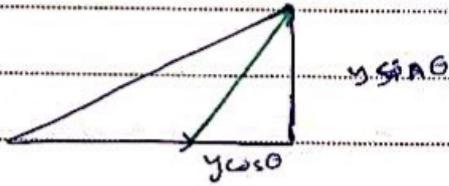


$$\begin{aligned} |z| &= \sqrt{(x + y \cos \theta)^2 + (y \sin \theta)^2} \\ &= \sqrt{x^2 + \underbrace{y^2 \cos^2 \theta + 2xy \cos \theta + y^2 \sin^2 \theta}_{y^2 + 1}} \end{aligned}$$

$$|z|^2 = x^2 + y^2 + 2xy \cos \theta$$


if $\theta = \text{zero}$
will back to
 $z^2 = x^2 + y^2$

EX 3

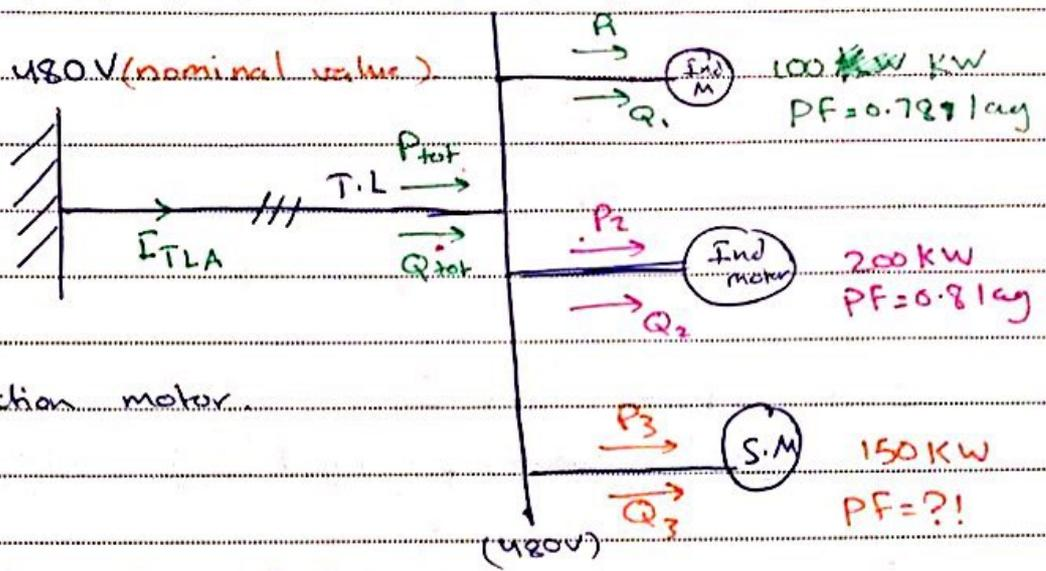

Ind M = Induction motor

a) S.M, PF = 0.85 PF

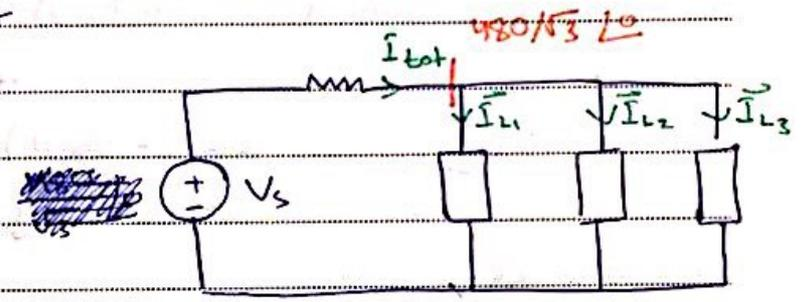

$$\Rightarrow \vec{I}_{L1} = \frac{P_3 \phi / PF}{\sqrt{3} V_L}$$

$$= \frac{100 \times 10^3 / 0.78}{\sqrt{3} \times 480} = 154.2 A$$

$$\theta_1 = \cos^{-1}(0.78) = 38.7^\circ$$


$$\Rightarrow \vec{I}_{L2} = \frac{200 \times 10^3 / 0.8}{\sqrt{3} \times 480} = 300.7 A$$

$$\theta_2 = \cos^{-1}(0.8) = 36.9^\circ$$

$$\Rightarrow \vec{I}_{L3} = \frac{150 \times 10^3 / 0.85}{\sqrt{3} \times 480} = 212.3^\circ$$

$$\theta_3 = \cos^{-1}(0.85) = 31.8^\circ$$

74

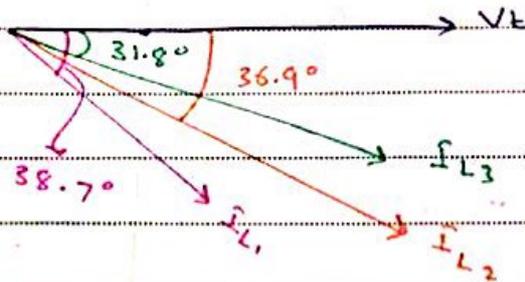



$$\vec{I}_{tot} = \vec{I}_{L1} + \vec{I}_{L2} + \vec{I}_{L3}$$

$$= (154.2 \angle -38.7) + (300.7 \angle -36.9) + (212.3 \angle -31.8)$$

$$\vec{I}_{tot} = 666.4 \angle -35.7^\circ \text{ A}$$

$$PF_{overall} = \cos(-35.7)$$

$$= 0.812 \text{ lag}$$

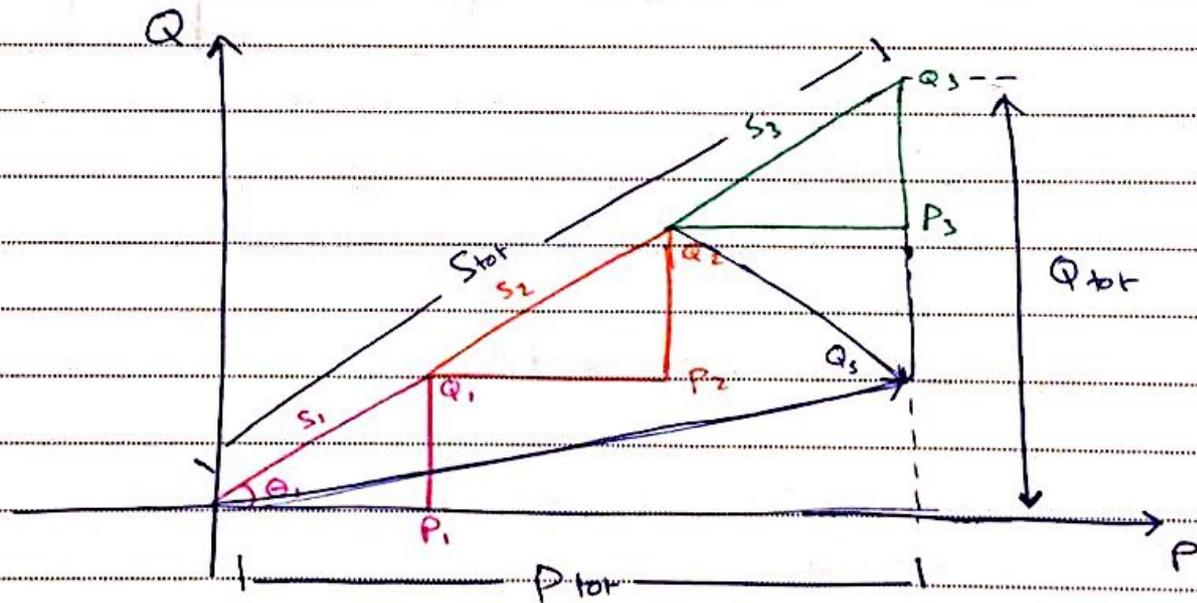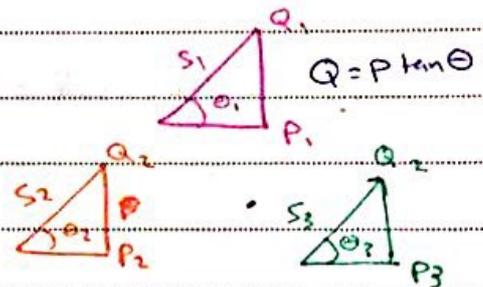

$$P_{tot} = P_1 + P_2 + P_3$$

$$= (100 + 200 + 150) = 450 \text{ kW}$$

$$Q_{tot} = P_1 \tan \theta_1 + P_2 \tan \theta_2 + P_3 \tan \theta_3$$


$$= (80.2 + 150 + 93) \text{ k}$$

$$= 323.2 \text{ KVAR}$$

751

$$\begin{aligned}\vec{S}_{tot} &= \vec{S}_1 + \vec{S}_2 + \vec{S}_3 \\ &= (P_1 + jQ_1) + (P_2 + jQ_2) + (P_3 + jQ_3) \\ &= (P_1 + P_2 + P_3) + j(Q_1 + Q_2 + Q_3) \\ &= P_{tot} + jQ_{tot}\end{aligned}$$

$$\begin{aligned}|S_{tot}| &= \sqrt{(450)^2 + (323.2)^2} \\ &= 554 \text{ KVA.}\end{aligned}$$

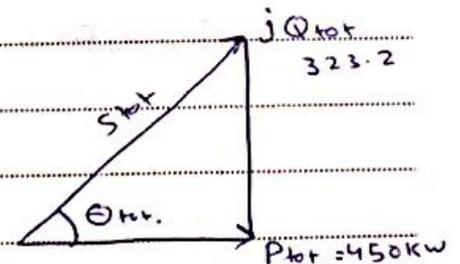

$$554 \times 10^3 = \sqrt{3} \times 450 \times I_{tot}$$

$$I_{tot} = \frac{554 \times 10^3}{\sqrt{3} \times 450} = 666.4$$

$$\theta_{tot} = \tan^{-1}\left(\frac{Q_{tot}}{S_{tot}}\right) = \tan^{-1}\left(\frac{323.2}{450}\right) = 35.9^\circ$$

$$PF_{tot} = \cos(35.9) = 0.810 \text{ lag}$$

$$PF_2 = 0.85 \text{ lead}$$

$$Q_3 = -93 \text{ KVAR}$$


$$\begin{aligned}Q_{tot} &= (-80.2 + 150 - 93) \\ &= 137.2\end{aligned}$$

$$S_{tot} = \sqrt{450^2 + 137.2^2} = 470 \text{ KVA.}$$

$$I_{tot} = \frac{470 \times 10^3}{\sqrt{3} \times 480} = 565 \text{ A}$$

$$PF_{tot} = \cos\left(\tan^{-1}\left(\frac{137.2}{450}\right)\right) = 0.956 \text{ lag}$$

76

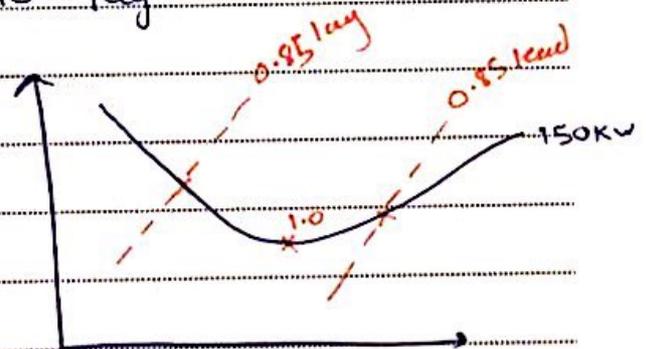

$$P_{\text{transmission}} = 3 \times |I_L| \times R_L$$
$$P_{\text{losses}_1} = 3 \times (666.4)^2 \times R_L$$


$$P_{T \text{ losses}_2} = 3 \times (565)^2 \times R_L$$

$$\frac{P_{TL_2}}{P_{TL_1}} = \frac{(565)^2}{(666.4)^2} = 0.72$$

Q1

3000 hp, 6600 V, 3-ph Y connection S.M
 operates at full load, leading PF = 0.8
 $\eta_{FL} = 74.6\% (0.746) \Rightarrow X_s = 11 \Omega$

- Find a) S_{ph}
 b) \vec{I}_L
 c) $|E_a|$ and S
 d) phasor diagram

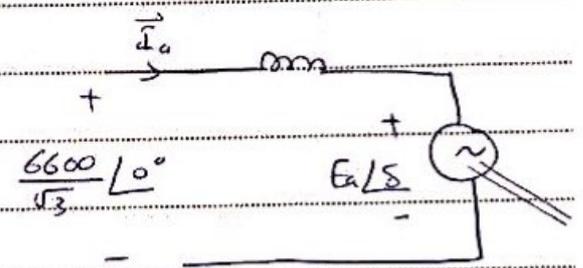


$$P_{in} = \frac{P_{out}}{\eta} = \frac{3000 \times 74.6}{0.746}$$

$$E_g = \vec{V}_t + j \vec{I}_a X_s$$

$$P_{in} = 3000 \text{ kW (3MW)}$$
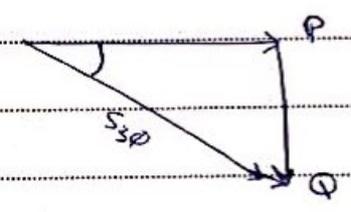
$$S_{3\phi} = \frac{P_m}{PF} = \frac{3M}{0.8} = 3.75 \text{ MVA}$$




$$Q_{3\phi} = P_{in} \times \tan(36.9)$$

$$= 2.25 \text{ MVAR}$$

the motor works as synchronous, supply VAR

$$|I_a| = |\vec{I}_L| = \frac{S_{3\phi}}{\sqrt{3} V_L} = \frac{P_{3\phi}}{\sqrt{3} V_L}$$

$$|I_a| = \frac{3.75 \times 10^6}{\sqrt{3} \times 6600} = 328 \text{ A}$$

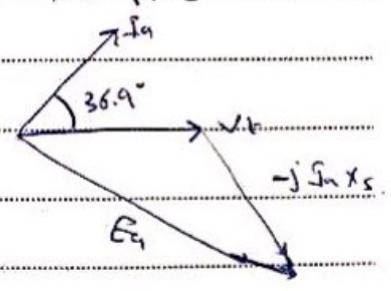

78

$$\begin{aligned}\vec{E}_a &= \vec{V}_t - j\vec{I}_a X_s \\ &= \frac{6600}{\sqrt{3}} - j(328 \angle +36.9^\circ)(11 \angle 90^\circ) \\ &= 6636 \angle -21^\circ\end{aligned}$$


$|E_a| = \sqrt{3} \times 6636 = 11493$ the motor is over excited.

Q2 3-ph, $P=4$, $f=60$ Hz SM, $V_{tLL} = 3980$ V
 Y-connection. $E_{aLL} = 3100$ V, $X_s = 22 \Omega$
 $\delta = 30^\circ$, $I_f = 25$ A
 Find a) I_L b) PF c) T_d

$$\vec{I}_a = \frac{\vec{V}_t - \vec{E}_a}{jX_s}$$

$$= \frac{\frac{3980}{\sqrt{3}} - \frac{3100}{\sqrt{3}} \angle -30^\circ}{j22}$$


$$= 53 \angle -39.8^\circ \text{ A}$$

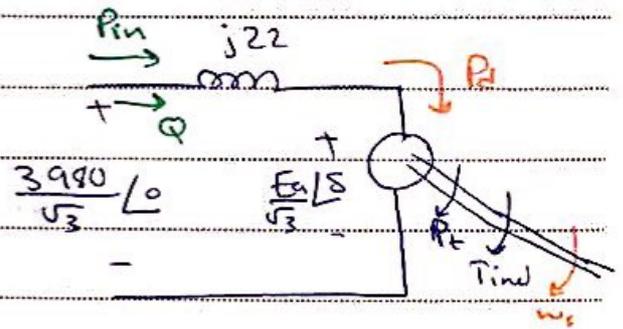

$$\text{PF} = \cos(39.8) = 0.768 \text{ lagging}$$

$$T_d = \frac{P_d}{\omega_s}, \quad \omega_s = \frac{2\pi n_s}{60}$$
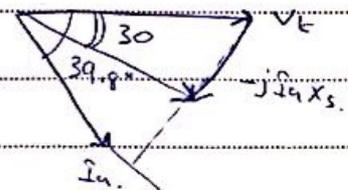
$$n_s = \frac{120f}{P} = \frac{120 \times 60}{4} = 1800 \text{ rpm}$$



$$\omega_s = 188.5 \text{ rad/s}$$

$$P_d = P_{in} \text{ since } R_a \approx 0.0 \Omega$$

$$P_{in} = \sqrt{3} V_L I_L \cos \theta = 3 V_E I_a \cos \theta$$


$$= \sqrt{3} \times 3980 \times 53 \times 0.768$$

$$= 280.7 \text{ kW}$$

$$T_d = \frac{280.7 \times 10^3}{188.5} = 1489 \text{ N.m}$$

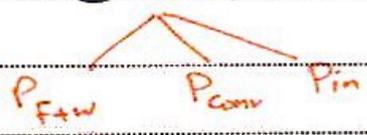Q3

3-ph, 400 V, Y connected $P_{out} = P_{shaf} = 12 \text{ hp}$
 PF = 0.866 lag, $\theta = 30^\circ$ $R_a = 0.75 \Omega / \text{ph}$
 $\Sigma \text{ losses} = 1200 \text{ W}$




Find η ?

$$\eta = \frac{P_{out} \times 100\%}{P_{in} = P_{out} + \Sigma \text{ losses}} = \frac{12 \times 746}{12 \times 746 + 1200} \times 100\%$$

$$\eta = 88.2\%$$

Q4

PF overall = 1.0

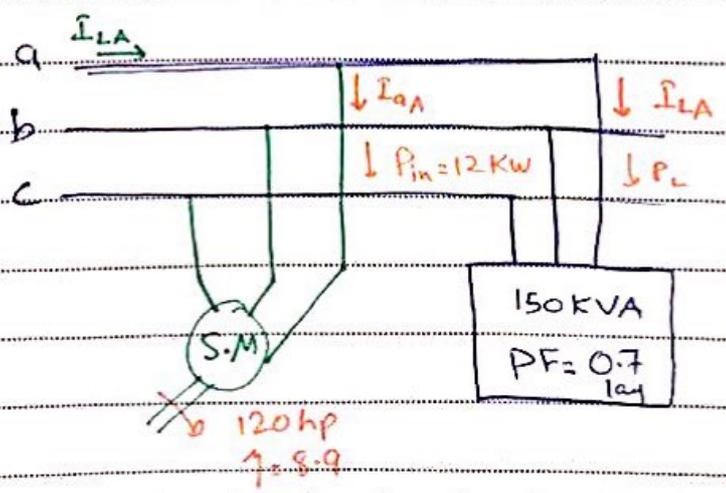

80

$$P_L = S_L \times \cos \theta_L$$


$$= 150 \text{ kVA} \times 0.7$$

$$= 105 \text{ kW}$$

$$Q_L = S_L \sin \theta_L$$

$$= 150 \text{ kVA} \times 0.7$$

$$= 107 \text{ KVAR.}$$

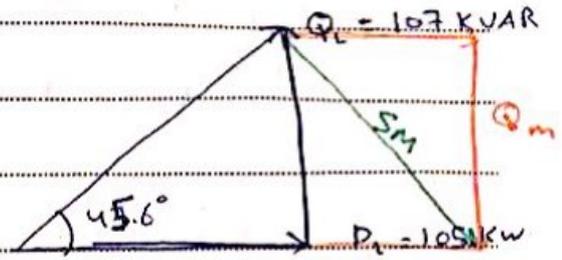

$$\vec{S}_{\text{total}} = \vec{S}_m + \vec{S}_L$$

$$P_m = 12 \text{ kW}$$

$$Q_m = -107 \text{ KVAR.}$$

$$S_m = P_m + jQ_m$$

$$= 12 - j107 \text{ K}$$


$$= 117.7 \angle -83.6^\circ \text{ KVA.}$$

$$P_m = \frac{P_{\text{out}}}{2} = \frac{100 \times 746}{0.9} = 82.9 \text{ kW}$$

$$\vec{S} = (82.9 - j107) \text{ K}$$


$$= 135.4 \angle -52.3^\circ \text{ KVA}$$
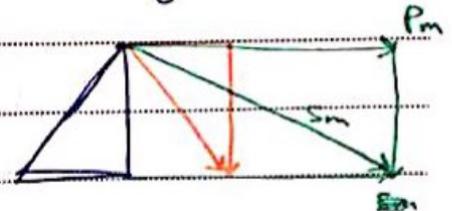
$$\text{PF}_m = \cos(52.3^\circ) = 0.611 \text{ leading}$$



Q5

6600 V, 50 Hz, 3-ph Y-connected S.M

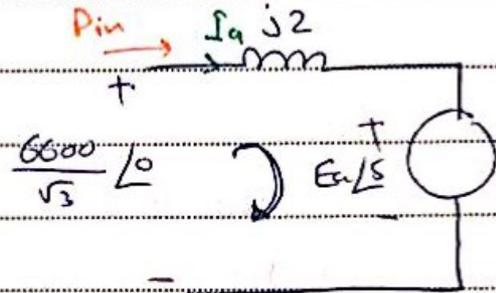 $P_{in} = 400 \text{ kW}$, $\text{PF} = 0.8 \text{ lag}$ ($\theta = 36.9^\circ$) $X_s = 2 \Omega/\text{ph}$ $R_a = 0$ Find a) \vec{I}_a b) E_a/δ c) T_{max} 

$$P_{in} = \sqrt{3} V_L I_L \cos \theta = 3 V_t I_a \cos \theta$$

$$400 \times 10^3 = \sqrt{3} \times 6600 \times I_L \times 0.8 = 3 \times \frac{6600}{\sqrt{3}} \times I_a \times 0.8$$

$$\vec{I}_a = \frac{400 \times 10^3}{0.8 \times \sqrt{3} \times 6600}$$

in Y connection

$$\sqrt{3} \times 6600$$

$$\rightarrow |I_a| = |I_L| = 43.7 \text{ A} \angle -36.9^\circ \text{ A}$$

$$\vec{E}_a = V_t - j I_a X_s$$

$$= \frac{6600}{\sqrt{3}} \angle 0^\circ - 2 \angle 90^\circ \times 43.7 \angle -36.9^\circ$$

~~Result~~

$$E_a = 3760 \angle -1^\circ \text{ V}$$

$$T_{max} = \frac{P_{max}}{\omega_s}$$

$$\omega_s = \frac{2\pi n}{60}, \quad n = \frac{120f}{P} = \frac{120 \times 50}{6} = 1000 \text{ rpm}$$

$$\omega_s = \frac{2\pi \times 1000}{60} = 104.7 \text{ rad/s}$$




82

$$P_{max} \Big|_{\delta=90} = \frac{3Vt E_a}{X_s} = 3 * \frac{6600}{\sqrt{2}} * \frac{3760}{2} = 21.5 \text{ MW}$$

$$T_{max} = \frac{21.5 \text{ MW}}{104.7} = 205.3 \text{ K.N.m.}$$

[2] Find a) $\delta_2 = ?!$

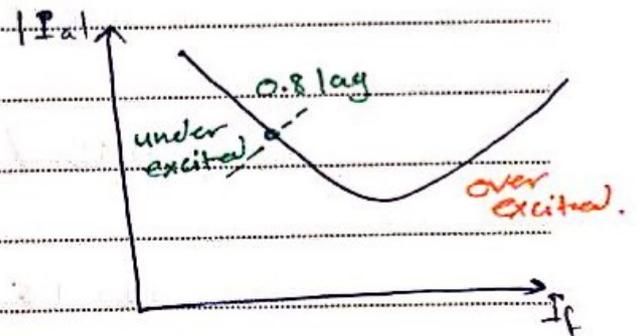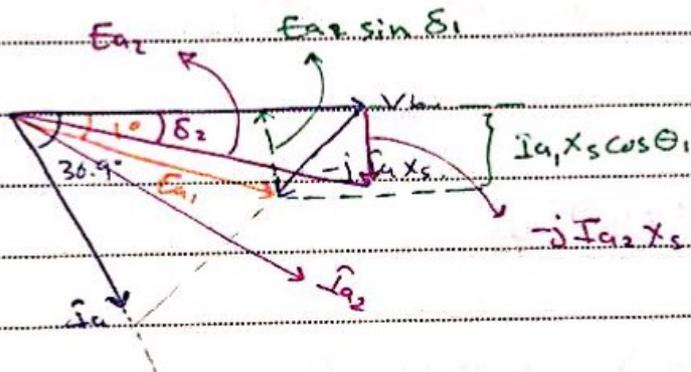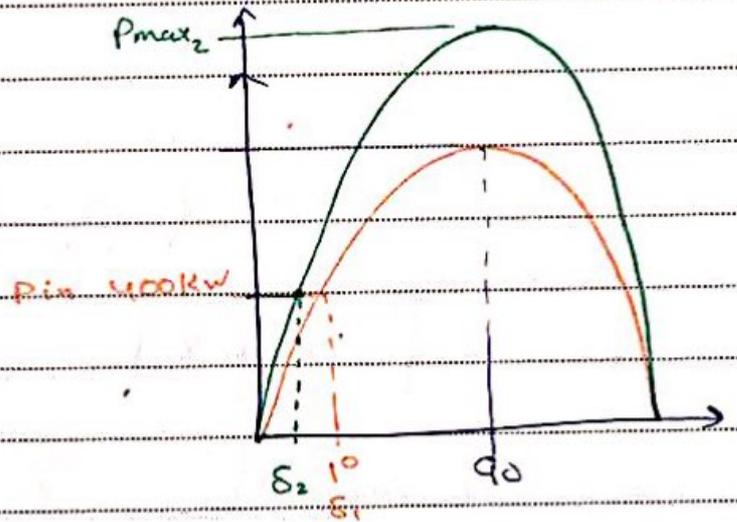- b) I_{a2}
- c) PF_2
- d) $P_d \text{ max}_2$



$$P_d = \frac{3Vt E_{a1} \sin \delta_1}{X_s} = \frac{3Vt E_{a2} \sin \delta_2}{X_s}$$

$$E_{a1} \sin \delta_1 = E_{a2} \sin \delta_2$$

$$3Vt I_{a1} \cos \theta_1 = 3Vt I_{a2} \cos \theta_2$$

$$I_{a1} \cos \theta_1 = I_{a2} \cos \theta_2$$

$$|E_{a2}| = 1.25 * |E_{a1}|$$

$$= 1.25 * 3760$$

$$= 4700 \text{ V}$$

$$\vec{E}_{a2} = \vec{V}_t - j I_{a2} X_s$$

$$4700 \angle \delta_2 = V_t - j I_{a2} \times 2 \angle 90$$

$$E_1 \sin \delta_1 = E_2 \sin \delta_2$$

$$E_1 \sin \delta_1 = E_1 1.25 \sin \delta_2$$

$$\sin \delta_2 = \frac{\sin \delta_1}{1.25}$$

$$\delta_2 = \sin^{-1} \left(\frac{\sin(1^\circ)}{1.25} \right)$$

$$\delta_2 = 0.8^\circ$$

$$\vec{I}_{a2} = \frac{\vec{V}_t - \vec{E}_{a2}}{j X_s} = \frac{\frac{6600}{\sqrt{3}} \angle 0^\circ - 4700 \angle 0.8^\circ}{2 \angle 90}$$


$$I_{a2} = 445 \angle +85.7^\circ \text{ A}$$

$$PF_2 = \cos(85.7^\circ) = 0.075 \text{ leading}$$

$$P_{dmax} = \frac{3 \times \frac{6600}{\sqrt{3}} \times 4700}{2}$$

$$= 1.25 P_{max1}$$

$$= 26.86 \text{ MW}$$

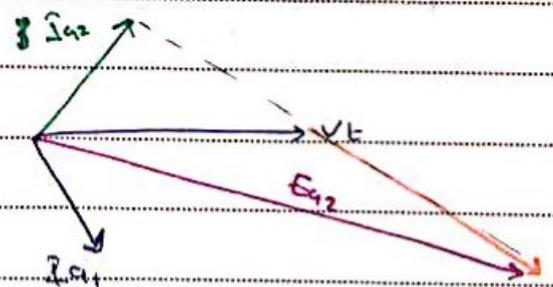


Q6

3.3 KV, 50 Hz, p=2, Y-connection.


$Z_s = 0 + j15$ [$X_s = 15$, $R = 0$]

a) $P_d \text{ max} = \frac{3 V_t E_f}{X_s} \sin \delta - 90$
 $= \frac{3300 \times 3300}{15}$

$P_d = 726 \text{ KW}$


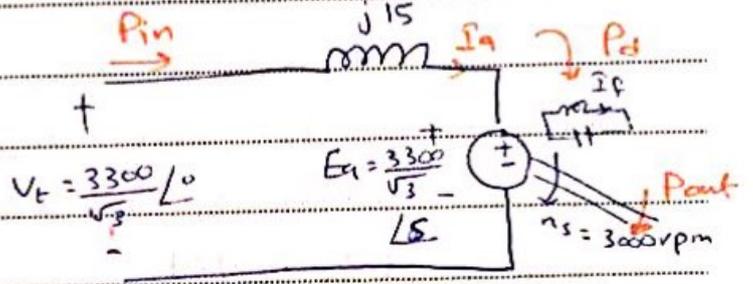


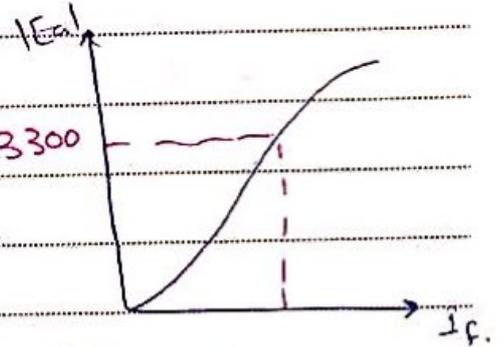$T_{d \text{ max}} = \frac{P_{d \text{ max}}}{\omega_s} = \frac{726 \text{ K}}{314} = 2.31 \text{ KN.m}$




$\omega_s = \frac{2\pi n}{60} = \frac{2\pi \times 120 \times f}{60 \times p}$
 $= \frac{2\pi \times 120 \times 50}{60 \times 2}$

$\omega_s = 314 \text{ rad/s}$

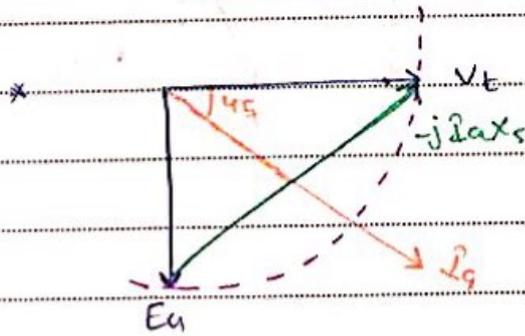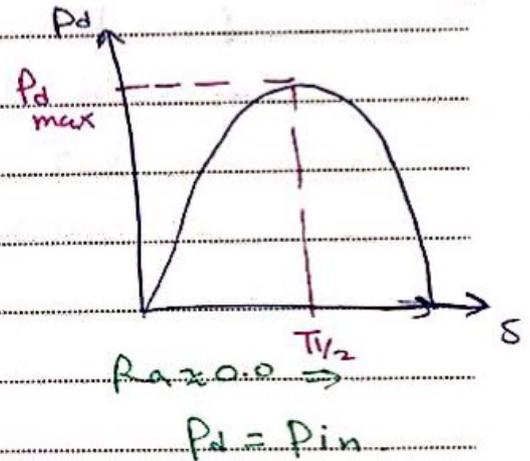


$V_t = E_f - j I_a X_s$

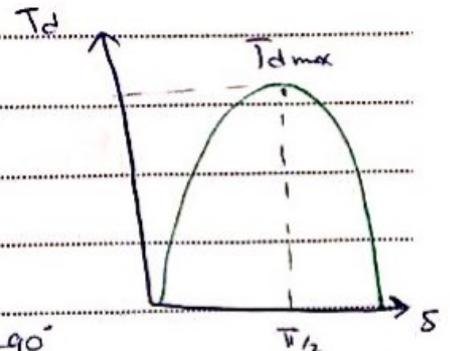$I_a = \frac{V_t - E_f}{j X_s} = \frac{\frac{3300}{\sqrt{3}} \angle 0^\circ - \frac{3300}{\sqrt{3}} \angle -90^\circ}{15 \angle 90^\circ}$



85
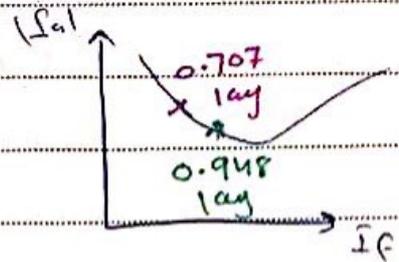
$$\hat{I}_a = 179.6 \angle -45^\circ \text{ A}$$



$$\text{PF} = \cos(45) = 0.707 \text{ lagging}$$

$$Q = \sqrt{3} V_L \hat{I}_L \sin \theta = 3 V_t \hat{I}_a \sin \theta$$

$$= \sqrt{3} \times 3300 \times 179.6 \times 0.707$$

$$Q = 726 \text{ KVAR}$$

$$= \frac{3 V_t}{X_s} [V_t - E_a \cos \delta]$$

$$= \frac{3 V_t^2}{X_s} = \frac{(3300)^2}{15} = 726 \text{ KVAR}$$


$$P_{in} = P_{out} = 3 V_t \hat{I}_a \cos \theta$$

$$E_{a1} \sin \delta_1 = 1.2 E_{a2} \sin \delta_2$$

$$1.2 \sin \delta_2 = 1.0$$

$$\sin \delta_2 = \frac{1}{1.2}$$

$$\delta_2 = 56.4$$

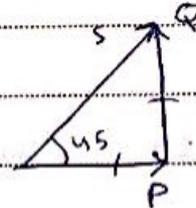

$$\hat{I}_{a2} = \frac{\vec{V}_t - \vec{E}_{a2}}{jX_s}$$


$$= \frac{3300 \angle 0^\circ - 1.2 \times 3300 \angle 56.4^\circ}{15 \angle 90^\circ}$$

$$= \frac{3300 \angle 0^\circ - 1.2 \times 3300 \angle 56.4^\circ}{15 \angle 90^\circ}$$

$$= 13.4 \angle -18.9^\circ \text{ A}$$

$$\hat{I}_{a2} = 13.4 \angle -18.9^\circ \text{ A}$$

$$\text{PF}_2 = \cos(18.9) = 0.948$$

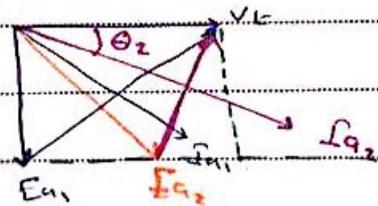

$$Q = 3V_t I_{a2} \sin \theta_2$$

$$= 3 \times \frac{3300}{\sqrt{3}} \times 134 \times \sin(18.9)$$

$$Q = 243 \text{ KVAR.}$$

$$Q_{X_s} = 3 |I_{a1}|^2 X_s = 3 (134)^2 \times 15$$

$$Q_{X_s} = 808 \text{ KVAR}$$

$$E_{a2} \cos \delta_2 = 1.2 \times \frac{3300}{\sqrt{3}} \times \cos(56.4) = 1265 \text{ V}$$

still machine under excited.

$E_a \cos \delta > V_t \rightarrow$ supply VAR.

$E_a \cos \delta < V_t \rightarrow$ absorb VAR.

d)


$$P_{d \max 2} = 1.2 P_{d \max 1}$$

$$P_{d1} = P_{d2} = P_{d \max 1}$$

$$P_{d3} = 1.1 P_{d \max 1}$$

$$= 1.1 \times 726$$

$$P_{d3} = 798.6 \text{ kW}$$

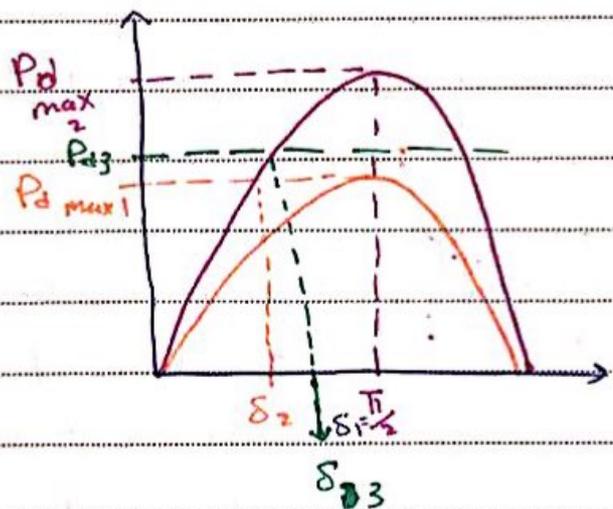

$$P_{d3} = \frac{3V_t E_a}{X_s} \sin \delta_3$$

$$798.6 \text{ K} = \frac{3 \times \frac{3300}{\sqrt{3}} \times 1.2 \times \frac{3300}{\sqrt{3}} \times \sin \delta_3}{15}$$

$$\delta_3 = \sin^{-1} \left(\frac{798.6 \text{ k} \times 15}{(3300)^2 \times 1.2} \right)$$

$$\delta_3 = 66.4^\circ$$

$$\vec{I}_{a3} = \frac{\vec{V}_T - \vec{E}_{a3}}{jX_s} = \frac{\frac{3300}{\sqrt{3}} \angle 0^\circ - \frac{1.2 \times 3300}{\sqrt{3}} \angle -66.4^\circ}{15 \angle 90^\circ}$$

$$\vec{I}_{a3} = 154.5 \angle -25.93^\circ \text{ A}$$

$$\text{PF}_3 = \cos(25.3) = 0.904 \text{ lag}$$

$$\begin{aligned} Q_3 &= 3V_T I_{a3} \sin \delta_3 \\ &= 3 * \left(\frac{3300}{\sqrt{3}} \right) (154.5) * \sin(25.3) \end{aligned}$$

$$Q_3 = 377 \text{ KVAR}$$

Q8


480 kV, 60 Hz, 400 hp, 0.8 PF lead


$p = 8$, Δ -Connection armature

$X_s = 0.6 \Omega/\text{ph}$, $R_a \approx 0.0$, $P_{rot} \approx 0.0 \Rightarrow$

($P_{out} = P_d = P_{in}$), $|E_a| \propto I_f$


a) Find n_s ?!

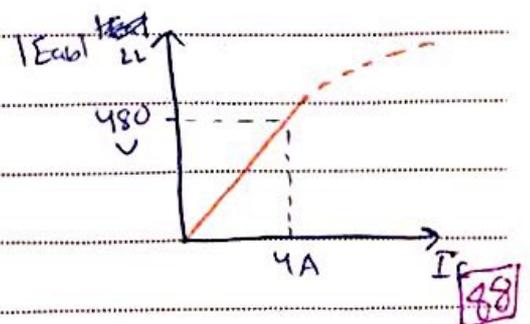



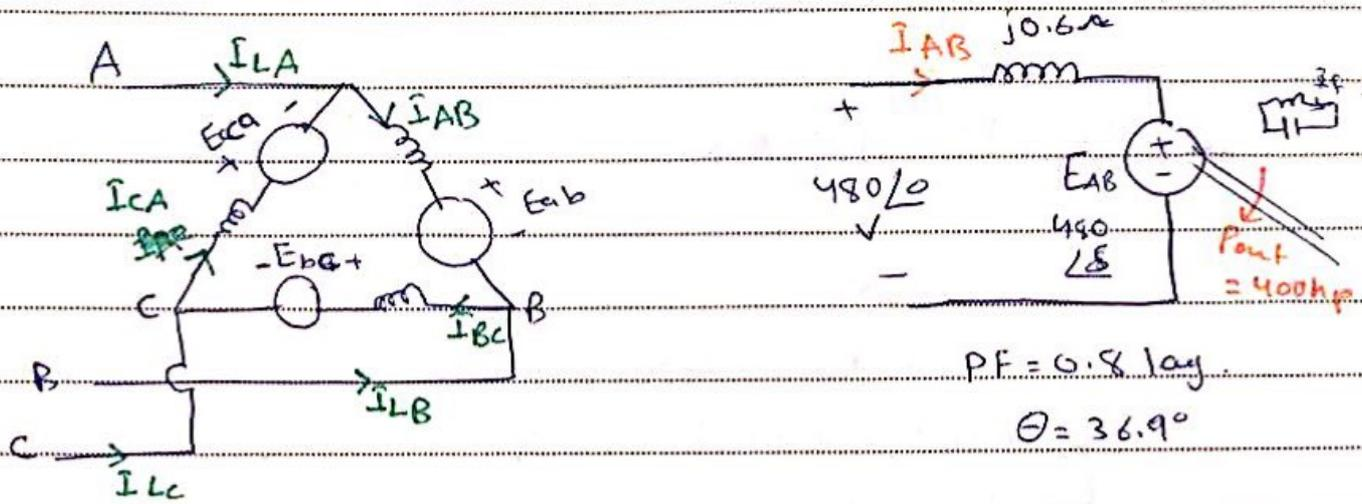


a) $n_s = \frac{120f}{P} = \frac{120 \times 60}{8} = 900 \text{ rpm}$


b) $\angle \delta$ and I_A ?!

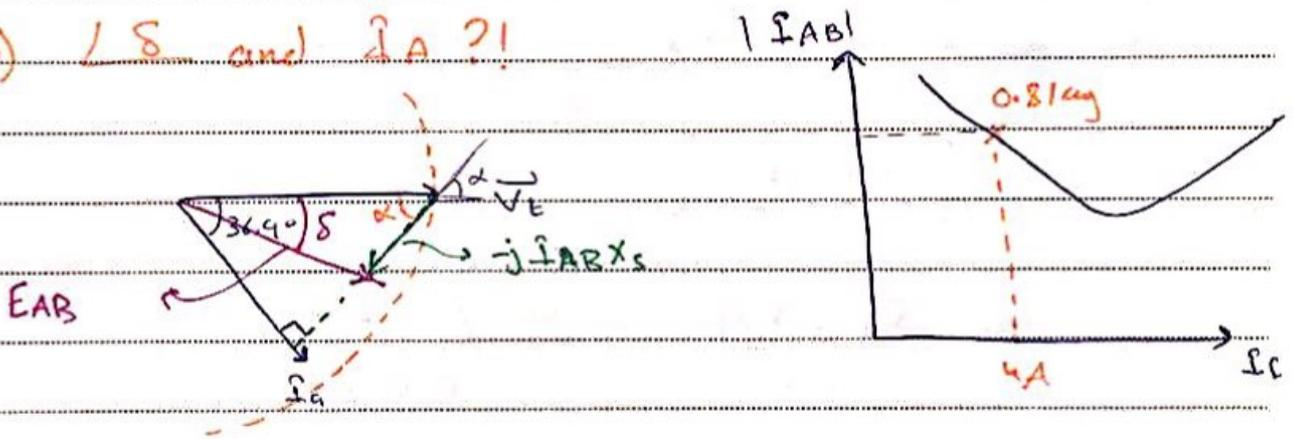

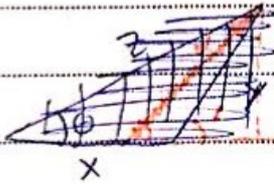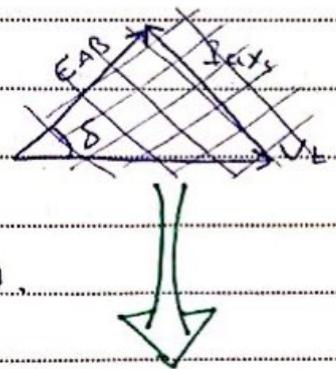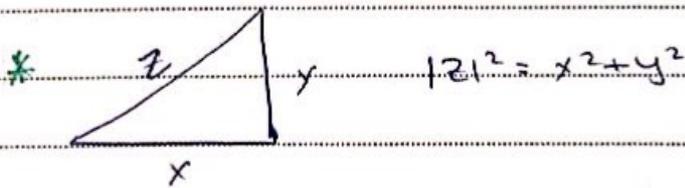$\vec{E}_{AB} = \vec{V}_E - j I_{AB} X_s$




$|z|^2 = x^2 + y^2 + 2xy \cos \theta$

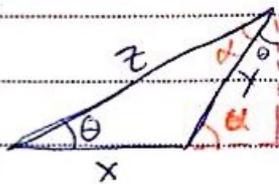

$|E_{AB}|^2 = |V_E|^2 + |I_{AB} X_s|^2 + 2|V_E||I_{AB} X_s| \cos \delta$

$$|E_{AB}|^2 = |V_E|^2 + |\hat{I}_a X_s|^2$$

$$\Rightarrow 2 |V_E| |\hat{I}_a X_s| \cos \alpha$$

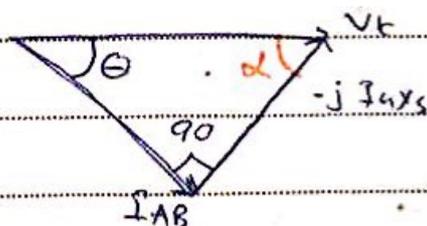

$$(480)^2 = (480)^2 + (\hat{I}_a * 0.6)^2$$

$$\Rightarrow 2 (480) (\hat{I}_a * 0.6)^2 \cos (53.1)$$

$$0.36 \hat{I}_a^2 - 3.45.8 \hat{I}_a = 0.$$

$$\text{Solve for } \hat{I}_a = \frac{345.8}{0.36} \Rightarrow$$

$$\hat{I}_a = 960 \text{ A} \quad \hat{I}_{AB} = 960 / \underline{3}$$

another solution:

$$P_{out} = P_d = P_{in}$$

$$400 * 746 = \frac{3 * 480 * 480}{0.6} \sin \delta$$

$$\delta = 15^\circ$$

$$\vec{I}_{AB} = \frac{\vec{V}_E - \vec{E}_{AB}}{3 X_s} = \frac{480 \angle 0^\circ - 480 \angle -15^\circ}{0.6 \angle 90^\circ}$$

$$\hat{I}_{AB} = 208.8 \angle -7.5^\circ$$

another solution:

$$\alpha = 53.1$$

$$\sin \alpha = \frac{|\hat{I}_{AB}|}{V_E} = 0.8$$

$$\hat{I}_{AB} = 0.8 * 480$$

$$\hat{I}_{AB} = 383 \text{ A}$$

100

Question #1

A 3000-hp, 6600-V, 60-Hz, 3-Phase, Y-connected synchronous motor operates at full-load at a leading PF of 0.8 and efficiency of 74.6%. If the synchronous reactance is 11Ω , calculate:

- the apparent power of the motor per phase,
- the ac line current,
- the value and phase of the induced EMF,
- draw the phasor diagram,
- determine the torque angle δ .

Question #2

A 3-phase, 4-pole, 60-Hz, Y-connected synchronous motor is connected to a 3980 V, 3-phase transmission line. The motor generates an induced EMF of 3100 V when the field current is 25 A. The synchronous reactance is $X_s = 22 \Omega$ and the torque angle $\delta = 30^\circ$. Calculate:

- the transmission line current,
- the power factor of the motor,
- the developed torque.

Question #3

A 3-phase, 400-V, Y-connected synchronous motor delivers 12 hp at the shaft and operates at 0.866 lagging PF. The total core, friction, and field copper losses are 1200 W. If the armature resistance is $R_a = 0.75 \Omega$ per phase, determine the efficiency of the motor.

Question #4

An overexcited synchronous motor is connected across a 150-kVA inductive load of 0.7 lagging PF. The motor takes 12 kW while running on no load.

- Calculate the kVA rating of the motor if it is desired to bring the overall PF of the motor-inductive load combination to unity.
- What would be the kVA rating of the motor if the synchronous motor were used to supply a 100-hp load at an efficiency of 90%.

Question #5

A 6600-V, 50-Hz, 6-pole, 3-phase, Y-connected synchronous motor takes 400 kW at 0.8 PF lagging. The synchronous reactance $X_s = 2 \Omega/\text{phase}$ and a negligible armature resistance.

I. Determine:

- The armature current,
- The induced EMF and torque angle δ ,
- The maximum torque the motor can develop T_{\max} .

II. If the induced voltage is increased by 25% and the power input to the motor remains the same, i.e. 400 kW, find:

- The new power angle δ ,
- The new value of armature current,
- The new power factor,
- The new maximum developed power,

Question #6

A 3.3 kV, 50-Hz, 2-pole, star-connected synchronous motor has $Z_s = 0 + j15 \Omega$. The motor is connected to 3.3 kV, 3-phase supply and its excitation is set so that the internal generated voltage is 3.3 kV.

- What is the maximum power, P_{\max} , and maximum torque, T_{\max} , the motor can develop?
- What are the motor current, I_a , PF, and reactive power, Q , at the load condition of part (a)?
- If the torque remains constant at this value and the excitation is increased by 20%, calculate the new torque angle, δ , armature current, I_a , PF, and reactive power, Q .
- At the new excitation level as in part (c) the loads is increased by 10%, calculate the new power angle, δ , motor current, I_a , PF and reactive power, Q .

Illustrate your analysis by showing the phasor diagrams and power angle curves at the various load conditions mentioned above.

Question #7

A 208-V, 45-kVA, 0.8-PF-leading, Δ -connected, 60-Hz synchronous machine has a synchronous reactance of 2.5Ω and a negligible armature resistance. Its friction and windage losses are 1.5 kW, and its core losses are 1.0 kW. Initially, the shaft is supplying a 15-hp load, and the motor's power factor is 0.80 leading.

- Sketch the phasor diagram of this motor, and find the values of I_a , I_L , and E_a .
- Assume that the shaft load is now increased to 30 hp. Sketch the behavior of the phasor diagram in response to this change.
- Find I_a , I_L , and E_a after the load change. What is the new motor power factor?

Question #8

A 480-V, 60 Hz, 400-hp 0.8-PF-leading eight-pole Δ -connected synchronous motor has a synchronous reactance of 0.6Ω and negligible armature resistance. Ignore its friction, windage, and core losses for the purposes of this problem. Assume that $|E_A|$ is directly proportional to the field current I_F (in other words, assume that the motor operates in the linear part of the magnetization curve), and that $|E_A| = 480$ V when $I_F = 4$ A.

- What is the speed of this motor?
- If this motor is initially supplying 400 hp at 0.8 PF lagging, what are the magnitudes and angles of E_A and I_A ?
- How much torque is this motor producing? What is the torque angle δ ? How near is this value to the maximum possible induced torque of the motor for this field current setting?
- If $|E_A|$ is increased by 30 percent, what is the new magnitude of the armature current? What is the motor's new power factor?
- Calculate and plot the motor's V-curve for this load condition.

$$s = \frac{n_s - n_m}{n_s} \quad (s = \text{step})$$

$n_s \Rightarrow$ Stator speed

$n_m \Rightarrow$ motor speed

rotor speed (slip)

$$n_m \downarrow \rightarrow s \uparrow$$


$$n_s = \frac{120f}{P}$$

stator speed, rotor speed

Current \rightarrow magnetic field \rightarrow magnetic field \rightarrow source

induction.

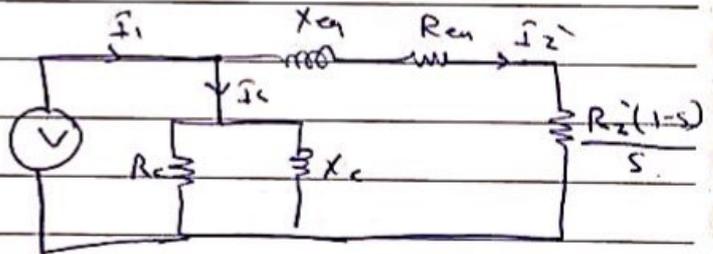Slide 35 * Consider the approximate equivalent ckt.



$$|I_2'| = \frac{V_1}{R_{eq} + \frac{R_2'(1-s)}{s}}$$

$$R_{eq} = R_1 + R_2'$$

$$X_{eq} = X_1 + X_2'$$

$$= \frac{V_1}{\sqrt{(R_1 + \frac{R_2'}{s})^2 + X_2'^2}}$$


$$P_{eq} = 3 I_2'^2 R_{eq}$$

$$P_d = 3 I_2'^2 \frac{R_2'(1-s)}{s}$$

$$P_d = \frac{3 |V_1|^2 \left(\frac{1-s}{s} R_2' \right)}{\left(R_1 + \frac{R_2'}{s} \right)^2 + X_{eq}^2}$$

92

IEEE model :-

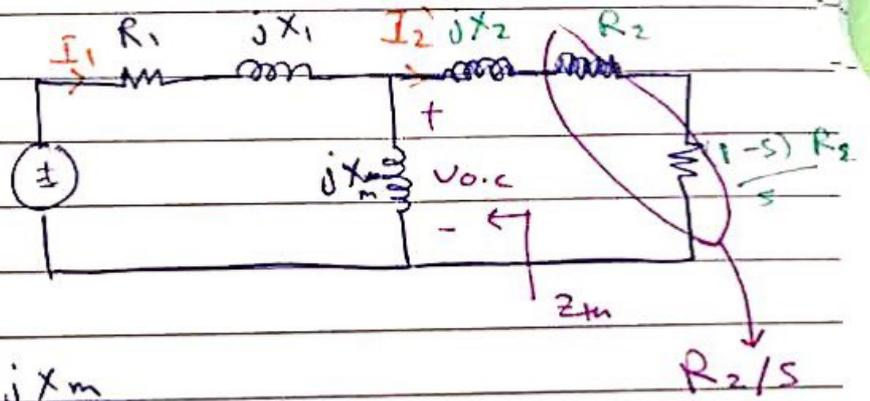


$$\vec{V}_{th} = \vec{V}_{o.c.} = \vec{V}_1 * \frac{jX_m}{R_1 + j(X_1 + X_m)}$$

$$Z_{th} = (jX_m) // (R_1 + jX_1)$$


$$= jX_m$$

$$R_1 + j(X_1 + X_m)$$

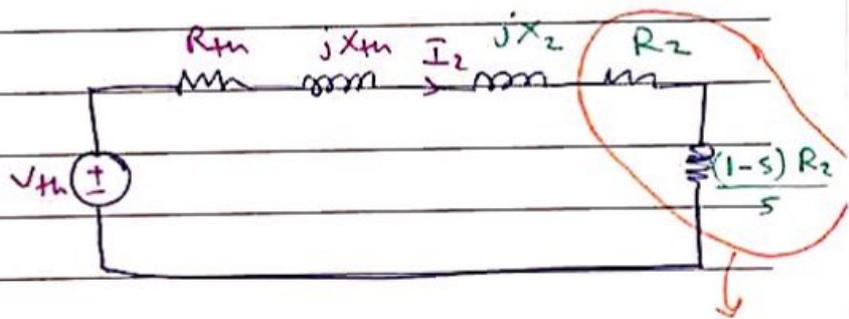

$$I_2 = \frac{|V_{th}|}{\sqrt{(R_{th} + \frac{R_2}{s})^2 + (X_{th} + X_2)^2}}$$

slide: 2) No load test ($s=0$)

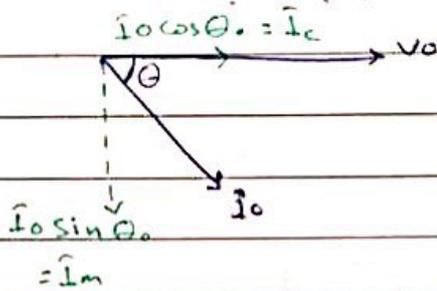

$$P_0 = V_0 I_0 \cos \theta_0$$



$$\cos \theta_0 = \frac{P_0}{V_0 I_0}$$

Example:

* Determine R_1

$$R_{DC} = \frac{1}{2} \frac{V_{DC}}{I_{DC}}$$

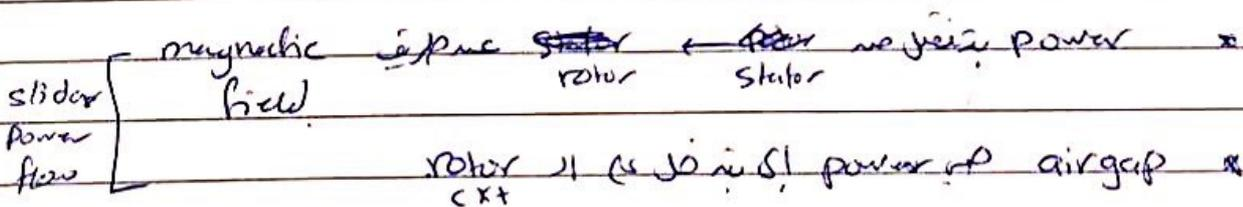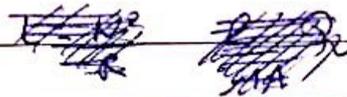$X_m \Rightarrow$ $\text{current} \rightarrow$ magnetic field



rotor \rightarrow (air gap) power of air gap

* power on $R_2' (1-s)$ \rightarrow $P_{develop}$


$$P_g = 3 I_2'^2 R_s$$

$$= \frac{P_{ag}}{s}$$


\uparrow load \downarrow speed

$$P_{ag} = P_g \cdot s$$

$$P_d = (1-s) P_g$$

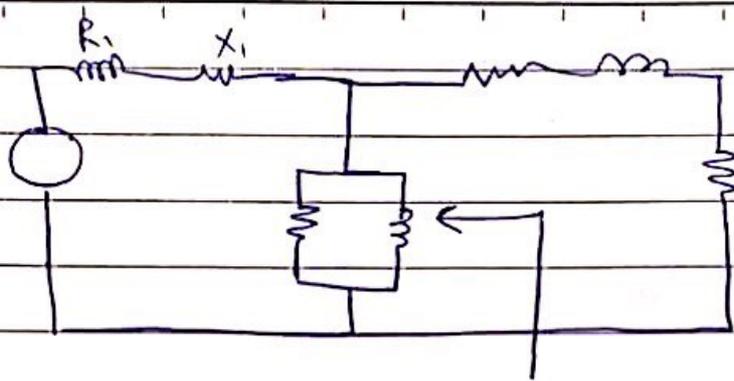

$$Z_{th} = R_{12} + jX_{th}$$

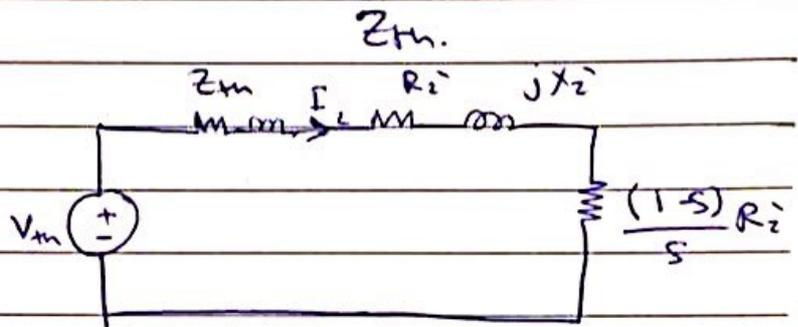

$$|Z_{th}| = \sqrt{\left(R_{12} + \frac{R_2'}{s}\right)^2 + (X_{12} + X_2')^2}$$

$$\sqrt{\left(R_{12} + \frac{R_2'}{s}\right)^2 + (X_{12} + X_2')^2}$$

$$s = \frac{n_s - n_m}{n_s}$$

$$s n_s = n_s - n_m$$

$$n_m = -s n_s + n_s$$


$$= (1-s) n_s$$

$$\omega_m = (1-s) \omega_s$$


$$T_d = \frac{3 |V|^2}{\omega_s} \frac{R_2' / s}{\left(\frac{R_1 + R_2'}{s}\right)^2 + (R_1 + X_1)^2}$$

Fixed

broken machine
machine

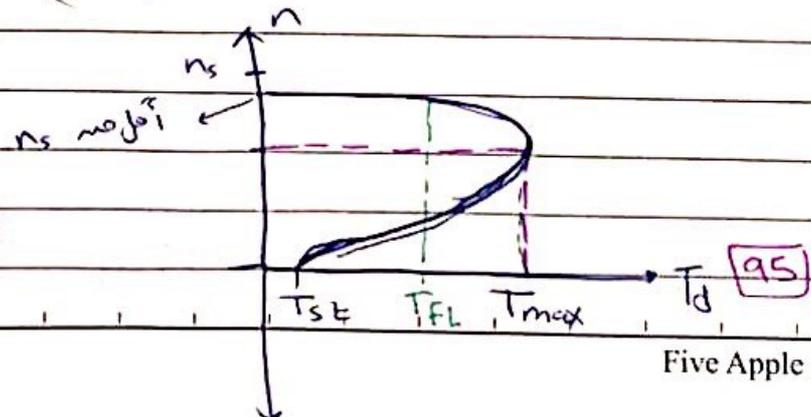

st = stand, still or started.

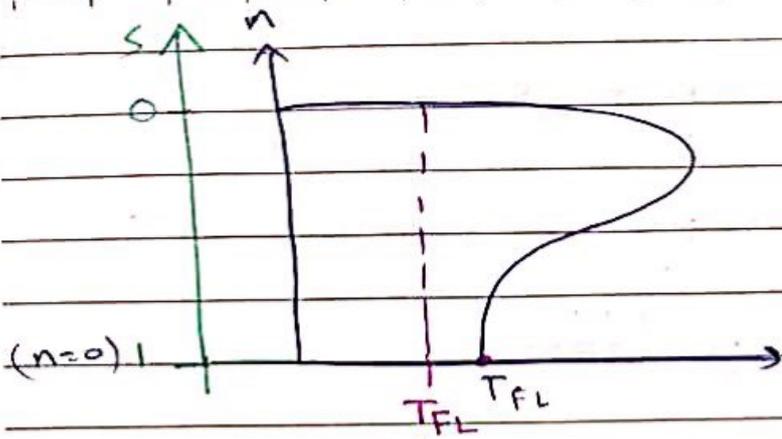

$T_f > T_{st} \rightarrow$ machine will run

$$T_{st} (s=1) = \frac{3 |V|^2}{\omega_s} \times \frac{R_2'}{(R_1 + R_2')^2 + X_{eq}^2}$$

$$T_{dFL} (s = s_{FL}) = \frac{3 |V|^2}{\omega_s} \times \frac{R_2' / s_{FL}}{(R_1 + \frac{R_2'}{s_{FL}})^2 + X_{eq}^2}$$


(parameter is given T)

$$n_s = \frac{120f}{P}$$

$$n_s = \frac{120 \times 50}{P}$$

\uparrow poles $\rightarrow \uparrow$ Torque.

$\uparrow f \rightarrow \downarrow T$

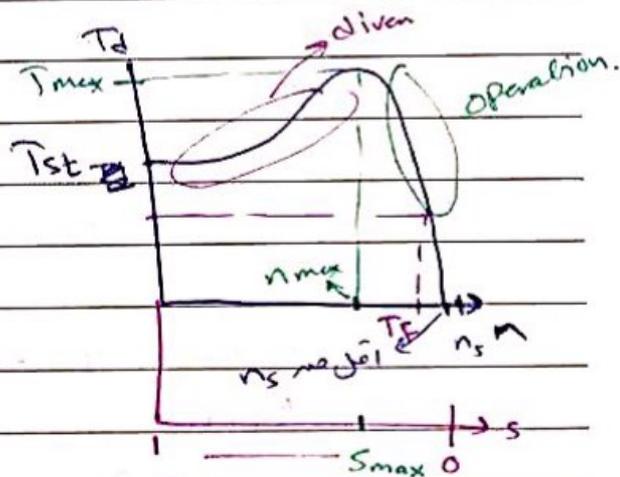


$$s_{max} = \frac{n_s - n}{n_s}$$

$$P_d = (1-s) P_g$$

$P_g \text{ max} \rightarrow P_d \text{ max}$

$$\text{at } T_{max} \rightarrow \frac{R_2'}{s_{max}} = \sqrt{R_1^2 + X_{eq}^2}$$

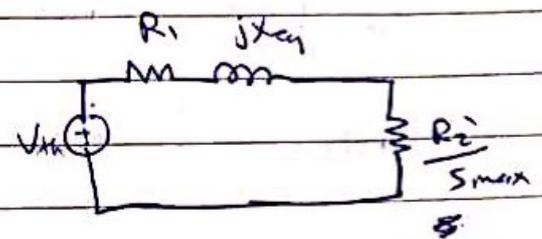
$$s_{max} = \frac{R_2'}{\sqrt{R_1^2 + X_{eq}^2}}$$




$$T_d (S_{max}) = \frac{3|V|^2}{2\omega_s} \frac{1}{R_1 + \sqrt{R_1^2 + X_{eq}^2}}$$

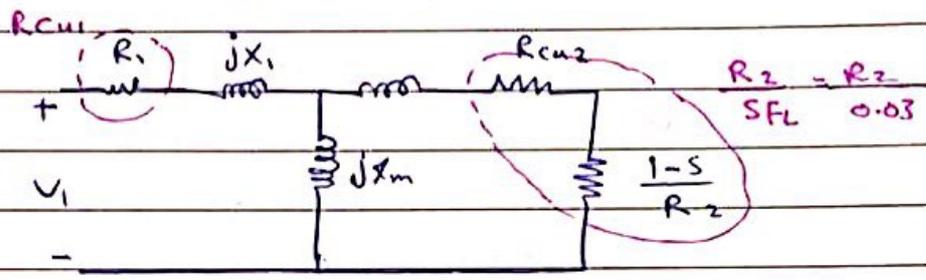Q1

100 hp, 60 Hz, 3ph IM, SFL = 0.03 (3%)
 find η_{FL} given $P_{Fandw} = 900W$
 $P_{core} = 4200W$, $P_{cu} = 2700W$



a) Full load condition $s \Delta$

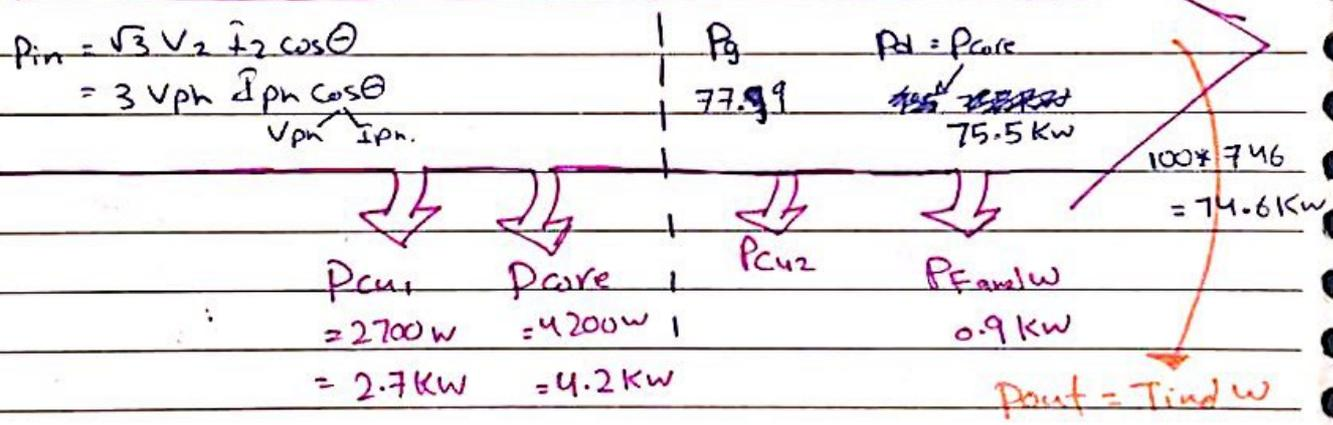

$$\eta = \frac{P_{out FL}}{P_{in FL}} \times 100\% = \frac{P_{out}}{P_{out} + \sum \text{losses}} \times 100\%$$

$$= \frac{74.6 \times 100}{84.8} = \boxed{88\%}$$

$$P_{in} = P_{out} + P_{rot} = 74.6 + 0.9 = 75.5 \text{ kW}$$

$$P_{dFL} = (1-s)_{FL} = P_{gFL} \Rightarrow P_{gFL} = \frac{P_{dFL}}{1-s_{FL}} = \frac{75.5 \text{ kW}}{0.97}$$

$$P_{gFL} = 77.9 \text{ kW} = \frac{P_{cu2}}{SFL} \quad \boxed{97}$$

$$P_{Cu2} = S_{FL} \times P_{gFL} = 0.03 \times 77.9 \text{ K}$$

$$P_{inFL} = P_{gFL} + P_{CuFL} + P_{core}$$

$$= (77.9 + 0.9 + 4.2) \text{ K}$$

$$= 84.8 \text{ KW}$$

Q2

3-ph, 4800, 60 Hz, ϕ 12, 2M y-connection

$$R_1 = 1 \Omega, R_2 = 0.5 \Omega, X_{eq} = 10 \Omega$$


$$X_s = 100 \Omega, R_c = 800 \Omega$$

Find a) S_{max} ?

b) I_2' max ?

c) W max ?

d) T max ?

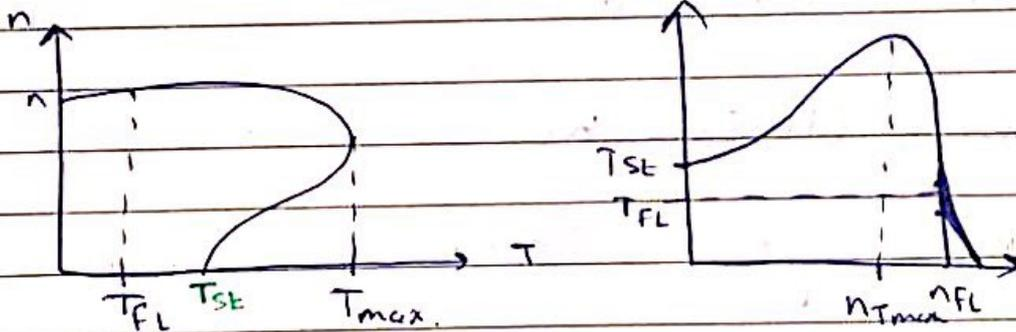



a) S_{max} ?!

$$R_2' = |R_1 + jX_{eq}|$$

$$S_{max} = |R_2 + jX_{eq}|$$

$$S_{max} = \frac{R_2'}{\sqrt{R_1^2 + X_{eq}^2}} = \frac{0.5}{\sqrt{1^2 + 10^2}} = \frac{0.5}{\sqrt{1+100}}$$

98

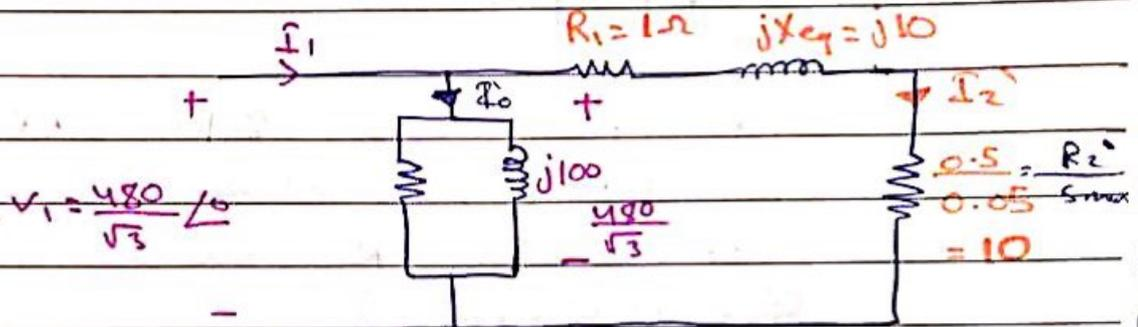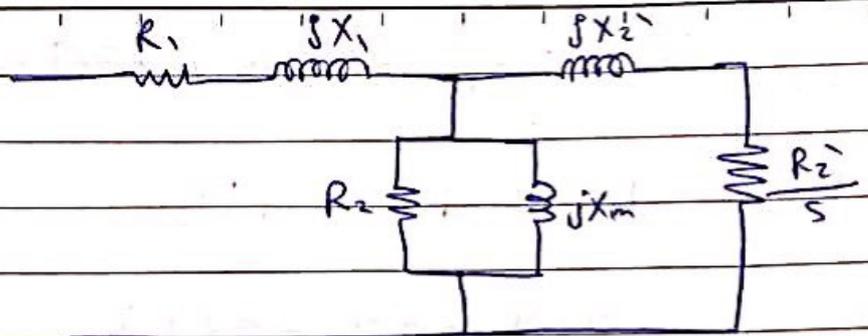

$$I_1 = I_0 + I_2'$$

$$b) I_2' \Big|_{\max} = \frac{480/\sqrt{3} \angle 0}{(1+10) + j10} = 18.6 \angle -49.5^\circ \text{ A}$$

$$c) n_{T\max} = (1 - S_{\text{new}}) n_s$$

$$n_s = \frac{120 f}{P} = \frac{120 \times 60}{12} = 600 \text{ rpm}$$

$$n_{T\max} = (1 - 0.05) (600) = 570 \text{ rpm}$$

$$d) T_{\max} = \frac{3 |V_1|^2}{2 \omega_s} \cdot \frac{1}{R_1 + \sqrt{R_1^2 + X_{eq}^2}}$$

$$\text{OR } \tau = \frac{3 |V_1|^2}{\omega_s} \cdot \frac{R_1' / S_{\max}}{\left(R_1 + \frac{R_2'}{S_{\max}}\right) + X_{eq}^2}$$


$$\omega_s = \frac{2\pi n_s}{60}$$

$$= \frac{2\pi \cdot 600}{60} = 20\pi = 62.8 \text{ rad/s}$$

99

$$T_{max} = \frac{3 * (480/\sqrt{3})^2}{2 * 62.8} \cdot \frac{1}{1 + \sqrt{1^2 + 10^2}}$$

$$T_{max} < 166.7 \text{ N.m}$$

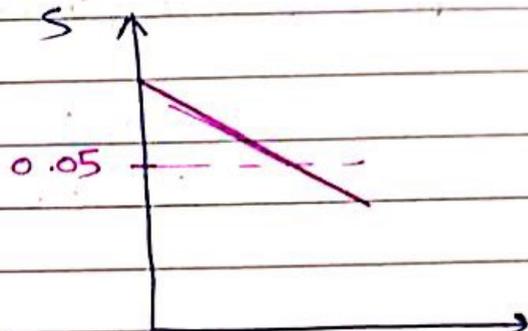

$$T_d = \frac{3IV_1^2}{\omega_s} \times \frac{R_2'/s}{(R_1 + R_2'/s)^2 + X_{eq}^2}$$

$$T_d = \frac{3IV_1^2}{\omega_s} \cdot \frac{R_2'/s}{(R_2'/s)}$$

$$T_d \propto \frac{s}{R_2'} \rightarrow \boxed{T_d \propto s}$$

Q3

3-ph, 480 V, p=4, f=60Hz, 30hp → rotor
SCIM, Y connected.

$$R_1 = 0.25 \Omega, R_2 = 0.2 \Omega, X_1 = 1.3$$

$$X_2 = 1.2, X_m = 35, P_{rot} = P_{Fandw} + P_{core}$$


$$P_{rot} = 1.25 \text{ kW}, V_{applied} = 440 \text{ V}$$

$$s = 3.5\% \quad \text{Find a) } I_m, \text{ PF}_1 \text{ ?!}$$

' I_1 = input current'

$$\text{b) } P_{in}, T_{sh}, T_{out}, \eta \text{ ?!}$$

mechanical torque slip

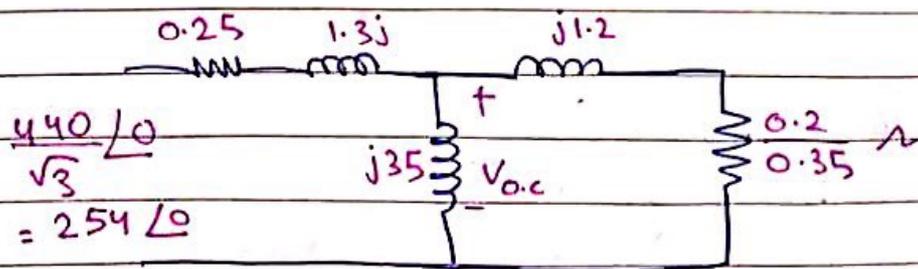

$$\frac{440/\sqrt{3}}{\sqrt{3}} = 254 \angle 0$$

100


use Thevenin equivalent's

$$V_{th} = V_{o.c} = \frac{(440/\sqrt{3})/0}{0.25 + j(1.3 + 35)} * j35 = 245 / 0.4$$

$$Z_{th} = j35 // (0.25 + j1.3)$$

$$\frac{j35 * (0.25 + j1.3)}{0.25 + j(35 + 1.3)} = 0.23 + j1.25 \Omega$$

$$= 1.28 / 7^\circ$$

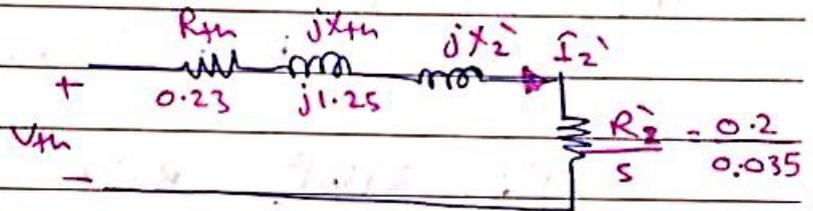

a) $n_m = (1-s)n_s$
 $= (1 - 0.035) * 1800$

$$n_m = 1737 \text{ rpm}$$

$$I_2' = \frac{V_{th}}{(R_{th} + \frac{R_2'}{s}) + j(X_{th} + X_2')}$$

$$= \frac{245 / 0.4^\circ}{(0.23 + \frac{0.2}{0.035}) + j(1.25 + 1.2)}$$

$$I_2' = 38 / -22^\circ$$

$$I_1 = I_m + I_2'$$

$$I_2' = \frac{I_1' * jX_m}{\frac{R_2'}{s} + (jX_2' + jX_m)}$$

$$\vec{I}_1 = \frac{(R_2/s) + j(X_2 + X_m)}{jX_m} \cdot \vec{I}_2'$$

$$\vec{I}_1 = \frac{\left(\frac{0.2}{0.035} + j(1.2 + 35)\right) \times 38 \angle -22^\circ}{j35}$$

$$\vec{I}_1 = 39.8 \angle -31^\circ \text{ A}$$

$$\text{PF} = \cos(31) = 0.857 \text{ lag.}$$

* another solution for \vec{I}_1 :-

$$Z_{eq} = \left(\frac{0.2}{0.035} + j1.2\right) // j35 + (0.25 + j1.3)$$

$$Z_{eq} = 6.37 \angle 31^\circ$$

$$\vec{I}_1 = \frac{V}{Z_{eq}} = \frac{\frac{440}{\sqrt{3}} \angle 0}{6.37 \angle 31} = 39.3 \angle -31 \text{ A}$$

$$\begin{aligned} \text{b) } P_{in} &= \sqrt{3} V_L I_L \cos\theta = 3 V_{ph} I_{ph} \cos\theta \\ &= \sqrt{3} \times 440 \times 39.8 \times 0.857 = 3 \times \frac{440}{\sqrt{3}} \times 39.8 \times 0.857 \end{aligned}$$

$$P_{in} = 22.75 \text{ kW}$$

$$T_{out} = \frac{P_{out}}{\omega_m}$$

$$P_{out} = P_d = P_{rot}$$

$$P_d = 3 |\vec{I}_2'| \left(\frac{1-s}{s}\right) R_2' = (1-s) P_g$$

$$\text{102.1} \quad = 3 (38)^2 \left(\frac{1-0.035}{0.035}\right) \times 0.2 \Rightarrow P_d = 23.88 \text{ kW}$$

$$P_{out} = 23.88 - 1.25 = 22.63 \text{ kW}$$

$$P_{out \text{ hp}} = \frac{22.63 \text{ kW}}{746} = 30.35 \text{ hp}$$

$$\begin{aligned} \omega_m &= \frac{2\pi n_m}{60} = (1-s)\omega_m \\ &= (1-0.035) \times 188.5 \\ &= 181.9 \text{ rad/s} \end{aligned}$$

$$T_{out} = \frac{22.63 \times 10^3}{181.9} = 124.4 \text{ N}\cdot\text{m}$$


$$\eta = \frac{P_{out}}{P_{in}} \times 100\% = \frac{22.63}{27.75} \times 100\%$$

$$\eta = 81.5\%$$

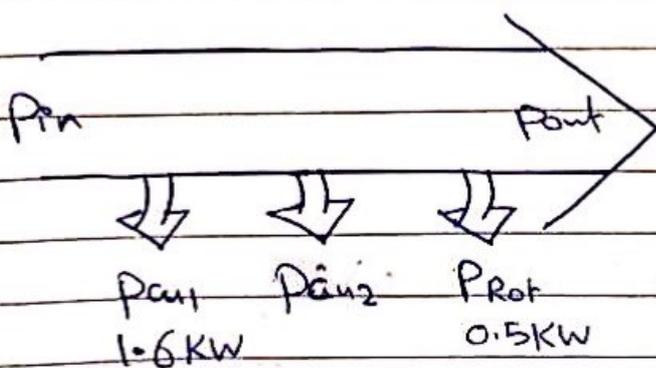Q4

$p = 6, 60 \text{ Hz}, n_m = 1152 \rightarrow P_{in} = 44 \text{ kW}$
 $P_{rot} = 0.5 \text{ kW}, P_{cu1} = 1.6 \text{ kW}$

find a) $S, P_g, P_{cu2} ?!$
 b) $T_d, P_{dhp}, P_{out \text{ hp}}, T_{out} ?!$



P	50 Hz	60 Hz
2	3000	3600
4	1500	1800
6	1000	1200
8	750	500

103

$$a) \Rightarrow S = \frac{1200 - 1152}{1200} = \frac{48}{1200} = 0.04 = \boxed{4\%}$$

$$\Rightarrow P_g = P_{in} - P_{out} = 44 \text{ K} - 1.6 \text{ K} = \boxed{42.4 \text{ KW}}$$

$$\Rightarrow P_{aux} = S \cdot P_g = 0.04 \times 42.4 \text{ K} = \boxed{1.7 \text{ KW}}$$

$$\Rightarrow T_d = \frac{P_d}{\omega_m} = \frac{(1-S)P_g}{(1-S)\omega_s} = \frac{P_g}{\omega_s}$$

$$P_d = (1-0.04) \times 42.4 \text{ KW} = 40.7 \text{ K}$$

$$\omega_s = \frac{2\pi \times 1200}{60} = 40\pi$$

$$\omega_m = (1-0.04)\omega_s = 0.96 \times 40\pi$$

$$b) \Rightarrow T_d = \frac{40.7}{40\pi} = \boxed{337 \text{ Nm}}$$

$$\Rightarrow P_{dhp} = \frac{40.7 \times 10^3}{746} = \boxed{57 \text{ hp}}$$

$$P_{out} = P_d - P_{rot} = (40.7 - 0.5) \text{ K} = 40.2 \text{ KW}$$

$$\Rightarrow P_{outhp} = \frac{40.2 \times 10^3}{746} = \boxed{53.9 \text{ hp}}$$


$$\Rightarrow T_{out} = \frac{P_{out}}{\omega_m} = \frac{40.2 \times 10^3}{0.96 \times 40\pi} = \boxed{333 \text{ N.m}}$$

Q5 $V_{LL} = 230V$, $p = 4$, $P_{out} = 10hp$ of $f = 60Hz$
 $S_{FL} = 0.045$, $R_1 = 0.35$, $R_2 = ?$
 $X_1 = 0.5$, $X_2 = 0.5$, $X_m = 15$, $P_{rot} \approx 0.0$

Sol:

$$T_{st} = \frac{3|V_1|^2 R_2}{\omega_s (R_1 + R_2)^2 + (X_1 + X_2)^2}$$

$$T_{max} = \frac{3|V_1|^2}{2\omega_s} \times \frac{1}{R_1 + \sqrt{R_1^2 + (X_1 + X_2)^2}}$$

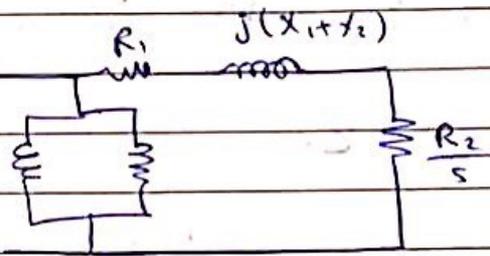

$$S_{max} = \frac{R_2}{\sqrt{R_1^2 + (X_1 + X_2)^2}}$$

$$T_{FL} = \frac{3|V_1|^2}{\omega_s} \times \frac{R_2 / S_{FL}}{(R_1 + \frac{R_2}{S_{FL}})^2 + (X_1 + X_2)^2}$$

⇒ solve for R_2 $\begin{matrix} \nearrow R_{21} \\ \searrow R_{22} \end{matrix}$
 chose one.

Since $P_{rot} \approx 0.0$

$$P_{out} = P_d \Rightarrow T_{out} = T_d$$

$$T_{out} = \frac{P_{out}}{\omega_{mFL}}$$

$$\omega_{mFL} = (1 - S_{FL}) \times \omega_s$$

$$\omega_s = 188.5 \text{ rad/s} = \left(2\pi \times \frac{120 \times 60}{40} \right) = 60\pi$$

$$P_{out} = 10 \times 746 = 7460 \text{ W}$$

$$T_{out} = \frac{7460}{188.5} = 39.6 \text{ N.m}$$

$$n_{Tmax} = (1 - S_{max}) n_s = (1 - S_{max}) \cdot 1800$$

105

Q6 $P_{outFL} = 20hp$, $V_{LL} = 440V$, Δ connected.


$T_{st1} = 98 N.m$
 ~~$T_{FL1} = 72 N.m$~~ $T_{FL1} = 72 N.m$ } at $V_{LL1} = 440V$

Find $T_{st2} = ?!$ at $V_{LL2} = 300V$

Sol:


$$T_{st2} = \left(\frac{300}{440}\right)^2 \times 98 = 45.6 N.m$$

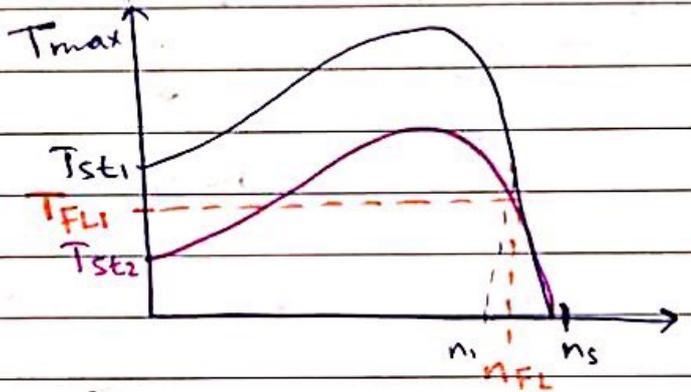$n_s \rightarrow$ constant
 $n_m = (1-s)n_s$
 \downarrow
 n_m change when s change
 $s \Rightarrow$ depend on load.



$$T_{st3} = T_{FL1} = 72$$
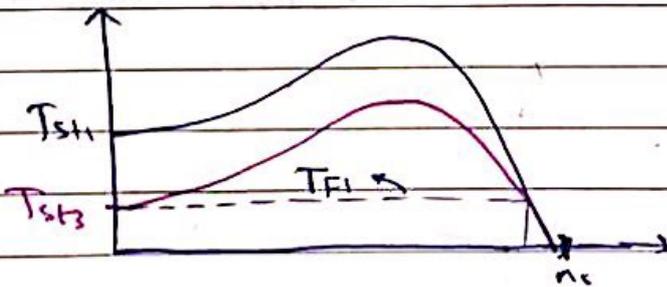
$$\frac{T_{st3}}{T_{st1}} = \left(\frac{V_3}{V_1}\right)^2 \Rightarrow T_{st3} = \left(\frac{V_3}{440}\right)^2 \times 98 = 72$$





$$V_3 = \sqrt{\frac{72}{98}} \times 440 = 377V$$


Q7 $V_{LL} = 440V$, $P_{outFL} = 40hp$, $f = 60Hz$
 $n_{FL} = 1750rpm$ ($n_s = 1800rpm \rightarrow f = 60$
 $\rightarrow p = 4$

wound Rotor "WRIM"

'WRIM' 80

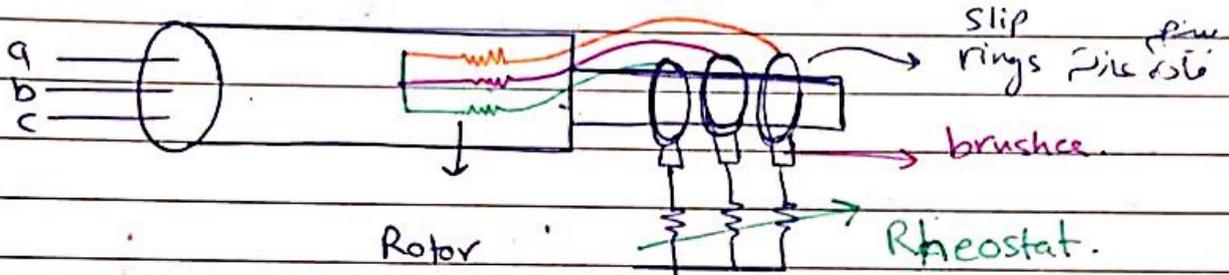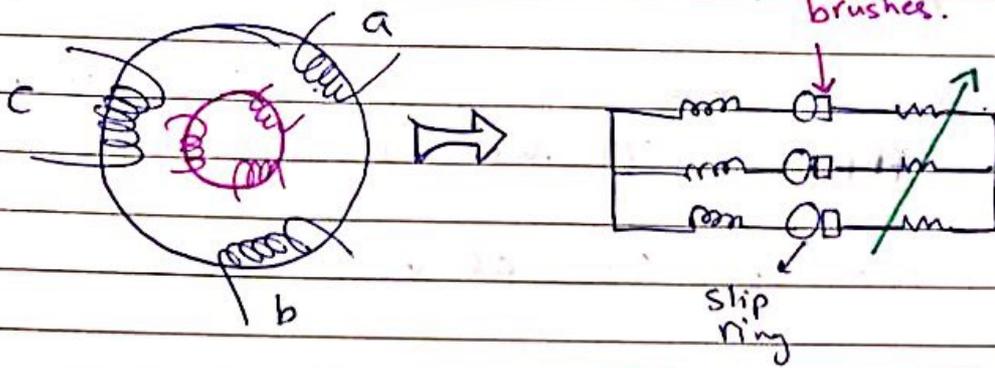


notes for SCIM "Squard Cage"

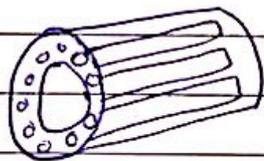

$R \rightarrow R_1, R_2$

$R_1 = 0.2 \Omega$, $R_2 = 0.15 \Omega$, $X_1 = 1.0 \Omega$
 $X_2 = 0.8 \Omega$, $X_m = 30 \Omega$ Final $R_{rh} \Rightarrow T_{nst} = T_{max}$

$$T_d = \frac{3|V|^2}{\omega_s} \cdot \frac{R_2/s}{(R_1 + \frac{R_2}{s})^2 + (X_1 + X_2)^2}$$

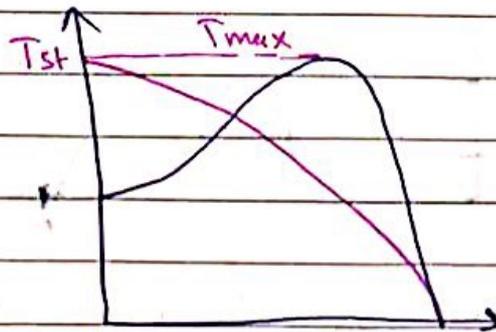


$$T_{dst} \Big|_{s=1.0} = \frac{3|V|^2}{\omega_s} \cdot \frac{R_2}{(R_1 + R_2)^2 + (X_1 + X_2)^2}$$

we change R_2 depend on R_2

$$T_{max} = \frac{3|V|^2}{2\omega_s} \cdot \frac{1}{R_1 + \sqrt{R_1^2 + (X_1 + X_2)^2}}$$

107

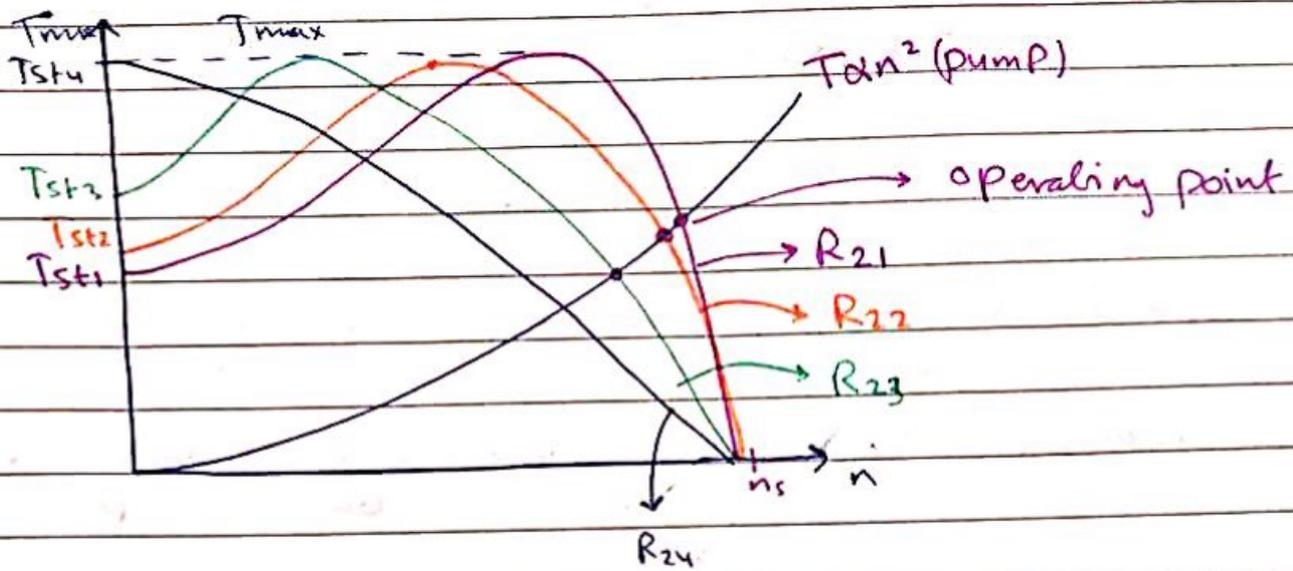


Where $R_{24} > R_{23} > R_{22} > R_{21}$

"Mechanical speed torque."

if we control the R_2
we can control the
speed

→ for max torque.

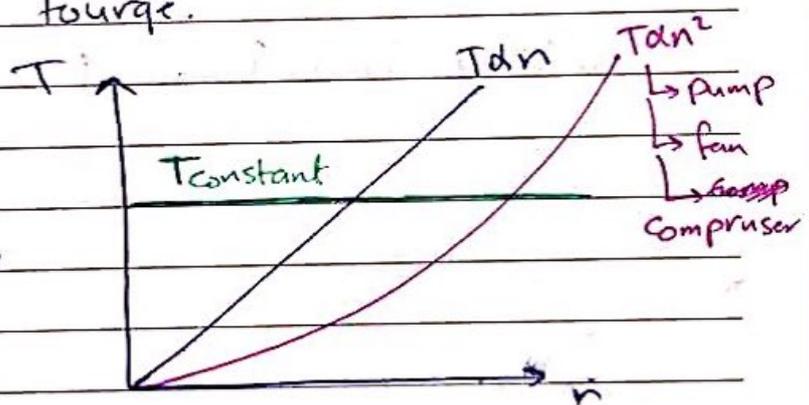

$$\frac{R_2}{S_{max}} = |R_1 + j(x_1 + x_2)| = \sqrt{R_1^2 + (x_1 + x_2)^2}$$

$$S_{max} = \frac{R_2 + R_{rh}}{\sqrt{R_2^2 + (x_1 + x_2)^2}} = 1 \text{ (at starting)}$$

$$R_{rh} = \sqrt{R_1^2 + (x_1 + x_2)^2} - R_2$$

$$= \sqrt{(0.2)^2 + (1.8)^2} - 0.15$$

$$T_{max} = \frac{3 \left(\frac{440}{\sqrt{3}} \right)^2}{2 \times 188.5} \times \frac{1}{0.2 + \sqrt{0.2^2 + 1.8^2}}$$

$$= 255 \text{ Nm} = T_{dst}$$

Speed Control of induction Motor 84



$$N_m = (1-s)n_s \quad \omega_s = \frac{2\pi n_s}{60} = \frac{2\pi \times 120 \times f}{60}$$

$$= \frac{4\pi f}{P}$$

$$T_{dmax} = \frac{3|V|^2 \cdot P}{8\pi \times f \cdot R_1 + \sqrt{R_1^2 + (X_1 + X_2)^2}}$$

$$V \uparrow \rightarrow T_{max} \uparrow \rightarrow T_{st} \uparrow$$

① by varying the applied voltages

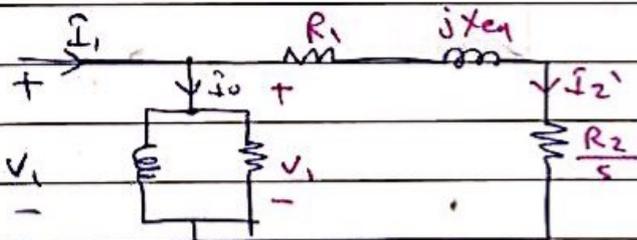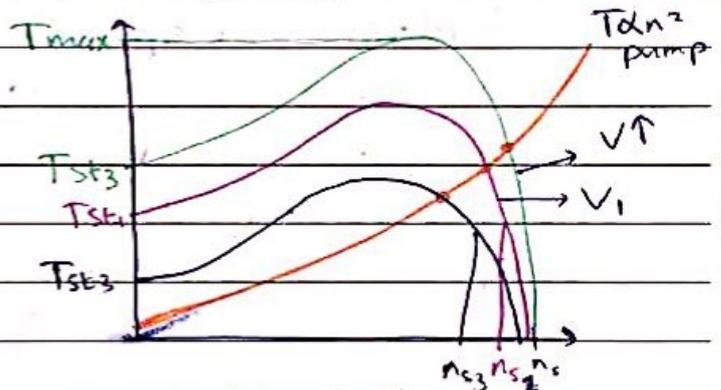



$$\begin{aligned} I_1 &= I_0 + I_2' \\ \uparrow I_1 &\rightarrow I_2' \uparrow \\ I_0 &\text{ is almost fixed} \end{aligned}$$

$$|I_2'|_{st} = \frac{|V_1|}{\sqrt{(R_1 + R_2)^2 + X_{eq}^2}}$$

at starting the T.M draws very large current
Inrush times full load current

② Varying the frequency


$$n_s = \frac{120 f}{P}$$

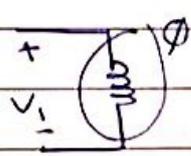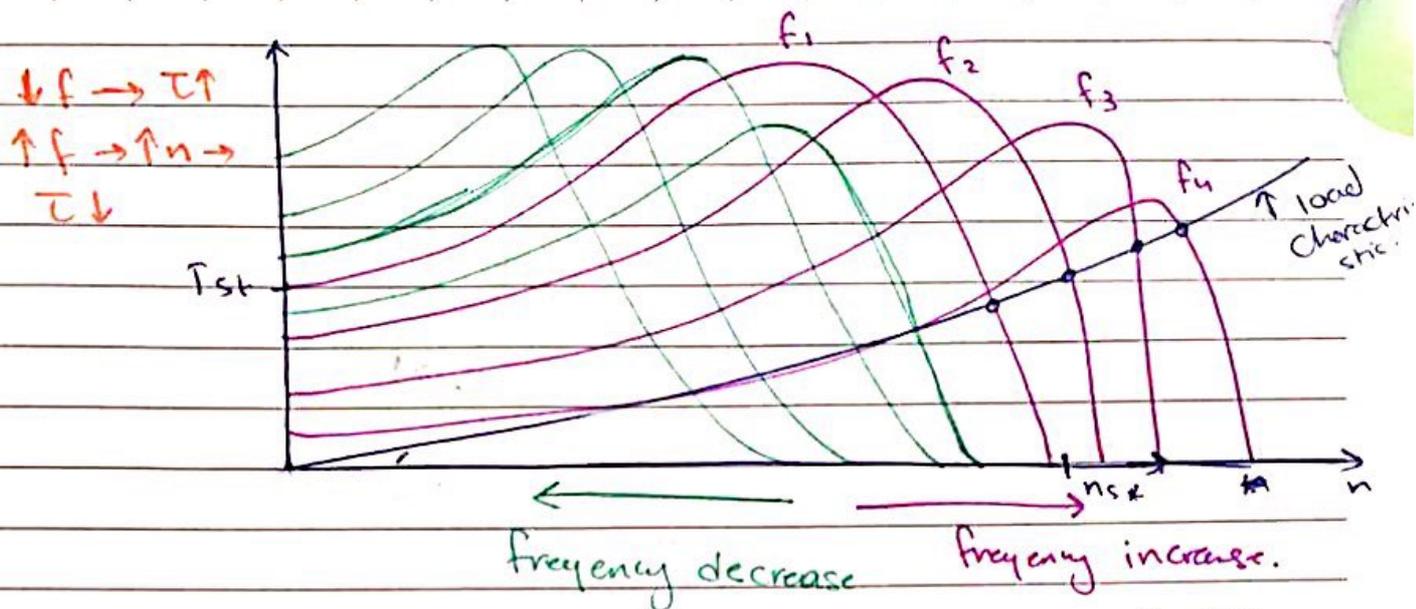

$$|V_1| = 4.44 f N_{ph} \Phi_m$$

$$* n_s = 3000 \text{ rpm}$$

$$p=2 \quad f=50 \text{ Hz}$$

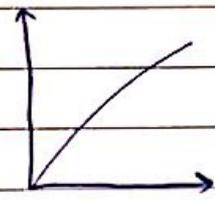

$$\Phi_1 = \Phi_2$$

$$V_1 \propto f_1 \Phi_1$$

$$V_2 \propto f_2 \Phi_2$$

$$\frac{V_1}{V_2} = \frac{f_1}{f_2} \frac{\Phi_1}{\Phi_2}$$

$$\Phi = \frac{V}{4.44 f N_{ph}} \quad \Phi \uparrow \rightarrow f \downarrow$$

" Φ constant $\rightarrow f \downarrow \rightarrow V \downarrow$ "


* the problem is when we decrease f we need to decrease the voltage.

③ change number of pole :-

$$f = 50 \text{ Hz} \quad p=2 \rightarrow n_s = 3000 \text{ rpm}$$

$$p=4 \rightarrow n_s = 1500 \text{ rpm}$$
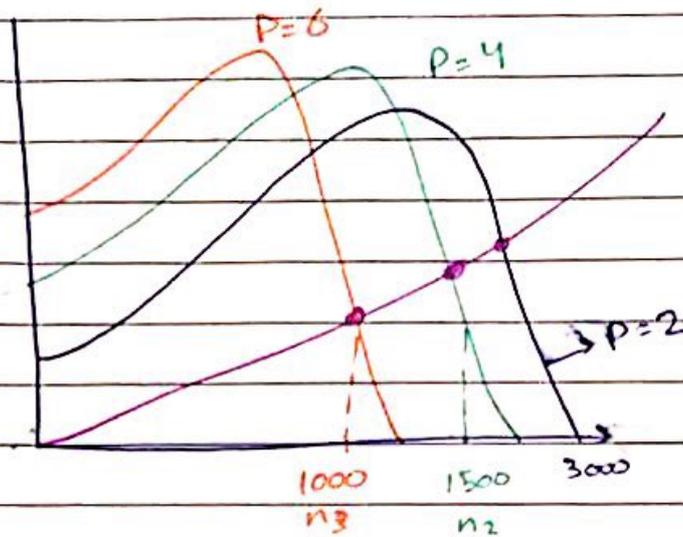
$$p=6 \rightarrow n_s = 1000 \text{ rpm}$$



④ Varying Rotor resistance Δ

① and ④ \Rightarrow "variable slip method."

note: we can change the direction of the motor by change the 3-phase input voltage (abc sequence)



Question #1

A 100 hp, 60-Hz, three-phase induction motor has a slip of 0.03 at full load. Compute the efficiency of the motor at full load when the friction and windage losses are 900W, the stator core loss is 4200W, and the stator copper loss is 2700W.

Solution:

$$P_{out} = \frac{100}{1.34} = 74.63 \text{ kW}$$

$$P_d = P_{out} + P_{rotational} = 74.63 + 0.9 = 75.53 \text{ kW}$$

$$P_g = \frac{P_d}{1-s} = \frac{75.53}{1-0.03} = 77.87 \text{ kW}$$

$$P_m = P_g + P_{iron} + P_{cwl} = 77.87 + 4.2 + 2.7 = 84.77 \text{ kW} \Rightarrow \eta = \frac{P_{out}}{P_m} = \frac{74.63}{84.77} = 88\%$$

Question #2

A three-phase, 480-volt, 60-Hz, 12-pole, induction motor has the following parameters: $R_1 = 1.0 \Omega$; $R'_2 = 0.5 \Omega$; $X_{eq} = 10 \Omega$; $X_c = 100 \Omega$; $R_c = 800 \Omega$ Calculate the following:

- The slip at maximum torque.
- The current at maximum torque
- The speed at maximum torque
- The maximum torque.

Solution:

$$a. \quad S_{max} = \frac{R'_2}{\sqrt{R_1^2 + X_{eq}^2}} = \frac{0.5}{\sqrt{1+100}} \approx 0.05$$

- b. The current at maximum torque

$$I'_2 = \frac{V_{ph}}{\sqrt{\left(R_1 + \frac{R'_2}{S_{max}}\right)^2 + X_{eq}^2}} = \frac{480/\sqrt{3}}{\sqrt{\left(1.0 + \frac{0.5}{0.05}\right)^2 + 100}} = 18.64 \text{ A}$$

- c. The speed at maximum torque

$$n_s = 120 \frac{f}{p} = 120 \frac{60}{12} = 600 \text{ rpm}$$

$$\omega_s = 2\pi \frac{n_s}{60} = 62.83 \text{ rad/s}$$

- d. The maximum torque

$$T_{max} = \frac{3V^2}{2\omega_s \left[R_1 + \sqrt{R_1^2 + X_{eq}^2} \right]} = \frac{480^2}{2 * 62.83 \left[1.0 + \sqrt{1.0 + 100} \right]} = 166.68 \text{ Nm}$$

Question #3

A three-phase, 30-hp, 480-V, 4-pole, 60-Hz induction motor has the following equivalent circuit parameters in Ω per phase referred to stator:

$$R_1 = 0.25 \quad R_2 = 0.20 \quad X_1 = 1.30 \quad X_2 = 1.20 \quad X_m = 35$$

The total core, friction, and windage losses may be assumed constant at 1250 W. The motor is connected directly to a 440-V source, and it runs at a slip of 3.5%. Compute the following:

- Motor speed, input current, and power factor and
- Power input, shaft output torque, and efficiency of the motor.

Question #4

A three-phase, 6-pole, 60-Hz induction motor is operating at a speed of 1152 rpm. The power input to the motor is 44 kW, the rotational losses are 500 W, and the stator copper loss is 1600 W. Find the following:

- Slip, airgap power, and rotor copper loss
- Developed torque, developed horsepower, output torque, and output horsepower

Question #5

A 3-phase, 10-hp, 230-V, 4-pole, 60-Hz, Y-connected induction motor develops its full-load torque at a slip of 4.5% when operating at 230 V and 60-Hz. The per-phase equivalent circuit impedances of the motor are

$$R_1 = 0.35 \quad X_1 = 0.5 \quad X_2 = 0.5 \quad X_m = 15.0$$

The mechanical and core losses are assumed to be negligible. Determine the following:

- Rotor resistance R_2 , and slip S ,
- Starting torque, maximum torque, and rotor speed at maximum torque.

Question #6

A 3-phase, 20-hp, 440-V, 6-pole, 60-Hz, Y-connected induction motor has a starting torque of 98 N-m and a full-load torque of 72 N-m. Calculate:

- The starting torque when the applied voltage is reduced to 300 V.
- The applied voltage in order to develop a starting torque equal to the full-load torque.

Question #7

A 3-phase, 440-V, 25-hp, 60-Hz, 1750-rpm, Y-connected, wound-rotor induction motor has the following equivalent circuit parameters.

$$R_1 = 0.20 \quad R_2 = 0.15 \quad X_1 = 1.0 \quad X_2 = 0.80 \quad X_m = 30$$

Determine the resistance of the rheostat in the rotor circuit such that the maximum torque occurs at starting. Calculate the starting torque before and after adding the resistance.

Question #8

A 480V, 60 Hz, 6-pole, three-phase, delta-connected induction motor with the following parameters:

$$R_1=0.461 \Omega, R_2=0.258 \Omega, X_1=0.507 \Omega, X_2=0.309 \Omega, X_m=30.74 \Omega$$

Rotational losses are 2450W. Now, suppose that the machine is being driven by a mechanical system such that it is rotating at 1224 rpm. Calculate the following information:

- slip
- Line Current
- Power and Reactive Power at the terminals
- Airgap Power
- Torque Developed
- Mechanical Power
- Efficiency
- Much of the theory for this problem is identical to a motor problem:

Solution:

Slip is given by

$$s = \frac{\omega_s - \omega_m}{\omega_s} = \frac{n_s - n_m}{n_s}$$

Using the rpm equation, $s = (1200-1224)/1200 = -0.02$

Now, phase current is given by

$$I_1 = \frac{V_1}{Z_m}$$

where phase impedance is given by

$$Z_m = R_1 + jX_1 + \frac{jX_m \left(\frac{R_2}{s} + jX_2 \right)}{\frac{R_2}{s} + j(X_2 + X_m)}$$

Using the above equation, $Z_m = -10.3 + j5.29 \Omega$

And noting that the machine is delta connected, $V_1 = V_{LL} = 480V$, $I_1 = -36.7 - j18.8 A$. $|I_1| = 41.4 A$.
Therefore, $I_L = \sqrt{3} \times 41.4 = 71.7 A$

Note that the real part of phase current is negative, indicating that real power flows out of the terminals. Also, the imaginary part of the phase current, which indicates that reactive power must flow into the terminals. An induction generator cannot operate without a reactive power supply, either from a power grid or capacitor bank

Using complex notation, $S = 3VI^*$

or

$$P_{elec} = 3 \times V \times \text{Re}\{I\} = -53.0 \text{ kW}, \quad Q_{elec} = -3 \times V \times \text{Im}\{I\} = +27.2 \text{ kVAR}$$

Airgap Power is given by

$$P_{ag} = \frac{3I_2^2 R_2}{s}$$

This approach requires rotor current to be found. With no core loss resistance:

$$I_2 = \frac{jX_m}{\frac{R_2}{s} + j(X_2 + X_m)} I_1$$

$$I_2 = \left| \frac{jX_m}{\frac{R_2}{s} + j(X_2 + X_m)} \right| I_1$$

Giving $I_2 = 37.8$ A. Substituting into the power equation $P_{gap} = -55.4$ kW

Torque developed can be found from

$$\tau = \frac{P_{gap}}{\omega_s}$$

where synchronous speed in radians per second is given by

$$\omega_s = \frac{4\pi f_e}{p}$$

giving $\tau = -441$ Nm

Mechanical power can be found using

$$P_{mech} = P_{conv} - P_{rotational}$$

and

$$P_{conv} = (1-s) P_{gap}$$

Therefore mechanical power in kW is: $P_{out} = -55.4 \times (1.0+0.02) - 2.45$, $P_{mech} = -58.9$ kW

Efficiency is given by

$$\eta = \frac{P_{elec}}{P_{out}} \times 100\%$$

Therefore, $\eta = 53.0/58.9 = 89.9$ %

Summary

It can be seen from the above analysis that the equations for an induction motor can all be applied to an induction generator. (As long as output and input power are correctly described as either electrical or mechanical).. Induction generation used to be relatively rare. However, it is becoming increasingly common as induction generators are the generator of choice for large wind turbines. The requirement of an induction generator to have an independent reactive power supply has caused significant research into the impact of large wind farms of power system stability.

Question #9

As an example, consider the use of a 10 hp, 1760 r/min, 440 V, three-phase induction motor as an asynchronous generator. The full-load current of the motor is 10 A and the full-load power factor is 0.8.

Required capacitance per phase if capacitors are connected in delta:

$$\text{Apparent power } S = \sqrt{3} E I = 1.73 \times 440 \times 10 = 7612 \text{ VA}$$

$$\text{Active power } P = S \cos \theta = 7612 \times 0.8 = 6090 \text{ W}$$

$$\text{Reactive power } Q = \sqrt{S^2 - P^2} = 4567 \text{ VAR}$$

For a machine to run as an asynchronous generator, capacitor bank must supply minimum $4567 / 3$ phases = 1523 VAR per phase. Voltage per capacitor is 440 V because capacitors are connected in delta.

$$\text{Capacitive current } I_c = Q/E = 1523/440 = 3.46 \text{ A}$$

$$\text{Capacitive reactance per phase } X_c = E/I_c = 127 \Omega$$

Minimum capacitance per phase:

$$C = 1 / (2 \times \pi \times f \times X_c) = 1 / (2 \times 3.141 \times 60 \times 127) = 21 \text{ microfarads.}$$

If the load also absorbs reactive power, capacitor bank must be increased in size to compensate.


Prime mover speed should be used to generate frequency of 60 Hz:

Typically, slip should be similar to full-load value when machine is running as motor, but negative (generator operation):


if $N_s = 1800$, one can choose $N = N_s + 40$ rpm

Required prime mover speed $N = 1800 + 40 = 1840$ rpm.



DC Shunt

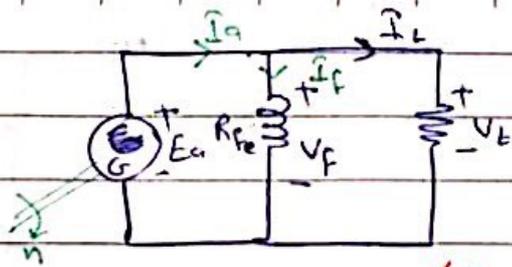

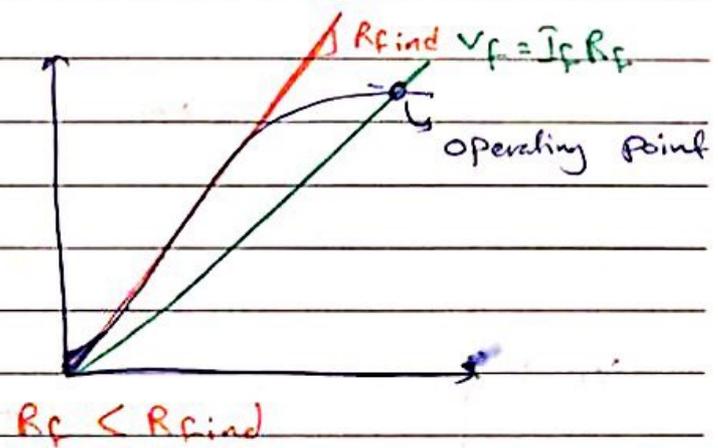$E_b = K_n \Phi \omega$
 $E_b \propto \hat{i}_f \cdot n$
 $n \equiv \text{constant}$
 $E_b \propto \hat{i}_f$
 $V_f = R_f \hat{i}_f$



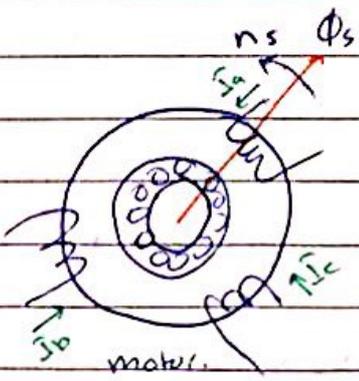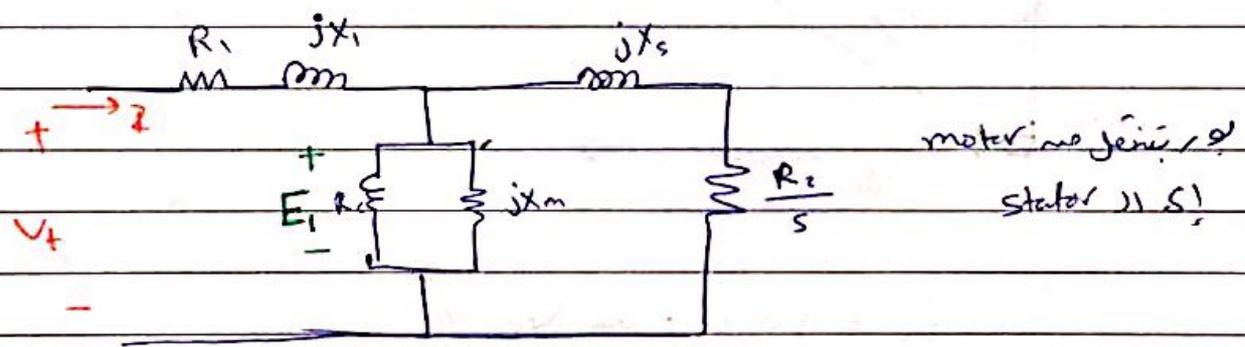
$R_{find} \Rightarrow$ maximum (ω vs \hat{i}_f)
curve ω





$E = 4.44 N_{ph} \Phi$
 $V_t = \hat{i}_a Z_1 + E_1$
 $\uparrow E \rightarrow \Phi \uparrow$

$Q_{cph} = \frac{V_c^2 P_h}{X_s} = \frac{V_c^2 P_h}{1/\omega c}$

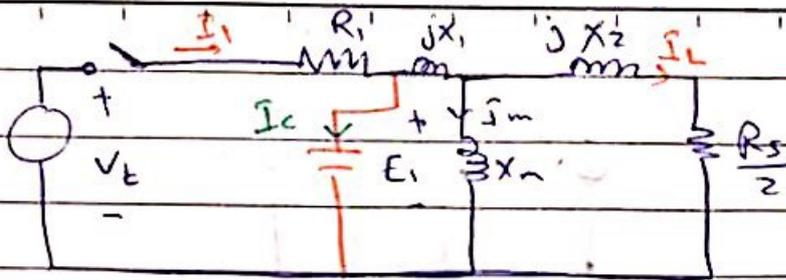$Q_c = \omega c V_c^2 P_h$
 $\omega \uparrow \rightarrow Q_c \uparrow$



$$E_i = I_m X_m$$

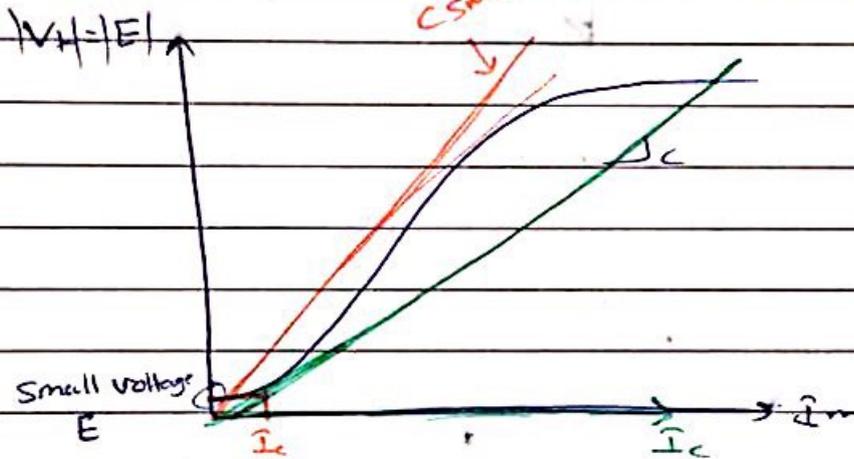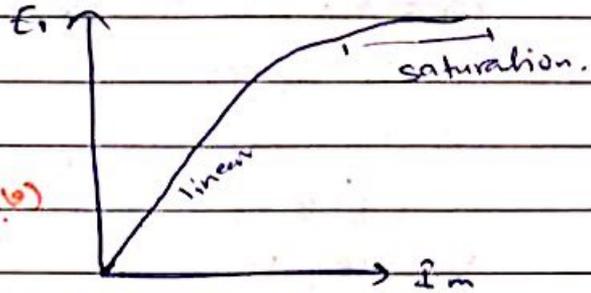


$(C_{small} \rightarrow \text{large slope})$

Capacitor of Δ connection *

$$I_c = \frac{|V_c|}{X_c} = \omega C V_c$$

$$V_c = \frac{1}{\omega C} \cdot I_c$$

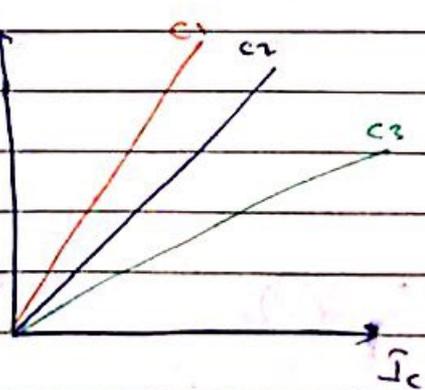

Flux $\propto I_m$ $\propto I_c$ *
Small voltage E

$I_c = I_m$ at no load.

$$C_1 < C_2 < C_3$$

(Δ connection capacitor bank in (slide 18))

Resistance $\rightarrow -v_c \rightarrow$ angle $> 90 \rightarrow$ work as generator.


(Real part negative) \rightarrow negative power.

Var is li
generate real power

113

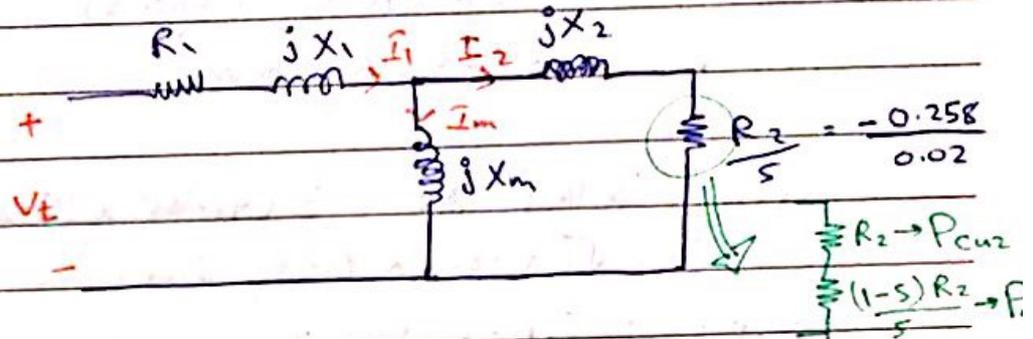Q8

480V, 60 Hz, $p=6$, 3-ph I.G. D Conn
 $R_1 = 0.461 \Omega$, $R_2 = 0.258 \Omega$, $X_1 = 0.507$
 $X_2 = 0.309$, $X_m = 30.7 \Omega$, $P_{rot} = 2450 W$
 $n_m = 1224 \text{ rpm}$



a) $s = \frac{n_s - n_m}{n_s} \times 100 = \frac{1200 - 1224}{1200} = 2\% = 0.02$

Find a) slip %

b) I_1 ?

$|I_L| = \sqrt{3} |I_{ph}$



c) P and Q at the terminals ?

d) P_g ?

e) T_d ?

f) P_{mech} ?

g) γ ?

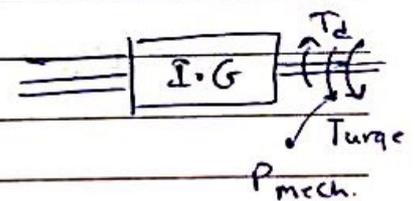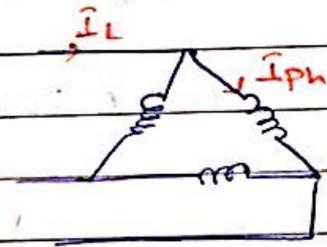


b) $Z_{in} = R_1 + jX_1 + jX_m \parallel (R_2/s + jX_2)$
 $= -10.3 + j5.29$


$I_1 = \frac{480 \angle 0}{-10.3 + j5.29}$

$= -36.7 - j18.8 A$

$I_1 = 41.4 \angle -152^\circ$

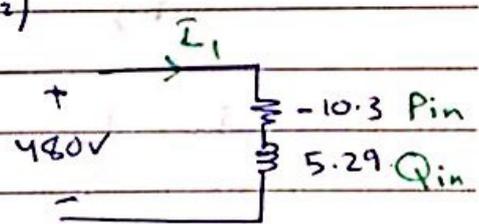

$I_L = \sqrt{3} \times 41.4 = 71.7 A$

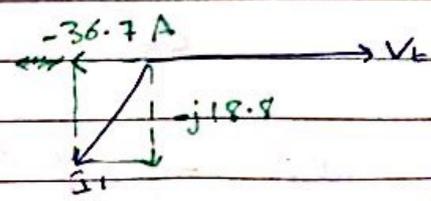

(114)

$$\begin{aligned}
 \textcircled{c} \quad P_{in3\phi} &= \sqrt{3} V_L \hat{I}_L \cos \theta = 3 V_{ph} \hat{I}_{ph} \cos \theta \\
 &= 3 |\hat{I}_1|^2 R_{in} \\
 &= \sqrt{3} \times 480 \times 71.7 \times \cos(152^\circ) \\
 &= 3 \times 480 \times 41.4 \times \cos(152^\circ) \\
 &= 3 \times (41.4^2) (-10.3)
 \end{aligned}$$

$$P_{in3\phi} = -53.0 \text{ kW}$$

$$\begin{aligned}
 Q_{in} &= 3 |\hat{I}_1|^2 X_s = 3 (41.4)^2 \times (5.29) \\
 &= \sqrt{3} \times 480 \times 71.7 \sin(152^\circ)
 \end{aligned}$$

$$Q_{in} = 27.2 \text{ KVAR}$$

$$\textcircled{d} \quad P_g = 3 |\hat{I}_2|^2 \frac{R_2}{s} = P_{in} - P_{cu}$$

by C.D.R.

$$\hat{I}_2 = \frac{\hat{I}_1 * j X_m}{\frac{R_2}{s} + j(X_2 + X_m)} \Rightarrow \hat{I}_2 = 37.8 \text{ A}$$

$$P_g = 3 \times (37.8)^2 \times \frac{-0.258}{0.02}$$

$$= 3 \times (37.8)^2 \times (-12.9)$$


$$P_g = -55.4 \text{ kW}$$

$$\textcircled{e} \quad T_d = \frac{P_g}{\omega_s} = \frac{P_d}{\omega_m} = \frac{(1-s)P_g}{(1-s)\omega_s}$$

$$\omega_s = \frac{2\pi n_s}{60} = \frac{2\pi \times 1200}{60} = 40\pi \text{ rad/s}$$

$$T_d = \frac{-55.4 \times 10^3}{40\pi} = -441 \text{ N.m}$$

115

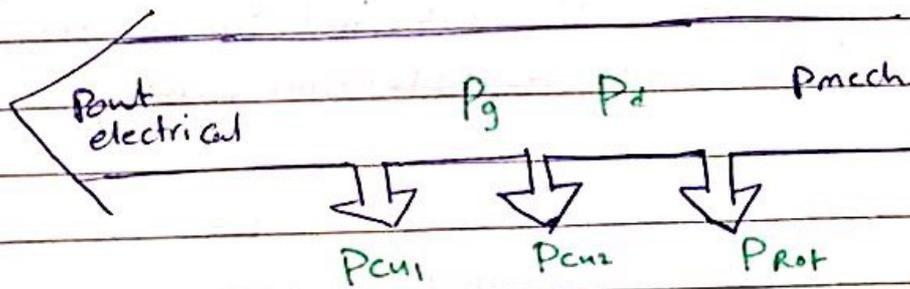

$$f) P_{mech} = P_d - P_{rot}$$

$$P_d = (1-s) P_g$$

$$= (1-0.02) * (-55.4 \text{ K})$$

~~$$= 53.9 \text{ Kw}$$~~

$$P_d = -56.5 \text{ Kw}$$

$$P_{mech} = ~~53.9~~ - 56.5 \text{ K} - 2.45 \text{ K}$$

$$P_{mech} = -58.9 \text{ Kw}$$

$$\eta = \frac{P_{out \text{ elect}}}{P_{in \text{ (mech)}}} = \frac{53}{58.9} \times 100 = 89.97\%$$

slide 6

Phase 90° mechanical phase between main winding and starting winding.

winding ϵ δ : D
 . ϵ all types

slide 8 * main field \Rightarrow counter clock \swarrow 2 field in steps
 clock wise \searrow


starting winding \Rightarrow magnetic field \swarrow

δ S \leftarrow rotor field \rightarrow rotor
 $n_m \rightarrow$ forward.
 $n_s \rightarrow$ backward.

- single
- * ~~one~~ phase \Rightarrow hp < 1
- * angle $\delta < > 45^\circ \rightarrow$ PF < 0.7
- * ~~one~~ single phase \rightarrow very poor PF

slide 29
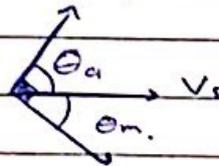
$$\tan \left(\frac{X_c - X_a}{R} \right) = \text{angle } \theta_a$$



Q1



120V, 1/4 hp, P = 4

$R_1 = 2 \Omega$, $X_1 = 2.56 \Omega$

$R_2 = 2.8 \Omega$, $X_2 = 2.56 \Omega$, $X_M = 60.5 \Omega$

$S = 0.05$, $P_{rot} = 51W$

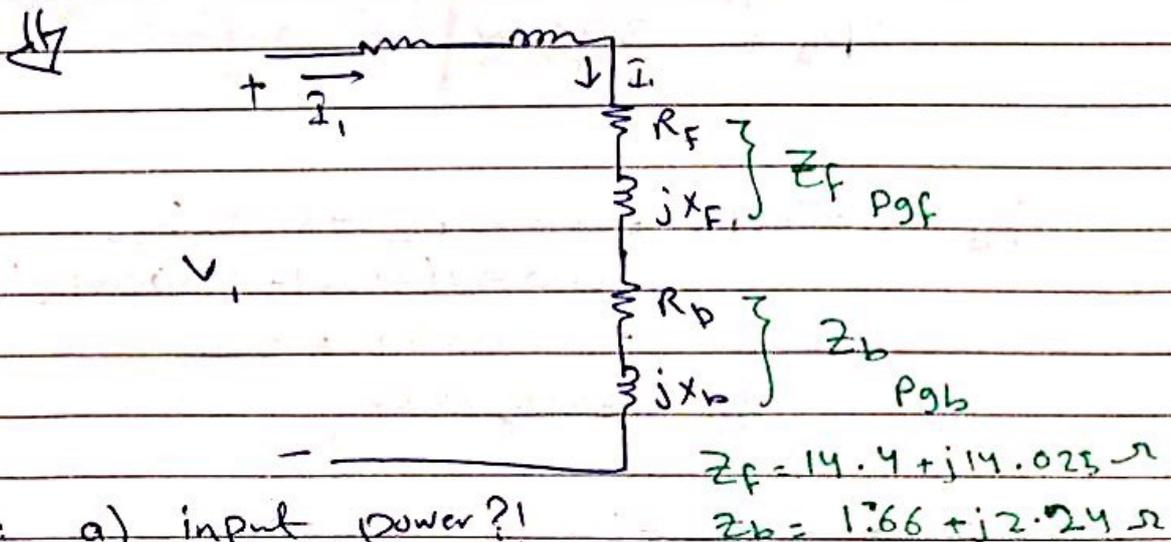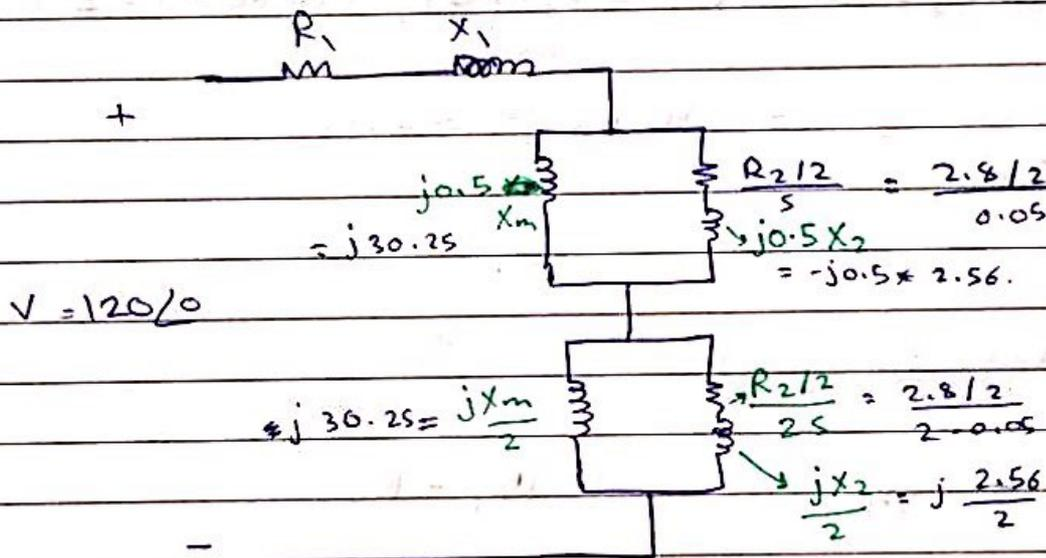- Find
- a) Input power.
 - b) P_g
 - c) P_{conv}
 - d) P_{out}
 - e) T_d
 - f) T_{out}
 - g) η



Sol: a) input power?

$$P_{in} = V_1 I_1 \cos \theta$$

$$Z_F = 14.4 + j14.025 \Omega$$

$$Z_b = 1.66 + j2.24 \Omega$$


$$\hat{I}_1 = \frac{V_1}{R_1 + jX_1 + Z_f + Z_b} = \frac{V_1}{Z_{eq}}$$

$$Z_{eq} = 2 + j2.56 + \frac{1}{2} j60.5 // \left(\frac{2.8}{0.05} + j2.56 \right)$$

$$+ \frac{1}{2} 60.5 // \left(\frac{2.8}{1.95} + j2.56 \right)$$

$$= 2 + j2.56 + \underbrace{(14.4 + j14.03)}_{Z_f} + \underbrace{(1.66 + j2.25)}_{Z_b}$$
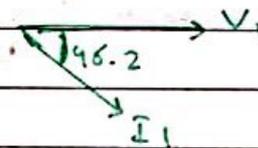
$$\hat{I}_1 = \frac{120}{Z_{eq}} = 4.86 \angle -46.2^\circ \text{ A}$$



(b) P_g (net air gap)

$$P_g = P_{gf} - P_{gb} = I_1^2 (R_f - R_b)$$

forward backward

$$= (4.86)^2 (14.4 - 1.66) = 340.6 - 15.6$$

$$P_g = 325 \text{ W}$$

$$\begin{aligned} \text{(c)} \quad P_d &= (1-s)P_g = (1-s)P_{gf} - (1-s)P_{gb} \\ &= (1-0.05)(340.6) - (1-0.05)(15.6) \\ &= (1-0.05) \times 325 \end{aligned}$$

$$P_d = 323 \text{ W}$$

$$\begin{aligned} \text{(d)} \quad P_{out} &= P_d - P_{rot} \\ &= 323 - 51 \end{aligned}$$

$$P_{out} = 272 \text{ W}$$

119

e) $T_d = ?!$

$$T_d = \frac{P_d}{\omega_m} = \frac{P_g}{\omega_s}$$


$p = 4, f = 60, n_s = 1800 \text{ rpm}$
 $\omega_s = 188.5 \text{ rad/s}$

$$T_d = \frac{325}{188.5} = 1.72 \text{ N.m}$$

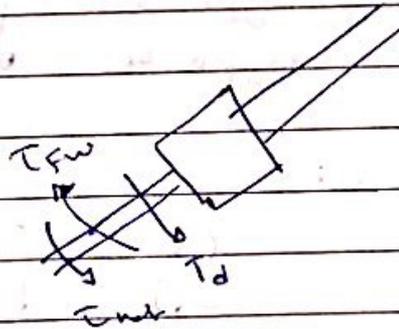f) $T_{out} = \frac{P_{out}}{\omega_m}$

$$\omega_m = (1-s)\omega_s = (1-0.05)(188.5)$$

$$T_{out} = \frac{272}{\omega_s} = 1.507$$



g) $\eta = \frac{P_{out}}{P_{in}}$

ولا يظهر الكون :-


التركيب ← induction motor ← توصيل المحرك

Single phase 4 pole


Voltage بطرفين -

→ Y-Δ Switch

→ Soft Starter.

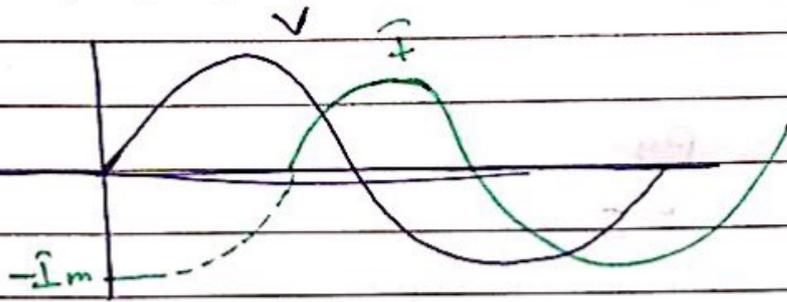

Start at $V=0$

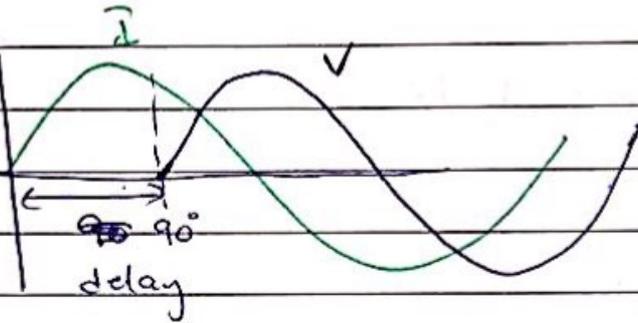


Start at $V=90^\circ$


* 4 types of induction motor:-

- | | | |
|--------|-----|---------------------------|
| type 1 | } ⇒ | سواء في المحرك أو المولد |
| type 2 | | لا يمكن أن يكون في المولد |
| type 3 | | لا يمكن أن يكون في المحرك |
| type 4 | | لا يمكن أن يكون في المولد |


type 1:-

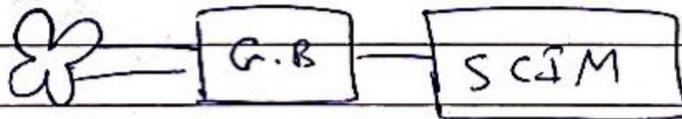

type 2:

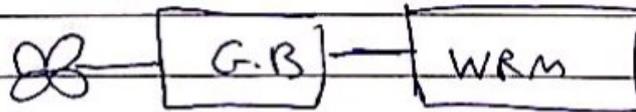


type 3: DFIG

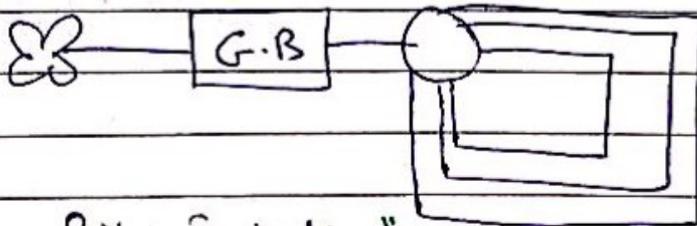

DFIG: "double fed induction generator" | control rotor frequency and speed

type 4:

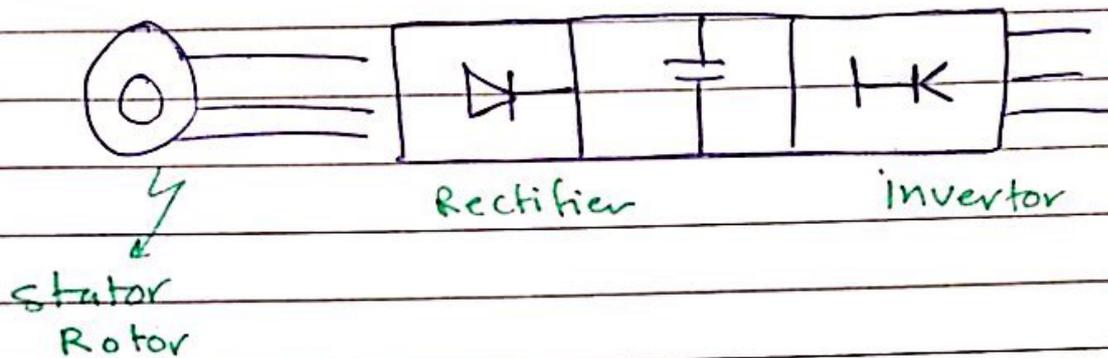

↑ discription full all types about
2-3 lines.

* classes in Motor



D ⇒ high starting torque.

Induction motor only X2 distribution.

Question #1

A 120-V 1/4-hp 60-Hz four-pole split-phase induction motor has the following impedances:

$$\begin{aligned} R_1 &= 2.00 \, \Omega & X_1 &= 2.56 \, \Omega & X_M &= 60.5 \, \Omega \\ R_2 &= 2.80 \, \Omega & X_2 &= 2.56 \, \Omega & & \end{aligned}$$

At a slip of 0.05, the motor's rotational losses are 51 W. The rotational losses may be assumed constant over the normal operating range of the motor. If the slip is 0.05, find the following quantities for this motor:

- Input power
- Air-gap power
- P_{conv}
- P_{out}
- T_d
- T_{out}
- Overall motor efficiency
- Stator power factor

Question #2

Repeat Problem 1 for a rotor slip of 0.025.

Question #3

Suppose that the motor in Problem 1 is started and the auxiliary winding fails open while the rotor is accelerating through 400 r/min. How much induced torque will the motor be able to produce on its main winding alone?

Question #4

A 220-V 1.5-hp 50-Hz six-pole capacitor-start induction motor has the following main-winding impedances:

$$\begin{aligned} R_1 &= 1.30 \, \Omega & X_1 &= 2.01 \, \Omega & X_M &= 105 \, \Omega \\ R_2 &= 1.73 \, \Omega & X_2 &= 2.01 \, \Omega & & \end{aligned}$$

At a slip of 0.05, the motor's rotational losses are 291 W. The rotational losses may be assumed constant over the normal operating range of the motor. Find the following quantities for this motor at 5 percent slip:

- Stator current
- Stator power factor
- P_{in}
- P_g
- P_d
- P_{out}
- T_d
- T_{out}
- η

Question #5

Find the induced torque in the motor in Problem 9-5 if it is operating at 5 percent slip and its terminal voltage is (a) 190 V, (b) 208 V, (c) 230 V.

Question #6

What type of motor would you select to perform each of the following jobs? Why?

- (a) Vacuum cleaner
- (b) Refrigerator
- (c) Air conditioner compressor
- (d) Air conditioner fan
- (e) Variable-speed sewing machine
- (f) Clock
- (g) Electric drill

SOLUTION

- (a) *Universal motor*—for its high torque
- (b) *Capacitor start* or *Capacitor start and run*—For its high starting torque and relatively constant speed at a wide variety of loads
- (c) Same as (b) above
- (d) *Split-phase*—Fans are low-starting-torque applications, and a split-phase motor is appropriate
- (e) *Universal Motor*—Direction and speed are easy to control with solid-state drives
- (f) *Hysteresis motor*—for its easy starting and operation at n_{sync} . A reluctance motor would also do nicely.
- (g) *Universal Motor*—for easy speed control with solid-state drives, plus high torque under loaded conditions.