

1st
Key


University of Jordan
Electrical Engineering Department

Student Name (Arabic):
Instrumentations and Measurements, EE 0903341
Date: 14/03/2017

Student I.D.:
Second Term 2016/2017
Time: 1 hour

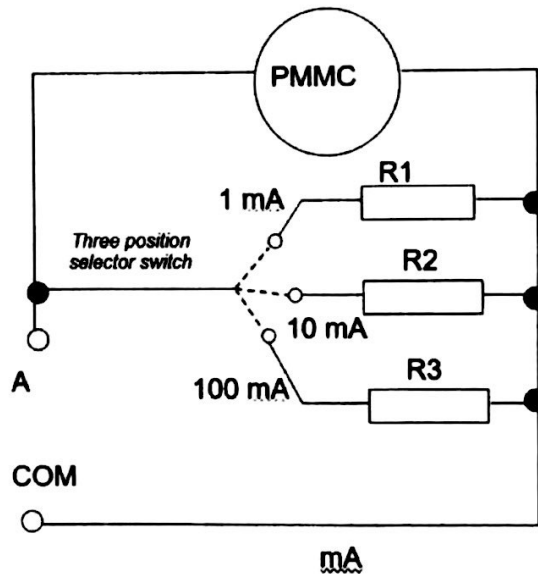Problem 1: [3 marks]

A PMMC with a full-scale deflection of $50 \mu\text{A}$ and an internal resistance of 2400Ω and a 3-way rotary selector switch are used to build an analogue ammeter that can measure DC current in 3 ranges. The three ranges have full-scale deflections of 1 mA , 10 mA , and 100 mA . Find the values of the three resistors R_1 , R_2 , and R_3 .




$$\downarrow R_1 = \frac{50 \mu\text{A} (2400)}{1 \text{ mA} - 50 \mu\text{A}} = 1263 \Omega$$

$$\downarrow R_2 = \frac{50 \mu (2400)}{10 \text{ m} - 50 \mu} = 12.06 \Omega$$

$$\downarrow R_3 = \frac{50 \mu (2400)}{100 \text{ m} - 50 \mu} = 1.20 \Omega$$

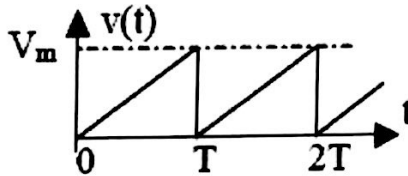Problem 3: [4 marks]

A signal generator with 500Ω internal resistance is used to produce a saw tooth signal. The output of the generator is presented in the figure below. A moving coil voltmeter with internal resistance of $10 \text{ k}\Omega$ is used to measure the RMS of the generator output. The voltmeter uses a full wave rectifier and it is calibrated for sinusoidal waveforms. Calculate the total error in the rms measurement?



$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} = \sqrt{\frac{1}{T} \int_0^T \left(\frac{V_m}{T}\right)^2 t^2 dt}$$

$$\downarrow V_{rms} = \sqrt{\frac{V_m^2}{T^3} \frac{T^3}{3}} = \boxed{\frac{V_m}{\sqrt{3}}}$$

$$V_{avg} = \frac{1}{T} \int_0^T \frac{V_m}{T} t dt = \boxed{\frac{V_m}{2}}$$

$$\downarrow \text{AC signal} \Rightarrow V_{rms} = \frac{V_m}{\sqrt{2}} \quad \int_0^T V_m \sin \omega t dt = \frac{2V_m}{\pi}$$
$$V_{avg} = \frac{1}{T} \int_0^T V_m \sin \omega t dt = \frac{2V_m}{\pi}$$

$$\text{Factor} \Rightarrow \frac{2V_m}{\pi} k = \frac{V_m}{\sqrt{2}}$$


$$\boxed{k = \frac{\pi}{2\sqrt{2}} = 1.11}$$

$$V_o = \frac{V_m}{2} (1.11) = 0.555 V_m$$

$$\text{error} = \frac{\frac{V_m}{\sqrt{2}} - 0.555 V_m}{\frac{V_m}{\sqrt{2}}} = \underline{\underline{5\%}} \quad \downarrow$$

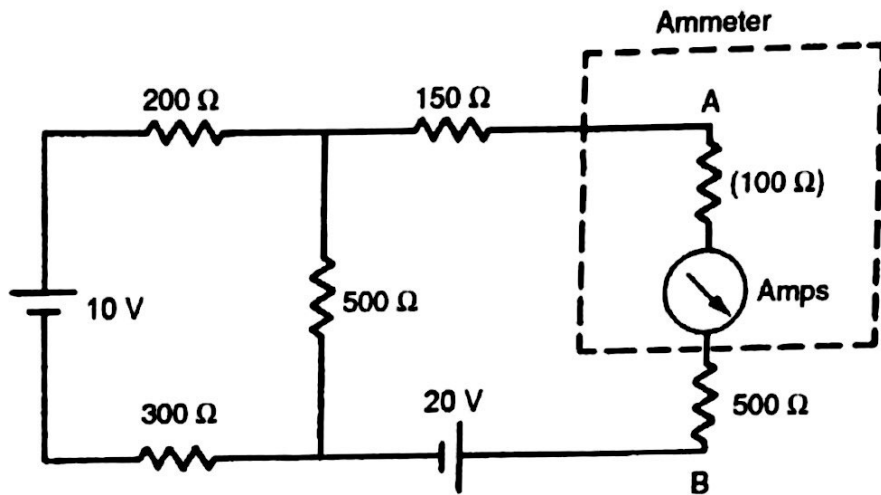Problem 2: [4 marks]

In the circuit shown in the following figure, the current flowing between A and B is measured by an ammeter whose internal resistance is 100Ω . What is the measurement error (in %) caused by the internal resistance of the ammeter?



$$R_{th} = (200 + 300) \parallel 500 + 150 \Rightarrow 250 + 150 \Rightarrow$$

$$R_{th} = 400\Omega$$

$$V_{th} = \frac{(10)(500)}{1000} - 20 = -15V$$

$$I_{act} = \frac{-15}{400 + 500} = -0.0167A$$


$$I_{meas} = \frac{-15}{400 + 500 + 100} = -0.015A$$

$$\% \text{ error} = \frac{-0.015 \pm 0.0167}{-0.0167} = [-10\%]$$

$$= 10\%$$

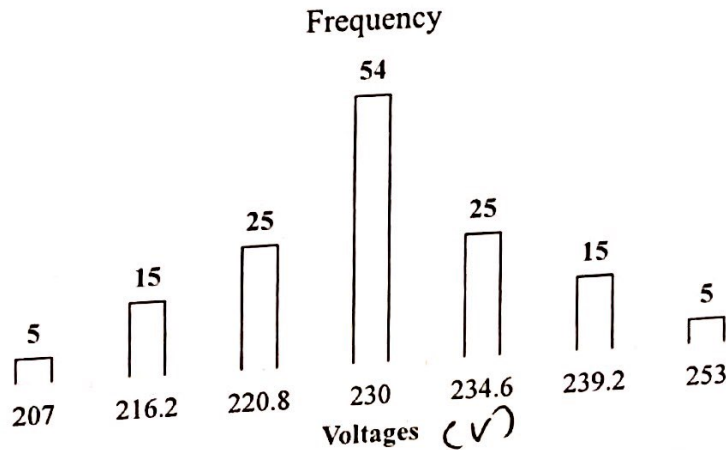Problem 5 [4 marks]: ABET

To understand the voltage variations at a house in winter season, voltage measurement instrument is used to collect voltages for one day. The voltage is recorded each 10 minutes. The statistical distribution of the results is shown in the figure below. By considering a confidence level of 95%, express the value of the voltage during winter season?



$$\bar{X} = 230 \left(\frac{54}{144} \right) + 234.6 \left(\frac{25}{144} \right) + 239.2 \left(\frac{15}{144} \right) + 253 \left(\frac{5}{144} \right) + 207 \left(\frac{5}{144} \right) + 216.2 \left(\frac{15}{144} \right) + 220.8 \left(\frac{25}{144} \right) = \boxed{228.72 \text{ V}}$$

$$\sigma^2 = E[(x - \bar{x})^2] = \sum P_i (x_i - \bar{x})^2 = 82.125$$

$$\sigma = \boxed{9.06}$$

$$\alpha = \frac{\sigma}{\sqrt{n}} = \frac{9.09}{\sqrt{144}} = 0.755$$

$$X^* = 228.72 \pm 1.96 (0.755)$$

$$227.24 \leq X \leq 230.2$$

Problem 4: [5 marks]

A digital meter has 3 ½ digital display and an accuracy of $\pm 1.2\%$ reading ± 3 counts is used to measure DC current. Its specification is presented in the Table below.

DC current range	Accuracy
200 μ A	$\pm 1.2\%$ reading ± 3 counts
2 mA	
20 mA	
200mA	

(a) What is the accuracy of the meter when it gives a reading of 1.234mA?

\downarrow

$$\pm 1.234 \times 1.2\% \pm 3 \times 0.001 \text{ mA}$$
$$\pm 0.014808 \pm 0.003 \text{ mA}$$

(b) The meter shows a dc measurement of 1.711mA using the 2mA range. What is the error?

\downarrow

$$1.2\% (1.711) \pm 3 \times 0.1 \text{ mA} = \pm 2.95\%$$

(c) The 20 mA range is used to measure the same current as considered in part (b). What is the resulting increase in the error?

\downarrow

$$1.2\% (1.711 \text{ mA}) \pm 3 \times 0.1 \text{ mA} = 0.320532$$
$$\text{error} = 18.7\%$$

(d) This meter and a perfect resistor of 1 Ω (i.e. no error) are used as a power meter based on the calculation, $P=I^2R$. What is the maximum likely error in the power value using the 200 mA range?

\downarrow

$$e = \pm \sqrt{\left(\frac{18.7}{100}\right)^2 + (18.7)^2} = 26.45\%$$


17/8

Problem 6 [3, 5 marks]:

Two sinusoidal voltages are applied to an oscilloscope in dual-trace operation. The vertical settings are 10mV/cm and 0.5V/cm for CH-1 and CH-2 respectively. The time base setting is 10ms/cm CH-1 and CH-2

- (i) For the dual trace shown, find:
 (a) The peak to peak values for voltages in CH-1 and CH-2
 (b) The frequency of both signals
 (c) The phase shift between V_1 (CH-1) and V_2 (CH-2). Does V_1 leads or lags V_2 ?

3

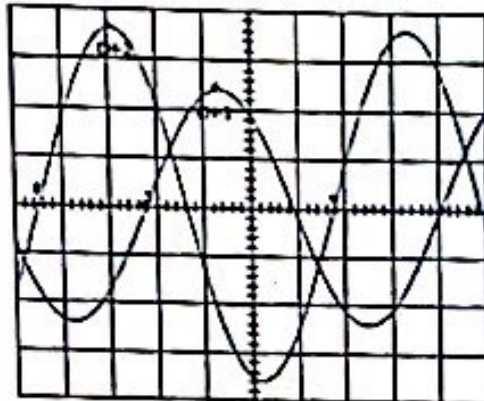

$5 \times 0.5 = 0.7$
 $0.5 \times 1 = 0.5$

~~V_1 lag V_2~~

$1 + 0.9 = 0.4$
 1.2

$V_{CH1} = 5 \times (10\text{mV})$
 P-P
 $= 50\text{mV}$

$V_{CH2} = 7.2\text{cm} \times (0.5\text{V/cm})$
 P-P
 $= 3.6\text{V}$

$f = \frac{1}{T}$
 $T_{CH1} = 6.2\text{cm} \times (10\text{ms/cm})$
 $= 62\text{ms}$

$T_{CH2} = 6.2\text{cm} \times (10\text{ms/cm})$
 $= 62\text{ms}$

$f_{CH1} = 16.12\text{Hz}$

$f_{CH2} = 16.12\text{Hz}$

$\theta = 2.3 \times \frac{360}{6.2} = 133.5^\circ$

V_1 lag V_2

$$V_2 = 1.76 \sin(\omega t + 0.33)$$

1/5

(iii) If the oscilloscope is switched to XY mode of operation, V_1 is connected to the X input with setting (10mV/cm) and V_2 is connected to the Y input with setting (0.5V/cm). Draw the resulting graph, and mark on the graph all the corresponding values (e.g., minimum, maximum and zero crossing points)

maximum value

$$V_{max} V_1 = 25 \text{ mV}$$

$$V_{max} V_2 = 1.84 \text{ V}$$

~~Handwritten scribbles~~

$$\ominus V_0 = 19 \text{ mV}$$

$$V_0 = 1.7 \text{ V}$$



minimum value

$$V_{min} V_1 = -25 \text{ mV}$$

$$V_{min} V_2 = 1.84 \text{ V}$$

$$\ominus V_0 = -19 \text{ mV}$$

$$V_0 = 1.7 \text{ V}$$

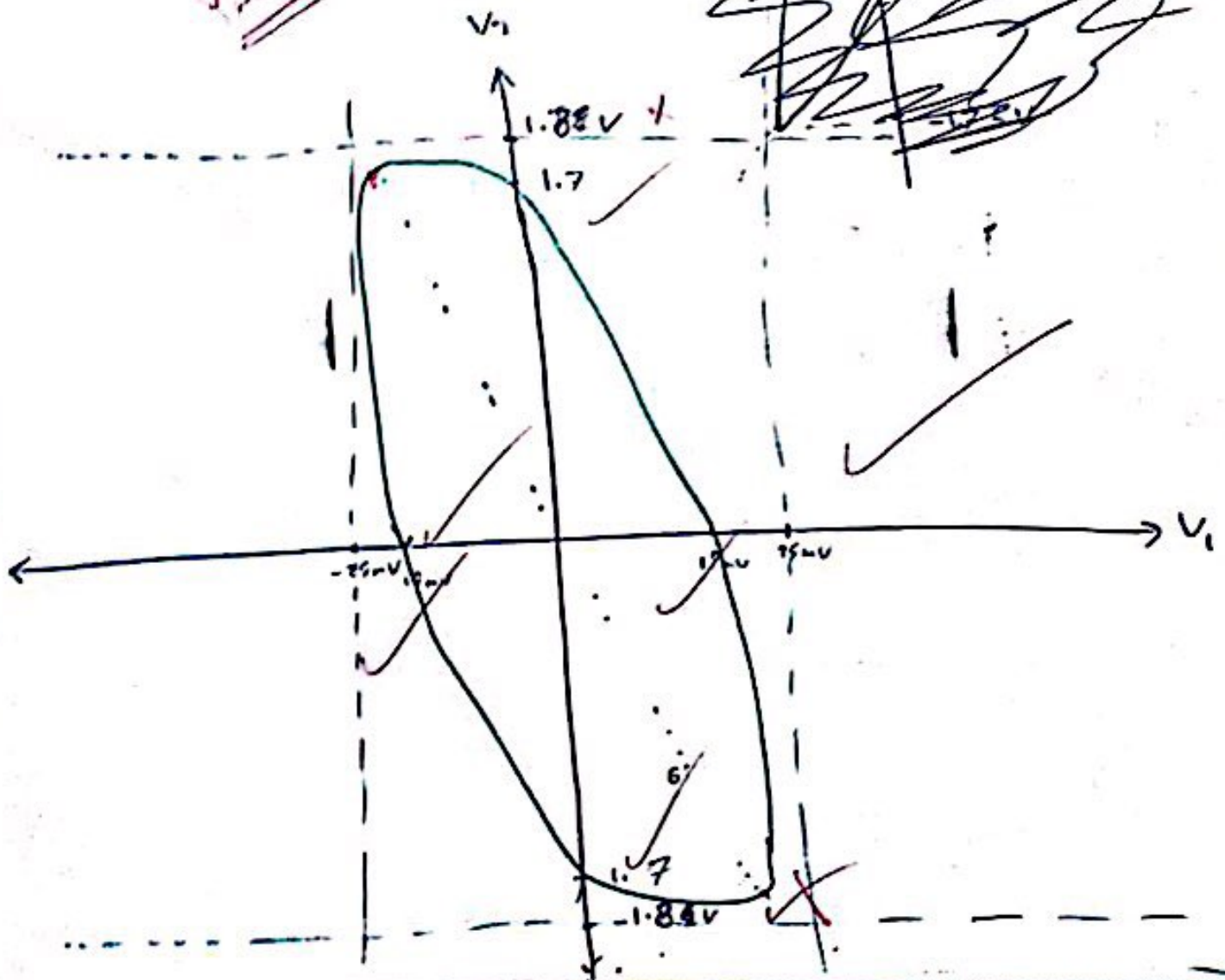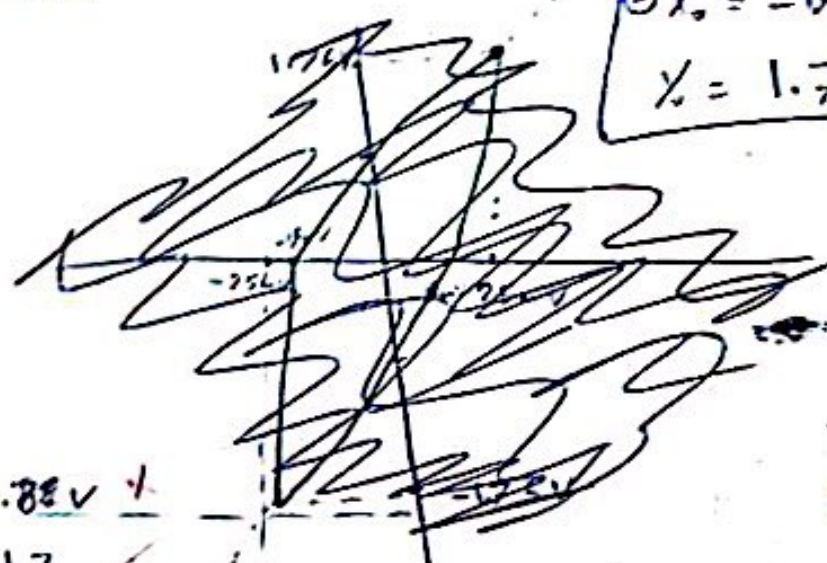


26/30

University of Jordan
Electrical Engineering Department

Student Name (Arabic): زيد الدين
Electrical measurements and instruments, EE 0933341
Date: 30/11/2016

Student I.D: 014 2208
First Term 2016/2017
Time: 90minutes

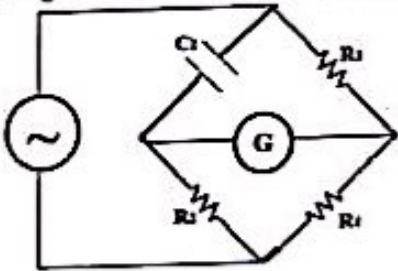Problem 1 [2 marks]:
Explain why the following bridge circuit can never achieve balance condition



$$\frac{R_2}{X_1} = \frac{R_4}{R_3}$$

$$\frac{R_2}{\omega C_1} = \frac{R_4}{R_3} \Rightarrow \omega C_1 R_2 R_3 \neq R_4$$

Real + Imaginary impossible

Because the voltage drop across C_1 is not equal the voltage drop in R_3 .

the impedance in a branch is imaginary and that's not imaginary part in another side

Problem 2 [3, 2 marks]:

(i) In the context of Cathode Ray Tube (CRT) oscilloscope, explain the purposes of the following components: Delay line, Sweep circuit, HV supply

Delay line → to synchronize the V plates and H plates working and this is by delay the V signal at the sweep time processing

Sweep circuit → matching the start point of H signal to H plates and generate the sawtooth

HV supply: to supply

(ii) List two main differences between analog and digital oscilloscope


	analog	digital
1-	show the signal instantly at now time	save the signal and show it in any time.
2-	in low freq the spot scrub has slow and can trace this to human eye	in low freq the plot is continuous and fast.

The CRT to generate the Beam and, luminance, and Focus, and this process takes a HV and H power to heat the plate.


4

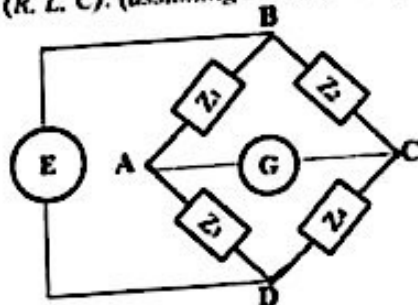Problem 4 [5 marks]:

An AC bridge shown below is balanced at 1000 Hz and has the following constants: AB: 0.2 μ F; BC: 500 Ω (pure resistance); DA: $R = 300 \Omega$ in parallel with $C = 0.1 \mu$ F; CD: unknown. Find the Z value connected through the arm CD and determine the corresponding element(s) (R, L, C). (assuming series circuit).



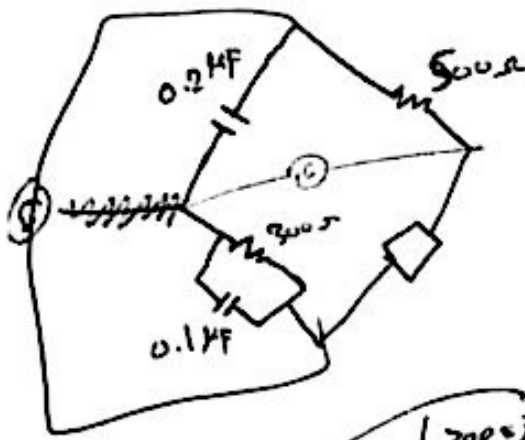$f = 1000 \text{ Hz}$
 $\omega = 2\pi f = 6283.18$



$$\frac{Z_3}{Z_1} = \frac{Z_4}{Z_2}$$

$$Z_3 Z_2 = Z_4 Z_1$$

$$\left(\frac{300 \parallel \frac{1}{j\omega 0.1}}{300 + \frac{1}{j\omega 0.1}} \right) 500 \Omega = Z_4$$

$$-1591.55j$$


$$\left(\frac{1}{j\omega 0.2} \right)$$

$$-795.77j$$

$$X_L = j\omega L$$

$$Z_4 = 34.3 + 182.029j$$
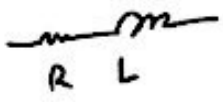
$$Z_4 \Rightarrow R = 34.3 \Omega \quad L = 28.9 \text{ mH}$$



$P = 994.718 \text{ kHz}$

$\omega = 2\pi f$


$f = 0.994 \text{ MHz}$

Problem 5 [2, 4 marks]:

The arms of a four-arm bridge ABCD supplied with a sinusoidal source have the following values: AB: 200Ω resistances in parallel with $1\mu\text{F}$, BC: 400Ω resistance, CD: 1000Ω resistance, and DA: resistance R in series with capacitance $2\mu\text{F}$.

2
3

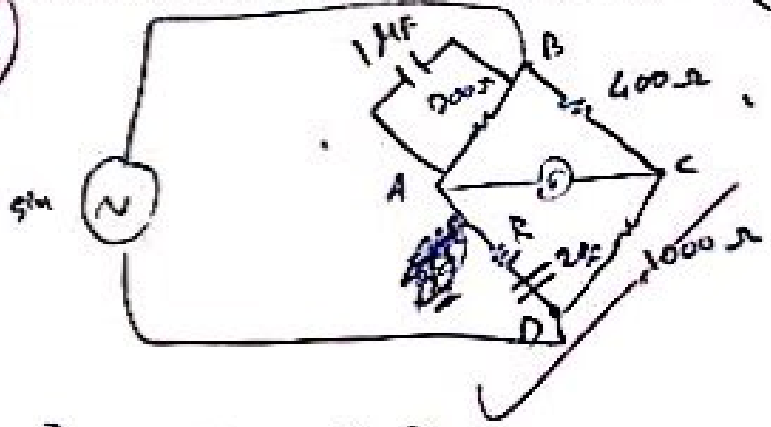- (i) Draw the corresponding bridge and provide its type
- (ii) Find the value of resistance R and the source frequency (under null condition)



Wheat Bridge
for calculate the
freq.

$\frac{Z_1}{Z_2} = \frac{Z_4}{Z_3}$ $Z_3 = \frac{Z_1 Z_2}{Z_2}$

$Z_{AD} = \frac{(1000) \left(\frac{200 + \frac{1}{j\omega 1\mu}}{200 + \frac{1}{j\omega 1\mu}} \right)}{400}$

$f = \frac{1}{2\pi \sqrt{C_1 C_2 R_1 R_2}}$

$R + \frac{1}{j\omega 2\mu} = 2.5 \left(\frac{\frac{200}{j\omega 1\mu}}{200 + \frac{1}{j\omega 1\mu}} \right)$

$R - j \frac{1}{\omega 2\mu} = 2.5 \left(\frac{200}{200(j\omega 1\mu) + 1} \right)$

$R - j \frac{1}{\omega 2\mu} = \frac{500}{j\omega 200\mu + 1}$

$R j\omega 200\mu + R + \frac{\omega 200\mu^2}{\omega 2\mu} - j \frac{1}{\omega 2\mu} = 500 + j0$

Im Real Im Real Im

$R + \frac{200}{2} = 500$

$R = 400\Omega$

$R j\omega 200\mu = j \frac{1}{\omega 2\mu}$


$\omega = \frac{1}{(2\mu)(200\mu) R}$

$\omega = 6.25 \text{ Mrad}$

$f = 994.718 \text{ kHz}$

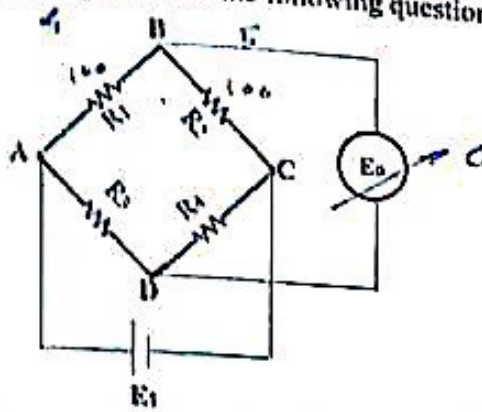Problem 3 [2, 2 marks]

For the following Wheatstone bridge, answer the following questions:



- (i) Determine the value of \$E_1\$, given that all resistances are \$100\Omega\$ and the power consumption through \$R_1\$ is \$0.25W\$ (neglect meter resistance)

$$P = VI = I^2 R \quad \text{at } R_1 \rightarrow V = 5V$$

$$0.25 = \frac{V^2}{R}$$

$$I = 0.05A$$

$$E_1 = 10V$$

- (ii) Find \$E_0\$, given that \$E_1 = 5V\$ and the resistor values of the Wheatstone bridge are: \$R_1 = 200\Omega\$, \$R_2 = 100\Omega\$, \$R_3 = 500\Omega\$, and \$R_4 = 600\Omega\$ (neglect meter resistance)


$$V_{DE} = E_1 \left(\frac{R_3}{R_3 + R_4} - \frac{R_1}{R_1 + R_2} \right) = 0.606V$$

if deflection = $1 \text{ mA} / R_m = 10 \Omega$


Design voltmeter to measure

- ① Range (0-10)V
- ② Range (0-50)V

Find R_1, R_2

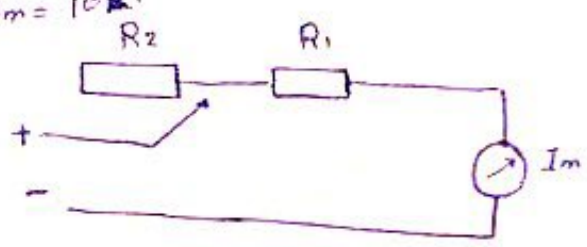

⑤

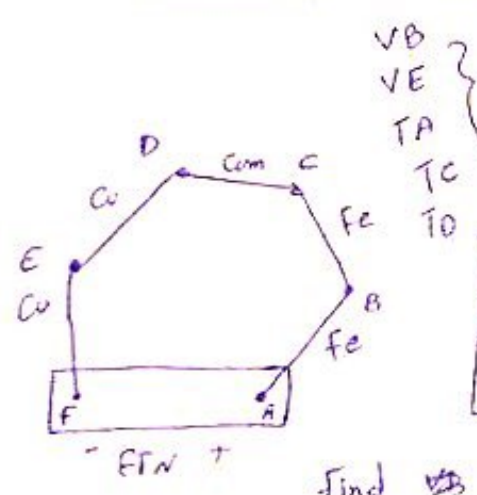

V_B, V_E, T_A, T_C, T_D } given
given table

T	
Cu	
Fe	

Find other quantities and ETN

⑧

if we have f of soil safety factor, I_{fault} correction factor,


Find V_{touch} and V_{step}

and $R_g \rightarrow$ GRP $> V_{\text{step, touch}}$

- f
- c
- I_f
- SF

⑧

معادلات حسابية
بالقوس والمقادير

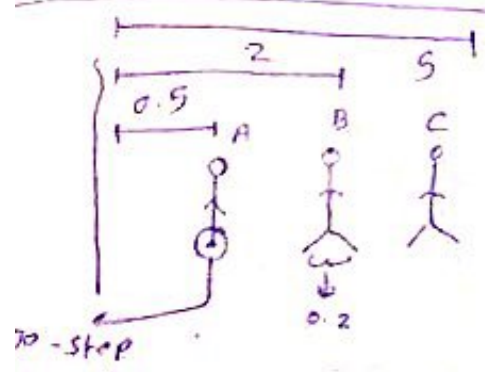

find V_A, V_B, V_C
 V_{step} :

$$V_A = 55 \left(\frac{1}{X_1} + \frac{1}{X_1 + 0.2} \right)$$

$$V_{XX} = \frac{55}{X}$$

Voltage curve

التيار في كل نقطة من النقاط


في سعة ال كان بدوها ترسم رسم graph كيف ما

6

Common-mode

اشتر صيد تكتبي

المعادلة و صيد

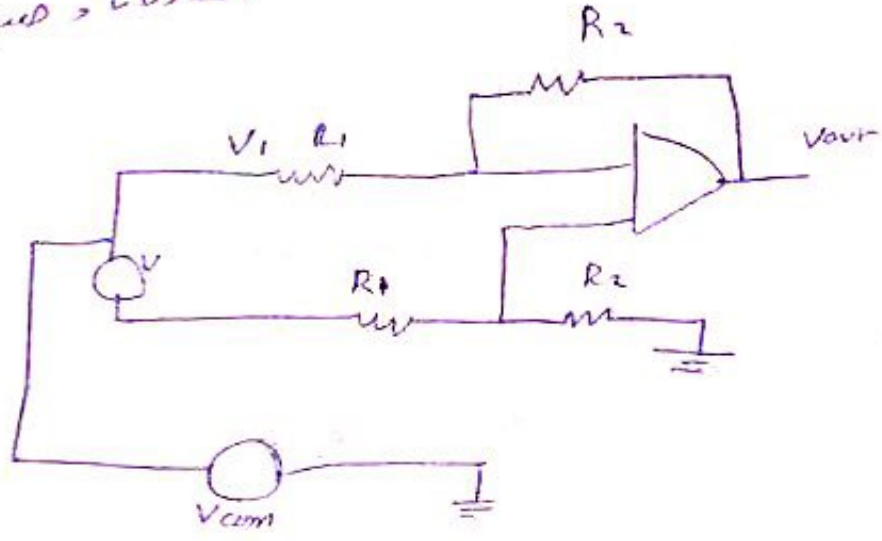

$$V_o = (V_1 - V_{com} - V_2 + V_{com}) \frac{R_2}{R_1}$$

Without Common

$$V_o = (V_1 - V_2) \frac{R_2}{R_1}$$

اشتر صيد تكتبي
صيد تكتبي

- ⊖ Multi range Ammeter → Add shunt R
- ⊖ " " Voltmeter → " Series R
- ⊖ Horizontal axis in CRO is ~~~~~
- ⊖ Principle of inductive transducers
① ②
- ⊖ Application for pmmc.
- ⊖ disadvantage of pmmc

- ⊖ Transducer definition
- ⊖ Block diagrams for linear and switched (section power supply)
- ⊖ Transformer type in linear and switched
- ⊖ First material
200 Ω ± 0.1 / 300 Ω ± 0.2 / 150 Ω ± 0.4 } → في كان
اشتر صيد تكتبي
اشتر صيد تكتبي
- ⊖ find ε of meas. eqv R if there is connected in series
- ⊖ ~~old battery and new battery~~
- ⊖ example of rechargeable and rechargeable battery