

~~write~~ power unit

Q) 1 :

A) Define the following terms :-

- 1) Skin effect :
- 2) Limiting error

B) what is methods that used to measure the internal resistance of ammeter ?? Draw the circuit's ?? explain

C) Sketch shunt type ohmmeter circuit and series type ohmmeter circuit then explain??


Q) 2 : ~~Design~~

using the Ayrton shunt method. design a multi-range Ammeter ~~with~~ knowing that

- $R_m = 100 \Omega$
- the full scale deflection of the pmmc = $50 \mu A$
- \rightarrow the needed ranges :-
(0-1mA), (0-10mA), (0-50mA), (0-100mA)

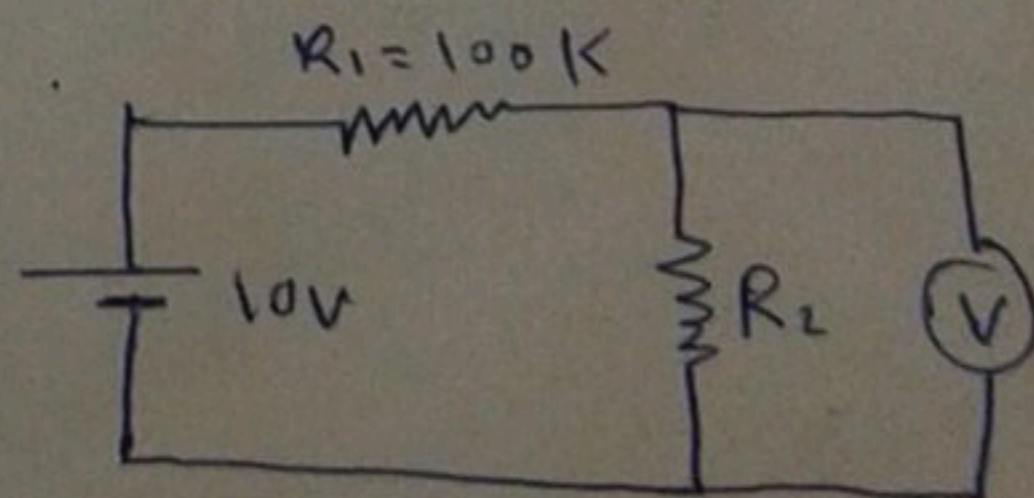Q3) : consider the following circuit with the following information Determine the sensitivity of the voltmeter (2)

* the voltage on the resistance R_2 is measured by voltmeter (1) with sensitivity of $5 K\Omega/V$ the reading was $1.49V$ with range (0-10V)



* the voltmeter (2) is inserted instead of voltmeter (1) the reading was $1.75V$ with (0-5) Range

الكلية

المستوى

المادة

القسم

التاريخ

العلامات

19
20

a) ~~(1)~~)


1) Skin Effect : one type of instrument ~~that~~ influence and ~~some~~ sometimes it's very large and maybe erotic and will change the reading of measured value to improve it we must adjust device to regular adjustment

2) Limiting error : the ammeter must be guaranteed to be within certain range of errors called limiting errors and it's equal accuracy multiply full scale deflection of ammeter

$$\text{Limiting error} = \text{Full scale} \times \text{Accuracy}$$

b)

1) half scale method

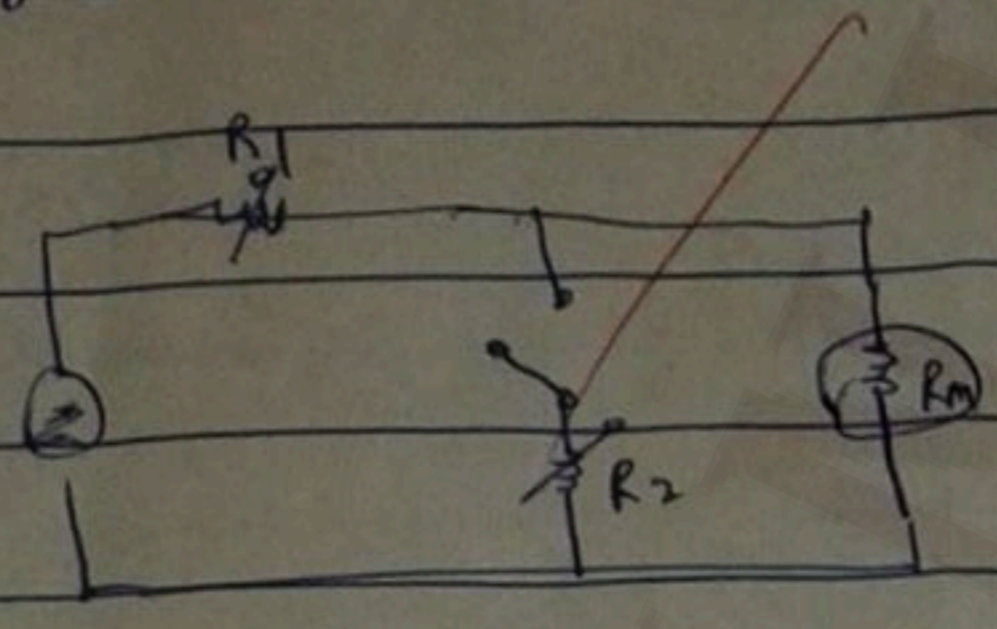


2) half scale method

First we adjust R_1 until ammeter give Full scale deflection (I_F) then we close the switch and adjust R_2 to give half value of Full scale then the value of R_m will be equal value of R_2


$$R_m = R_2$$

2) current-voltage method

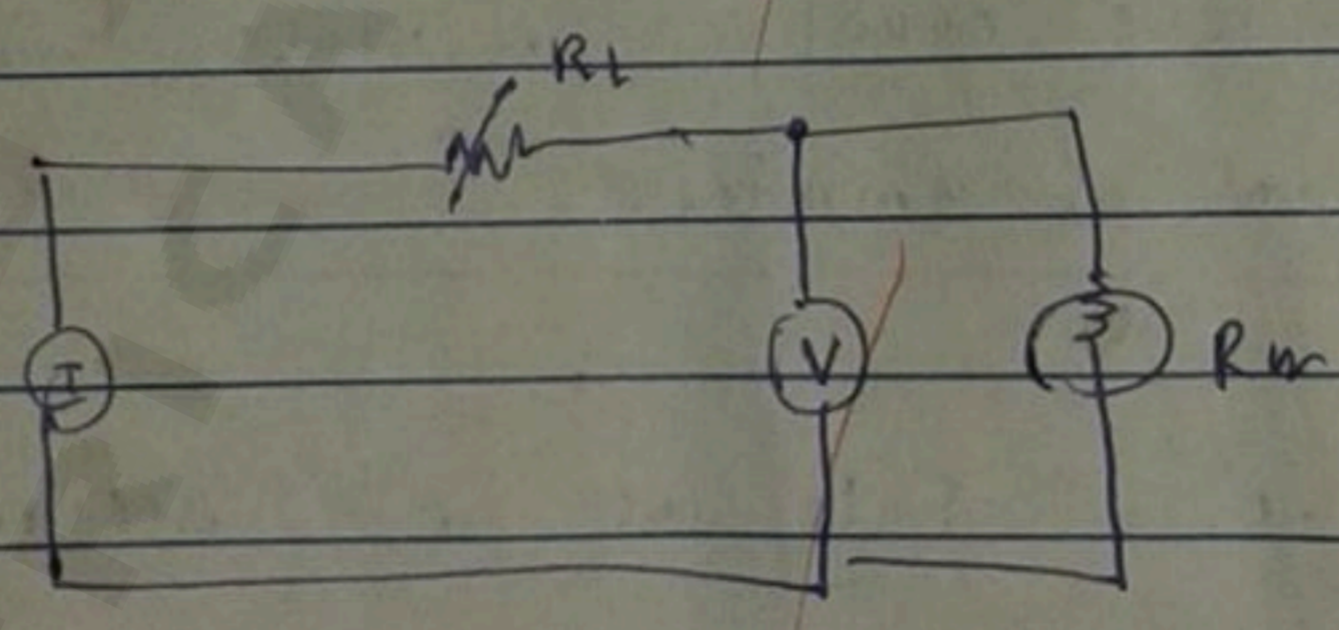

First we adjust R_1 to give full scale deflection until ammeter give Full scale deflection then we calculate R_m by using following method
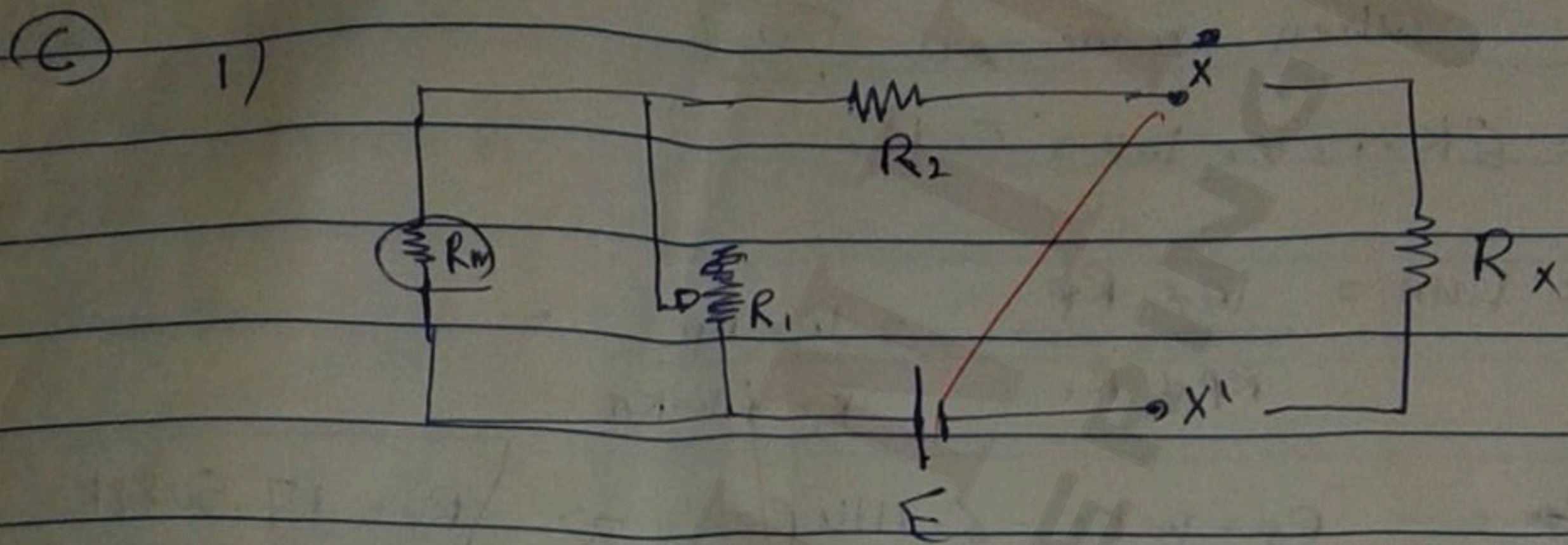
$$R_m = \frac{V}{I_{Fs}} \rightarrow \text{reading of voltmeter}$$




2) Shunt type contain from R_1 which represent changing resistor (shunt) to select suitable scale we adjacent R_1 to give demand value R_2 it is series resistor called multiplier.

(Rm) ~~represent~~ NOTE that R_1 connect in series with R_m and R_1 connect in series with R_x parallel. Keep in mind R_x : represents unknown resistor. The different between series type and shunt type ohmmeter is:

series-type	we	in	measure	high	resistor
shunt-type	"	"	"	low	resistor

QUESTION (2)

when switch at position (a)

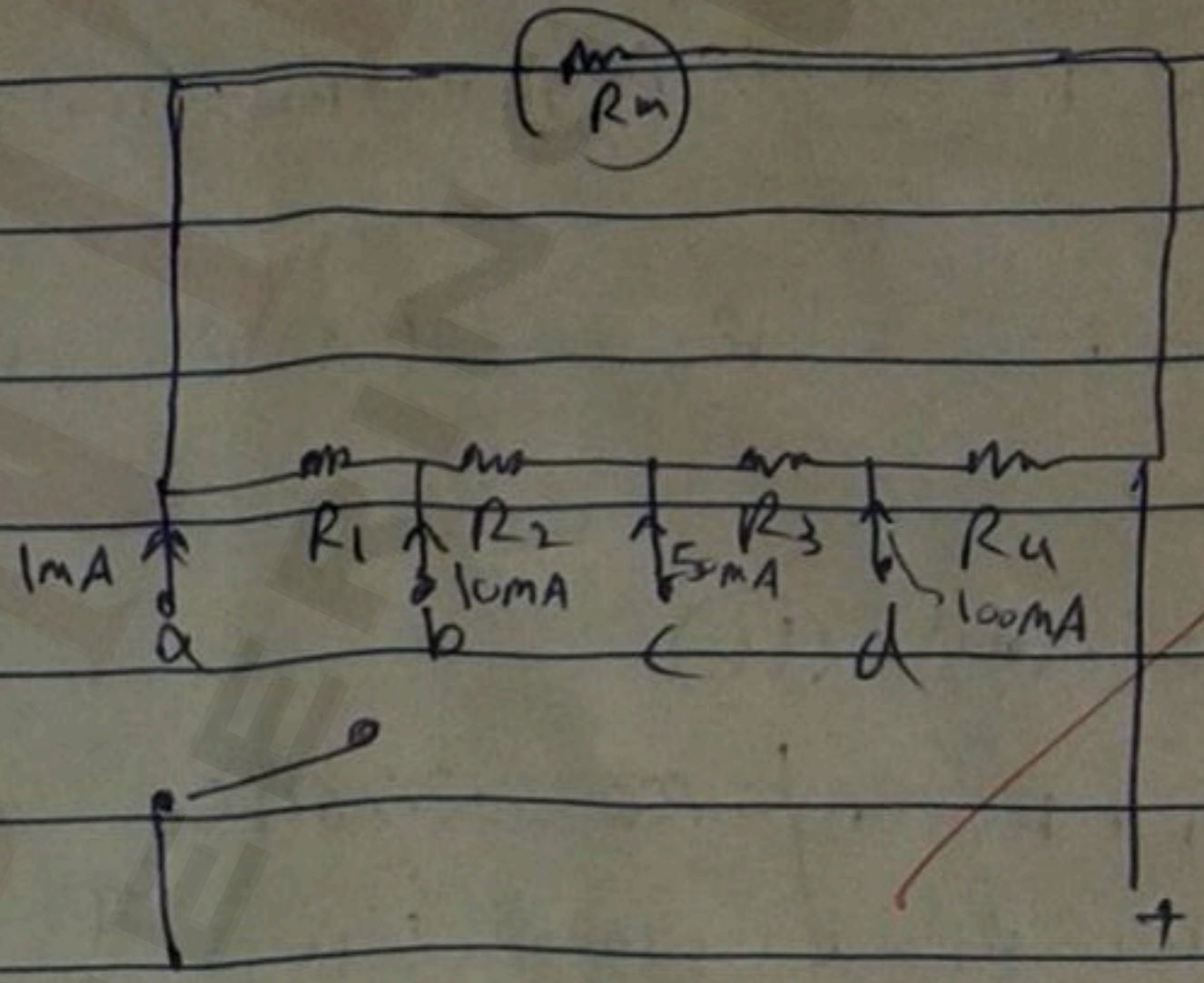

$$R_m = R_1$$

$$R_1 + R_2 + R_3 + R_4 = \frac{R_m}{\frac{I_T}{I_{R_1}} - 1}$$

$$R_1 + R_2 + R_3 + R_4 = \frac{100}{\frac{50mA}{1mA} - 1} = \frac{100}{49}$$

$$19R_1 + 19R_2 + 19R_3 + 19R_4 = 100$$

$$R_1 + R_2 + R_3 + R_4 = 5.26315 \quad \text{--- (1)}$$

when switch @ position (b)

$$R_2 + R_3 + R_4 = \frac{R_m + R_1}{199} = \frac{R_1 + R_m}{199}$$

$$-R_1 + 199R_2 + 199R_3 + 199R_4 = 100 \quad \text{--- (2)}$$

when switch @ position (c)

$$R_3 + R_4 = \frac{R_1 + R_2 + R_m}{999} = \frac{R_1 + R_2 + R_m}{999}$$

$$-R_1 - R_2 + 999R_3 + 999R_4 = 100 \quad \text{--- (3)}$$

$$R_4 = \frac{R_1 + R_2 + R_3 + R_m}{1000} = \frac{R_1 + R_2 + R_3 + R_m}{1000}$$

$$-R_1 - R_2 - R_3 + 1000R_4 = 100 \quad \text{--- (4)}$$

$$R_1 + R_2 + R_3 + R_4 = 5.26315 \quad (1)$$

$$-R_1 + 199R_2 + 199R_3 + 199R_4 = 100 \quad (2)$$

$$-R_1 - R_2 + 999R_3 + 999R_4 = 100 \quad (3)$$

$$-R_1 - R_2 - R_3 + 1999R_4 = 100 \quad (4)$$

(1) and (4)

$$R_1 + R_2 + R_3 + R_4 = 5.26315$$

$$-R_1 - R_2 - R_3 + 1999R_4 = 100 \quad +$$

$$2000R_4 = 105.26315$$

$$R_4 = 0.052631575$$

(1) and (3)

$$-R_1 - R_2 + 999R_3 + 999R_4 = 100$$

$$R_1 + R_2 + R_3 + R_4 = 5.26312$$

$$1000R_3 + 1000R_4 = 105.26312$$

$$R_3 = 0.05263152$$

(1) and (2)

$$R_1 + R_2 + R_3 + R_4 = 5.26315$$

$$-R_1 + 199R_2 + 199R_3 + 199R_4 = 100$$

$$R_2 = 105.2631 - 200 \times (0.05263152) - 200 \times (0.052631)$$

$$R_2 = 2.421$$

$$R_1 = 1.73683451$$

Q13 When connected V_1

$$R_v = 5K \Omega / V \times 10V = 50K \Omega$$

$$V = 1.49 = \frac{10 \times R_p}{R_p + R_1} = \frac{10 \times R_p}{R_p + 100K \Omega}$$

$$R_p = R_p + 100K \Omega - 6.7114 R_p \Rightarrow R_2 = 17.5088K$$

$$R_p = \frac{R_v \times R_2}{R_v + R_2} = 17.5088K \quad - \quad \frac{50K \Omega \times R_2}{17.5088K} = 50K + R_2$$

$$R_2 = 26.9439K \Omega$$

When connected V_2

$$1.75 = \frac{10 \times R_p}{R_p + R_1} = \frac{10 R_p}{R_p + 100K}$$

$$R_p = 21.2121K$$

$$R_p = \frac{R_2 \times R_v}{R_2 + R_v} = \frac{26.9439K \times R_v}{26.9439K + R_v} = 21.2121K$$

$$R_v = 99.70997$$

$$S = \text{sensitivity} = \frac{R_{\text{Total}}}{V_{FS}} = \frac{99.70997}{5} = 19.94199$$

$\Lambda \Lambda$