



Name (in Arabic):

No.:

Section:

Instructor:

12.5
30

** Solve the following questions and choose the one best answer. Fill in your answers in the Answer Table.


1	2	3	4	5	6	7	8	9	10	11	12
E	B	A	A	D	E	C	A	C	C	C	D

5

* Useful Constants: $k_e = 9 \times 10^9 \text{ N.m}^2/\text{C}^2$, $m_e = 9.11 \times 10^{-31} \text{ kg}$, $e = 1.6 \times 10^{-19} \text{ C}$, $\mu_0 = 4\pi \times 10^{-7} \text{ T.m/A}$, $1 \text{ eV} = 1.6 \times 10^{-19} \text{ J}$


1. An electric device delivers a current of 5.0 A to a circuit. How many electrons flow through this circuit in 5 s ?
A) 30 B) 50 C) 25 D) 3.1×10^{20} E) 1.6×10^{20}

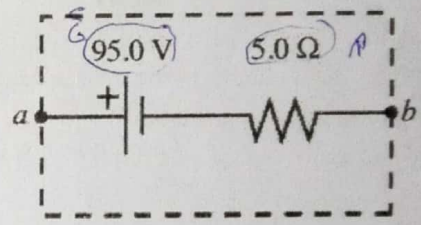2. The emf and the internal resistance of a battery are as shown in the figure. If a current of 3.8 A is drawn from the battery when a resistor R is connected across the terminals ab of the battery, what is the power dissipated by the internal resistor (i.e the 5Ω)?




A) 72 W B) 361 W C) 62 W
D) 530 W E) 289 W

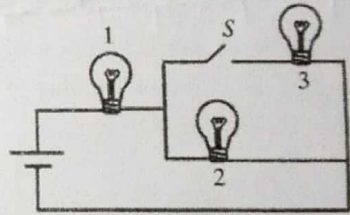3. The figure shows three identical light bulbs connected to a battery having a constant voltage across its terminals. When the switch S is closed, the brightness of light bulb 1 will:



A) remain the same as before the switch is closed.
B) decrease.
C) increase.

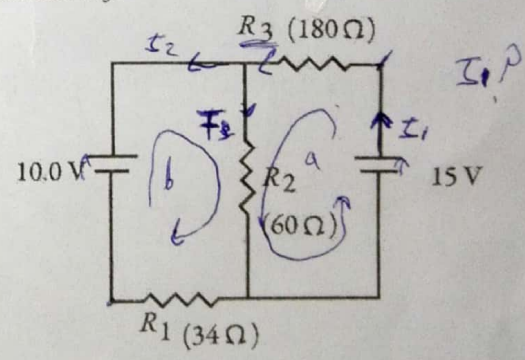4. For the circuit shown in the figure, what is the current through resistor R_3 ?




A) 0.043 A
B) 1.5 A
C) 0.028 A
D) 0.068 A
E) 0.086 A

5. What is the kinetic energy (in eV) of an electron that passes undeviated through perpendicular electric and magnetic fields if $E = 2.0 \text{ kV/m}$ and $B = 8.0 \text{ mT}$?
A) 0.71 eV B) 0.18 eV C) 0.32 eV D) 0.54 eV E) 1.4 eV

$v = 90$
 $E = 2$
 $B = 8$

6. For the circuit shown in the figure, the capacitors are all initially uncharged, the connecting leads have no resistance, the battery has no appreciable internal resistance, and the switch S is originally open. After the switch S has been closed for a very long time, what is the current in the $20.0\text{-}\Omega$ resistor?

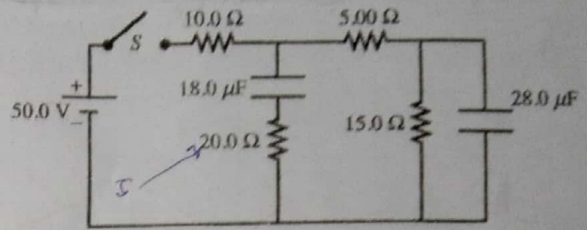- A) Zero
 B) 1.67 A
 C) 2.50 A
 D) 3.33 A
 E) 5.00 A



7. An electron moving with velocity v to the left enters a region of uniform magnetic field that points out of the paper. After the electron enters this region, it will be:

- A) deflected out of the plane of the paper. B) deflected into the plane of the paper.
 C) deflected upward. D) deflected downward. E) undeflected in its motion.

8. A circular coil of wire of 200 turns and diameter 2.0 cm carries a current of 4.0 A. It is placed in a magnetic field of 0.35 T, with the plane of the coil making an angle of 30° with the magnetic field. What is magnitude of the magnetic torque on the coil?


- A) 0.15 N.m B) 0.076 N.m C) 0.29 N.m D) 0.044 N.m E) 0.088 N.m

9. When the number of turns in a solenoid and its length are both doubled, the ratio of the magnitude of the new magnetic field inside to the magnitude of the original magnetic field inside is:

- A) 0.25 B) 0.50 C) 1 D) 2 E) 4


10. The figure shows a cross section of three parallel wires each carrying a current of 20 A. The currents in wires A and B are out of the paper, while that in wire C is into the paper. If the distance $R = 5.0$ mm, what is the magnitude of the force on a 1.0-m length of wire A?

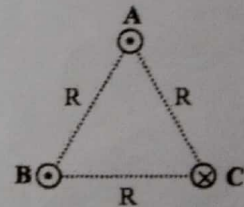- A) 23 mN B) 32 mN C) 16 mN
 D) 64 mN E) 55 mN



11. If $a = 1.0$ cm, $b = 3.0$ cm, and $I = 10$ A, what is the magnitude of the magnetic field at point P?

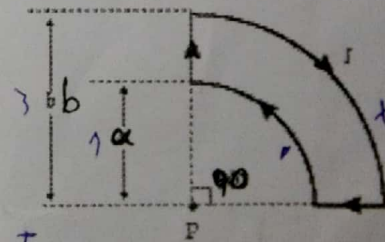- A) 0.62 mT B) 0.59 mT C) 0.35 mT
 D) 0.31 mT E) 0.10 mT



12. A long cylindrical wire (radius = 2.0 cm) carries a current of 20 A that is uniformly distributed over a cross section of the wire. What is the magnitude of the magnetic field at a point which is 1.5 cm from the axis of the wire?

- A) 0.53 mT B) 28 mT C) 0.30 mT D) 0.15 mT E) 1.9 mT

**** ALL THE BEST ****