

Student's Name: عمر عبد الرحمن علي

Student's Number: 0144364

Lecturer's Name: Dr. Ziad

Section Number:

$e = -1.6 \times 10^{-19} \text{ C}, m_e = 9.11 \times 10^{-31} \text{ kg}, g = 9.8 \text{ m/s}^2$

Q1) The quantity of charge (in Coulombs) that has passed through a surface area of 2.0 cm^2 varies with time as $q = 4t^3 + 11t + 6$ where t is in seconds. The instantaneous current (in A) through the surface at $t = 1.0 \text{ s}$

- a) 12 b) 23 c) 0 d) 17 e) 31

Q2) A light bulb is rated at 30 W when operated at 150 V . How much charge (in Coulombs) passes through this bulb in 1.0 min ?


- a) 17 b) 15 c) 12 d) 30 e) 60

Q3) A conductor of radius r , length L and resistivity ρ has resistance R . What is the new resistance if it is stretched to 2 times its original length **keeping its volume constant**?

- a) 4R b) ~~R/4~~ c) R d) 2R e) R/2


Q4) What is the rate at which thermal energy is generated in the 30Ω resistor shown?

- a) 13 W b) 27 W c) 60 d) 20 W e) 30 W

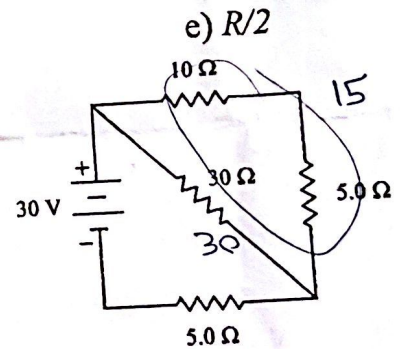


Q5) In the figure shown, if $I = 0.50 \text{ A}$ and $R = 8 \Omega$, determine ϵ (in Volt).

- a) 12 b) 24 c) 30 d) 15 V e) 16.0

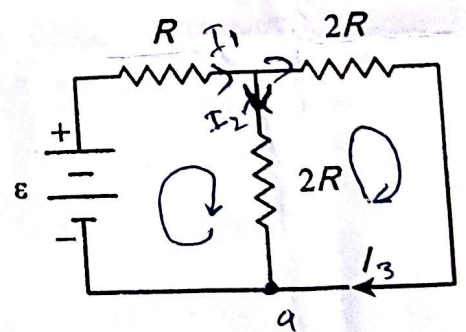

Q6) In the figure, if $I = 3.0 \text{ A}$ in the circuit segment shown, what is the potential difference $V_B - V_A$ (in volt)?


- a) +28 b) -52 c) -28 d) +52 e) +2.0

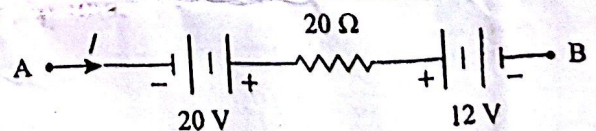

sanfoor mohandes

Q7) In the figure, if $R = 15 \Omega$, what is the equivalent resistance between points a and b

- a) 16 b) 28 c) 24
d) 20 e) 6.0

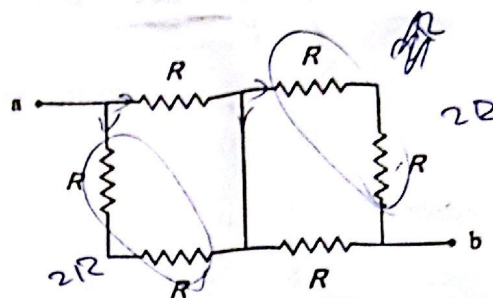

8) An RC circuit consists of uncharged $50 \mu F$ capacitor, 30 V battery and a 10Ω resistor. When the switch is closed the initial current (in A) in the circuit is


- a) 30 b) 15 c) 6.0 d) 10.0 e) 3.0

Q9) An electron has a velocity of 6×10^6 m/s in the positive x direction at a point where the magnetic field has the components, $B_x = 3$ T, $B_y = B_z = 0$. What is the magnitude of the magnetic force acting on the electron (in N)?

- a) 4.1 b) 1.6 c) 3.6 d) 0 e) 2.9

Q10) A straight wire is bent into the shape shown. Determine the net magnetic force on the wire.

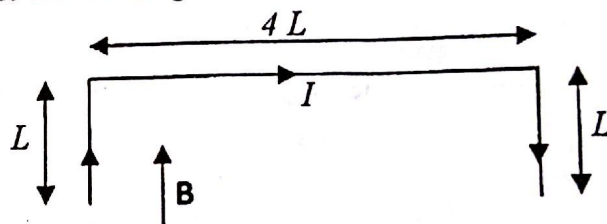- a) $2IBL$ into the page b) $2IBL$ out of the page
c) $4IBL$ out of the page d) $4IBL$ into the page
 e) zero




Q11) A circular loop (radius = 0.50 m) carries a current of 3.0 A and has unit normal vector of $(2i - j + 2k)/3$. What is the x component of the torque (in N.m) on this loop when it is placed in a uniform magnetic field of $(2i - 6j)$ T?

- a) 4.7 b) 9.4 c) 19 d) 3.1 e) 12 N

Q12) A horizontal wire (mass = 25 g, length = 40 cm) is suspended by two massless vertical wires which conduct a current $I = 4.0$ A, as shown in the figure. The horizontal wire is subjected to a magnetic field of magnitude 60 mT into the paper. What is the value of the tension (in N) in each of the vertical wires?

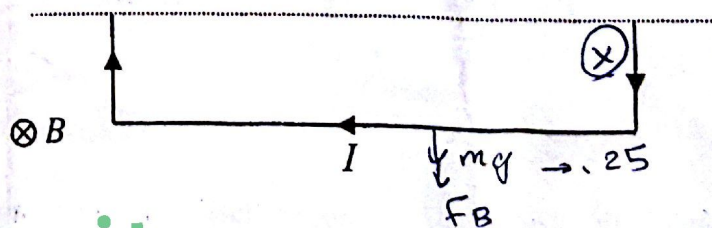- a) 0.39 b) 0.32 c) 0.13
 d) 0.08 e) 0.17



power unit

Q1	Q2	Q3	Q4	Q5	Q6	Q7	Q8	Q9	Q10	Q11	Q12
b	c	b a	a	e	b	d	e	d	c	b	e