

Name(in Arabic)

Student No.
Section



2 (12-1pm)

Programmable calculators are not allowed.
Derive any formula you use.

1. A voltage of $v(t) = 100 \sin(100\pi t)$ V, is applied to a certain non-linear load. The flowing current is given by:
 $i(t) = 2 + 9 \sin(100\pi t) - 12 \cos(100\pi t) + 5 \sin(300\pi t)$ A
Find:

(i) The rms value of the current

4marks

$$2 + 9 \cos(100\pi t - \pi/2) - 12 \cos(100\pi t) + 5 \cos(300\pi t - \pi/2)$$

$$2 + 15 \angle -143.13^\circ + 5 \angle -\pi/2$$

$$= \sqrt{129}$$

(ii) The power factor

$$F = \frac{P}{V_{rms} * I_{rms}} = \frac{(\sqrt{129}) (\frac{15}{\sqrt{2}})}{(\frac{100}{\sqrt{2}}) \sqrt{129}}$$

$$\frac{(15/\sqrt{2})}{\sqrt{129}} \neq \cos(-90 - (-143.13)) = 0.933$$

$$= 0.560$$

(iii) The distortion volt ampere

$$= S^2 - P^2 - Q^2$$

$$\frac{I_{rms}}{I_{rms}} = \frac{(15/\sqrt{2})}{(\sqrt{129})} = 0.933$$

3

(iv) The total harmonic distortion

2. A single phase half wave rectifier with an RL load and a freewheeling diode.
 $V_m = 200V$, $R = 10 \Omega$, $L = 0.05H$, $f = 50Hz$.

Find

(i) The output average current

4marks

$$\phi = \tan^{-1} \left(\frac{\omega L}{R} \right)$$

$$V_{rms} = \frac{200}{\sqrt{2}} = 141.42$$

$$I_{dc} = \frac{V_m}{\pi R} = 6.369$$

(ii) The rms value of the output current

$$\frac{V_m}{\pi} + \frac{V_m}{2} \sin(\omega_0 t) - \sum \frac{2V_m}{\pi n^2 - 1} \cos(2n\omega_0 t)$$

n	V_n	Z	X	I_n	I_{rms}
0	63.7	10	0	6.37	6.37
1	100	12.6	15.7	5.37	3.798
2	8.44 42.4	32.95	31.9	1.28	.909
4	8.44	63.6	62.8	.133	0.094

4

$n = 4$
 $x = (2\pi f) L$
 $n\pi$
 u

$$I_{rms} = \sqrt{(6.37)^2 + (3.798)^2 + (0.909)^2}$$

$$= 7.416$$

(iii) The output power


$$P = I_{rms}^2 (R)$$

$$= (7.416)^2 (10) = 550.01$$

(iv) The supply power factor

$$PF = \frac{(550)}{(200/\sqrt{2})(7.416)} = 0.524$$

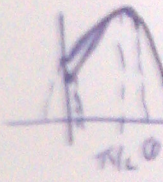3. A single phase half wave rectifier with a resistive load and a smoothing capacitor
 $V_m = 200V$, $R = 1 k\Omega$, $C = 100\mu F$, $f = 50Hz$
 Find the following



a. Value of the angle θ in degrees (When the diode stops)

~~ωRC~~ $\omega = 2\pi f$
 $\omega RC = 31.4$
 $\theta = 82^\circ$

b. Value of the angle α in degrees (When the diode starts)

$\alpha = 96.82$
 $= 83.18$
 55°

c. The output voltage ripple.

$\frac{\Delta V}{V_m} = V_m (1 - \sin \alpha) = 3616$
 ~~ΔV~~
 Ripple = $\frac{\Delta V}{V_m} = 180\%$




d. The equation of the diode current as function of time

$i_D(t) = \frac{V_m}{R} \sin \omega t + \omega C V_m \cos(\omega t - \theta)$

4. A full wave bridge rectifier with $V_m = 200V$, $50Hz$, a resistance of 4Ω , an inductance of $20mH$ and a dc source of $100V$. 3marks

(i) Is the current continuous or discontinuous? Why?

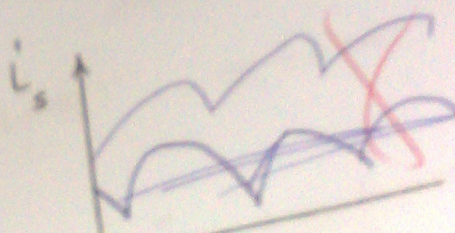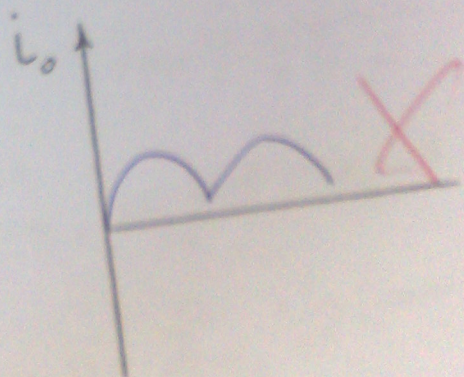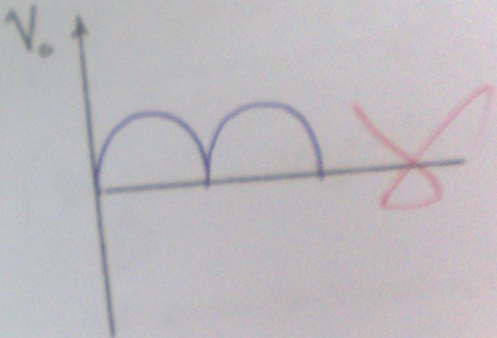(ii) Sketch the waveform of the output voltage, output current and the supply current showing the exact values of the angles on the waveforms



① voltage of $v(t) = 100 \sin(100\pi t)$ is applied to a certain non-linear load. The following current is given by:

$$i(t) = 2 + 9 \sin(100\pi t) - 12 \cos(\pi t) + 5 \sin(300\pi t) \text{ A}$$

① Find The rms value:

$$(i) I_{rms} = \sqrt{2^2 + \frac{9^2}{2} + \frac{5^2}{2}} = 11.36 \text{ A}$$

$$(ii) P.F. = \frac{I_{rms1}}{I_{rms}} = \frac{15}{11.36} = 0.933 \cos(+53) = 0.59$$

$$(iii) P = \frac{100}{\sqrt{2}} \times \frac{15}{\sqrt{2}} \cos(53) = 450$$

$$Q = \frac{100}{\sqrt{2}} \times \frac{15}{\sqrt{2}} \sin(53) = 600$$

$$VA = \frac{100}{\sqrt{2}} \times 11.36 = 803$$

$$D = \sqrt{803^2 - 600^2 - 450^2} = 286.9 \text{ VA}$$

$$(iv) THD = \sqrt{\frac{1}{Df^2} - 1} = \sqrt{\frac{1}{0.933^2} - 1} = 0.383$$

A single phase halfwave, RL load and freewheeling diode, $V_m = 200\text{V}$

$R = 10 \Omega$, $L = 0.05\text{H}$, $f = 50\text{Hz}$

n	V_n	X_n	Z_n	I_n	I_{rms}	$I_{rms} = \sqrt{6.28^2 + 3.8^2 + 0.91^2}$
0	62.8	0	10	6.28	6.28	
1	100	15.7	18.6	5.376	3.8	
2	12.4	31.4	18.8 32.15	1.287	0.91	

$= 7.4$
 $7.4^2 \times 10 = 0.547\text{W}$

3. A single phase half wave rectifier with resistive load and a smoothing capacitor
 $V_m = 200$, $R = 1k\Omega$, $C = 100\mu F$, $f = 50Hz$

$$\theta = \pi - \tan^{-1} \omega RC$$

$$= 91.72$$

$$\alpha = 56^\circ$$

$$\Delta V = V_m (1 - \sin \alpha) = 200(1 - \sin \alpha)$$

$$= \boxed{34.13V}$$

4. full wave bridge rectifier with $V_m = 200V$, $50Hz$, $R = 4\Omega$
 inductance $20mH$, dc source $= 100V$

$$(i) \sin \alpha = \frac{E}{V_m} = \frac{100}{200}$$

$$\alpha = 30^\circ$$

$$\beta = 190^\circ$$

$$\frac{\omega L}{R} = 1.57$$

29/3

static Induction Thyristor. slide M

Light - Activated Silicon : Si \rightarrow Si^{+} \rightarrow Si^{+}
 \rightarrow Si^{+} \rightarrow Si^{+}