

$$\left(\frac{71}{80}\right) \equiv \left(\frac{18}{20}\right)$$

1) 10/10
 2) 13/15
 3) 30/35
 4) 18/20

University of Jordan
 Electrical Eng. Dept

EE 0933481 Power Systems (1)


First Exam.
 30-10-2014

الرقم الجامعي: 0129244 رقم التفقد (38)

الاسم: بتول سليمان الدرديسي محمد

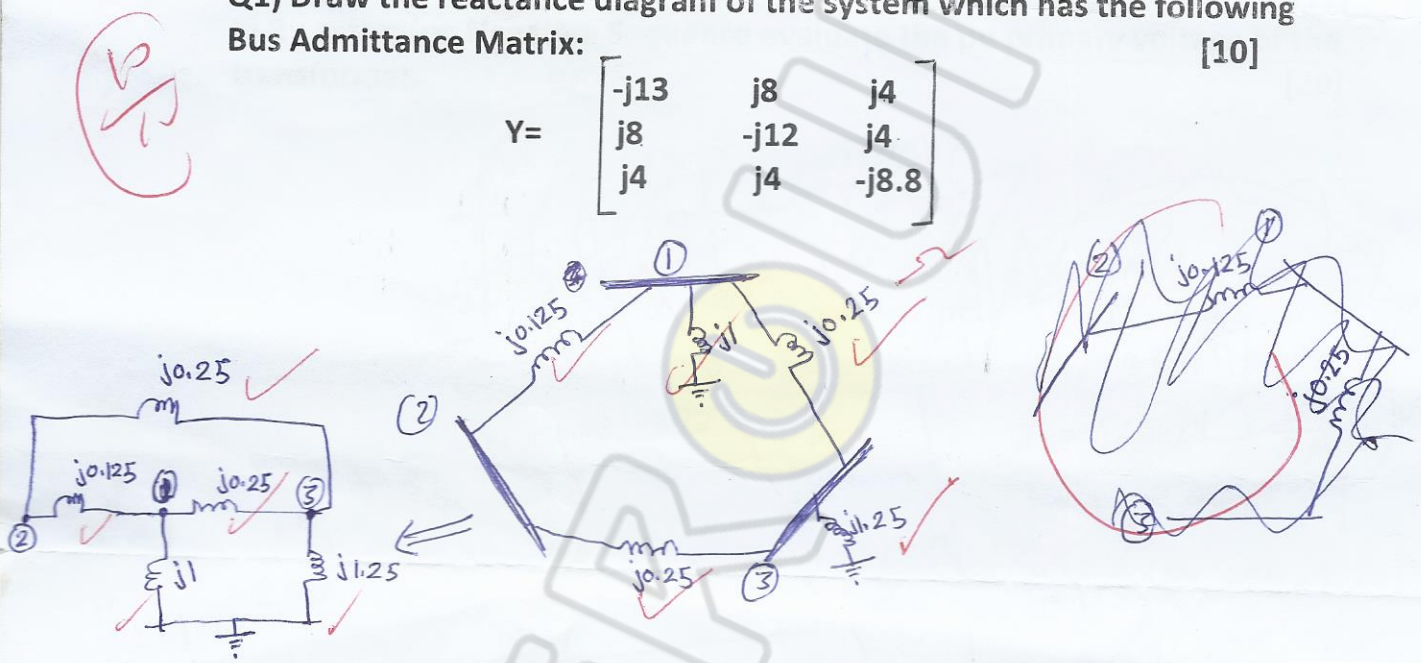Q1) Draw the reactance diagram of the system which has the following Bus Admittance Matrix: [10]

$$Y = \begin{bmatrix} -j13 & j8 & j4 \\ j8 & -j12 & j4 \\ j4 & j4 & -j8.8 \end{bmatrix}$$



Q2) A 60 Hz, 3-ph cylindrical synchronous generator has the following parameters:

- $L_s = 2.77 \text{ mH}$ $M_f = 31.7 \text{ mH}$
- $M_s = 1.38 \text{ mH}$ $L_{ff} = 434 \text{ mH}$


During balanced steady state operation, the armature and field current are as follows: $i_a = 20 \sin(\theta_d - 30^\circ) \text{ kA}$ $i_f = 4 \text{ kA}$

Evaluate λ_a at $\theta_d = 60^\circ$ [15]

$$|I_a| = \frac{20}{\sqrt{2}} = 14.142$$

$$\begin{aligned} \lambda_a &= (L_s + M_s) i_a + M_f i_f \cos(\theta_d) \\ &= (2.77 \text{ m} + 1.38 \text{ m}) (14.142 \text{ k}) + (31.7 \text{ m}) (4 \text{ k}) \cos(60) \\ &= 122.19 \end{aligned}$$


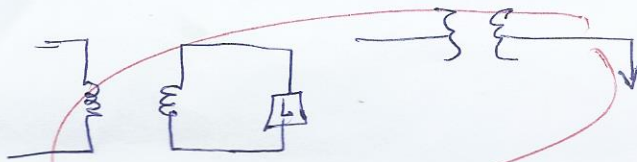
$$\lambda_a = (L_s + M_s) i_a + L_{ff} i_f \cos(\theta_d)$$



Q3) A 3-ph transformer rated at 5 MVA, (115 y/13.2 Δ) kV and per-phase series impedance of $0.0753 / 84.7^\circ$ pu. The transformer is supplying a balanced 3-ph load rated at 4 MVA, 13.2 kV and 0.85 pf lagging, through a transmission line which has a series impedance per phase of $0.102 / 78.7^\circ$ pu on a base of 10 MVA and 13.2 kV.

By using base values of 10 MVA and 13.2 kV:

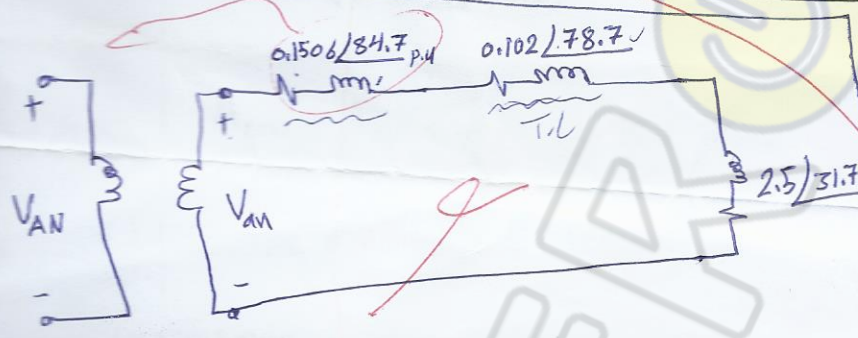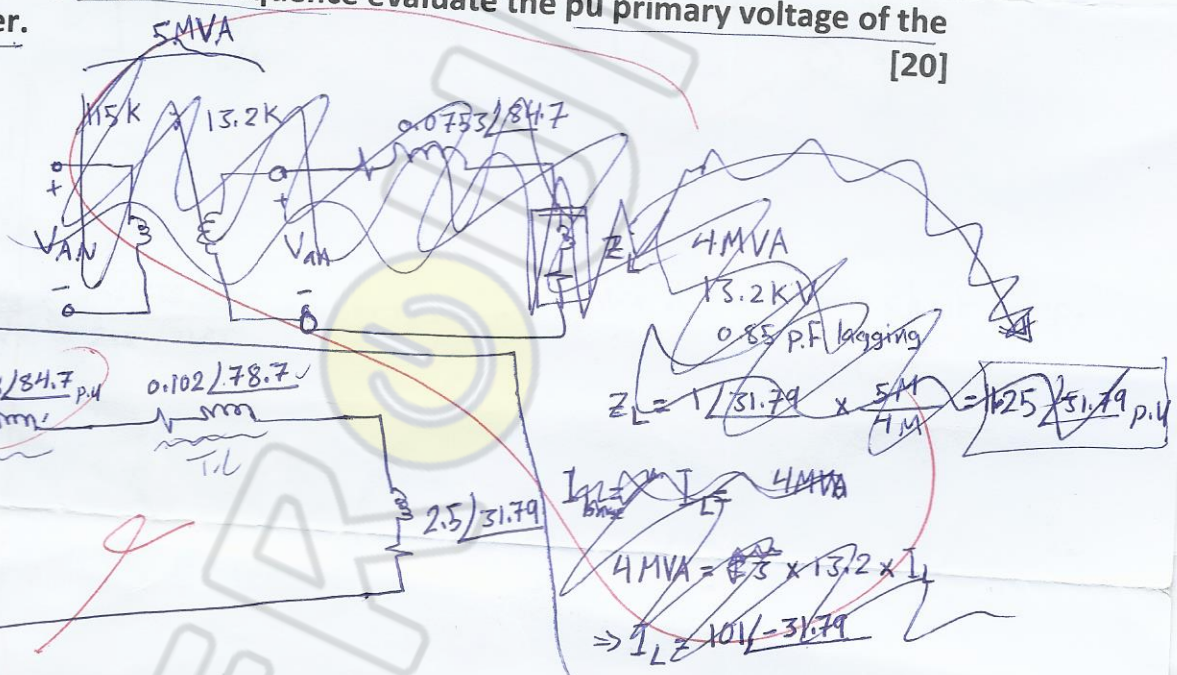- i) Evaluate and draw the pu impedance diagram of the system. [15]
- ii) By assuming Negative Sequence evaluate the pu primary voltage of the transformer. [20]



$T: Z = 0.0753 / 84.7 \times \frac{10}{5} = 0.1506 / 84.7$

$T.L: Z = 0.102 / 78.7$

$Load: Z_L = \frac{1}{31.79} \times \frac{10}{4} = 2.5 / 31.79 \text{ pu}$

$I_L = \frac{4 \text{ MVA}}{\sqrt{3} \times 13.2 \text{ kV}} = 174.95 \text{ A} \angle -31.79^\circ$

$I_{base} = \frac{10 \text{ MVA}}{\sqrt{3} \times 13.2 \text{ kV}} = 437.39$

$I_{pu} = 0.4 \angle -31.79 \text{ pu}$

$V_{an} = 0.4 \angle -31.79 \times (0.1506 / 84.7 + 0.102 / 78.7 + 2.5 / 31.79)$
 $= 1.067 \angle 4.184 \text{ pu}$

$V_{AN} = V_{an} \angle -30 = 1.067 \angle -25.816 \text{ pu} \times 115 = 122.7 \angle -25.82 \text{ V}$

Q4) A 3-PH transmission line is ^{long} 480 km long and having the following parameters: $A = D = 0.818 / 1.3^\circ$, $B = 172.2 / 84.2^\circ$, $C = 0.0001933 / 20.4^\circ$. Design a compensation network to be located at the receiving end in such away to maintain the voltages at no-load as follows: $V_S = 256.738 / 20.15^\circ$ kV and $V_R = 218 / 21.03^\circ$ kV [20]

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} 1 \\ \frac{-j}{jX_L} \end{bmatrix} = \begin{bmatrix} A_{\text{new}} & B \\ C_{\text{new}} & D \end{bmatrix}$$

@ no load.

$$V_S = A_{\text{new}} V_R$$

$$\Rightarrow A_{\text{new}} = \frac{V_S}{V_R} = \frac{256.738 / 20.15^\circ}{218 / 21.03^\circ} = 1.1777 / -0.88^\circ \quad \text{since } A \text{ changes} \Rightarrow \text{shunt comp.}$$

$$A_{\text{new}} = A_{\text{old}} + \frac{B}{jX_L} \quad B_{\text{old}} = B_{\text{new}}$$

$$1.1777 / -0.88^\circ = 0.818 / 1.3^\circ + \frac{172.2 / 84.2^\circ}{jX_L}$$

$$\frac{172.2 / 84.2^\circ}{jX_L} = 0.3616 / -5.82^\circ$$

$$jX_L = 476.173 / 90^\circ$$

$$X_L = 476.173 \, \Omega$$

for sw / call