

(20 marks) Q(1):

(a) (10 marks) For the circuit shown in Fig. 1.a, find the equivalent capacitance between terminals a and b.

$$\text{3 series with } 6 = \frac{3 \times 6}{9} = \frac{18}{9} = 2$$

$$\text{5 series with } 2 = \frac{5 \times 2}{7} = \frac{10}{7} = 1.428$$

$$\text{10 series with } 15 = \frac{10 \times 15}{25} = 6$$

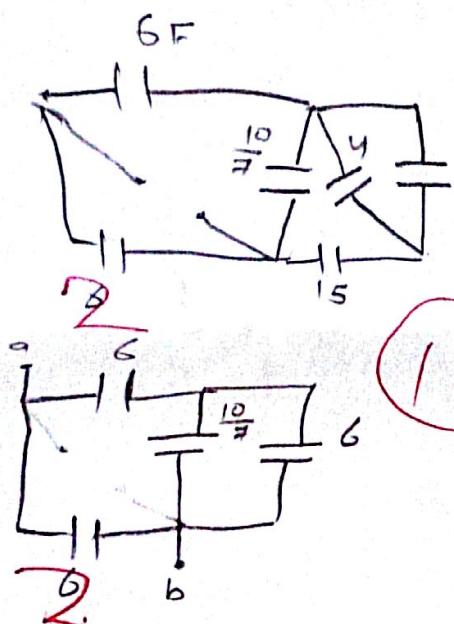
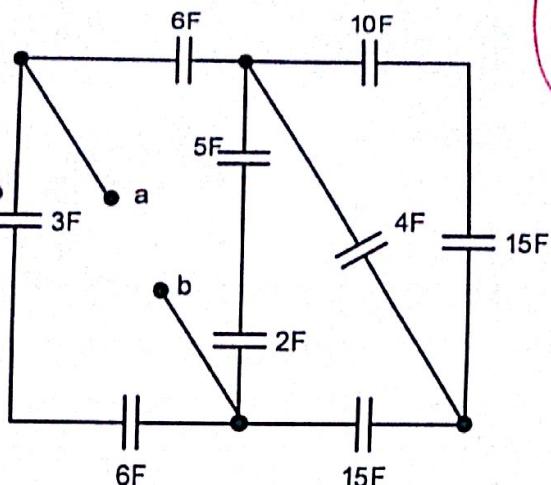



Fig. 1.a

$$6 + 4 = 10$$

10 series with 15 = 6

$$6 + \frac{10}{7} = \frac{52}{7}$$
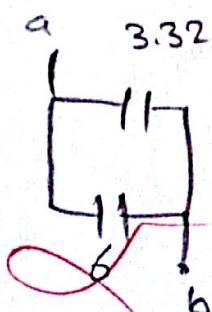
$$\frac{52}{7} \text{ series with } 6 = \frac{\frac{52}{7} \times 6}{6 + \frac{52}{7}} = \frac{312}{94} = 3.32$$



$$C_{eq} = 3.32 + 6 = 9.32 \text{ F}$$

(10 marks) For the circuit shown in Fig.1.b, find the equivalent inductance between terminals a and b.


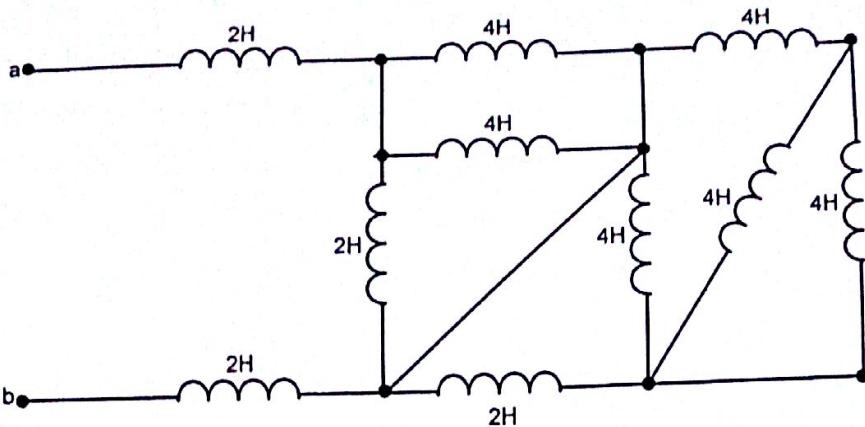


Fig.1.b

10


$$4 \parallel 4 = 2$$

$$2 + 4 = 6$$

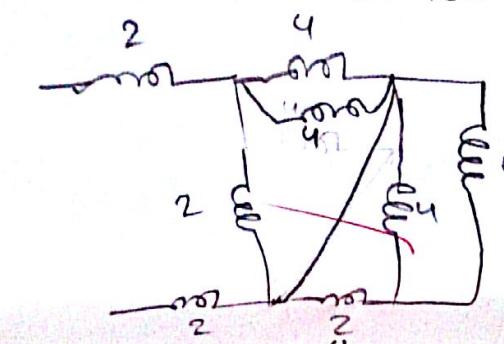


$$6 \parallel 4 = \frac{6 \times 4}{10} = 2.4$$

$$2.4 + 2 = 4.4$$

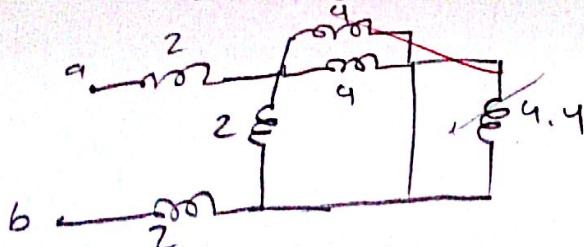

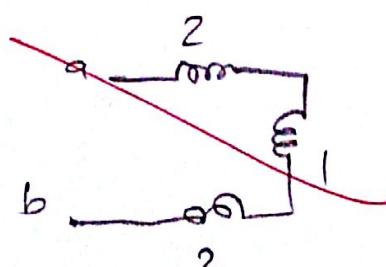
$$4 \parallel 4 \parallel 2 = \frac{1}{\frac{1}{4} + \frac{1}{4} + \frac{1}{2}} = 1$$



$$L_{eq} = 2 + 1 + 2 = 5H$$

(25 marks) Q(2): For the circuit shown in Fig. 2.

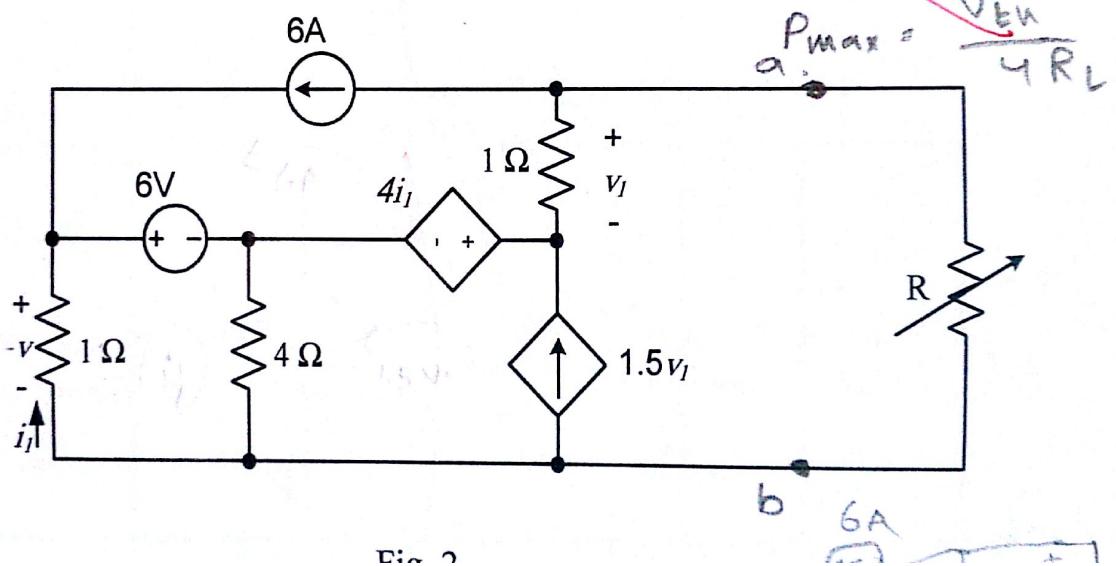
- (a) (15 marks) Find the Thévenin equivalent circuit for the circuit seen by the variable resistor R .
- (b) (10 marks) What value of R that will absorb maximum power from the other parts of the circuit, find this **maximum power**?



(a)

$$V_1 = I$$

Fig. 2

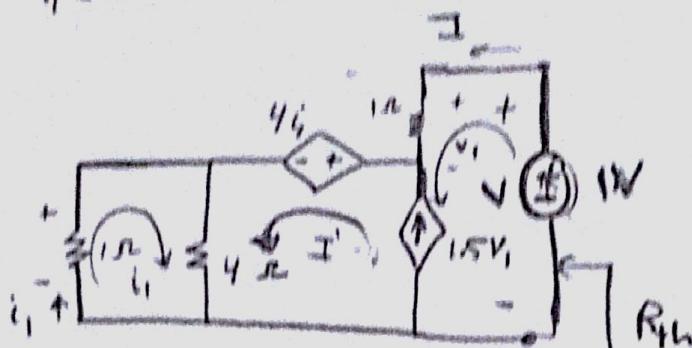

$$R_{th} = \frac{1}{I}$$

$$-1 + I + 4i + 4I + 4i_1 = 0 \Rightarrow [I + 4I + 8i_1 = 1] \quad \textcircled{1}$$


$$i + 4i + 4I' = 0 \Rightarrow [0 + 4I' + 5i_1 = 0] \quad \textcircled{2}$$

$$I' - I = 1.5V_1 \Rightarrow I' - I = 1.5I \Rightarrow [-2.5I + I + 0 = 0] \quad \textcircled{3}$$

$$I = \frac{-1}{5} \quad I' = \frac{-1}{2} \quad i_1 = \frac{2}{5}$$

$\Rightarrow R_{th} = -5$

(P.S.)

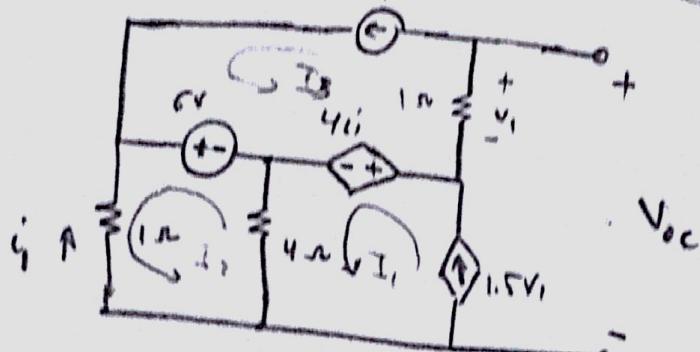

$$V_1 = -6$$

$$I_1 = 1.5V_1 \Rightarrow I_1 = -9$$

$$4(I_2 + 9) - 6 + I_2 = 0 \Rightarrow 4I_2 + 36 - 6 + I_2 = 0$$

$$\Rightarrow 5I_2 = -30 \Rightarrow [I_2 = -6], [i_1 = 6]$$


(7.5)

$$V_{oc} = V_1 + 4i_1 + 4(I_1 - I_2)$$

$$V_{oc} = -6 + 4 \times 6 + 4(-9 + 6) = -6 + 24 - 12 = 6 \text{ V}$$

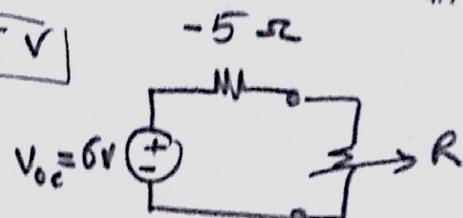(b) If it exist then it will be -5Ω

$$P = \frac{V_1^2}{-5} = \frac{(3)^2}{-5} = -1.8 \text{ Watt.}$$



(30 marks) Q(3): For the circuit shown in Fig. 3.

1. (8 marks) Write the required Nodal equations.
2. (7 marks) Draw the dual circuit, show the numerical values of the different elements.
3. (15 marks) If the circuit is in steady-state where $v(t) = 5V$ and $i(t) = 2A$, then find V_c , i_L , and i_x .

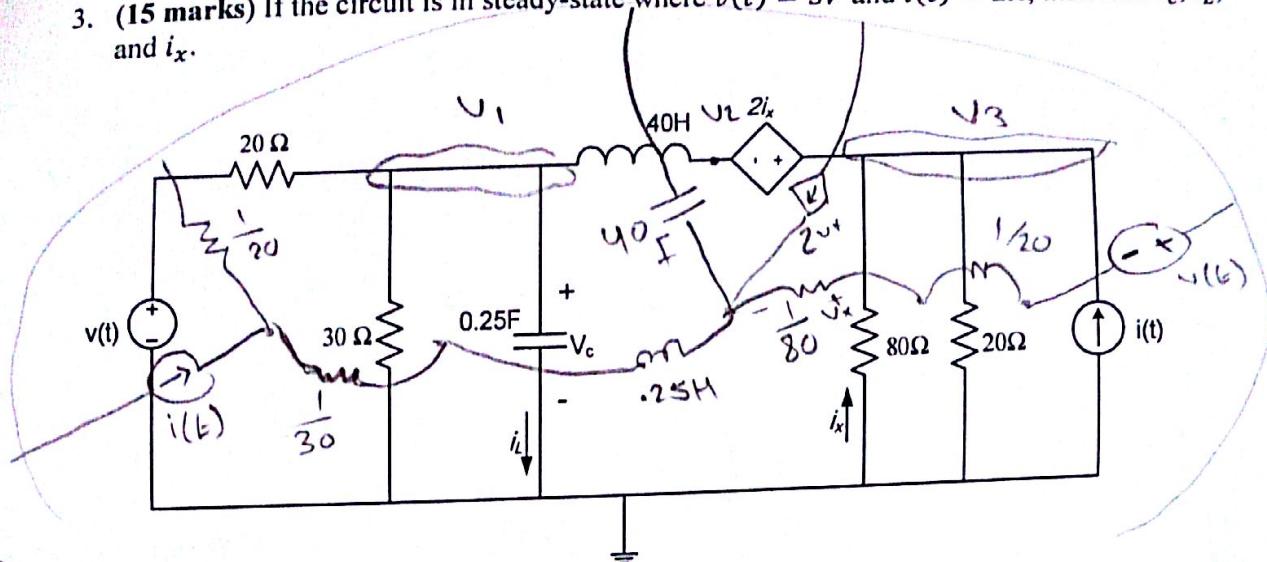


Fig. 3

1. @ node 1: $\frac{V_1 - V_E}{20} + \frac{V_1}{30} + \frac{0.25 \frac{dV_1}{dt}}{0.25H} + \frac{1}{40} \int_{t_0}^t (V_1 - V_2) dV = 0$ $+ i(t)$


@ Super node (2-3): $\frac{1}{40} \int_{t_0}^t (V_2 - V_1) dV + \frac{V_3}{80} + \frac{V_3}{20} = i(t)$

$$i_x = \frac{-V_3}{80}$$

$$V_3 - V_2 = 2 \left(\frac{-V_3}{80} \right)$$


7

2

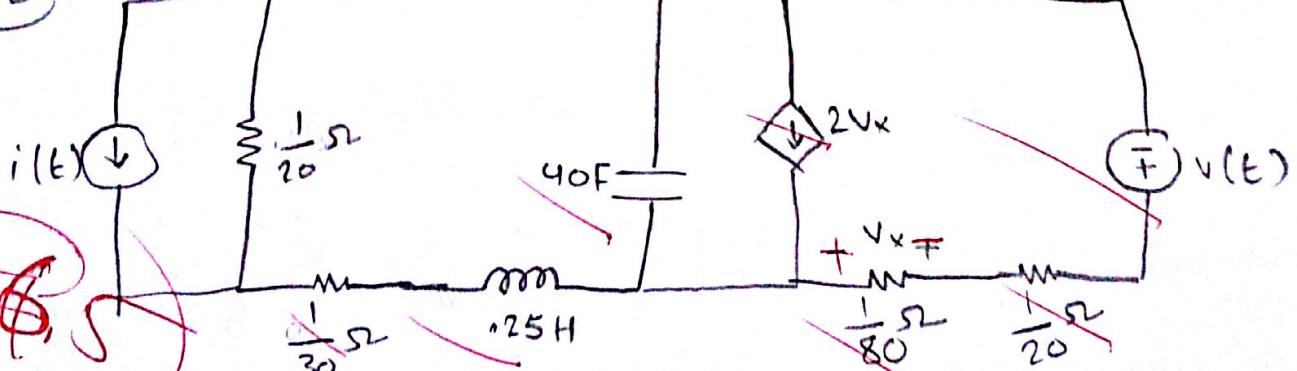

6, 5

(3)

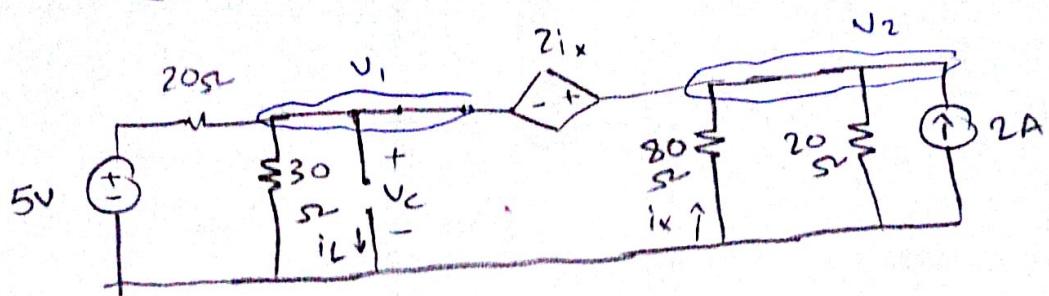

$i_L = 0$

@ Supernode (1-2) : $\frac{v_1 - 5}{20} + \frac{v_1}{30} + \frac{v_2}{80} + \frac{v_2}{20} = 2$

$$\frac{1}{12}v_1 + \frac{1}{16}v_2 = 2 + \frac{1}{4} = 2.25 \quad \dots (1)$$

$$i_X = -\frac{v_2}{80}$$

$$v_2 - v_1 = 2 \left(-\frac{v_2}{80} \right)$$

$$-v_1 + \frac{41}{40}v_2 = 0 \quad \dots (2)$$


$v_1 = 15.6 \text{ V}$

$v_2 = 15.2 \text{ V}$

~~$v_C = v_1 - \frac{v_1}{30} = \frac{v_1}{30} = 0.52 \text{ V}$~~

~~$i_X = -\frac{v_2}{80} = -0.19 \text{ A}$~~

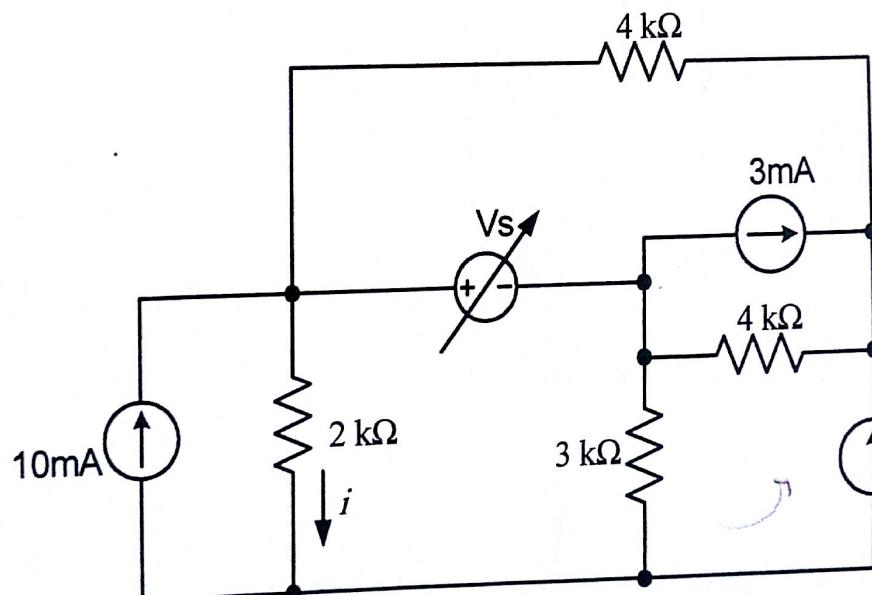(25 marks) Q(4): The variable dc voltage source V_s in the circuit shown in Fig.4 is adjusted so that i is zero, find the value of V_s .



(25 marks) Q(4): The value of i is zero, find the value of V_s .


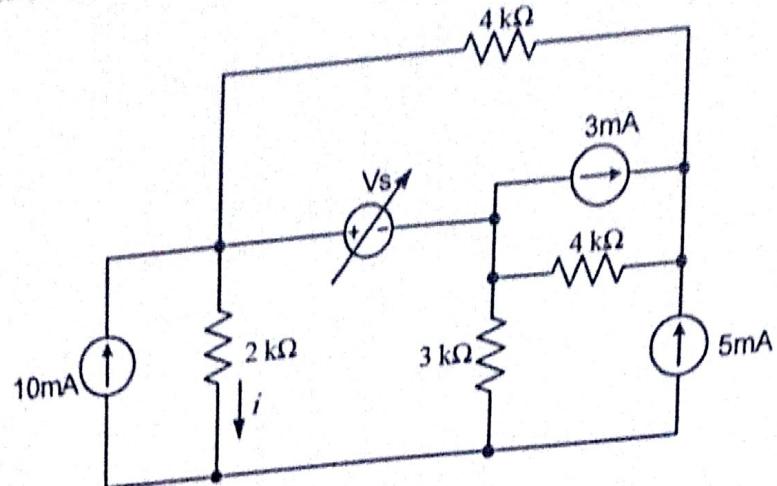
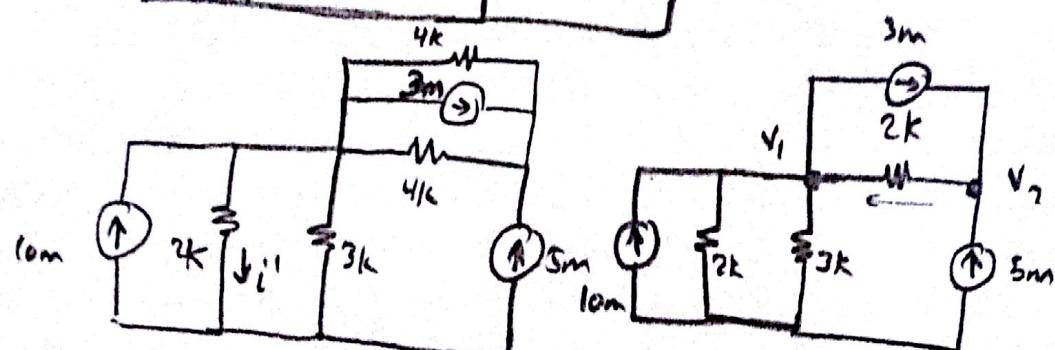


Fig. 4


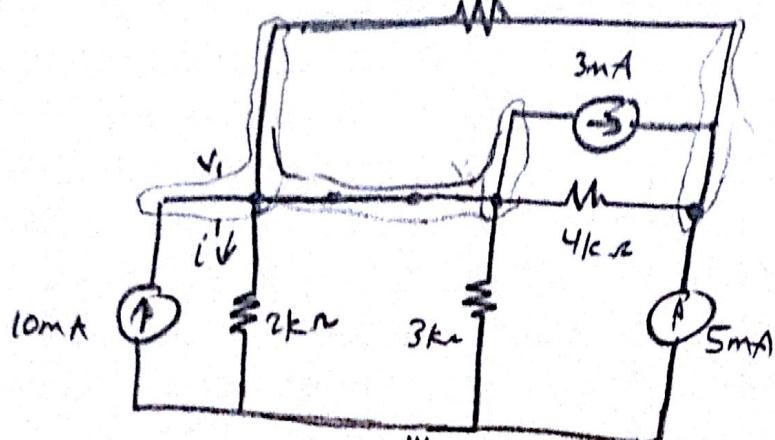


$$\text{At Node 1: } \frac{V_1}{2k} + \frac{V_1}{3k} + \frac{V_1 - V_2}{2k} + 3m = 10m \Rightarrow \frac{V_1}{1k} + \frac{V_1}{3k} - \frac{V_2}{2k} = 7m$$

$$V_1 + \frac{V_1}{3} - V_2 = 7 \Rightarrow \boxed{\frac{4}{3}V_1 - V_2 = 7} \quad \text{--- (1)}$$

$$\text{At Node 2: } \frac{V_2 - V_1}{2k} = 8m \Rightarrow \boxed{-V_1 + V_2 = 16} \quad \text{--- (2)} \quad \left. \begin{array}{l} V_1 = 69 \\ V_2 = 86 \end{array} \right\}$$
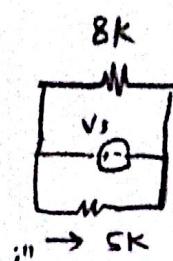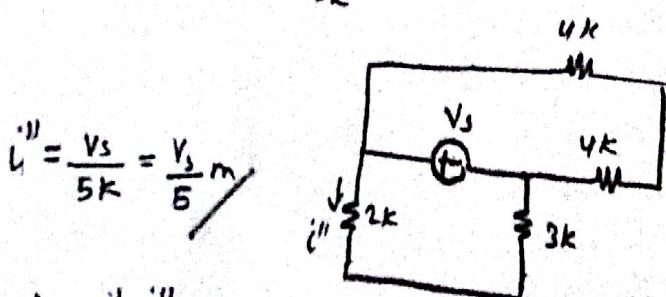
$$\Rightarrow i' = \frac{V_1}{2k} = \frac{69}{2k} = 34.5mA$$



Good Luck

7/7

$$i'' = \frac{V_s}{5k} = \frac{V_s}{5}$$

$$\Rightarrow i' + i'' = 0 \Rightarrow 34.5 + \frac{V_s}{5} = 0 \Rightarrow \frac{V_s}{5} = -34.5 \Rightarrow \boxed{V_s = -172.5V}$$