

Questions # 1 (7 points) SHOW YOUR CALCULATIONS

A balanced 3-ph *abc* sequence Y-connected source with phase voltage $V_{an} = 220 \angle 0^\circ$ V_n supplying unbalanced 3-ph Y-connected load as shown below, determine:

$$\begin{aligned} V_{a\bar{s}} &= 220 \angle 12^\circ \\ V_{n\bar{s}} &= 220 \angle -12^\circ \end{aligned}$$

- a. the load's phasor currents, I_a , I_b and I_c

$$I_a = 7,64 \angle 20,32^\circ$$

$$I_b = 10 \angle -120^\circ$$

$$I_c = 16,92 \angle 97,35^\circ$$

- b. the load's phase phasor voltages, V_{AN} , V_{BN} and V_{CN}

$$V_{AN} = 205,71 \angle -1,43^\circ$$

$$V_{BN} = 200 \angle -110^\circ$$

$$V_{CN} = 189,17 \angle 123,5^\circ$$

- c. the load's phasor line voltages, V_{AB} , V_{BC} and V_{CA}

$$\begin{aligned} V_{AB} &= 204,94 \angle -175^\circ \\ V_{BC} &= 182,9 \angle 56,41^\circ \\ V_{CA} &= 189,17 \angle 150^\circ \end{aligned}$$

~~$$V_{AB} = 204,94 \angle -175^\circ$$~~

~~$$V_{BC} = 182,9 \angle 56,41^\circ$$~~

~~$$V_{CA} = 189,17 \angle 150^\circ$$~~

- d. the load's complex power absorbed by each phase, S_A , S_B and S_C

$$S_A = 153,22 \angle -21,3^\circ$$

$$S_B = 2000$$


~~$$S_C = 3201,31 \angle 26,5^\circ$$~~

~~$$S_0 = 6651,36 \angle 0^\circ$$~~

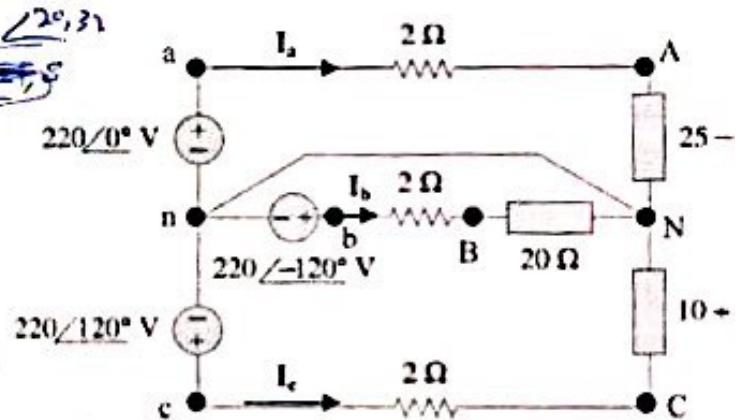- e. the total complex power supplied by the source, S_{source}

~~$$S_{source} = 6651,36 \angle 0^\circ$$~~

$$\begin{aligned} I_a &= \frac{V_{an}}{2 - (25 - 10j)} = \frac{220}{2 + 10j} = 7,64 \angle 20,31^\circ \\ I_b &= \frac{220 \angle -120^\circ}{2 + 20} = 10 \angle -120^\circ \\ I_c &= \frac{220 \angle 120^\circ}{2 + 20} = 16,92 \angle 97,35^\circ \end{aligned}$$



$$S_A = I_a \cdot V_{PN} = 7,64 \angle 20,32^\circ \times [25 - 10j] \times 205,71 \angle -1,43^\circ$$

$$V_{PN} = \frac{V_{an} - V_{n\bar{s}}}{2} = 220 \angle 12^\circ - 220 \angle -12^\circ = 220 \angle 24^\circ$$

$$V_{AB} = 204,94 \angle -175^\circ$$

$$\begin{aligned} S_A &= 153,22 \angle -21,3^\circ \\ S_B &= 2000 \\ S_C &= 3201,31 \angle 26,5^\circ \end{aligned}$$

$$\begin{aligned} S_A &= I_a \cdot V_{PN} = 7,64 \angle 20,32^\circ \times 205,71 \angle -1,43^\circ \\ S_B &= I_b \cdot V_{PN} = 10 \angle -120^\circ \times 205,71 \angle -1,43^\circ \\ S_C &= I_c \cdot V_{PN} = 16,92 \angle 97,35^\circ \times 205,71 \angle -1,43^\circ \end{aligned}$$

$$S_A = 153,22 \angle -21,3^\circ$$

$$S_B = 2000$$

$$S_C = 3201,31 \angle 26,5^\circ$$

Question # 2 (3 points) SHOW YOUR CALCULATIONS

A balanced Y-connected load as shown below is fed from a 50 Hz, three-phase Y-connected source with line voltage of 400 V_{rms}. The resistance R in each phase of the load is 10 Ω and the load draws a total power P_{tot} of 15 kW. Calculate:

a. the magnitude of the line current drawn by the load, $ I_L $	$ I_L = 70.7, 1^\circ$
b. the load power factor, PF	$PF = \cos 0.30^\circ = 0.95$
c. the total reactive power drawn by the load, Q_{tot}	$Q_{tot} = 230.22 \text{ kvar}$
d. the total apparent power drawn by the load, $ S_{tot} $	$S_{tot} = 230.22 \text{ kVA}$
e. the load's inductance, L in mH.	$L = 15.07 \text{ mH}$

~~$P_{tot} = \sqrt{3} V_L I_L \cos \phi$~~

$$P_{tot} = 15 \text{ kW}$$

$$P_{tot} = \frac{15}{\sqrt{3}} \text{ kW}$$

$$P_{tot} = V_L^2 / R$$

$$\frac{15}{\sqrt{3}} = V_L^2 / 10 \Omega$$


$$|I_L| = 70.7, 1^\circ$$

$$\Rightarrow P_{tot} = \sqrt{3} V_L |I_L| \cos \phi$$

$$15 \text{ kW} = \sqrt{3} \cdot 400 \cdot 70.7, 1^\circ \cos \phi$$

$$PF = \cos 0.30^\circ = 0.95$$

$$\phi = 82.24^\circ$$

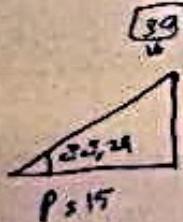


$$\tan \phi = \frac{q}{P}$$

$$q = P \tan \phi$$

$$\phi = 82.24^\circ, q = 42.23, 10$$

$$q = 230.22, 10 \angle 82.24^\circ$$

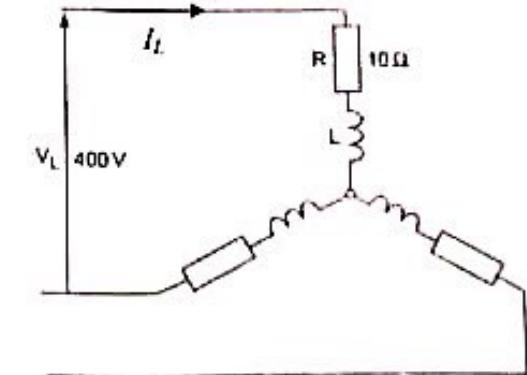

$$Q_{tot} = \sqrt{3} V_L |I_L| \sin \phi$$

$$Q = |I_L|^2 \cdot X_L$$

$$230.22, 10 = (70.7, 1^\circ)^2 \cdot X_L$$

$$X_L = 0.0473 = j\omega L = 2\pi f L$$

$$0.0473 \times 100 \Omega \cdot L$$

$$L = 15.07 \text{ mH}$$

$$Q = |I_L|^2 \cdot R_L$$

$$42.23, 10 = (70.7, 1^\circ)^2 \cdot 10$$

$$R_L = 400 \Omega = 100 \Omega \cdot L =$$

$$L = 3.10 \text{ mH}$$

(3)

Question # 3 (3 points) SHOW YOUR CALCULATIONS

A three-phase abc Y-connected source feeds a balanced Y-connected load with an impedance as indicated in the figure shown below. If the load takes $4 A_{rms}$, find

a. the load's power factor, PF	$0,8$
b. the wattmeter reading, W	640
c. The total real, reactive and apparent power drawn by the load	$P_{tot} = 1920$
d. the magnitude of the load's line voltage	$ V_{LL} = 346,41$

$$V_{ab} = [4 + j3\sqrt{3}] 4$$

$$V_{ab} = 200 \angle 36,86^\circ V_{ac}$$

$$I_a = 4 A$$

$$P_a = \omega s |V_{ab}| |I_a| \cos \theta$$


$$\omega s = 200 \times 4 \cos 36,86^\circ$$

$$W = 640$$

$$P_{tot} = 3P_a = 1920$$

$$P_{tot} = 1920 = \sqrt{3} |V_L| |I_L| \cos \theta / V_L = \sqrt{3} 200 = 346,41$$
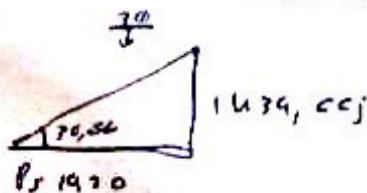
$$\cos \theta = PF_{load} = \frac{1920}{\sqrt{3} \cdot 346,41 \times 4} = 0,8$$




Ans: 640

Ans: 1920

$$Q = 1439,48 VA$$

$$S = 2399,8 \angle 36,86^\circ$$

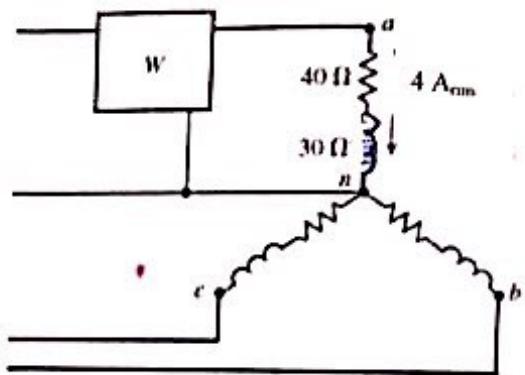

(2)

Questions # 4 (2 points) SHOW YOUR CALCULATIONS


In the figure shown below, two-wattmeter method have been used to measure the power input to a 440 V_{rms}, 3-ph, induction motor running at full load. The wattmeter readings are $W_1 = 115 \text{ kW}$ and $W_2 = 50 \text{ kW}$. Calculate:

a. the total input real power to the motor in kW	$P_{\text{tot}} = 165 \text{ kW}$
b. the total input reactive power to the motor in kVAR	$Q_{\text{tot}} = 112,5 \text{ kVAR}$
c. the motor's power factor	$\text{PF} = 0,826 \text{ lagging}$
d. the magnitude of the line current drawn by the motor.	$ I_L = 222,03 \text{ A}$

$$P_{\text{tot}} = W_1 + W_2 = 115 + 50$$

$$\boxed{P_{\text{tot}} = 165}$$

$V_{11} = 440 \text{ V}_{\text{rms}}$

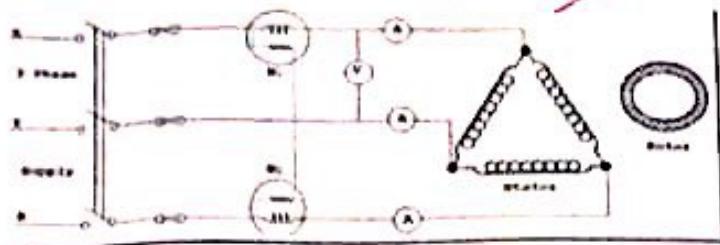

$$Q = \sqrt{3} [W_1 - W_2]$$

$$\boxed{Q = 112,5 \text{ kVAR}}$$

$$\vec{S} = 144,7 \angle 34,3^\circ$$

$$\text{PF} = \cos 34,3^\circ = 0,826 \text{ lagging}$$

$$P_{\text{tot}} = \sqrt{3} |V_L| \cdot |I_L| \cdot \cos \phi$$

$$\frac{165 \text{ k}}{\sqrt{3} \cdot 440 \cdot \cos 34,3^\circ} = |I_L|$$

$$\boxed{|I_L| = 222,03}$$


Question # 5 (5 points) SHOW YOUR CALCULATIONS

A balanced three-phase *abc* sequence Y-connected source is connected to a balanced Y-connected load through a transmission line with an impedance of $j1 \Omega$ per phase as shown below. The source consumes 8.64 kVA at 0.8 pf lagging. Given the line-to-line voltage $V_{CB} = 208/90^\circ$ V_{rms} at terminals A, B, C, answer questions 6.1-6.5.


$$V_{p0} = 208^\circ \angle 2^\circ$$

$$V_{pe} = -V_p = 208^\circ \angle -4^\circ$$

$$V_{PA} = 208^\circ \angle 15^\circ$$

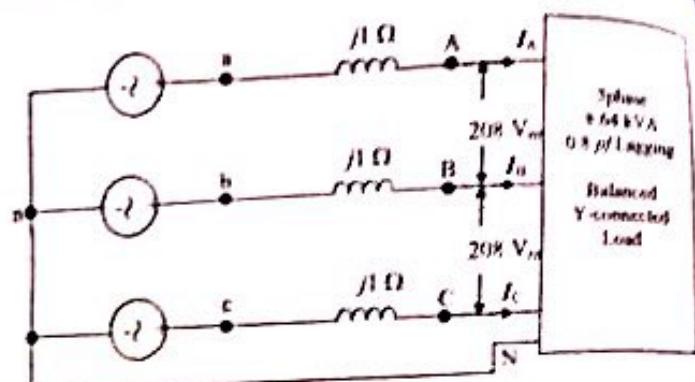

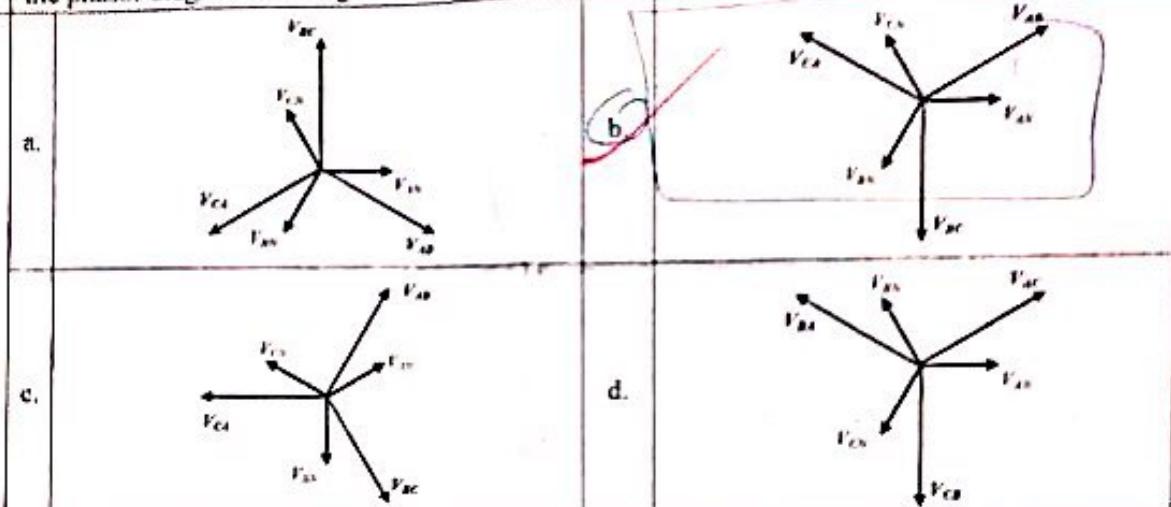- 6.1 the phasor diagram showing the load phase and line voltages is shown in Fig. (•).



- 6.2 The load phase voltage V_{AN} is given as ____.

$$V_{AN} = 12^\circ \angle c^\circ \text{ Vrms}$$

- 6.3 the phasor current I_A is ____.

$$I_A = 39,97 \angle -36^\circ$$

- 6.4 the load impedance per phase Z_L is ____.

$$Z_L = 3 \angle 26.56^\circ \Omega$$


- 6.5 the magnitude of the source voltage $|V_s|$ is ____.

$$V_s = 141,40 \angle 12,52^\circ \text{ Vrms}$$

$$V_{AN} = I_A j + V_{AN}$$

$$V_{AN} = \frac{V_{p0}}{\sqrt{3}} \angle -1^\circ$$
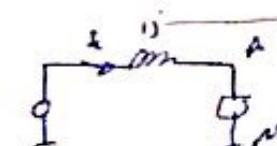
$$V_{AN} = \frac{V_p}{\sqrt{3}} \angle 2^\circ$$



$$Z = \frac{V_{AN}}{I_A}$$

$$= \frac{12^\circ}{39,97 \angle -36^\circ}$$

$$Z = 3 \angle 26.56^\circ$$

$$P = \frac{V_s^2}{Z}$$


$$P = 11,52 \text{ kW}$$

at the load

Question # 6 (10 points) SHOW YOUR CALCULATIONS

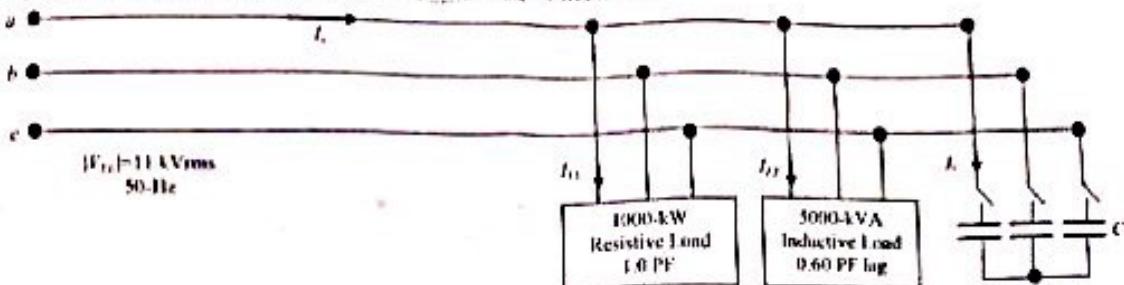(3)

A small industrial plant has a 3-ph 1000-kW Y-connected resistive heating load and a 3-ph 5000-kVA, 0.6 PF lagging Y-connected inductive load as shown below. The two loads are connected to a 50 Hz 3-ph source with a line voltage of 11 kV_{rms}. Calculate:



a.	the magnitude of the line current drawn by the heating load, $ I_{L1} $	$ I_{L1} = 52,45$
b.	the magnitude of the line current drawn by the inductive load, $ I_{L2} $	$ I_{L2} = 328,04$
c.	the total real and reactive power P_{tot} and Q_{tot} supplied by the source in kW and kVAR	$P_{tot} = 1003,75 \text{ kW}$ $Q_{tot} = 5000 \text{ kVA}$
d.	the power factor at the source, PF_s	$PF_s = 0,1962 \text{ lagging}$
e.	the magnitude of the source line current, $ I_s $	$ I_s = 328,52$
f.	the size of the Y-connected capacitor bank, in terms of Q_c and C_T , that must be placed in parallel with the two loads to raise the overall PF to 0.90 lagging	$Q_c = 4520,07 \text{ kVA}$ $C_T = 39,7 \mu\text{F}$
g.	the magnitude of the capacitor line current, $ I_C $	$ I_C = 164,75$
h.	the magnitude of the source current after adding the capacitor, $ I_s $	$ I_s = 545,27$

$$P_{36} = \sqrt{3} V_L I_{L1} \cos \phi$$

$$\frac{1000 \text{ k}}{\sqrt{3} \times 11 \text{ k}} \Rightarrow |I_{L1}| = 52,45$$

$$Q_p = 0,5 V_L I_{L1} \sin \phi = 53,13$$

$$\frac{5000 \text{ k}}{\sqrt{3} \cdot 11 \text{ k}} \Rightarrow |I_{L2}| = 328,04$$

$$P_{tot} = P_1 + P_2 = 1000 \text{ k} + 3,5 \text{ k} \Rightarrow |I_s| = \sqrt{3} V_L / R_s = 1003,75 \text{ kW}$$

$$P_2 = \sqrt{3} V_L I_{L2} \cos \phi = 3550,00$$

$$Q_{tot} = Q_1 + Q_2 = 0,9 \cdot 5000 \text{ k} \text{ VAR}$$

$$Q_s = 25,34$$

$$S_{tot} = 1003,75 + 5000 \text{ kVA}$$

$$S = 5099,04 / 73,00 \text{ kVA}$$

$$\cos \phi = 0,196$$

$$|I_s| = \sqrt{3} V_L / R_s$$

$$\frac{5099,04 \text{ k}}{\sqrt{3} \cdot 11 \text{ k}} \Rightarrow |I_s| = 545,27$$

$$Q_c = P [I_{max} - I_{min}] \Rightarrow Q_c = 25,34$$

$$Q_c = 4520,07$$

$$C = \frac{Q_c}{2 \pi f V^2} = \frac{4520,07 \text{ k}}{3 \cdot 100 \pi \cdot 11 \text{ kV}} = 39,7 \mu\text{F}$$